

$R = 5 \text{ Kohm}$

$I \text{ at } 1100 = 1.5 \text{ mA}$