

# Electrical Circuits Simulation Using Xcos

National Workshop on Scilab

Fr. C. Rodrigues Institute of Technology, Vashi

By

**Vishwesh A. Vyawahare**

IDP in Systems and Control Engineering  
Indian Institute of Technology Bombay


December 1, 2010

- DC source with R without switch.
- Switch logic in Scilab
- DC source with R, RL, RC, and RLC, with switch.
- AC source with RLC with switch.
- Demos of some more complicated ckts.

# DC source with R


- We have

$$i(t) = \frac{V}{R}.$$

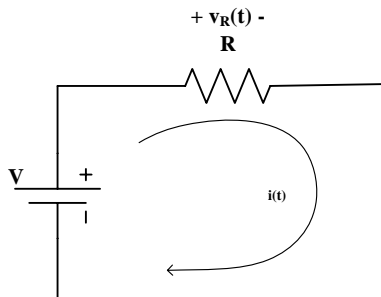

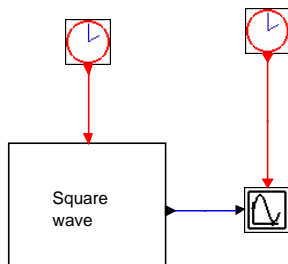
# Switch Logic in Scilab

- Opening or closing of switch is an important operation.
- Useful in Power Electronics ckt.
- Adding a switch in the ckt makes the ODE stiff for solving.


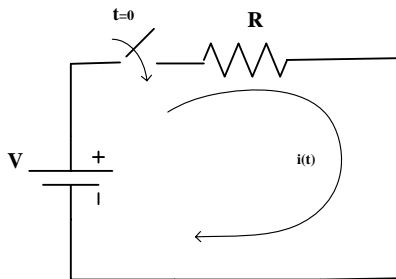
# DC source with R with Switch





- Memory-less system. Current and voltage change instantaneously after the closing of switch at  $t = 0$ .



# DC source with RL with Switch

- Current through the inductor cannot change instantaneously.
- At  $t(0+)$ , inductor  $\rightarrow$  Open Circuit  $\Rightarrow i_L(0+) = i(0+) = 0$ .  
 $v_L(0+) = V$ .
- For general  $t > 0$ ,

$$V = Ri(t) + L \frac{di(t)}{dt}.$$

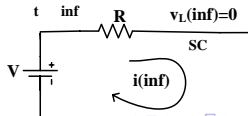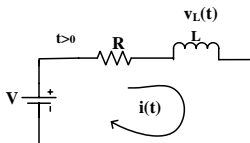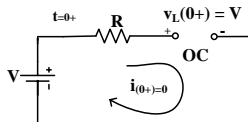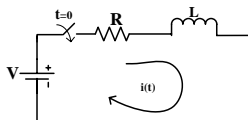

- Expression for current is

$$i(t) = \frac{V}{R} - \frac{V}{R}e^{-\frac{R}{L}t}.$$

- Expression for inductor voltage is





$$v(t) = Ve^{-\frac{R}{L}t}.$$

- At steady-state ( $t \rightarrow \infty$ ), inductor acts as a short-circuit,  $v_L(\infty) = 0$  and  $i(\infty) = \frac{V}{R}$ .
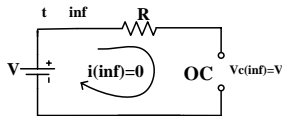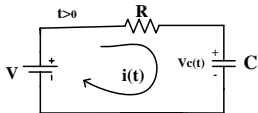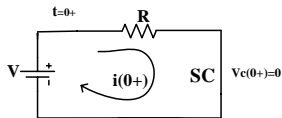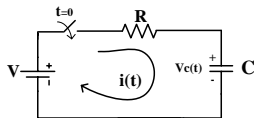
# DC source with RC with Switch

- Voltage across the capacitor cannot change instantaneously.
- At  $t(0+)$ , capacitor  $\rightarrow$  Short Circuit  $\Rightarrow v_C(0+) = 0$ .  
 $i_C(0+) = i(0+) = \frac{V}{R}$ .
- For general  $t > 0$ ,

$$V = Ri(t) + \frac{1}{C} \int_0^t i(t) dt.$$





# DC source with RC with Switch

- Expression for capacitor voltage is

$$v_C(t) = V - Ve^{-\frac{t}{RC}}.$$


- Expression for capacitor current is

$$i(t) = \frac{V}{R}e^{-\frac{t}{RC}}.$$

- At steady-state ( $t \rightarrow \infty$ ), capacitor acts as a open-circuit,  $v_C(\infty) = V$  and  $i(\infty) = 0$ .
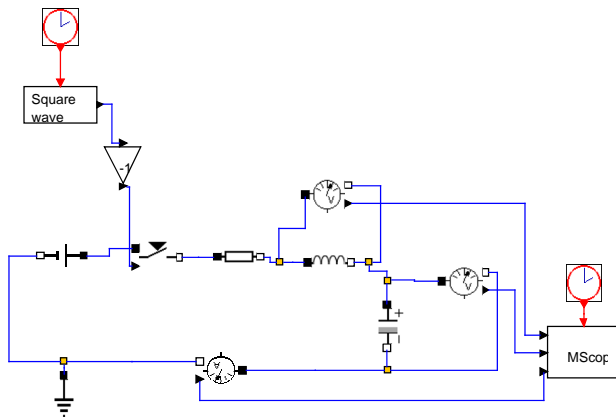
# DC source with RLC with Switch

- Two storing elements.
- Second-order system.



# DC source with RLC with Switch

- KVL gives

$$V = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i(t) dt.$$

- The second-order ODE is

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0.$$

- At  $t(0+)$ ,  $i(0+) = 0$ ,  $\frac{di}{dt}(0+) = \frac{V}{L} = \frac{v_L(0+)}{L}$ .

# DC source with RLC with Switch

- Using Laplace transform

$$I(s) = \frac{V/L^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

- As  $t \rightarrow \infty$ , current  $i(t)$  will decay to zero. But the way it will decay to zero will be decided by the value of  $R$ .
- Equating the denominator polynomial to zero,

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- The roots are

$$s_{1,2} = \frac{-R/L \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2}$$

# DC source with RLC with Switch

- The transient behaviour of  $i(t)$  will be decided by the factor

$$D \doteq \frac{R^2}{L^2} - \frac{4}{LC} (<, >, =) 0.$$

- If  $D = 0$  then

$$R = 2\sqrt{\frac{L}{C}}.$$

Response is overdamped.


- If

$$R < 2\sqrt{\frac{L}{C}}.$$

Response is underdamped.

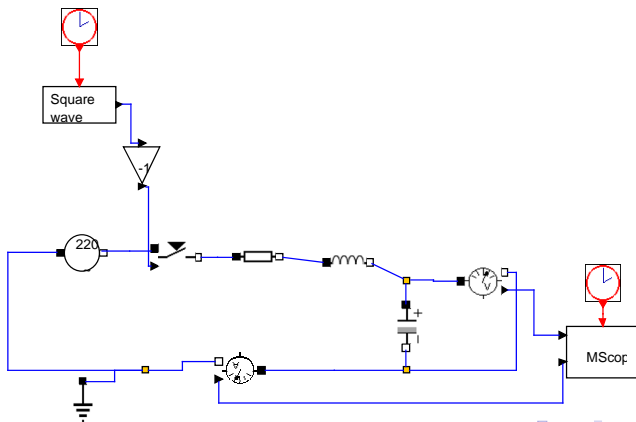
# AC source with RLC with Switch

- Sinusoidal source connected to a series RLC ckt through the switch.
- Second-order system.



# Complicated Networks

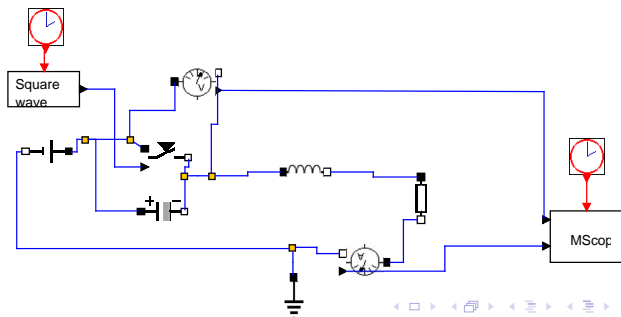- Examples taken from the book: Network Analysis, by M.E. Van Valkenburg, PHI Publishers, New Delhi, 2006.
- Ex. 5-6, Page 132.
- Steady-state is reached with switch closed. At  $t = 0$ , the switch is opened. Find voltage across the switch and the value of its first time derivative at  $t = 0+$ .



# Complicated Networks

- Ex. 4-1, Page 112.
- Steady-state is reached with switch in position 1. At  $t = 0$ , the switch moved from 1 to 2. Find  $i(t)$ .

