

Scilab Manual for
Power Electronics Lab
by Prof C Harinatha Reddy
Electrical Engineering
G Pulla Reddy Engineering College ¹

Solutions provided by
Prof C Harinatha Reddy
Electrical Engineering
G Pulla Reddy ENgineering College (Autonomous)

May 24, 2026

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website <http://scilab.in>

Contents

| | |
|---|----|
| List of Scilab Solutions | 3 |
| 1 Uncontrolled 1-phase Half and Full wave rectifier with R load | 5 |
| 2 Uncontrolled 3-phase Half wave and Full wave rectifier | 6 |
| 3 Controlled 1-phase Half and Full wave rectifier with R Load | 9 |
| 4 Controlled 3-phase Half and Full wave rectifier with R Load | 12 |
| 5 Step Down and Step up chopper with R load | 17 |
| 6 1-phase AC- voltage controller with R load | 20 |
| 7 1-phase Inverter (Half Bridge and H bridge) with R load | 22 |

List of Experiments

List of Figures

| | | |
|-----|--|----|
| 2.1 | Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load | 7 |
| 2.2 | Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load | 7 |
| 2.3 | Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load | 8 |
| 2.4 | Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load | 8 |
| 3.1 | Circuit Diagram of 1phase Half Wave controlled Rectifier with R load | 10 |
| 3.2 | Circuit Diagram of 1phase Full Wave uncontrolled Rectifier with R load | 11 |
| 4.1 | Circuit Diagram of 3phase Half controlled Rectifier with R load | 13 |
| 4.2 | Circuit Diagram of 3phase Half controlled Rectifier with R load | 14 |
| 4.3 | Circuit Diagram of 3phase Full Wave controlled Rectifier with R load | 15 |
| 4.4 | Circuit Diagram of 3phase Full Wave controlled Rectifier with R load | 16 |
| 5.1 | Circuit Diagram of StepDownchopper with R load | 18 |
| 5.2 | Circuit Diagram of Step Up chopper with R load | 19 |
| 6.1 | Circuit Diagram of 1phase AC Vokltage controller with R load | 21 |
| 7.1 | Circuit Diagram of Half bridge Inverter with R load | 23 |
| 7.2 | Circuit Diagram of Half bridge Inverter with R load | 24 |
| 7.3 | Circuit Diagram of Full bridge Inverter with R load | 25 |
| 7.4 | Circuit Diagram of Full bridge Inverter with R load | 26 |

Experiment: 1

Uncontrolled 1-phase Half and Full wave rectifier with R load

This code can be downloaded from the website www.scilab.in This code

can be downloaded from the website www.scilab.in

Experiment: 2

Uncontrolled 3-phase Half wave and Full wave rectifier

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

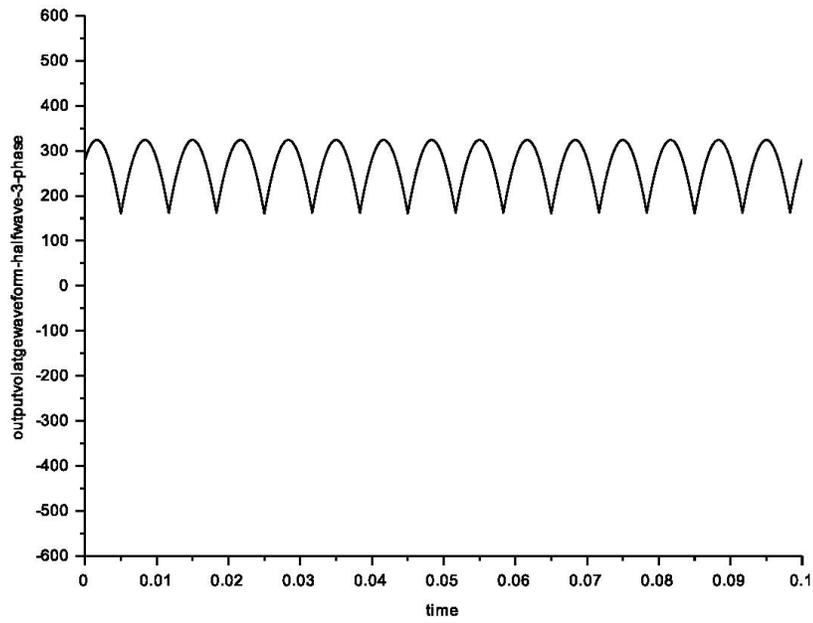


Figure 2.1: Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load

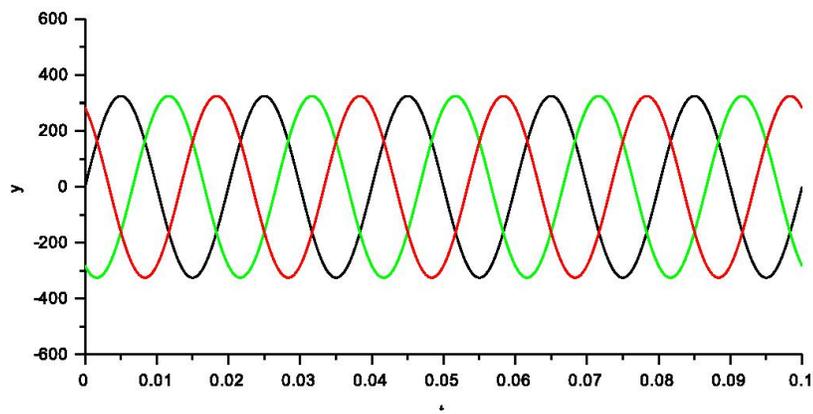


Figure 2.2: Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load

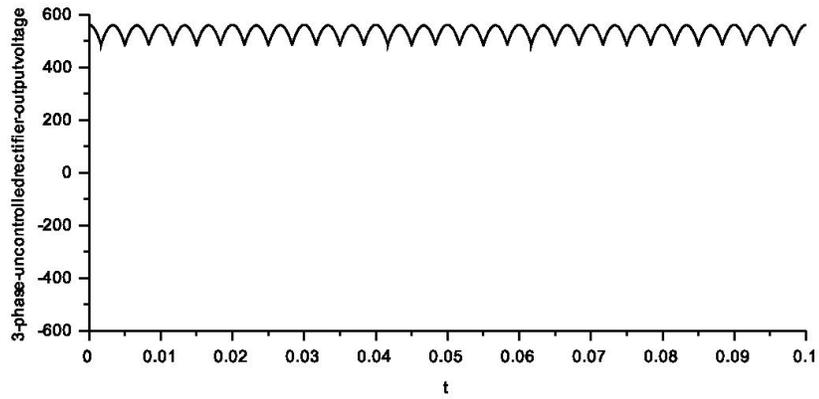


Figure 2.3: Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load

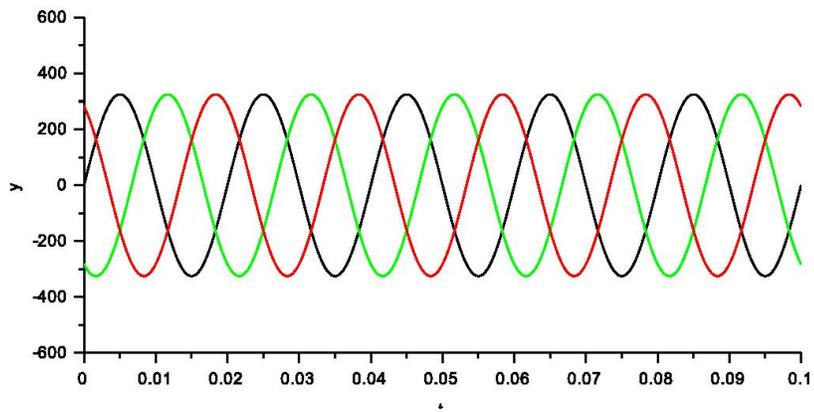


Figure 2.4: Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load

Experiment: 3

Controlled 1-phase Half and Full wave rectifier with R Load

This code can be downloaded from the website www.scilab.in This code

can be downloaded from the website www.scilab.in

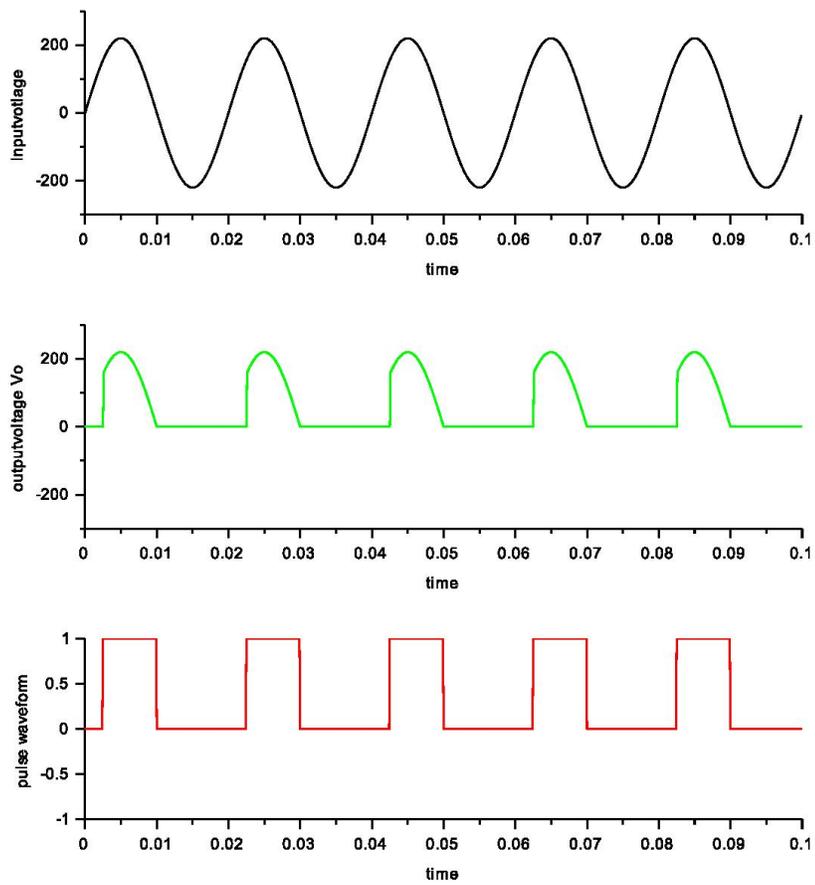


Figure 3.1: Circuit Diagram of 1phase Half Wave controlled Rectifier with R load

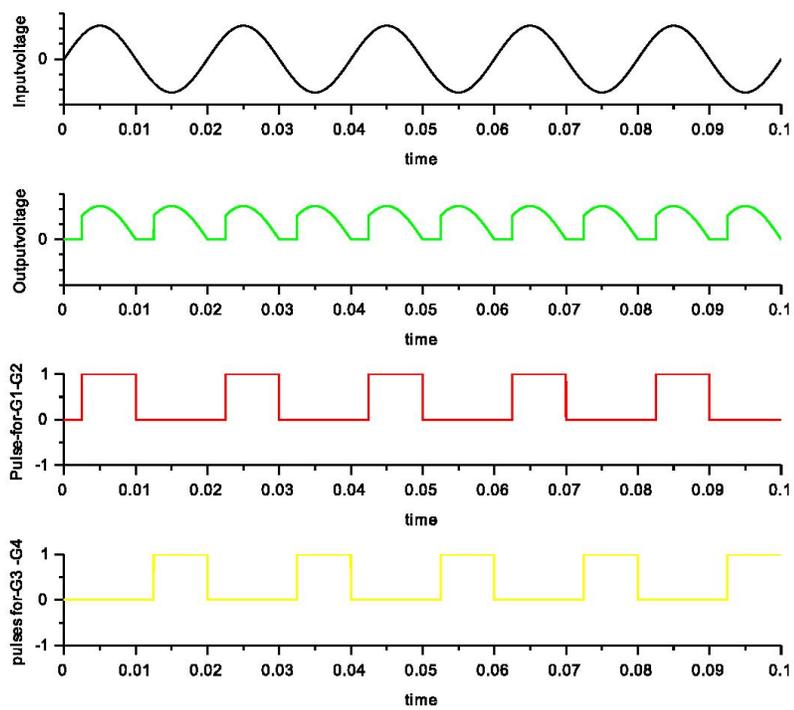


Figure 3.2: Circuit Diagram of 1phase Full Wave uncontrolled Rectifier with R load

Experiment: 4

Controlled 3-phase Half and Full wave rectifier with R Load

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

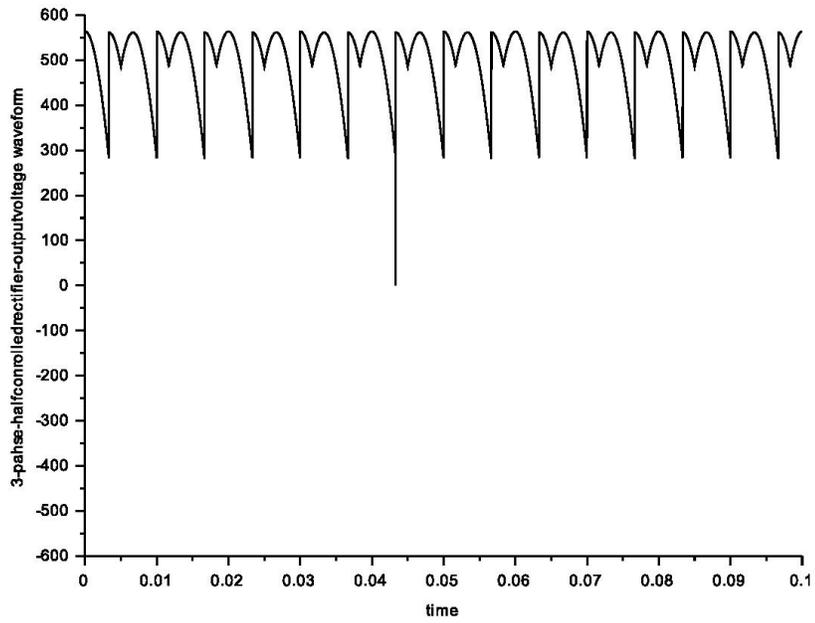


Figure 4.1: Circuit Diagram of 3phase Half controlled Rectifier with R load

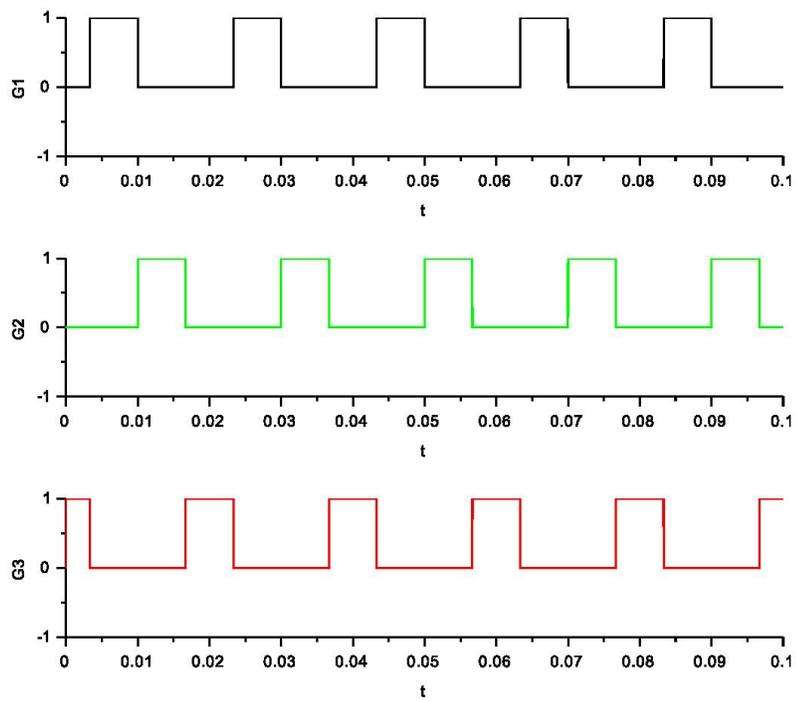


Figure 4.2: Circuit Diagram of 3phase Half controlled Rectifier with R load

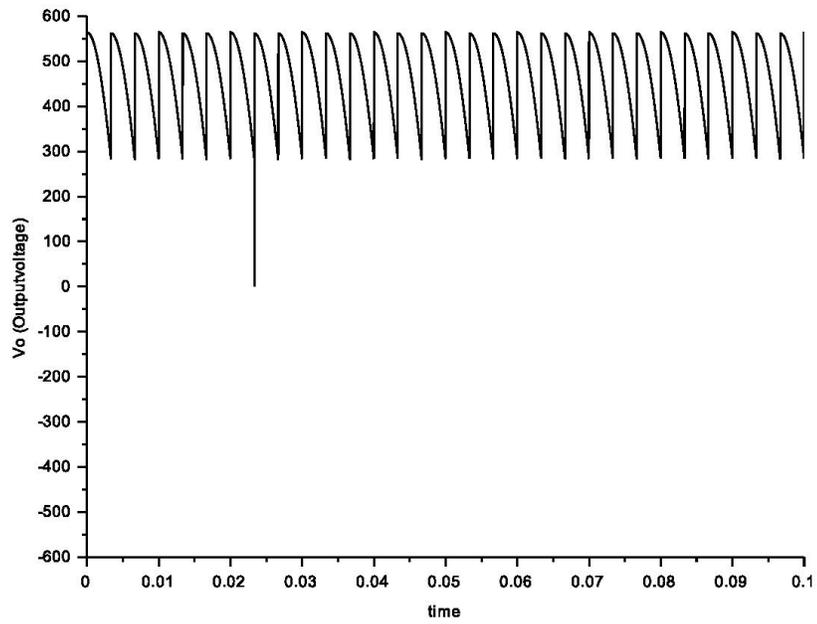


Figure 4.3: Circuit Diagram of 3phase Full Wave controlled Rectifier with R load

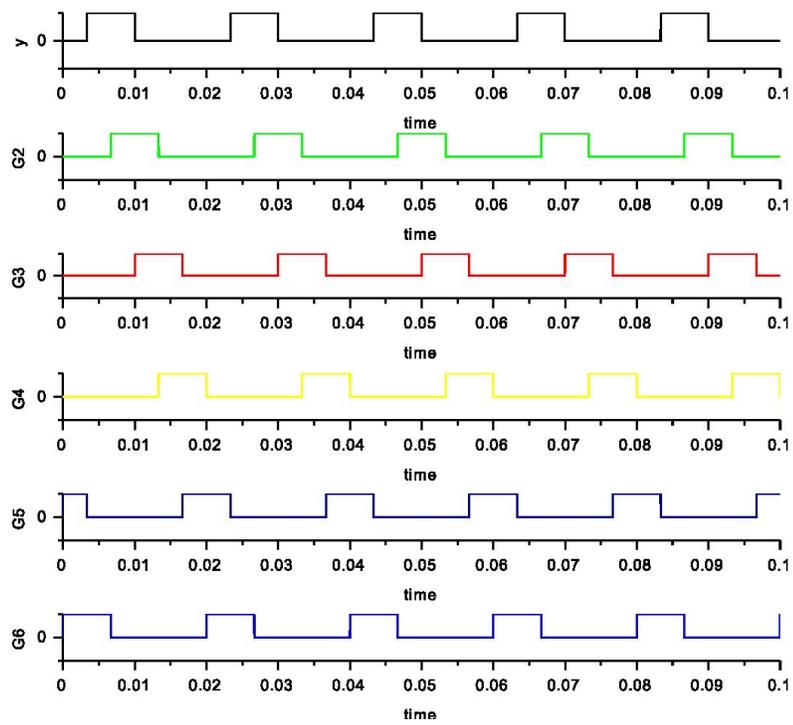


Figure 4.4: Circuit Diagram of 3phase Full Wave controlled Rectifier with R load

Experiment: 5

Step Down and Step up chopper with R load

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

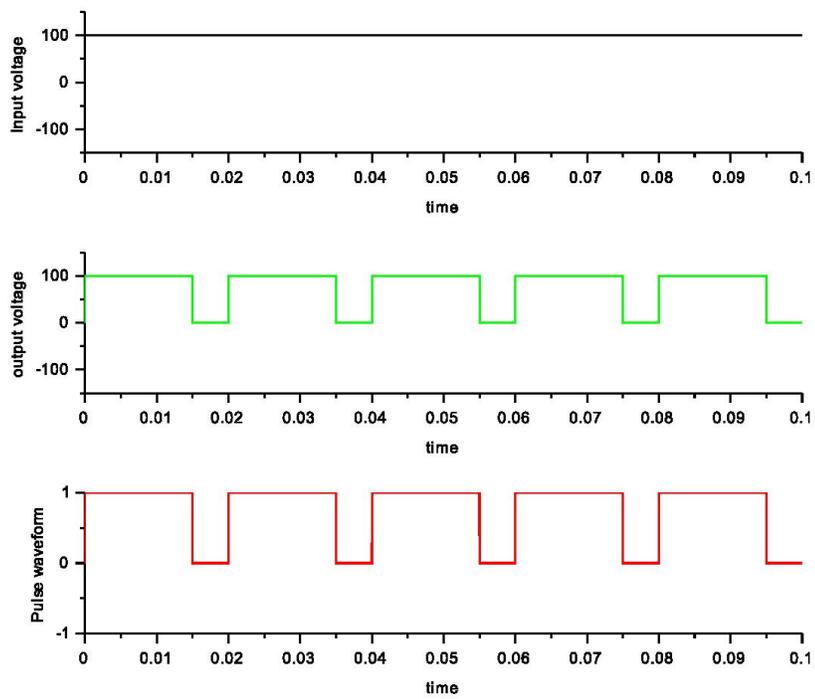


Figure 5.1: Circuit Diagram of StepDownchopper with R load

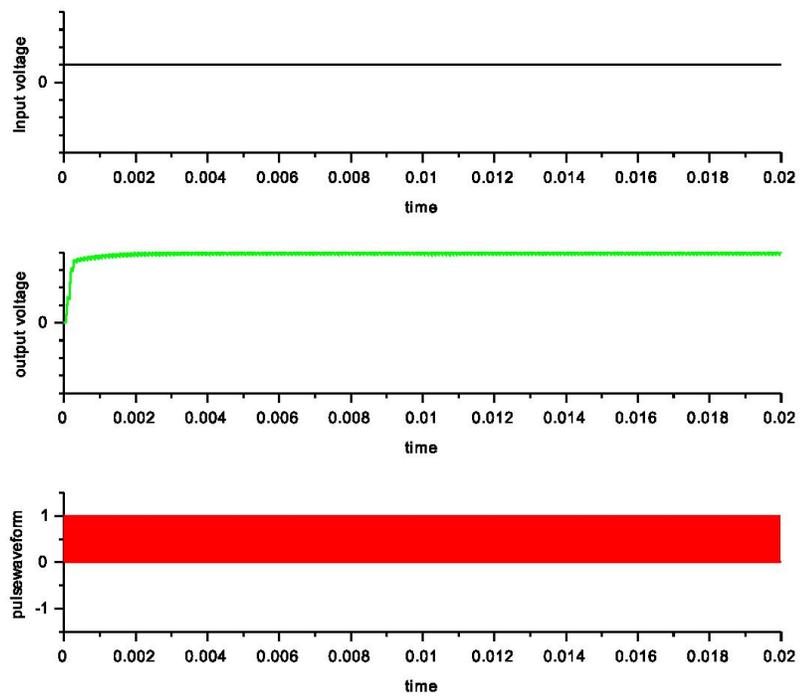


Figure 5.2: Circuit Diagram of Step Up chopper with R load

Experiment: 6

1-phase AC- voltage controller with R load

This code can be downloaded from the website www.scilab.in

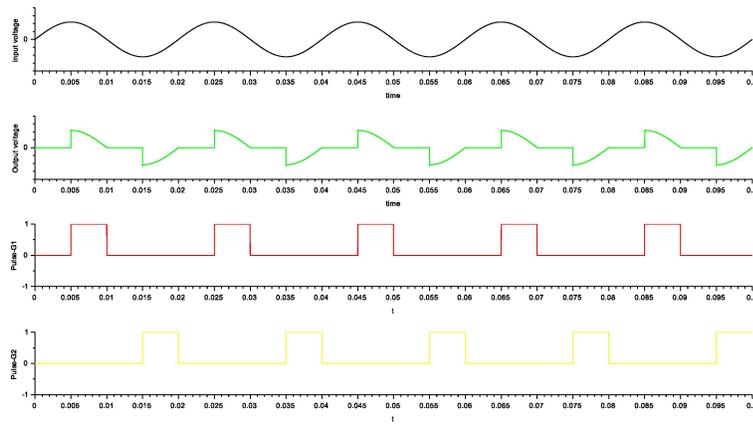


Figure 6.1: Circuit Diagram of 1phase AC Vokltage controller with R load

Experiment: 7

1-phase Inverter (Half Bridge and H bridge) with R load

This code can be downloaded from the website www.scilab.in This code

can be downloaded from the website www.scilab.in

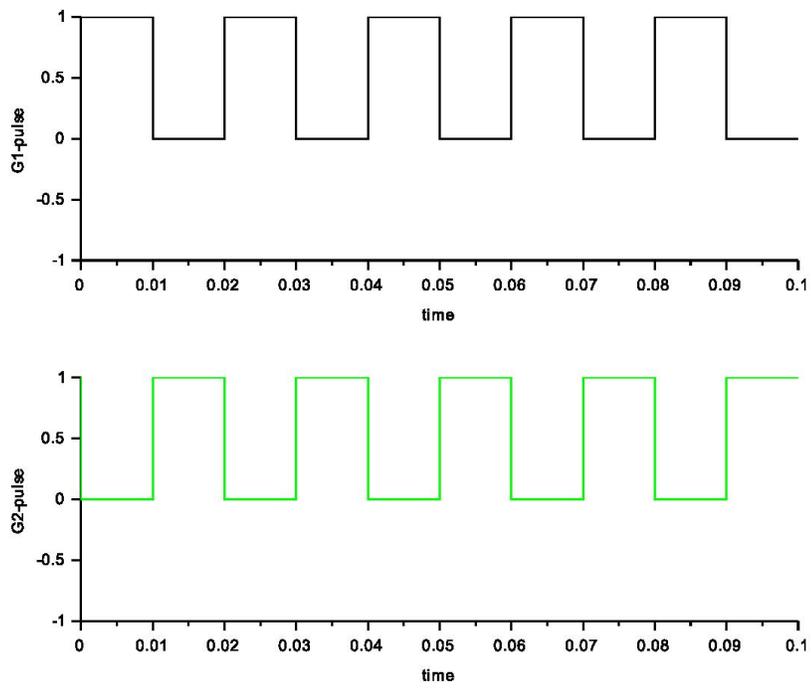


Figure 7.1: Circuit Diagram of Half bridge Inverter with R load

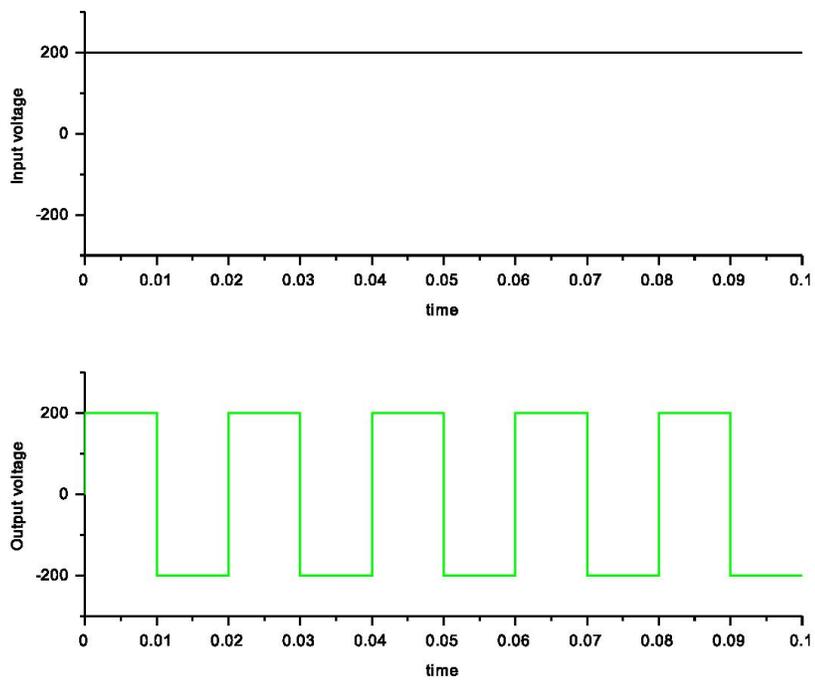


Figure 7.2: Circuit Diagram of Half bridge Inverter with R load

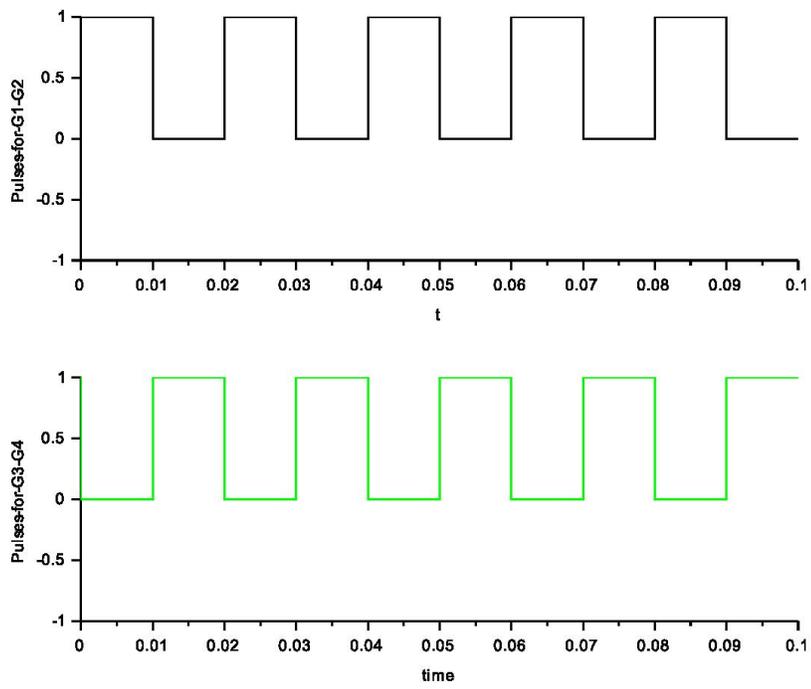


Figure 7.3: Circuit Diagram of Full bridge Inverter with R load

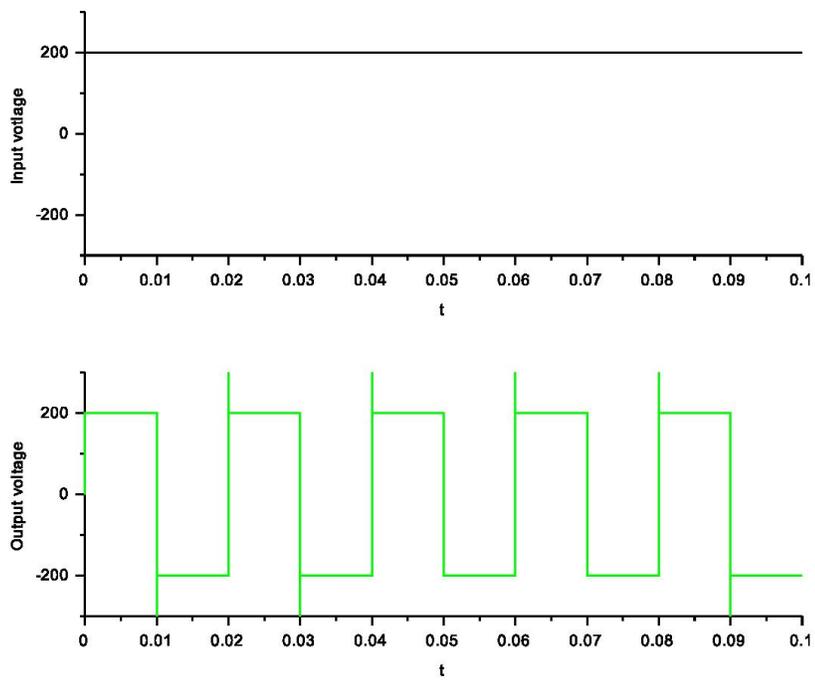


Figure 7.4: Circuit Diagram of Full bridge Inverter with R load