

Scilab Manual for
Simulation lab / Pulse & Digital Circuits lab /
SEEK Course (Skill for Employability
Enhancement of Knowledge) / DLDMP lab
by Dr Jitesh Ramdas Shinde
Others
Vaagdevi College Of Engineering¹

Solutions provided by
Dr Jitesh Ramdas Shinde
Others
Vaagdevi College Of Engineering

April 27, 2024

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website <http://scilab.in>

Contents

List of Scilab Solutions	4
1 Digital Logic Gates Design & Implementation in Xcos	7
2 Half Adder and Full Adder Design & Implementation in Xcos	11
3 Half Subtractor and Full Subtractor Design & Implementation in Xcos	14
4 4 bit Ripple Carry Adder Design & Implementation in Xcos	17
5 BCD Adder Design & Implementation in Xcos	20
6 Multiplexer Design and implementation & its application in Xcos	22
7 Demultiplexer Design and implementation & its application in Xcos	25
8 Decoder Design and implementation & its application in Xcos	28
9 Flip flop Design & Implementation in Xcos	31
10 Asynchronous Counter Design & Implementation in Xcos	34
11 Synchronous Counter Design & Implementation in Xcos	36

12 Code Converter Design (eg.binary to gray code conversion) & Implementation in Xcos	39
--	----

List of Experiments

List of Figures

1.1	XOR gate design using basic logic gates	8
1.2	XOR gate design using basic logic gates	8
1.3	XOR gate design using NAND gate	9
1.4	XOR gate design using NAND gate	9
1.5	XOR gate design using NOR gate	10
1.6	XOR gate design using NOR gate	10
2.1	Half Adder design	12
2.2	Half Adder design	12
2.3	Full Adder Design	13
2.4	Full Adder Design	13
3.1	Half Subtractor design	15
3.2	Half Subtractor design	15
3.3	Full Subtractor Design	16
3.4	Full Subtractor Design	16
4.1	Ripple Carry Adder Design	18
4.2	Ripple Carry Adder Design	19
4.3	Ripple Carry Adder Design	19
5.1	BCD Adder Design	21
5.2	BCD Adder Design	21
6.1	Multiplexer 4 to 1 design	23
6.2	Multiplexer 4 to 1 design	23
6.3	Multiplexer Application Half Adder design	24
6.4	Multiplexer Application Half Adder design	24
7.1	Demultiplexer 1 to 4	26

7.2	Demultiplexer 1 to 4	26
7.3	Demultiplexer Application Half Adder design	27
7.4	Demultiplexer Application Half Adder design	27
8.1	Decoder 2 to 4 design	29
8.2	Decoder 2 to 4 design	29
8.3	Decoder Application Half Subtractor design	30
8.4	Decoder Application Half Subtractor design	30
9.1	JK flip flop	32
9.2	JK flip flop	32
9.3	D flip flop	33
9.4	D flip flop	33
10.1	Asynchronous 3 bit up counter design	35
10.2	Asynchronous 3 bit up counter design	35
11.1	Three bit up synchronous counter	37
11.2	Three bit up synchronous counter	37
11.3	Three bit down synchronous counter	38
11.4	Three bit down synchronous counter	38
12.1	Binary to Gray code converter	40
12.2	Binary to Gray code converter	41
12.3	Binary to Gray code converter	42
12.4	Binary to Gray code converter	42

Experiment: 1

Digital Logic Gates Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

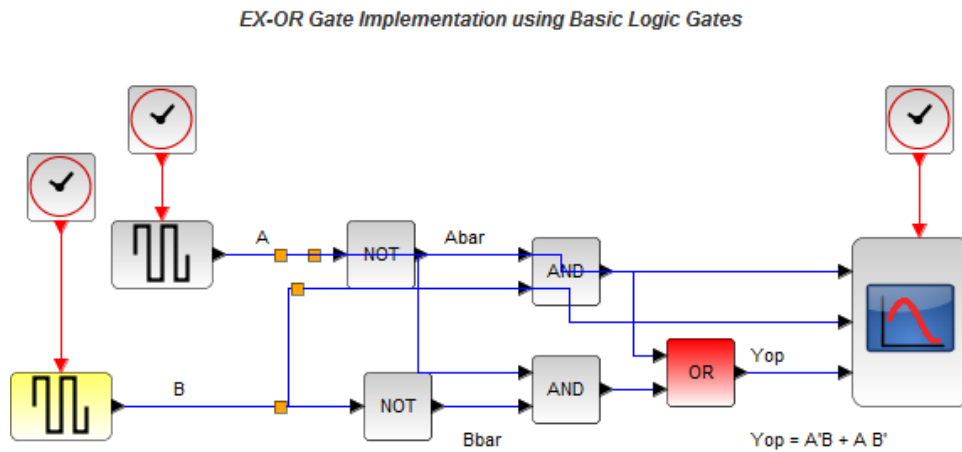


Figure 1.1: XOR gate design using basic logic gates

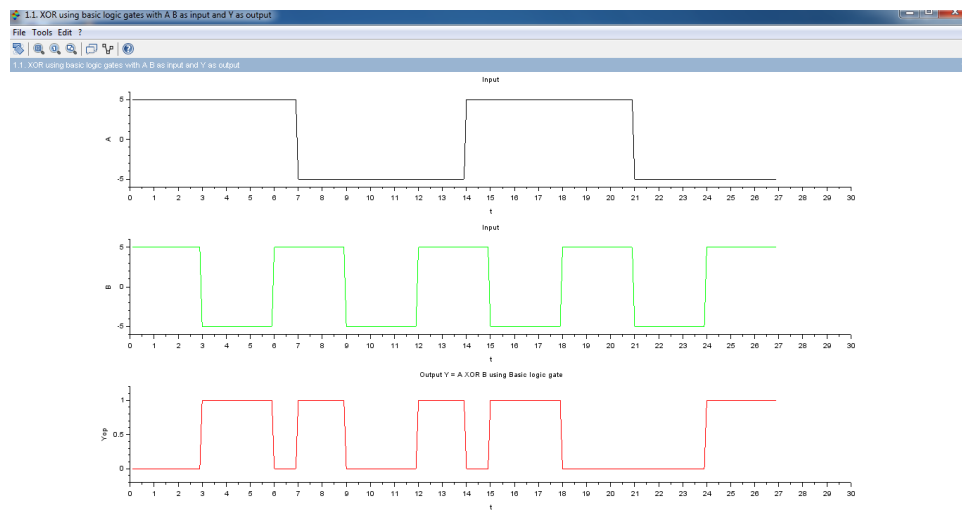


Figure 1.2: XOR gate design using basic logic gates

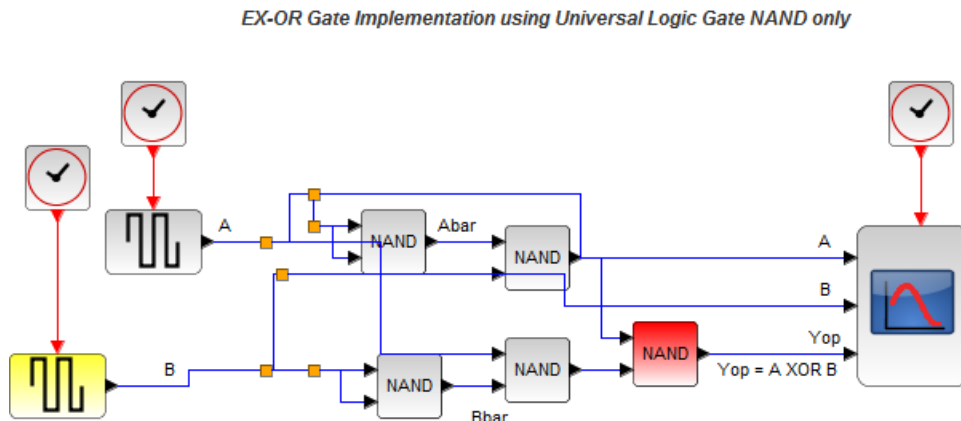


Figure 1.3: XOR gate design using NAND gate

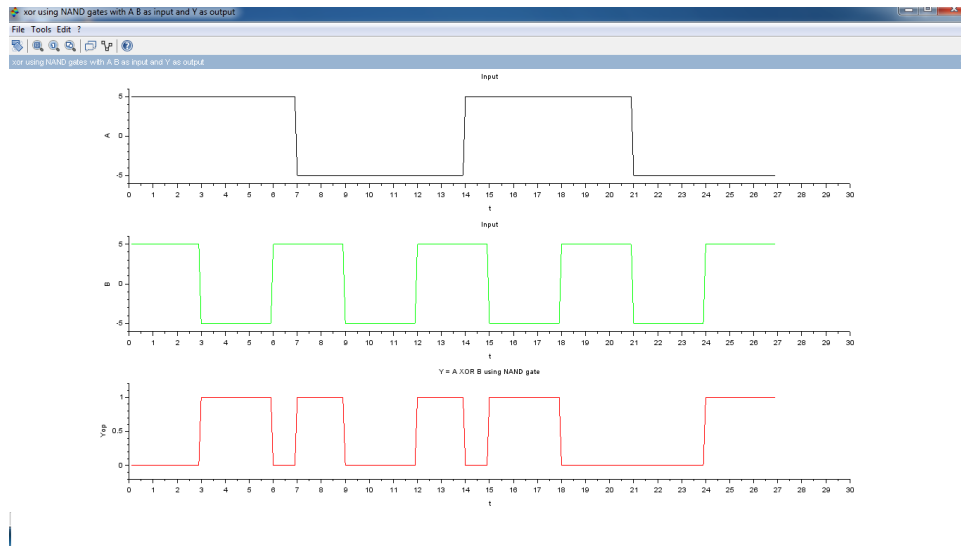


Figure 1.4: XOR gate design using NAND gate

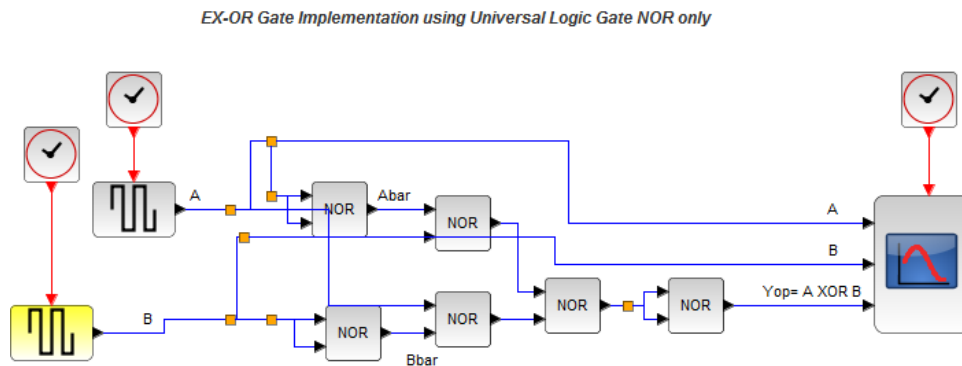


Figure 1.5: XOR gate design using NOR gate

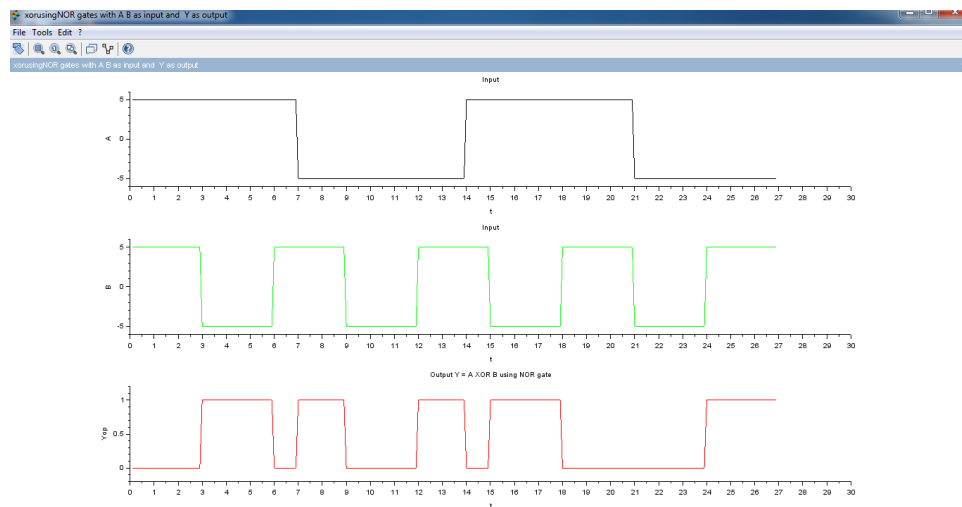


Figure 1.6: XOR gate design using NOR gate

Experiment: 2

Half Adder and Full Adder Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

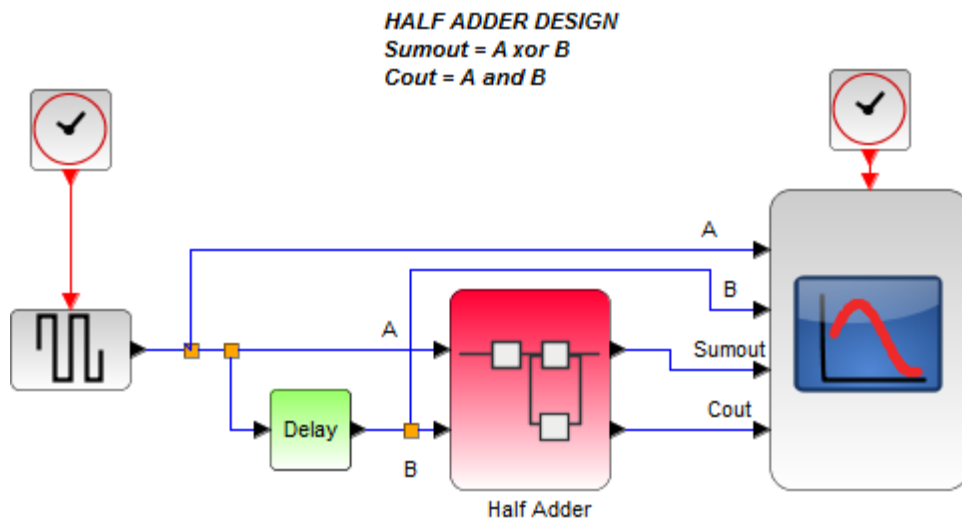


Figure 2.1: Half Adder design


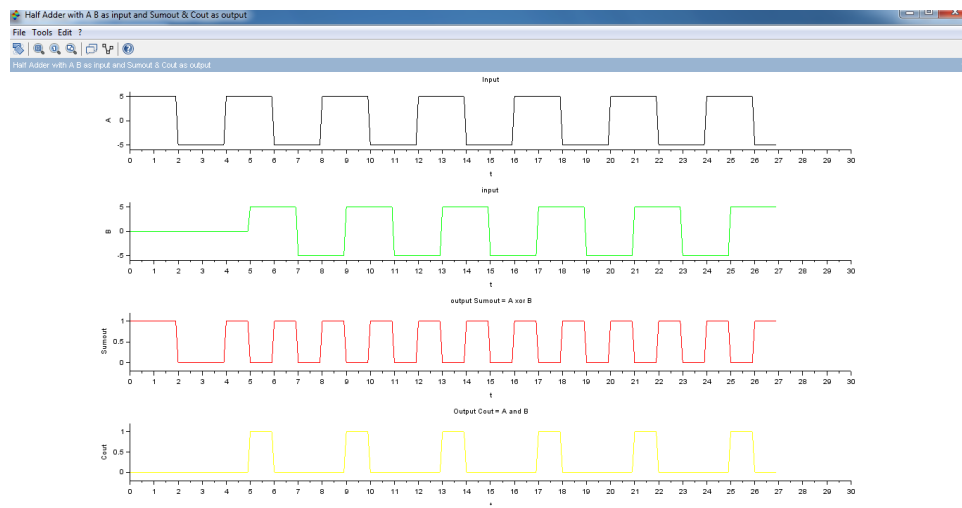


Figure 2.2: Half Adder design

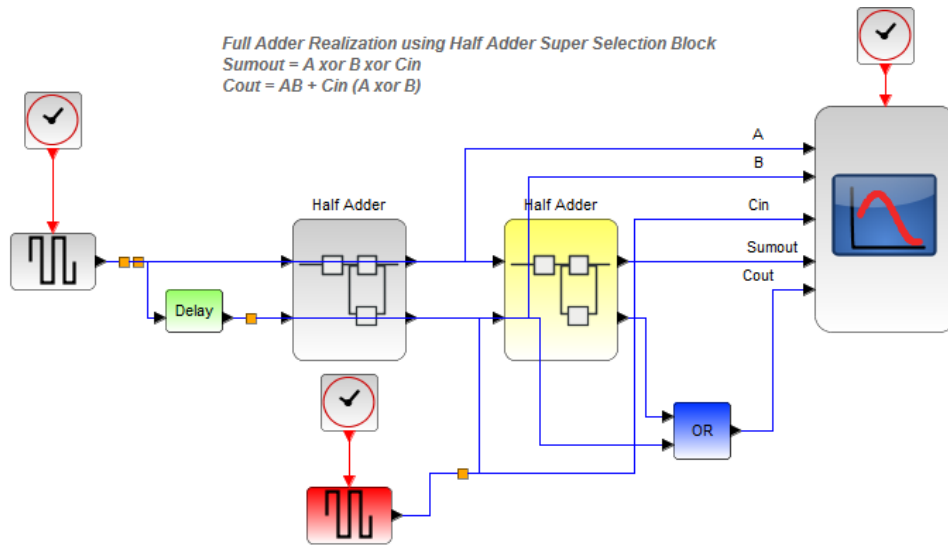

Note : Superselection of superselection not supported in Scilab Xcos.

Figure 2.3: Full Adder Design

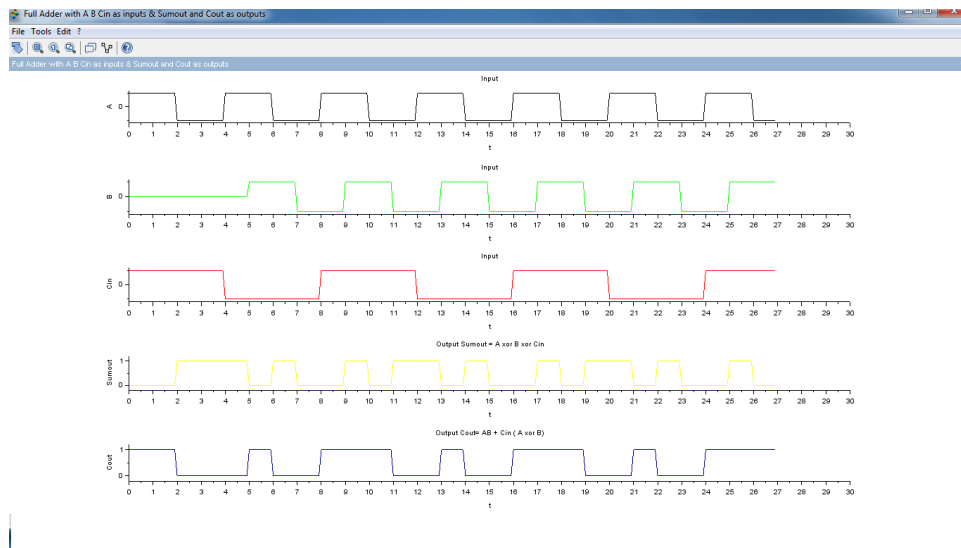


Figure 2.4: Full Adder Design

Experiment: 3

Half Subtractor and Full Subtractor Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

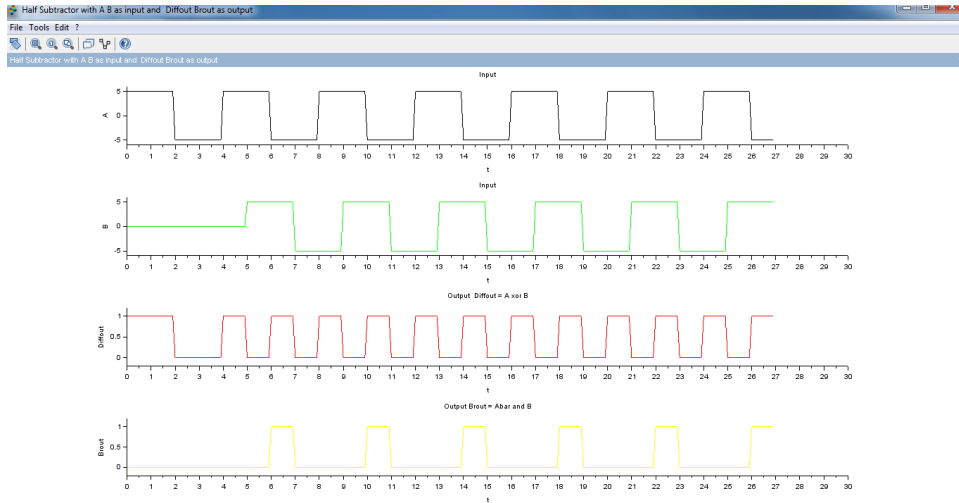


Figure 3.1: Half Subtractor design

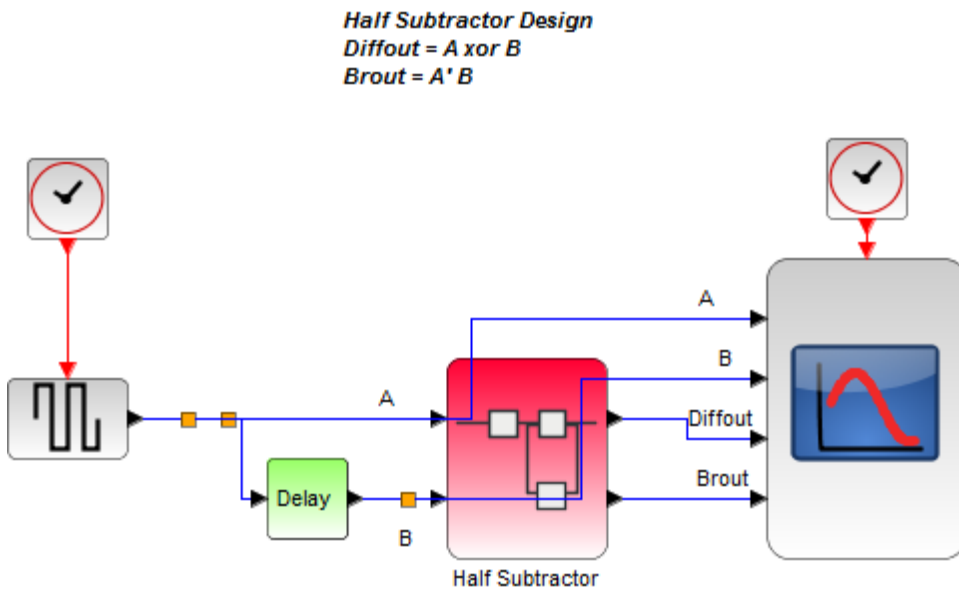


Figure 3.2: Half Subtractor design

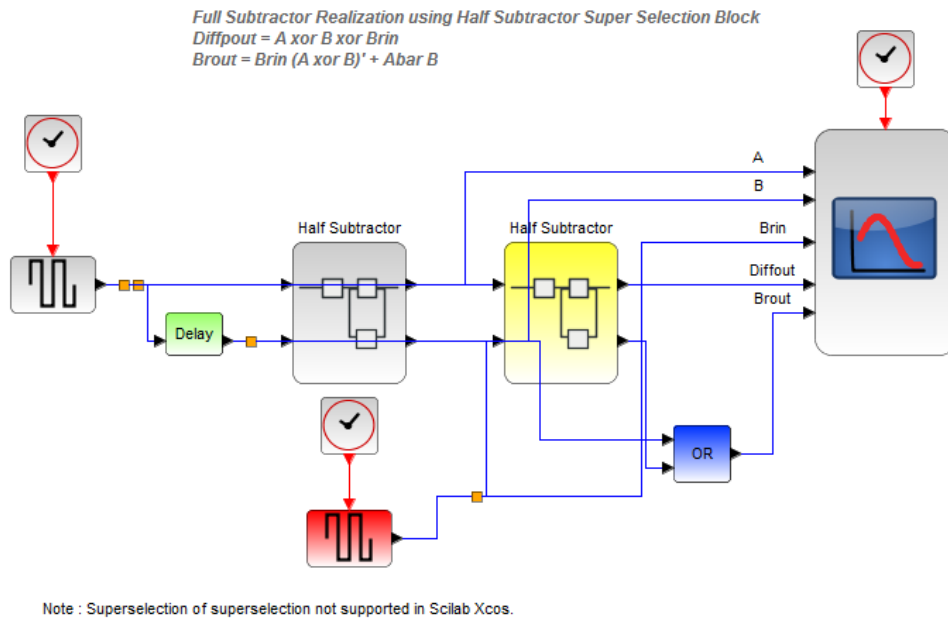


Figure 3.3: Full Subtractor Design

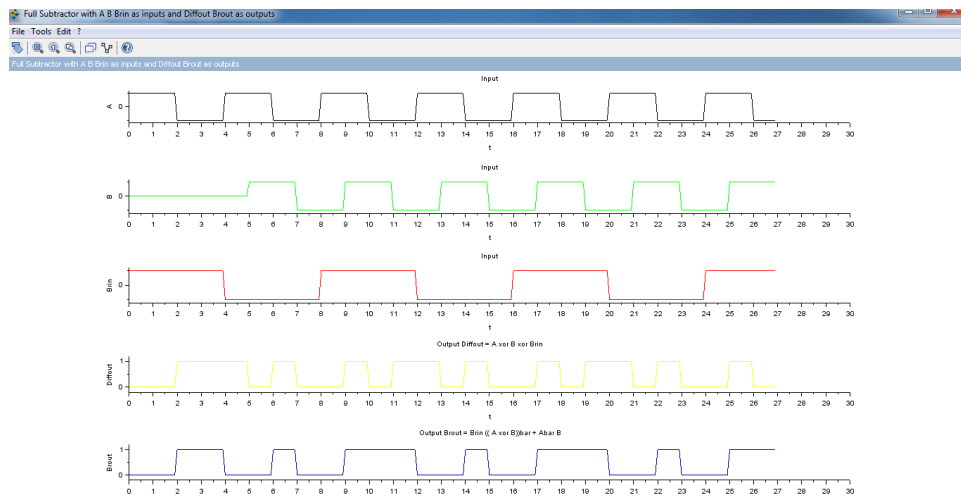


Figure 3.4: Full Subtractor Design

Experiment: 4

4 bit Ripple Carry Adder Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in


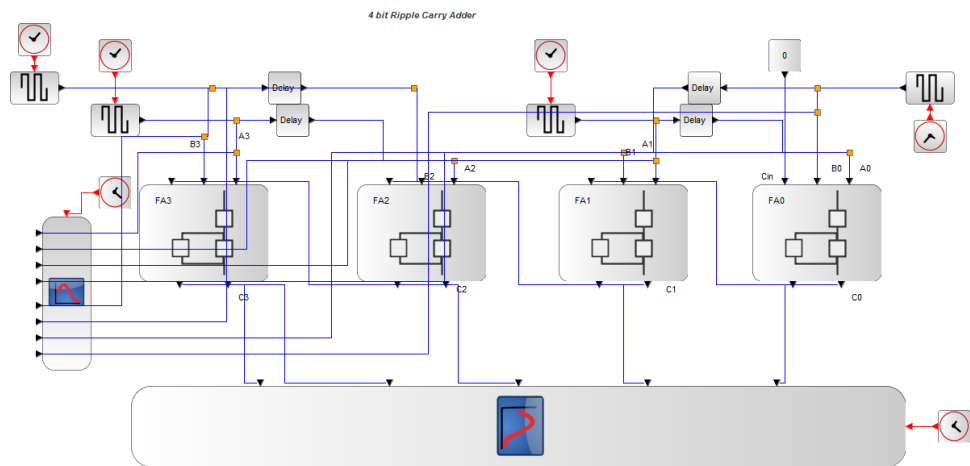
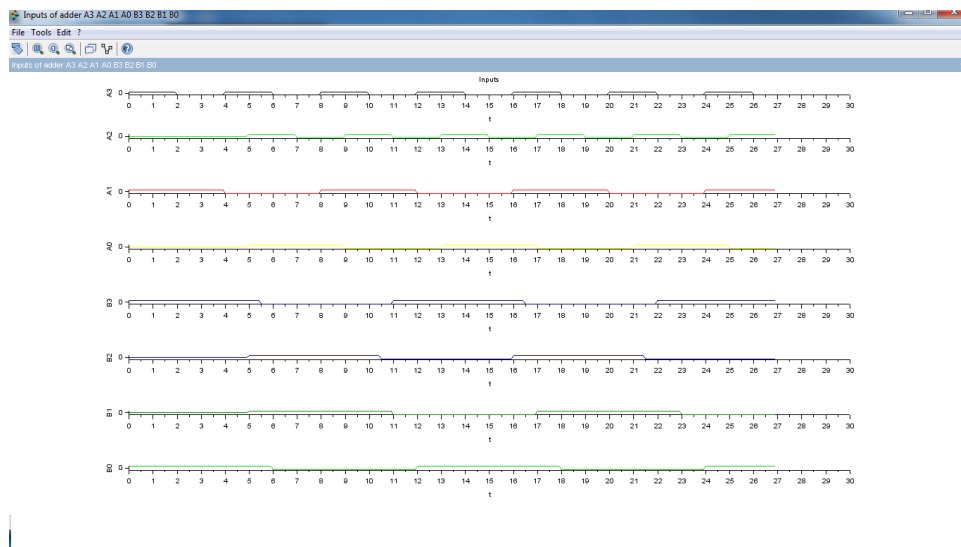


Figure 4.1: Ripple Carry Adder Design

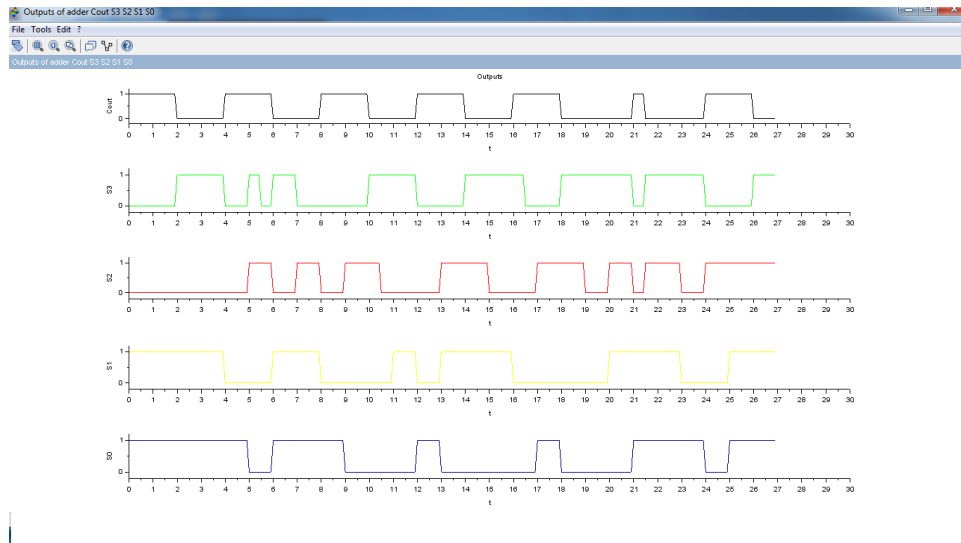

Experiment: 5

BCD Adder Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

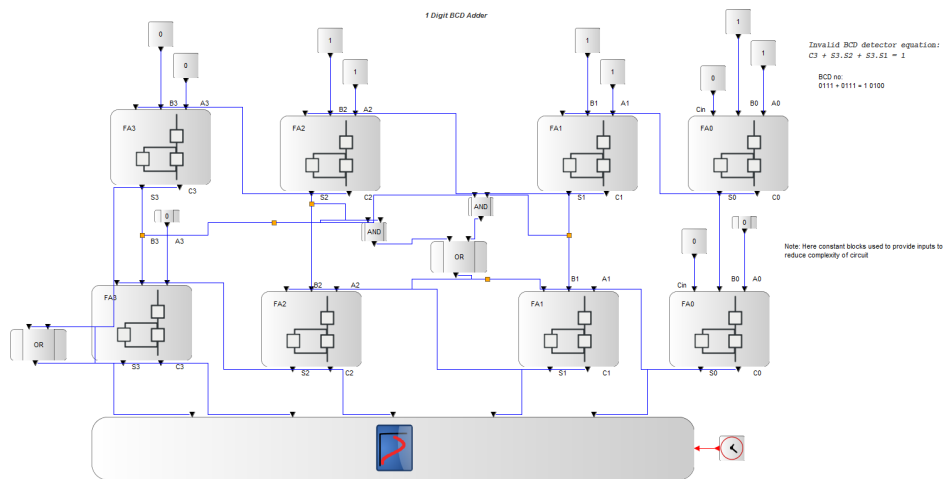


Figure 5.1: BCD Adder Design

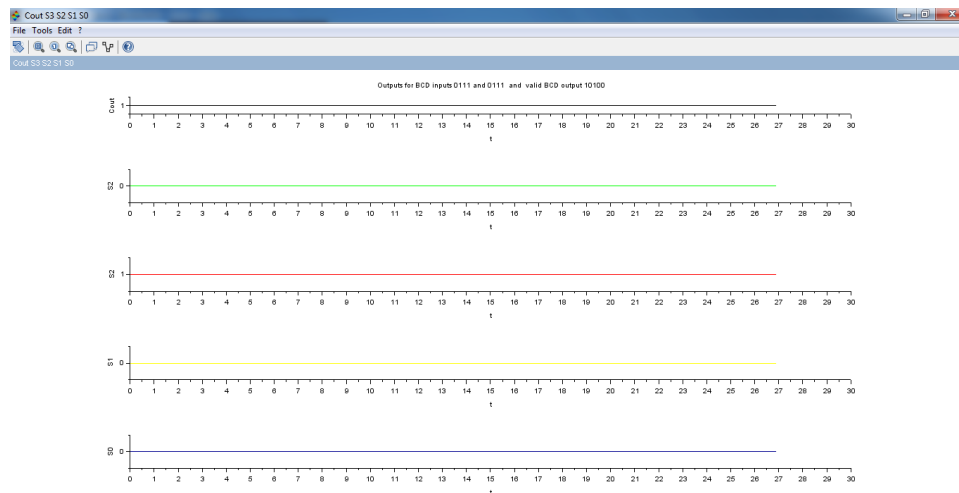


Figure 5.2: BCD Adder Design

Experiment: 6

Multiplexer Design and implementation & its application in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

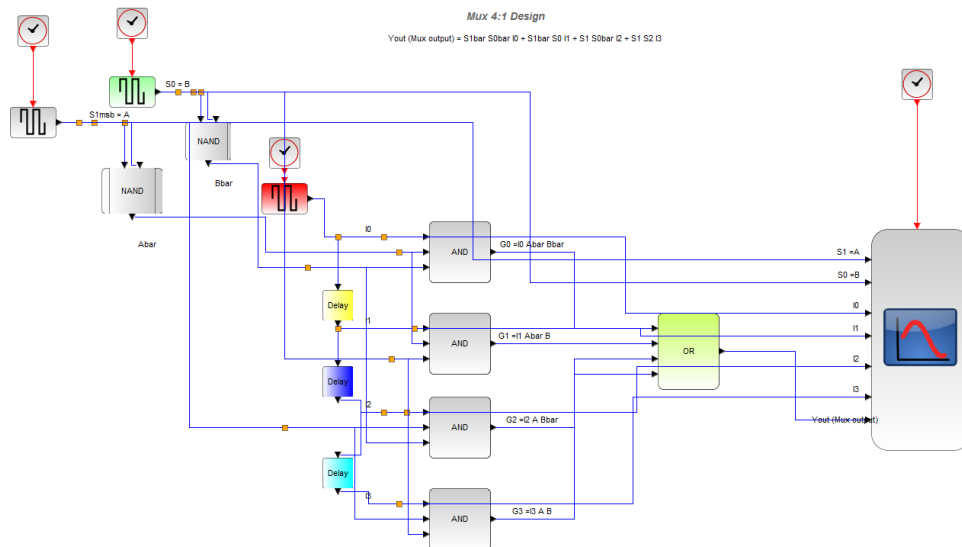


Figure 6.1: Multiplexer 4 to 1 design

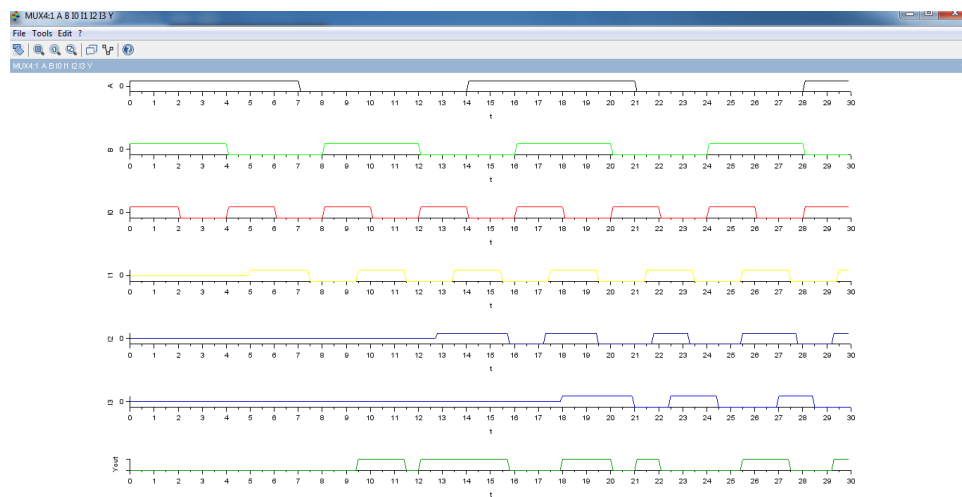


Figure 6.2: Multiplexer 4 to 1 design

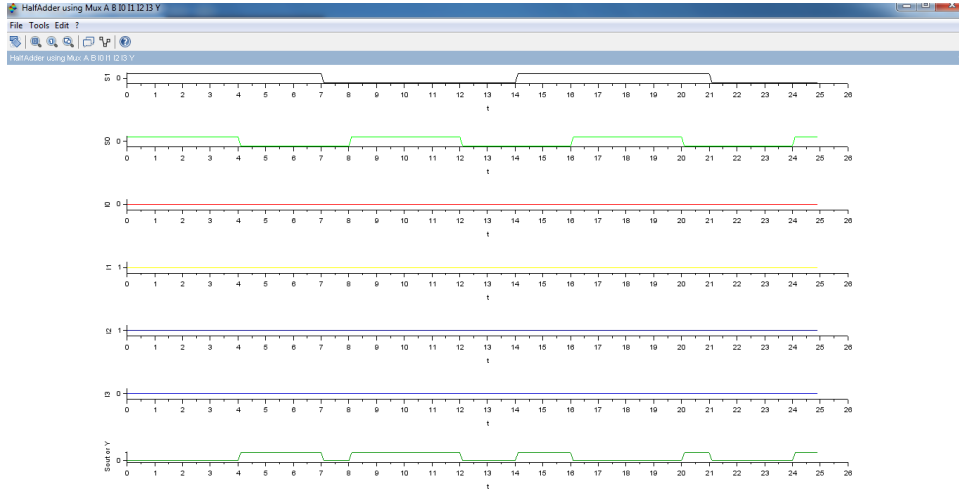


Figure 6.3: Multiplexer Application Half Adder design

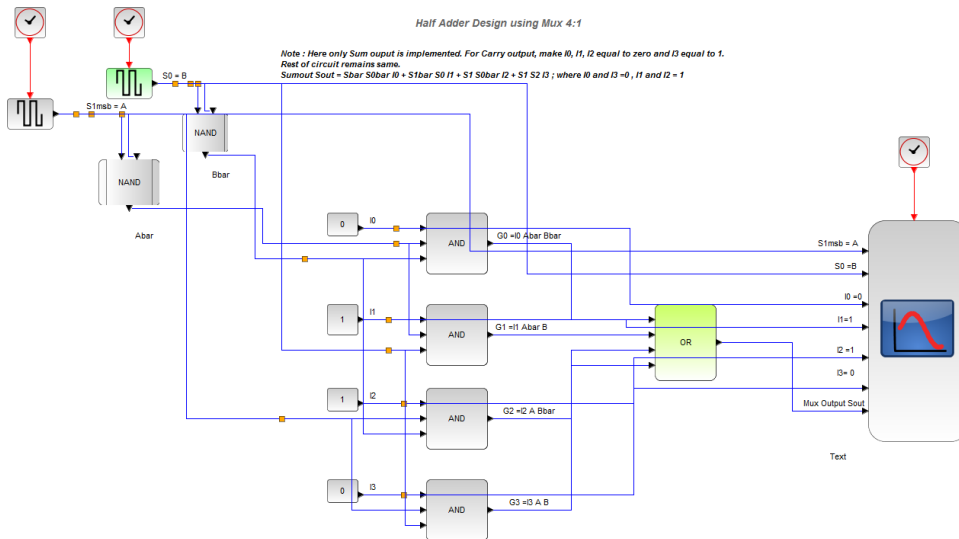


Figure 6.4: Multiplexer Application Half Adder design

Experiment: 7

Demultiplexer Design and implementation & its application in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

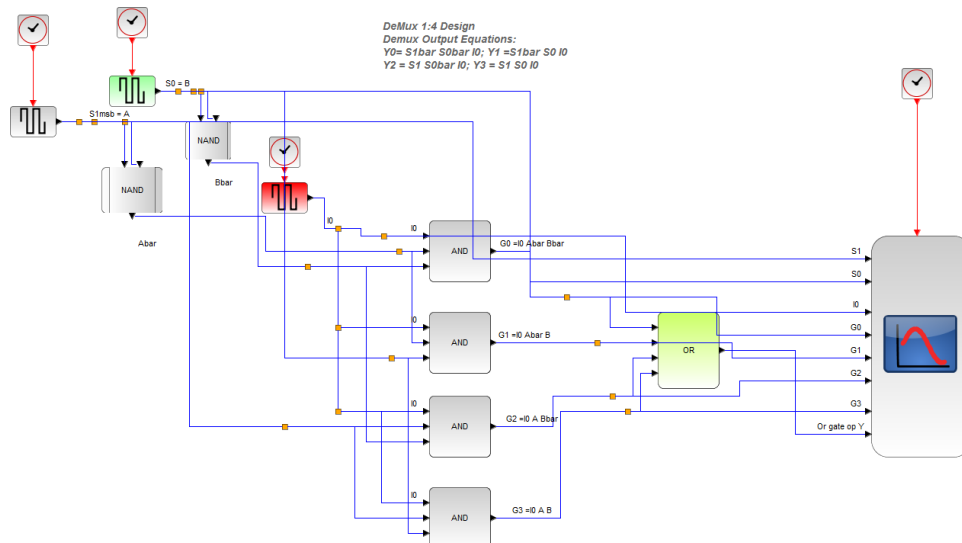


Figure 7.1: Demultiplexer 1 to 4

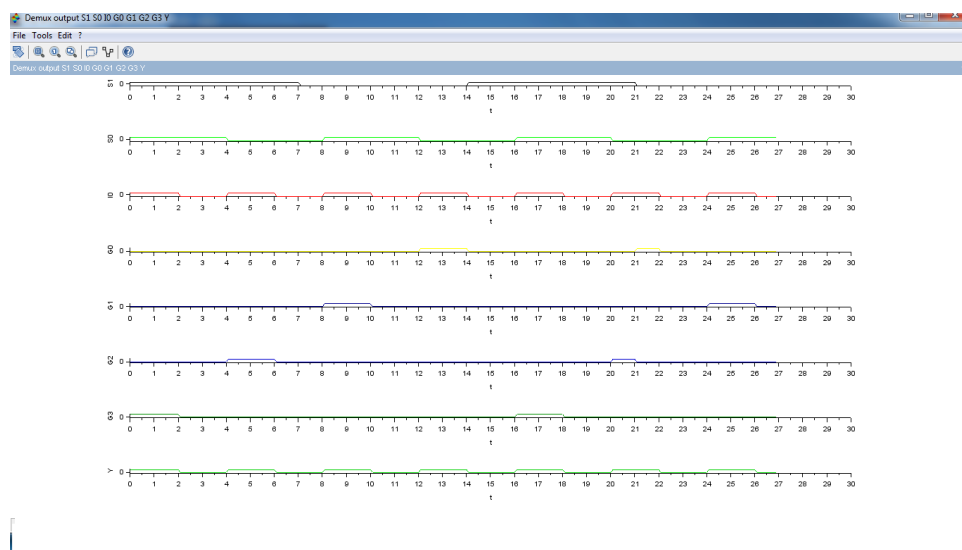


Figure 7.2: Demultiplexer 1 to 4

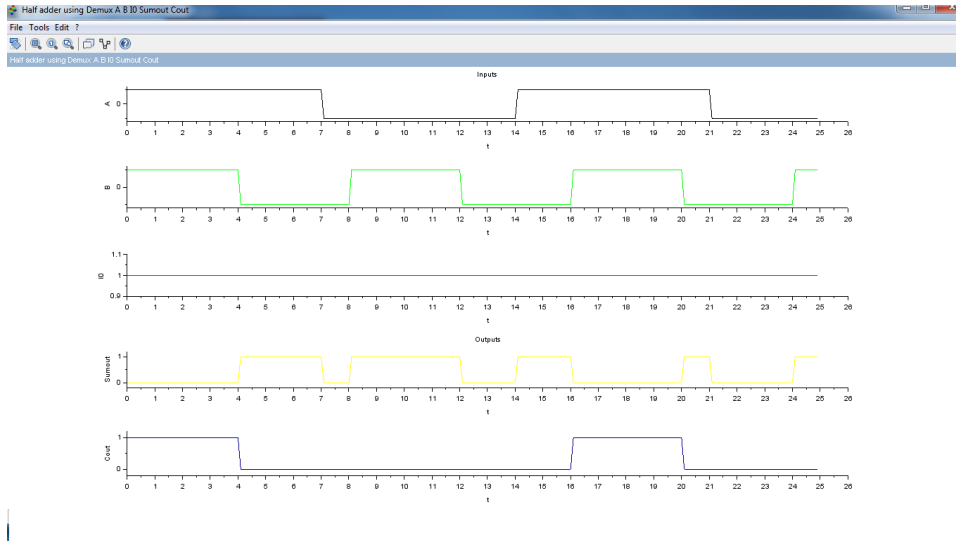


Figure 7.3: Demultiplexer Application Half Adder design

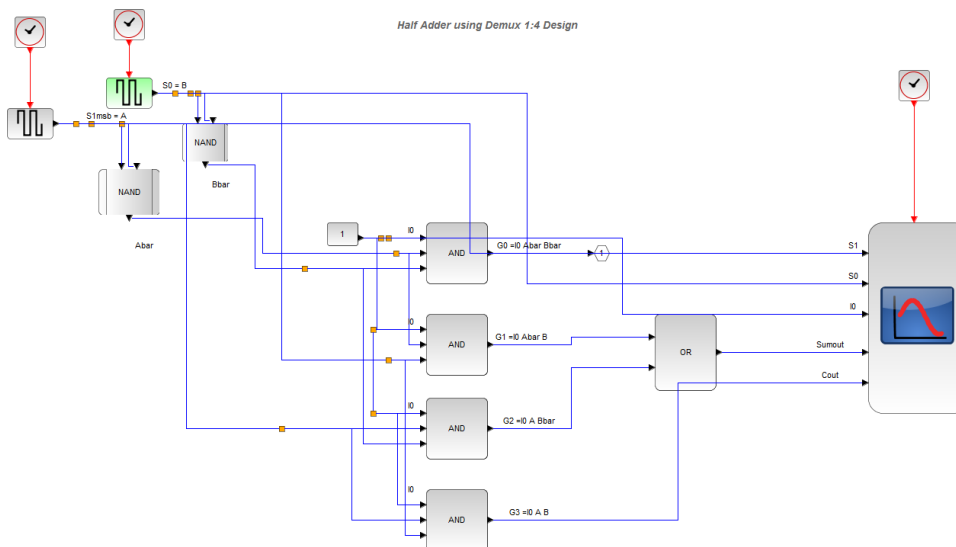


Figure 7.4: Demultiplexer Application Half Adder design

Experiment: 8

Decoder Design and implementation & its application in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

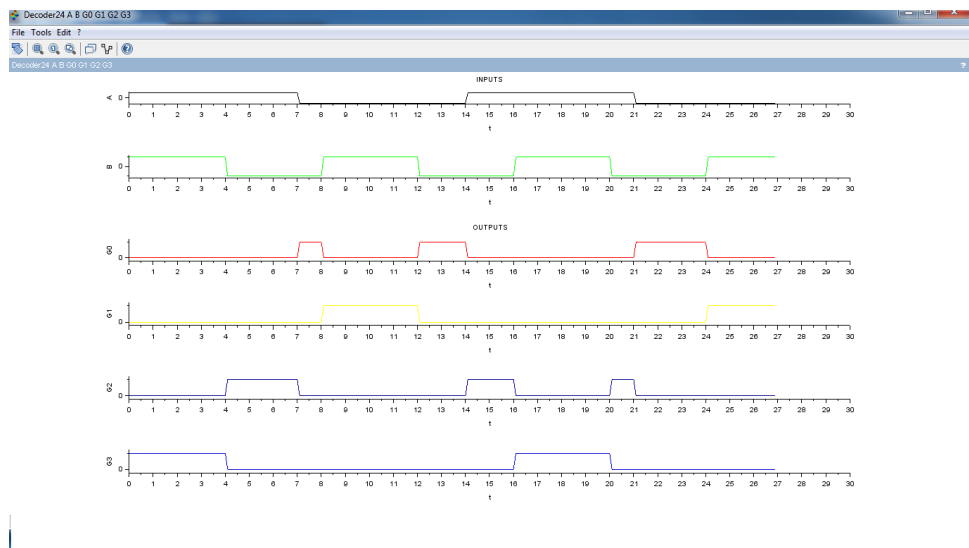


Figure 8.1: Decoder 2 to 4 design

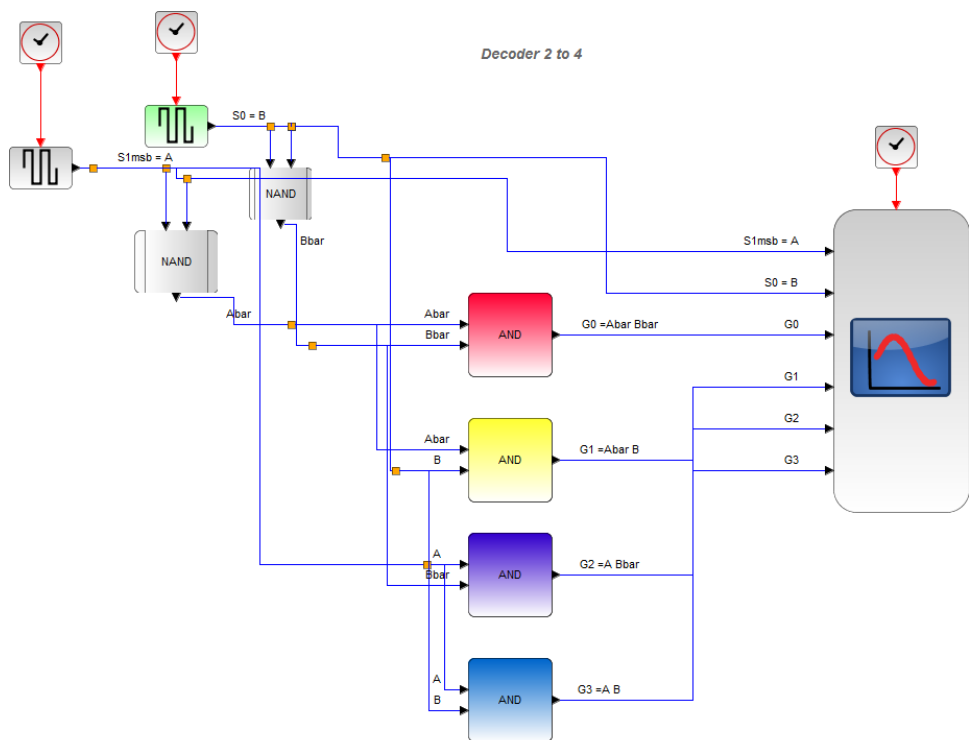


Figure 8.2: Decoder 2 to 4 design

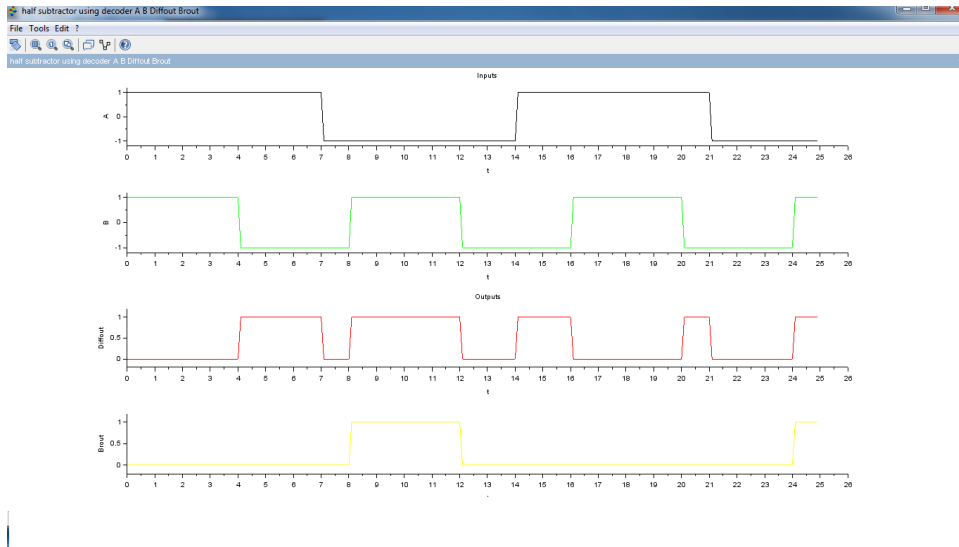


Figure 8.3: Decoder Application Half Subtractor design

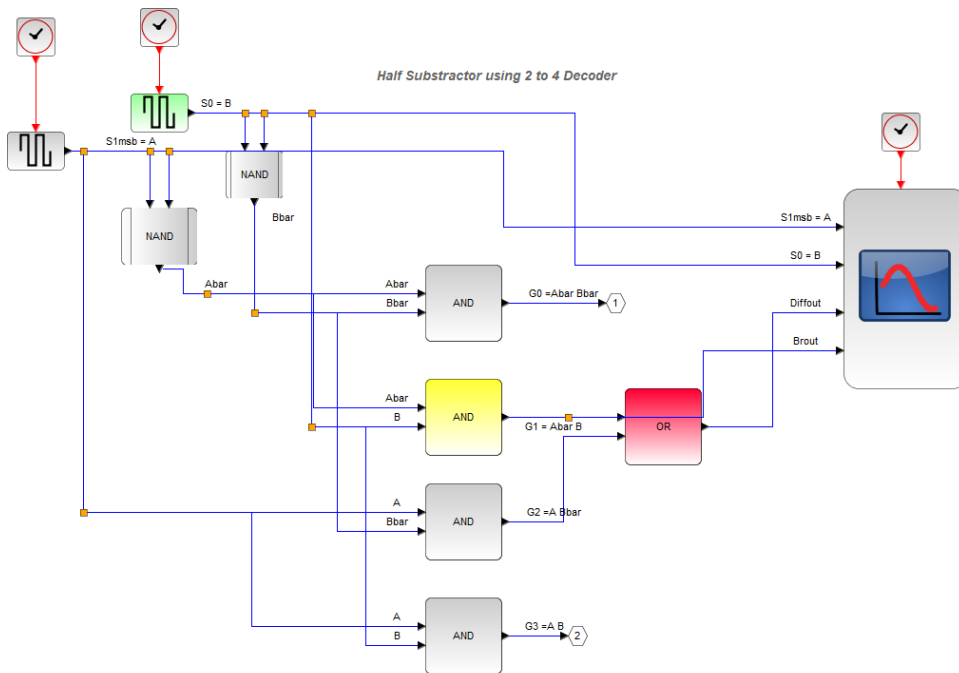


Figure 8.4: Decoder Application Half Subtractor design

Experiment: 9

Flip flop Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

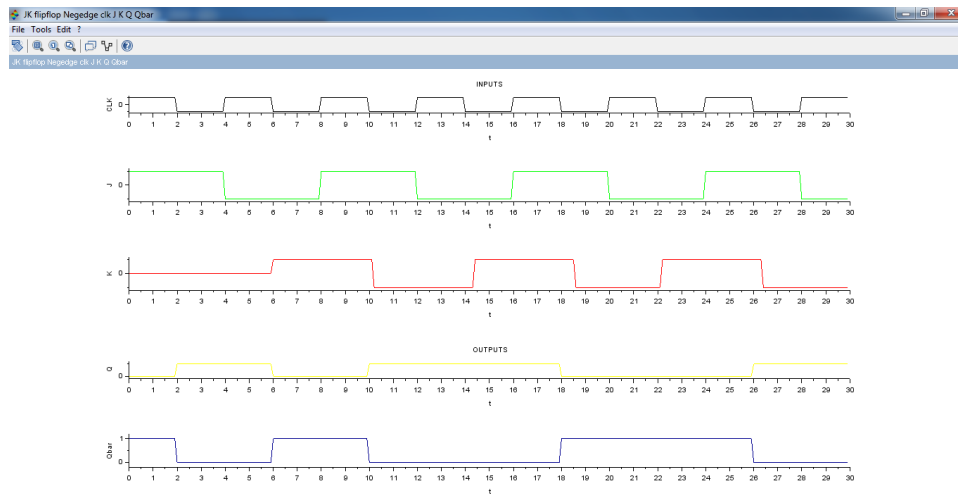


Figure 9.1: JK flip flop

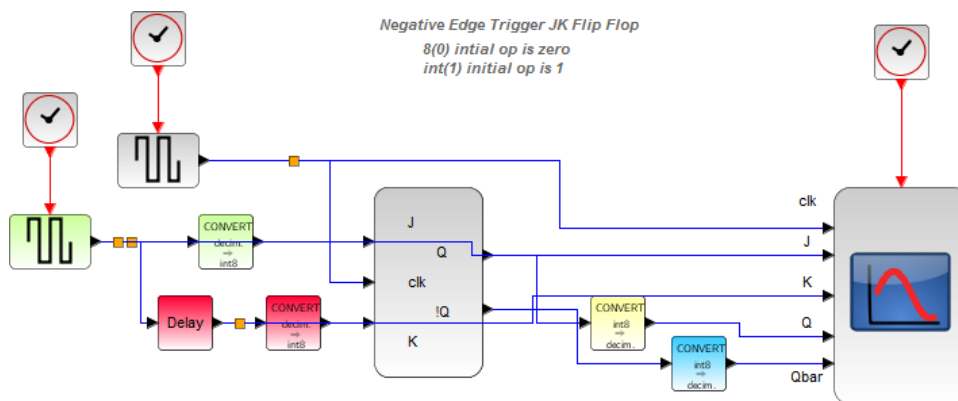


Figure 9.2: JK flip flop

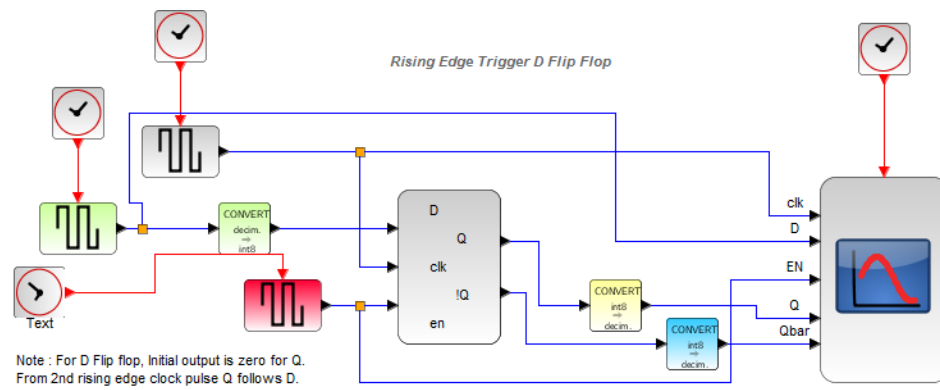


Figure 9.3: D flip flop

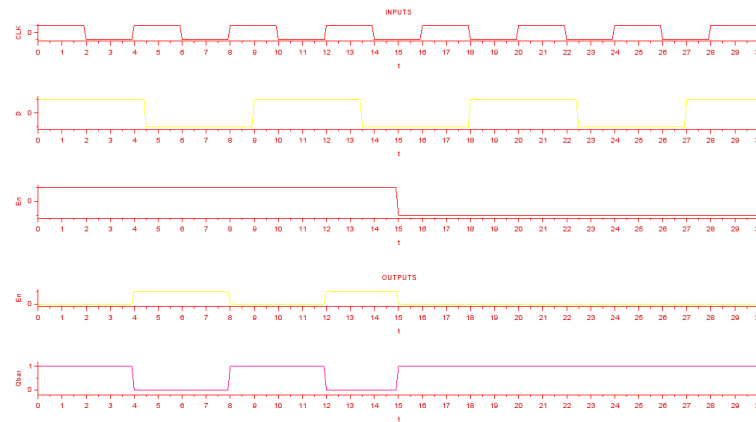


Figure 9.4: D flip flop

Experiment: 10

Asynchronous Counter Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

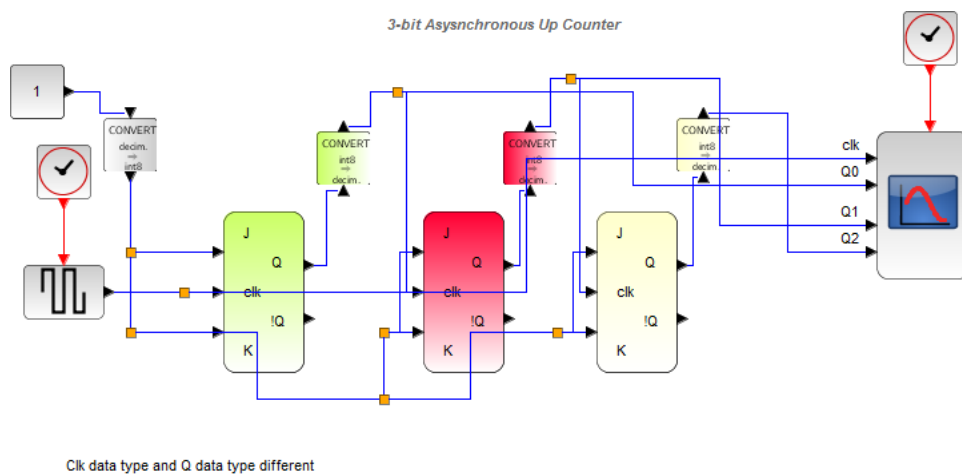


Figure 10.1: Asynchronous 3 bit up counter design

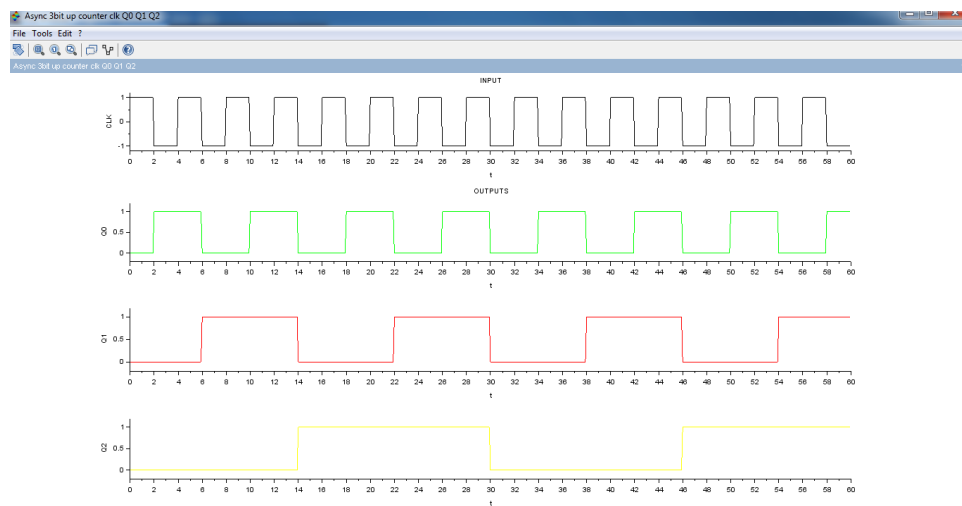


Figure 10.2: Asynchronous 3 bit up counter design

Experiment: 11

Synchronous Counter Design & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

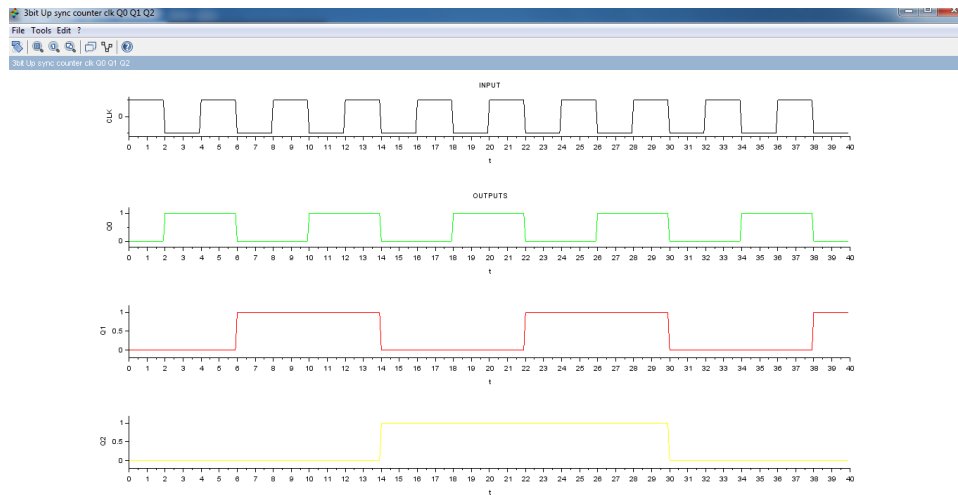


Figure 11.1: Three bit up synchronous counter

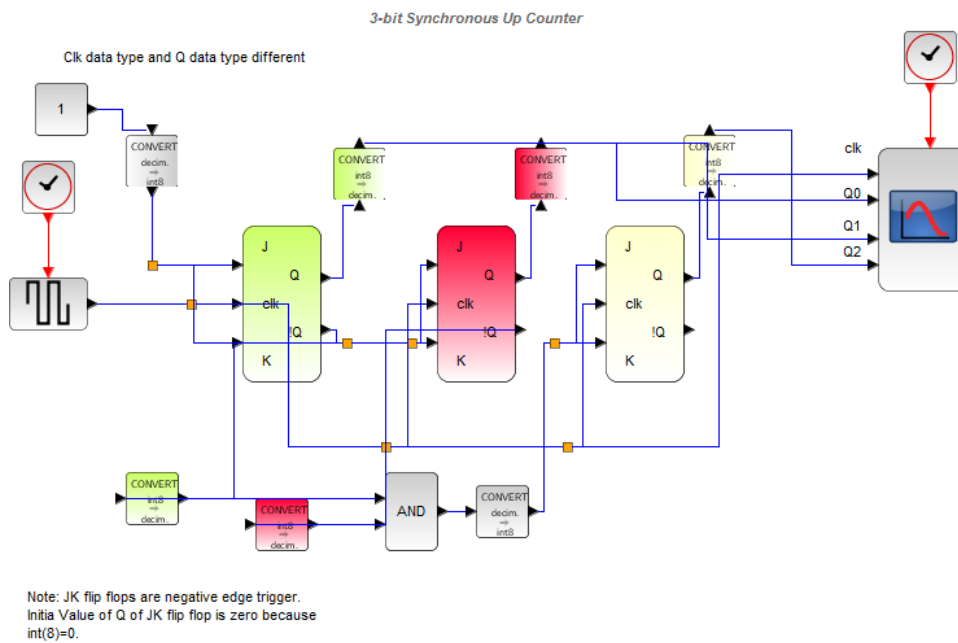


Figure 11.2: Three bit up synchronous counter

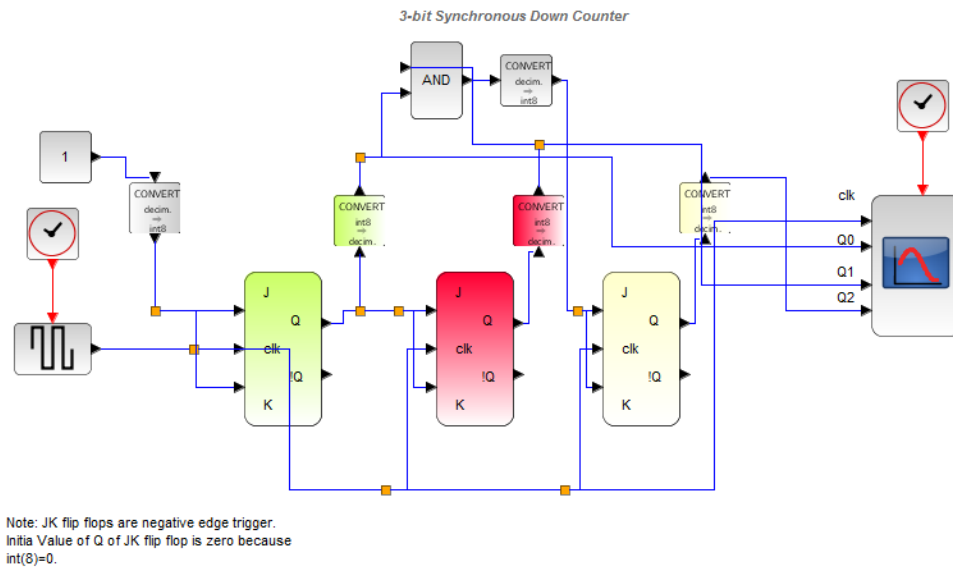


Figure 11.3: Three bit down synchronous counter

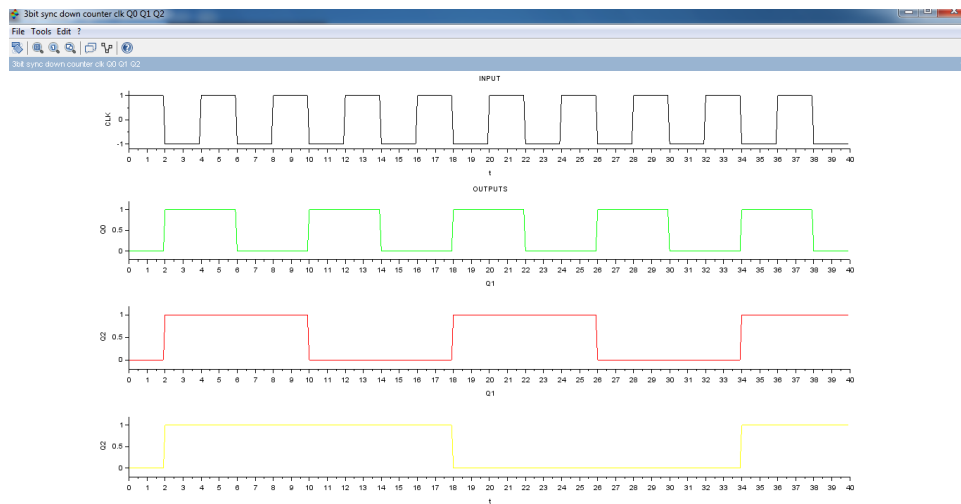


Figure 11.4: Three bit down synchronous counter

Experiment: 12

Code Converter Design (eg.binary to gray code conversion) & Implementation in Xcos

This code can be downloaded from the website www.scilab.in

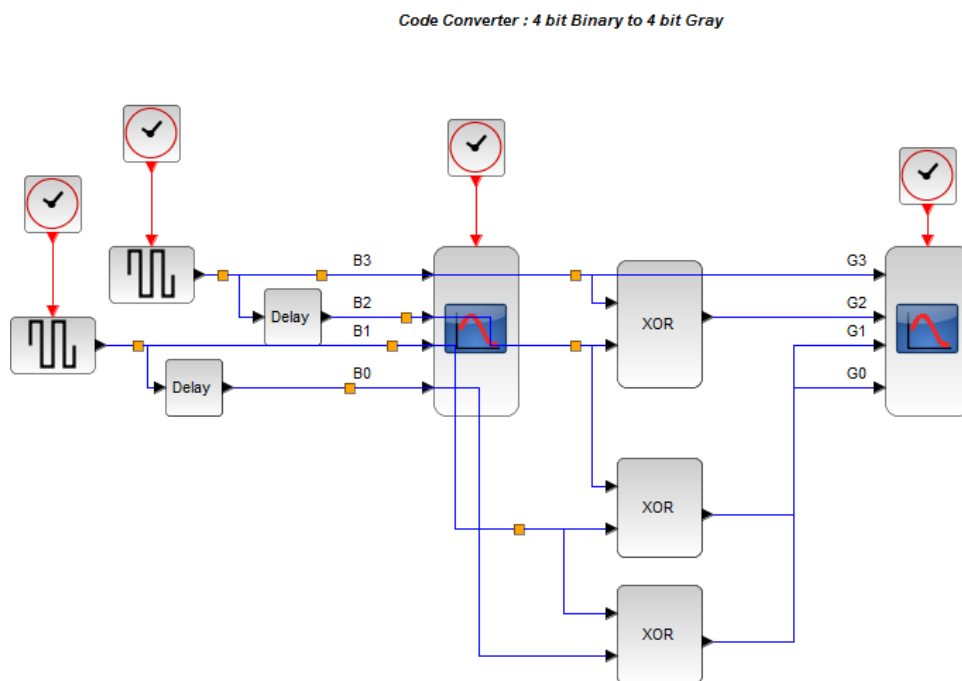


Figure 12.1: Binary to Gray code converter

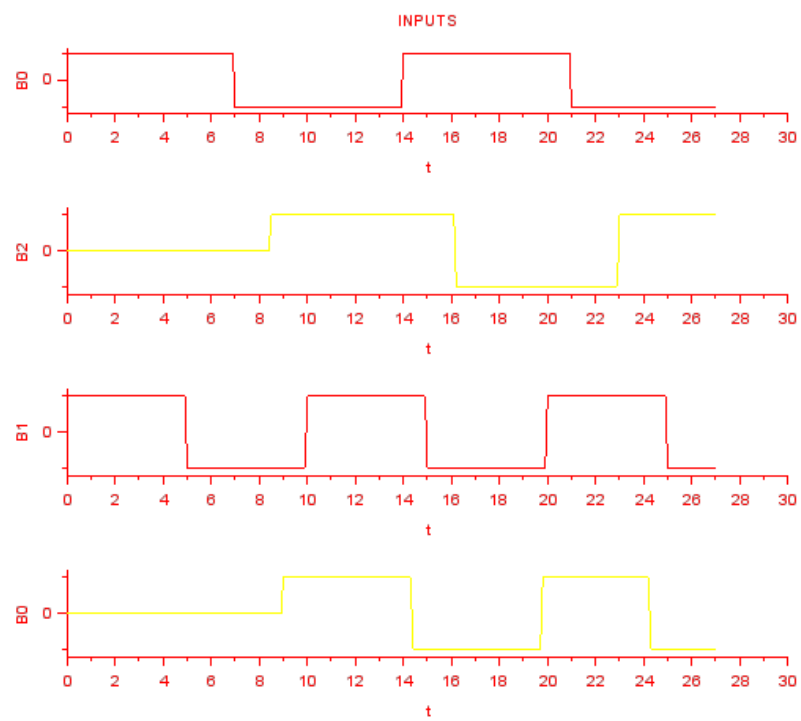


Figure 12.2: Binary to Gray code converter

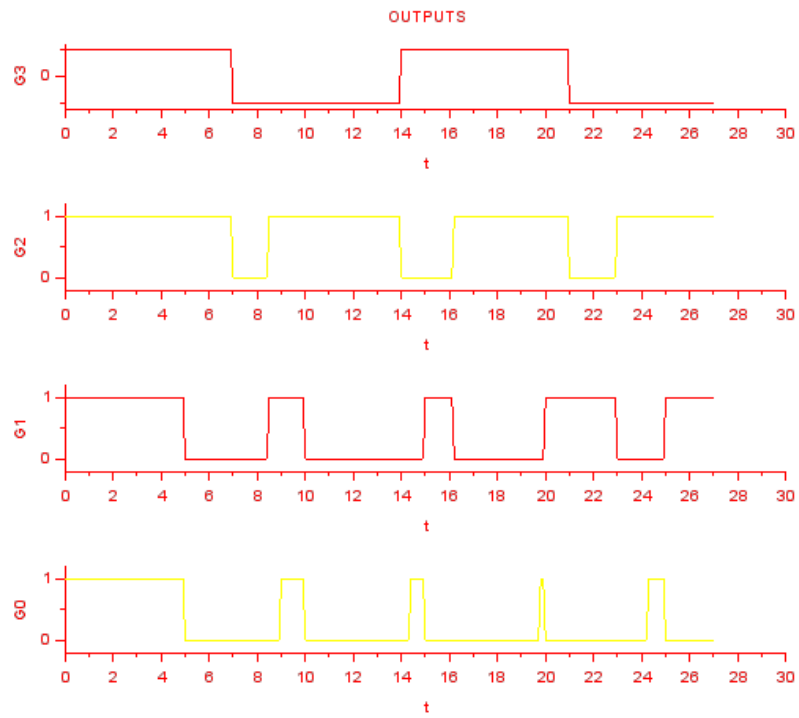


Figure 12.3: Binary to Gray code converter

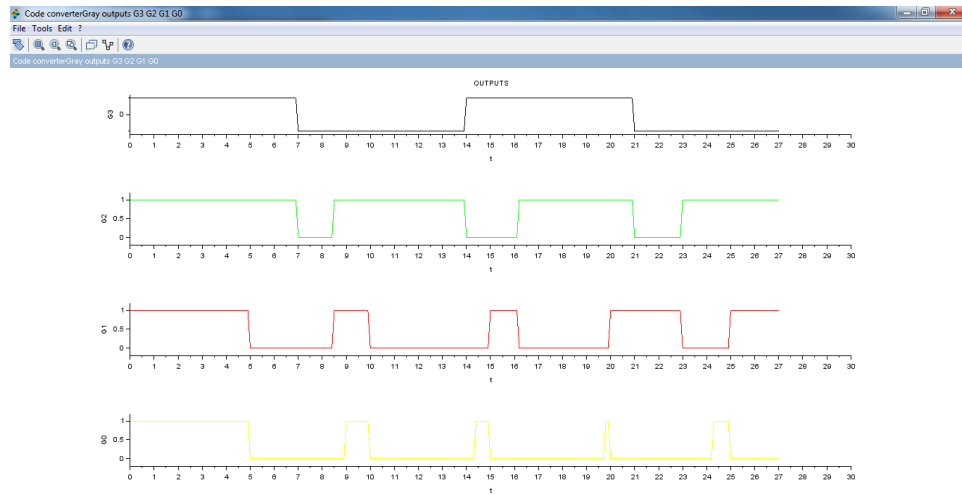


Figure 12.4: Binary to Gray code converter