

Scilab Textbook Companion for
Basic Electronics
by S. Biswas¹

Created by
Yagnesh Kamleshkumar Badiyani
B.Tech.
Electronics Engineering
Dharmsinh Desai University
College Teacher
None
Cross-Checked by
None

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Basic Electronics

Author: S. Biswas

Publisher: Khanna Publishing, New Delhi

Edition: 1

Year: 2000

ISBN: 9788187522164

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Introduction to Electronics	5
2 Fundamental Concepts Energy Bands in Solids	15
3 Semiconductor Diodes and Miscellaneous Devices	22
4 Bipolar Junction Transistor	43
5 Bipolar Transistor Biasing	52
6 Single Stage BJT Amplifiers	72
7 Field Effect Transistors	92
8 Power Amplifiers	112
9 Frequency Response of Amplifiers	123
10 Feedback in Amplifiers	143
11 Oscillators and Multivibrators	154
12 Modulation and Demodulation	160

13 Integrated Circuits	169
14 Operational Amplifiers	171

List of Scilab Codes

Exa 1.1	Colour coding of resistors	5
Exa 1.2	Colour coding of resistors	6
Exa 1.3	Colour coding of resistors	7
Exa 1.4	Calculation of Parallel Plate Capacitance . .	7
Exa 1.6	Colour coding of Tantalum Capacitors . . .	8
Exa 1.7	Calculation of Output Voltage of an Amplifier equivalent circuit	9
Exa 1.8	Calculation of maximum current capacity . .	10
Exa 1.9	Calculation of Power in a Resistor	10
Exa 1.10	Calculation of Current rating of Resistor . .	11
Exa 1.11	Calculation of Current rating of Resistor . .	11
Exa 1.12	Potentiometer for Motor Speed Control . . .	12
Exa 2.1	KE PE and Total Energy of Electron	15
Exa 2.2	Total electrons in K L M shells	16
Exa 2.3	Calculation of KE and velocity of electron . .	17
Exa 2.4	Calculation of KE and velocity of positively charged particle	18
Exa 2.5	Calculation of mass of electron	19
Exa 2.6	Determination of Balmer series for hydrogen atom	20
Exa 3.1	Calculation of output voltage for half wave transformer rectifier	22
Exa 3.2	Calculation of important quantities for half wave rectifier	23
Exa 3.3	Calculation of important quantities for center tapped full wave rectifier	24
Exa 3.4	Calculation of capacitance for half wave rec- tifier with shunt capacitance filter	26

Exa 3.5	Calculation of output power in filter capacitor connected full wave rectifier	26
Exa 3.6	Calculation of ripple factor for full wave rectifier	27
Exa 3.7	Calculation of capacitance for full wave rectifier with shunt capacitance filter	28
Exa 3.8	Calculation of turns ratio of a full wave rectifier with transformer	29
Exa 3.9	Calculation of output voltages and regulation for a bridge rectifier	30
Exa 3.10	Calculation of V_z for zener diode at given temperature	31
Exa 3.11	Determination of bias for a zener diode . . .	32
Exa 3.12	Determination of bias for a zener diode and calculating power dissipation	32
Exa 3.13	Determination of bias for a zener diode and calculating power dissipation and I_z	33
Exa 3.14	Calculation of output voltage for given zener circuit	34
Exa 3.15	Calculation of all branch currents for given zener circuit	35
Exa 3.16	Calculation of zener current for different load resistances	37
Exa 3.17	Calculation of resistor for construction a power supply and current when the supply voltage changes	38
Exa 3.18	Design of a zener voltage regulator	39
Exa 3.19	Calculation of range of voltage for zener diode to be on	40
Exa 3.20	Calculation of series resistance and dark current for given relay circuit	41
Exa 4.1	Calculation of CE and CB current gains . .	43
Exa 4.2	Calculation of CB current gain and collector current	44
Exa 4.3	Calculation of CE current gain and base current	44
Exa 4.4	Determination of whether transistor is saturated	45

Exa 4.5	Determination of whether transistor is saturated	46
Exa 4.6	Calculation of voltage gain and output voltage for given amplifier figure	47
Exa 4.7	Calculation of input and output impedance and current and voltage gain at given load .	48
Exa 4.8	Calculation of input impedance and current and voltage gain at given load	49
Exa 4.9	Determination of CE hybrid model and CB re model	50
Exa 5.1	Calculation of quantities for Q point for given figure	52
Exa 5.2	Calculation of saturation current for given figure	53
Exa 5.3	Calculation of V_{cc} and given resistances for the load line and Q point given	54
Exa 5.4	Calculation of parameters for emitter biased circuit	55
Exa 5.5	Calculation of Q point for given dc bias circuit	56
Exa 5.6	Calculation of stability factors for given circuit	58
Exa 5.7	Calculation of Q point for given circuit . . .	59
Exa 5.8	Calculation of Q point for given circuit and given beta	60
Exa 5.9	Calculation of dc level of I_B and V_C for given circuit	61
Exa 5.10	Design of a bias circuit for amplifier for given current I_E	62
Exa 5.11	Calculation of stability factor for collector to base bias circuit	63
Exa 5.12	Calculation of stability factor for given circuit and load	64
Exa 5.13	Calculation of stability factors for given circuit and parameters	64
Exa 5.14	Calculation of Q point for given circuit . . .	65
Exa 5.15	Calculation of Q point for given circuit and given beta	66
Exa 5.16	Calculation of Q point and stability factors for given circuit and parameters	67

Exa 5.17	Calculation of unknown resistances for the given circuit and parameters	68
Exa 5.18	Calculation of given parameters for circuit and stated parameters	69
Exa 6.1	Plot of DC and AC load lines for given circuit	72
Exa 6.2	DC and AC analysis of given circuit	73
Exa 6.3	Calculation of base voltage for given circuit parameters	75
Exa 6.4	Calculation of base to collector gain for given conditions of RE	76
Exa 6.5	Calculations of specific gains for given circuit parameters	77
Exa 6.6	Calculation of output voltage for given circuit	79
Exa 6.7	Calculation of output voltage for given value of load resistances	81
Exa 6.8	Calculation of current gain and power gain for given circuit	83
Exa 6.9	Calculations of specific gains and impedances for given CC amplifier	85
Exa 6.10	Calculations of specific gains and impedances for given CB amplifier	86
Exa 6.11	Calculation of current gain for a superbeta transistor	87
Exa 6.12	Calculation dc bias voltages and currents for given circuits	88
Exa 6.13	Calculation of input impedances for given circuit	89
Exa 6.14	Calculation of base current and ac current gain for given circuit	89
Exa 6.15	Calculation of ac output impedances and voltage gain for given circuit	90
Exa 7.1	Calculation of drain current for given circuit specifications	92
Exa 7.2	Calculation of drain current and transconductance for given circuit specifications	93
Exa 7.3	Calculation of drain current and transconductances for given circuit specifications	94

Exa 7.4	Calculation of drain current for given circuit specifications	95
Exa 7.5	Calculation of circuit parameters for given circuit	95
Exa 7.6	Calculation of circuit parameters for given circuit	97
Exa 7.7	Calculation of circuit parameters for given circuit	98
Exa 7.8	Calculation of circuit parameters for given circuit	100
Exa 7.9	Calculation of voltage gain for given circuit parameters	101
Exa 7.10	Calculation of voltage gain for given circuit parameters	102
Exa 7.11	Calculation of voltage gain for given circuit parameters	102
Exa 7.12	Calculation of voltage gain for given circuit parameters	103
Exa 7.13	Calculation of circuit parameters for given circuit	103
Exa 7.14	Calculation of drain current for given circuit specifications	106
Exa 7.15	Determination of n channel or p channel D MOSFET using circuit specifications	107
Exa 7.16	Calculation of VGS and VDS for given circuit parameters	108
Exa 7.17	Calculation of VDS for given D MOSFET circuit parameters	109
Exa 7.18	Calculation of VDS for given E MOSFET circuit parameters	109
Exa 7.19	Calculation of VDS for given circuit parameters	110
Exa 8.1	Calculation of maximum collector current for given VCC and PD	112
Exa 8.2	Calculation of ac output voltage and current for given circuit	112
Exa 8.3	Calculation of effective resistance at primary of transformer	113

Exa 8.4	Calculation of turns ratio of a transformer for given parameters	114
Exa 8.5	Calculation of power parameters and efficiency of transistor	114
Exa 8.6	Calculation of maximum load power of amplifier	116
Exa 8.7	Calculation of input and output powers and efficiency for given amplifier circuit	117
Exa 8.8	Calculation of harmonic distortion and increase in power due to it for an amplifier	118
Exa 8.9	Calculation of output power for given amplifier circuit	119
Exa 8.10	Calculation of maximum efficiency for an inductor coupled amplifier	119
Exa 8.11	Calculation of maximum load power of amplifier for given VCC and RL	120
Exa 8.12	Calculation of turns ratio of a transformer for given parameters	120
Exa 8.13	Calculation of supplied and collector dissipated power for an amplifier	121
Exa 8.14	Calculation of efficiency of complementary symmetry amplifier for given parameters	122
Exa 9.1	Calculation of voltage and power gains in dB units	123
Exa 9.2	Calculation of input and output miller capacitances for given amplifier circuit	125
Exa 9.3	Calculation of input and output miller capacitances for given amplifier circuit	126
Exa 9.4	Calculation of gain magnitude from dB units	126
Exa 9.5	Calculation of input voltage and power required for given amplifier parameters	127
Exa 9.6	Calculation of critical frequency for a given bypass network	128
Exa 9.7	Calculation of corner frequency for a given bypass network	129
Exa 9.8	Plot of total frequency response for given amplifier	130

Exa 9.9	Design of input RC network and calculation of cutoff frequency for a given amplifier . . .	131
Exa 9.10	Calculation of phase shift of input RC network of a given amplifier	133
Exa 9.11	Design of output RC network and calculation of critical frequency for a given amplifier . .	134
Exa 9.12	Calculation of bandwidth of an amplifier for given cutoff frequencies	135
Exa 9.13	Calculation of bandwidth of an amplifier for given transition frequency and midband gain	136
Exa 9.14	Determination of cutoff frequency for given input RC network	137
Exa 9.15	Determination of cutoff frequency for given output RC network	137
Exa 9.16	Calculation of C_{gd} C_{ds} and C_{gs} for 2N3796 using datasheet values	138
Exa 9.17	Design of input RC network and calculation of cutoff frequency for a given amplifier . . .	139
Exa 9.18	Design of input RC network and calculation of cutoff frequency for a given amplifier . . .	140
Exa 9.19	Design of output RC network and calculation of cutoff frequency for a given amplifier . . .	141
Exa 10.1	Calculation of closed loop gain and feedback factor for given amplifier	143
Exa 10.2	Calculation of feedback parameters and output voltage for given amplifier	143
Exa 10.3	Calculation of variation in closed loop gain with variation in open loop gain	144
Exa 10.4	Calculation of variation in closed loop gain with variation in open loop gain	145
Exa 10.5	Calculation of output voltage and distortion voltage for given closed loop amplifier	146
Exa 10.6	Calculation of first stage gain and second harmonic distortion for a closed loop amplifier .	147
Exa 10.7	Calculation of bandwidth after introduction of feedback in an amplifier	147
Exa 10.8	Calculation of open and closed loop gain for given FET amplifier	148

Exa 10.9	Calculation of open and closed loop gain for given amplifier circuit	149
Exa 10.10	Calculation of open and closed loop gain for given amplifier circuit	150
Exa 10.11	Calculation of closed loop gain for given amplifier circuit	150
Exa 10.12	Calculation of closed loop gain and feedback transfer ratio for given amplifier	151
Exa 10.13	Calculation of lower cutoff frequency after introduction of negative feedback in an amplifier	152
Exa 10.14	Calculation of upper cutoff frequency after introduction of negative feedback in an amplifier	152
Exa 11.1	Calculation of frequency of oscillations for Colpitts oscillator	154
Exa 11.2	Calculation of frequency of oscillations for given circuit and Q values	155
Exa 11.3	Calculation of Q value for a crystal oscillator with given parameters	156
Exa 11.4	Calculation of frequency of oscillations for given oscillator circuit	156
Exa 11.5	Calculation of oscillation frequency and feedback resistance for given OPAMP oscillator	157
Exa 11.6	Calculation of oscillation frequency for Wien Bridge oscillator	158
Exa 11.7	Calculation of oscillation frequency for astable multivibrator with given parameters	159
Exa 12.1	Calculation of percentage modulation and amplitude of carrier wave for given AM wave	160
Exa 12.2	Calculations of sideband parameters and width for given AM wave	161
Exa 12.3	Calculation of power developed by AM wave	162
Exa 12.4	Calculation of the modulation index and side lengths ratio for given trapezoidal pattern AM wave	162
Exa 12.6	Plot of frequency spectrum and calculation of modulation index for AM wave	163
Exa 12.7	Calculation of the modulation index for given transmitter currents	164

Exa 12.8	Calculation of required audio power for given AM signal	165
Exa 12.9	Calculation of maximum carrier power for given transmission of AM wave	165
Exa 12.10	Calculation of modulation index for given FM transmission	166
Exa 12.11	Calculation of bandwidth for given FM wave transmission	167
Exa 12.12	Calculation of average power output for a FM signal	167
Exa 13.1	Design of diffused resistors of given value . .	169
Exa 14.1	Calculation of output voltage for a balanced differential amplifier	171
Exa 14.2	Calculation of input and output common mode voltage for given balanced differential amplifier	172
Exa 14.3	Calculation of output common mode voltage for given balanced differential amplifier . . .	173
Exa 14.4	Calculation of common mode gain for a balanced differential amplifier	174
Exa 14.5	Calculation of CMRR in dB units for given operational amplifier	174
Exa 14.6	Calculation of slew rate for given operational amplifier	175
Exa 14.7	Calculation of feedback resistance for given opamp closed loop amplifier	176
Exa 14.8	Calculation of input and output impedances for given operational amplifier	176
Exa 14.9	Calculation of closed loop voltage gain and input and output impedances for given operational amplifier	177
Exa 14.10	Calculation of input and output impedances for given operational amplifier voltage follower	178
Exa 14.11	Calculation of oscillation frequency and feedback resistance for given phase shift oscillator	179
Exa 14.13	Calculation of output voltage for given conditions in a summer circuit	179
Exa 14.14	Calculation of output voltage for given conditions in a summer circuit	180

Chapter 1

Introduction to Electronics

Scilab code Exa 1.1 Colour coding of resistors

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 8
3 clear;
4 clc;
5
6 //Given Data
7
8 //Colour coding of four band resistor
9 //Given Sequence: [Gray Red Red Gold]
10 gray=8;
11 red=2;
12 gold=0.05;
13
14 //Solution
15
16 R=(gray*10+red)*(10^(red)); //Base resistance in ohms
17 R_min=R*(1-0.05); //Least possible resistance in ohms
    using variance
18 R_max=R*(1+0.05); //Most possible resistance in ohms
    using variance
19
```

```

20 printf("Resistance should be in between %d ohms and
    %d ohms",R_min,R_max);
21 //Error in textbook as 5% of 8200 is 410 and not 41

```

Scilab code Exa 1.2 Colour coding of resistors

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 9
3 clear;
4 clc;
5
6 //Given Data
7
8 //Colour coding of four band resistor
9 //Given Sequence: [Orange Orange Yellow Silver]
10 orange=3;
11 yellow=4;
12 silver=0.1;
13
14 //Solution
15
16 R=(orange*10+orange)*(10^(yellow)); //Base resistance
    in ohms
17 R_min=R*(1-silver); //Least possible resistance in
    ohms using variance
18 R_max=R*(1+silver); //Most possible resistance in
    ohms using variance
19
20 printf("Resistance should be in between %d ohms and
    %d ohms",R_min,R_max);
21 //Error in textbook as 330K is not 33000 and is
    330000

```

Scilab code Exa 1.3 Colour coding of resistors

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 9
3 clear;
4 clc;
5
6 //Given Data
7
8 //Colour coding of five band resistor
9 //Given Sequence: [Yellow Gray Violet Black Green]
10 yellow=4;
11 gray=8;
12 violet=7;
13 black=0;
14 green=0.005;
15
16 //Solution
17
18 R=(yellow*100+gray*10+violet)*(10^(black)); //Base
    resistance in ohms
19 R_min=R*(1-green); //Least possible resistance in
    ohms using variance
20 R_max=R*(1+green); //Most possible resistance in ohms
    using variance
21
22 printf("Resistance should be in between %.2f ohms
    and %.2f ohms",R_min,R_max); //Upto 2 decimal
    points
23 //Decimal approximation error w.r.t. textbook
```

Scilab code Exa 1.4 Calculation of Parallel Plate Capacitance

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 12
```

```

3  clear;
4  clc;
5
6  //Given Data
7
8  area=1; //meter squares
9  d=0.25; //distance between plates in centimeters
10 e=8.85D-12; //permittivity of air
11
12 //Solution
13
14 d=d*10^-2; //converting distance into meters
15 C=e*area/d; //Capacitance in Farads
16 C=C*10^12; //Coverting capacitance to pF from F
17 printf("C= %d pF\n",C);
18 printf("The capacitor can thus store a charge of %d
    *10^-12 C with 1 Volt.",C);

```

Scilab code Exa 1.6 Colour coding of Tantalum Capacitors

```

1  //Tested on Windows 7 Ultimate 32-bit
2  //Chapter 1 Introduction to Electronics Pg no. 17
3  clear;
4  clc;
5
6  //Given Data
7  //Fig. 1.16
8
9  //Solution
10 blue=6;
11 gray=8;
12 violet=50;
13 gold=0.05;
14
15 C=(blue*10+gray)*10^blue*10^-12; //Capacitance in

```

```

        Farads
16 C=C*10^6; // Converting from Farads to micro Farads
17
18 printf("The value of capacitance is %d uF \n and
        voltage rating is %d volts and tolerance of %d
        percent.",C,violet,gold*100);

```

Scilab code Exa 1.7 Calculation of Output Voltage of an Amplifier equivalent circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 29
3 clear;
4 clc;
5
6 //Given Data
7 //Fig 1.33
8 vi=6D-3; //input volatage in volts
9 Rin=1200; //input resistance in ohms
10 Ai=100; //current gain
11 Ro=25000; //output resistance in ohms
12 Rl=1000; //load impedance
13
14 //Solution
15
16 is=vi/Rin; //Input current
17 i2=Ai*is; //Output circuit current source value
18 iL=i2*(Ro/(Ro+Rl)); //Current divider to find load
        current
19 Vout=iL*Rl;
20
21 printf("The output voltage is Vout=%0.2f V",Vout); //
        Displaying upto 2 places of decimal

```

Scilab code Exa 1.8 Calculation of maximum current capacity

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 33
3 //Solved Problem 1
4 clear;
5 clc;
6
7 //Given Data
8
9 wattage=100; //wattage in watts
10 voltage=220; //voltage in volts
11
12 //Solution
13
14 I=wattage/voltage; //current in amperes
15
16 printf(" I=%0.3 f Amp. ",I); //Displaying upto 3 places
    of decimal
17 //Error due to decimal approximations
```

Scilab code Exa 1.9 Calculation of Power in a Resistor

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 33
3 //Solved Problem 2
4 clear;
5 clc;
6
7 //Given Data
8
9 I=6; //current in amperes
10 R=36; //resistance in ohms
11
12 //Solution
```

```

13
14 P=I^2*R; //power in watts
15
16 printf("P=%d W.",P);

```

Scilab code Exa 1.10 Calculation of Current rating of Resistor

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 33
3 //Solved Problem 3
4 clear;
5 clc;
6
7 //Given Data
8
9 R=120; //resistance in ohms
10 P=1000; //power in watts
11
12 //Solution
13
14 I=sqrt(P/R); //current in amperes
15
16 printf("I=%0.2f Amperes.",I); //Displaying upto 2
    places of decimal

```

Scilab code Exa 1.11 Calculation of Current rating of Resistor

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 33
3 //Solved Problem 4
4 clear;
5 clc;
6

```

```

7 //Given Data
8
9 R=10;//resistance in ohms
10 P=4;//power in watts
11
12 //Solution
13
14 I=sqrt(P/R);//current in amperes
15
16 printf("Maximum safe current is I=%.3f Amperes.",I);
    //Displaying upto 3 places of decimal

```

Scilab code Exa 1.12 Potentiometer for Motor Speed Control

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 1 Introduction to Electronics Pg no. 33
   and 34
3 //Solved Problem 5
4 clear;
5 clc;
6
7 //Given Data
8 //Figure 1.34
9
10 Rm=2;//resistance of motor in ohms
11 V=10;//battery voltage in volts
12 Rpot=10;//maximum resistance of potentiometer in
    ohms
13 Ppot=100;//maximum power rating of potentiometer in
    watts
14
15 //Solution
16
17 Ipot=sqrt(Ppot/(Rpot+Rm));//maximum safe current
    possible through potentiometer in amperes

```

```

18 printf("Current rating of potentiometer I = %.2f
    Amps\n\n",Ipot);
19
20 Rp=10;//Resistance of potentiometer set in ohms
21 I10=V/(Rp+Rm);//Current for corresponding resistance
    of potentiometer
22
23 printf("When the potentiometer is set to %d Ohms,\
    nthe total resistance of the circuit is %d ohms.\
    n",Rp,Rp+Rm);
24 printf("I = %.1f Amps\n",I10);
25
26 if(I10<Ipot)
27     printf("\nThe amount of current is less than %.2
        f Amps and the potentiometer is safe.\n\n",
        Ipot);
28 end
29
30
31 Rp=2;//Resistance of potentiometer set in ohms
32 I2=V/(Rp+Rm);//Current for corresponding resistance
    of potentiometer
33
34 printf("When the potentiometer is set to %d Ohms,\
    nthe total resistance of the circuit is %d ohms\n
    ",Rp,Rp+Rm);
35 printf("I = %.1f Amps\n",I2);
36
37 if(I10<Ipot)
38     printf("\nThe amount of current is less than %.2
        f Amps and the potentiometer is safe \n",Ipot
        );
39 end
40
41 Rp=1;//Resistance of potentiometer set in ohms
42 I3=V/(Rp+Rm);//Current for corresponding resistance
    of potentiometer
43

```

```
44 printf("\n However when potentiometer resistance is
%d ohms, I= %d/%d = %.1f Amp.\nThis is greater
than %.2f Amperes.\nThe potentiometer wire will
get heated and temperature will rise.\nFor still
lower values of potentiometer setting,\nI will be
still higher and the potentiometer will be
damaged.\nIt may even burn out.",Rp,V,(Rp+Rm),I3,
Ipot)
```

Chapter 2

Fundamental Concepts Energy Bands in Solids

Scilab code Exa 2.1 KE PE and Total Energy of Electron

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 2 Fundamental Concepts: Energy Bands in
   Solids Pg no. 49
3 clear;
4 clc;
5
6 //Given Data
7 m0=9.1D-31;//mass of electron in kg
8 e=1.602D-19;//charge on a electron in Coulombs
9 e0=8.854D-12;//electric permittivity of air
10 h=6.625D-34;//planck's constant in Joules-sec
11 n=2;//index of the Bohr orbit
12
13 //Solution
14
15 KE=(m0*e^4)/(8*e0^2*n^2*h^2);//Kinetic Energy of
   electron in Joules
16 KE=KE/(1.6D-19);//Converting it into electron volts
   eV
```

```

17
18 PE=-(m0*e^4)/(4*e0^2*n^2*h^2); //Potential Energy of
    electron in Joules
19 PE=PE/(1.6D-19); //Converting it into electron volts
    eV
20
21 TE=KE+PE; //Total energy is the sum of kinetic and
    potential energy of electron
22
23 printf("Kinetic Energy=%0.1f eV \n Potential Energy=%
    .1f eV \n Total Energy=%0.1f eV",KE,PE,TE);

```

Scilab code Exa 2.2 Total electrons in K L M shells

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 2 Fundamental Concepts: Energy Bands in
    Solids Pg no. 49
3 clear;
4 clc;
5
6 printf("According to Paulis principle no two
    electrons can possess same set of values for four
    quantum numbers.\n\n");
7 printf("Total electrons that can reside in eacvh
    shell is as follows\n");
8 printf("K shell: \n n=1,l=0,m=0,s= 1 /2 \t\t\t 2
    electrons Subshell:1s\n");
9 printf("\t\t\t\t Total:2 electrons\n");
10 printf("L shell: \n n=2,l=0,m=0,s= 1 /2 \t\t\t 2
    electrons Subshell:2s\n");
11 printf(" n=2,l=1,m=-1,0,+1,s= 1 /2 \t\t 6 electrons
    Subshell:2p\n");
12 printf("\t\t\t\t Total:8 electrons\n");
13 printf("M shell: \n n=3,l=0,m=0,s= 1 /2 \t\t\t 2
    electrons Subshell:3s\n");

```

```

14 printf(" n=3,l=1,m=-1,0,+1,s= 1 /2\t\t 6 electrons
    Subshell:3p\n");
15 printf(" n=3,l=2,m=-2,-1,0,+1,+2,s= 1 /2 \t 10
    electrons Subshell:3d\n");
16 printf("\t\t\t\t Total:18 electrons\n");

```

Scilab code Exa 2.3 Calculation of KE and velocity of electron

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 2 Fundamental Concepts: Energy Bands in
    Solids Pg no. 50
3 clear;
4 clc;
5
6 //Given Data
7 m0=9.1D-31;//mass of electron in kg
8 e=1.602D-19;//charge on a electron in Coulombs
9 V1=100;//Accelerating potential difference in volts
    for case (i)
10 V2=500;//Accelerating potential difference in volts
    for case (ii)
11
12 //Solution
13 disp('case (i)')
14
15 KE1=e*V1;//Kinetic Energy of electron in Joules
16 KE2=KE1/(1.6D-19);//Converting it into electron
    volts eV
17 v=sqrt(2*KE1/m0);//Velocity of electron in meters
    per second
18
19 printf("The Kinetic energy for V=%d volts is \n",V1)
    ;
20 printf("K.E.=%0.3e Joules \nK.E.=%d eV\n",KE1,KE2);
21 printf("The corresponding velocity is %0.2e m/sec\n",

```

```

        v);
22
23 disp('case (ii)')
24
25 KE1=e*V2;//Kinetic Energy of electron in Joules
26 KE2=KE1/(1.6D-19);//Converting it into electron
    volts eV
27 v=sqrt(2*KE1/m0);//Velocity of electron in meters
    per second
28
29 printf("The Kinetic energy for V=%d volts is \n",V1)
    ;
30 printf("K.E.=%0.3e Joules \nK.E.=%d eV\n",KE1,KE2);
31 printf("The corresponding velocity is %0.2e m/sec\n",
    v);
32
33 //Decimal errors with respect to textbook due to
    approximations

```

Scilab code Exa 2.4 Calculation of KE and velocity of positively charged particle

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 2 Fundamental Concepts: Energy Bands in
    Solids Pg no. 50
3 clear;
4 clc;
5
6 //Given Data
7 m0=9.1D-31;//mass of electron in kg
8 e=1.602D-19;//charge on a electron in Coulombs
9 V=5000;//Accelerating potential difference in volts
    for case (ii)
10 m=3674*m0;//mass of positively charged particle in
    kg;
11 q=2*e;//charge of positively charged particle in

```

```

        Coulombs;
12
13
14 //Solution
15
16
17 KE1=q*V;//Kinetic Energy of positively charged
    particle in Joules
18 KE2=KE1/(1.6D-19);//Converting it into electron
    volts eV
19
20 v=sqrt(2*KE1/m);//Velocity of positively charged
    particle in meters per second
21 v=v/1000;//Converting it into kilometers per second
22
23 printf("The Kinetic energy is %d eV\n",KE2);
24 printf("The corresponding velocity is %d km/sec\n",v
    );
25
26 //Error in kinetic energy due to approximations of
    decimals in textbook

```

Scilab code Exa 2.5 Calculation of mass of electron

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 2 Fundamental Concepts: Energy Bands in
    Solids Pg no. 50 and 51
3 clear;
4 clc;
5
6 //Given Data
7 m0=9.1D-31;//mass of electron in kg
8 v_to_c_ratio=0.2;
9
10 //Solution

```

```

11
12 m=m0/sqrt(1-v_to_c_ratio^2); //mass of electron in kg
13
14 printf("Mass of electron for v=0.2c is equal to m=%
    .2e kg",m);

```

Scilab code Exa 2.6 Determination of Balmer series for hydrogen atom

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 2 Fundamental Concepts: Energy Bands in
   Solids Pg no. 51
3 clear;
4 clc;
5
6 //Given Data
7
8 n=2; //orbit for Balmer series
9 h=6.625D-34; //planck's constant in Joules-sec
10 c=3D8; //speed of light in meter per second
11
12 //Solution
13
14 for k=3:6
15     hf=-13.6*(1/(k^2)-1/(2^2)); //radiated energy in
        eV
16     hf2=hf*1.6D-19; //converting from eV to Joules
17     f=hf2/h; //frequency of emitted radiation in Hz
18     l=c/f; //wavelength of emitted radiation in
        meters
19     u=1*10^6; //converting wavelength into micro
        meter
20     A=1*10^10; //converting wavelength into angstroms
21
22     printf("n=%d, hf%d2=%0.2 f eV, =%0.3 f m = %d \
        n",k,k,hf,u,A);

```

```

23 end
24
25 hf=-13.6*(0-1/(2^2)); //as k tends to infinity 1/k
    tends to zero
26 hf2=hf*1.6D-19; //converting from eV to Joules
27 f=hf2/h; //frequency of emitted radiation in Hz
28 l=c/f; //wavelength of emitted radiation in meters
29 u=1*10^6; //converting wavelength into micro meter
30 A=1*10^10; //converting wavelength into angstroms
31
32 printf("n=      , h f 2 =%.2 f eV,  =%.3 f m  = %d
    \n",hf,u,A);
33
34
35 //Errors with respect to book due to decimal
    approximations

```

Chapter 3

Semiconductor Diodes and Miscellaneous Devices

Scilab code Exa 3.1 Calculation of output voltage for half wave transformer rectifier

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 71
3 clear;
4 clc;
5
6 //Given Data
7
8 //Figure 3.14
9 e1=4; //Relative emf of primary side
10 e2=1; //Relative emf of secondary side
11 vinp=220; //Input peak voltage in volts
12 Vd=0.7; //Forward voltage drop of diode
13
14 //Solution
15
16 tr=e2/e1; //turns ratio n2/n1
17 V2=tr*vinp; //as v2/v1=n2/n1
18 Voutp=V2-Vd; //Vout across Rl in volts
```

```

19
20 printf("The peak value of rectified output voltage
    is :\n(Vout)peak=%0.1 f V",Voutp);

```

Scilab code Exa 3.2 Calculation of important quantities for half wave rectifier

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
  Devices Pg no. 89
3 clear;
4 clc;
5
6 //Given Data
7
8 r=1.0;//Diode resistance in ohms
9 Rl=100;//Load resistance in ohms
10 Ep=30;//Input supply voltage in volts peak
11
12 //Solution
13
14 disp(" (a) ");
15 Ip=Ep/(Rl+r)*1000;//peak current in milli-amperes
16 Irms=Ip/sqrt(2);//rms current in milli-amperes
17 Iavg=Ip/%pi;//average or d.c. value of current in in
    milli-amperes
18
19 printf("The peak value of current = Ip=%0d mA\n",Ip);
20 printf("The rms value of current = Irms=%0.1 f mA\n",
    Irms);
21 printf("The average or d.c. value of current = Iav=%
    .1 f mA\n",Iavg);
22
23 disp(" (b) ");
24 Pdc=(Iavg/1000)^2*Rl//d.c. output power in watts
25

```

```

26 printf("The d.c. output power = Pdc=%0.3f watts\n",
    Pdc);
27
28 disp("(c)");
29 Pac=(Irms/1000)^2*(Rl+r); //input ac power in watts
30
31 printf("The a.c. input power = Pin=%0.2f watts\n",Pac
    );
32
33 disp("(d)");
34 n=Pdc/Pac; //Rectification efficiency is output dc
    power over input ac power
35
36 printf("Rectification efficiency= %d percentage",n
    *100);
37
38
39 //Error in textbook as Irms=Ip/sqrt(2) and not Ip/2

```

Scilab code Exa 3.3 Calculation of important quantities for center tapped full wave

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
    Devices Pg no. 89
3 clear;
4 clc;
5
6 //Given Data
7
8 Rl=470; //Load resistance in ohms
9 r=2; //Diodes dynamic resistance in ohms
10 esp=50; //Input signal voltage magnitude in volts
    peak
11 esf=314/(2*%pi); //Input signal frequency in hertz
12

```

```

13 //Solution
14
15 disp(" (a) ");
16 Ep=esp*sqrt(2); //peak voltage in volts
17 Ip=Ep/(Rl+r)*1000; //peak current in amperes
18
19 printf("The peak value of current = Ip=%0.1f mA\n",Ip
    *1000);
20
21 disp(" (b) ");
22 Iavg=2*Ip/%pi; //average or d.c. value of current in
    in milli-amperes
23
24 printf("The average or d.c. value of current = Iav=%
    .2f mA\n",Iavg);
25
26 disp(" (c) ");
27 Irms=Ip/sqrt(2); //rms current in milli-amperes
28
29 printf("The rms value of current = Irms=%0.2f mA\n",
    Irms);
30
31 disp(" (d) ");
32 RF=sqrt((Irms/Iavg)^2-1); //ripple factor
33
34 printf("The ripple factor = RF=%0.4f\n",RF);
35
36 disp(" (e) ");
37 Pdc=(Iavg/1000)^2*Rl //d.c. output power in watts
38 Pac=(Irms/1000)^2*(Rl+r); //input ac power in watts
39 n=Pdc/Pac; //Rectification efficiency is output dc
    power over input ac power
40
41 printf("Rectification efficiency= %0.2f percentage",n
    *100);
42
43 //Efficiency calculation error in textbook and also
    decimal errors due to approximations

```

Scilab code Exa 3.4 Calculation of capacitance for half wave rectifier with shunt

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 90
3 clear;
4 clc;
5
6 //Given Data
7
8 Rl=2D3;//Load resistance in ohms
9 esp=50;//Input signal voltage magnitude in volts
   peak
10 esf=314/(2*%pi);//Input signal frequency in hertz
11 Vr_to_Vdc=6/100;//Ratio of peak to peak ripple
   voltage to d.c. output voltage
12
13 //Solution
14
15 //Using figure E3.4
16 //From right angled triangle pqr
17
18 C=1/(esf*Rl*Vr_to_Vdc)*10^6;//Capacitance in micro
   faraday;
19
20 printf("The size of filter capacitor is C = %.1f F
   ",C);
21
22 //Decimal errors in textbook due to approximations
```

Scilab code Exa 3.5 Calculation of output power in filter capacitor connected full

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 90 and 91
3 clear;
4 clc;
5
6 //Given Data
7 //Taken as in Example 3.4
8 esp=50; //Input signal voltage magnitude in volts
   peak
9 esf=314/(2*pi); //Input signal frequency in hertz
10 Vr_to_Vdc=6/100; //Ratio of peak to peak ripple
   voltage to d.c. output voltage
11
12 //Solution
13
14 //Using figure E3.5
15
16 e0av=esp*(1-Vr_to_Vdc/2); //average value of d.c.
   output voltage in volts
17 printf("The average value of d.c. output voltage
   e0av = %.1f Volts",e0av);

```

Scilab code Exa 3.6 Calculation of ripple factor for full wave rectifier

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 91
3 clear;
4 clc;
5
6 //Given Data
7
8 Rl=1D3; //Load resistance in ohms
9 esf=50; //Input signal frequency in hertz

```

```

10 RF=4/100; //Ripple Factor
11
12 //Solution
13
14 //Using figure E3.6
15 //From right angled triangle pqr
16
17 C=1/(esf*Rl*2*RF)*10^6; //Capacitance in micro
    faraday;
18
19 printf("The size of filter capacitor is C = %d F ",
    C);
20
21 //Error in textbook as ripple factor is already
    given and capacitance is calculated

```

Scilab code Exa 3.7 Calculation of capacitance for full wave rectifier with shunt

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
    Devices Pg no. 91
3 clear;
4 clc;
5
6 //Given Data
7
8 Rl=200; //Load resistance in ohms
9 esf=50; //Input signal frequency in hertz
10 RF=5/100; //Ripple Factor
11
12 //Solution
13
14 C=1/(esf*Rl*2*RF)*10^6; //Capacitance in micro
    faraday;
15

```

```
16 printf("The size of shunt capacitor is C = %d F ",C
    );
```

Scilab code Exa 3.8 Calculation of turns ratio of a full wave rectifier with trans

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 91 and 92
3 clear;
4 clc;
5
6 //Given Data
7
8 Rl=220; //Load resistance in ohms
9 r=4; //Diodes dynamic resistance in ohms
10 esp=50*sqrt(2); //Input signal voltage magnitude in
    volts peak
11 esf=314/(2*%pi); //Input signal frequency in hertz
12 Vdc=30; //output dc voltage in volts
13
14 //Solution
15
16 ne0dc=2*esp/%pi; //output dc voltage multiplied by
    turns ratio
17 i0dc=30/(2/%pi)/220; //output dc current
18 Vd=r*i0dc; //voltage across conducting diode
19 eout=i0dc*Rl; //output voltage across Rl
20 e0dc=(eout+Vd)*2/%pi; //output dc voltage of
    transformer
21 n=ne0dc/e0dc; //transformer ratio
22 printf("The transformer turns ratio = n = %.3f",n);
23
24 //Error in decimal places in textbook due to
    approximations
```

Scilab code Exa 3.9 Calculation of output voltages and regulation for a bridge rectifier

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 92 and 93
3 clear;
4 clc;
5
6 //Given Data
7
8 Rl=1500; //Load resistance in ohms
9 Rf=10; //Diodes dynamic resistance in ohms
10 esp=110*sqrt(2); //Input signal voltage magnitude in
   volts peak
11 esf=314/(2*%pi); //Input signal frequency in hertz
12
13 //Solution
14
15 disp("(a)");
16 Ip=esp/(Rl+2*Rf)*1000; //peak output current in milli-
   -ampere
17 I0av=2*Ip/%pi; //average value of output current in
   milli-ampere
18 E0av=I0av*Rl/1000; //DC load voltage in volts
19
20 printf("DC load voltage (E0)dc = %.2f Volts",E0av);
21
22 disp("(b)");
23 I0rms=Ip/sqrt(2); //rms output current in milli-
   ampere
24 Vr=sqrt((I0rms/1000)^2-(I0av/1000)^2)*Rl; //output
   ripple voltage in volts
25
26 printf("Output ripple voltage Vr = %.1f Volts",Vr);
```

```

27
28 disp("(c)");
29 pr=2*Rf/Rl*100;//Percentage Regulation of voltage
30
31 printf("The percentage regulation is = %.2f
    percentage",pr);
32
33 //Error in textbook in calculation of average
    current

```

Scilab code Exa 3.10 Calculation of Vz for zener diode at given temperature

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
    Devices Pg no. 95
3 clear;
4 clc;
5
6 //Given Data
7
8 Pz=0.5;//power dissipation of zener diode in watts
9 Vz=12;//zener breakdown voltage in volts
10 Tr=25;//reference temperature in degree celsius
11 T=90;//given temperature in degree celcius
12 Tc=0.075/100;//Temperature co-efficient in degree
    celcius inverse
13
14 //Solution
15
16 dVz=Vz*Tc*(T-Tr);//Change in Vz in volts
17 Vz90=Vz+dVz;//Zener voltage at T=90 degree celsius
18
19 printf("The value of Vz at T=90 C Vz=%.2f Volts",
    Vz90);

```

Scilab code Exa 3.11 Determination of bias for a zener diode

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 96
3 clear;
4 clc;
5
6 //Given Data
7 //From Figure 3.27
8
9 V=15; //value of voltage source in volts
10 Vz=12; //zener breakdown voltage in volts
11 R=390; //series resistance in ohms
12 Izmax=10; //maximum zener current in milli-amperes
13
14 //Solution
15
16 //Assuming ideal diode Vz=12V and Rz=0 ohms
17 Vr=V-Vz; //voltage across resistor in volts
18 Iz=Vr/R*1000; //current through circuit in milli-
   amperes
19 printf("Iz max=%d mA\n Iz=%0.2 f mA\n",Izmax,Iz);
20
21 if Iz<Izmax then
22     printf("The diode is properly biased.");
23 else printf("The diode is not properly biased.");
24 end
```

Scilab code Exa 3.12 Determination of bias for a zener diode and calculating power

```
1 //Tested on Windows 7 Ultimate 32-bit
```

```

2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 96
3 clear;
4 clc;
5
6 //Given Data
7 //From Figure 3.27
8
9 V=15; //value of voltage source in volts
10 Vz=12; //zener breakdown voltage in volts
11 R=390; //series resistance in ohms
12 rz=10; //diode resistance in ohms
13 Izmax=10; //maximum zener current in milli-amperes
14
15 //Solution
16
17 //Assuming ideal diode Vz=12V and Rz=0 ohms
18 Vr=V-Vz; //voltage across resistor in volts
19 Iz=Vr/(R+rz)*1000; //current through circuit in milli
   -amperes
20
21 if Iz<Izmax then
22     printf("The diode is properly biased.\n");
23 else printf("The diode is not biased properly.\n");
24 end
25
26 Pz=Vz*Iz; //power dissipation in milli-watts
27
28 printf("The dissipated power = Pz = %d mW",Pz);

```

Scilab code Exa 3.13 Determination of bias for a zener diode and calculating power

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 97

```

```

3  clear;
4  clc;
5
6  //Given Data
7  //From Figure 3.28
8
9  V=15; //value of voltage source in volts
10 Vz=10; //zener breakdown voltage in volts
11 Rs=300; //series resistance R in ohms
12 Rp=900; //shunt resistance R' in ohms
13 Izmax=10; //maximum zener current in milli-amperes
14
15 //Solution
16
17 //Assuming ideal diode Vz=12V and Rz=0 ohms
18 Vrs=V-Vz; //voltage across resistor in volts
19 Irs=Vrs/Rs*1000; //current through resistor R in
    milli-amperes
20 Irp=Vz/Rp*1000; //current through resistor R' in
    milli-amperes
21
22 Iz=Irs-Irp; //current through diode in milli-amperes
23
24 if Iz<Izmax then
25     printf("The diode is properly biased.\n");
26 else printf("The diode is not biased properly.\n");
27 end
28
29 Pd=Vz*Iz; //power dissipation in milli-watts
30
31 printf("The dissipated power = Pd = %.1f mW",Pd);

```

Scilab code Exa 3.14 Calculation of output voltage for given zener circuit

```

1  //Tested on Windows 7 Ultimate 32-bit

```

```

2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 97 and 98
3 clear;
4 clc;
5
6 //Given Data
7
8 Vin=18;//input voltage in volts
9 Vz=10;//zener breakdown voltage in volts
10 Tr=20;//reference temperature in degree celsius
11 T=40;//given temperature in degree celcius
12 Tc=0.075/100;//Temperature co-efficient in degree
   celcius inverse
13 R=150;//value of resistor in ohms
14
15 //Solution
16
17 dVz=Vz*Tc*(T-Tr);//Change in Vz in volts
18 Vz40=Vz+dVz;//Zener voltage at T=40 degree celsius
19 Vr=Vin-Vz40;//voltage drop across resistor
20
21 printf("The output voltage Vo = Vr =%.2f Volts",Vr);

```

Scilab code Exa 3.15 Calculation of all branch currents for given zener circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 99 and 100
3 clear;
4 clc;
5
6 //Given Data
7
8 Vin1=50;//input voltage in volts
9 Vin2=75;//input voltage in volts

```

```

10 Vz=15; //zener breakdown voltage in volts
11 Pmax=1; //diode maximum power dissipation in watts
12 R=3.9D3; //value of resistor in ohms
13 Rload=3D3; //value of load resistance in ohms
14
15 //Solution
16 //With reference to Figure 3.32
17 disp(" Case (a)");
18 disp(" Vin=50V");
19 Vbc=Vz; //voltage across diode in volts
20 Vab=Vin1-Vbc; //voltage across resistor in volts
21 I=Vab/R*1000; //battery current in milli-amperes
22 Iload=Vbc/Rload*1000; //current through load in milli-
    -amperes
23 Iz=I-Iload; //current through diode in milli-amperes
24 Izmax=Pmax/Vz*1000; //maximum current through diode
    in milli-amperes
25
26 printf("\n Battery current I = %.2f mA\n Zenner
    current Iz = %.2f mA\n Load current Iload = %d mA
    ",I,Iz,Iload)
27
28 disp(" Case (b)");
29 disp(" Vin=75V");
30 Vbc=Vz; //voltage across diode in volts
31 Vab=Vin2-Vbc; //voltage across resistor in volts
32 I=Vab/R*1000; //battery current in milli-amperes
33 Iload=Vbc/Rload*1000; //current through load in milli-
    -amperes
34 Iz=I-Iload; //current through diode in milli-amperes
35 Izmax=Pmax/Vz*1000; //maximum current through diode
    in milli-amperes
36
37 printf("\n Battery current I = %.2f mA\n Zenner
    current Iz = %.2f mA\n Load current Iload = %d mA
    ",I,Iz,Iload)
38
39 printf("\n\n Load current remains constant for any

```

```
voltage input.");
```

Scilab code Exa 3.16 Calculation of zener current for different load resistances

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
   Devices Pg no. 100
3 clear;
4 clc;
5
6 //Given Data
7
8 Vin=50;//input voltage in volts
9 Vz=30;//zener breakdown voltage in volts
10 R=2D3;//value of resistor in ohms
11
12 //Solution
13 //With reference to Figure 3.32
14
15 disp(" Case (i)");
16 disp(" Rload=30 kohm");
17 Rload=30D3;//load resistance in ohms
18 Vbc=Vz;//voltage across diode in volts
19 Vab=Vin-Vbc;//voltage across resiston in volts
20 I=Vab/R*1000;//battery current in milli-amperes
21 Iload=Vbc/Rload*1000;//current through load in milli
   -amperes
22 Iz=I-Iload;//current through diode in milli-amperes
23
24 printf("\n Zenner current Iz = %d mA\n",Iz)
25
26 disp(" Case (ii)");
27 disp(" Rload=10 kohm");
28 Rload=10D3;//load resistance in ohms
29 Vbc=Vz;//voltage across diode in volts
```

```

30 Vab=Vin-Vbc;//voltage across resistor in volts
31 I=Vab/R*1000;//battery current in milli-amperes
32 Iload=Vbc/Rload*1000;//current through load in milli
    -amperes
33 Iz=I-Iload;//current through diode in milli-amperes
34
35 printf("\n Zenner current Iz = %d mA\n",Iz)
36
37 disp("Case (iii)");
38 disp("Rload=3 kohm");
39 Rload=3000;//load resistance in ohms
40 Vbc=Vz;//voltage across diode in volts
41 Vab=Vin-Vbc;//voltage across resistor in volts
42 I=Vab/R*1000;//battery current in milli-amperes
43 Iload=Vbc/Rload*1000;//current through load in milli
    -amperes
44 Iz=I-Iload;//current through diode in milli-amperes
45
46 printf("\n Zenner current Iz = %d mA\n",Iz)
47
48 printf("\n Since Iz=0 the diode will come out of
    breakdown region\n and diode will no longer act
    as a voltage regulator.");

```

Scilab code Exa 3.17 Calculation of resistor for construction a power supply and c

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
    Devices Pg no. 101
3 clear;
4 clc;
5
6 //Given Data
7
8 Vin1=24;//value of voltage source in volts

```

```

9 Vin2=20; //value of voltage source in volts
10 Vz=12; //zener breakdown voltage in volts
11 Izmax=20; //maximum zener current in milli-amperes
12
13 //Solution
14
15 disp(" Vin=24V" );
16 R=(Vin1-Vz)/Izmax*1000; //series resistance required
    for maximum safe current in ohms
17
18 printf("The minimum value of resistor required R=%d
    ohms.",R);
19 printf("Using R=680 ohms i.e. standaed value.")
20 R=680; //standard value of resistor selected
21 disp(" Vin=20V" );
22 Iz=(Vin2-Vz)/R*1000; //value of zener current in
    milli-amperes
23
24 printf("Current level at Vin=20V is Iz=%0.1f mA",Iz);

```

Scilab code Exa 3.18 Design of a zener voltage regulator

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
    Devices Pg no. 101 and 102
3 clear;
4 clc;
5
6 //Given Data
7
8 Vin=20; //supply input voltage in volts
9 Vz=9.1; //zener breakdown voltage in volts
10 Pmax=400D-3; //diode maximum power dissipation in
    watts
11 Izmin=5; //minimum current for diode to be in

```

```

        breakdown region in milli-amperes
12
13 //Solution
14
15 Izmax=Pmax/Vz;//maximum safe current through diode
    in milli-amperes
16 R=(Vin-Vz)/Izmax;
17
18 printf("Optimum value of resistor R=%0.2f ohms.\n",R)
    ;
19 printf(" Standard value is 270 ohms.\n");
20
21 Iloadmax=Izmax*1000-Izmin;//maximum load current in
    milli-amperes
22 printf("Maximum load current in the circuit Iload
    max=%0.2f mA",Iloadmax)

```

Scilab code Exa 3.19 Calculation of range of voltage for zener diode to be on

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
    Devices Pg no. 102
3 clear;
4 clc;
5
6 //Given Data
7
8 Vz=18;//zener breakdown voltage in volts
9 Izmax=60;//maximum safe current through diode in
    milli-amperes
10 R=150;//series resistance in ohms
11 Rl=1D3;//load resistance in ohms
12
13 //Solution
14

```

```

15 Vinmin=((Rl+R)/Rl)*Vz; //minimum value of input
    voltage
16 Iload=Vz/Rl*1000; //load current in milli-amperes
17 Imax=Izmax+Iload; //maximum current through battery
    in milli-amperes
18 Vinmax=Vz+Imax/1000*R; //maximum value of input
    voltage
19
20 printf("So the input voltage ranges from %.1f volts
    to %.1f volts",Vinmin,Vinmax);

```

Scilab code Exa 3.20 Calculation of series resistance and dark current for given r

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 3 Semiconductor Diodes and Miscellaneous
    Devices Pg no. 119 and 120
3 clear;
4 clc;
5
6 //Given Data
7
8 Irelay=10; //relay current in milli-amperes
9 Int=400 //light intensity in lm/m^2
10 Rc_d=100D3; //cell resistance in ohms when it is dark
11 Rc_i=1200; //cell resistance in ohms when
    illumination is 500lm/m^2
12 V=30; //source voltage in volts
13
14 //Solution
15
16 R=V/Irelay*1000-Rc_i; //series resistance in ohms
17 Id=V/(R+Rc_d)*1000; //dark current in milli-amperes
18
19 printf("Series resistance R = %d ohms\n Dark current
    = %.3f mA ",R,Id)

```


Chapter 4

Bipolar Junction Transistor

Scilab code Exa 4.1 Calculation of CE and CB current gains

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 131
3 clear;
4 clc;
5
6 //Given Data
7
8 IB=40D-6;//base current in amperes
9 IC=4.25D-3;//collector current in amperes
10
11 //Solution
12
13 Bdc=IC/IB;//value of dc CE current gain
14 Adc=Bdc/(Bdc+1);//value of dc CB current gain
15
16 printf("The value of dc = %.2f and dc = %.4f",
        Bdc,Adc);
17
18 //Error in decimal places due to approximations in
    textbook
```

Scilab code Exa 4.2 Calculation of CB current gain and collector current

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 131
3 clear;
4 clc;
5
6 //Given Data
7
8 Bdc=175; //value of dc CE current gain
9 IB=40D-6; //base current in amperes
10
11 //Solution
12
13 IC=IB*Bdc*1000; //collector current in milli-amperes
14 Adc=Bdc/(Bdc+1); //value of dc CB current gain
15
16 printf("The value of IC = %d mA and dc = %.4f", IC,
    Adc);
17
18 //Error in decimal places due to approximations in
    textbook
```

Scilab code Exa 4.3 Calculation of CE current gain and base current

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 131
3 clear;
4 clc;
5
6 //Given Data
7
```

```

8 IC=7.5D-3; //collector current in amperes
9 Adc=0.9914; //value of dc CB current gain
10
11 //Solution
12
13 IE=IC/Adc; //emitter current in amperes
14 IB=IE-IC; //base current in amperes
15 IB=IB*10^6; //converting base current to mICro-
    amperes
16 Bdc=Adc/(1-Adc); //value of dc CE current gain
17
18 printf("The value of IB = %d A and dc = %.2 f",IB
    ,Bdc);
19
20 //Error in decimal places due to approximations in
    textbook

```

Scilab code Exa 4.4 Determination of whether transistor is saturated

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 133
3 clear;
4 clc;
5
6 //Given Data
7
8 VCEsat=0.25; //VCEsat in volts
9 VBB=4.5; //base driving source in volts
10 RB=20; //base resistance in kilo-ohms
11 RC=680; //collector resistance in ohms
12 VCC=9; //collector driving source in volts
13 VBE=0.7; //forward drop of emitter diode
14 Bdc=100; //dc current gain for CE configuration
15
16 //Solution

```

```

17 //Figure 4.12
18
19 ICsat=(VCC-VCEsat)/RC*1000; //value of collector
    saturation current in milli-amperes
20 printf("IC(sat)=%.2 f mA\n\n",ICsat);
21 IB=(VBB-VBE)/RB; //value of base current in milli-
    amperes
22 printf("IB=%.2 f mA\n\n",IB);
23 IC=Bdc*IB; //collector current for given IB in milli-
    amperes
24 printf("IC=%d mA\n\n",IC);
25
26 if IC>ICsat then
27     printf("Since IC(calculated) = %d mA is greater
        than IC(sat),\nthe transistor is in
        saturation.\nThe collector current of %d mA
        is never reached.\nIf you increase IB further
        ,\nthe collector current is at the saturation
        value.",IC,IC);
28 end
29
30 //Error of 0.01 mA in textbook in the calculation of
    IC(sat)

```

Scilab code Exa 4.5 Determination of whether transistor is saturated

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 133
    and 134
3 clear;
4 clc;
5
6 //Given Data
7
8 Bdc=50; //dc current gain for CE configuration

```

```

 9 VBB=3; //base driving source in volts
10 RB=15; //base resistance in kilo-ohms
11 RC=1; //collector resistance in kilo-ohms
12 VCC=12; //collector driving source in volts
13 VCEsat=0.25; //VCEsat in volts
14 VBE=0.7; //forward drop of emitter diode
15
16
17 //Solution
18
19 ICsat=(VCC-VCEsat)/RC; //value of collector
    saturation current in milli-amperes
20 IB=(VBB-VBE)/RB; //value of base current in milli-
    amperes
21 IC=Bdc*IB; //collector current for given IB in milli-
    amperes
22
23 if IC>ICsat then
24     printf("The transistor is in saturation and VCE=
        VCEsat=%.2f Volts",VCEsat);
25 else
26     printf("The transistor is not in saturation and
        VCE=VCC-IC*Rc = %.2fVolts", (VCC-IC*RC));
27 end

```

Scilab code Exa 4.6 Calculation of voltage gain and output voltage for given ampli

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 135
3 clear;
4 clc;
5
6 //Given Data
7
8 Vin=50D-3; //rms value of input ac voltage in volts

```

```

9 Rl=1D3; //load resistance in ohms
10 re=40; //emitter diode resistance in ohms
11
12 //Solution
13 //Figure 4.16
14
15 Gv=Rl/re; //voltage gain
16 Vout=Gv*Vin; //output voltage in volts
17
18 printf("Voltage Gain Gv = %d and Output Voltage Vout
        = %.2 f Vrms( Volts) .", Gv, Vout);

```

Scilab code Exa 4.7 Calculation of input and output impedance and current and volt

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 139
3 clear;
4 clc;
5
6 //Given Data
7
8 IE=2D-3; //emitter current in amperes
9 A=0.97; //dc current gain of CB configuration
10 Vi=1D-3; //rms value of input ac voltage in volts
11 Rl=500; //load resistance in ohms
12 VT=26D-3; //temperature equivalent voltage of pn
    junction
13
14 //Solution
15
16 disp("(a)");
17 re=VT/IE; //emitter diode resistance in ohms
18 Zi=re; //input impedance in ohms
19 printf("Input impedance of CB circuit = re = %d ohms
        \n", Zi);

```

```

20
21 disp("(b)");
22 Ii=Vi/Zi;//input current in amperes
23 Vo=A*Ii*Rl;//output voltage in volts
24 Gv=Vo/Vi;//voltage gain
25
26 printf("Voltage gain of CB circuit Gv = %.1f\n",Gv);
27
28 disp("(c)");
29 //as output cicuit contains reverse biased junction
    output impedance is infinite
30 Gi=-A;//current gain
31
32 printf("Output impedance Zo=      and Current Gain Gi
    = %.2f",Gi);

```

Scilab code Exa 4.8 Calculation of input impedance and current and voltage gain at

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 139
3 clear;
4 clc;
5
6 //Given Data
7
8 B=140;//dc current gain of CE configuration
9 IE=2D-3;//emitter current in amperes
10 Rl1=2D3;//load resistance in ohms
11 Rl2=1.2D3;//load resistance in ohms
12 VT=26D-3;//temperature equivalent voltage of pn
    junction
13
14 //Solution
15
16 disp("(a)");

```

```

17 re=VT/IE; //emitter diode resistance in ohms
18 Zi=B*re; //input impedance in ohms
19 printf("Input impedance of CE circuit = re = %d ohms
    \n", Zi);
20
21 disp("(b)");
22 Gv=-Rl1/re; //voltage gain
23
24 printf("Voltage gain of CE circuit at 2k-ohm load =
    Gv = %.1f\n", Gv);
25
26 disp("(c)");
27 Gi=B; //current gain
28
29 printf("Current Gain Gi = %d", Gi);
30
31 //Error in voltage gain in part (b) as Rl is
    mistaken as 1.2 kilo-ohm instead of 2 kilo-ohm

```

Scilab code Exa 4.9 Determination of CE hybrid model and CB re model

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 4 Bipolar Junction transistors Pg no. 141
    and 142
3 clear;
4 clc;
5
6 //Given Data
7
8 hfe=120; //forward transfer current ratio of CE
    configuration
9 hoe=20D-6; //output conductance of CE configuration
    in siemens
10 hohfe=1D-6; //output conductance of Chfe
    configuration in siemens

```

```

11 IE=2D-3; //emitter current in amperes
12 VT=26D-3; //temperature equivalent voltage of pn
    junction
13
14 //Solution
15
16 disp("(a)");
17 re=VT/IE; //emitter diode resistance in ohms
18 hi=hfe*re/1000; //input impedance in kilo-ohms
19 ro=1/hoe/1000; //output impedance in kilo-ohms
20 printf("hi = %.2f kilo-ohms\nro = %d kilo-ohms\n
    Value of current source is %d*Ib",hi,ro,hfe);
21 //output circuit is given as Figure 4.24
22
23 disp("(b)");
24 hi=re; //input impedance in ohms
25 A=hfe/(hfe+1); //current gain alpha of Chfe circuit
26 A=round(A); //taking approximate value
27 ro=1/hohfe/10^6; //output impedance in mega-ohms
28 printf("hi = %d ohms\nro = %d mega-ohms\nValue of
    current source is %d*Ib",hi,ro,A);
29 //output circuit is given as Figure 4.25
30
31 //Error in decimal places due to approximations in
    textbook

```

Chapter 5

Bipolar Transistor Biasing

Scilab code Exa 5.1 Calculation of quantities for Q point for given figure

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 147
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.4
8
9 B=100; //current gain of CE configuration
10 VCC=15; //biasing voltage in volts
11 R=180D3; //biasing resistance in ohms
12 Rl=1.5D3; //load resistance in ohms
13 VBE=0.7; //forward drop of emitter diode in volts
14
15 //Solution
16
17 disp("(i)");
18 IB=(VCC-VBE)/R*10^6; //base current in micro-amperes
19 IC=B*IB/1000; //colelctor current in milli-amperes
20
21 printf("IB = %.2 f A \nIC = %.2 f mA\n",IB,IC);
```

```

22
23 disp("( ii )");
24 VCE=VCC-IC*R1/1000; //volatage between collector and
    emitter in volts
25
26 printf("VCE = %.1 f   Volts",VCE);
27
28 disp("( iii )");
29 VB=VBE; //base voltage w.r.t. ground in volts
30 VC=VCE; //coollector voltage w.r.t. ground in volts
31
32 printf("VB = %.1 f   Volts\nVC = %.1 f   Volts\n",VB,VC);
33
34 disp("( iv )");
35 VCB=VC-VB; //voltage between collector and base in
    volts
36 VBC=-VCB; //voltage between base and collector in
    volts
37
38 printf("VCB = %.1 f   Volts\n",VCB);
39 if VBC<0 then
40     printf("Base collector junction is reverse
        biased.\n")
41 end

```

Scilab code Exa 5.2 Calculation of saturation current for given figure

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 149
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.4
8

```

```

9 VCC=15; //biasing voltage in volts
10 Rl=1.5D3; //load resistance in ohms
11
12 //Solution
13
14 //Assuming VCEsat=0 volts
15 ICsat=VCC/Rl*1000; //saturation current in milli-
    amperes
16
17 printf("ICsat = %d mA\n",ICsat);

```

Scilab code Exa 5.3 Calculation of Vcc and given resistances for the load line and

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 151
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.10
8
9 VCE=15; //voltage between collector and emitter in
    volts at IC = 0 mA
10 IC=15D-3; //collecoetr current in amperes in VCE = 0
    Volts
11 IB=35D-6; //base current at Q point in amperes
12 VBE=0.7; //forward voltage drop of emitter diode in
    volts
13
14 //Solution
15
16 VCC=VCE; //biasing voltage in volts = VCE at IC = 0
    mA
17 R=(VCC-VBE)/IB/1000; //base biasing resistance in
    kilo-ohms

```

```

18 Rl=VCC/IC/1000; //load resistance in kilo-ohms
19
20 printf("VCC = %d Volts\n R = %.1f kilo-ohms\n Rl =
    %d kilo-ohm",VCC,R,Rl);

```

Scilab code Exa 5.4 Calculation of parameters for emitter biased circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 153
   and 154
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.14
8
9 VCC=15; //supply voltage in volts
10 RB=330D3; //base resistance in ohms
11 RL=2D3; //load collector resistance in ohms
12 RE=820; //emitter resistance in ohms
13 B=75; //DC CE current gain beta
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 Cb=12D-6; //base coupling capacitor in farads
16 Ce=50D-6; //emitter bypass capacitor in farads
17
18 //Solution
19
20 disp("( i )");
21 IB=(VCC-VBE)/(RB+B*RE)*10^6; //base current in micro
    ampere
22 printf("IB = %.2f A \n",IB);
23
24 disp("( ii )");
25 IC=B*IB/1000; //collector current in milli ampere

```

```

26 printf("IC = %.2 f mA\n",IC);
27
28 disp("( iii )");
29 VCE=VCC-IC*(RL+RE)/1000; //collector to emitter
    voltage in volts
30 printf("VCE = %.1 f Volts\n",VCE);
31
32 disp("( iv )");
33 VC=VCC-IC*RL/1000; //collector to ground voltage in
    volts
34 printf("VC = %.2 f Volts\n",VC);
35
36 disp("( v )");
37 VE=VC-VCE; //emitter to ground voltage in volts
38 printf("VE = %.2 f Volts\n",VE);
39
40 disp("( vi )");
41 VB=VBE+VE; //base to ground voltage in volts
42 printf("VB = %.2 f Volts\n",VB);
43
44 disp("( vi )");
45 VCB=VC-VB; //collector to base voltage in volts
46 printf("VCB = %.1 f Volts\n",VCB);
47
48 if VCB>0
49     printf("VBC is less than zero indicating
        collector base junction is reverse biased.")
50 end
51
52 //error in answers w.r.t. text book as BETA in
    figure is 75 and in calculations is 76
53 //here BETA is taken as 75
54 //also in (iv) answer is not printed in textbook

```

Scilab code Exa 5.5 Calculation of Q point for given dc bias circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 157
   and 158
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.19
8
9 VCC=20; //supply voltage in volts
10 R1=22D3; //bias resistance in ohms
11 R2=2.2D3; //bias resistance in ohms
12 RL=10D3; //load collector resistance in ohms
13 RE=820; //emitter resistance in ohms
14 B=100; //DC CE current gain beta
15 VBE=0.7; //forward voltage drop of emitter diode in
   volts
16 Cb=15D-6; //base coupling capacitor in farads
17 Ce=40D-6; //emitter bypass capacitor in farads
18 Cc=15D-6; //collector coupling capacitor in farads
19
20 //Solution
21
22 Rth=R1*R2/(R1+R2); //thevenin resistance of R1 and R2
   at base in ohms
23 Vth=VCC*R2/(R1+R2); //thevenin voltage at base in
   volts
24
25 IB=(Vth-VBE)/(Rth+(B+1)*RE)*10^6; //base current in
   micro ampere
26 printf("IB = %.2 f   A \n", IB);
27
28 IC=B*IB/1000; //collector current in milli ampere
29 printf("IC = %.2 f mA\n", IC);
30
31 VCE=VCC-IC*(RL+RE)/1000; //collector to emitter
   voltage in volts
32 printf("VCE = %.3 f Volts\n", VCE);

```

33

34 //calculation error in textbook as Vth turns out to
be 1.818 V instead of 1.67 V

Scilab code Exa 5.6 Calculation of stability factors for given circuit

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 158
  and 159
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.19
8
9 VCC=20; //supply voltage in volts
10 R1=22D3; //bias resistance in ohms
11 R2=2.2D3; //bias resistance in ohms
12 RL=10D3; //load collector resistance in ohms
13 RE=820; //emitter resistance in ohms
14 B=100; //DC CE current gain beta
15 VBE=0.7; //forward voltage drop of emitter diode in
  volts
16 Cb=15D-6; //base coupling capacitor in farads
17 Ce=40D-6; //emitter bypass capacitor in farads
18 Cc=15D-6; //collector coupling capacitor in farads
19 IC0=1D-6; //leakage current in amperes
20
21 //Solution
22
23 Rth=R1*R2/(R1+R2); //thevenin resistance of R1 and R2
  at base in ohms
24 Vth=VCC*R2/(R1+R2); //thevenin voltage at base in
  volts
25 IB=(Vth-VBE)/(Rth+(B+1)*RE); //base current in ampere
```

```

26 IC=B*IB; //collector current in ampere
27
28 S1=(B+1)*(1+Rth/RE)/(1+B+Rth/RE); //Stability factor
    S of IC against ICO
29
30 S2=-B/(Rth+RE+B*RE); //Stability factor S' of IC
    against VBE
31
32 S3=1/(B*(1+B))*(IC*((Rth+RE)*(1+B)-B*S1*RE)/(RE+Rth)
    -S1*ICO); //Stability factor S'' of IC against
    BETA
33
34 printf("S= IC / ICO =%.3 f\n",S1);
35 printf("S''= IC / VBE =%.3 e\n",S2);
36 printf("S''''= IC / B =%.3 e\n",S3);
37
38 //error in calculation in textbook for IC and S''

```

Scilab code Exa 5.7 Calculation of Q point for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 161
    and 162
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.23
8
9 VCC=11; //supply voltage in volts
10 R=220D3; //base bias resistance in ohms
11 RL=5.6D3; //load collector resistance in ohms
12 RE=1.5D3; //emitter resistance in ohms
13 B=75; //DC CE current gain beta
14 VBE=0.7; //forward voltage drop of emitter diode in

```

```

        volts
15 Cb=12D-6; //base coupling capacitor in farads
16 Cc=12D-6; //collector coupling capacitor in farads
17
18 //Solution
19
20 IB=(VCC-VBE)/(B*(RL+RE)+R); //base current in ampere
21 ICQ=B*IB*1000; //quiescent collector current in milli
    ampere
22 VCEQ=VCC-ICQ*(RE+RL)/1000; //quiescent collector to
    emitter voltage in volts
23 printf("ICQ = %.2 f mA\n",ICQ);
24 printf("VCEQ = %.2 f Volts\n",VCEQ);
25
26 //decimal approximation error w.r.t textbook

```

Scilab code Exa 5.8 Calculation of Q point for given circuit and given beta

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 162
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.23
8
9 VCC=11; //supply voltage in volts
10 R=220D3; //base bias resistance in ohms
11 RL=5.6D3; //load collector resistance in ohms
12 RE=1.5D3; //emitter resistance in ohms
13 B=120; //DC CE current gain beta
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 Cb=12D-6; //base coupling capacitor in farads
16 Cc=12D-6; //collector coupling capacitor in farads

```

```

17
18 //Solution
19
20 IB=(VCC-VBE)/(B*(RL+RE)+R); //base current in ampere
21 ICQ=B*IB*1000; //quiescent collector current in milli
    ampere
22 VCEQ=VCC-ICQ*(RE+RL)/1000; //quiescent collector to
    emitter voltage in volts
23 printf("ICQ = %.2 f mA\n",ICQ);
24 printf("VCEQ = %.2 f Volts\n",VCEQ);
25
26 //decimal approximation error w.r.t textbook

```

Scilab code Exa 5.9 Calculation of dc level of IB and VC for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 162
    and 163
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.24
8
9 VCC=20; //supply voltage in volts
10 R=270D3; //base bias resistance in ohms(60k+90k+120k)
11 RL=3.9D3; //load collector resistance in ohms
12 RE=410; //emitter resistance in ohms
13 B=100; //DC CE current gain beta
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 Cb=12D-6; //base coupling capacitor in farads
16 Cc=12D-6; //collector coupling capacitor in farads
17 Ce=60D-6; //emitter bypass capacitor in farads
18

```

```

19 //Solution
20
21 IB=(VCC-VBE)/(B*(RL+RE)+R); //base current in ampere
22 IC=B*IB*1000; //collector current in milli ampere
23 VC=VCC-IC*RL/1000; //collector to ground voltage in
    volts
24 printf("d.c. level of IB = %.1f A \n",IB*10^6);
25 printf("d.c. level of VC = %.2f Volts\n",VC);
26
27 //decimal approximation error w.r.t textbook

```

Scilab code Exa 5.10 Design of a bias circuit for amplifier for given current IE

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 164
    and 165
3 clear;
4 clc;
5
6 //Given Data
7
8 IE=1.5D-3; //emitter current in amperes
9 VCC=15; //supply voltage in volts
10 B=100; //DC CE current gain beta
11 VBE=0.7; //forward voltage drop of emitter diode in
    volts
12
13 //Solution
14
15 //Approximations
16 VR2=VCC/3; //voltage across R2 is 1/3rd of supply
    voltage
17 VRL=VCC/3; //voltage across RL is 1/3rd of supply
    voltage
18

```

```

19 VB=VR2;//voltage of base to ground in volts
20 VE=VB-VBE;//voltage of emitter to ground in volts
21 RE=VE/IE;//emitter resistance in ohms
22 I=0.1*IE;//setting voltage divider current as 0.1IE
    and neglecting base current
23 R1_plus_R2=VCC/I;//R1+R2 in ohms
24 R2=VR2/VCC*R1_plus_R2;//R2 in ohms
25 R1=R1_plus_R2-R2;//R1 in ohms
26
27 printf("RE = %.2f kilo-ohms\n",RE/1000);
28 printf("R1 = %.2f kilo-ohms\n",R1/1000);
29 printf("R2 = %.2f kilo-ohms\n",R2/1000);
30 //design is given in Figure E5.10
31 //IE for this circuit is 1.40 mA and more accuracy
    can be obtained by exact equations and
    eliminating approximations

```

Scilab code Exa 5.11 Calculation of stability factor for collector to base bias ci

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 165
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.26
8
9 RL=470;//collector load resistance in ohms
10 R=20D3;//base collector parallel resistance in ohms
11 B=90;//DC CE current gain beta
12
13 //Solution
14
15 S=(B+1)/(1+(B*RL)/(RL+R));//stability factor S
16 printf("S = %.2f",S);

```

```
17
18 //decimal error as calculation is not accurate in
    textbook
```

Scilab code Exa 5.12 Calculation of stability factor for given circuit and load

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 165
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.26
8
9 RL=10; //load resistance in ohms which is dc
    resistance of primary coil of transistor
10 R=20D3; //base collector parallel resistance in ohms
11 B=90; //DC CE current gain beta
12
13 //Solution
14
15 S=(B+1)/(1+(B*RL)/(RL+R)); //stability factor S
16 printf("S = %.2 f", S);
```

Scilab code Exa 5.13 Calculation of stability factors for given circuit and parame

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 166
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.27
```

```

8
9 IC=20D-3; //collector current in amperes
10 VCE=6; //collector to emitter voltage in volts
11 VCC=15; //supply voltage in volts
12 RL=390; //collector load resistance in ohms
13 IB=2D-3; //base bias current in amperes
14 B=90; //DC CE current gain beta
15 RE=82; //emitter resistance in ohms
16 C1=10D-6; //base coupling capacitance in farads
17 C2=10D-6; //collector coupling capacitance in farads
18 VBE=0.7; //forward voltage drop of emitter diode in
    volts
19
20 //Solution
21
22 R=(VCC-VBE-IC*RL-(IC+IB)*RE)/IB; //base collector
    parallel resistance in ohms
23 S=(B+1)/(1+(B*RE)/(RE+R)); //stability factor S
24 printf("S = %.2f",S);
25
26 //calculation errors in textbook as KVL is
    incorrectly applied

```

Scilab code Exa 5.14 Calculation of Q point for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 166
    and 167
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.28
8
9 VCC=12; //supply voltage in volts

```

```

10 RL=6.8D3; //collector load resistance in ohms
11 B=75; //DC CE current gain beta
12 R=82D3; //base collector parallel resistance in ohms
13 VBE=0.7; //forward voltage drop of emitter diode in
    volts
14
15 //Solution
16
17 IC=(VCC-VBE)/(RL+R/B); //collector current in amperes
18 VCE=VCC-IC*RL; //collector to emitter voltage in
    volts and VCE = VC as VE = 0 V since emitter is
    grounded
19 printf("IC = %.2f mA\n", IC*1000);
20 printf("VCE = %.2f Volts\n", VCE);

```

Scilab code Exa 5.15 Calculation of Q point for given circuit and given beta

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 167
    and 168
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.28
8
9 VCC=12; //supply voltage in volts
10 RL=6.8D3; //collector load resistance in ohms
11 B=200; //DC CE current gain beta
12 R=82D3; //base collector parallel resistance in ohms
13 VBE=0.7; //forward voltage drop of emitter diode in
    volts
14
15 //Solution
16

```

```

17 IC=(VCC-VBE)/(RL+R/B); //collector current in amperes
18 VCE=VCC-IC*RL; //collector to emitter voltage in
    volts and VCE = VC as VE = 0 V since emitter is
    grounded
19 printf("IC = %.2 f mA\n",IC*1000);
20 printf("VCE = %.2 f Volts\n",VCE);
21
22 //error in textbooks as question is about Fig 5.27
    and solved for Fig 5.28 , here solved as Fig 5.28
23 //decimal approximation error in textbook

```

Scilab code Exa 5.16 Calculation of Q point and stability factors for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 168
3 clear;
4 clc;
5
6 //Given Data
7 //Figure E5.15
8
9 VCC=15; //supply voltage in volts
10 RL=1.5D3; //collector load resistance in ohms
11 B=100; //DC CE current gain beta
12 R=82D3; //base collector parallel resistance in ohms
13 VBE=0.7; //forward voltage drop of emitter diode in
    volts
14
15 //Solution
16
17 IC=(VCC-VBE)/(RL+R/B); //collector current in amperes
18 VCE=VCC-IC*RL; //collector to emitter voltage in
    volts and VCE = VC as VE = 0 V since emitter is
    grounded
19 disp("Q - point");

```

```

20 printf("IB = %.2 f  A \n",IC*1D6/B);
21 printf("IC = %.2 f  mA\n",IC*1000);
22 printf("VCE = %.2 f  Volts\n",VCE);
23
24 disp("Stability  factors");
25
26 S1=(B+1)/(1+(B*RL)/(RL+R)); //stability factor S
27 printf("S = %.2 f\n",S1);
28
29 S2=-B/(R+RL+B*RL); //Stability factor S'
30 printf("S' ' = %.3 f  mA/V\n",S2*1000);
31
32 S3=(VCC-VBE-IC*RL)/(R+RL/(1+B)); //Stability factor S
   ,,
33 printf("S' ' ' ' = %.2 f  A \n",S3*1D6);
34
35 //decimal approximation error w.r.t textbook

```

Scilab code Exa 5.17 Calculation of unknown resistances for the given circuit and

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 168
   and 169
3 clear;
4 clc;
5
6 //Given Data
7 //Figure E5.17
8
9 B=100; //DC CE current gain beta
10 VCC=15; //supply voltage in volts
11 RL=1D3; //collector load resistance in ohms
12 VCE=7.5; //collector to emitter voltage in volts
13 IC=6D-3; //collector current in amperes
14 VBE=0.7; //forward voltage drop of emitter diode in

```

```

        volts
15 S=12; //stability factor S
16
17
18 //Solution
19
20 IB=IC/B; //base current in amperes
21 RE=(VCC-VCE-IC*RL)/(IC+IB); //emitter resistance in
    ohms
22 Rth=RE*(S-1)/(1-S/(1+B)); //thevenin resistance of
    divider network in ohms
23 R1=VCC*Rth/(IB*Rth+VBE+(IC+IB)*RE); //resistance R1
    in ohms
24 R2=R1*Rth/(R1-Rth); //resistance R2 in ohms
25
26 printf("RE = %.3f kilo-ohms\n",RE/1000);
27 printf("R1 = %.2f kilo-ohms\n",R1/1000);
28 printf("R2 = %.2f kilo-ohms\n",R2/1000);
29
30 //error in calculations in textbook for R1 and R2 as
    R2 cannot be less than Rth which is parallel
    resistance of R1 and R2

```

Scilab code Exa 5.18 Calculation of given parameters for circuit and stated parameters

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 5 Bipolar Transistor Biasing Pg no. 170
    and 171
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 5.30
8
9 B=100; //DC CE current gain beta

```

```

10 VCC=18; //collector supply voltage in volts
11 VEE=9; //emitter supply voltage in volts
12 VBE=0.7; //forward voltage drop of emitter diode in
    volts
13 RE=30D3; //emitter resistance in ohms
14 R=15D3; //base bias resistance in ohms
15 RL=15D3; //collector load resistance in ohms
16
17 //Solution
18
19 disp(" ( i ) ");
20 IE=(VEE-VBE)/(RE+R/B); //emitter current in amperes
21 printf(" IE = %.3 f mA\n", IE*1000);
22
23 disp(" ( ii ) ");
24 IC=IE; //collector current in amperes
25 printf(" IE = %.3 f mA\n", IC*1000);
26
27 disp(" ( iii ) ");
28 VC=VCC-IC*RL; //collector to ground voltage in volts
29 printf(" VC = %.2 f Volts\n", VC);
30
31 disp(" ( iv ) ");
32 VE=-(IC*R/B+VBE); //emitter to ground voltage in volts
33 printf(" VE = %.2 f Volts\n", VE);
34
35 disp(" ( v ) ");
36 VCE=VC-VE; //collector to emitter voltage in volts
37 printf(" VCE = %.2 f Volts\n", VCE);
38
39 disp(" ( vi ) ");
40 S=(1+R/RE)/(1+R/B/RE); //stability factor S
41 printf(" S = %.4 f\n", S);
42
43 //calculations are carried out taking RL=9 kilo-ohm
    instead of 15 kilo-ohm as in Figure 5.30 in
    textbook
44 //resulting in change in values of VC and VCE

```


Chapter 6

Single Stage BJT Amplifiers

Scilab code Exa 6.1 Plot of DC and AC load lines for given circuit

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no. 184
   and 185
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.7
8
9 VCC=20; //collector supply voltage in volts
10 RC=1.5D3; //collector resistance in ohms
11 RE=1.8D3; //emitter resistance in ohms
12 R1=8.2D3; //divider network resistance R1 in ohms
13 R2=3.9D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
   volts
15
16 //Solution
17
```

```

18 //For DC load line
19 VCEd=0:VCC;//as for load line maximum VCE is at IC=0
    mA ie. VCE=VCC
20 ICd=(VCC-VCEd)/(RC+RE)*1000;//equation for DC load
    line
21 VB=VCC*R2/(R1+R2);//base to ground voltage in volts
22 VE=VB-VBE;//emitter to ground voltage in volts
23 IE=VE/RE;//emitter current in milli-amperes
24 IC=IE;//collector current is approximately equal to
    emitter current
25 VCE=VCC-IC*(RC+RE);//collector to emitter voltage in
    volts
26
27 //For AC load line
28 m=-1/RC;//slope of AC load line i.e. IC / VCE
29 c=IC-m*VCE;//load line passes through Q point
30 ICa=(m*VCEd+c)*1000;//AC load line equation
31
32 plot2d(VCEd,[ICd' ICa'],[1,2],leg="DC LOAD LINE@AC
    LOAD LINE",rect=[0,0,21,7]);
33 plot2d(VCE,IC*1000,-1);
34 xlabel("VCE (in Volts)");
35 ylabel("IC (in mA)");
36 xstring(VCE+.1,IC*1000+.1,"Q point");
37 xstring(VCC,.1,"R");
38 xstring(.1,VCC/(RC+RE)*1000,"P");
39 title("LOAD LINES FOR EXAMPLE 6.1")

```

Scilab code Exa 6.2 DC and AC analysis of given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Staje BJT Amplifiers Pg no.
    186,187 and 188
3 clear;
4 clc;

```

```

5
6 //Given Data
7 //Figure 6.9,6.10,6.11,6.12,6.13
8
9 VCC=15; //collector supply voltage in volts
10 RC=1D3; //collector resistance in ohms
11 RE=390; //emitter resistance in ohms
12 R1=18D3; //divider network resistance R1 in ohms
13 R2=3.9D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 Bdc=120; //DC CE current gain beta
16 Bac=130; //AC CE current gain beta
17
18 //Solution
19
20 disp("DC analysis for Figure 6.10");
21 Rin_dc=Bdc*RE; //dc input resistance in ohms
22 if 0.1*Rin_dc>R2 then
23     VB=VCC*R2/(R1+R2); //base to ground voltage in
        volts , since Rin>10*R2 it can be neglected
24 end
25 VE=VB-VBE; //emitter to ground voltage in volts
26 IE=VE/RE; //emitter current in amperes
27 IC=IE; //collector current is approximately equal to
    emitter current
28 VC=VCC-IC*RC; //collector to ground voltage in volts
29 VCE=VC-VE; //collector to emitter voltage in volts
30
31 printf("IC = %.2f mA\n",IC*1000);
32 printf("VCE = %.2f Volts\n",VCE);
33
34 disp("AC analysis for Figure 6.12");
35 printf("Rin'' = R1||R2||Rin where Rin=Vb/Ib\n");
36 printf("Vb=Ie*(re+RE)\n =Bac*Ib*(re+RE)\n");
37 printf("(Rin)''= Bac*(re+RE)\n");
38 printf("Rout = RC||rC = RC\n as rC>>RC\n");
39

```

40 //decimal error w.r.t. textbook due to
approximations

Scilab code Exa 6.3 Calculation of base voltage for given circuit parameters

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Staje BJT Amplifiers Pg no. 188
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.11
8
9 VCC=15; //collector supply voltage in volts
10 RC=1D3; //collector resistance in ohms
11 RE=390; //emitter resistance in ohms
12 R1=18D3; //divider network resistance R1 in ohms
13 R2=3.9D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 Bdc=120; //DC CE current gain beta
16 Bac=130; //AC CE current gain beta
17 VT=0.25D-3; //voltage equivalent of temperature in
    volts
18 Vs=5D-3; //source rms voltage in volts
19 Rs=600; //source internal impedance in ohms
20
21 //Solution
22
23 Rin_dc=Bdc*RE; //dc input resistance in ohms
24 if 0.1*Rin_dc>R2 then
25     VB=VCC*R2/(R1+R2); //base to ground voltage in
        volts , since Rin>10*R2 it can be neglected
26 end
27 VE=VB-VBE; //emitter to ground voltage in volts
```

```

28 IE=VE/RE; //emitter current in amperes
29 IC=IE; //collector current is approximately equal to
    emitter current
30 VC=VCC-IC*RC; //collector to ground voltage in volts
31 VCE=VC-VE; //collector to emitter voltage in volts
32
33 re=VT/IE; //equivalent BJT model emitter resistance
    in ohms
34 Rin_dash=Bac*(RE+re); //internal resistance of BJT in
    ohms
35 Rin=1/(1/R1+1/R2+1/Rin_dash); //total internal
    resistance is Rin=R1||R2||Rin'
36 Vb=Rin/(Rs+Rin)*Vs; //signal voltage at base in volts
37 printf("Vb = %.2 f mV",Vb*1000);

```

Scilab code Exa 6.4 Calculation of base to collector gain for given conditions of

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Staje BJT Amplifiers Pg no. 190
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.11
8
9 VCC=15; //collector supply voltage in volts
10 RC=1D3; //collector resistance in ohms
11 RE=390; //emitter resistance in ohms
12 R1=18D3; //divider network resistance R1 in ohms
13 R2=3.9D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 Bdc=120; //DC CE current gain beta
16 Bac=130; //AC CE current gain beta
17 VT=25D-3; //voltage equivalent of temperature in

```

```

        volts
18
19 //Solution
20
21 Rin_dc=Bdc*RE;//dc input resistance in ohms
22 if 0.1*Rin_dc>R2 then
23     VB=VCC*R2/(R1+R2);//base to ground voltage in
        volts , since Rin>10*R2 it can be neglected
24 end
25 VE=VB-VBE;//emitter to ground voltage in volts
26 IE=VE/RE;//emitter current in amperes
27 IC=IE;//collector current is approximately equal to
        emitter current
28 VC=VCC-IC*RC;//collector to ground voltage in volts
29 VCE=VC-VE;//collector to emitter voltage in volts
30 re=VT/IE;//equivalent BJT model emitter resistance
        in ohms
31
32 disp("( i)");
33 printf("Without emitter bypass capacitor.\n");
34 gain=RC/(re+RE);//base to collector voltage gain
35 printf("Base to collector voltage gain = %.2f\n",
        gain);
36
37 disp("( ii)");
38 printf("With RE shorted.\n");
39 gain=RC/re;//base to collector voltage gain
40 printf("Base to collector voltage gain = %d\n",gain)
        ;
41
42 //gain deviation due to approximations in textbook

```

Scilab code Exa 6.5 Calculations of specific gains for given circuit parameters

```

1 //Tested on Windows 7 Ultimate 32-bit

```

```

2 //Chapter 6 Single Staje BJT Amplifiers Pg no. 191
   and 192
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.9
8
9 VCC=15; //collector supply voltage in volts
10 RC=1D3; //collector resistance in ohms
11 RE=390; //emitter resistance in ohms
12 R1=18D3; //divider network resistance R1 in ohms
13 R2=3.9D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
   volts
15 Bdc=120; //DC CE current gain beta
16 Bac=130; //AC CE current gain beta
17 VT=25D-3; //voltage equivalent of temperature in
   volts
18 Vs=5D-3; //source rms voltage in volts
19 Rs=600; //source internal impedance in ohms
20 re=5; //equivalent BJT model emitter resistance in
   ohms
21 RL=6.8D3; //load resistance in ohms
22 C2=50D-6; //emitter bypass capacitance in farads
23
24 //Solution
25
26 disp("( i)");
27 RL_dash=RC*RL/(RC+RL); //a.c. value of collector
   resistance in ohms
28 Gv=RL_dash/re; //a.c. voltage gain
29 printf("A.C. Voltage gain Gv = %.1f\n",Gv);
30
31 disp("( ii)");
32 Rin_dash=Bac*(RE+re); //internal resistance of BJT in
   ohms
33 Rin=1/(1/R1+1/R2+1/Rin_dash); //total internal

```

```

    resistance is Rin=R1||R2||Rin'
34 f=Rin/(Rs+Rin); //input attenuation factor
35 Gv_dash=f*Gv; //overall a.c. voltage gain
36 printf("Overall A.C. Voltage gain Gv'' = %.1f\n",
    Gv_dash);
37
38 //gain deviation due to approximations in textbook

```

Scilab code Exa 6.6 Calculation of output voltage for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no.
   193,194 and 195
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.18,6.19,6.20
8
9 VCC=15; //collector supply voltage in volts
10 RC=5.6D3; //collector resistance in ohms
11 RE0=390; //unbypassed emitter resistance in ohms
12 RE1=390; //bypassed emitter resistance in ohms
13 R1=33D3; //divider network resistance R1 in ohms
14 R2=4.7D3; //divider network resistance R2 in ohms
15 VBE=0.7; //forward voltage drop of emitter diode in
   volts
16 Bdc=140; //DC CE current gain beta
17 Bac=160; //AC CE current gain beta
18 VT=25D-3; //voltage equivalent of temperature in
   volts
19 Vs=15D-3; //source rms voltage in volts
20 Rs=600; //source internal impedance in ohms

```

```

21 RL=68D3; //load resistance in ohms
22 C1=10D-6; //input coupling capacitance in farads
23 C2=50D-6; //emitter bypass capacitance in farads
24 C3=10D-6; //output coupling capacitance in farads
25
26
27 //Solution
28
29 //DC analysis
30 Rin_dc=Bdc*(RE0+RE1); //dc input resistance in ohms
31 if 0.1*Rin_dc>R2 then
32     VB=VCC*R2/(R1+R2); //base to ground voltage in
        volts , since Rin>10*R2 it can be neglected
33 end
34 VE=VB-VBE; //emitter to ground voltage in volts
35 IE=VE/(RE0+RE1); //emitter current in amperes
36 IC=IE; //collector current is approximately equal to
        emitter current
37 VC=VCC-IC*RC; //collector to ground voltage in volts
38
39 //AC analysis
40 re=VT/IE; //equivalent BJT model emitter resistance
        in ohms
41 Rin_dash=Bac*(RE0+re); //internal resistance of BJT
        in ohms
42 Rin=1/(1/R1+1/R2+1/Rin_dash); //total internal
        resistance is Rin=R1||R2||Rin'
43 f=Rin/(Rs+Rin); //input attenuation factor
44 RL_dash=1/(1/RC+1/RL); //effective load resistance
45 Gv=RL_dash/(re+RE0); //a.c. voltage gain
46 Gv_dash=f*Gv; //overall a.c. voltage gain
47 vc=Gv_dash*Vs; //a.c voltage at collector in volts
48 printf("Output voltage will be a.c. signal of
        amplitude %d mV \nCollector voltage will be the
        same voltage mounted on a d.c. level of %.1f
        Volts",vc*1000,VC);
49 //plotting the curves
50 t=0:0.01:2*3.14; //one period

```

```

51 y1=VC+vc*sin(t); //total collector voltage
52 y2=vc*1000*sin(t); //output voltage
53
54 subplot(2,1,1);
55 plot(y1);
56 title("(a) Collector Voltage");
57 ylabel("Vc (volts)");
58 xlabel("time period");
59
60 subplot(2,1,2);
61 plot(y2);
62 title("(b) Output Voltage");
63 ylabel("Vc (milli-volts)");
64 xlabel("time period");

```

Scilab code Exa 6.7 Calculation of output voltage for given value of load resistance

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no. 195
   and 196
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.18,6.19,6.20
8
9 VCC=15; //collector supply voltage in volts
10 RC=5.6D3; //collector resistance in ohms
11 RE0=390; //unbypassed emitter resistance in ohms
12 RE1=390; //bypassed emitter resistance in ohms
13 R1=33D3; //divider network resistance R1 in ohms
14 R2=4.7D3; //divider network resistance R2 in ohms
15 VBE=0.7; //forward voltage drop of emitter diode in
   volts
16 Bdc=140; //DC CE current gain beta

```

```

17 Bac=160; //AC CE current gain beta
18 VT=25D-3; //voltage equivalent of temperature in
    volts
19 Vs=15D-3; //source rms voltage in volts
20 Rs=600; //source internal impedance in ohms
21 C1=10D-6; //input coupling capacitance in farads
22 C2=50D-6; //emitter bypass capacitance in farads
23 C3=10D-6; //output coupling capacitance in farads
24 RL=[3.3D3 10D3 33D3 100D3 500D3 %inf] ; //load
    resistances in ohms

25
26
27 //Solution
28
29 for i=1:6
30
31     printf(" Case  (%d)\n RL = %.1f kilo-ohms\n",i,RL(i)
        /1000);
32 Rin_dc=Bdc*(RE0+RE1); //dc input resistance in ohms
33 if 0.1*Rin_dc>R2 then
34     VB=VCC*R2/(R1+R2); //base to ground voltage in
        volts , since Rin>10*R2 it can be neglected
35 end
36 VE=VB-VBE; //emitter to ground voltage in volts
37 IE=VE/(RE0+RE1); //emitter current in amperes
38 IC=IE; //collector current is approximately equal to
    emitter current
39 VC=VCC-IC*RC; //collector to ground voltage in volts
40 re=VT/IE; //equivalent BJT model emitter resistance
    in ohms
41 Rin_dash=Bac*(RE0+re); //internal resistance of BJT
    in ohms
42 Rin=1/(1/R1+1/R2+1/Rin_dash); //total internal
    resistance is Rin=R1||R2||Rin'
43 f=Rin/(Rs+Rin); //input attenuation factor
44 if RL(i)==%inf then
45     RL_dash=RC; //effective load resistance
46 else

```

```

47     RL_dash=1/(1/RC+1/RL(i)); //effective load
        resistance
48 end
49 Gv=RL_dash/(re+RE0); //a.c. voltage gain
50 Gv_dash=f*Gv; //overall a.c. voltage gain
51 vc=Gv_dash*Vs; //a.c voltage at collector in volts
52
53 printf("Output voltage vc = %.2f mV\n",vc*1000);
54 end
55
56 //error in answers in textbook due to approximations

```

Scilab code Exa 6.8 Calculation of current gain and power gain for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no. 197
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.18,6.19,6.20
8
9 VCC=15; //collector supply voltage in volts
10 RC=5.6D3; //collector resistance in ohms
11 RE0=390; //unbypassed emitter resistance in ohms
12 RE1=390; //bypassed emitter resistance in ohms
13 R1=33D3; //divider network resistance R1 in ohms
14 R2=4.7D3; //divider network resistance R2 in ohms
15 VBE=0.7; //forward voltage drop of emitter diode in
        volts
16 Bdc=140; //DC CE current gain beta
17 Bac=160; //AC CE current gain beta
18 VT=25D-3; //voltage equivalent of temperature in
        volts
19 Vs=15D-3; //source rms voltage in volts

```

```

20 Rs=600; //source internal impedance in ohms
21 C1=10D-6; //input coupling capacitance in farads
22 C2=50D-6; //emitter bypass capacitance in farads
23 C3=10D-6; //output coupling capacitance in farads
24 RL=68D3; //load resistance in ohms
25
26 //Solution
27
28 Rin_dc=Bdc*(RE0+RE1); //dc input resistance in ohms
29 if 0.1*Rin_dc>R2 then
30     VB=VCC*R2/(R1+R2); //base to ground voltage in
        volts , since Rin>10*R2 it can be neglected
31 end
32 VE=VB-VBE; //emitter to ground voltage in volts
33 IE=VE/(RE0+RE1); //emitter current in amperes
34 IC=IE; //collector current is approximately equal to
        emitter current
35 VC=VCC-IC*RC; //collector to ground voltage in volts
36
37 re=VT/IE; //equivalent BJT model emitter resistance
        in ohms
38 Rin_dash=Bac*(RE0+re); //internal resistance of BJT
        in ohms
39 Rin=1/(1/R1+1/R2+1/Rin_dash); //total internal
        resistance is Rin=R1||R2||Rin'
40 Vb=Rin/(Rs+Rin)*Vs; //signal voltage at base in volts
41 Ib=Vb/Rin_dash; //base current due to source
42 Is=Vs/(Rin+Rs); //current driven from source in
        amperes
43 Ic=Bac*Ib; //collector a.c. current
44 Gi_dash=Ic/Is; //overall a.c. current gain
45 RL_dash=RC*RL/(RC+RL); //a.c. value of collector
        resistance in ohms
46 Gv=RL_dash/re; //a.c. voltage gain
47 f=Rin/(Rs+Rin); //input attenuation factor
48 Gv_dash=f*Gv; //overall a.c. voltage gain
49 Gp_dash=Gv_dash*Gi_dash; //a.c. power gain
50

```

```

51 printf("Current gain Gi'' = %.2f and power gain Gp''
    = %.2f",Gi_dash,Gp_dash);
52
53
54 //error in calculation and missing calculation of
    power gain in textbook

```

Scilab code Exa 6.9 Calculations of specific gains and impedances for given CC amp

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no. 200
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.25
8
9 VCC=15; //collector supply voltage in volts
10 RE=1.5D3; //emitter resistance in ohms
11 R1=12D3; //divider network resistance R1 in ohms
12 R2=10D3; //divider network resistance R2 in ohms
13 VBE=0.7; //forward voltage drop of emitter diode in
    volts
14 Bac=150; //AC CE current gain beta
15 VT=25D-3; //voltage equivalent of temperature in
    volts
16 Vs=1; //input rms a.c. voltage in volts
17 Rs=600; //source internal impedance in ohms
18 RL=12D3; //load resistance in ohms
19
20 //Solution
21
22 Req=RE*RL/(RE+RL); //equivalent output resistance in
    ohms
23 Rin_dash=Bac*Req; //base input resistance

```

```

24 Rin=1/(1/R1+1/R2+1/Rin_dash); //total input
    resistance in ohms
25 VB=VCC*R2/(R1+R2); //d.c. base to ground voltage in
    volts
26 VE=VB-VBE; //d.c. emitter to ground voltage in volts
27 IE=VE/RE; //d.c. emitter current in amperes
28 re=VT/IE; //equivalent BJT model emitter resistance
    in ohms
29 Gv=Req/(Req+re); //voltage gain of CC configuration
30 Ie=Gv*Vs/Req; //a.c. emitter current in amperes
31 Iin=Vs/Rin; //a.c. input current in amperes
32 Gi=Ie/Iin; //a.c. current gain
33 Gp=Gi*Gv; //a.c. power gain
34 printf("Voltage gain Gv = %.3f\n Current gain Gi = %
    .2f\n Power gain Gp = %.2f\n Total input
    resistance Rin = %.2f kilo-ohms",Gv,Gi,Gp,Rin
    /1000);
35
36 //decimal errors in textbook due to approximations

```

Scilab code Exa 6.10 Calculations of specific gains and impedances for given CB am

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Staje BJT Amplifiers Pg no. 202
    and 203
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.28
8
9 VCC=12; //collector supply voltage in volts
10 RC=1.5D3; //collector resistance in ohms
11 RE=1.5D3; //emitter resistance in ohms
12 R1=82D3; //divider network resistance R1 in ohms

```

```

13 R2=18D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 VT=25D-3; //voltage equivalent of temperature in
    volts
16 RL=15D3; //load resistance in ohms
17
18 //Solution
19
20 VB=VCC*R2/(R1+R2); //d.c. base to ground voltage in
    volts
21 VE=VB-VBE; //d.c. emitter to ground voltage in volts
22 IE=VE/RE; //d.c. emitter current in amperes
23 re=VT/IE; //equivalent BJT model emitter resistance
    in ohms
24 Rin=re; //total input resistance in ohms
25 RL_dash=RC*RL/(RC+RL); //equivalent output resistance
    in ohms
26 Gv=RL_dash/re; //voltage gain of CC configuration
27 Gi=1; //current gain for a CB amplifier is almost
    equal to unity
28 Gp=Gi*Gv; //a.c. power gain
29 printf("Voltage gain Gv = %.1f\n Current gain Gi =
    %d\n Power gain Gp = %.1f\n Total input
    resistance Rin = %.2f ohms",Gv,Gi,Gp,Rin);

```

Scilab code Exa 6.11 Calculation of current gain for a superbeta transistor

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no. 204
3 clear;
4 clc;
5
6 //Given Data
7

```

```

8 B=190; //current gain of single transistor
9
10 //Solution
11
12 Bac=B^2; //current gain of superbeta transistor if B
    is the gain of each of the employed transistor
13 printf("Bac = %d",Bac);

```

Scilab code Exa 6.12 Calculation dc bias voltages and currents for given circuits

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no. 205
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.31
8
9 VCC=18; //collector supply voltage in volts
10 RB=3.9D6; //base resistance in ohms
11 RE=470; //emitter resistance in ohms
12 VBE=1.6; //forward voltage drop of emitter diode of
    darlington pair in volts
13 Bac=10000; //DC current gain beta for darlington pair
14
15 //Solution
16
17 IB=(VCC-VBE)/(RB+Bac*RE); //base current in amperes
18 IE=Bac*IB; //emitter current in amperes
19 IC=IE; //collector current is almost equal to emitter
    current
20 VE=IE*RE; //emitter to ground voltage in volts
21 VB=VE+VBE; //base to ground voltage in volts
22 printf("IB = %.2 f A \n ",IB*10^6);
23 printf("IE = %.1 f mA\n ",IE*10^3);

```

```

24 printf("IC = %.1 f mA\n ", IC*103);
25 printf("VE = %.2 f Volts\n ", VE);
26 printf("VB = %.2 f Volts\n ", VB);
27
28 //error in calculation in textbook for VB

```

Scilab code Exa 6.13 Calculation of input impedances for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Stage BJT Amplifiers Pg no. 207
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.31
8
9 VCC=18; //collector supply voltage in volts
10 RB=3.9D6; //base resistance in ohms
11 RE=470; //emitter resistance in ohms
12 VBE=1.6; //forward voltage drop of emitter diode of
    darlington pair in volts
13 Bac=10000; //DC current gain beta for darlington pair
14 ri=6D3; //emitter diode forward resistance
15
16 //Solution
17
18 Zin=1/(1/RB+1/(ri+Bac*RE)); //input impedance of the
    circuit
19 printf("Zin = %.3 f Mega-ohms", Zin/106);

```

Scilab code Exa 6.14 Calculation of base current and ac current gain for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit

```

```

2 //Chapter 6 Single Staje BJT Amplifiers Pg no. 207
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.31
8
9 VCC=18; //collector supply voltage in volts
10 RB=3.9D6; //base resistance in ohms
11 RE=470; //emitter resistance in ohms
12 VBE=1.6; //forward voltage drop of emitter diode of
    darlington pair in volts
13 Bac=10000; //DC current gain beta for darlington pair
14
15 //Solution
16
17 Gi=RB/(RE+RB/Bac); //a.c. circuit current gain
18 printf("Gi = %d",Gi);
19
20 //error in question as base current can not be
    obtained without an input also not solved in
    textbook

```

Scilab code Exa 6.15 Calculation of ac output impedances and voltage gain for give

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 6 Single Staje BJT Amplifiers Pg no. 207
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 6.31
8
9 VCC=18; //collector supply voltage in volts
10 RB=3.9D6; //base resistance in ohms

```

```

11 RE=470; //emitter resistance in ohms
12 VBE=1.6; //forward voltage drop of emitter diode of
    darlington pair in volts
13 Bac=10000; //DC current gain beta for darlington pair
14 ri=6D3; //emitter forward resistance of darlington
    pair
15
16 //Solution
17
18 Zout=1/(1/RE+1/ri+1/(ri/Bac)); //output impedance of
    the overall circuit in ohms
19 Gv=(RE+Bac*RE)/(ri+RE+Bac*RE); //a.c. voltage gain
20 printf("Zout = %.1f ohms\n", Zout);
21 printf("Gv = %.4f", Gv);

```

Chapter 7

Field Effect Transistors

Scilab code Exa 7.1 Calculation of drain current for given circuit specifications

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 220
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.7
8
9 IDSS=15D-3; //drain saturation current in amperes
10 VGS_cutoff=-5; //gate to source cutoff voltage in
    volts
11 RD=300; //drain resistance in ohms
12
13 //Solution
14
15 VP=-VGS_cutoff; //pinch-off voltage in volts
16 VDS=VP; //drain to source voltage in volts should be
    equal to VP or more than that for constant
    current region
17 VGS=0; //gate to source voltage in volts
18 ID=IDSS; //drain current in amperes is saturation
```

```

        current because VGS=0 volts
19 VRD=ID*RD; //voltage drop across resistor
20 VD_dash_min=VRD+VDS; //minimum source voltage
    required for constant current region in volts
21 printf("Minimum VD'' required to place JFET into
    constant current region = %.1f Volts\n ",
    VD_dash_min);
22 VD_dash=15; //given value of VD'
23 if VD_dash>VD_dash_min then
24     ID=IDSS; //drain current in equal to saturation
        current
25 end
26 printf("Drain current for VD'' = %d Volts , ID = %d
    mA\n And increased voltage will appear as drop in
    drain source terminals.",VD_dash,ID*1000);

```

Scilab code Exa 7.2 Calculation of drain current and transconductance for given ci

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 224
3 clear;
4 clc;
5
6 //Given Data
7
8 IDSS=30D-3; //drain saturation current in amperes
9 VGS_cutoff=-10; //gate to source cutoff voltage in
    volts
10 gm0=5000D-6; //transconductance at VGS=0 Volts in
    Siemens
11 VGS=-5; //gate to source voltage in volts
12
13 //Solution
14
15 gm=gm0*(1-VGS/VGS_cutoff); //transconductance for

```

```

        given VGS in Siemens
16 ID=IDSS*(1-VGS/VGS_cutoff)^2; //drain current for
    given VGS in amperes
17 printf("gm = %d S \n ",gm*10^6);
18 printf("ID = %.1 f mA",ID*10^3);
19
20 //calculation of gm is incorrect in textbook as gm0
    =5000 S and not 500 S

```

Scilab code Exa 7.3 Calculation of drain current and transconductances for given c

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 224 and
    225
3 clear;
4 clc;
5
6 //Given Data
7
8 IDSS=10D-3; //drain saturation current in amperes
9 VP=6; //pinch-off voltage in volts
10 VGS=-3; //gate to source voltage in volts
11
12 //Solution
13
14 disp("( i)");
15 ID=IDSS*(1-VGS/(-VP))^2; //drain current for given
    VGS in amperes
16 printf("ID = %.1 f mA",ID*10^3);
17
18 disp("( ii)");
19 gm0=-2*IDSS/(-VP); //transconductance for VGS=0 Volts
    in Siemens
20 printf("gm0 = %.2 f mS",gm0*10^3);
21

```

```

22 disp(" ( i i i ) ");
23 gm=gm0*(1-VGS/(-VP)); //transconductance for given
    VGS in Siemens
24 printf("gm = %.2 f mS",gm*10^3);

```

Scilab code Exa 7.4 Calculation of drain current for given circuit specifications

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 225
3 clear;
4 clc;
5
6 //Given Data
7
8 IDSS=15D-3; //drain saturation current in amperes
9 gm0=5D-3; //transconductance for VGS=0 Volts in
    Siemens
10 gm=2.5D-3; //transconductance in Siemens
11
12 //Solution
13
14 ID=IDSS*(gm/gm0)^2; //drain current in amperes
15 printf("ID = %.2 f mA",ID*10^3);

```

Scilab code Exa 7.5 Calculation of circuit parameters for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 227
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.14

```

```

8
9 VDD=15; //drain supply voltage in volts
10 IDSS=15D-3; //drain saturation current in amperes
11 VP=-6; //pinchoff voltage in volts
12 RD=1D3; //drain resistance in ohms
13 RG=2D6; //gate resistance in ohms
14 VGG=1.5; //gate supply voltage in volts
15
16 //Solution
17
18 disp(" ( i ) ");
19 VGS_Q=-VGG; //quiescent gate to source voltage in
    volts (since gate current is zero and drop across
    RG=0 Volts)
20 printf("VGS_Q = %.1 f Volts",VGS_Q);
21
22 disp(" ( ii ) ");
23 IDQ=IDSS*(1-VGS_Q/VP)^2; //quiescent drain current in
    amperes
24 printf("IDQ = %.3 f mA",IDQ*10^3);
25
26 disp(" ( iii ) ");
27 VDS=VDD-IDQ*RD; //drain to source voltage in volts
28 printf("VDS = %.3 f Volts",VDS);
29
30 disp(" ( iv ) ");
31 VD=VDS; //drain to ground voltage in volts (since
    source is grounded)
32 printf("VD = %.3 f Volts",VD);
33
34 disp(" ( v ) ");
35 VG=VGS_Q; //gate to ground voltage in volts (since
    source is grounded)
36 printf("VG = %.1 f Volts",VG);
37
38 disp(" ( vi ) ");
39 VS=0; //source to ground voltage in volts (since
    source is grounded)

```

```
40 printf("VS = %d Volts",VS);
```

Scilab code Exa 7.6 Calculation of circuit parameters for given circuit

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 229
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.16
8
9 VDD=15; //drain supply voltage in volts
10 IDSS=10D-3; //drain saturation current in amperes
11 VP=-6; //pinchoff voltage in volts
12 RD=1D3; //drain resistance in ohms
13 RG=2D6; //gate resistance in ohms
14 RS=1D3; //source resistance in ohms
15
16 //Solution
17
18 disp("( i)");
19 ID_A=5D-3; ID_B=3D-3; //assuming two currents below
    and above the characteristic curve
20 VGS_A=ID_A*RS; VGS_B=ID_B*RS; //calculating
    corresponding gate to source voltages in volts
21 //constructing a line joining A and B. It intersects
    characteristic curve at Q point VGS_Q
22 VGS_Q=-3.2; //quiescent gate to source voltage in
    volts (solved using characteristic graph)
23 printf("VGS_Q = %.1 f Volts",VGS_Q);
24
25 disp("( ii)");
26 IDQ=-VGS_Q/RS; //quiescent drain current in amperes
27 printf("IDQ = %.1 f mA",IDQ*10^3);
```

```

28
29 disp("( iii)");
30 VDS=VDD-IDQ*(RD+RS); //drain to source voltage in
    volts
31 printf("VDS = %.1 f Volts",VDS);
32
33 disp("( iv)");
34 VS=IDQ*RS; //source to ground voltage in volts
35 printf("VS = %.1 f Volts",VS);
36
37 disp("( v)");
38 VG=0; //gate to ground voltage in volts (since gate
    current is almost zero, drop across RG is zero)
39 printf("VG = %d Volts",VG);
40
41 disp("( vi)");
42 VD=VDD-IDQ*RD; //drain to ground voltage in volts (
    since source is grounded)
43 printf("VD = %.1 f Volts",VD);
44
45 //error in calculations in textbook as values are
    not taken as per the figure

```

Scilab code Exa 7.7 Calculation of circuit parameters for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 230 and
    231
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.18 and 7.19
8
9 VDD=18; //drain supply voltage in volts

```

```

10 IDSS=12D-3; //drain saturation current in amperes
11 VP=-2; //pinchoff voltage in volts
12 RD=1172; //drain resistance in ohms
13 RS=1028; //source resistance in ohms
14 VSS=9; //source supply voltage in volts
15
16 //Solution
17
18 disp(" ( i ) ");
19 VGS_a=9; //for ID=0 mA VGS=VSS volts
20 ID_a=8.754D-3; //for VGS=0 volts ID=VSS/RS amperes0
21 //a load line is constructed using these values and
    the intersection with charecteristic curve gives
    Q point
22 IDQ=9D-3; //quiescent drain current found graphically
    in amperes
23 printf("IDQ = %d mA", IDQ*10^3);
24
25 disp(" ( ii ) ");
26 VGS_Q=-0.25; //quiescent gate to source voltage in
    volts found graphically
27 printf("VGS_Q = %.2 f Volts", VGS_Q);
28
29 disp(" ( iii ) ");
30 VDS=VDD-IDQ*(RD+RS)+VSS; //drain to source voltage in
    volts
31 printf("VDS = %.1 f Volts", VDS);
32
33 disp(" ( iv ) ");
34 VD=VDD-IDQ*RD; //drain to ground voltage in volts (
    since source is grounded)
35 printf("VD = %.2 f Volts", VD);
36
37 disp(" ( v ) ");
38 VS=VD-VDS; //source to ground voltage in volts
39 printf("VS = %.2 f Volts", VS);

```

Scilab code Exa 7.8 Calculation of circuit parameters for given circuit

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 232,233
   and 234
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.23 and 7.24
8
9 VDD=18; //drain supply voltage in volts
10 IDSS=10D-3; //drain saturation current in amperes
11 VP=-5; //pinchoff voltage in volts
12 RD=1.5D3; //drain resistance in ohms
13 RS=1D3; //source resistance in ohms
14 R1=1.5D6; //divider network resistance R1 in ohms
15 R2=180D3; //divider network resistance R2 in ohms
16 C1=5D-6; //gate coupling capacitance in farads
17 C2=25D-6; //source bypass capacitance in farads
18 C3=15D-6; //drain coupling capacitance in farads
19
20 //Solution
21
22 disp("( i)");
23 VG=VDD*R2/(R1+R2); //gate to ground voltage in volts
24 VGS_a=1.93; //for ID=0 mA VGS=VSS volts
25 ID_a=1.93D-3; //for VGS=0 volts ID=VG/RS amperes0
26 //a load line is constructed using these values and
   the intersection with charecteristic curve gives
   Q point
27 IDQ=3.64D-3; //quiscent drain current found
   graphically in amperes
28 printf("IDQ = %.2 f mA", IDQ*10^3);
```

```

29
30 disp("( ii)");
31 VGS_Q=-1.85; //quiescent gate to source voltage in
    volts found graphically
32 printf("VGS_Q = %.2 f Volts",VGS_Q);
33
34 disp("( iii)");
35 VD=VDD-IDQ*RD; //drain to ground voltage in volts (
    since source is grounded)
36 printf("VD = %.2 f Volts",VD);
37
38 disp("( iv)");
39 VS=IDQ*RS; //source to ground voltage in volts
40 printf("VS = %.2 f Volts",VS);
41
42 disp("( v)");
43 VDS=VDD-IDQ*(RD+RS); //drain to source voltage in
    volts
44 printf("VDS = %.1 f Volts",VDS);

```

Scilab code Exa 7.9 Calculation of voltage gain for given circuit parameters

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 237
3 clear;
4 clc;
5
6 //Given Data
7
8 gm=5D-3; //transconductance in Siemens
9 RD=1D3; //drain resistance in ohms
10 rd=7D3; //AC drain resistance in ohms
11
12 //Solution
13

```

```
14 GV=gm*RD*rd/(RD+rd); //voltage gain
15 printf("GV = %.3 f",GV);
```

Scilab code Exa 7.10 Calculation of voltage gain for given circuit parameters

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 237 and
   238
3 clear;
4 clc;
5
6 //Given Data
7
8 gm=5D-3; //transconductance in Siemens
9 RD=1D3; //drain resistance in ohms
10
11 //Solution
12
13 GV=gm*RD; //voltage gain
14 printf("GV = %d",GV);
```

Scilab code Exa 7.11 Calculation of voltage gain for given circuit parameters

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 238
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.30
8
9 gm=5D-3; //transconductance in Siemens
10 RD=1.2D3; //drain resistance in ohms
```

```

11 RS=330; //source resistance in ohms
12
13 //Solution
14
15 GV=gm*RD/(1+gm*RS); //voltage gain
16 printf("GV = %.2 f",GV);

```

Scilab code Exa 7.12 Calculation of voltage gain for given circuit parameters

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 241
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.31
8
9 gm=5D-3; //transconductance in Siemens
10 RD=2.7D3; //drain resistance in ohms
11 RL=3.3D3; //load resistance in ohms
12
13 //Solution
14
15 RL_eq=RD*RL/(RD+RL); //equivalent load resistance in
    ohms
16 GV_dash=gm*RL_eq; //voltage gain for loaded circuit
17 GV=gm*RD; //voltage gain for unloaded circuit
18 printf("Voltage gain GV' ' = %.2 f\n Unloaded a.c.
    voltage gain GV = %.1 f",GV_dash,GV);
19
20 //decimal approximation in textbook

```

Scilab code Exa 7.13 Calculation of circuit parameters for given circuit

```

1  clear;
2  clc;
3
4  disp("AS ON PAGE NUMBER 242");
5  //Tested on Windows 7 Ultimate 32-bit
6  //Chapter 7 Field Effect Transistors Pg no. 242,243
   and 244
7
8  //Given Data
9  //Figure 7.37
10
11 VGS_Q=-2.5; //quiescent gate to source voltage in
   volts
12 IDQ=5D-3; //quiescent drain current in amperes
13 VDD=12; //drain supply voltage in volts
14 IDSS=12D-3; //drain saturation current in amperes
15 VP=-5; //pinch off voltage in volts
16 YOS=20D-6; //AC drain admittance of JFET in Siemens
17 RS=1.5D3; //source resistance in ohms
18 RG=1.5D6; //gate resistance in ohms
19 C1=0.1D-6; //gate coupling capacitance in farads
20 C2=0.1D-6; //drain coupling capacitance in farads
21
22 //Solution
23
24 disp("( i)");
25 gm0=2*IDSS/abs(VP); //transconductance for VGS=0
   Volts in Siemens
26 gm=gm0*(1-VGS_Q/VP); //transconductance in Siemens
27 printf("gm = %.1 f mS\n",gm*10^3);
28
29 disp("( ii)");
30 rd=1/YOS; //AC drain resistance in ohms
31 printf("rd = %d kilo ohms\n",rd/10^3);
32
33 disp("( iii)");
34 Zin=RG; //input impedance in ohms
35 printf("Zin = %.1 f Mega-ohms\n",Zin/10^6);

```

```

36
37 disp("(iv)");
38 Zout=1/(1/rd+1/RS+gm); //output impedance with rd
    connected in ohms
39 printf("Zout with rd = %d ohms\n",Zout);
40 Zout_dash=1/(1/RS+gm); //output impedance with rd
    disconnected in ohms
41 printf("Zout without rd = %.2f ohms\n",Zout_dash);
42
43 disp("(v)");
44 GV=gm*rd*RS/(rd+RS+gm*rd*RS); //voltage gain with rd
    connected
45 printf("GV with rd = %.2f\n",GV);
46 GV_dash=gm*RS/(1+gm*RS); //voltage gain with rd
    disconnected
47 printf("GV without rd = %.3f\n",GV_dash);
48
49 //decimal approximations in textbook
50
51 disp("AS ON PAGE NUMBER 245");
52
53 //Tested on Windows 7 Ultimate 32-bit
54 //Chapter 7 Field Effect Transistors Pg no. 245 and
    246
55
56 //Given Data
57 //Figure E7.13
58
59 VDD=12; //drain supply voltage in volts
60 gm=4000D-6; //transconductance in Siemens
61 YOS=20D-6; //AC drain admittance of JFET in Siemens
62 RS=2.2D3; //source resistance in ohms
63 RD=5D3; //drain resistance in ohms
64 RL=5D3; //load resistance in ohms
65
66 //Solution
67
68 RL_dash=RD*RL/(RD+RL); //equivalent load resistance

```

```

        in ohms
69 GV=gm*RL_dash;//voltage gain
70 Rin_source=1/gm;//input resistance at source
    terminal in ohms
71 Rin_net=Rin_source*RS/(Rin_source+RS);//net input
    resistance in ohms
72 Rout=1/(1/rd+1/RD+1/RL);//output resistance in ohms
73 printf("Voltage gain GV = %d\n",GV);
74 printf("Input resistance Rin = %.1f ohms\n",Rin_net)
    ;
75 printf("Output resistance Rout = %.2f kilo-ohms\n",
    Rout/10^3);

```

Scilab code Exa 7.14 Calculation of drain current for given circuit specifications

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 251
3 clear;
4 clc;
5
6 //Given Data
7
8 IDSS=15D-3;//drain saturation current in amperes
9 VGS0=-6;//gate to source cutoff voltage in volts
10 VGS_1=-2;//gate to source voltage in volts
11 VGS_2=2;//gate to source voltage in volts
12
13 //Solution
14
15 ID_1=IDSS*(1-VGS_1/VGS0)^2;//drain current for VGS_1
    in amperes
16 ID_2=IDSS*(1-VGS_2/VGS0)^2;//drain current for VGS_2
    in amperes
17 printf("For VGS = %d Volts\nID = %.2f mA\n\n",VGS_1,
    ID_1*10^3);

```

```

18 printf("For VGS = %d Volts\nID = %.2f mA\n\n",VGS_2,
        ID_2*10^3);
19
20 //decimal are rounded off here

```

Scilab code Exa 7.15 Determination of n channel or p channel D MOSFET using circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 251 and
   252
3 clear;
4 clc;
5
6 //Given Data
7
8 IDSS=20D-3;//drain saturation current in amperes
9 VGS0=6;//gate to source cutoff voltage in volts
10 VGS_1=3;//gate to source voltage in volts
11 VGS_2=-3;//gate to source voltage in volts
12
13 //Solution
14
15 ID_1=IDSS*(1-VGS_1/VGS0)^2;//drain current for VGS_1
   in amperes
16 ID_2=IDSS*(1-VGS_2/VGS0)^2;//drain current for VGS_2
   in amperes
17 printf("For VGS = %d Volts\nID = %d mA\n\n",VGS_1,
        ID_1*10^3);
18 printf("For VGS = %d Volts\nID = %d mA\n\n",VGS_2,
        ID_2*10^3);
19 if VGS0>0 then
20     printf("Since VGS0 is positive ,this is an p-
        channel MOSFET");
21 else
22     printf("Since VGS0 is negative ,this is an n-

```

```

channel MOSFET");
23 end

```

Scilab code Exa 7.16 Calculation of VGS and VDS for given circuit parameters

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 253
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.47
8
9 ID_ON=5D-3; //ON drain current in amperes
10 VGS_th=5; //threshold gate to source voltage in volts
11 VGS=9; //gate to source voltage in volts
12 VDD=20; //drain supply voltage in volts
13 RD=1D3; //drain resistance in ohms
14 R1=2.2D3; //voltage divider network resistance R1 in
    ohms
15 R2=3.3D3; //voltage divider network resistance R2 in
    ohms
16
17 //Solution
18
19 VGS_Q=VDD*R2/(R1+R2); //gate to source voltage in
    volts
20 C=ID_ON/(VGS-VGS_th)^2; //constant C in ampere/volt^2
21 ID=C*(VGS_Q-VGS_th)^2; //drain current in amperes
22 VDS=VDD-ID*RD; //drain to source voltage in volts
23 printf("VGS = %d Volts\n VDS = %.2f Volts",VGS_Q,VDS
    );

```

Scilab code Exa 7.17 Calculation of VDS for given D MOSFET circuit parameters

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 254 and
   255
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.50
8
9 IDSS=15D-3; //drain saturation current in amperes
10 VGS0=-6; //cut-off gate to source voltage in volts
11 VDD=20; //drain supply voltage in volts
12 RD=470; //drain resistance in ohms
13 RG=8.2D6; //gate resistance in ohms
14
15 //Solution
16
17 ID=IDSS; //drain current in amperes
18 VDS=VDD-ID*RD; //drain to source voltage in volts
19 printf("VDS = %.2 f Volts",VDS);
```

Scilab code Exa 7.18 Calculation of VDS for given E MOSFET circuit parameters

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 255 and
   256
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.49(b)
8
9 R1=8.2D3; //divider network resistance R1 in ohms
```

```

10 R2=15D3; //divider network resistance R2 in ohms
11 RD=680; //drain resistance in ohms
12 RS=0; //source resistance in ohms
13 VDD=20; //drain supply voltage in volts
14 ID_ON=2D-3; //ON drain current in amperes
15 VGS=10; //gate to source voltage in volts
16 VGS_th=5; //threshold voltage in volts
17
18 //Solution
19
20 VGS_Q=VDD*R2/(R1+R2); //gate to source voltage in
    volts
21 C=ID_ON/(VGS-VGS_th)^2; //constant C in ampere/volt^2
22 ID=C*(VGS_Q-VGS_th)^2; //drain current in amperes
23 VDS=VDD-ID*RD; //drain to source voltage in volts
24 printf("VDS = %.2f Volts",VDS);

```

Scilab code Exa 7.19 Calculation of VDS for given circuit parameters

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 7 Field Effect Transistors Pg no. 255 and
    256
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 7.49(b)
8
9 R1=8.2D3; //divider network resistance R1 in ohms
10 R2=15D3; //divider network resistance R2 in ohms
11 RD=680; //drain resistance in ohms
12 RS=0; //source resistance in ohms
13 VDD=20; //drain supply voltage in volts
14 ID_ON=2D-3; //ON drain current in amperes
15 VGS=10; //gate to source voltage in volts

```

```
16 VGS_th=5; //threshold voltage in volts
17
18 //Solution
19
20 VGS_Q=VDD*R2/(R1+R2); //gate to source voltage in
    volts
21 C=ID_ON/(VGS-VGS_th)^2; //constant C in ampere/volt^2
22 ID=C*(VGS_Q-VGS_th)^2; //drain current in amperes
23 VDS=VDD-ID*RD; //drain to source voltage in volts
24 printf("VDS = %.2 f Volts",VDS);
```

Chapter 8

Power Amplifiers

Scilab code Exa 8.1 Calculation of maximum collector current for given VCC and PD

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 267
3 clear;
4 clc;
5
6 //Given Data
7
8 VCC=15;//battery voltage in volts
9 P_OUT=5;//output power in watts
10
11 //Solution
12
13 IC_MAX=P_OUT/VCC;//maximum collector current in
    amperes
14 printf("Maximum collector current IC = %d mA",IC_MAX
    *10^3);
```

Scilab code Exa 8.2 Calculation of ac output voltage and current for given circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 267,268 and 269
3 clear;
4 clc;
5
6 //Given Data
7
8 p_out=32;//output power of speaker in watts
9 Z_speaker=8;//impedance of speaker in ohms
10
11 //Solution
12
13 v_out=sqrt(p_out*Z_speaker);//output a.c. voltage in
    volts
14 i_out=v_out/Z_speaker;//output a.c. current in
    amperes
15 printf("The a.c. output voltage V = %d Volts\n The a
    .c. output current I = %d Amperes",v_out,i_out);

```

Scilab code Exa 8.3 Calculation of effective resistance at primary of transformer

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 271 and 272
3 clear;
4 clc;
5
6 //Given Data
7
8 k=10;//turn ratio of transformer
9 RL=8;//load resistance in ohms
10
11 //Solution
12
13 RL_eq=k^2*RL;//equivalent resistance at primary in
    ohms

```

```
14 printf("RL' ' = %d ohms",RL_eq);
```

Scilab code Exa 8.4 Calculation of turns ratio of a transformer for given parameters

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 272
3 clear;
4 clc;
5
6 //Given Data
7
8 RL=8;//load resistance in ohms
9 RL_eq=5D3;//equivalent resistance at primary in ohms
10
11 //Solution
12
13 k=sqrt(RL_eq/RL);//turns ratio N1/N2
14 printf("N1:N2 = %d:1",k);
```

Scilab code Exa 8.5 Calculation of power parameters and efficiency of transistor

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 277,278 and 279
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 8.13
8
9 VCC=20;//collector supply voltage in volts
10 RC=270;//collector resistance in ohms
11 RE=150;//emitter resistance in ohms
12 R1=3.3D3;//divider network resistance R1 in ohms
```

```

13 R2=1.5D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 B=100; //DC CE current gain beta
16 RL=470; //load resistance in ohms
17 C1=15D-6; //input coupling capacitance in farads
18 C2=15D-6; //output coupling capacitance in farads
19
20 //Solution
21
22 VB=VCC*R2/(R1+R2); //base to ground voltage in volts
23 VE=VB-VBE; //emitter to ground voltage in volts
24 IE=VE/RE; //emitter current in amperes
25 ICQ=IE; //neglecting base current, collector current
    is equal to emitter current in amperes
26 VC=VCC-ICQ*RC; //collector to ground voltage in volts
27 VCEQ=VC-VE; //collector to emitter quiescent voltage
    in volts
28 PD=VCEQ*ICQ; //power dissipation in watts
29 RL_dash=RC*RL/(RC+RL); //equivalent a.c. load
    resistance in ohms
30 IC_sat=ICQ+VCEQ/RL_dash; //saturation collector
    current in amperes
31 VCE_cutoff=VCEQ+ICQ*RL_dash; //cutoff collector to
    emitter voltage in volts
32 Pout=0.5*ICQ^2*RL_dash; //output a.c. power in watts
33 e=Pout/VCC/ICQ; //efficiency of circuit = Pout/Pin(dc
    )
34 printf("(a) The minimum transistor power rating
    required PD = %.3f Watts\n ",PD);
35 printf("(b) AC output power Pout = %d milli-Watts\n
    ",Pout*10^3);
36 printf("(c) Efficiency of the amplifier      = %.2f\n
    ",e);
37
38 //decimal approximation taken here in efficiency

```

Scilab code Exa 8.6 Calculation of maximum load power of amplifier

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 279
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 8.13
8
9 VCC=20; //collector supply voltage in volts
10 RC=270; //collector resistance in ohms
11 RE=150; //emitter resistance in ohms
12 R1=3.3D3; //divider network resistance R1 in ohms
13 R2=1.5D3; //divider network resistance R2 in ohms
14 VBE=0.7; //forward voltage drop of emitter diode in
    volts
15 B=100; //DC CE current gain beta
16 RL=470; //load resistance in ohms
17 C1=15D-6; //input coupling capacitance in farads
18 C2=15D-6; //output coupling capacitance in farads
19
20 //Solution
21
22 VB=VCC*R2/(R1+R2); //base to ground voltage in volts
23 VE=VB-VBE; //emitter to ground voltage in volts
24 IE=VE/RE; //emitter current in amperes
25 ICQ=IE; //neglecting base current, collector current
    is equal to emitter current in amperes
26 VC=VCC-ICQ*RC; //collector to ground voltage in volts
27 VCEQ=VC-VE; //collector to emitter quiescent voltage
    in volts
28 RL_dash=RC*RL/(RC+RL); //equivalent a.c. load
    resistance in ohms
```

```

29 VCEQ_midpt=(VCEQ+ICQ*RL_dash)/2; //collector to
    emitter voltage in Q point is set at midpoint of
    load line
30 Pout_max=0.5*VCEQ_midpt^2/RL_dash; //maximum output
    power for amplifier
31 printf("Maximum value of load power Pout(max) = %d
    milli-Watts",Pout_max*10^3);

```

Scilab code Exa 8.7 Calculation of input and output powers and efficiency for give

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 279 and 280
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 8.15
8
9 VCC=25; //collector supply voltage in volts
10 RL=25; //load collector resistance in ohms
11 RB=1.5D3; //base resistance in ohms
12 VBE=0.7; //forward voltage drop of emitter diode in
    volts
13 B=50; //DC CE current gain beta
14 Iin=12D-3; //input peak current in amperes
15
16 //Solution
17
18 IBQ=(VCC-VBE)/RB; //base quiescent current in amperes
19 ICQ=B*IBQ; //collector quiescent current in amperes
20 VCEQ=VCC-ICQ*RL; //quiescent collector to emitter
    voltage in volts
21 Ic_p=B*Iin; //peak collector current swing in amperes
22 Pout_ac=Ic_p^2*RL/2; //output a.c. power in watts
23 Pin_dc=VCC*ICQ; //input d.c. power in watts

```

```

24 e=Pout_ac/Pin_dc;//efficiency of amplifier
25 printf("(a) Input power = %.2f Watts\n ",Pin_dc);
26 printf("(b) Output power = %.1f Watts\n ",Pout_ac);
27 printf("(c) Efficiency of the amplifier      = %.2f %%\n ",e*100);

```

Scilab code Exa 8.8 Calculation of harmonic distortion and increase in power due to

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 288
3 clear;
4 clc;
5
6 //Given Data
7
8 vin_p=2;//input signal amplitude in volts
9 fin=50;//input signal frequency in hertz
10 I1=10;I2=1.5;I3=0.70;I4=0.3;//input current nth
    harmonic's amplitude in amperes
11
12 //Solution
13
14 D2=I2/I1;//second harmonic distortion
15 D3=I3/I1;//third harmonic distortion
16 D4=I4/I1;//fourth harmonic distortion
17 disp("(a)");
18 printf("Second harmonic distortion D2 = %.f %%\n ",
    D2*100);
19 printf("Third harmonic distortion D3 = %.f %%\n ",D3
    *100);
20 printf("Fourth harmonic distortion D4 = %.f %%\n ",
    D4*100);
21
22 D=sqrt(D2^2+D3^2+D4^2);//distortion factor
23 P=D^2;//percentage increase in power

```

```

24 disp("(b)");
25 printf("Percentage increase in power = %.2f %%",P
    *100);

```

Scilab code Exa 8.9 Calculation of output power for given amplifier circuit

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 288
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 8.23
8
9 VCC=25;//collector supply voltage in volts
10 RL=220;//load resistance in ohms
11
12 //Solution
13
14 PCC=VCC^2/RL;//power developed in watts
15 printf("Power developed in amplifier PCC = %.2f
    Watts",PCC);

```

Scilab code Exa 8.10 Calculation of maximum efficiency for an inductor coupled amp

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 288
3 clear;
4 clc;
5
6 //Given Data
7
8 VCC=12;//collector supply voltage in volts

```

```

9  RL=220; //load resistance in ohms
10
11 //Solution
12
13 PL_max=(VCC/RL)^2*RL/2; //maximum load power in watts
14 Pin=VCC*VCC/RL; //power delivered to load in watts
15 e=PL_max/Pin; //efficiency of amplifier
16 printf("Efficiency of the amplifier      = %.f %%",e
        *100);

```

Scilab code Exa 8.11 Calculation of maximum load power of amplifier for given VCC

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 289
3 clear;
4 clc;
5
6 //Given Data
7
8 VCC=12; //collector supply voltage in volts
9 RL=12; //load resistance in ohms
10
11 //Solution
12
13 PL_max=(VCC/RL)^2*RL/2; //power developed in watts
14 printf("Maximum value of load power = %.f Watts",
        PL_max);

```

Scilab code Exa 8.12 Calculation of turns ratio of a transformer for given paramet

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 289 and 290
3 clear;

```

```

4  clc;
5
6  //Given Data
7
8  VCC=12;//collector supply voltage in volts
9  RL=16;//load resistance of loudspeaker in ohms
10 Pmax=1;//input power of loudspeaker
11 VCE_sat=0.7;//collector to emitter saturation
    voltage in volts
12
13 //Solution
14
15 k=(VCC-VCE_sat)/sqrt(2*RL*Pmax);//turns ratio
16 printf("Turns ratio      = %.3f or %.f turns",k,k);

```

Scilab code Exa 8.13 Calculation of supplied and collector dissipated power for an

```

1  //Tested on Windows 7 Ultimate 32-bit
2  //Chapter 8 Power Amplifiers Pg no. 290
3  clear;
4  clc;
5
6  //Given Data
7
8  VCC=12;//collector supply voltage in volts
9  RL=16;//load resistance of loudspeaker in ohms
10 Pmax=1;//input power of loudspeaker
11 VCE_sat=0.7;//collector to emitter saturation
    voltage in volts
12
13 //Solution
14
15 PCC=4/%pi*Pmax;//supplied power in watts
16 P=0.5*(PCC-Pmax);//collector dissipated power in
    watts

```

```

17 printf(" Supplied power PCC = %.3f Watts\n ",PCC);
18 printf(" Collector dissipated power = %.3f Watts",P);
19
20 //decimal approximations taken here

```

Scilab code Exa 8.14 Calculation of efficiency of complementary symmetry amplifier

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 8 Power Amplifiers Pg no. 290
3 clear;
4 clc;
5
6 //Given Data
7 //Figure 8.21
8
9 VCC=12;//collector supply voltage in volts
10 RL=4;//load resistance in ohms
11 Pmax=15;//maximum load power in watts
12 IC_max=2.5;//maximum collector current in amperes
13
14 //Solution
15
16 P1=2/%pi*VCC*IC_max;//power supplied in watts
17 e=Pmax/P1;//maximum efficiency of the amplifier
18 printf("Maximum efficiency max = %.2f %%",e*100);

```

Chapter 9

Frequency Response of Amplifiers

Scilab code Exa 9.1 Calculation of voltage and power gains in dB units

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   299
3 clear;
4 clc;
5
6 //Solution
7 disp("( i )");
8 Gp1=200; //power gain
9 Gp_dB1=10*log10(Gp1); //power gain in decibels
10 printf("Gp(dB) = %.2 f dB", Gp_dB1);
11 disp("( ii )");
12 Gp2=100; //power gain
13 Gp_dB2=10*log10(Gp2); //power gain in decibels
14 printf("Gp(dB) = %. f dB", Gp_dB2);
15 disp("( iii )");
16 Gp3=50; //power gain
17 Gp_dB3=10*log10(Gp3); //power gain in decibels
18 printf("Gp(dB) = %.2 f dB", Gp_dB3);
```

```

19 disp(" (iv)");
20 Gp4=10; //power gain
21 Gp_dB4=10*log10(Gp4); //power gain in decibels
22 printf("Gp(dB) = %.f dB", Gp_dB4);
23 disp(" (v)");
24 Gv5=20; //voltage gain
25 Gv_dB5=20*log10(Gv5); //voltage gain in decibels
26 printf("Gv(dB) = %.f dB", Gv_dB5);
27 disp(" (vi)");
28 Gv6=0.707; //voltage gain
29 Gv_dB6=20*log10(Gv6); //voltage gain in decibels
30 printf("Gv(dB) = %.f dB", Gv_dB6);
31 disp(" (vii)");
32 Gp7=0.5; //power gain
33 Gp_dB7=10*log10(Gp7); //power gain in decibels
34 printf("Gp(dB) = %.f dB", Gp_dB7);
35 disp(" (viii)");
36 Gv8=0.25; //voltage gain
37 Gv_dB8=20*log10(Gv8); //voltage gain in decibels
38 printf("Gv(dB) = %.f dB", Gv_dB8);
39 disp(" (ix)");
40 Gv9=0.125; //voltage gain
41 Gv_dB9=20*log10(Gv9); //voltage gain in decibels
42 printf("Gv(dB) = %.f dB", Gv_dB9);
43 disp(" (x)");
44 Gv10=0.0625; //voltage gain
45 Gv_dB10=20*log10(Gv10); //voltage gain in decibels
46 printf("Gv(dB) = %.f dB", Gv_dB10);
47 disp(" (xi)");
48 Gv11=2; //voltage gain
49 Gv_dB11=20*log10(Gv11); //voltage gain in decibels
50 printf("Gv(dB) = %.f dB", Gv_dB11);
51 disp(" (xii)");
52 Gv12=4; //voltage gain
53 Gv_dB12=20*log10(Gv12); //voltage gain in decibels
54 printf("Gv(dB) = %.f dB", Gv_dB12);
55 disp(" (xiii)");
56 Gv13=8; //voltage gain

```

```

57 Gv_dB13=20*log10(Gv13); //voltage gain in decibles
58 printf("Gv(dB) = %.f dB",Gv_dB13);
59 disp("(xiv)");
60 Gv14=16; //voltage gain
61 Gv_dB14=20*log10(Gv14); //voltage gain in decibles
62 printf("Gv(dB) = %.f dB",Gv_dB14);

```

Scilab code Exa 9.2 Calculation of input and output miller capacitances for given

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   299 and 300
3 clear;
4 clc;
5
6 //Given
7
8 Gv=-48; //voltage gain of amplifier
9 Cbc=2D-12; //base to collector capacitance in farads
10 Cbe=0.5D-12; //base to emitter capacitance in farads
11
12 //Solution
13
14 Cin_miller=Cbc*(1-Gv); //input miller capacitance in
   farads
15 Cout_miller=Cbc*(1-1/Gv); //output miller capacitance
   in farads
16 disp("(i)");
17 printf("Input Miller capacitance Cin(Miller) = %.f
   pF",Cin_miller*10^12);
18 disp("(ii)");
19 printf("Output Miller capacitance Cout(Miller) = %.f
   pF",Cout_miller*10^12);

```

Scilab code Exa 9.3 Calculation of input and output miller capacitances for given

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   300
3 clear;
4 clc;
5
6 //Given
7
8 Gv=-120; //voltage gain of amplifier
9 Cbc=2D-12; //base to collector capacitance in farads
10 Cbe=0.5D-12; //base to emitter capacitance in farads
11
12 //Solution
13
14 Cin_miller=Cbc*(1-Gv); //input miller capacitance in
   farads
15 Cout_miller=Cbc*(1-1/Gv); //output miller capacitance
   in farads
16 disp("( i)");
17 printf("Input Miller capacitance Cin(Miller) = %.f
   pF",Cin_miller*10^12);
18 disp("( ii)");
19 printf("Output Miller capacitance Cout(Miller) = %.f
   pF",Cout_miller*10^12);
```

Scilab code Exa 9.4 Calculation of gain magnitude from dB units

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   301
```

```

3  clear;
4  clc;
5
6  //Given
7
8  Gv_dB=75; //voltage gain of amplifier in dB units
9
10 //Solution
11
12 Gv=10^(0.1*Gv_dB); //voltage gain magnitude
13 printf("P2/P1 = %.f",Gv);

```

Scilab code Exa 9.5 Calculation of input voltage and power required for given ampl

```

1  //Tested on Windows 7 Ultimate 32-bit
2  //Chapter 9 Frequency Response of Amplifier Pg no.
   301
3  clear;
4  clc;
5
6  //Given
7
8  P_rated=50; //wattage rating of amplifier
9  RL=16; //load resistance of speaker in ohms
10 Gp_dB=22; //power gain in dB units
11 Gv_dB=37; //voltage gain in dB units
12
13 //Solution
14
15 disp("( i)");
16 Pi=P_rated/10^(Gp_dB/10); //input power required in
   watts
17 printf("Pi = %.2 f mW",Pi*10^3);
18
19 disp("( ii)");

```

```

20 Vin=sqrt(P_rated*RL)/10^(Gv_dB/20); //input voltage
    required in volts
21 printf("Vin = %.2 f mV",Vin*10^3);
22
23 //calculation error in textbook as wattage mentioned
    in question is 50 W and in solution is 37 W

```

Scilab code Exa 9.6 Calculation of critical frequency for a given bypass network

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
    307 and 308
3 clear;
4 clc;
5
6 //Given
7
8 VCC=15; //collector supply voltage in volts
9 RC=2.2D3; //collector resistance in ohms
10 RE=470; //emitter resistance in ohms
11 R1=33D3; //divider network resistance R1 in ohms
12 R2=10D3; //divider network resistance R2 in ohms
13 VBE=0.7; //forward voltage drop of emitter diode in
    volts
14 B=150; //DC CE current gain beta
15 Rs=600; //source internal impedance in ohms
16 RL=4.7D3; //load resistance in ohms
17 C1=0.1D-6; //input coupling capacitance in farads
18 C2=50D-6; //emitter bypass capacitance in farads
19 C3=0.1D-6; //output coupling capacitance in farads
20 re=4; //a.c. emitter resistance in ohms
21
22 //Solution
23
24 Rth=1/(1/R1+1/R2+1/Rs); //thevenin resistance at base

```

```

        in ohms
25 Rin_emitter=re+Rth/B; //resistance looking into the
    emitter in ohms
26 R=1/(1/Rin_emitter+1/RE); //resistance of the
    equivalent RC network in ohms
27 fc=1/(2*pi*R*C2); //critical frequency of the bypass
    network in hertz
28
29 printf("critical frequency of the bypass network fc
    = %d Hz",fc);

```

Scilab code Exa 9.7 Calculation of corner frequency for a given bypass network

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
    308
3 clear;
4 clc;
5
6 //Given
7
8 VCC=12; //collector supply voltage in volts
9 RE=1D3; //emitter resistance in ohms
10 R1=47D3; //divider network resistance R1 in ohms
11 R2=15D3; //divider network resistance R2 in ohms
12 VBE=0.7; //forward voltage drop of emitter diode in
    volts
13 B=100; //DC CE current gain beta
14 Rs=1000; //source internal impedance in ohms
15 CE=100D-6; //emitter bypass capacitance in farads
16 re=11.5; //a.c. emitter resistance in ohms
17
18 //Solution
19
20 Rth=1/(1/R1+1/R2+1/Rs); //thevenin resistance at base

```

```

        in ohms
21 Rin_emitter=re+Rth/B;//resistance looking into the
    emitter in ohms
22 R=1/(1/Rin_emitter+1/RE);//resistance of the
    equivalent RC network in ohms
23 fc=1/(2*pi*R*CE);//critical frequency of the bypass
    network in hertz
24
25 printf("critical frequency of the bypass network fc
    = %.2f Hz",fc);
26
27 //decimal approximation taken here

```

Scilab code Exa 9.8 Plot of total frequency response for given amplifier

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
    310
3 clear;
4 clc;
5
6 //Given
7
8 VCC=15;//collector supply voltage in volts
9 RC=2.2D3;//collector resistance in ohms
10 RE=470;//emitter resistance in ohms
11 R1=33D3;//divider network resistance R1 in ohms
12 R2=10D3;//divider network resistance R2 in ohms
13 VBE=0.7;//forward voltage drop of emitter diode in
    volts
14 B=150;//DC CE current gain beta
15 Rs=600;//source internal impedance in ohms
16 RL=4.7D3;//load resistance in ohms

```

```

17 C1=0.1D-6; //input coupling capacitance in farads
18 C2=50D-6; //emitter bypass capacitance in farads
19 C3=0.1D-6; //output coupling capacitance in farads
20 re=4; //a.c. emitter resistance in ohms
21
22 //Solution
23
24 Rin=1/(1/R1+1/R2+1/(B*re)); //thevenised input
    network resistance in ohms
25 fc_input=1/(2*pi*(Rs+Rin)*C1); //input cutoff
    frequency in hertz
26 Rth=1/(1/R1+1/R2+1/Rs); //thevenised bypass network
    resistance in ohms
27 Rin_emitter=7.7; //resistance looking into the
    emitter in ohms
28 fc_bypass=1/(2*pi*1/(1/RE+1/Rin_emitter)*C2); //
    bypass cutoff frequency in hertz
29 Rout=RC+RL; //thevenised output network resistance in
    ohms
30 fc_output=1/(2*pi*Rout*C3); //output cutoff
    frequency in hertz
31
32 s=poly(0, 's')
33 F=syslin('c', 8*pi^3*(fc_input*fc_bypass*fc_output)
    /(s+2*pi*fc_output)/(s+2*pi*fc_bypass)/(s+2*pi
    *fc_input));
34 clf;
35 gainplot(F, 100, 10000, "Bode Plot for given amplifier
    in Example 9.8");

```

Scilab code Exa 9.9 Design of input RC network and calculation of cutoff frequency

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
    312 and 313

```

```

3  clear;
4  clc;
5
6  //Given
7
8  VCC=12; //collector supply voltage in volts
9  RC=2.7D3; //collector resistance in ohms
10 RE=560; //emitter resistance in ohms
11 R1=15D3; //divider network resistance R1 in ohms
12 R2=5.6D3; //divider network resistance R2 in ohms
13 VBE=0.7; //forward voltage drop of emitter diode in
    volts
14 VT=25D-3; //voltage equivalent of temperature in
    volts
15 B=100; //DC CE current gain bet
16 Rs=600; //source internal impedance in ohms
17 RL=2.7D3; //load resistance in ohms
18 Cbe=15D-12; //base to emitter capacitance in farads
19 Cbc=2D-12; //base to collector capacitance in farads
20 Cwi=5D-12; //wiring capacitance in farads
21
22
23 //Solution
24
25 VB=VCC*R2/(R1+R2); //base to ground voltage in volts
26 VE=VB-VBE; //emitter to ground voltage in volts
27 IE=VE/RE; //emitter current in amperes
28 re=VT/IE; //a.c. emitter resistance in ohms
29 RTH=1/(1/Rs+1/R1+1/R2+1/B/re); //thevenised input
    resistance in ohms
30 Gv_mid=RC*RL/(RC+RL)/re; //midrange gain of amplifier
31 Cin_miller=Cbc*(1+Gv_mid); //input miller capacitance
    in farads
32 C=Cwi+Cbe+Cin_miller; //total input capacitance in
    farads
33 printf("The high frequency input R-C network
    consists of\n ");
34 printf("R = %.2f ohms\n ",RTH);

```

```

35 printf("C = %.1 f pF\n\n ",C*10^12);
36
37 fc=1/2/%pi/RTH/C;//critical frequency in hertz
38 printf("fc = %.2 f MHz",fc/10^6);
39
40 //calculation errors in textbook

```

Scilab code Exa 9.10 Calculation of phase shift of input RC network of a given amp

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   313 and 314
3 clear;
4 clc;
5
6 //Given
7
8 VCC=12;//collector supply voltage in volts
9 RC=2.7D3;//collector resistance in ohms
10 RE=560;//emitter resistance in ohms
11 R1=15D3;//divider network resistance R1 in ohms
12 R2=5.6D3;//divider network resistance R2 in ohms
13 VBE=0.7;//forward voltage drop of emitter diode in
   volts
14 VT=25D-3;//voltage equivalent of temperature in
   volts
15 B=100;//DC CE current gain bet
16 Rs=600;//source internal impedance in ohms
17 RL=2.7D3;//load resistance in ohms
18 Cbe=15D-12;//base to emitter capacitance in farads
19 Cbc=2D-12;//base to collector capacitance in farads
20 Cwi=5D-12;//wiring capacitance in farads
21 f=[1.19D6 2.38D6 4.76D6];//frequency values in hertz
22
23 //Solution

```

```

24
25 VB=VCC*R2/(R1+R2); //base to ground voltage in volts
26 VE=VB-VBE; //emitter to ground voltage in volts
27 IE=VE/RE; //emitter current in amperes
28 re=VT/IE; //a.c. emitter resistance in ohms
29 RTH=1/(1/Rs+1/R1+1/R2+1/B/re); //thevenised input
    resistance in ohms
30 Gv_mid=RC*RL/(RC+RL)/re; //midrange gain of amplifier
31 Cin_miller=Cbc*(1+Gv_mid); //input miller capacitance
    in farads
32 C=Cwi+Cbe+Cin_miller; //total input capacitance in
    farads
33
34 for i=1:3
35     phi=atand(2*%pi*RTH*f(i)*C);
36     printf("At f=%0.2 f MHz      = %0.2 f  \n\n ",f(i)
        /10^6,phi);
37 end

```

Scilab code Exa 9.11 Design of output RC network and calculation of critical frequency

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
    314 and 315
3 clear;
4 clc;
5
6 //Given
7
8 VCC=12; //collector supply voltage in volts
9 RC=2.7D3; //collector resistance in ohms
10 RE=560; //emitter resistance in ohms
11 R1=15D3; //divider network resistance R1 in ohms
12 R2=5.6D3; //divider network resistance R2 in ohms
13 VBE=0.7; //forward voltage drop of emitter diode in

```

```

        volts
14  VT=25D-3; //voltage equivalent of temperature in
        volts
15  B=100; //DC CE current gain bet
16  Rs=600; //source internal impedance in ohms
17  RL=2.7D3; //load resistance in ohms
18  Cbe=15D-12; //base to emitter capacitance in farads
19  Cbc=2D-12; //base to collector capacitance in farads
20  Cwo=1D-12; //output wiring capacitance in farads
21  f=[1.19D6 2.38D6 4.76D6]; //frequency values in hertz
22
23  //Solution
24
25  VB=VCC*R2/(R1+R2); //base to ground voltage in volts
26  VE=VB-VBE; //emitter to ground voltage in volts
27  IE=VE/RE; //emitter current in amperes
28  re=VT/IE; //a.c. emitter resistance in ohms
29  RTH=1/(1/Rs+1/R1+1/R2+1/B/re); //thevenised input
        resistance in ohms
30  Gv_mid=RC*RL/(RC+RL)/re; //midrange gain of amplifier
31  Cout_miller=Cbc*(1+Gv_mid)/Gv_mid; //output miller
        capacitance in farads
32  Cout_dash=Cout_miller+Cwo; //total output capacitance
        in farads
33  RL_dash=RL*RC/(RL+RC); //total output resistance in
        ohms
34  printf("The high frequency input R-C network
        consists of\n ");
35  printf("R = %.2f kilo-ohms\n ", RL_dash/10^3);
36  printf("C = %.f pF\n\n ", Cout_dash*10^12);
37
38  fc=1/2/%pi/RL_dash/Cout_dash; //critical frequency in
        hertz
39  printf("fc = %.1f MHz", fc/10^6);

```

Scilab code Exa 9.12 Calculation of bandwidth of an amplifier for given cutoff frequency

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   316
3 clear;
4 clc;
5
6 //Given
7
8 fch1=5D3;//higher cut-off frequency in hertz
9 fcl1=20;//lower cut-off frequency in hertz
10
11 //Solution
12
13 BW=fch1-fcl1;//bandwidth in hertz
14 printf("BW = %.f Hz",BW);
```

Scilab code Exa 9.13 Calculation of bandwidth of an amplifier for given transition frequency

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   316
3 clear;
4 clc;
5
6 //Given
7
8 fT=150D6;//transition frequency in hertz
9 Gv_mid=25;//midband voltage gain
10
11 //Solution
12
13 BW=fT/Gv_mid;//bandwidth in hertz
14 printf("BW = %.f MHz",BW/10^6);
```

Scilab code Exa 9.14 Determination of cutoff frequency for given input RC network

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   318 and 319
3 clear;
4 clc;
5
6 //Given
7 //Figure 9.31
8
9 VGS=12; //gate to source voltage in volts
10 IGSS=40D-9; //gate saturation current in amperes
11 VDD=12; //drain supply voltage in volts
12 RD=6.8D3; //drain resistance in ohms
13 RG=15D6; //gate resistance in ohms
14 Cin=0.001D-6; //input coupling capacitance in farads
15 Cout=0.001D-6; //output coupling capacitance in
   farads
16
17 //Solution
18
19 Rin_gate=VGS/IGSS; //gate input resistance in ohms
20 Rin=Rin_gate*RG/(Rin_gate+RG); //input resistance in
   ohms
21 fc=1/(2*%pi*Rin*Cin); //cutoff frequency in hertz
22 printf("Cutoff frequency for input RC network fc = %
   .2 f Hz",fc);
```

Scilab code Exa 9.15 Determination of cutoff frequency for given output RC network

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
   319
3 clear;
4 clc;
5 //Given
6 //Figure 9.31
7 //Given data is from Fig 9.31
8 VGS=12; //gate to source voltage in volts
9 IGSS=40D-9; //gate saturation current in amperes
10 RD=6.8D3; //drain resistance in ohms
11 RG=15D6; //gate resistance in ohms
12 Cout=0.001D-6; //output coupling capacitance in
   farads
13
14 //Solution
15
16 Rin_gate=VGS/IGSS; //gate input resistance in ohms
17 Rin=Rin_gate*RG/(Rin_gate+RG); //input resistance in
   ohms
18 RL=Rin; //load resistance is input resistance of next
   stage in ohms
19 CC2=Cout; //output RC network capacitance is equal to
   Cout
20 //The following equation is given as Equation 9.45
   in textbook
21 fc=1/(2*%pi*(RD+RL)*CC2); //cutoff frequency in hertz
22 printf("Critical frequency for output RC network fc
   ' ' = %.2 f Hz",fc);
23
24 //Error in decimal approximation in textbook.

```

Scilab code Exa 9.16 Calculation of Cgd Cds and Cgs for 2N3796 using datasheet val

```

1 //Tested on Windows 7 Ultimate 32-bit

```

```

2 //Chapter 9 Frequency Response of Amplifier Pg no.
  320
3 clear;
4 clc;
5
6 //Given
7
8 Ciss=5D-12; //FET input capacitance in farads
9 Crss=0.5D-12; //FET reverse transfer capacitance in
  farads
10 Coss=2D-12; //FET output capacitance in farads
11
12 //Solution
13
14 Cgd=Crss; //gate to drain capacitance in farads
15 Cgs=Ciss-Crss; //gate to source capacitance in farads
16 Cds=Coss-Crss; //drain to source capacitance in
  farads
17 printf("Cgd = %.1 f pF\n ",Cgd*10^12);
18 printf("Cgs = %.1 f pF\n ",Cgs*10^12);
19 printf("Cds = %.1 f pF\n ",Cds*10^12);

```

Scilab code Exa 9.17 Design of input RC network and calculation of cutoff frequency

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 9 Frequency Response of Amplifier Pg no.
  321
3 clear;
4 clc;
5
6 //Given
7 //Figure 9.35
8
9 Ciss=6D-12; //FET input capacitance in farads
10 Crss=2.5D-12; //FET reverse transfer capacitance in

```

```

        farads
11  gm=7500D-6; //transconductance in Siemens
12  Cwi=2D-12; //wiring capacitance in farads
13  VDD=12; //drain supply voltage in volts
14  Rs=50; //source resistance in ohms
15  RG=15D6; //gate resistance in ohms
16  RD=1.2D3; //drain resistance in ohms
17  RS=1D3; //source resistance in ohms
18  RL=15D6; //load resistance in ohms
19
20  //Solution
21
22  Cgd=Crss; //gate to drain capacitance in farads
23  Cgs=Ciss-Crss; //gate to source capacitance in farads
24  RL_dash=RD*RL/(RD+RL); //total load resistance in
        ohms
25  GV=gm*RL_dash; //total voltage gain
26  Cin_miller=Cgd*(1+GV); //input miller capacitance in
        farads
27  Cin_dash=Cgs+Cwi+Cin_miller; //total input
        capacitance in farads
28  fc=1/(2*%pi*Rs*Cin_dash); //cutoff frequency in hertz
29  printf("Cut-off frequency fc = %.2f MHz\n ",fc/10^6)
        ;

```

Scilab code Exa 9.18 Design of input RC network and calculation of cutoff frequency

```

1  //Tested on Windows 7 Ultimate 32-bit
2  //Chapter 9 Frequency Response of Amplifier Pg no.
    321 and 322
3  clear;
4  clc;
5
6  //Given
7  //Figure 9.35

```

```

8
9  Ciss=6D-12; //FET input capacitance in farads
10 Crss=2.5D-12; //FET reverse transfer capacitance in
    farads
11  gm=5000D-6; //transconductance in Siemens
12  VDD=12; //drain supply voltage in volts
13  Rs=50; //source resistance in ohms
14  RG=15D6; //gate resistance in ohms
15  RD=1.2D3; //drain resistance in ohms
16  RS=1D3; //source resistance in ohms
17  RL=15D6; //load resistance in ohms
18
19  //Solution
20
21  Cgd=Crss; //gate to drain capacitance in farads
22  Cgs=Ciss-Crss; //gate to source capacitance in farads
23  RL_dash=RD*RL/(RD+RL); //total load resistance in
    ohms
24  GV=gm*RL_dash; //total voltage gain
25  Cin_miller=Cgd*(1+GV); //input miller capacitance in
    farads
26  Cin_dash=Cgs+Cin_miller; //total input capacitance in
    farads
27  fc=1/(2*%pi*Rs*Cin_dash); //cutoff frequency in hertz
28  printf("Critical frequency fc = %.2f MHz\n ",fc
    /10^6);
29
30  //calculation error in textbook

```

Scilab code Exa 9.19 Design of output RC network and calculation of cutoff frequency

```

1  //Tested on Windows 7 Ultimate 32-bit
2  //Chapter 9 Frequency Response of Amplifier Pg no.
    322
3  clear;

```

```

4  clc;
5
6  //Given
7  //Figure 9.35
8
9  Ciss=6D-12; //FET input capacitance in farads
10 Crss=2.5D-12; //FET reverse transfer capacitance in
    farads
11 gm=7500D-6; //transconductance in Siemens
12 VDD=12; //drain supply voltage in volts
13 Rs=50; //source resistance in ohms
14 RG=15D6; //gate resistance in ohms
15 RD=1.2D3; //drain resistance in ohms
16 RS=1D3; //source resistance in ohms
17 RL=15D6; //load resistance in ohms
18 Cwo=1D-12; //output wiring capacitance in farads
19
20 //Solution
21
22 Cgd=Crss; //gate to drain capacitance in farads
23 Cgs=Ciss-Crss; //gate to source capacitance in farads
24 RL_dash=RD*RL/(RD+RL); //total load resistance in
    ohms
25 GV=gm*RL_dash; //total voltage gain
26 Cout_miller=Cgd*(1+GV)/GV; //output miller
    capacitance in farads
27 Cout_dash=Cwo+Cout_miller; //total output capacitance
    in farads
28 fc=1/(2*%pi*RL_dash*Cout_dash); //cutoff frequency in
    hertz
29 printf("Critical frequency fc = %.2f MHz\n ",fc
    /10^6);

```

Chapter 10

Feedback in Amplifiers

Scilab code Exa 10.1 Calculation of closed loop gain and feedback factor for given

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 330
3 clear;
4 clc;
5
6 //Given
7
8 Vi=2D-3;//input voltage in volts
9 Vo_dash=10;//output voltage with feedback in volts
10 BVo_dash=200D-3;//feedback voltage in volts
11
12 //Solution
13
14 A=Vo_dash/Vi;//open loop gain
15 Afb=Vo_dash/(Vi+BVo_dash);//closed loop gain
16 B=1/Afb-1/A;//feedback gain beta
17 printf("    = %.2 f",B);
```

Scilab code Exa 10.2 Calculation of feedback parameters and output voltage for giv

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 330
3 clear;
4 clc;
5
6 //Given
7
8 Vi=25D-3;//input voltage in volts
9 A=300;//open loop gain
10 B=0.01;//feedback factor beta
11
12 //Solution
13
14 disp("( i)");
15 Afb=A/(1+A*B);//closed loop gain
16 printf("Afb = %d\n ",Afb);
17
18 disp("( ii)");
19 Vo_dash=Afb*Vi;//output voltage with feedback in
    volts
20 printf("Vo'' = %.3f Volts\n ",Vo_dash);
21
22 disp("( iii)");
23 AB=A*B;//feedback factor A
24 printf("Feedback factor A = %d\n ",AB);
25
26 disp("( iv)");
27 BVo_dash=B*Vo_dash;//feedback voltage in volts
28 printf("Feedback voltage Vo'' = %.4f Volts",
    BVo_dash);

```

Scilab code Exa 10.3 Calculation of variation in closed loop gain with variation i

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 330 and

```

```

331
3  clear;
4  clc;
5
6  //Given
7
8  A=500; //open loop gain
9  B=0.1; //feedback factor beta
10 dA_to_A=10/100; //variation in open loop gain
11
12 //Solution
13
14 dAfb_to_Afb=dA_to_A*1/(A*B); //variation in closed
    loop gain
15 printf("Percentage variation in closed loop gain = %
    .1 f %%",dAfb_to_Afb*100);

```

Scilab code Exa 10.4 Calculation of variation in closed loop gain with variation i

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 331
3 clear;
4 clc;
5
6 //Given
7
8 A=70; //open loop gain
9 B=0.1; //feedback factor beta
10 A_dash=A+0.05*A; //open loop gain increases by 5%
11
12 //Solution
13
14 Afb=A/(1+A*B); //closed loop gain at A open loop gain
15 Afb_dash=A_dash/(1+A_dash*B); //closed loop gain at
    A_dash open loop gain

```

```

16 PC=(Afb_dash-Afb)/Afb*100; //percentage change in
    closed loop gain
17 printf("Percentage change in closed loop gain = %.1f
    %%",PC);
18
19 //approximations taken in textbook

```

Scilab code Exa 10.5 Calculation of output voltage and distortion voltage for give

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 332
3 clear;
4 clc;
5
6 //Given
7
8 A=100; //open loop gain
9 D=0.05; //distortion
10 Vi=0.5; //input voltage in volts
11
12 //Solution
13
14 disp("(a)");
15 Vo=A*Vi; //output voltage in volts
16 printf("Output signal voltage = %d Volts",Vo);
17
18 disp("(b)");
19 DV=D*Vo; //distortion voltage in volts
20 printf("Distortion voltage = %.1f Volts",DV);
21
22 disp("(c)");
23 AOV=DV+Vo; //amplifier output voltage in volts
24 printf("Amplifier output voltage = %.1f Volts",AOV);

```

Scilab code Exa 10.6 Calculation of first stage gain and second harmonic distortion

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 332
3 clear;
4 clc;
5
6 //Given
7
8 A2=200; //second stage open loop gain
9 B=0.1; //feedback gain beta
10 D2=0.02; //second harmonic distortion
11
12 //Solution
13
14 disp('(a)');
15 A2_dash=A2/(1+B*A2); //second stage closed loop gain
16 A1=A2/A2_dash; //gain of the first stage
17 printf('The gain of the first stage A1 = %d',A1);
18
19 disp('(b)');
20 D2_dash=D2/(1+B*A2); //total second harmonic
    distortion
21 printf('The second harmonic distortion D2''= %.1f %%
    ',D2_dash*100);
22
23 //calculation error in textbook as A*B=20 and not 2
```

Scilab code Exa 10.7 Calculation of bandwidth after introduction of feedback in an

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 333
```

```

3  clear;
4  clc;
5
6  //Given
7
8  A=250; //mid frequency open loop gain
9  f1=100; //open loop lower cutoff frequency in hertz
10 f2=25D3; //open loop higher cutoff frequency in hertz
11 B=0.025; //feedback gain beta
12 D2=0.02; //second harmonic distortion
13
14 //Solution
15
16 Afb=A/(1+A*B); //closed loop gain
17 f1_dash=f1/(1+A*B); //closed loop lower cutoff
    frequency in hertz
18 f2_dash=f2*(1+A*B); //closed loop higher cutoff
    frequency in hertz
19 BW=f2_dash-f1_dash; //closed loop bandwidth
20 printf("Closed loop gain Afb = %.2 f\n ",Afb);
21 printf("Closed loop bandwidth BW = %.2 f kHz",BW
    /10^3);

```

Scilab code Exa 10.8 Calculation of open and closed loop gain for given FET amplif

```

1  //Tested on Windows 7 Ultimate 32-bit
2  //Chapter 10 Feedback in Amplifiers Pg no. 341
3  clear;
4  clc;
5
6  //Given
7  //Figure 10.13
8
9  RL=6.8D3; //load resistance in ohms
10 RD=6.8D3; //drain resistance in ohms

```

```

11 Rs=400; //source resistance in ohms
12 R1=400D3; //voltage divider resistance R1 in ohms
13 R2=100D3; //voltage divider resistance R2 in ohms
14 gm=5000D-6; //transconductance in Siemens
15
16 //Solution
17
18 RL_dash=RL*RD/(RL+RD); //total equivalent load
    resistance in ohms
19 A=-gm*RL_dash; //open loop gain
20 B=-R2/(R1+R2); //feedback factor beta
21 Afb=A/(1+A*B); //closed loop gain
22 printf("Gain without feedback A = %d\n ",A);
23 printf("Gain with feedback Afb = %.2f",Afb);

```

Scilab code Exa 10.9 Calculation of open and closed loop gain for given amplifier

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 343
3 clear;
4 clc;
5
6 //Given
7 //Figure 10.16
8
9 RD=4.7D3; //drain resistance in ohms
10 Rs=1D3; //source resistance in ohms
11 RF=10D6; //feedback resistance in ohms
12 gm=2D-3; //transconductance in Siemens
13
14 //Solution
15
16 A=-gm*RD; //open loop gain
17 Afb=A*RF/(RF-A*Rs); //closed loop gain
18 printf("Gain without feedback A = %.1f\n ",A);

```

```
19 printf("Gain with feedback Afb = %.1f",Afb);
```

Scilab code Exa 10.10 Calculation of open and closed loop gain for given amplifier

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 343 and
   344
3 clear;
4 clc;
5
6 //Given
7 //Figure 10.16
8
9 RD=4.7D3;//drain resistance in ohms
10 Rs=1D3;//source resistance in ohms
11 RF=15D3;//feedback resistance in ohms
12 gm=5D-3;//transconductance in Siemens
13
14 //Solution
15
16 A=-gm*RD;//open loop gain
17 Afb=A*RF/(RF-A*Rs);//closed loop gain
18 printf("Gain without feedback A = %.1f\n ",A);
19 printf("Gain with feedback Afb = %.2f",Afb);
```

Scilab code Exa 10.11 Calculation of closed loop gain for given amplifier circuit

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 345
3 clear;
4 clc;
5
6 //Given
```

```

7 //Figure 10.18
8
9 VCC=15; //collector supply voltage in volts
10 RC=1.8D3; //collector resistance in ohms
11 RB=330; //base resistance in ohms
12 RE=390; //emitter resistance in ohms
13 hfe=150; //forward current gain
14 hie=1000; //input resistance of transistor in ohms
15 Vi=5D-3; //input rms voltage in volts
16
17 //Solution
18
19 A=-hfe/(hie+RE); //open loop gain
20 B=-RE; //feedback factor beta
21 Afb=A/(1+A*B); //closed loop gain
22 AVfb=Afb*RC; //closed loop voltage gain
23 printf("Voltage gain of the circuit (Av)fb = %.2f\n", AVfb);

```

Scilab code Exa 10.12 Calculation of closed loop gain and feedback transfer ratio

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 345
3 clear;
4 clc;
5
6 //Given
7
8 A0=200; //open loop midband gain
9 B=0.05; //feedback factor beta
10
11 //Solution
12
13 Afb=A0/(1+A0*B); //closed loop midband gain
14 printf("Voltage gain of the circuit (Av)fb = %.2f\n", Afb);

```

```
”,Afb);
```

Scilab code Exa 10.13 Calculation of lower cutoff frequency after introduction of

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 345 and
   346
3 clear;
4 clc;
5
6 //Given
7
8 A0=200; //open loop midband gain
9 B=0.05; //feedback factor beta
10 fL=25; //open loop lower cutoff frequency in hertz
11
12 //Solution
13
14 fLfb=fL/(1+A0*B); //closed loop lower cutoff
   frequency in hertz
15 printf("Closed loop lower cutoff frequency (fL)fb =
   %.2 f Hz\n ",fLfb);
```

Scilab code Exa 10.14 Calculation of upper cutoff frequency after introduction of

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 10 Feedback in Amplifiers Pg no. 346
3 clear;
4 clc;
5
6 //Given
7
8 A0=200; //open loop midband gain
```

```

9  B=0.05; //feedback factor beta
10 fH=100D3; //open loop higher cutoff frequency in
    hertz
11
12 //Solution
13
14 fHfb=fH*(1+A0*B); //closed loop higher cutoff
    frequency in hertz
15 printf("Closed loop higher cutoff frequency (fH)fb =
    %.1f MHz\n ",fHfb/10^6);

```

Chapter 11

Oscillators and Multivibrators

Scilab code Exa 11.1 Calculation of frequency of oscillations for Colpitts oscillator

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 11 Oscillators and Multivibrators Pg no.
   355 and 356
3 clear;
4 clc;
5
6 //Given
7 //Figure E 11.1
8
9 L=20D-3;//colpitts inductance in henry
10 C1=0.2D-6;//colpitts capacitor C1 in farads
11 C2=0.02D-6;//colpitts capacitor C2 in farads
12
13 //Solution
14
15 Ce=C1*C2/(C1+C2);//equivalent capacitance in farads
16 f0=1/(2*%pi*sqrt(L*Ce));//frequency of oscillations
   in hertz
17 printf("Frequency of oscillations f0 = %.2f kHz",f0
   /10^3);
```

Scilab code Exa 11.2 Calculation of frequency of oscillations for given circuit an

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 11 Oscillators and Multivibrators Pg no.
   356
3 clear;
4 clc;
5
6 //Given
7 //Figure E 11.1
8
9 L=20D-3;//colpitts inductance in henry
10 C1=0.2D-6;//colpitts capacitor C1 in farads
11 C2=0.02D-6;//colpitts capacitor C2 in farads
12 Qa=10;//Q point (a)
13 Qb=5;//Q point (b)
14
15 //Solution
16
17 Ce=C1*C2/(C1+C2);//equivalent capacitance in farads
18 disp("(a)");
19 f0=1/(2*%pi*sqrt(L*Ce))*sqrt(Qa^2/(Qa^2+1));//
   frequency of oscillations in hertz
20 printf("Q = %d\n",Qa);
21 printf("Frequency of oscillations f0 = %.f Hz",f0);
22
23 disp("(b)");
24 f0=1/(2*%pi*sqrt(L*Ce))*sqrt(Qb^2/(Qb^2+1));//
   frequency of oscillations in hertz
25 printf("Q = %d\n",Qb);
26 printf("Frequency of oscillations f0 = %.f Hz",f0);
27
28 //Round-off error in textbook
```

Scilab code Exa 11.3 Calculation of Q value for a crystal oscillator with given pa

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 11 Oscillators and Multivibrators Pg no.
   359
3 clear;
4 clc;
5
6 //Given
7
8 f=3.8D6;//frequency of oscillations in hertz
9 L=0.2;//equivalent inductance in henry
10 R=6000;//series resistance in ohms
11
12 //Solution
13
14 Q=2*%pi*f*L/R;//quality factor Q
15 printf("Q = %d\n",Q);
```

Scilab code Exa 11.4 Calculation of frequency of oscillations for given oscillator

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 11 Oscillators and Multivibrators Pg no.
   361
3 clear;
4 clc;
5
6 //Given
7
8 R=4.7D3;//R1,R2,R3 resistances in RC filter circuit
   in ohms
```

```

9 C=2.2D-9; //C1,C2,C3 resistances in RC filter circuit
   in farads
10
11 //Solution
12
13 f0=1/(2*%pi*R*C*sqrt(6)); //frequency of oscillation
   in hertz
14 printf("Frequency of oscillation f0 = %.3f kHz",f0
   /10^3);

```

Scilab code Exa 11.5 Calculation of oscillation frequency and feedback resistance

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 11 Oscillators and Multivibrators Pg no.
   361
3 clear;
4 clc;
5
6 //Given
7
8 R=4.7D3; //R1,R2,R3 resistances in RC filter circuit
   in ohms
9 C=4.7D-9; //C1,C2,C3 resistances in RC filter circuit
   in farads
10 A=29; //voltage gain of RC phase shift oscillator
11
12 //Solution
13
14 f0=1/(2*%pi*R*C*sqrt(6)); //frequency of oscillation
   in hertz
15 printf("Frequency of oscillation f0 = %.2f kHz\n ",
   f0/10^3);
16 Rf=A*R; //feedback resistance in ohms
17 printf("Feedback resistance Rf = %.1f kilo-ohms",Rf
   /10^3);

```

Scilab code Exa 11.6 Calculation of oscillation frequency for Wien Bridge oscillator

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 11 Oscillators and Multivibrators Pg no.
   367 and 368
3 clear;
4 clc;
5
6 //Given
7
8 f1=40; //lowest operating frequency in hertz
9 f2=40D3; //highest operating frequency in hertz
10 C1=40D-12; //lowest capacitance of variable capacitor
    in farads
11 C2=400D-12; //highest capacitance of variable
    capacitor in farads
12 A=10; //gain of amplifier
13 R2=7D3; //resistance of other arm of bridge in ohms
14
15 //Solution
16
17 R=1/(2*pi*f1*C2); //resistance R of Wien bridge
    oscillator in ohms
18 printf("Since ,capacitance can change in the ratio of
    10:1 only\n ");
19 printf("For R = %.2f Mega-ohms frequency range 40 Hz
    to 400 Hz\n ",R/10^6);
20 printf("For R = %.2f kilo-ohms frequency range 400
    Hz to 4 kHz\n ",R/10^5);
21 printf("For R = %.2f kilo-ohms frequency range 4 kHz
    to 40 kHz\n\n ",R/10^6);
22
23 AB=1; //loop gain is unity for oscillator
24 B=AB/A; //feedback factor beta
```

```

25 R1_to_R2=1/(1/3-B)-1; //ratio of R1/R2 for wien
    bridge oscillator
26 R1=R1_to_R2*R2; //resistor R1 in ohms
27 printf("Resistance R1 = %d kilo-ohms",R1/10^3);

```

Scilab code Exa 11.7 Calculation of oscillation frequency for astable mutivibrator

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 11 Oscillators and Multivibrators Pg no.
    368
3 clear;
4 clc;
5
6 //Given
7 //Figure 11.18
8
9 R1=1.5D3; //resistance R1 in ohms
10 R2=1.5D3; //resistance R2 in ohms
11 R3=12D3; //resistance R3 in ohms
12 R4=12D3; //resistance R4 in ohms
13 C1=0.068D-6; //capacitance C1 in farads
14 C2=0.068D-6; //capacitance C2 in farads
15
16 //Solution
17
18 T1=0.693*R3*C1; //time period of initial part of
    waveform in seconds
19 T2=0.693*R4*C2; //time period of final part of
    waveform in seconds
20 T=T1+T2; //total time period of waveform in seconds
21 f=1/T; //frequency of wave in hertz
22 printf("Frequency of oscillations of astable
    multivibrator f = %d Hz",f);

```

Chapter 12

Modulation and Demodulation

Scilab code Exa 12.1 Calculation of percentage modulation and amplitude of carrier

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 378
3 clear;
4 clc;
5
6 //Given
7
8 Emax=10;//maximum peak to peak voltage of an AM
   signal
9 Emin=3;//minimum peak to peak voltage of an AM
   signal
10
11 //Solution
12
13 m=(Emax-Emin)/(Emax+Emin);//modulation index m
14 printf("Percent modulation = %.2f %%\n\n",m*100);
15 Ac=(Emax-Emin)/(2*m);//amplitude of unmodulated
   carrier wave
16 printf("Amplitude of unmodulated carrier wave Ac = %
   .1f Volts",Ac);
```

Scilab code Exa 12.2 Calculations of sideband parameters and width for given AM wa

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 378
   and 379
3 clear;
4 clc;
5
6 //Given
7
8 fc=1000D3;//frequency of carrier wave in hertz
9 fa1=450;//lowest audio frequency of modulating
   signal in hertz
10 fa2=1650;//highest audio frequency of modulating
   signal in hertz
11
12 //Solution
13
14 disp("( i )");
15 FS=fa2-fa1;//frequency span of each sideband in
   hertz
16 printf("Frequency span of each sideband = %d Hz",FS)
   ;
17
18 disp("( ii )");
19 FMAX=fc+fa2;//maximum upper side frequency in hertz
20 printf("Maximum upper side frequency = %.2 f kHz",
   FMAX/10^3);
21
22 disp("( iii )");
23 FMIN=fc-fa2;//minimum upper side frequency in hertz
24 printf("Minimum upper side frequency = %.2 f kHz",
   FMIN/10^3);
25
```

```

26 disp("(iv)");
27 CW=FMAX-FMIN;//channel width in hertz
28 printf("Channel width = %.1f kHz",CW/10^3);

```

Scilab code Exa 12.3 Calculation of power developed by AM wave

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 379
3 clear;
4 clc;
5
6 //Given
7
8 RL=180;//load resistance in ohms
9 Vc=90;//peak voltage of carrier wave in volts
10 m=0.5;//modulation index of AM wave
11
12 //Solution
13
14 Pc=Vc^2/(2*RL);//unmodulated carrier power in watts
15 Pt=Pc*(1+m^2/2);//total power developed by AM wave
   in watts
16 Pcs=Pc*m^2/2;//power in sideband in watts
17 printf("Total power developed by AM wave Pt = %.4f
   Watts\n ",Pt);
18 printf("Power in sideband Pc = %.4f Watts",Pcs);

```

Scilab code Exa 12.4 Calculation of the modulation index and side lengths ratio fo

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 379
3 clear;
4 clc;

```

```

5
6 //Given
7
8 Vm=12; //modulating signal peak to peak voltage in
    volts
9 Vc=9; //carrier wave peak amplitude in volts
10
11 //Solution
12
13 Emax=Vc+Vm/2; //maximum amplitude of AM signal in
    volts
14 Emin=Vc-Vm/2; //minimum amplitude of AM signal in
    volts
15 m=(Emax-Emin)/(Emax+Emin); //depth of modulation
16 L1_to_L2=Emin/Emax; //ratio of side lengths
17 printf("Depth of modulation = %.2f %%\n",m*100);
18 printf("Ratio of side-lengths L1/L2 = %.1f",L1_to_L2
    );

```

Scilab code Exa 12.6 Plot of frequency spectrum and calculation of modulation index

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 380
3 clear;
4 clc;
5
6 //Given
7
8 fc=9D6; //frequency of carrier wave in hertz
9 Vc=9; //peak value of carrier wave in volts
10 fm=10D3; //frequency of modulating wave in hertz
11 Vm=4.5; //amplitude of modulating sine wave in volts
12

```

```

13 //Solution
14
15 m=Vm/Vc; //modulation index
16 printf("Modulation index m = %d %%",m*100);
17 fu=fc+fm; //upper side band frequency in hertz
18 fl=fc-fm; //lower side band frequency in hertz
19 f=[fc-2*fm fc-fm fc fc+fm fc+2*fm]; //frequency range
20 for i=1:5
21     if f(i)==fu | f(i)==fl then
22         A(i)=m*Vc/2; //amplitude of side frequency in
                volts
23     else
24         A(i)=0; //amplitude of side frequency in
                volts
25     end
26 end
27
28 bar(f/10^6,A,0.1,'red');
29 title("Frequency spectrum of AM wave");
30 xlabel("Frequency in MHz");
31 ylabel("Amplitude in volts");
32 xstring(8.988,2.3,"lower side band");
33 xstring(9.008,2.3,"upper side band");

```

Scilab code Exa 12.7 Calculation of the modulation index for given transmitter cur

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 380
   and 381
3 clear;
4 clc;
5
6 //Given
7
8 Ic=12; //rms current of unmodulated carrier in

```

```

    amperes
9  I=14; //rms current of modulated carrier in amperes
10
11 //Solution
12
13 m=sqrt(2*((I/Ic)^2-1)); //modulation index of AM wave
14 printf("Modulation index m = %.2f %%",m*100);

```

Scilab code Exa 12.8 Calculation of required audio power for given AM signal

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 381
3 clear;
4 clc;
5
6 //Given
7
8 Pc=10D3; //carrier wave power in watts
9 m=0.75; //depth of modulation
10 e=0.65; //efficiency of modulator
11
12 //Solution
13
14 Ps=0.5*m^2*Pc; //total sideband power in watts
15 Pa=Ps/e; //required audio power in watts
16 printf("Required audio power P = %.3f kW",Pa/10^3);

```

Scilab code Exa 12.9 Calculation of maximum carrier power for given transmission o

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 381
3 clear;
4 clc;

```

```

5
6 //Given
7
8 Pc1=12D3;//carrier wave power in watts
9 m1=0.75;//maximum modulation index that can be
    achieved
10 m2=0.45;//modulation index for AM wave
11
12 //Solution
13
14 Pt=Pc1*(1+m1^2/2);//total power of AM wave in watts
15 Pc2=Pt/(1+m2^2/2);//carrier power in watts for m=m2
16 printf("Carrier power can be raised to Pc = %.2f kW
    ",Pc2/10^3);

```

Scilab code Exa 12.10 Calculation of modulation index for given FM transmission

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 393
3 clear;
4 clc;
5
6 //Given
7
8 fc=150D6;//frequency of carrier wave in hertz
9 fm=10D3;//frequency of modulating wave in hertz
10 df=25D3;//maximum frequency deviation
11
12 //Solution
13
14 disp("(i)");
15 B=df/fm;//modulation index for FM wave
16 printf("Modulation index      = %.1f",B);
17 disp("(ii)");
18 printf("The three significant side frequency pairs

```

```

        are:\n ");
19 printf("%d MHz      %d kHz\n ",fc/10^6, fm/10^3);
20 printf("%d MHz      %d kHz\n ",fc/10^6, fm*2/10^3);
21 printf("%d MHz      %d kHz\n ",fc/10^6, fm*3/10^3);

```

Scilab code Exa 12.11 Calculation of bandwidth for given FM wave transmission

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 394
3 clear;
4 clc;
5
6 //Given
7
8 df=75D3;//maximum frequency deviation
9 fm=20D3;//frequency of modulating wave in hertz
10
11 //Solution
12
13 BW=2*(df+fm);//bandwidth for FM wave
14 printf("Bandwidth required in FM wave transmission B
        = %d kHz",BW/10^3);

```

Scilab code Exa 12.12 Calculation of average power output for a FM signal

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 12 Modulation and Demodulation Pg no. 394
3 clear;
4 clc;
5
6 //Given
7
8 df=6D3;//maximum frequency deviation

```

```

9  fm=1.5D3; //frequency of modulating wave in hertz
10 Pc=25; //carrier power in watts
11 J=[-0.4 -0.07 0.36 0.43 0.28 0.13 0.05 0.02]; //
    Bessel function values required for given problem
    's modulation index
12
13 //Solution
14
15 B=df/fm; //modulation index
16 PT=Pc*(J(1)^2+2*(J(2)^2+J(3)^2+J(4)^2+J(5)^2+J(6)^2+
    J(7)^2+J(8)^2)); //total carrier power in watts
17 printf("Total carrier power PT = %.f Watts",PT);

```

Chapter 13

Integrated Circuits

Scilab code Exa 13.1 Design of diffused resistors of given value

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 13 Integrated Circuit Pg no. 414
3 clear;
4 clc;
5
6 //Given
7
8 R_a=0.5D3;//diffused resistor value in ohms
9 R_b=10D3;//diffused resistor value in ohms
10 Rs_n=10;//n-type emitter diffusion sheet resistance
    in ohms
11 Rs_p=250;//p-type emitter diffusion sheet resistance
    in ohms
12
13 //Solution
14
15 disp("(a)");
16 L_to_W_a=R_a/Rs_n;//length to width ratio of
    resistor
17 printf(" Thus a %d ohm resistor of n-type emitter
    diffusion ,\n can be fabricated by using a pattern
```

```

        of\n ",R_a);
18 printf("%d mils long by 1 mil wide",L_to_W_a);
19
20 disp("(b)");
21 L_to_W_b=R_b/Rs_p;//length to width ratio of
    resistor
22 printf(" Thus a %d kilo-ohm resistor of p-type
    emitter diffusion,\n can be fabricated by using a
    pattern of\n ",R_b/10^3);
23 printf("%d mils long by 1 mil wide",L_to_W_b);

```

Chapter 14

Operational Amplifiers

Scilab code Exa 14.1 Calculation of output voltage for a balanced differential amp

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 418
3 clear;
4 clc;
5
6 //Given
7
8 vICM1=0; //input common mode vOltage in volts
9 vOCM1=5.4; //output common mode vOltage in volts
10 vICM2=1.05; //input common mode vOltage in volts
11 vOCM2=5.0; //output common mode vOltage in volts
12 vO2=5.4; //vOltage at collector of transistor Q2 in
    volts
13
14 //Solution
15
16 disp("vOCM=5.4 Volts");
17 vO1=2*vOCM1-vO2; //vOltage at collector of transistor
    Q1 in volts
18 printf("Voltage at collector of transistor Q1 vO1 =
    %.1f volts\n ",vO1);
```

```

19
20 disp("vOCM=5.0 Volts");
21 vO1=2*vOCM2-vO2; //vOltage at collector of transistor
    Q1 in volts
22 printf("Voltage at collector of transistor Q1 vO1 =
    %.1f volts",vO1);
23
24 //calculation for vOCM=5 Volts not done in textbook

```

Scilab code Exa 14.2 Calculation of input and output common mode voltage for given

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 418
3 clear;
4 clc;
5
6 //Given
7
8 vI1=1.15; //voltage at base of transistor Q1 in volts
9 vI2=0.95; //voltage at base of transistor Q2 in volts
10 vO1=2; //voltage at collector of transistor Q1 in
    volts
11 vO2=8; //voltage at collector of transistor Q2 in
    volts
12
13 //Solution
14
15 vICM=(vI1+vI2)/2; //input common mode voltage in
    volts
16 vOCM=(vO1+vO2)/2; //output common mode voltage in
    volts
17 printf("Input common mode voltage vICM = %.2f Volts\
    n ",vICM);
18 printf("Output common mode voltage vOCM = %.1f Volts
    ",vOCM);

```

Scilab code Exa 14.3 Calculation of output common mode voltage for given balanced

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 418 and
   419
3 clear;
4 clc;
5
6 //Given
7
8 vI1=0;//voltage at base of transistor Q1 in volts
9 vI2p=5D-3;//peak voltage at base of transistor Q2 in
   volts
10 vI2w=0.2;//frequency of vI2 in hertz
11 vICM_a=0;//input common mode voltage in volts
12 vOCM_a=5;//output common mode voltage in volts
13 vICM_b=-2D-3;//input common mode voltage in volts
14 vOCM_b=5.01;//output common mode voltage in volts
15 vICM_c=2D-3;//input common mode voltage in volts
16 vOCM_c=4.99;//output common mode voltage in volts
17
18 //Solution
19
20 dvICMp=vI2p/2;//peak input common mode voltage in
   volts
21 dvICMw=vI2w;//input common mode frequency in hertz
22 printf("vICM = %.1f sin(%.1f pi t) mV\n",dvICMp
   *10^3,dvICMw*2);
23 dvOCMp=(vOCM_b-vOCM_a)/vICM_b*dvICMp;//peak output
   common mode voltage in volts
24 dvOCMw=dvICMw;//output common mode frequency in
   hertz
25 printf("vOCM =5 V %.f sin(%.1f pi t) mV",dvOCMp
   *10^3,dvOCMw*2);
```

26

27 //error in calculation of vOCM in textbook

Scilab code Exa 14.4 Calculation of common mode gain for a balanced differential a

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 418
3 clear;
4 clc;
5
6 //Given
7
8 vI1=[-3.3 1.9]; //voltage at base of transistor Q1 at
    instants T1 and T2 in volts
9 vI2=[-3.7 1.1]; //voltage at base of transistor Q2 at
    instants T1 and T2 in volts
10 vO1=[4.3 2.7]; //voltage at collector of transistor
    Q1 at instants T1 and T2 in volts
11 vO2=[4.5 3.1]; //voltage at collector of transistor
    Q2 at instants T1 and T2 in volts
12
13 //Solution
14
15 vICM=((vI1(2)-vI1(1))+(vI2(2)-vI2(1)))/2; //input
    common mode voltage in volts
16 vOCM=((vO1(2)-vO1(1))+(vO2(2)-vO2(1)))/2; //output
    common mode voltage in volts
17 ACM=vOCM/vICM; //common mode gain
18 printf("Common mode gain ACM = %.2 f",ACM);
```

Scilab code Exa 14.5 Calculation of CMRR in dB units for given operational amplifi

```
1 //Tested on Windows 7 Ultimate 32-bit
```

```

2 //Chapter 14 Operational Amplifiers Pg no. 423
3 clear;
4 clc;
5
6 //Given
7
8 Ad=15000; //differential gain
9 Ac=15; //common mode gain
10
11 //Solution
12
13 CMRR=Ad/Ac; //common mode rejection ratio
14 CMRR_dB=20*log10(CMRR); //common mode rejection ratio
    in dB units
15 printf("(CMRR)dB = %.f dB",CMRR_dB);

```

Scilab code Exa 14.6 Calculation of slew rate for given operational amplifier

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 425 and
    426
3 clear;
4 clc;
5
6 //Given
7
8 V1=-10.8; //output at time instant t1 in volts
9 V2=10.8; //output at time instant t2 in volts
10 t2_t1=2D-6; //time gap between t1 and t2 in seconds
11
12 //Solution
13
14 SR=(V2-V1)/t2_t1/10^6; //slew rate in Volts/micro-
    seconds
15 printf("Slew Rate S.R. = %.1f V/ S ",SR);

```

Scilab code Exa 14.7 Calculation of feedback resistance for given opamp closed loop

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 428 and
   429
3 clear;
4 clc;
5
6 //Given
7 //Figure E 14.7
8
9 Av_cl=50;//closed loop voltage gain
10 Ri=2.7D3;//resistance Ri in ohms
11
12 //Solution
13
14 Rf=Av_cl*Ri;//feedback resistance in ohms
15 printf("Feedback resistor Rf = %d kilo-ohms",Rf
   /10^3);
```

Scilab code Exa 14.8 Calculation of input and output impedances for given operation

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 429
3 clear;
4 clc;
5
6 //Given
7 //Figure E 14.7
8
9 Av_ol=200000;//open loop voltage gain
```

```

10 Zin=5; //input impedance in ohms
11 Zout=50; //output impedance in ohms
12 Ri=2.7D3; //resistance Ri in ohms
13 Rf=135D3; //feedback resistance in ohms
14
15 //Solution
16
17 Zin=Ri; //input impedance of amplifier in ohms
18 Zout_miller=Rf*Av_ol/(1+Av_ol); //miller output
    impedance in ohms
19 Zout_total=1/(1/Zout+1/Zout_miller); //total output
    impedance of amplifier in ohms
20 printf("Input impedance Zin = %.1f kilo-ohms\n ",Zin
    /10^3);
21 printf("Output impedance Zout = %.f ohms",Zout_total
    );

```

Scilab code Exa 14.9 Calculation of closed loop voltage gain and input and output

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 431 and
    432
3 clear;
4 clc;
5
6 //Given
7
8 A=175000; //open loop voltage gain
9 Zin=1.5D6; //input impedance in ohms
10 Zout=70; //output impedance in ohms
11 Ri=8.2D3; //resistance Ri in ohms
12 Rf=180D3; //feedback resistance in ohms
13
14 //Solution
15

```

```

16 X=Ri/(Ri+Rf); //voltage divider ratio
17 Zin_n=Zin*(1+A*X); //input impedance in ohms
18 Zout_n=Zout/(1+A*X); //output impedance in ohms
19 Av_cl=1/X; //closed loop voltage gain
20 printf("Input impedance Zin = %.f Mega-ohms\n ",
        Zin_n/10^6);
21 printf("Output impedance Zout = %.4f ohms\n ",Zout_n
        );
22 printf("Closed loop voltage gain (Av)cl = %.f",Av_cl
        );

```

Scilab code Exa 14.10 Calculation of input and output impedances for given operati

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 432
3 clear;
4 clc;
5
6 //Given
7
8 Av_ol=175000; //open loop voltage gain
9 Zin=1.5D6; //input impedance in ohms
10 Zout=70; //output impedance in ohms
11
12 //Solution
13
14 Zi_vf=(1+Av_ol)*Zin; //input impedance of voltage
        follower in ohms
15 Zo_vf=Zout/(1+Av_ol); //output impedance of voltage
        follower in ohms
16 printf("Input impedance (Zi)VF = %.f Mega-ohms\n ",
        Zi_vf/10^6);
17 printf("Output impedance (Zo)VF = %.4f ohms\n ",
        Zo_vf);

```

Scilab code Exa 14.11 Calculation of oscillation frequency and feedback resistance

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 435 and
   436
3 clear;
4 clc;
5
6 //Given
7 //Figure 14.21
8
9 R=12D3; //resistances R1,R2,R3 in RC network in ohms
10 C=0.001D-6; //capacitances C1,C2,C3 in RC network in
   ohms
11 A=29; //gain for oscillator operation
12
13 //Solution
14
15 fr=1/(2*%pi*R*C*sqrt(6)); //frequency of oscillations
   in hertz
16 Rf=A*R; //feedback resistance in ohms
17 printf("Frequency of oscillations fr = %.2f kHz\n ",
   fr/10^3);
18 printf("Feedback resistance Rf = %.f kilo-ohms\n ",
   Rf/10^3);
```

Scilab code Exa 14.13 Calculation of output voltage for given conditions in a summing

```
1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 442
3 clear;
4 clc;
```

```

5
6 //Given
7 //Figure 14.32
8
9 V1=2;V2=1;V3=0.5;V4=0.2;//input voltages in volts
10 R=20D3;//input resistances R1,R2,R3,R4 in ohms
11 R5=20D3;//feedback resistance in ohms
12
13 //Solution
14
15 A=-R5/R;//gain for each input
16 disp("(a)");
17 Vo=A*(V1+V2+V3+V4);//output voltage in volts
18 printf("Normal output voltage Vo = %.1f Volts",Vo);
19 disp("(b)");
20 Vo=A*(V1+V2+V4);//output voltage in volts
21 printf("For R3 open, output voltage Vo = %.1f Volts"
        ,Vo);
22 disp("(c)");
23 printf("If resistor R5 opens output becomes -Vsat.")

```

Scilab code Exa 14.14 Calculation of output voltage for given conditions in a summing amplifier

```

1 //Tested on Windows 7 Ultimate 32-bit
2 //Chapter 14 Operational Amplifiers Pg no. 442 and
   443
3 clear;
4 clc;
5
6 //Given
7 //Figure 14.33
8
9 V1=2;V2=1;V3=5.5;V4=2.2;V5=1.1//input voltages in
   volts
10 R=50D3;//input resistances R1,R2,R3,R4 in ohms

```

```

11 R5=10D3; //feedback resistance in ohms
12
13 //Solution
14
15 A=-R5/R; //gain for each input
16 disp(" (a) ");
17 Vo=A*(V1+V2+V3+V4+V5); //output voltage in volts
18 printf("Normal output voltage Vo = %.2f Volts",Vo);
19 disp(" (b) ");
20 Vo=A*(V1+V2+V4+V5); //output voltage in volts
21 printf("For R3 open, output voltage Vo = %.2f Volts"
    ,Vo);

```
