

Scilab Textbook Companion for
Integrated Electronics: Analog And Digital
Circuits and Systems
by J. Millman And C. C. Halkias¹

Created by
Shivam
B-Tech
Electronics Engineering
Institute of Technology, BHU
College Teacher
Arif Jamal
Cross-Checked by

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Integrated Electronics: Analog And Digital Circuits and Systems

Author: J. Millman And C. C. Halkias

Publisher: Tata McGraw - Hill Education, New Delhi

Edition: 50

Year: 1991

ISBN: 978-0-07-462245-2

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Energy Band in Solid	5
2 Transport Phenomena in Semiconductor	7
5 Transistor Characteristic	11
6 Digital Circuits	19
7 Integrated Circuit Fabrication and Characteristic	32
8 The Transistor at Low Frequency	36
9 Transistor Biasing and Thermal Stabilization	43
10 Field Effect Transistor	54
12 MultiStage Amplifiers	62
13 Feedback Amplifier	64
14 Stability and Oscillators	79
15 Operational Amplifier	82

16 Integrated Circuits as Analog System Building blocks	86
18 Power Circuits and Systems	98

List of Scilab Codes

Exa 1.1	Plane Parallel plate Capacitor	5
Exa 2.1.a	Using Avogadro no find the numerical value of concentration of atom in Germanium	7
Exa 2.1.b	Resistivity of intrinsic Germanium	8
Exa 2.1.c	Resistivity with given condition in germanium atoms	8
Exa 2.1.d	Ratio of Conductivities	9
Exa 5.1.a	To find transistor currents for npn transistor	11
Exa 5.1.b	To find transistor currents for npn transistor after adding resistor to circuit	12
Exa 5.2.a	Check whether transistor is in saturation re- gion or not	14
Exa 5.2.b	Check whether transistor is in saturation re- gion or not after adding a Emitter Transistor	15
Exa 6.1	Output Levels for a given input in a silicon transistor	19
Exa 6.2	To verify given equation	20
Exa 6.3.a	To find wether a given circuit is positive NAND	21
Exa 6.3.b	To find wether with given conditions NAND gate is satisfied	22
Exa 6.3.c	Silicon Transistors and diodes are used in pos- itive NAND	23
Exa 6.4	To verify that AND OR topology is equiva- lent to NAND NAND system	24
Exa 6.5.a	To find hFemin	25
Exa 6.5.b	When atleast one input is at V0 in NAND gate	27
Exa 6.5.c	If input is high in NAND gate	28
Exa 6.5.d	If input is low in NAND gate	29

Exa 6.6	Calculation of FAN OUT of NAND gate	30
Exa 7.1	Diffusion of a pn junction	32
Exa 7.2.a	Fabrication and Characteristics	33
Exa 7.2.b	Fabrication and Characteristics	34
Exa 8.2	transistor as a Common Emitter Amplifier	36
Exa 8.3	To derive output impedance of given figure in open circuit voltage short circuit current theorem	37
Exa 8.4	Parameters of a Common Emitter Amplifier	38
Exa 8.5	CE CC configuration	39
Exa 8.6	Parameters of CE CC configuration	41
Exa 9.1	To find Q point	43
Exa 9.2	To find resistances in 2N335 transistor	44
Exa 9.3.a	Variation of I_c in given Transistor	45
Exa 9.3.b	Variation of I_c in given Transistor	47
Exa 9.4	To design a self bias circuit	49
Exa 9.5	Value of theta for Ge Transistor	51
Exa 9.6.a	To find parameters of power amplifier using pnp germanium transistor	51
Exa 9.6.b	To find parameters of power amplifier using pnp germanium transistor	52
Exa 10.1.a	Pinch off V and channel half width of silicon FET	54
Exa 10.1.b	Pinch off V and channel half width of silicon FET	55
Exa 10.2.a	Amplifier using n channel FET	55
Exa 10.2.b	Amplifier using n channel FET	56
Exa 10.2.c	Amplifier using n channel FET	57
Exa 10.2.d	Amplifier using n channel FET	57
Exa 10.3.a	To find the parameters of a FET 2N3684	58
Exa 10.3.b	To find the range of possible values of I_d in FET 2N3684 from the graph	59
Exa 10.4	Voltage Gain of MOSFET as a single stage and then as first transistor	60
Exa 12.1.a	Minimum value of coupling capacitance for a given FET	62
Exa 12.1.b	Minimum value of coupling capacitance for a given FET	63

Exa 13.1	parameters of a Second collector to first emitter feedback amplifier	64
Exa 13.2.a	To find parameters of Current series Feedback Amplifier	66
Exa 13.2.b	To find parameters of Current series Feedback Amplifier	66
Exa 13.2.c	To find parameters of Current series Feedback Amplifier	68
Exa 13.2.d	To find parameters of Current seris Feedback Amplifier	69
Exa 13.3.a	Gain of second emitter to first basefeedback pair	70
Exa 13.3.b	Gain of second emitter to first basefeedback pair	71
Exa 13.3.c	Gain of second emitter to first basefeedback pair	72
Exa 13.3.d	Gain of second emitter to first basefeedback pair	73
Exa 13.4.a	To find gain and resistance of Voltage Shunt Feedback	75
Exa 13.4.b	To find gain and resistance of Voltage Shunt Feedback	76
Exa 13.4.c	To find gain and resistance of Voltage Shunt Feedback	77
Exa 14.1.a	Lowest poles of an Amplifier	79
Exa 14.1.b	Frequency Response Peak	80
Exa 15.1.a	difference in output voltage for two set of output signals	82
Exa 15.1.b	difference in output voltage for two set of output signals	83
Exa 15.2	Design an amplifier using yA702A	84
Exa 16.1	Fourth Order Butterworth Filter	86
Exa 16.2	Design a second order bandpass filter	87
Exa 16.3	Design a video amplifier using MC1550	88
Exa 16.4.a	Logic Level Output of an ECL gate	89
Exa 16.4.b	Calculation of noise margin	91
Exa 16.4.c	Verify that conducting transistor is in active region	92

Exa 16.4.d	Calculation of R	94
Exa 16.4.e	Average power dissipated by the gate	95
Exa 18.1.a	Design a series regulated power supply	98
Exa 18.1.b	Calculation of S_v	100
Exa 18.1.c	Find output resistance R_o	101
Exa 18.1.d	Calculation of change in output voltage due to change in input voltage and load current	103
Exa 18.2.a	SCR half wave power control circuit	105
Exa 18.2.b	SCR half wave power control circuit	106
Exa 18.2.c	SCR half wave power control circuit	107
Exa 18.3	SCR Relaxation Oscillator Phase control Cir- cuit	108

Chapter 1

Energy Band in Solid

Scilab code Exa 1.1 Plane Parallel plate Capacitor

```
1 clear;
2 clc;
3
4 //Caption: Plane Parallel plate Capacitor
5 //Given Data
6 d=0.001;//distance between parallel plate in m
7 V=1000;//applied voltage
8 q=1.6*(10^-19);//charge on an electron
9 m = 9.1*(10^-31);//mass of electron in kg
10 //Time taken by electron to reach other side of
    parallel plate capacitor
11 E=V/d;//Electric Field in V/m
12 //Formulae : s = u*t + (a*t^2)/2
13 a = (q*E)/m;//acceleration on electron in m/s^2
14 t = (2*d/a)^0.5;//time taken to reach the other side
    of plate
15 disp('sec ',t,'Time taken to reach other side = ');
16
17 //Magnitude of force exerted on electron
18 disp('Since the potential is constant the force will
    be constant between the paltes of capacitor');
```

```
19 F=q*E; //force
20 disp('N',F,'Force on electron = ');
21
22 //Velocity of electron at the other plate
23 //Formulae: v = u + a*t
24 v = a*t;//velocity at the end of other plate
25 disp('m/sec',v,'v=');
26
27
28 //end
```

Chapter 2

Transport Phenomena in Semiconductor

Scilab code Exa 2.1.a Using Avogadro no find the numerical value of concentration of atom in Germanium

```
1 clear;
2 clc
3
4 //Example 2a
5 //Using Avogadro no. find the numerical value of
   concentration of atom in Germanium
6
7 //Given Values
8
9 Av=6.02*(10^23) //Avogadro No.
10 m=72.6 //Molar mass of germanium in gm/moles
11 d=5.32 //density in gm/cm^3
12
13 conc = (Av/m)*d //Concentration of atom in germanium
14
15 disp('atom/cm^3',conc,'The concentration of
   germanium atom is=');
16
17 //End
```

Scilab code Exa 2.1.b Resistivity of intrinsic Germanium

```
1 clear;
2 clc
3
4 //Example 2b
5 //To find the resistivity of intrinsic germanium at
6 // 300K
7 // Given Values
8
9 Av=6.02*(10^23) //Avogadro No.
10 m=72.6 //Molar mass of germanium in gm/moles
11 d=5.32 //density in gm/cm^3
12 ni=2.5*(10^13); //in cm^-3
13 n=ni;
14 p=ni; //n=magnitude of free electrons , p=magnitude of
       // holes , ni=magnitude of intrinsic concentration
15 q=1.6*(10^-19); //Charge of an Electron
16 yn=3800; //in cm^2/V-s
17 yp=1800; //in cm^2/V-s
18
19 //Required Formula
20 A=ni*q*(yn+yp); //Conductivity
21 disp('ohm-cm^-1',A,'Conductivity is =');
22
23 R =1/A // Resistivity
24 disp('ohm-cm',R,'Resistivity is =');
25
26 //End
```

Scilab code Exa 2.1.c Resistivity with given condition in germanium atoms

```

1 clear;
2 clc;
3
4 disp('We know that n=p=ni where n is conc of free
      electron p is conc of holes and ni is conc of
      intrinsic carriers');
5 //Given data
6 //Resistivity if 1 donor atom per 10^8 germanium
      atoms
7 Nd=4.41*(10^14); //in atoms/cm^3
8 ni=2.5*(10^13); //in cm^3
9 yn=3800; //in cm^2/V-s
10 q=1.6*(10^-19);
11
12 n=Nd;
13 p=(ni^2)/Nd;
14
15 disp('holes/cm^3',p,'the concentration of holes is='
      );
16 if(n>p)
17     A=n*q*yn; //Conductivity
18     disp('ohm-cm^-1',A,'The conductivity is =');
19 end
20
21 R=1/A; //Resistivity
22 disp('ohm-cm',R,'The resistivity is=');
23
24
25 //End

```

Scilab code Exa 2.1.d Ratio of Conductivities

```

1 clear;
2 clc;
3

```

```

4 disp('We know that n=p=ni where n is conc of free
      electron p is conc of holes and ni is conc of
      intrinsic carriers');
5 //Given data
6 //Ratio of Conductivities
7 Nd=4.41*(10^14); //in atoms/cm^3
8 ni=2.5*(10^13); //in cm^3
9 yn=3800; //in cm^2/V-s
10 q=1.6*(10^-19);
11
12 n=Nd;
13 A=n*q*yn; //Conductivity
14
15 //If germanium atom were monovalent metal , ratio of
      conductivity to that of n-type semiconductor
16
17 n=4.41*(10^22); //in electrons/cm^3
18
19 disp('If germanium atom were monovalent metal');
20 A1=n*q*yn;
21 disp('ohm=cm^-1',A1,'the conductivity of metal is=');
22
23 F=A1/A;
24 disp(F,'The factor by which the conductivity of metal
      is higher than that of n type semiconductor is')
      ;
25
26 //End

```

Chapter 5

Transistor Characteristic

Scilab code Exa 5.1.a To find transistor currents for npn transistor

```
1 clear;
2 clc;
3
4 //Example 1.1
5 //Caption : Program to find transistor currents for
      npn transistor .
6
7 //Given Values
8
9 //Silicon Transistor
10 B=100;    //Beta
11 Ico=20;   //in nA
12 Rc=3;
13 Rb=200;
14 Vbb=5;    //in V
15 Vcc=10;   //in V
16 Vbe=0.7;  //in Active region
17
18 //Applying KVL to base circuit
19
20 //Vbb+Rb*Ib+Vbe=0
```

```

21
22 Ib=(Vbb-Vbe)/Rb; // in mA
23
24 //Ico<<Ib
25
26 Ic=B*Ib; // in mA
27
28 //To verify the Active region Assumption
29
30 //Vcc+Rc*Ic+Vcb+Vbe=0
31
32 Vcb=(-Rc*Ic)+Vcc-Vbe; // in V
33
34 disp('V',Vcb,'Vcb = ');
35
36 if(Vcb>0)
37     disp('Positive value of Vcb represents reversed
           biased collector junction and Transistor in
           active region');
38 end
39
40 disp('mA',Ic,'Current in transistor(Ic) is ');
41
42 disp('mA',Ib,'Current in transistor(Ib) is ');
43
44 //End

```

Scilab code Exa 5.1.b To find transistor currents for npn transistor after adding resistor to circuit.

```

1 clear;
2 clc;
3
4 //Example 1.2
5 //Caption : Program to find transistor currents for
           npn transistor after adding resistor to circuit.

```

```

6
7 // Given Values
8
9 // Silicon Transistor
10 B=100; //Beta
11 Ico=20; //in nA
12 Rc=3;
13 Ico=20; //in nA
14 Rb=200;
15 Re=2;
16 Vbb=5; //in V
17 Vcc=10; //in V
18 Vbe=0.7; //in Active region
19
20 //Ico<<Ib Assuming
21
22 // Itot=Ib+Ic=Ib+B*Ib=(B+1)*Ib
23
24 // Applying KVL to base circuit
25
26 //Vbb+Rb*Ib+Vbe+Re*Itot=0
27
28 Ib=(Vbb-Vbe)/(Rb+(Re*(B+1))); //in mA
29
30 Ic=B*Ib; //in mA
31
32 //Hence Ico<<Ib
33
34 //To verify the Active region Assumption
35
36 //Vcc+Rc*Ic+Vcb+Vbe=0
37
38 Vcb=(-Rc*Ic)+Vcc-Vbe-(Re*(B+1)*Ib); //in V
39
40 disp('V',Vcb,'Vcb = ');
41
42 if(Vcb>0)
43 disp('Positive value of Vcb represents reversed

```

```

        biased collector junction and Transistor in
        active region');

44 end
45
46 disp('mA',Ic,'Current in transistor(Ic) is ');
47
48 disp('mA',Ib,'Current in transistor(Ib) is ');
49
50
51 //End

```

Scilab code Exa 5.2.a Check whether transistor is in saturation region or not

```

1 clear;
2 clc;
3
4 //Caption : Program to find transistor currents for
        npn transistor and check whether transistor is in
        saturation region or not.
5
6 //Given Values
7
8 //Silicon Transistor
9
10 Rc=3;
11 Rb=50;
12 Vbb=5;    //in V
13 Vcc=10;   //in V
14 Vce=0.2;  //in V
15 Vbe=0.8;  //in Active region
16 hFE=100;
17
18 //Assuming transistor in saturated region
19
20 //Applying KVL to base circuit

```

```

21
22 //Vbb+Rb*Ib+Vbe=0
23
24 Ib=(Vbb-Vbe)/Rb; //in mA
25
26 //Applying KVL to Collector circuit
27
28 //Vcc+Rc*Ic+Vce=0
29
30 Ic=(Vcc-Vce)/Rc; //in mA
31
32 Ib_min=Ic/hFE;
33
34 disp('mA', Ib_min, 'Minimum Ib = ');
35
36 if(Ib>Ib_min)
37     disp('Transistor in saturated Region');
38 end
39
40 disp('mA', Ic, 'Current in transistor (Ic) is ');
41
42 disp('mA', Ib, 'Current in transistor (Ib) is ');
43
44
45 //End

```

Scilab code Exa 5.2.b Check whether transistor is in saturation region or not after adding a Emitter Transistor .

```

1 clear;
2 clc;
3
4 //Caption : Program to find transistor currents for
        //npn transistor and check whether transistor is in
        //saturation region or not after adding a Emitter
        //Transistor .

```

```

5
6 // Given Values
7
8 // Silicon Transistor
9
10 Beta=100;      //Beta
11 Rc=3;
12 Rb=50;
13 Re=2;
14 Vbb=5;        //in V
15 Vcc=10;        //in V
16 Vce=0.2;       //in V
17 Vbe=0.8;       //in Active region
18 hFE=100;
19
20 //Assuming transistor in saturated region
21
22 // Applying KVL to base circuit
23
24 // -Vbb+Rb*Ib+Vbe+Re*(Ic+Ib)=0
25
26 // Simplifying (Rb+Re)Ib+Re*Ic=Vbb-Vbe
27
28 // Applying KVL to Collector circuit
29
30 // -Vcc+Rc*Ic+Vce+Re*(Ic+Ib)=0
31
32 // Simplifying Re*Ib+(Rc+Re)Ic=Vcc-Vce
33
34
35 A=[(Rb+Re) Re ,Re ,(Rc+Re)];
36 B=[(Vbb-Vbe);(Vcc-Vce)];
37 X=A\B;
38 Ib=X(1);
39 Ic=X(2);
40
41 Ib_min=Ic/hFE;
42

```

```

43 disp('mA', Ib_min, 'Minimum Ib = ');
44
45
46 disp('mA', Ic, 'Current in transistor (Ic)');
47
48 disp('mA', Ib, 'Current in transistor (Ib)');
49
50 if(Ib>Ib_min)
51     disp('Transistor in Saturated Region');
52 else
53     disp('Transistor not in Saturated Region. Hence
54         must be operating in Active region');
55 end
56
57 // Ico<<Ib Assuming
58 // Itot=Ib+Ic=Ib+B*Ib=(B+1)*Ib
59
60 // Applying KVL to base circuit
61
62 //Vbb+Rb*Ib+Vbe+Re*Itot=0
63
64 Ib=(Vbb-Vbe)/(Rb+(Re*(Beta+1))); // in mA
65
66 Ic=Beta*Ib; // in mA
67
68 //Hence Ico<<Ib
69
70 //To verify the Active region Assumption
71
72 //Vcc+Rc*Ic+Vcb+Vbe=0
73
74 Vcb=(-Rc*Ic)+Vcc-Vbe-(Re*(Beta+1)*Ib); // in V
75
76 disp('V', Vcb, 'Vcb = ');
77
78 if(Vcb>0)
79     disp('Positive value of Vcb represents reversed

```

```
biased collector junction and Transistor in
active region');
80 end
81
82 disp('mA',Ic,'Current in transistor(Ic) is ');
83
84 disp('mA',Ib,'Current in transistor(Ib) is ');
85
86
87
88 //End
```

Chapter 6

Digital Circuits

Scilab code Exa 6.1 Output Levels for a given input in a silicon transistor

```
1 clear;
2 clc;
3
4 //Caption:Output Levels for a given input in a
      silicon transistor
5 //Given Data
6 R1=15; //in K
7 R2=100; //in K
8 //R1 and R2 are voltages at base which acts as
      potential divider
9 Rc=2.2; //voltage at collector in K
10 hfe=30;
11
12 //For vi=0
13 Vb = (R1/(R1+R2))*(-12); //Voltage at base in V
14 disp('V',Vb,'Vb=');
15 //A bias of 0V is required to cut off a silicon
      emitter junction transistor given in table
16 Vo = 0; //in V
17 disp('Vo',Vo,'Vo = ');
18
```

```

19 //For vi=12
20 vi=12; //in V
21 //Few standard values for silicon transistor
22 Vbesat=0.8; //in V
23 Vcesat=0.2; //in V
24 //Assumption: Q is in saturation region
25 Ic = (vi-Vcesat)/Rc; //Collector Current
26 disp('mA',Ic,'Ic=');
27 Ibmin=(Ic/hfe); //Mininmum current at the base
28 disp('mA',Ibmin,'Ibmin=');
29 I1=(vi-Vbesat)/R1; //Current in R1
30 I2=(Vbesat-(-12))/100; //Current in R2
31 Ib = I1-I2; //Base current
32 disp('mA',Ib,'Ib=');
33
34 if(Ib>Ibmin)
35     disp('Since Ib>Ibmin , The transistor is in
            saturation region and drop is Vcesat');
36     vo=Vcesat;
37     disp('V',vo,'vo=');
38 end
39
40 //end

```

Scilab code Exa 6.2 To verify given equation

```

1 clear;
2 clc;
3
4 //Caption: To verify given equation
5
6 disp('NOTE: We will write A with a bar on its top as
      a ');
7 disp('To verify ');
8 disp(' A + aB = A + B');

```

```

9
10 disp('We know that B + 1 = 1 and A1 = A');
11 disp('A + aB = A(B+1) + aB = AB + A + aB =');
12 disp('(A + a)B + A = B + A');
13 disp('which is equal to RHS')
14 //end

```

Scilab code Exa 6.3.a To find whether a given circuit is positive NAND

```

1 clear;
2 clc;
3
4 //Caption:To find whether a given circuit is positive
        NAND
5 //Given Data
6 R=15; //in K
7 R1=15; //in K
8 R2=100; //in K
9 R3=2.2; //in K
10 V0=0; //in V
11 V1=12; //in V
12 Vcc=12; //in V
13
14 //If input is at V0=0V
15 Vb = -Vcc*(R1/(R1+R2)); //The base voltage of the
        transistor
16 disp('V',Vb,'The base voltage of transistor Vb=');
17 if(Vb<0)
18     disp('Q is cutoff and Y is at 12V');
19     disp('The result confirms the first three rows
        of truth table');
20 end
21
22 //If input is at V1 = 12V
23 //Assumption:All the diodes are reversed biased and

```

```

        transistor is in saturation
24 //If Q is in saturation
25 Vbe=0; //in V
26 Vp = V1*(R/(R+R1)); //voltage at point P in front of
    all diodes
27 disp(Vp, 'All diodes are reversed biased by');
28 Iq = (V1/(R+R1)-(V1/R2)); //The base current of Q
29 Ic=V1/R3; //Current in the collector junction
30 disp('mA', Ic, 'Ic=');
31 hFEmin = Ic/Iq;
32 disp(hFEmin, 'hFEmin=');
33 disp(hFEmin, 'When hFE >');
34 disp('Under these condition the output is at ground
    and this satisfies the first three rows of truth
    table');

35
36
37 //end

```

Scilab code Exa 6.3.b To find wether with given conditions NAND gate is satisfied

```

1 clear;
2 clc;
3
4 //Caption://To find wether with given conditions
    NAND gate is satisfied
5 //Given Data
6 R=15; //in K
7 R1=15; //in K
8 R2=100; //in K
9 R3=2.2; //in K
10 V0=0; //in V
11 V1=12; //in V
12 Vcc=12; //in V
13

```

```

14 // If input is at V0=0V
15 Vb = -Vcc*(R1/(R1+R2)); //Base Current in V
16
17 //Finding thevenin equivalent from P to ground
18 Rd = 1; //in K
19 Vd=0.7; //in v
20 Vr=1; //in K
21 //Thevenin Equivallent Voltage and resistance from P
   to ground
22 v = (Vcc*(Rd/(Rd+R)))+(Vd*(R/(R+Rd)));
23 rs = Rd*(R/(R+Rd));
24 //Open Circuit Voltage at base of the transistor
25 Vb1 = (-Vcc*((R1+rs)/(R1+R2+rs))) + (v*(R2/(R1+R2+rs
      )));
26 disp('V',Vb1,'Vb1=');
27 if(Vb1>Vb)
28     disp('The voltage is adequate to reverse bias Q'
          );
29 end
30
31
32 //end

```

Scilab code Exa 6.3.c Silicon Transistors and diodes are used in positive NAND

```

1 clear;
2 clc;
3
4 //Caption: Silicon Transistors and diodes are used in
   positive NAND
5 //Given Data
6 R=15; //in K
7 R1=15; //in K
8 R2=100; //in K
9 R3=2.2; //in K

```

```

10 V0=0; //in V
11 V1=12; //in V
12 Vcc=12; //in V
13
14 //To find wether with given conditions NANAD gate is
   satisfied
15 //Finding thevenin equivalent from P to ground
16 Rd = 1; //in K
17 Vd=0.7; //in v
18 Vr=1; //in K
19 v = (Vcc*(Rd/(Rd+R)))+(Vd*(R/(R+Rd)));
20 rs = Rd*(R/(R+Rd));
21
22 //If the inputs are high
23
24 Vcesat = 0.2; //in V
25 Vb2 = (-Vcc*(R1/(R1+R2)) + ((Vd+Vcesat)*R2/(R1+R2)))
;
26 disp('V',Vb2,'Vb2=');
27 disp('It cuts off Q Y=1 ');
28
29 //end

```

Scilab code Exa 6.4 To verify that AND OR topology is equivalent to NAND NAND sys

```

1 clear;
2 clc;
3
4 //Caption: To verify that AND-OR topology is
   equivalent to NAND-NAND system
5 disp('In digital electronics we have to come across
   situations where we need to use an input with a
   bar but here we will denote as ');
6 disp('X with a bar = Xb and X with two bars = Xbb');
7

```

```

8 // Solution
9 disp('We know that X =Xbb');
10 disp('For AND OR logic the output of AND and
    simultaneously neglecting the input to following
    OR does not change the logic');
11 disp('We have also neglected the output of the OR
    gate and at the same time have added an INVERTER
    so that logic is once again unaffected');
12 disp('AN OR gate neglected at each terminal is an an
    AND circuit');
13 disp('Since AND followed by an inverter is NAND ');
14 disp('Hencee the NAND NAND is equivallent to AND OR'
    );
15
16 //end

```

Scilab code Exa 6.5.a To find hFEmin

```

1 clear;
2 clc;
3
4 //Caption :To find hFEmin
5 //Given Data
6 //For transistor
7 Vbesat=0.8; //Vgamma of diode in V
8 Vy=0.5; //in V
9 Vcesat=0.2; //in V
10 R = 5; //in K
11 Rc = 2.2; //in K
12
13 //For diode
14 Vyd=0.6; //in V
15 Vdrop=0.7; //in V
16
17 //The logic levels are Vcesato=0.2V for 0 state

```

```

18 Vcesato=0.2; //in V
19 //The logic levels are Vcc=5V for 1 state
20 Vcc=5; //in V
21 disp('If atleast one input is in 0 state');
22 Vp = Vcesato + Vy; //Potential at point P
23 disp('V',Vp,'Vp=');
24 //For diodes D1 and D2 to be conducting
25 v = 2*Vdrop;
26 disp('For diodes D1 and D2 to be conducting');
27 disp(v,'required voltage = ');
28 //These diodes cutoff
29 Vbe = 0;
30 if(Vbe<Vy)
31     disp('Q is OFF');
32     disp('Output rises to 5V and Y = 1');
33     disp('This confirms first 3 rows of NAND truth
            table');
34 end
35
36 // if all inputs are at V(1)=5V , we shall assume all
            input diodes OFF and D1 and D2 conduct and Q is
            in saturation
37 disp('When inputs are at 5V');
38 Vp = Vdrop + Vdrop + Vbesat;
39 disp('V',Vp,'Vp=');
40 disp(Vcc-Vp,'The voltage across all input diode');
41
42 //For finding hFEmin
43 I1 = (Vcc-Vp)/R;
44 I2 = Vbesat/R;
45 Ib = I1-I2;
46 Ic = (Vcc-Vcesat)/Rc;
47 hFEmin = Ic/Ib;
48 disp(hFEmin,'hFEmin=');
49
50 //end

```

Scilab code Exa 6.5.b When atleast one input is at V0 in NAND gate

```
1 clear;
2 clc;
3
4 //Caption :When atleast one input is at V(0) in NAND
      gate
5 //Given Data
6 //For transistor
7 Vbesat=0.8; //in V
8 Vy=0.5; //in V
9 Vcesat=0.2; //in V
10 R = 5; //in K
11 Rc = 2.2; //in K
12
13 //For diode
14 Vyd=0.6; //Vgamma in V
15 Vdrop=0.7; //in V
16
17 //The logic levels are Vcesato=0.2V for 0 state
18 Vcesato=0.2; //in V
19
20 disp('If atleast one input is in 0 state');
21 Vp = Vcesato + Vdrop; //Voltage at point P
22 disp('V',Vp,'Vp=');
23 Vbe = Vp-Vyd; //Voltage at base emitter
24 disp('V',Vbe,'Vbe=');
25 if(Vbe<Vy)
    disp('Q is cutoff');
26 end
27 if(Vbe>Vy)
    disp('Q is ON');
28 end
31 //end
```

Scilab code Exa 6.5.c If input is high in NAND gate

```
1 clear;
2 clc;
3
4 //Caption:If input is high in NAND gate
5 //Given Data
6 //For transistor
7 Vbesat=0.8; //in V
8 Vy=0.5; //in V
9 R = 5; //in K
10 Rc = 2.2; //in K
11
12 //For diode
13 Vyd=0.6; //in V
14 Vdrop=0.7; //in V
15
16 //The logic levels are Vcesato=0.2V for 0 state
17 Vcesato=0.2; //in V
18 //And Vcc = 5V for 1 state .
19 Vcc = 5; // volts
20
21 Vp = Vdrop + Vdrop + Vbesat; //Voltage at point P
22 disp('V',Vp,'Vp=');
23 disp('V',Vcc-Vp,'Each diode is reversed biased by ')
;
24 disp('V',Vyd,'A diode starts to conduct when it is
forward bias by ');
25 vn = (Vcc-Vp) + Vyd; //Noise Spike which will cause
the malfunction
26 disp('V',vn,'A noise spike which will cause
malfunction is ');
27
28
```

29 //end

Scilab code Exa 6.5.d If input is low in NAND gate

```
1 clear;
2 clc;
3
4 //Caption: If input is low in NAND gate
5 //Given Data
6 //For transistor
7 Vbesat=0.8; //in V
8 Vy=0.5; //in V
9 R = 5; //in K
10 Rc = 2.2; //in K
11
12 //The logic levels are Vcesato=0.2V for 0 state
13 Vcesato=0.2; //in V
14 //For diode
15
16 Vyd=0.6; //in V
17 Vdrop=0.7; //in V
18
19 Vp = Vcesato + Vdrop; //Voltage at point P
20 disp('V',Vp,'Vp=');
21 Vbe = Vy; //Voltage at base emitter will be same as
    Vgamma
22 vp = Vbe + Vyd + Vyd; //The level to which vp should
    increase
23 Vn = vp - Vp; //Noise Margin
24 disp('V',Vn,'Noise Margin = ');
25
26 //end
```

Scilab code Exa 6.6 Calculation of FAN OUT of NAND gate

```
1 clear;
2 clc;
3
4 //Caption : Calculation of FAN OUT of NAND gate
5 //Given Values
6 hFE=30;
7 Vbe1active=0.7; //in V
8 Vd2=0.7; //in V
9 Vbe2sat=0.8; //in V
10 Vcc=5; //in V
11 R1=1.75; //in K
12 R2=2; //in K
13 R3=2.2; //in K
14 R4=5; //in K
15
16 Vp = Vbe1active + Vd2 + Vbe2sat; //Voltage at point P
17 //The current in 2K resistor is Ib1
18 //In active region
19 //Ic1=hFE*Ib1
20 //I1 = Ib1+Ic1=(1+hFE)*Ib1.... Now applying KVL
    between Vcc and Vp
21 //Vcc-Vp = R1*(1+hFE)*Ib1 + 2*Ib1
22 Ib1 = (Vcc-Vp)/(R1*(1+hFE)+2); //Base current in
    transistor 1
23 disp('mA', Ib1, 'Ib1=');
24 Ic1=hFE*Ib1; //Collector Current in transistor 1
25 disp('mA', Ic1, 'Ic1=');
26 I1 = Ib1 + Ic1; //in mA
27 I2=Vbe2sat/R4; //in mA
28 Ib2 = I1-I2; //Base Current in Transistor 2
29 //The unloaded current of Q2
30 Iq2=(Vcc-0.2)/R3;
31 //For each gate which it drive ,Q2 must sink a
    standard load of
32 I=(Vcc-Vd2-0.2)/(R1+R2);
33 //To Calculate the FAN OUT
```

```
34 //The maximum current is hFE*Ib2
35 //hFE*Ib2 = ( I*N) + Iq2
36 N=((hFE*Ib2)-Iq2)/I; //FAN OUT
37 disp(N, 'N=') ;
38
39 // end
```

Chapter 7

Integrated Circuit Fabrication and Characteristic

Scilab code Exa 7.1 Diffusion of a pn junction

```
1 clear;
2 clc;
3
4 //caption: Diffusion of a pn junction
5
6 disp('At distance equal to x=xi at which N =
    concentration n of doped silicon wafers , the net
    impurity density is zero. Thus xi is the
    distance at which junction is formed');
7
8 //Given Data
9 q = 1.6*(10^-19); //Charge of electron
10 yn=1300; //mobility of silicon
11 p = 0.5; //resistivity in ohm=cm
12 y=2.2;
13 t=2*3600; //in sec.
14 xi = 2.7*(10^-4); // Junction Depth in cm.
15
16 n = 1/(p*yn*q); //Concentration of doped silicon
```

```

        wafer
17 disp('cm^-3',n,'The concentration n =');
18 disp('The junction is formed when N = n');
19
20 //y = xi/(2*(D*t)^0.5)
21 D=((xi)^2/((2*y)^2*t)); //Diffusion Constant
22
23 disp('cm^2/sec',D,'The value of Diffusion Constant
      for Boron = ');
24
25 //end

```

Scilab code Exa 7.2.a Fabrication and Characteristics

```

1 clear;
2 clc;
3
4 //Caption : Fabrication and Characteristics
5 //Given Data
6 y = 2.2; //from the figure y=2.2
7 Nob = 5*10^18 //Uniform Concentration of Boron
      Profile
8
9 //y = 2.7/(2*(D*t)^0.5)
10 //2*(D*t)^0.5 = a
11 a = 2.7/y;
12 x = 2; //distance at which emitter junction is formed
      in micrometer
13 Nb = Nob*erfc(x/a); //boron Profile
14 disp('cm^-3',Nb,'Nb=');
15 disp('The boron diffusion equation is ');
16 disp(a,'5*10^18*erfc x / ');
17 //At x=2 Np = Nb
18 //erfc (2/(2*(D*t)^0.5))=k
19 Nop=10^21;

```

```

20 k = Nb/Nop;
21 a = 2/2.7;
22 disp('The phosphorous diffusion equation is');
23 disp(a, '10^21*erfc x / ');
24
25
26 //end

```

Scilab code Exa 7.2.b Fabrication and Characteristics

```

1 clear;
2 clc;
3
4 //Caption : Fabrication and Characteristics
5 //Given Data
6 y = 2.2; //from the figure y=2.2
7 Nob = 5*10^18 //Uniform Concentration of Boron
    Profile
8
9 //y = 2.7/(2*(D*t)^0.5)
10 //2*(D*t)^0.5 = a( let )
11 a = 2.7/y;
12 x = 2; //distance at which emitter junction is formed
    in micrometer
13 Nb = Nob*erfc(x/a); //boron Profile
14
15 //At x=2 Np = Nb
16 //erfc (2/(2*(D*t)^0.5))=k
17 Nop=10^21;
18 k = Nb/Nop;
19 a = 2/2.7;
20 //Time allowed for diffusion if diffusion of
    Phosphorous is conducted at 1100 degreeC
21 //From the figure D=3.8*10^-13 cm^2/sec
22 D=3.8*10^-13 //in cm^2/sec

```

```
23 t = ((a*10^-4)/2)^2*(1/D);  
24 disp('sec ',t,'t=');  
25  
26 //end
```

Chapter 8

The Transistor at Low Frequency

Scilab code Exa 8.2 transistor as a Common Emitter Amplifier

```
1 clear;
2 clc;
3
4 //Caption:transistor as a Common Emitter Amplifier
5 //Given Data
6
7 Rl=10; //in K
8 Rs=1; //in K
9 hie=1.1; //in K
10 hre=2.5*(10^-4);
11 hfe=50;
12 hoe=25*(10^-3); //in K^-1
13
14 Ai= -hfe/(1+(hoe*Rl)); //Current Gain or Current
   Amplification
15 disp(Ai, 'Ai=');
16
17 Ri = hie + (hre*Rl*Ai);
18 disp('K', Ri, 'Ri=');
```

```

19
20 Av=(Ai*Rl)/Ri; // Voltage Gain
21 disp(Av , 'Av=');
22
23 Avs=(Av*Ri)/(Ri+Rs); //Overall Voltage Gain taking
    source resistance into account
24 disp(Avs , 'Avs=');
25
26 Ais=(Ai*Rs)/(Ri+Rs); //Overall current gain taking
    source resistance into account
27 disp(Ais , 'Ais=');
28
29 Yo=hoe-((hfe*hre)/(hie+Rs)); //Admittance
30 disp('K^-1' , Yo , 'Yo=');
31
32 Zo = 1/Yo; //Impedence
33 disp('K' , Zo , 'Zo=');
34
35 //end

```

Scilab code Exa 8.3 To derive output impedance of given figure in open circuit voltage

```

1 clear;
2 clc;
3
4 //Caption:To derive output impedance of given figure
    in open circuit-voltage short-circuit-current
    theorem
5 //Solution
6
7 //Yo = I/Vo
8 //When current in a short circuit placed across the
    output terminals and V is the open circuit
    voltage
9 disp('When current in a short circuit placed across'

```

```

        the output terminals and V is the open circuit
        voltage');
10 disp('I = -hf*I1=-(hf*Vs)/(Rs+hi)');
11 // Applying KVL
12 disp('Vs = I1*(Rs+hi)+hr*V = -ho*V*(Rs+hi)/hf+hr*V')
    ;
13 disp('or');
14 disp('V = -(hf*Vs/(Rs+hi))/(ho-hf*hr(Rs+hi))');
15
16 //end

```

Scilab code Exa 8.4 Parameters of a Common Emitter Amplifier

```

1 clear;
2 clc;
3
4 //Caption : Parameters of a Common Emitter Amplifier
5 //Given Data
6 hie=1.1;//in K
7 hre=2.5*(10^-4);
8 hfe=50;
9 hoe=25*(10^-3); //in K^-1
10 r=200; //in K
11 Rs=10; //in K
12 Ri=1; //in K
13 Rl=10; //in K
14
15 rl=(r*Rs)/(r+Rs); //in K
16
17 Ai = -hfe/(1+(hoe*rl)); //Current Gain
18 disp(Ai,'Ai = ');
19
20 Ri = hie + (hre*Ai*rl);
21 disp('K',Ri,'Ri=');
22

```

```

23 Av=(Ai*r1)/Ri; //Voltage Gain
24 disp(Av, 'Av = ');
25
26 k = r/(1-Av);
27 ri = (Ri*k)/(Ri+k);
28 disp('K', ri, 'ri = ');
29
30 Avs = Av*(ri/(ri+Rs)); //Overall voltage Gain taking
    Source resistance into account
31 disp(Avs, 'Avs = ');
32
33 ai = Avs*((ri+Rs)/Rl);
34 disp(ai, 'ai = -I2/I1');
35
36 //End

```

Scilab code Exa 8.5 CE CC configuration

```

1 clear;
2 clc;
3
4 //Caption : CE-CC configuration
5 //Given Data
6 hie = 2; //in K
7 hfe = 50;
8 hre = 6*(10^-4);
9 hoe = 25*(10^-3); //in K^-1
10 hic=2; //in K
11 hfc=-51;
12 hrc=1;
13 hoc=25*(10^-3); ///in K^-1
14 Re2=5; //in K
15 Rs=1; //in K
16 Rc1=5; //in K
17

```

```

18 //The Second Stage
19
20 Rl = Re2;
21 Ai2 = -hfc/(1+(hoc*Re2)); //Current Gain in @nd
    Transistor
22 disp(Ai2, 'Ai2=');
23
24 Ri2 = hic + (hrc*Ai2*Re2);
25 disp('K',Ri2, 'Ri2=');
26
27 Av2 = (Ai2*Re2)/Ri2; //Voltage Gain in 2nd Transistor
28 disp(Av2, 'Av2=');
29
30 //The First Stage
31
32 Rl1 = (Rc1*Ri2)/(Rc1+Ri2);
33 disp('K',Rl1, 'Rl1=');
34
35 Ai1 = -hfe/(1+(hoe*Rl1)); //Current Gain in 1st
    Transistor
36 disp(Ai1, 'Ai1=');
37
38 Ri1 = hie + (hre*Ai1*Rl1);
39 disp('K',Ri1, 'Ri1=');
40
41 Av1 = (Ai1*Rl1)/Ri1; //Voltage Gain in 1st Transistor
42 disp(Av1, 'Av1=');
43
44 disp('The output Admittance of Transistor');
45 Yo1 = hoe - ((hfe*hre)/(hie+Rs));
46 disp('K^-1',Yo1, 'Yo1=');
47
48 Ro1 = 1/Yo1;
49
50 //Output Impedence of First Stage
51 disp('Output Impedence of First Stage');
52 ro1 = (Ro1*Rc1)/(Ro1+Rc1);
53 disp('K',ro1, 'ro1=');

```

```

54
55 rs2 = ro1;
56
57 Yo2 = hoc - ((hfc*hrc)/(hic+rs2));
58 disp('K^-1',Yo2,'Yo2=');
59
60 A1 = (Ai2*Ai2*Rc1)/(Ri2+Rc1); //Overall Current gain
61 disp(A1,'A1=');
62
63 Av = Av2*Av1; //Overall Voltage Gain
64 disp(Av,'Voltage Gain = Av=');
65
66 Avs = (Av*Ri1)/(Ri1+Rs); //Overall Voltage gain with
   Source Impedence
67 disp(Avs,'Overall Voltage gain taking Source
   Impedence into account = Avs = ');
68
69
70 //End

```

Scilab code Exa 8.6 Parameters of CE CC configuration

```

1 clear;
2clc;
3
4 //Caption : Parameters of CE-CC configuration
5 //Given Data
6
7 hie = 2; //in K
8 hfe = 50;
9 hre = 6*(10^-4);
10 hoe = 25*(10^-3); //in K^-1
11 hic=2; //in K
12 hfc=-51;
13 hrc=1;

```

```

14 hoc=25*(10^-3); //in K^-1
15 Re2=5; //in K
16 Rs=5; //in K
17 Rc1=5; //in K
18
19 //For the CC output Stage
20 disp('For the CC output Stage');
21 Rl = Re2;
22 Ai2 = 1+ hfe; //Current gain in 2nd Transistor
23 disp(Ai2, 'Ai2=');
24 Ri2 = hie+((1+hfe)*Rl);
25 disp('K', Ri2, 'Ri2=');
26 Av2=1-(hie/Ri2); //voltage gain in 2nd transistor
27 disp(Av2, 'Av2=');
28
29 //For the CE input Stage
30 disp('For the CE input Stage');
31
32 Ai1=-hfe; //Current gain in 1st transistor
33 Ri1 = hie;
34 disp(Ai1, 'Ai1=');
35 Rl1=(Rc1*Ri2)/(Rc1+Ri2);
36 disp('K', Rl1, 'Rl1=');
37 Av1=(Ai1*Rl1)/Ri1; //Voltage gain in 1st transistor
38 disp(Av1, 'Av1=');
39 ro1=Rc1;
40 Ro2 = (hie+Rs)/(1+hfe);
41 ro2=(Ro2*Rl)/(Ro2+Rl);
42 disp('K', ro2, ' Effective Source Impedence ');
43
44 Av = Av1*Av2; //Overall voltage gain
45 disp(Av, 'Overall Voltage Gain=');
46 Ai = Ai1*Ai2*(Rc1/(Rc1+Ri2)); //Overall current Gain
47 disp(Ai, 'Overall Current Gain=');
48
49 //End

```

Chapter 9

Transistor Biasing and Thermal Stabilization

Scilab code Exa 9.1 To find Q point

```
1 clear;
2 clc;
3
4 //Caption :To find Q point
5 //Given Data
6 Vcc=22.5//in V
7 Rc=5.6; //in K
8 Re=1; //in K
9 R2=10; //in K
10 R1=90; //in K
11 B=55; //beta
12
13
14 V=(R2*Vcc)/(R2+R1); //Thevenin Equivallent Voltage
15 Rb=(R2*R1)/(R2+R1); //Thevenin Equivallent Resistance
16 disp('Volts ',V,'The equivallent Vbb =');
17 disp('ohm ',Rb,'The equivallent Rb is ');
18
19 //For base current large compared to reverse
```

```

    saturation current ie Ib>>Ico it follows that Ic=
B*Ib
20
21 //Applying KVL to the base circuit
22 //0.65-2.25+Ic+10*Ib=0
23 disp('As B=55 we have Ic=55*Ib');
24
25 //We have -1.60+Ic+(10/55)*Ic=0
26 Ic=1.60/(65/55);
27 Ib=Ic/55;
28 disp(' milli amp',Ic,'Ic=');
29 disp(' micro amp',Ib,'Ib=');
30
31 //Applying KVL to the collector circuit yields
32 // -22.5+6.6*Ic+Ib+Vce
33
34 Vce = 22.5-(6.6*1.36)-0.025;
35 disp('Volts',Vce,'Vce=');
36
37 //end

```

Scilab code Exa 9.2 To find resistances in 2N335 transistor

```

1 clear;
2 clc;
3
4 //Caption:To find resistances in 2N335 transistor
5 //Given Data
6 Rc=4; //in K
7 Vcc=20; //in V
8 Vce=10; //in V
9 Ic=2; //in mA
10 //Ic varies from 1.75 to 2.25 and B(beta) varies
     from 36 to 90
11

```

```

12 Re = (Vcc-Vce)/Ic - Rc;
13
14 //S=delta Ic/delta B
15 Ic2=2.25; //in mA
16 Ic1=1.75; //in mA
17 B2=90;
18 B1=36;
19 S=(Ic2-Ic1)/(B2-B1);
20 S2=(S*36*(1+90))/1.75;
21 disp(S2, 'S2=' , 'K' , Re , 'Re=' , 'B2=90');
22
23 //S2=(1+B)*(1+(Rb/Re))/(1+B+(Rb/Re))
24 Rb=(S2-1)*(1+B2)*Re/(1+B2-S2);
25 disp('K' , Rb , 'Rb=' );
26
27 Vbe=0.65; //in V
28 disp('V' , Vbe , 'We know that Vbe = ');
29
30 V = Vbe + ((Rb+Re*(1+B1))*Ic1/B1);
31 disp('Volts' , V , 'V = ');
32
33 R1=Rb*Vcc/V;
34 R2=R1*V/(Vcc-V);
35 disp('K' , R1 , 'R1=' );
36 disp('K' , R2 , 'R2=' );
37
38 //end

```

Scilab code Exa 9.3.a Variation of Ic in given Transistor

```

1 clear;
2 clc;
3
4 //Caption: Variation of Ic in given Transistor
5 //Given Data at 25degree C

```

```

6 Re=4.7; //in K
7 Rb=7.75; //in K
8 B1=55; //beta at 25degree C
9 Ic1=1.5; //in mA
10 Ico1=1;
11 Vbe1=0.6; //in V
12
13 //Part a
14
15 Ico2=33000; //in nA
16 Vbe2=0.225; //in V
17 M1=1/(1+(Rb/(Re*B1))); //Stability Factor
18 disp(M1,'Stability Factor at 25deree C=');
19 B2=100; //at 175degree C
20 M2=1/(1+(Rb/(Re*B2))); //Stability Factor
21 disp(M2,'Stability Factor at 175degree C=');
22
23 if(M2>M1)
24     M1=1;
25     M2=1;
26 end
27
28 //Let k = (delta Ic)/(Ic1)
29 k=(1+(Rb/Re))*(M1*(Ico2-Ico1)*(10^-9)/Ic1*(10^-3))-
    M1*(Vbe2-Vbe1)/(Ic1*Re)+(1+(Rb/Re))*(M2*(B2-B1)-
    /(B2*B1));
30 deltaIc=k*Ic1;
31 disp('mA',deltaIc,'Change in Collector Current at
    175degree C is =');
32
33 //Given Data at -65degree C
34 Ico2=1.95*(10^-3);
35 B2=25;
36 Vbe2=0.78;
37
38 M2=1/(1+(Rb/(Re*B2))); //Stability Factor
39 disp(M2,'Stability Factor at -65degree C=');
40

```

```

41 //Let k = ( delta Ic )/(Ic1)
42 k=(1+(Rb/Re))*(M1*(Ico2-Ico1)*(10^-9)/Ic1*(10^-3))-
    M1*(Vbe2-Vbe1)/(Ic1*Re))+(1+(Rb/Re))*(M2*(B2-B1)
    /(B2*B1));
43 deltaIc=k*Ic1;
44 disp('mA',deltaIc,'Change in Collector Current at
-65degree C is =')
45
46
47 //End

```

Scilab code Exa 9.3.b Variation of Ic in given Transistor

```

1 clear;
2 clc;
3
4 //Caption: Variation of Ic in given Transistor
5 //Given Data at 25degree C
6 Re=4.7; //in K
7 Rb=7.75; //in K
8 B1=55; //beta at 25degree C
9 Ic1=1.5; //in mA
10 Ico1=1;
11 Vbe1=0.6; //in V
12
13 //Part b
14
15 Ico2=33000; //in nA
16 Vbe2=0.225; //in V
17 M1=1/(1+(Rb/(Re*B1))); //Stability Factor
18 //Given Data at -65degree C
19 Ico2=1.95*(10^-3);
20 B2=25;
21 Vbe2=0.78;
22

```

```

23 M2=1/(1+(Rb/(Re*B2))); //Stability Factor
24
25 //Let k = (delta Ic)/(Ic1)
26 k=(1+(Rb/Re))*(M1*(Ico2-Ico1)*(10^-9)/Ic1*(10^-3))-
    M1*(Vbe2-Vbe1)/(Ic1*Re)+(1+(Rb/Re))*(M2*(B2-B1)-
    /(B2*B1));
27 deltaIc=k*Ic1;
28
29
30 //Given Data
31 Ico2=32; //in nA
32 Vbe2=0.10; //in V
33 M1=1/(1+(Rb/(Re*B1))); //Stability Factor
34 disp(M1, 'Stability Factor at 25degree C=');
35 B2=90; //at 175degree C
36 M2=1/(1+(Rb/(Re*B2))); //Stability Factor
37 disp(M2, 'Stability Factor at 75degree C=');
38
39 if(M2>M1)
40     M1=1;
41     M2=1;
42 end
43
44 //Let k = (delta Ic)/(Ic1)
45 k=(1+(Rb/Re))*(M1*(Ico2-Ico1)*(10^-9)/Ic1*(10^-3))-
    M1*(Vbe2-Vbe1)/(Ic1*Re)+(1+(Rb/Re))*(M2*(B2-B1)-
    /(B2*B1));
46 deltaIc=k*Ic1;
47 disp('mA',deltaIc, 'Change in Collector Current at 75
    degree C is =');
48
49 //Given Data at -65degree C
50 Ico2=1.95*(10^-3);
51 B2=20;
52 Vbe2=0.38;
53
54 M2=1/(1+(Rb/(Re*B2))); //Stability Factor
55 disp(M2, 'Stability Factor at -65degree C=');

```

```

56
57 //Let k = ( delta Ic ) / ( Ic1 )
58 k=(1+(Rb/Re))*(M1*(Ico2-Ico1)*(10^-9)/Ic1*(10^-3))-
      M1*(Vbe2-Vbe1)/(Ic1*Re)+(1+(Rb/Re))*(M2*(B2-B1)-
      /(B2*B1));
59 deltaIc=k*Ic1;
60 disp( 'mA' ,deltaIc , 'Change in Collector Current at
      -65 degree C is =' );
61
62 //End

```

Scilab code Exa 9.4 To design a self bias circuit

```

1 clear;
2 clc;
3
4 //Caption: To design a self bias circuit
5
6 //Given Data at 25degree C
7 B1=150; //beta
8 Ico1=50; //in nA
9
10 //Given Data at 65degree C
11 B2=1200; //beta
12 Ico2=3; //in micro A
13
14 Vbe=0.65; //in mV
15 Vcc=20; //in V
16 M=1;
17 //Assumption: Each factor Ico ,B, and Vbe cuses the
      same percentge change(5%)
18
19 //Let Rb/Re=k
20 //(1+k)*((1200 -150 )/(1200*150 ))=0.05
21

```

```

22 k=((0.05)*((1200*150)/(1200-150)))-1;
23 disp(k,'Rb/Re=');
24 //Let us check our assumption
25
26 if(M>(1/(1+(k/B1))))
27     M=1;
28 end
29
30 // (1+(Rb/Re))*((Ico2-Ico1)/Ic1)=0.05      Since Ico2>>
31           Ico1 , we consider only Ico2
32 Ic1=((1+k)*Ico2)/(0.05*1000);
33 disp('mA',Ic1,'Ic1=');
34
35 //Vbe changes 2.5mV/degree
36 DVbe=2.5*40;
37 //Total increment
38 dVbe=2*DVBbe*(10^-3);
39
40 //Let l=(Ic1*Re)
41 l=dVbe/0.05;
42
43 Re=l/Ic1;
44 disp(Re,'Re=');
45 Rb=k*Re;
46 disp(Rb,'Rb=');
47
48 B=(B1+B2)/2; //beta
49 V=((Ic1/B)*Rb)+(Vbe)+(((Ic1/B)+Ic1)*Re);
50 disp('Volts',V,'V=');
51 R1=(Rb*Vcc)/V;
52 R2=(R1*V)/(Vcc-V);
53
54 disp('ohm',R1,'R1=');
55 disp('ohm',R2,'R2=');
56
57 //end

```

Scilab code Exa 9.5 Value of theta for Ge Transistor

```
1 clear;
2 clc;
3
4 //Caption:Value of theta for Ge Transistor
5
6 //Given Data
7 Vcc=30; //in V
8 Rc=2; //in K
9 Re=4.7; //in K
10 Ic=1.5; //in mA
11
12 //We know that dPc/dIc = Vcc - (2*Ic*(Rc+Re))
13 //Let D=dPc/dIc
14
15 D = Vcc - (2*Ic*(Re+Rc));
16 disp('Ic increases by 0.131mA over a temprature
      range of 35 to 75 degree C');
17 disp('theta<(A=(dPc/dIc)*(dIc/dTc))');
18 A=D*((0.131*(10^-3))/(75-25));
19
20 disp('degreeC/W',1/A,'theta<');
21 disp('The upper bound on theta is so high that
      transistor would not violate it and therefore
      circuit will be safe from thermal runaway');
22
23 //End
```

Scilab code Exa 9.6.a To find parameters of power amplifier using pnp germanium tra

```
1 clear;
```

```

2 clc;
3
4 //Caption: To find parameters of power amplifier
   using pnp gemanium transistor
5
6 //Given Data
7 B=100; //beta
8 Ico=-5; //in mA
9 Ic=-1; //in mA
10 Vcc=40;
11 Re=5; //in ohm
12 Rc=10; //in ohm
13
14 //Ic= BIb + (1+B)*Ico
15 //Ic=B(Ib+Ico)
16 Ib=-(Ic/B)+Ico;
17 disp('mA', Ib, ' Ib=');
18
19 //Neglecting Vbe
20 Rb=(5-Vcc)/(Ib*0.001);
21 disp('ohm', Rb, 'Rb=');
22
23 Vce=Vcc-15;
24 if(Vce>(Vcc/2))
25     S=(1+B)*(1+(Rb/Re))/(1+B+(Rb/Re));
26     disp(S, ' Stability Factor is=');
27 end
28
29 A=-(Vcc+(2*Ic*(Re+Rc)))*(S)*(0.007*Ico*0.01);
30
31 disp('degreeC/W', 1/A, 'theta=');
32
33 //end

```

Scilab code Exa 9.6.b To find parameters of power amplifier using pnp gemanium tra

```

1 clear;
2 clc;
3
4 //Caption: To find parameters of power amplifier
      using pnp germanium transistor
5
6 //Given Data
7 B=100; //beta
8 Ico=-5; //in mA
9 Ic=-1; //in mA
10 Vcc=40;
11 Re=5; //in ohm
12 Rc=10; //in ohm
13
14 //Ic= BIb + (1+B)*Ico
15 // Ic=B(Ib+Ico)
16 Ib=-(Ic/B)+Ico;
17
18 //Neglecting Vbe
19 Rb=(5-Vcc)/(Ib*0.001);
20
21 Vce=Vcc-15;
22 if(Vce>(Vcc/2))
23     S=(1+B)*(1+(Rb/Re))/(1+B+(Rb/Re));
24     disp(S,'Stability Factor is=');
25 end
26
27 A=-(Vcc+(2*Ic*(Re+Rc)))*(S)*(0.007*Ico*0.01);
28
29 disp('degreeC/W',1/A,'theta=');
30
31 //end

```

Chapter 10

Field Effect Transistor

Scilab code Exa 10.1.a Pinch off V and channel half width of silicon FET

```
1 clear;
2 clc;
3
4 //Caption: Pinch off V and channel half width of
      silicon FET
5
6 //Given Values
7 a=3*(10^-4); //in cm
8 Nd=10^15; //in electrons/cm^3
9 q=1.6*(10^-19) //in C
10 eo=8.85*(10^-12); //Permittivity of free space
11 e=12*eo; //Relative Permittivity
12
13 Vp=(q*Nd*a*a*10^6*10^-4)/(2*e); //in V
14 //a is in cm so 10^-4 is multiplied and Nd is in
      electrons/cm^3 so 10^6 is multiplied
15 disp('V',Vp,'Pinch off Voltage =');
16
17 //end
```

Scilab code Exa 10.1.b Pinch off V and channel half width of silicon FET

```
1 clear;
2 clc;
3
4 //Caption: Pinch off V and channel half width of
   silicon FET
5
6 //Given Values
7 a=3*(10^-4); //in m
8 Nd=10^15; //in electrons/m^3
9 q=1.6*(10^-19) //in C
10 eo=8.85*(10^-12); //Permittivity of free space
11 e=12*eo; //Relative Permittivity
12
13 Vp=(q*Nd*a*a*10^6*10^-4)/(2*e); //in V
14 //a is in cm so 10^-4 is multiplied and Nd is in
   electrons/cm^3 so 10^6 is multiplied
15 Vgs= Vp/2;
16
17 b=a*((Vgs/Vp)^(0.5)); //in cm
18
19 disp( 'cm' ,b , 'Channel Half Width = ' );
20
21 //end
```

Scilab code Exa 10.2.a Amplifier using n channel FET

```
1 clear;
2 clc;
3
4 //Caption: amplifier using n channel FET
```

```

5
6 // Given Data
7
8 Vp=-2; //in V
9 Idss=1.65; //in mA
10 // it is desired to bias the circut at Id=0.8mA
11 Ids=0.8; //in mA
12 Vdd=24; //in V
13 //Assumption: rd>Rd
14
15 Vgs=Vp*(1-(Ids/Idss)^0.5); //in V
16 disp('V',Vgs,'Vgs=');
17
18
19 //end

```

Scilab code Exa 10.2.b Amplifier using n channel FET

```

1 clear;
2 clc;
3
4 //Caption: amplifier using n channel FET
5
6 // Given Data
7
8 Vp=-2; //in V
9 Idss=1.65; //in mA
10 // it is desired to bias the circut at Id=0.8mA
11 Ids=0.8; //in mA
12 Vdd=24; //in V
13 //Assumption: rd>Rd
14
15 Vgs=Vp*(1-(Ids/Idss)^0.5); //in V
16
17 gmo=-(2*Idss/Vp);

```

```
18 disp('mA/V',gmo,'gmo=');
19 gm=gmo*(1-(Vgs/Vp));
20 disp('mA/V',gm,'gm=');
21
22 //end
```

Scilab code Exa 10.2.c Amplifier using n channel FET

```
1 clear;
2 clc;
3
4 //Caption: amplifier using n channel FET
5
6 //Given Data
7
8 Vp=-2; //in V
9 Idss=1.65; //in mA
10 //it is desired to bias the circut at Id=0.8mA
11 Ids=0.8; //in mA
12 Vdd=24; //in V
13 //Assumption: rd>Rd
14
15 Vgs=Vp*(1-(Ids/Idss)^0.5); //in V
16
17 gmo=-(2*Idss/Vp);
18 gm=gmo*(1-(Vgs/Vp));
19
20 Rs=-(Vgs/Ids); //in ohm
21 disp('K',Rs,'Rs=');
22
23 //end
```

Scilab code Exa 10.2.d Amplifier using n channel FET

```

1 clear;
2 clc;
3
4 //Caption: amplifier using n channel FET
5
6 //Given Data
7
8 Vp=-2; //in V
9 Idss=1.65; //in mA
10 //it is desired to bias the circuit at Id=0.8mA
11 Ids=0.8; //in mA
12 Vdd=24; //in V
13 //Assumption: rd>Rd
14
15 Vgs=Vp*(1-(Ids/Idss)^0.5); //in V
16
17 gmo=-(2*Idss/Vp);
18 gm=gmo*(1-(Vgs/Vp));
19
20 Rs=-(Vgs/Ids); //in ohm
21
22 disp('20dB corresponds to voltage gain of i0');
23 Av=10;
24 Rd=Av/gm; //in ohm
25 disp('ohm',Rd,'Rd=');
26
27 //end

```

Scilab code Exa 10.3.a To find the parameters of a FET 2N3684

```

1 clear;
2 clc;
3
4 //Caption: To find the parameters of a FET 2N3684
5

```

```

6 // Given Values
7 Vpmin=-2; // in V
8 Vpmax=-5; // in V
9 Idssmin=1.6; // in mA
10 Idssmax=7.05; // in mA
11 Idmin=0.8; // in mA
12 Ia=Idmin;
13 Idmax=1.2; // in mA
14 Ib=Idmax;
15 Vdd=24; // in V
16 Vgs1=0; // in V
17 Id1=0.9; // in mA
18 Vgs2=-4; // in V
19 Id2=1.1; // in mA
20 // Slope determines Rs
21 Rs=(Vgs1-Vgs2)/(Id2-Id1);
22 disp('ohm',Rs,'Rs=');
23 Vgg=Id1*Rs;
24 disp('V',Vgg,'Vgg=');
25
26 // end

```

Scilab code Exa 10.3.b To find the range of possible values of Id in FET 2N3684 fr

```

1 clear;
2 clc;
3
4 //Caption:To find the range of possible values of Id
      in FET 2N3684 from the graph
5
6 //In the figure given The line of Rs=3.3K cuts Vp =
      -2V at Id = 0.4 mA
7 Idmin = 0.4; //in mA
8 disp('mA',Idmin,'Idmin=');
9

```

```

10 //In the figure given The line of Rs=3.3K cuts Vp =
   -5V at Id = 1.2 mA
11 Idmax = 1.2; //in mA
12 disp('mA', Idmax, 'Idmax=');
13
14 //end

```

Scilab code Exa 10.4 Voltage Gain of MOSFET as a single stage and then as first tr

```

1 clear;
2 clc;
3
4 //Caption: Voltage Gain of MOSFET as a single stage
   and then as first transistor
5
6 //Given Data
7 Rd=100; //in K
8 f=20000; //frequency in Hertz
9 //MOSFET parameters
10 gm=1.6; //in mA/V
11 rd=44; //in k
12 Cgs=3*(10^-12); //in F
13 Cds=1*(10^-12); //in F
14 Cgd=2.8*(10^-12); //in F
15 m=gm*rd; //mew
16
17 //Required Formulae
18 Ygs=2*pi*f*Cgs*%i; //in mho
19 Yds=2*pi*f*Cds*%i; //in mho
20 Ygd=2*pi*f*Cgd*%i; //in mho
21 gd=1/rd; //in mho
22 Yd=1/Rd; //in mho
23 gm=1.6*(10^-3); //in mho
24 disp('Gain of one stage amplifier');
25 Av=(-gm+Ygd)/(gd+Yd+Yds+Ygd); //Voltage Gain

```

```

26 disp(Av, 'Av=');
27
28 disp('Gain after selecting the interelectrode
      capacitance');
29 Av=-(m*Rd)/(Rd+rd); //Voltage Gain
30 disp(Av, 'Av=');
31
32 //Let k= gm*Rd'
33 k=-Av;
34 Ci = (Cgs*(10^12)) +((1+k)*Cgd*(10^12));
35 disp('Value of Input Impedence Capacitance');
36 disp('pF', Ci, 'Ci=');
37
38 //Now considering a two stage amplifier consisting
      of an FET operating
39 //New input Impedence taking into account various
      factors for present codition
40 Ci=200*(10^-12);
41 disp('Now considering a two stage amplifier
      consisting of an FET operating');
42 Yl=(0.001/Rd)+(2*pi*f*Ci*i);
43 disp(Yl, 'Load Admittance =');
44
45 gd=gd*0.001;
46 disp('Gain');
47 Av=-(gm)/(gd+Yl); //Voltage Gain
48 disp(Av, 'Av=');
49
50 //end

```

Chapter 12

MultiStage Amplifiers

Scilab code Exa 12.1.a Minimum value of coupling capacitance for a given FET

```
1 clear;
2 clc;
3
4 //Caption :Minimum value of coupling capacitance for
5 //a given FET
6 //Given Value
7 Ry=1; //in K
8 Rg=1; //in M
9 Ri=1; //in K
10 hOE=1/40; //in K^-1
11 //fL=1/(2*pi*(ro+ri)*Cb)<=10
12 //Since ri=1M , ro<Ry=1K , then ro+ri=1M
13
14 Cb=1/(2*pi*1*10);
15 disp(Cb, 'Minimum Value of coupling Capacitance for
given FET=');
16
17 //end
```

Scilab code Exa 12.1.b Minimum value of coupling capacitance for a given FET

```
1 clear;
2 clc;
3
4 //Caption :Minimum value of coupling capacitance for
5 // a given FET
6 //Given Value
7 Ry=1; //in K
8 Rg=1; //in M
9 Ri=1; //in K
10 hOE=1/40; //in K^-1
11 //fL=1/(2*pi*(ro+ri)*Cb)<=10
12
13 //Ro>1/hOE=40K ro=Rc=1K. Rb>Ri=1K then ri=1K
14
15 ro=1000; //in ohm
16 ri=1000; //in ohm
17
18 Cb=1/(2*pi*10*(ro+ri));
19 disp('pF',Cb*(10^6), 'Coupling Capacitance for given
transistor=');
20
21 //end
```

Chapter 13

Feedback Amplifier

Scilab code Exa 13.1 parameters of a Second collector to first emmitter feedback a

```
1 clear;
2 clc;
3
4 //Caption : parameters of a Second collector to
        //first emmitter feedback ampkifier
5 //Given Data
6 Rs=0; //in V
7 hfe=50; //in K
8 hie=1.1; //in K
9 hre=0; //in K
10 hoe=0; //in K
11
12 disp('We first calculate the effective load Rl1 at
        the first calculator');
13 r1=10; //in K
14 r2=47; //in K
15 r3=33; //in K
16 r4=1+0.1; //in K
17
18 Rl1=(r1*r2*r3*r4)/((r1*r2*r3)+(r1*r2*r4)+(r1*r3*r4)
        +(r2*r3*r4));
```

```

19 disp('K',Rl1,'Rl1=');
20
21 disp('Similarly for 2nd Transistor');
22 R1=0.1; //in K
23 R2=4.7; //in K
24 Rc1=R1+R2;
25 Rc2=4.7; //in K
26
27 Rl2=(Rc1*Rc2)/(Rc1+Rc2);
28 disp('K',Rl2,'Rl2=');
29
30 Re=(R1*R2)/(R1+R2);
31
32 disp('Voltage Gain of Transistor Q1');
33 Av1 = -(hfe*Rl1)/(hie+((1+hfe)*Re));
34 disp(Av1,'Av1=');
35
36 disp('Voltage Gain of Transistor Q2');
37 Av2=-(hfe*Rl2)/hie;
38 disp(Av2,'Av2=');
39
40 disp('Voltage Gain of two transistors in cascade
      without feedback');
41 Av=Av1*Av2;
42 disp(Av,'Av=');
43
44 B=R1/(R1+R2); //beta which is feedback
45 D=1+(B*Av);
46
47 Avf=Av/D;
48 disp(Avf,'Avf=');
49
50 disp('Input resistance without external feedback');
51 Ri=hie+((1+hfe)*Re);
52 disp('K',Ri,'Ri=');
53
54 Rif=Ri*D;
55 disp('K',Rif,'Rif=');

```

```
56
57 Ro=R12;
58 Rof=Ro/D;
59 disp( 'K' , Rof , 'Rof=' );
60
61 //end
```

Scilab code Exa 13.2.a To find parameters of Current series Feedback Amplifier

```
1 clear;
2 clc;
3
4 //Caption:To find parameters of Current series
   Fwwdback Amplifier
5 //Given Data
6 Gmf=-1; //Transconductance in mA/V
7 D=50; //Desensivity
8 Avf=-4; //Voltage Gain
9 Rs=1; //in K
10 hfe=150;
11 Vt=0.026; //in V
12
13 Gm=Gmf*D;
14 disp( 'mA/V' , Gm , 'Gm=' );
15
16 //B=Re, D = 1+B*Gm = 1-B*Gm
17 Re=(1-D)/Gm; //in K
18 disp( 'K' , Re , 'Re=' );
19
20 //end
```

Scilab code Exa 13.2.b To find parameters of Current series Feedback Amplifier

```

1 clear;
2 clc;
3
4 //Caption: Gain of second emitter to first
   basefeedback pair
5 //Given Data
6 Rc1=3; //in K
7 Rc2=0.5; //in K
8 Re=0.05; //in K
9 Rs=1.2; //in K
10 hfe=50;
11 hie=1.1; //in K
12 hre=0;
13 hoe=0;
14
15 R=Rs;
16
17 //Ai==Ic2/Is==-(Ic2/Ib2)*(Ib2/Ic1)*(Ic1/Ib1)*(Ib1/Is)
18 // -Ic2/Ib2 == hfe = -50
19 // Ic1/Ib1 = hfe
20 //Let Ib2/Ic1 = k
21 Ri2= hie + ((1+hfe)*(Re*R/(Re+R)));
22 k=-Rc1/(Rc1+Ri2);
23
24 r= Rs*(Rs+Re)/(Rs+R+Re);
25 //Let Ib1/Is = l
26 l=r/(r+hie);
27
28 Ai=(-hfe)*(k)*(hfe)*(l);
29
30 B=Re/(Re+R); //beta
31 D=1+(B*Ai);
32
33 Aif=Ai/D;
34
35 Avf=(Aif*Rc2)/Rs;
36
37 //To find Rif

```

```

38
39 Ri=(r*hie)/(r+hie);
40 Rif=Ri/D;
41 disp( 'ohm' ,Rif*1000 , 'Rif=' );
42
43 //End

```

Scilab code Exa 13.2.c To find parameters of Current series Feedback Amplifier

```

1 clear;
2 clc;
3
4 //Caption:To find parameters of Current seris
      Fwwdback Amplifier
5 //Given Data
6 Gmf=-1; //Transconductance in mA/V
7 D=50; //Desensivity
8 Avf=-4; //Voltage Gain
9 Rs=1; //in K
10 hfe=150;
11 Vt=0.026; //in V
12
13 Gm=Gmf*D;
14
15 //B=Re, D = 1+B*Gm = 1-B*Gm
16 Re=(1-D)/Gm; //in K
17
18 Rl=Avf/Gmf; //in K
19
20 // Gm= -hfe/(Rs+hie+Re)
21 hie= -(hfe/Gm)-Rs-Re;
22 Ri = Rs + hie +Re;
23 Rif = Ri*D
24 disp( 'K' ,Rif , 'Rif=' );
25

```

```
26
27 //end
```

Scilab code Exa 13.2.d To find parameters of Current series Feedback Amplifier

```
1 clear;
2 clc;
3
4 //Caption:To find parameters of Current series
   Feedback Amplifier
5 //Given Data
6 Gmf=-1; //Transconductance in mA/V
7 D=50; //Desensivity
8 Avf=-4; //Voltage Gain
9 Rs=1; //in K
10 hfe=150;
11 Vt=0.026; //in V
12
13 Gm=Gmf*D;
14
15 //B=Re, D = 1+B*Gm = 1-B*Gm
16 Re=(1-D)/Gm; //in K
17
18 Rl=Avf/Gmf; //in K
19
20 // Gm= -hfe/(Rs+hie+Re)
21 hie= -(hfe/Gm)-Rs-Re;
22 Ri = Rs + hie +Re;
23 Rif = Ri*D
24
25 Ic=(hfe*Vt)/hie;
26 disp('mA',Ic,'Quiescent Collector Current = ');
27
28 //end
```

Scilab code Exa 13.3.a Gain of second emitter to first basefeedback pair

```
1 clear;
2 clc;
3
4 //Caption:Gain of second emitter to first
   basefeedback pair
5 //Given Data
6 Rc1=3; //in K
7 Rc2=0.5; //in K
8 Re=0.05; //in K
9 Rs=1.2; //in K
10 hfe=50;
11 hie=1.1; //in K
12 hre=0;
13 hoe=0;
14
15 R=Rs;
16
17 //Ai==Ic2 / Is==-(Ic2 / Ib2 )*( Ib2 / Ic1 )*( Ic1 / Ib1 )*( Ib1 / Is )
18 // -Ic2 / Ib2 == hfe = -50
19 // Ic1 / Ib1 = hfe
20 //Let Ib2 / Ic1 = k
21 Ri2= hie + ((1+hfe)*(Re*R/(Re+R)));
22 k=-Rc1/(Rc1+Ri2);
23
24 r= Rs*(Rs+Re)/(Rs+R+Re);
25 //Let Ib1 / Is = 1
26 l=r/(r+hie);
27
28 Ai=(-hfe)*(k)*(hfe)*(l);
29 disp(Ai , 'Ai=' );
30
31 B=Re/(Re+R); //beta
```

```

32 D=1+(B*Ai);
33
34 Aif=Ai/D;
35 disp(Aif,'Aif=');
36
37 Avf=(Aif*Rc2)/Rs;
38 disp(Avf,'Avf=');
39
40 //End

```

Scilab code Exa 13.3.b Gain of second emitter to first basefeedback pair

```

1 clear;
2 clc;
3
4 //Caption:Gain of second emitter to first
   basefeedback pair
5 //Given Data
6 Rc1=3; //in K
7 Rc2=0.5; //in K
8 Re=0.05; //in K
9 Rs=1.2; //in K
10 hfe=50;
11 hie=1.1; //in K
12 hre=0;
13 hoe=0;
14
15 R=Rs;
16
17 //Ai==Ic2/Is==-(Ic2/Ib2)*(Ib2/Ic1)*(Ic1/Ib1)*(Ib1/Is)
18 // -Ic2/Ib2 == hfe = -50
19 // Ic1/Ib1 = hfe
20 //Let Ib2/Ic1 = k
21 Ri2= hie + ((1+hfe)*(Re*R/(Re+R)));
22 k=-Rc1/(Rc1+Ri2);

```

```

23
24 r= Rs*(Rs+Re)/(Rs+R+Re);
25 //Let Ib1/Is = 1
26 l=r/(r+hie);
27
28 Ai=(-hfe)*(k)*(hfe)*(l);
29
30 B=Re/(Re+R); //beta
31 D=1+(B*Ai);
32
33 Aif=Ai/D;
34
35 Avf=(Aif*Rc2)/Rs;
36
37 //To find Rif
38
39 Ri=(r*hie)/(r+hie);
40 Rif=Ri/D;
41 disp('ohm',Rif*1000,'Rif=');
42
43 //End

```

Scilab code Exa 13.3.c Gain of second emitter to first basefeedback pair

```

1 clear;
2 clc;
3
4 //Caption:Gain of second emitter to first
        basefeedback pair
5 //Given Data
6 Rc1=3; //in K
7 Rc2=0.5; //in K
8 Re=0.05; //in K
9 Rs=1.2; //in K
10 hfe=50;

```

```

11 hie=1.1; // in K
12 hre=0;
13 hoe=0;
14
15 R=Rs;
16
17 //Ai==Ic2/Is==-(Ic2/Ib2)*(Ib2/Ic1)*(Ic1/Ib1)*(Ib1/Is)
18 // -Ic2/Ib2 == hfe = -50
19 // Ic1/Ib1 = hfe
20 //Let Ib2/Ic1 = k
21 Ri2= hie + ((1+hfe)*(Re*R/(Re+R)));
22 k=-Rc1/(Rc1+Ri2);
23
24 r= Rs*(Rs+Re)/(Rs+R+Re);
25 //Let Ib1/Is = l
26 l=r/(r+hie);
27
28 Ai=(-hfe)*(k)*(hfe)*(l);
29
30 B=Re/(Re+R); //beta
31 D=1+(B*Ai);
32
33 Aif=Ai/D;
34
35 Avf=(Aif*Rc2)/Rs;
36
37 Ri=(r*hie)/(r+hie);
38 Rif=Ri/D;
39
40 rif=(Rif*Rs)/(Rs-Rif);
41 disp('K',rif+Rs, 'Resistance with feedback seen by
      voltage source');
42
43 //End

```

Scilab code Exa 13.3.d Gain of second emitter to first basefeedback pair

```
1 clear;
2 clc;
3
4 //Caption : Gain of second emitter to first
   basefeedback pair
5 //Given Data
6 Rc1=3; //in K
7 Rc2=0.5; //in K
8 Re=0.05; //in K
9 Rs=1.2; //in K
10 hfe=50;
11 hie=1.1; //in K
12 hre=0;
13 hoe=0;
14
15 R=Rs;
16
17 //Ai==Ic2/Is==-(Ic2/Ib2)*(Ib2/Ic1)*(Ic1/Ib1)*(Ib1/Is)
18 // -Ic2/Ib2 == hfe = -50
19 // Ic1/Ib1 = hfe
20 //Let Ib2/Ic1 = k
21 Ri2= hie + ((1+hfe)*(Re*R/(Re+R)));
22 k=-Rc1/(Rc1+Ri2);
23
24 r= Rs*(Rs+Re)/(Rs+R+Re);
25 //Let Ib1/Is = 1
26 l=r/(r+hie);
27
28 Ai=(-hfe)*(k)*(hfe)*(l);
29
30 B=Re/(Re+R); //beta
31 D=1+(B*Ai);
32
33 Aif=Ai/D;
34
35 Avf=(Aif*Rc2)/Rs;
```

```

36
37 Rof=(Avf*Rs)/Aif;
38 disp('K',Rof,'Output Resistance = ');
39
40 //End

```

Scilab code Exa 13.4.a To find gain and resistance of Voltage Shunt Feedback

```

1 clear;
2 clc;
3
4 //Caption: To find gain and resistance of Voltage
   Shunt Feedback
5 //Given Values
6 Rc=4; //in K
7 r=40; //in K
8 Rs=10; //in K
9 hie=1.1; //in K
10 hfe=50;
11 hre=0;
12 hoe=0;
13
14 //Required Formulae
15 rc=(Rc*r)/(Rc+r);
16 R=(Rs*r)/(Rs+r);
17 Rm=-(hfe*rc*R)/(R+hie);
18 disp('K',Rm,'Rm=');
19 B=-1/r; //in mA/V
20 D=1+(B*Rm);
21 Rmf=Rm/D;
22
23 //Avf = Vo/Vs = Vo/( Is*Rs) = Rmf/Rs
24 Avf=Rmf/Rs;
25 disp(Avf,'Avf=');
26

```

27
28 //End

Scilab code Exa 13.4.b To find gain and resistance of Voltage Shunt Feedback

```
1 clear;
2 clc;
3
4 //Caption: To find gain and resistance of Voltage
   Shunt Feedback
5 //Given Values
6 Rc=4; //in K
7 r=40; //in K
8 Rs=10; //in K
9 hie=1.1;//in K
10 hfe=50;
11 hre=0;
12 hoe=0;
13
14 //Required Formulae
15 rc=(Rc*r)/(Rc+r);
16 R=(Rs*r)/(Rs+r);
17 Rm=-(hfe*rc*R)/(R+hie);
18 B=-1/r; //in mA/V
19 D=1+(B*Rm);
20 Rmf=Rm/D;
21
22 //Avf = Vo/Vs = Vo/( Is*Rs) = Rmf/Rs
23 Avf=Rmf/Rs;
24
25 Ri = (R*hie)/(R+hie);
26 Rif=Ri/D;
27 disp('K',Rif,'Rif=');
28
29 //End
```

Scilab code Exa 13.4.c To find gain and resistance of Voltage Shunt Feedback

```
1 clear;
2 clc;
3
4 //Caption: To find gain and resistance of Voltage
      Shunt Feedback
5 //Given Values
6 Rc=4; //in K
7 r=40; //in K
8 Rs=10; //in K
9 hie=1.1; //in K
10 hfe=50;
11 hre=0;
12 hoe=0;
13
14 //Required Formulae
15 rc=(Rc*r)/(Rc+r);
16 R=(Rs*r)/(Rs+r);
17 Rm=-(hfe*rc*R)/(R+hie);
18 disp('K',Rm, 'Rm' );
19 B=-1/r; //in mA/V
20 D=1+(B*Rm);
21 Rmf=Rm/D;
22
23 //Avf = Vo/Vs = Vo/( Is*Rs) = Rmf/Rs
24 Avf=Rmf/Rs;
25
26 Ri = (R*hie)/(R+hie);
27 Rif=Ri/D;
28
29 //If the input resistance looking to the right of Rs
      is rif then Rif=(rif*Rs)/(rif+Rs)
30 rif=(Rif*Rs)/(Rs-Rif);
```

```
31
32 disp('K',Rs+rif,'The impedance seen by the voltage
      source=Rif=') ;
33
34 Ro=40; //in K
35 r=40; //in K
36
37 Rm = -(hfe*r*R)/(R+hie);
38 Rof=Ro/(1+(B*Rm));
39 //We are writting Rof' = rof
40 rof=(Rof*Rc)/(Rof+Rc);
41 disp('K',rof,'rof=') ;
42
43 //End
```

Chapter 14

Stability and Oscillators

Scilab code Exa 14.1.a Lowest poles of an Amplifier

```
1 clear;
2 clc;
3
4 //Caption : Lowest poles of an Amplifier
5 //Given Data
6
7 //Poles in radians per sec
8 s1 = -46.2*(10^5);
9 s2 = -45.9*(10^6);
10 s3 = -11.4*(10^8);
11 s4 = -30.4*(10^8);
12
13 //Zeros
14 s5 = 16.65*(10^9);
15 s6 = 15.4*(10^8);
16 s7 = -22.55*(10^8);
17 s = 6.28*(10^6);
18 B = 0.040;
19 Ai = 410; //Gain
20
21 n = s2/s1;
```

```

22 disp(n, 'n=') ;
23 Q = (n*(1+(B*Ai)))^0.5/(n+1) ;
24 disp(Q, 'Q=') ;
25 k = 1/(2*Q) ;
26 disp(k, 'k=') ;
27
28 s1f = s1*((n+1)/2)*(1-%i*((4*Q*Q)-1)^0.5) ;
29 disp(s1f, 'The first pole is ') ;
30 s2f = s1*((n+1)/2)*(1+%i*((4*Q*Q)-1)^0.5) ;
31 disp(s2f, 'The second pole is ') ;
32
33
34 //end

```

Scilab code Exa 14.1.b Frequency Response Peak

```

1 clear;
2 clc;
3
4 //Frequency Response Peak
5 //Given Data
6
7 //Poles in radians per sec
8 s1 = -46.2*(10^5);
9 s2 = -45.9*(10^6);
10 s3 = -11.4*(10^8);
11 s4 = -30.4*(10^8);
12
13 //Zeros
14 s5 = 16.65*(10^9);
15 s6 = 15.4*(10^8);
16 s7 = -22.55*(10^8);
17 s = 6.28*(10^6);
18 B = 0.040;
19 Ai = 410; //Gain

```

```

20
21 n = s2/s1;
22 Q = (n*(1+(B*Ai)))^0.5/(n+1);
23 k = 1/(2*Q);
24
25 s1f = s1*((n+1)/2)*(1-%i*((4*Q*Q)-1)^0.5);
26 s2f = s1*((n+1)/2)*(1+%i*((4*Q*Q)-1)^0.5);
27
28 //Frequency Response Peak
29 wo = -Q*(s1+s2);
30 disp(wo, 'wo=');
31 w = wo*(1-(2*k*k))^0.5 //frequency at which frequency
    response peak occurs
32 disp(w, 'w=');
33 fpeak = (wo/s)*(1-(2*k*k))^0.5;
34 disp('MHz', fpeak, 'fpeak=');
35 //At peak
36 a = 1/(2*k*(1-(k*k))^0.5);
37 overshoot = 20*log10(a);
38 disp('dB', overshoot, 'Overshoot is ');
39
40
41 //end

```

Chapter 15

Operational Amplifier

Scilab code Exa 15.1.a difference in output voltage for two set of output signals

```
1 clear;
2 clc;
3
4 //Caption: difference in output voltage for two set
   of output signals
5 //Given Data
6 //First Set of Input Signal
7 v11=50; //in microV
8 v21=-50; //in microV
9 //Second Set of Input Signal
10 v12=1050; //in microV
11 v22=950; //in microV
12 p=100; //Common Mode Rejection Ratio
13
14 //Required Formulae
15 //vo = Ad*vd*(1+vc/p*vd) .... p = commom mode
   rejection ratio
16 //Ad will be same for both case , So let us write Vo
   = vo/Ad = Ad*(1+vc/p*vd)
17
18 //First Set of Values
```

```

19 vd1=v11-v21; //in microV
20 vc1=(v11+v21)/2; //in microV
21 Vo1 = vd1*(1+vc1/(p*vd1));
22
23 //Second Set of Values
24 vd2=v12-v22; //in microV
25 vc2=(v12+v22)/2; //in microV
26 Vo2 = vd2*(1+vc2/(p*vd2));
27
28 disp(100*(Vo2-Vo1)/Vo1, 'Percentage difference in
      output signal=');
29
30
31 //end

```

Scilab code Exa 15.1.b difference in output voltage for two set of output signals

```

1 clear;
2 clc;
3
4 //Caption: difference in output voltage for two set
   of output signals when Common Mode Rejection
   Ratio =10000
5 //Given Data
6 //First Set of Input Signal
7 v11=50; //in microV
8 v21=-50; //in microV
9 //Second Set of Input Signal
10 v12=1050; //in microV
11 v22=950; //in microV
12 p=100; //Common Mode Rejection Ratio
13
14 //Required Formulae
15 //vo = Ad*vd*(1+vc/p*vd) .... p = commom mode
   rejection ratio

```

```

16 //Ad will be same for both case , So let us write Vo
    = vo/Ad = Ad*(1+vc/p*vd)
17
18 //First Set of Values
19 vd1=v11-v21; //in microV
20 vc1=(v11+v21)/2; //in microV
21 Vo1 = vd1*(1+vc1/(p*vd1));
22
23 //Second Set of Values
24 vd2=v12-v22; //in microV
25 vc2=(v12+v22)/2; //in microV
26 Vo2 = vd2*(1+vc2/(p*vd2));
27
28
29 //Now we have to calculate the same thing with
   common mode rejection ratio = 10000
30
31 p=10000; //Common Mode Rejection Ratio
32
33 //First Set of Values
34 vd1=v11-v21; //in microV
35 vc1=(v11+v21)/2; //in microV
36 Vo1 = vd1*(1+vc1/(p*vd1));
37
38 //Second Set of Values
39 vd2=v12-v22; //in microV
40 vc2=(v12+v22)/2; //in microV
41 Vo2 = vd2*(1+vc2/(p*vd2));
42
43 disp(100*(Vo2-Vo1)/Vo1, 'Percentage difference in
   output signal=');
44
45 //end

```

Scilab code Exa 15.2 Design an amplifier using yA702A

```

1 clear;
2 clc;
3
4 //Caption: Design an amplifier using yA702A
5 //Given Data
6 f=32; //feedback in dB
7 //from the Bodes plot we get that Avo = 2510
8 Avo = 2510; //gain
9 disp('The parameters are R , r (for Rdash) , C (for
      Cdash)');
10 //Desensivity D = B*Rmo = Avo*(R/(R+r))
11 //20log10(D ) = f
12 k = f - (20*log10(Avo));
13 //Let (R+r)/R = l
14 l = 1/(10^(k/20));
15 //R/(R+r) = fp/fz
16 //For 45degree phase margin and 32dB of low
      frequency feedback we find by trial and error
      method from the graph
17 fz = 10;//in MHz
18 fp = fz*l;
19 //to determine c we can arbitrarily choose R
20 R = 1000;//in ohm
21 disp('ohm',R,'R = ');
22 r = (l-1)*R
23 disp('ohm',r,'r = ');
24 C = 1/(2*pi*fz*r*10^-6);
25 disp('pF',C,'C = ');
26
27
28 //end

```

Chapter 16

Integrated Circuits as Analog System Building blocks

Scilab code Exa 16.1 Fourth Order Butterworth Filter

```
1 clear;
2 clc;
3
4 //Caption :Fourth Order Butterworth Filter
5 //Given Data
6 fo=1; //Cutoff Frequency in Hz
7 //For n = 4
8 k1=0.765;
9 k2=1.848;
10
11 Av1 = 3-k1;
12 Av2 = 3-k2;
13 disp('For a fourth order Buttworth filter we cascade
      2 second order Buttworth filter with parameters
      R1 R2 R1d R2d R C');
14 //we arbitrarily choose
15 R1=10; //in K
16 disp('K',R1,'R1=');
17 //Av1=(R1+R1d)/R1
```

```

18 R1d=(Av1*R1)-R1;
19 disp(R1d,'R1d = ');
20
21 R2 = 10; //in K
22 disp('K',R2,'R2=');
23 R2d=(Av2*R2)-R2;
24 disp(R2d,'R2d = ');
25
26 //To satisfy fo = 1/(2*pi*r*c) = 1kHz
27 R=1; //in K
28 C = 1/(2*pi*R*fo);
29 disp('K',R,'R=');
30 disp('microF',C,'C = ');

```

Scilab code Exa 16.2 Design a second order bandpass filter

```

1 clear;
2 clc;
3 //Caption : Design a second order bandpass filter
4 //Given Value
5 Ao=50; //Gain
6 fo=160; //center frequency
7 B=16; //Bandwidth in Hz
8 C1=0.1; //in microF
9 C2=0.1; //in microF
10
11 //Required Formulae
12
13 Q=fo/B;
14 R1=(1000*Q)/(Ao*2*pi*fo*C1);
15 R3=(1000*Q)/((2*pi*fo)*(C1*C2/(C1+C2)));
16 //As C is in microFarad to compensate for it 1000 is
     multiplied
17 //Let r = R'
18 r=(10^6)/((2*pi*fo)^2*R3*C1*C2);

```

```

19 R2=(R1*r)/(R1-r);
20
21 disp('K',R1,'R1=');
22 disp('K',R3,'R3=');
23 disp('K',r,'r=');
24 disp('K',R2,'R2=');
25
26 //end

```

Scilab code Exa 16.3 Design a video amplifier using MC1550

```

1 clear;
2 clc;
3
4 //Caption: Design a video amplifier using MC1550
5 //Given Data
6 Avo=-25;
7 Vagc=20; //in V
8 Vcc=6; //in V
9 hfe=50;
10 rbb=50; //in ohm
11 Cs=5; //in pF
12 Cl=5; //in pF
13 Ie1=1; //in mA
14 ft=900; //in MHz
15 Vt=26; //in V
16 n=2; //eeta
17 //re2 = infinity
18
19 //Since Vage=0 , transistor Q2 is in cut off region
   and collector current of Q1 flows through Q3.....
   So
20 Ie2=0;
21 Ie3=1; //in mA
22 re3 = (n*Vt)/Ie3; //in ohm

```

```

23 disp('ohm',re3,'re3=') ;
24 gm = (Ie1)/Vt; // in ohm^-1
25 disp('ohm^-1',gm,'gm=') ;
26 rbe=hfe/gm;
27 disp('ohm',rbe,'rbe=') ;
28 Ce=gm/(2*pi*ft*10^-6) ;
29 disp('pF',Ce,'Ce=') ;
30 a3=1; //we make an assumption that alpha is one
31 s=0;
32 //Av0 = -((a3*gm)/(re3*rbb))*(1/(((1/rbb)+(1/rbe)+(s
    *Ce))*((1/re3)+(s*Cs))*((1/Rl)+(s*(Cs+Cl))))) ;
33 //From here we can find Rl
34 k = -((a3*gm)/(re3*rbb))*(1/(((1/rbb)+(1/rbe)+(s*Ce)
    )*((1/re3)+(s*Cs)))) ;
35 Rl=Avo/k;
36 disp('ohm',Rl,'Rl=') ;
37
38 //C is in picoFarad so to compensate the whole
    equation some constants are multiplied
39 f1 = 1/(2*pi*Rl*(Cs+Cl)*10^-6) ;
40 disp('MHz',f1,'f1=') ;
41 f2 = 1/(2*pi*Ce*10^-6*((rbe*rbb)/(rbe+rbb))) ;
42 disp('MHz',f2,'f2=') ;
43 f3 = 1/(2*pi*Cs*re3*10^-6) ;
44 disp('MHz',f3,'f3=') ;
45
46
47 // end

```

Scilab code Exa 16.4.a Logic Level Output of an ECL gate

```

1 clear;
2 clc;
3
4 //Caption : Logic Level Output of an ECL gate

```

```

5 //Given Data
6 Vbb = 1.15; //in V
7 Vee=5.20; //in V
8 Vbe5=0.7; //in V
9 R=1.18; //in K
10 r=300; //in ohm
11 Vbecutin=0.5; //in V
12
13 //If all inputs are low then we assume that Q1,Q2
   and Q3 are cutoff and Q4 is conducting
14 Ve=-Vbb-Vbe5; //Voltage at Common Emitter in V
15 //Current I in 1.18K Resistor
16 I = (Ve+Vee)/R; //in mA
17 I1=I;
18 disp('mA',I,'Current in 300 ohm resistance I=');
19 //Output Voltage at Y
20 vy = -(r*I/1000)-Vbe5; //I is in mA so 1000 is
   multiplied
21 Vbe = vy-Ve;
22 disp('V',Vbe,'Vbe = ');
23 if(Vbe<Vbecutin)
24     disp('Input transistors are non conducting as
           was assumed');
25     disp('If atleast one input is high then it is
           assumed that current in 1.18K resistance is
           switched to R and Q4 is cutoff');
26     disp('Drop in 300 ohm resistance is zero. Since
           the base aand collector are tied together Q5
           now behaves as a diode');
27     disp('Across Q5');
28 v=0.7; //voltage across Q5 in V
29 rQ5 = 1.5; //in K
30 i = (Vee-v)/rQ5;
31 v = 0.75; //from the graph in V
32 disp('mA',i,'i=');
33 disp('V',v,'v=');
34 Ve = -v-Vbe5;
35 Vbe4=-Vbb-Ve;

```

```

36      disp( 'V' , Vbe4 , 'Vbe4=' ) ;
37 end
38 disp( 'The total output swing between two logic gates
') ;
39 vo = -vy-v ;
40 disp( 'V' , vo , 'vo=' ) ;
41
42
43 // end

```

Scilab code Exa 16.4.b Calculation of noise margin

```

1 clear;
2 clc;
3
4 //Calculation of noise margin
5 //Given Data
6 Vbb = 1.15; //in V
7 Vee=5.20; //in V
8 Vbe5=0.7; //in V
9 R=1.18; //in K
10 r=300; //in ohm
11 Vbecutin=0.5; //in V
12
13 //If all inputs are low then we assume that Q1,Q2
   and Q3 are cutoff and Q4 is conducting
14 Ve=-Vbb-Vbe5; //Voltage at Common Emitter in V
15 //Current I in 1.18K Resistor
16 I = (Ve+Vee)/R; //in mA
17 I1=I;
18 //Output Voltage at Y
19 vy = -(r*I/1000)-Vbe5; //I is in mA so 1000 is
   multiplied
20 Vbe = vy-Ve;
21 if(Vbe<Vbecutin)

```

```

22     v=0.7; //voltage across Q5 in V
23     rQ5 = 1.5; //in K
24     i = (Vee-v)/rQ5;
25     v = 0.75; //from the graph in V
26     Ve = -v-Vbe5;
27     Vbe4=-Vbb-Ve;
28 end
29 vo = -vy-v;
30
31 //Calculation of noise margin
32 vn = Vbecutin-Vbe4;
33 disp('Positive noise spike which will cause the gate
      to malfunction');
34 disp('V',vn,'vn=');
35
36 //end

```

Scilab code Exa 16.4.c Verify that conducting transistor is in active region

```

1 clear;
2 clc;
3
4 //Verify that conducting transistor is in active
   region
5 //Given Data
6 Vbb = 1.15; //in V
7 Vee=5.20; //in V
8 Vbe5=0.7; //in V
9 R=1.18; //in K
10 r=300; //in ohm
11 Vbecutin=0.5; //in V
12
13 //If all inputs are low then we assume that Q1,Q2
   and Q3 are cutoff and Q4 is conducting
14 Ve=-Vbb-Vbe5; //Voltage at Common Emitter in V

```

```

15 //Current I in 1.18K Resistor
16 I = (Ve+Vee)/R; //in mA
17 I1=I;
18 //Output Voltage at Y
19 vy = -(r*I/1000)-Vbe5; //I is in mA so 1000 is
    multiplied
20 Vbe = vy-Ve;
21 if(Vbe<Vbecutin)
22     v=0.7; //voltage across Q5 in V
23     rQ5 = 1.5; //in K
24     i = (Vee-v)/rQ5;
25     v = 0.75; //from the graph in V
26     Ve = -v-Vbe5;
27     Vbe4=-Vbb-Ve;
28 end
29 vo = -vy-v;
30
31 Vb4 = Vbb;
32 Vc4 = -(I*r)/1000; //in V
33 Vcb4 = Vc4+Vb4;
34 disp('V',Vcb4,'Vcb4 = ');
35 if(Vcb4>0)
36     disp('For on npn transistor this represents a
            reverse bias and Q4 must be in active region',
            );
37 end
38 Vb1 = v;
39 Vc1 = vy+Vbe5;
40 Vcb1 = Vc1 + Vb1;
41 disp('V',Vc1,'Vc1=');
42 disp('V',Vcb1,'Vcb1=');
43 if(Vcb1<0)
44     disp('For an npn transistor this represents a
            forward bias.... therefore Q1 is in
            saturation region');
45 end
46
47 //end

```

Scilab code Exa 16.4.d Calculation of R

```
1 clear;
2 clc;
3
4 //Calculation of R
5 //Given Data
6 Vbb = 1.15; //in V
7 Vee=5.20; //in V
8 Vbe5=0.7; //in V
9 R=1.18; //in K
10 r=300; //in ohm
11 Vbecutin=0.5; //in V
12
13 // If all inputs are low then we assume that Q1,Q2
   and Q3 are cutoff and Q4 is conducting
14 Ve=-Vbb-Vbe5; //Voltage at Common Emitter in V
15 //Current I in 1.18K Resistor
16 I = (Ve+Vee)/R; //in mA
17 I1=I;
18 //Output Voltage at Y
19 vy = -(r*I/1000)-Vbe5; //I is in mA so 1000 is
   multiplied
20 Vbe = vy-Ve;
21 if(Vbe<Vbecutin)
22     v=0.7; //voltage across Q5 in V
23     rQ5 = 1.5; //in K
24     i = (Vee-v)/rQ5;
25     v = 0.75; //from the graph in V
26     Ve = -v-Vbe5;
27     Vbe4=-Vbb-Ve;
28 end
29 vo = -vy-v;
30
```

```

31 //Verify that conducting transistor is in active
    region
32 Vb4 = Vbb;
33 Vc4 = -(I*r)/1000; //in V
34 Vcb4 = Vc4+Vb4;
35 Vb1 = v;
36 Vc1 = vy+Vbe5;
37 Vcb1 = Vc1 + Vb1;
38
39 Vbe1 = Vbe5;
40 Ve = -(Vb1+Vbe1);
41 disp('V',Ve,'Ve=');
42 I = (Ve + Vee)/R;
43 I2=I;
44 R = -Vc1/I;
45 disp('ohm',R,'R=');
46
47 //end

```

Scilab code Exa 16.4.e Average power dissipated by the gate

```

1 clear;
2 clc;
3
4 //Average power dissipated by the gate
5 //Given Data
6 Vbb = 1.15; //in V
7 Vee=5.20; //in V
8 Vbe5=0.7; //in V
9 R=1.18; //in K
10 r=300; //in ohm
11 Vbecutin=0.5; //in V
12
13 //If all inputs are low then we assume that Q1,Q2
    and Q3 are cutoff and Q4 is conducting

```

```

14 Ve=-Vbb-Vbe5; //Voltage at Common Emitter in V
15 //Current I in 1.18K Resistor
16 I = (Ve+Vee)/R; //in mA
17 I1=I;
18 //Output Voltage at Y
19 vy = -(r*I/1000)-Vbe5; //I is in mA so 1000 is
    multiplied
20 Vbe = vy-Ve;
21 if(Vbe<Vbecutin)
22     v=0.7; //voltage across Q5 in V
23     rQ5 = 1.5; //in K
24     i = (Vee-v)/rQ5;
25     v = 0.75; //from the graph in V
26     Ve = -v-Vbe5;
27     Vbe4=-Vbb-Ve;
28 end
29
30 vo = -vy-v;
31
32 Vb4 = Vbb;
33 Vc4 = -(I*r)/1000; //in V
34 Vcb4 = Vc4+Vb4;
35 Vb1 = v;
36 Vc1 = vy+Vbe5;
37 Vcb1 = Vc1 + Vb1;
38
39 Vbe1 = Vbe5;
40 Ve = -(Vb1+Vbe1);
41 I = (Ve + Vee)/R;
42 I2=I;
43
44 I =(I1+I2)/2;
45 disp( 'mA' , I , ' I=' );
46 I2 = (Vee-v)/rQ5;
47 I3 = (Vee+vy)/rQ5;
48 I = I + I2 + I3;
49 P = Vee*I;
50 disp( 'mW' , P , 'Power dissipated = ' );

```

51
52 //end

Chapter 18

Power Circuits and Systems

Scilab code Exa 18.1.a Design a series regulated power supply

```
1 clear;
2 clc;
3
4 //Caption : Design a series regulated power supply
5 //Given Data
6 Vo=25; //in V
7 ro=10; //in ohm
8
9 disp('select a silicon reference diode');
10 disp('two IN7555 diodes are provided');
11 Rz = 12; //in ohm
12 Vo=25; //output voltage in V
13 Vr = 7.5 + 7.5; //because two diodes are used
14 Iz = 20; //in mA
15 Ie2=10; //in mA
16 Ic2 = Ie2;
17 Icmax=30; //in mA
18 Vcemax=45; //in V
19 hFE2=220;
20 hfe2=200;
21 hie2=800; //in ohm
```

```

22 Id=10; //in mA
23 I1 = 1000; //in mA
24 Vi = 50; //in V
25 dVi = 10; //change in input voltage
26 dI1 = 1; //change in load current
27
28 //For D1 and D2 operate
29 Iz = Id + Id;
30 Rd = (Vo-Vr)/Id;
31 disp('K',Rd,'Rd=');
32
33 Ib2 = (1000*Ic2)/hFE2;
34 disp('microA',Ib2,'Ib2=');
35
36 //Since we require I1>Ib2 , we select
37 I1=10*(10^-3); //in A
38 Vbe = 0.7; //in V
39
40 V2 = Vbe + Vr;
41 disp('V',V2,'V2=');
42
43 R1 = (Vo-V2)/I1;
44 R2 = V2/I1;
45 disp('ohm',R1,'R1=');
46 disp('ohm',R2,'R2=');
47
48 //We are selecting Texas Instruments 2N1722 silicon
   power transistor , so following parameters are
   required
49 disp('We are selecting Texas Instruments 2N1722
   silicon power transistor');
50 Ic1 = 1; //in A
51 hFE1=125;
52 hfe1=100;
53 hie1=20;
54
55 Ib1 =(1000*I1 + I1 + Id)/hFE1;
56 disp('mA',Ib1+Ic2,'The current through resistor R3

```

```

        is ');
57 I=Ib1 + Ic2;
58
59 R3 = (Vi - (Vbe + Vo))/I;
60 disp('K',R3,'The value of R3 is ');
61
62 //End

```

Scilab code Exa 18.1.b Calculation of Sv

```

1 clear;
2 clc;
3
4 //Caption : Calculation of Sv
5 //Given Data
6 Vo=25; //in V
7 ro=10; //in ohm
8
9 Rz = 12; //in ohm
10 Vo=25; //output voltage in V
11 Vr = 7.5 + 7.5; //because two diodes are used
12 Iz = 20; //in mA
13 Ie2=10; //in mA
14 Ic2 = Ie2;
15 Icmax=30; //in mA
16 Vcemax=45; //in V
17 hFE2=220;
18 hfe2=200;
19 hie2=800; //in ohm
20 Id=10; //in mA
21 Il = 1000; //in mA
22 Vi = 50; //in V
23 dVi = 10; //change in input voltage
24 dIl = 1; //change in load current
25

```

```

26 //For D1 and D2 operate
27 Iz = Id + Id;
28 Rd = (Vo-Vr)/Id;
29
30 Ib2 = (1000*Ic2)/hFE2;
31
32 //Since we require I1>Ib2 , we select
33 I1=10*(10^-3); //in A
34 Vbe = 0.7; //in V
35
36 V2 = Vbe + Vr;
37
38 R1 = (Vo-V2)/I1;
39 R2 = V2/I1;
40
41 //We are selecting Texas Instruments 2N1722 silicon
   power transistor , so following parameters are
   required
42 Ic1 = 1;//in A
43 hFE1=125;
44 hfe1=100;
45 hie1=20;
46
47 Ib1 =(1000*I1 + Il + Id)/hFE1;
48 //The current through resistor R3
49 I=Ib1 + Ic2;
50
51 R3 = (Vi - (Vbe + Vo))/I;
52 Gm = hfe2*(R2/(R2+R1))*(1/((R1*R2/(R1+R2))+hie2+(1+
   hfe2)*Rz)) ;
53 Sv = (10^-3)/(Gm*R3);
54 disp(Sv, 'Sv=');
55
56 //End

```

Scilab code Exa 18.1.c Find output resistance Ro

```
1 clear;
2 clc;
3
4 //Caption :Find output resistance Ro
5 //Given Data
6 Vo=25; //in V
7 ro=10; //in ohm
8 Rz = 12; //in ohm
9 Vo=25; //output voltage in V
10 Vr = 7.5 + 7.5; //because two diodes are used
11 Iz = 20; //in mA
12 Ie2=10; //in mA
13 Ic2 = Ie2;
14 Icmax=30; //in mA
15 Vcemax=45; //in V
16 hFE2=220;
17 hfe2=200;
18 hie2=800; //in ohm
19 Id=10; //in mA
20 Il = 1000; //in mA
21 Vi = 50; //in V
22 dVi = 10; //change in input voltage
23 dIl = 1; //change in load current
24
25 //For D1 and D2 operate
26 Iz = Id + Id;
27 Rd = (Vo-Vr)/Id;
28
29 Ib2 = (1000*Ic2)/hFE2;
30
31 //Since we require I1>Ib2 , we select
32 I1=10*(10^-3); //in A
33 Vbe = 0.7; //in V
34
35 V2 = Vbe + Vr;
36
```

```

37 R1 = (Vo-V2)/I1;
38 R2 = V2/I1;
39
40 //We are selecting Texas Instruments 2N1722 silicon
   power transistor , so following parameters are
   required
41 Ic1 = 1;//in A
42 hFE1=125;
43 hfe1=100;
44 hie1=20;
45
46 Ib1 =(1000*I1 + Il + Id)/hFE1;
47 //The current through resistor R3 is
48 I=Ib1 + Ic2;
49
50 R3 = (Vi - (Vbe + Vo))/I;
51
52 Gm = hfe2*(R2/(R2+R1))*(1/((R1*R2/(R1+R2))+hie2+(1+
   hfe2)*Rz)) ;
53 disp(Gm, 'Gm=' );
54
55 Ro = (ro + (((1000*R3) + hie1)/(1+hfe1)))/(1 + (Gm
   *((1000*R3) + ro)));
56 disp('K',Ro, 'The output impedance is = ');
57
58 //End

```

Scilab code Exa 18.1.d Calculation of change in output voltage due to change in in

```

1 clear;
2 clc;
3
4 //Caption: Calculation of change in output voltage
   due to change in input voltage and load current
5 //Given Data

```

```

6 Vo=25; //in V
7 ro=10; //in ohm
8
9 Rz = 12; //in ohm
10 Vo=25; //output voltage in V
11 Vr = 7.5 + 7.5; //because two diodes are used
12 Iz = 20; //in mA
13 Ie2=10; //in mA
14 Ic2 = Ie2;
15 Icmax=30; //in mA
16 Vcemax=45; //in V
17 hFE2=220;
18 hfe2=200;
19 hie2=800; //in ohm
20 Id=10; //in mA
21 Il = 1000; //in mA
22 Vi = 50; //in V
23 dVi = 10; //change in input voltage
24 dIl = 1; //change in load current
25
26 //For D1 and D2 operate
27 Iz = Id + Id;
28 Rd = (Vo-Vr)/Id;
29
30 Ib2 = (1000*Ic2)/hFE2;
31
32 //Since we require I1>Ib2 , we select
33 I1=10*(10^-3); //in A
34 Vbe = 0.7; //in V
35
36 V2 = Vbe + Vr;
37
38 R1 = (Vo-V2)/I1;
39 R2 = V2/I1;
40
41 //We are selecting Texas Instruments 2N1722 silicon
   power transistor , so following parameters are
   required

```

```

42 Ic1 = 1; //in A
43 hFE1=125;
44 hfe1=100;
45 hie1=20;
46
47 Ib1 =(1000*I1 + I1 + Id)/hFE1;
48 //The current through resistor R3 is
49 I=Ib1 + Ic2;
50
51 R3 = (Vi - (Vbe + Vo))/I;
52
53 Gm = hfe2*(R2/(R2+R1))*(1/((R1*R2/(R1+R2))+hie2+(1+
    hfe2)*Rz)) ;
54 Sv = (10^-3)/(Gm*R3);
55
56 Ro = (ro + (((1000*R3) + hie1)/(1+hfe1)))/(1 + (Gm
    *((1000*R3) + ro)));
57
58 dVo = (Sv*dVi)+(Ro*dI1);
59 disp('V',dVo,'Change in output voltage = ');
60
61 //End

```

Scilab code Exa 18.2.a SCR half wave power control circuit

```

1 clear;
2 clc;
3
4 //Caption:SCR half wave power control circuit
5 //Given Data
6 Vs=230; //in V
7 Rl=200; //in ohm
8 //Trigger is adjusted so that conduction starts
     after 60degree of start of cycle
9 //Instantaneous Current il = (230*2^0.5*sin(a))/200

```

```

10
11 // to find rms value
12 xo = %pi/3; //lower limit of integration
13 x1 = %pi; //upper limit of integration
14
15 X = integrate( '( (230*(2^0.5)*sin(x))/200)^2 ', 'x' ,xo ,
    x1);
16 Irms = (X/(2*pi))^0.5;
17 disp('A',Irms,'Irms = ');
18
19 //End

```

Scilab code Exa 18.2.b SCR half wave power control circuit

```

1 clear;
2 clc;
3
4 //Caption:SCR half wave power control circuit
5 //Given Data
6 Vs=230; //in V
7 Rl=200; //in ohm
8 //Trigger is adjusted so that conduction starts
    after 60degree of start of cycle
9 //Instantaneous Current il = (230*2^0.5*sin(a))/200
10 //It is noted that between 0 to pi/3 SCR voltage
    equals line voltage and between pi/3 to pi it is
    zero and for the rest it is equal to line voltage
11 //Vl = 230*2^0.5*sin(x)
12 //To find instantaneous power
13
14 x0=%pi/3; //lower limit of integral
15 x1=%pi; //upper limit of integral
16 X = integrate( '(230*230*2*(sin(x)^2))/200 ', 'x' ,x0 ,x1
    );
17 P = X/(2*3.14);

```

```
18 disp( 'W' ,P , 'P=' ) ;
19
20 //End
```

Scilab code Exa 18.2.c SCR half wave power control circuit

```
1 clear;
2 clc;
3
4 //Caption:SCR half wave power control circuit
5 //Given Data
6 Vs=230; //in V
7 Rl=200; //in ohm
8 //Trigger is adjusted so that conduction starts
   after 60degree of start of cycle
9 //Instantaneous Current il = (230*2^0.5*sin(a))/200
10
11 //To find Vrms
12
13 //It is noted that between 0 to pi/3 SCR voltage
   equals line voltage and between pi/3 to pi it is
   zero and for the rest it is equal to line voltage
14 xo=0; //lower limit of first integral
15 x1=%pi/3; //upper limit of first integral
16 x2=%pi; //lower limit of second integral
17 x3=2*(%pi); //upper limit of second integral
18 X1 = integrate( '(230*(2^0.5)*sin(x))^2' , 'x' , xo , x1 );
19 X2 = integrate( '(230*(2^0.5)*sin(x))^2' , 'x' , x2 , x3 );
20 Vrms = ((X1+X2)/(2*%pi)) ^0.5;
21 disp( 'V' ,Vrms , 'Vrms=' );
22
23 //End
```

Scilab code Exa 18.3 SCR Relaxation Oscillator Phase control Circuit

```
1 clear;
2 clc;
3
4 //Caption:SCR Relaxation Oscillator Phase control
5 // Given Data
6 C=0.1; //in microF
7 V=60; //in V
8 Vb=32; //in V
9 Vh=10; //holding voltage in V
10 Ih=100; //in microA
11 c=45; //conductance angle in degree
12 cd = 360 - c; //angle in which capacitor will get
    charged
13 td = (cd/360)*(1/60); //in ms
14
15 //if the anode voltage is positive ,the SCR will fire
    when vc=32V
16 vc=32; //in V
17 //let time constant = t = R*C
18 //vc-Vh = (V-Vh)(1-exp(-td/t))
19 t = -td*log(1-((vc-Vh)/(V-Vh)));
20 disp('sec ',t,'time constant = ');
21 R = t/C; //Resistance in K
22 disp('K',R*1000,'R=');
23
24
25 //end
```
