

collector current at beta 160 = 0.001073292ampere

vce at beta 160 = -5.690062112volt

collector current at beta 80 = 0.001066667ampere

vce at beta 80 = -3.033333333volt