

voltage gain = $250 \angle 180^\circ$

input impedance = 2000ohm

current gain = 100