

voltage gain = -50

input resistance = 2600ohm

ce removed

voltage gain = -14.18439716

input resistance = 12700ohm