

Result Example-3.5(b)

when $V(i)=5V$, the transistor is operating at point M and $V(o)=0$

this corresponds to ON stage!