

Result Example-3.7(b)

when $V(i)=5V$, the transistor T(1) is operating at point C

output voltage in volts=

0.