

Result Example-3.4(b)

when $V(i)=0V$, the JFET is operating at point B, where $I(D)=3.8mA$ and $V(o)$

$=1V$

this corresponds to the switch in ON stage