

Result Example-3.4(a)

when the input voltage = $-5V$, the JFET is opening at point A, where $I(D)=$

0 and $V(0)=V(DD)=20V$

this corresponds to the switch in OFF state