

//example 3.5(a)//

when $V(i)=0$, the transistor is cutoff because the voltage between the gate and the source is below the threshold voltage. Correspondingly the output

voltage $V(0)=5V$ (point (N) as in figure)