

Result Example-7.2

for SR flip flop $Q(n+1) = S + R'Q(n)$

thus with $S = JQ'$ & $R = KQ$ we get circuit which behaves like JK flip flop