

Scilab Manual for  
Power Electronics Lab  
by Prof C Harinatha Reddy  
Electrical Engineering  
G Pulla Reddy Engineering College <sup>1</sup>

Solutions provided by  
Prof C Harinatha Reddy  
Electrical Engineering  
G Pulla Reddy ENgineering College (Autonomous)

May 10, 2025

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website <http://scilab.in>



# Contents

List of Scilab Solutions	3
1 Uncontrolled 1-phase Half and Full wave rectifier with R load	5
2 Uncontrolled 3-phase Half wave and Full wave rectifier	6
3 Controlled 1-phase Half and Full wave rectifier with R Load	9
4 Controlled 3-phase Half and Full wave rectifier with R Load	12
5 Step Down and Step up chopper with R load	17
6 1-phase AC- voltage controller with R load	20
7 1-phase Inverter (Half Bridge and H bridge ) with R load	22

# List of Experiments

# List of Figures

2.1	Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load . . . . .	7
2.2	Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load . . . . .	7
2.3	Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load . . . . .	8
2.4	Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load . . . . .	8
3.1	Circuit Diagram of 1phase Half Wave controlled Rectifier with R load . . . . .	10
3.2	Circuit Diagram of 1phase Full Wave uncontrolled Rectifier with R load . . . . .	11
4.1	Circuit Diagram of 3phase Half controlled Rectifier with R load	13
4.2	Circuit Diagram of 3phase Half controlled Rectifier with R load	14
4.3	Circuit Diagram of 3phase Full Wave controlled Rectifier with R load . . . . .	15
4.4	Circuit Diagram of 3phase Full Wave controlled Rectifier with R load . . . . .	16
5.1	Circuit Diagram of StepDownchopper with R load . . . . .	18
5.2	Circuit Diagram of Step Up chopper with R load . . . . .	19
6.1	Circuit Diagram of 1phase AC Vokltage controller with R load	21
7.1	Circuit Diagram of Half bridge Inverter with R load . . . . .	23
7.2	Circuit Diagram of Half bridge Inverter with R load . . . . .	24
7.3	Circuit Diagram of Full bridge Inverter with R load . . . . .	25
7.4	Circuit Diagram of Full bridge Inverter with R load . . . . .	26

## **Experiment: 1**

### **Uncontrolled 1-phase Half and Full wave rectifier with R load**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in) This code

can be downloaded from the website [www.scilab.in](http://www.scilab.in)

## **Experiment: 2**

### **Uncontrolled 3-phase Half wave and Full wave rectifier**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

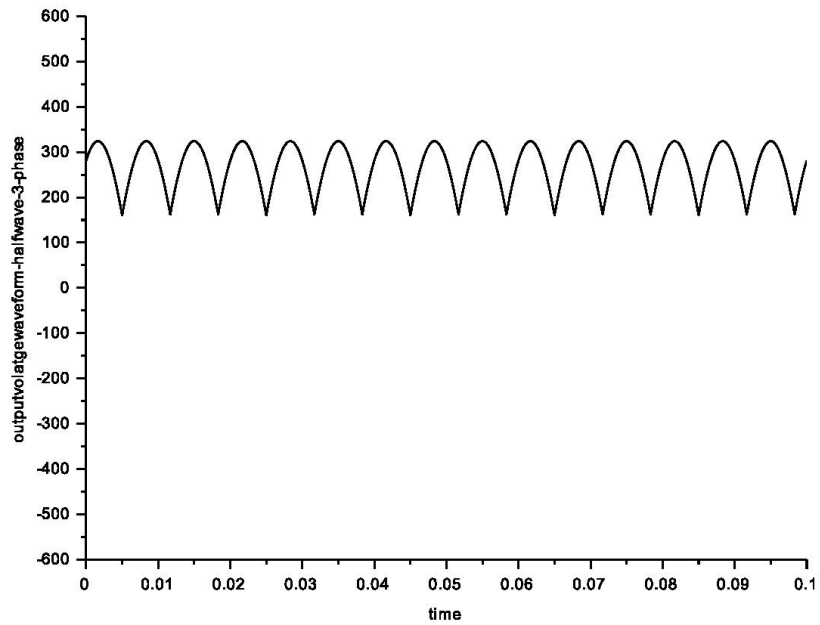


Figure 2.1: Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load

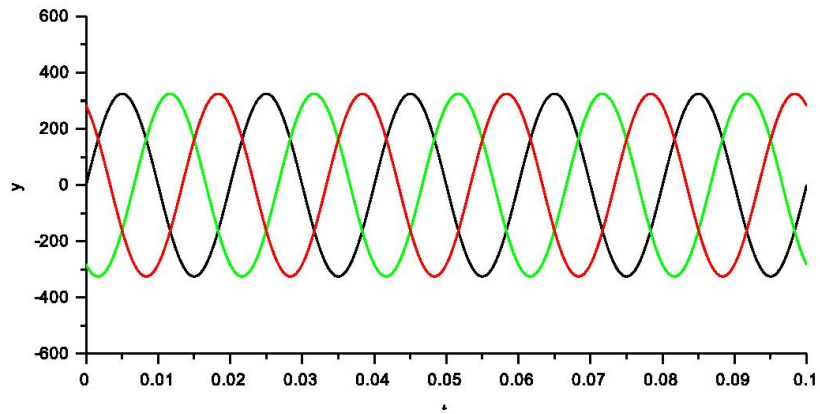


Figure 2.2: Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load



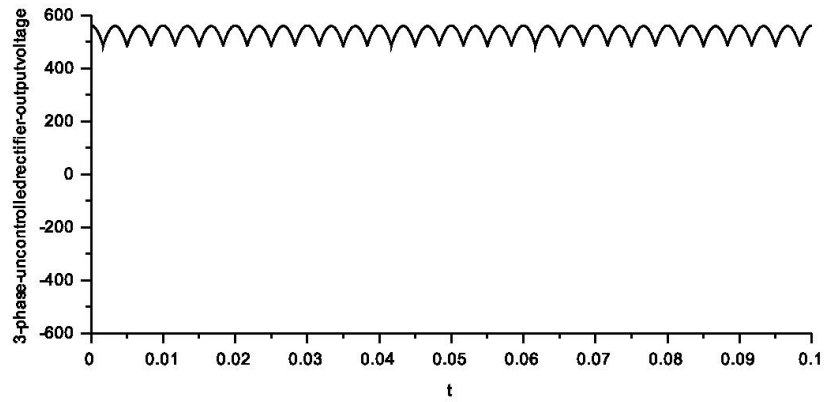


Figure 2.3: Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load

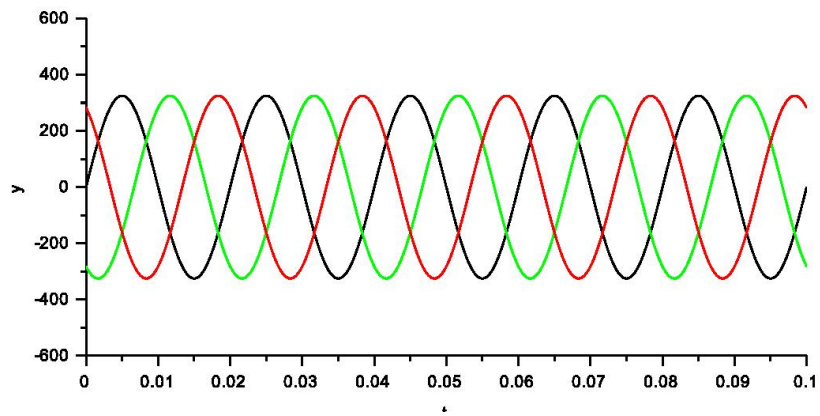


Figure 2.4: Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load

## **Experiment: 3**

### **Controlled 1-phase Half and Full wave rectifier with R Load**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in) This code

can be downloaded from the website [www.scilab.in](http://www.scilab.in)

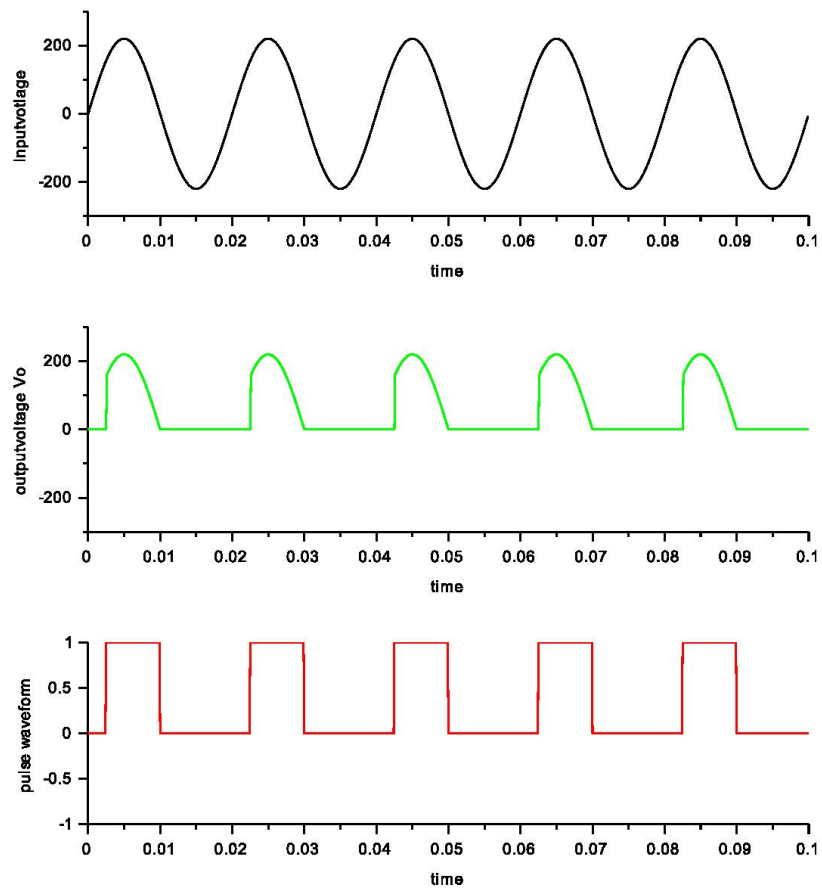


Figure 3.1: Circuit Diagram of 1phase Half Wave controlled Rectifier with R load

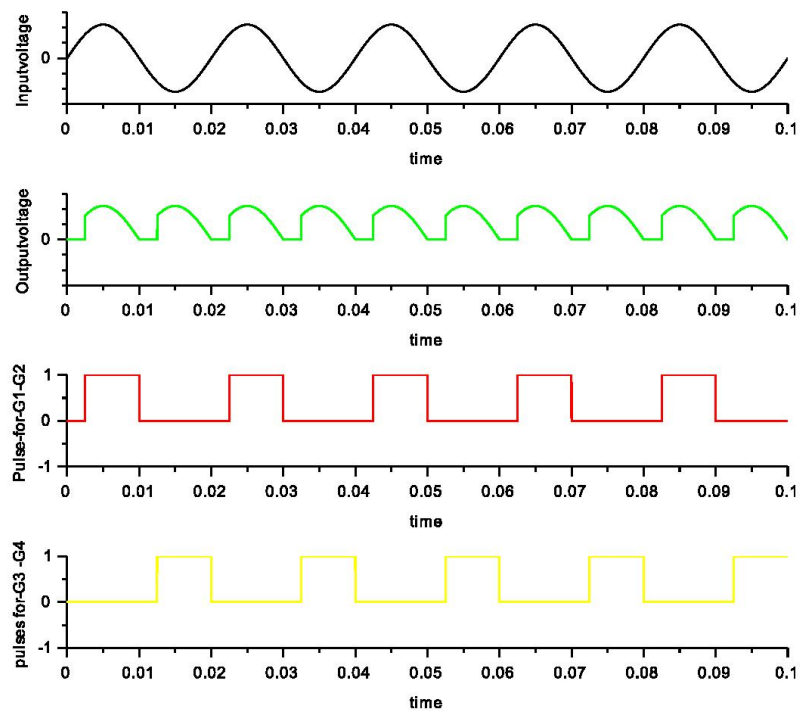


Figure 3.2: Circuit Diagram of 1phase Full Wave uncontrolled Rectifier with R load

## **Experiment: 4**

# **Controlled 3-phase Half and Full wave rectifier with R Load**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

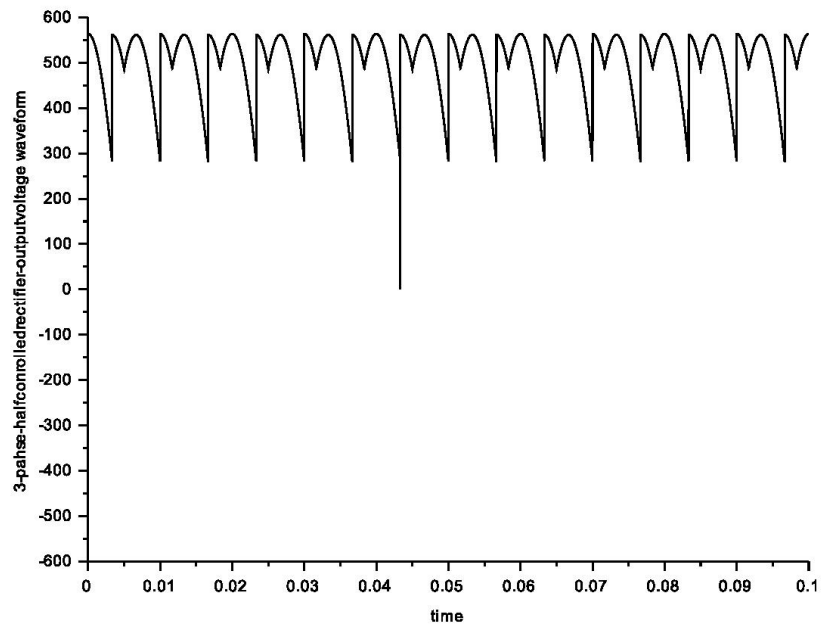


Figure 4.1: Circuit Diagram of 3phase Half controlled Rectifier with R load

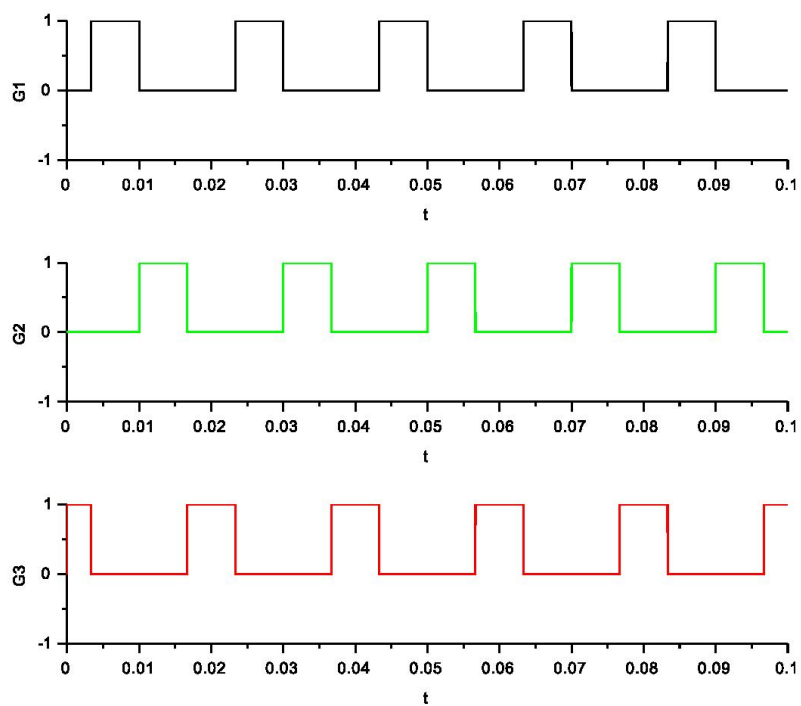


Figure 4.2: Circuit Diagram of 3phase Half controlled Rectifier with R load

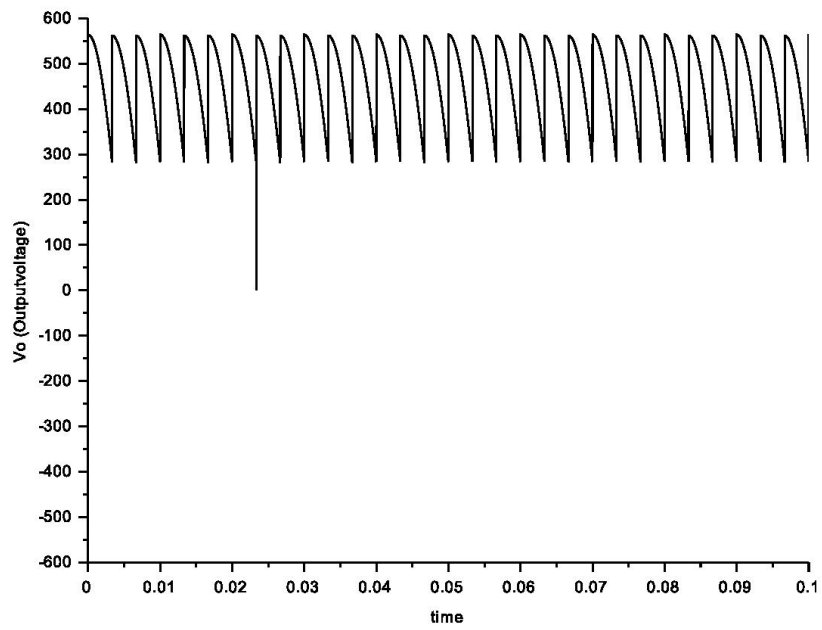


Figure 4.3: Circuit Diagram of 3phase Full Wave controlled Rectifier with R load



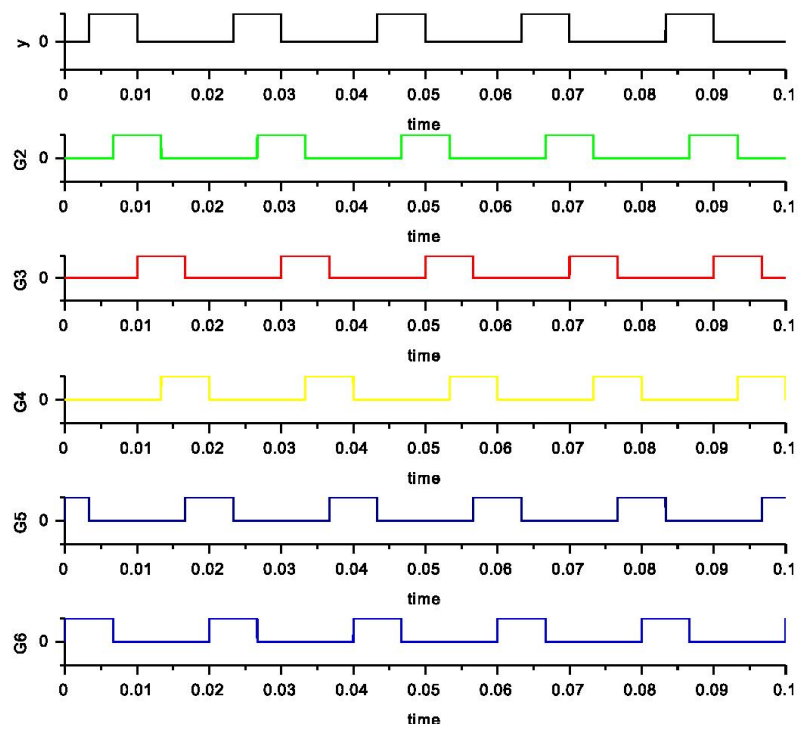


Figure 4.4: Circuit Diagram of 3phase Full Wave controlled Rectifier with R load

## **Experiment: 5**

### **Step Down and Step up chopper with R load**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

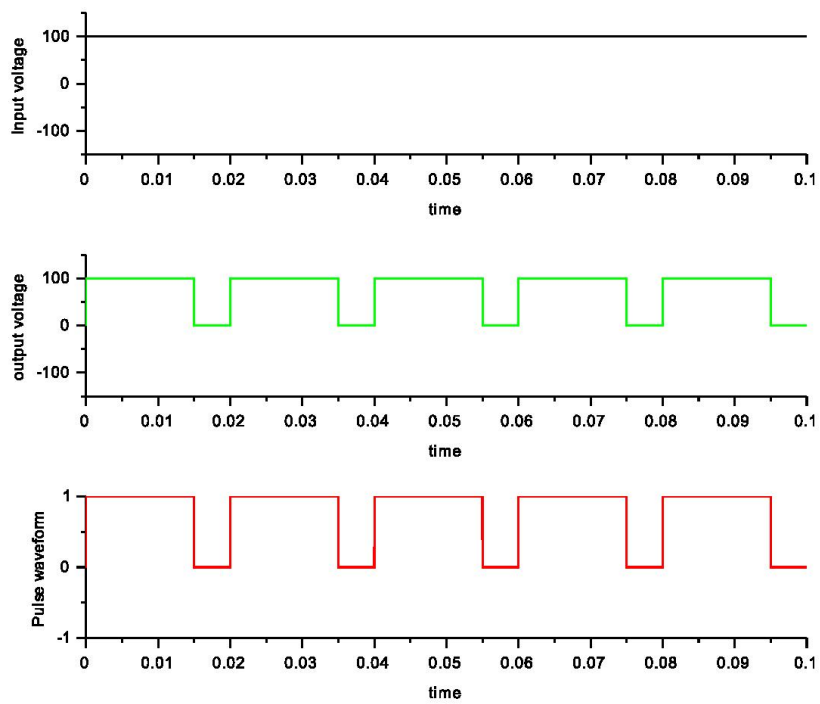


Figure 5.1: Circuit Diagram of StepDownchopper with R load

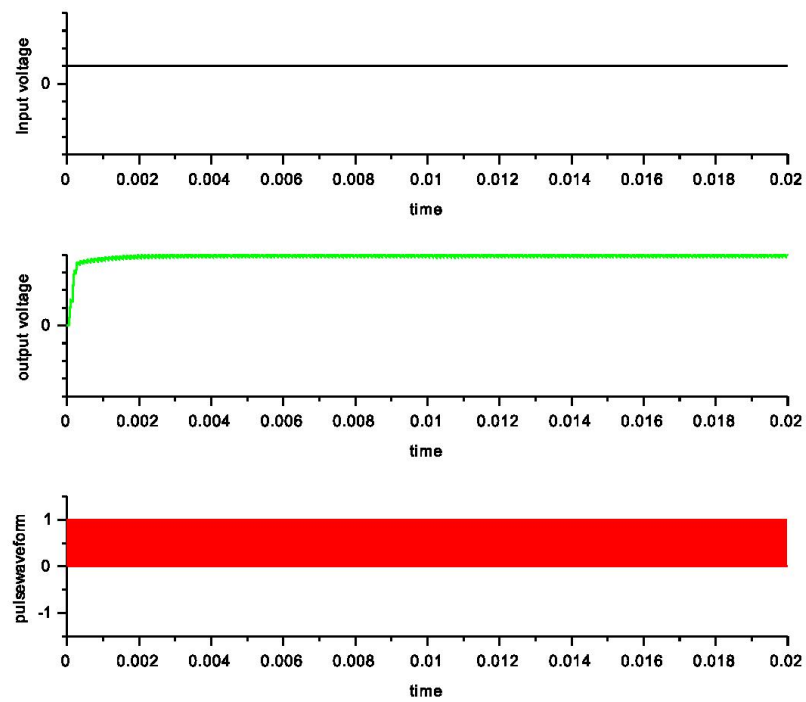


Figure 5.2: Circuit Diagram of Step Up chopper with R load

## Experiment: 6

### 1-phase AC- voltage controller with R load

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

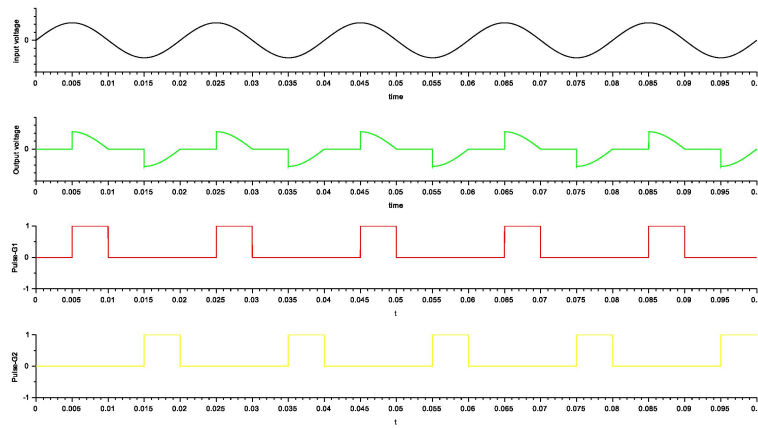


Figure 6.1: Circuit Diagram of 1phase AC Vokltage controller with R load

## Experiment: 7

### 1-phase Inverter (Half Bridge and H bridge ) with R load

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in) This code

can be downloaded from the website [www.scilab.in](http://www.scilab.in)

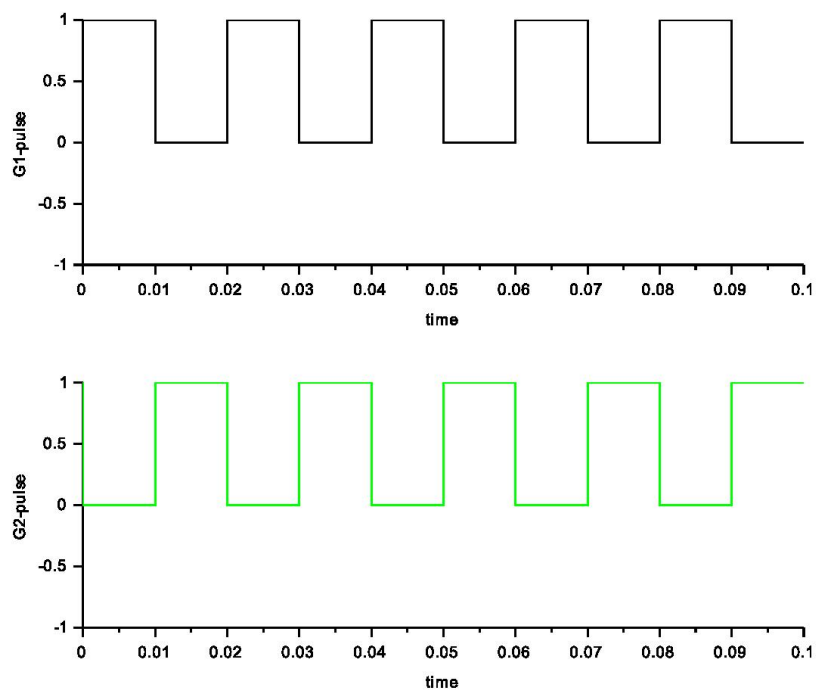


Figure 7.1: Circuit Diagram of Half bridge Inverter with R load



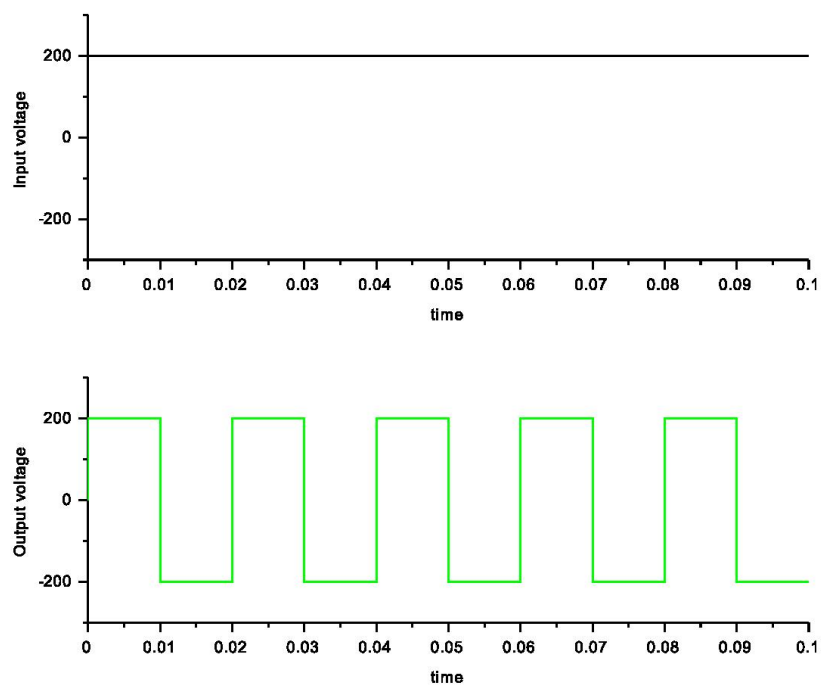


Figure 7.2: Circuit Diagram of Half bridge Inverter with R load

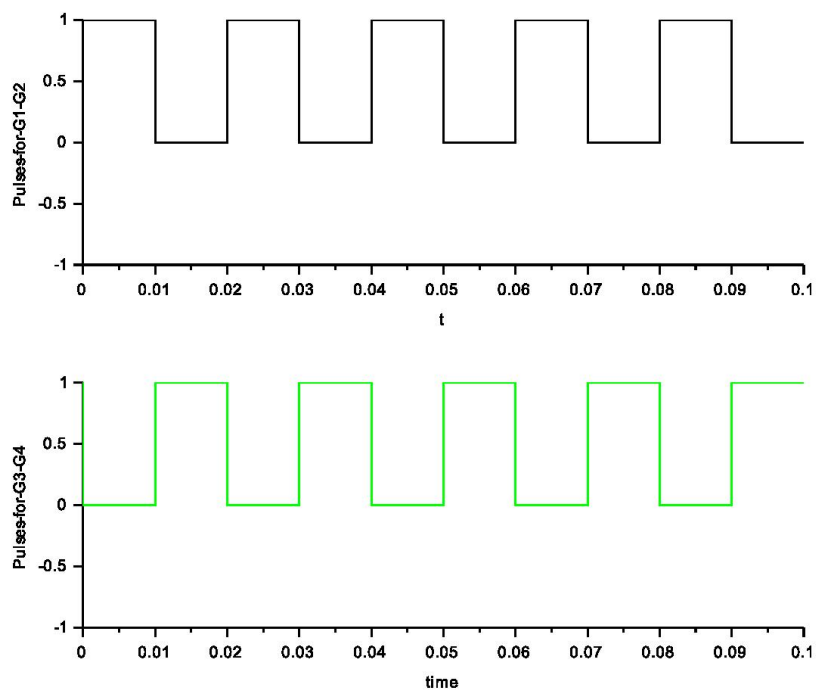


Figure 7.3: Circuit Diagram of Full bridge Inverter with R load

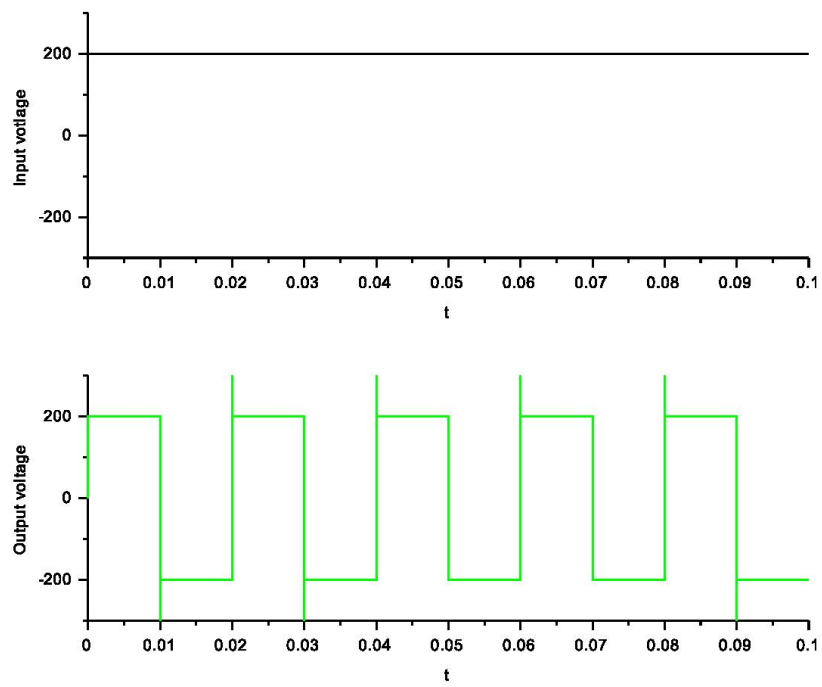


Figure 7.4: Circuit Diagram of Full bridge Inverter with R load