

Scilab Manual for  
Basic Analog VLSI lab  
by Dr Sandhya Save  
Electronics Engineering  
University of Mumbai<sup>1</sup>

Solutions provided by  
Dr Dr. Sandhya Save  
Electronics Engineering  
University of Mumbai

July 7, 2026

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website <http://scilab.in>



# Contents

List of Scilab Solutions	3
1 CMOS Inverter Amplifier	5
2 CMOS transmission gate	7
3 NMOS current mirror circuit	9
4 NMOS Cascode current mirror circuit	11
5 NMOS Wilson current mirror circuit	13

# List of Experiments

# List of Figures

1.1	CMOS inverter . . . . .	6
1.2	CMOS inverter . . . . .	6
2.1	CMOS transmission gate . . . . .	8
2.2	CMOS transmission gate . . . . .	8
3.1	Basic current mirror circuit . . . . .	10
3.2	Basic current mirror circuit . . . . .	10
4.1	Cascode current source . . . . .	12
4.2	Cascode current source . . . . .	12
5.1	Wilson current mirror . . . . .	14
5.2	Wilson current mirror . . . . .	14

# Experiment: 1

## CMOS Inverter Amplifier

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

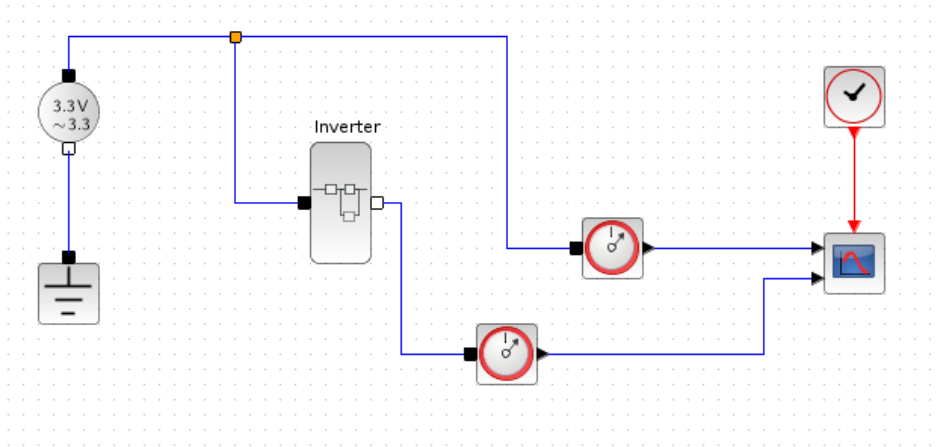


Figure 1.1: CMOS inverter

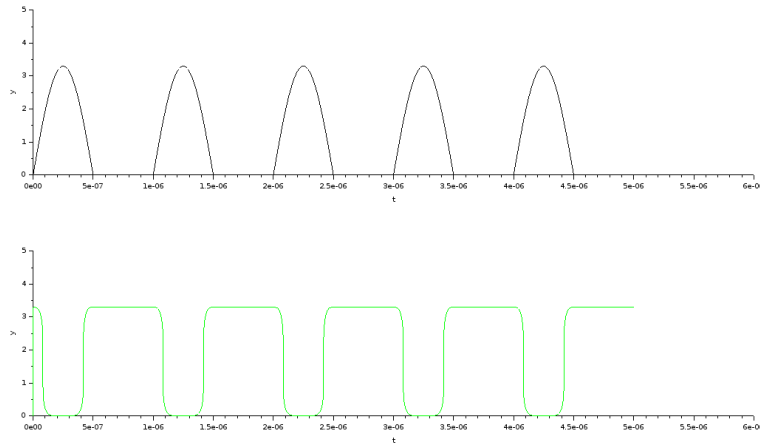


Figure 1.2: CMOS inverter

# Experiment: 2

## CMOS transmission gate

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

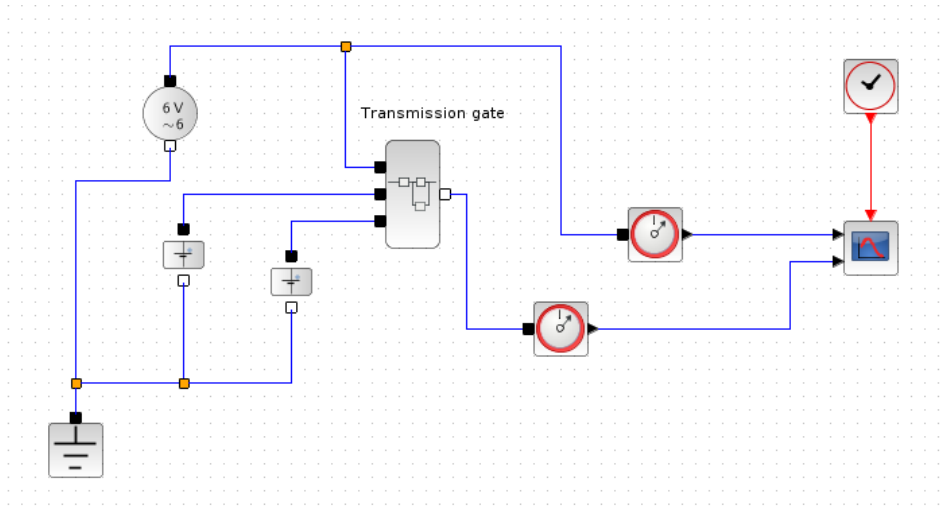


Figure 2.1: CMOS transmission gate

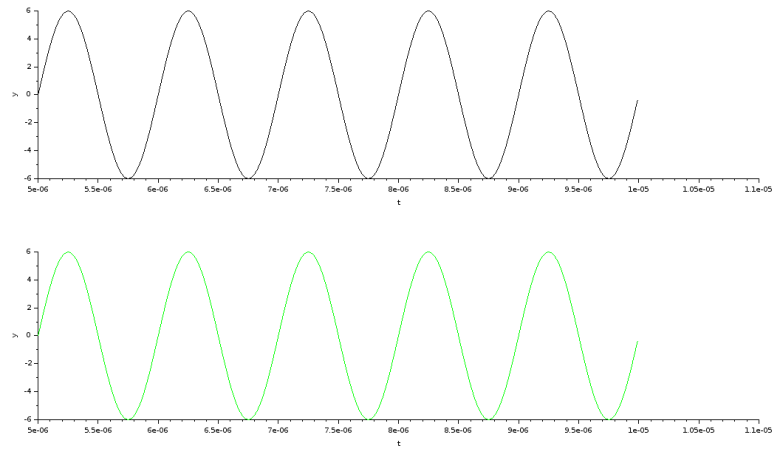


Figure 2.2: CMOS transmission gate

## **Experiment: 3**

# **NMOS current mirror circuit**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

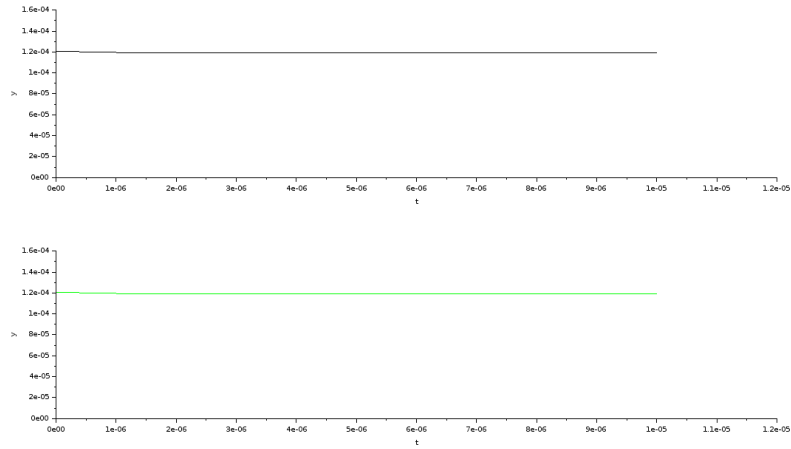


Figure 3.1: Basic current mirror circuit

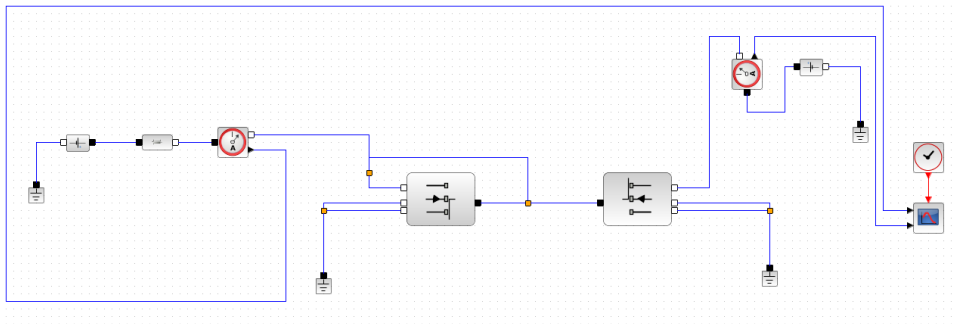


Figure 3.2: Basic current mirror circuit

## **Experiment: 4**

# **NMOS Cascode current mirror circuit**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

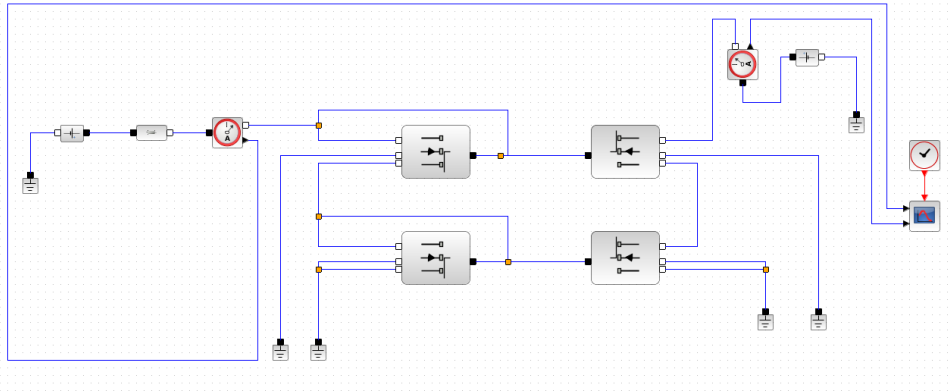


Figure 4.1: Cascode current source

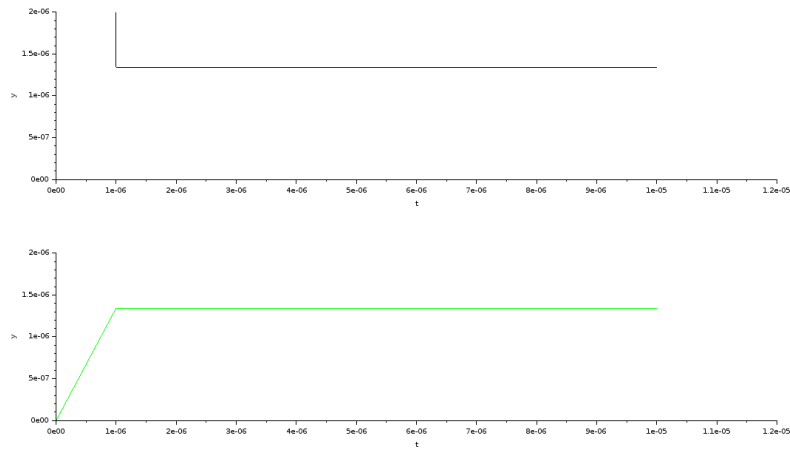


Figure 4.2: Cascode current source

## **Experiment: 5**

### **NMOS Wilson current mirror circuit**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

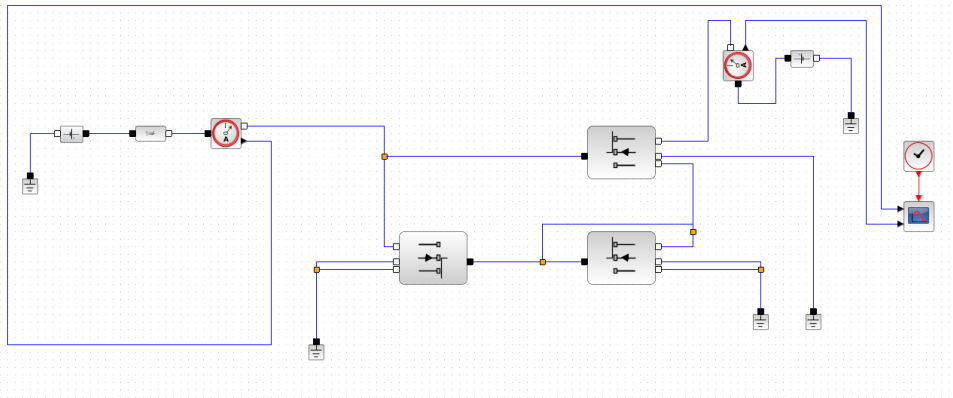


Figure 5.1: Wilson current mirror

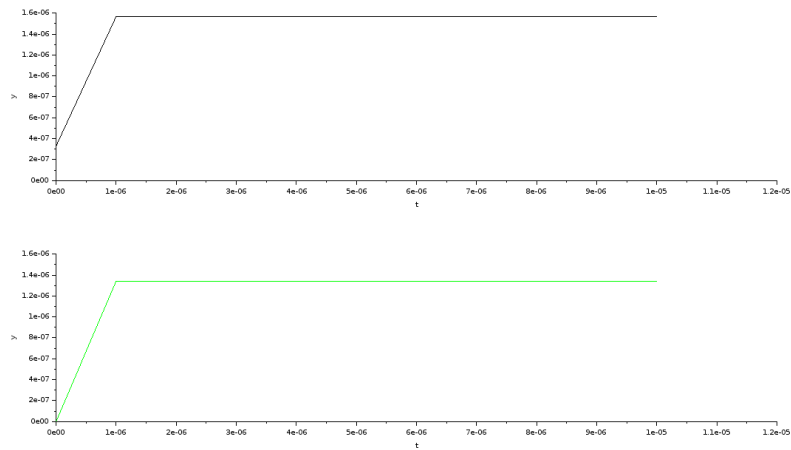


Figure 5.2: Wilson current mirror