

Scilab Manual for  
Basic Analog VLSI lab  
by Dr Sandhya Save  
Electronics Engineering  
University of Mumbai<sup>1</sup>

Solutions provided by  
Dr Dr. Sandhya Save  
Electronics Engineering  
University of Mumbai

June 17, 2026

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website <http://scilab.in>



# Contents

List of Scilab Solutions	3
1 CMOS Inverter Amplifier	5
2 CMOS transmission gate	7
3 NMOS current mirror circuit	9
4 NMOS Cascode current mirror circuit	11
5 NMOS Wilson current mirror circuit	13

# List of Experiments

# List of Figures

1.1	CMOS inverter	6
1.2	CMOS inverter	6
2.1	CMOS transmission gate	8
2.2	CMOS transmission gate	8
3.1	Basic current mirror circuit	10
3.2	Basic current mirror circuit	10
4.1	Cascode current source	12
4.2	Cascode current source	12
5.1	Wilson current mirror	14
5.2	Wilson current mirror	14

# Experiment: 1

## CMOS Inverter Amplifier

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

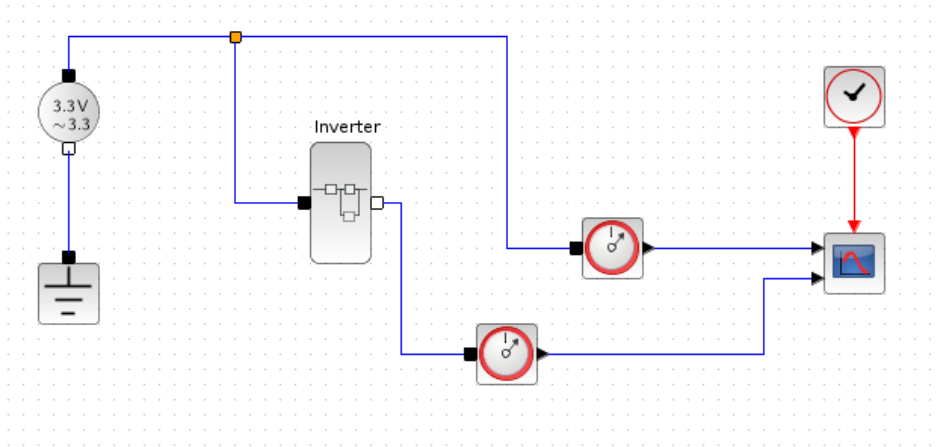


Figure 1.1: CMOS inverter

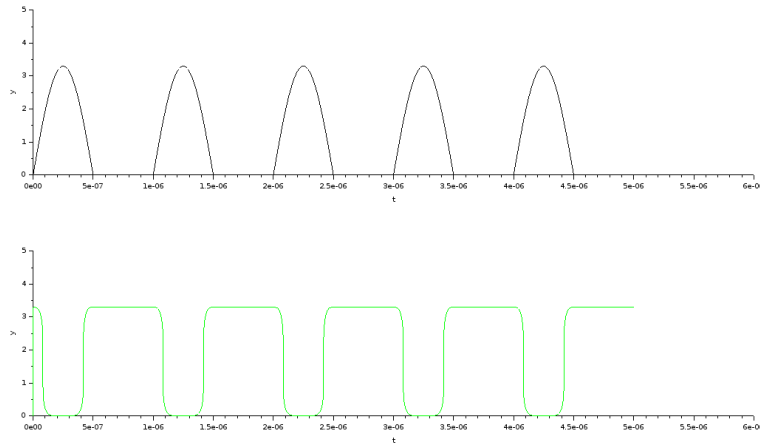


Figure 1.2: CMOS inverter

## **Experiment: 2**

# **CMOS transmission gate**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

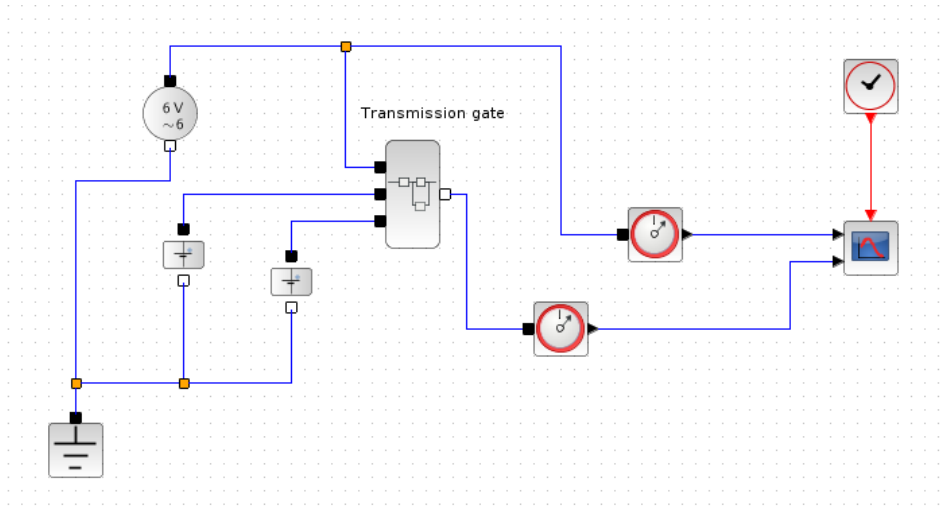


Figure 2.1: CMOS transmission gate

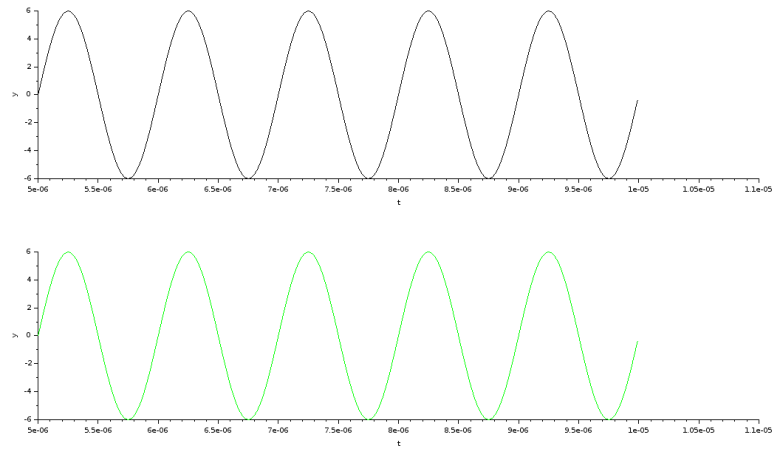


Figure 2.2: CMOS transmission gate

## **Experiment: 3**

# **NMOS current mirror circuit**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

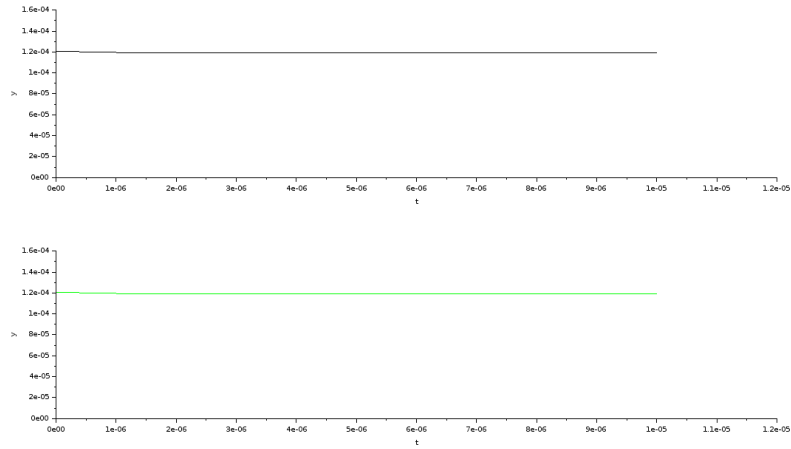


Figure 3.1: Basic current mirror circuit

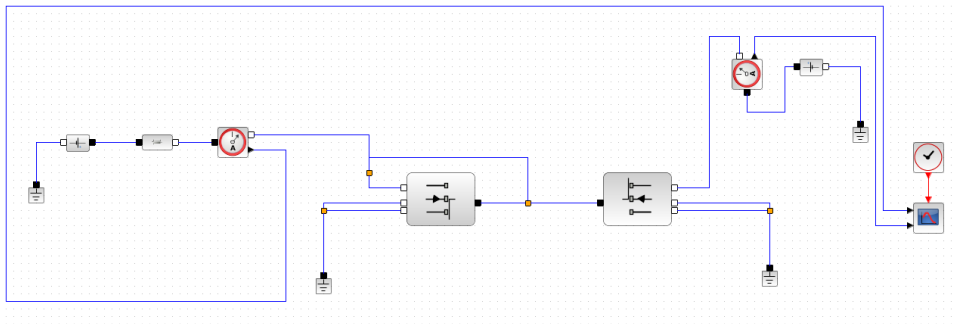


Figure 3.2: Basic current mirror circuit

## **Experiment: 4**

# **NMOS Cascode current mirror circuit**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

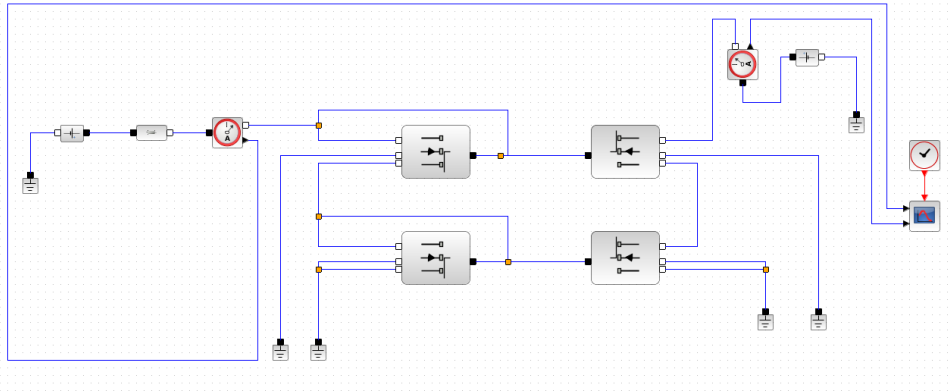


Figure 4.1: Cascode current source

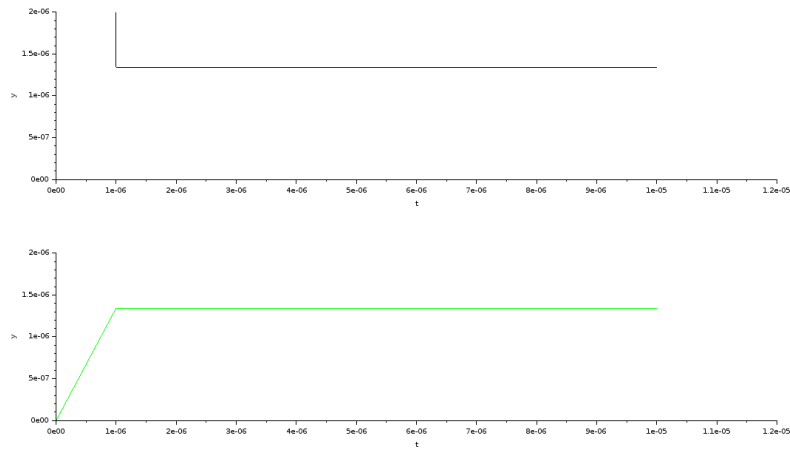


Figure 4.2: Cascode current source

## **Experiment: 5**

### **NMOS Wilson current mirror circuit**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

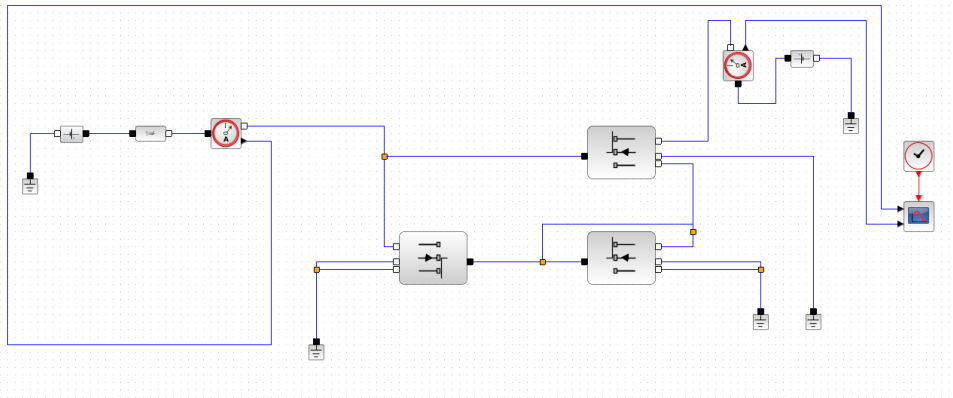


Figure 5.1: Wilson current mirror

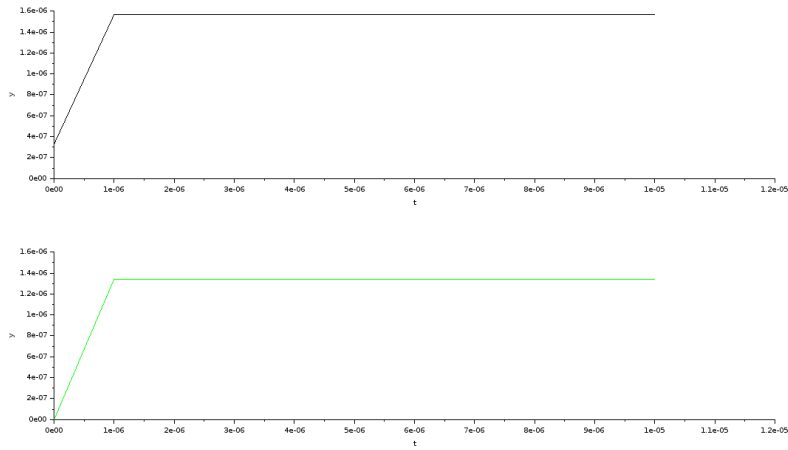


Figure 5.2: Wilson current mirror