

Scilab Textbook Companion for
Power Electronics
by P. S. Bimbra¹

Created by
Navdeep Kumar
B.E.
Electrical Engineering
Thapar University
College Teacher
Dr. Sunil Kumar Singla
Cross-Checked by
Lavitha Pereira

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Power Electronics

Author: P. S. Bimbra

Publisher: Khanna Publishers, New Delhi

Edition: 5

Year: 2012

ISBN: 978-81-7409-279-3

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
2 Power Semiconductor Diodes and Transistors	5
3 Diode Circuits and Rectifiers	9
4 Thyristors	21
5 Thyristor Commutation Techniques	35
6 Phase Controlled Rectifiers	41
7 Choppers	64
8 Inverters	78
9 AC Voltage Controllers	92
10 Cycloconverters	98
11 Some Applications	101
12 Electric Drives	105
13 Power Factor Improvement	134

List of Scilab Codes

Exa 2.1	to find switching freq of the transistor . . .	5
Exa 2.2	to determine avg power loss due to collector current and also to find peak instantaneous power loss due to collector current	6
Exa 2.3	to obtain power loss during turn off time and turn off period and also instant power loss during fall time	7
Exa 2.4	to find switching freq of the transistor . . .	8
Exa 3.2	to find the conduction time of diode peak current through diode and final steady state voltage	9
Exa 3.6	to determine conduction time of diode and rate of change of current	9
Exa 3.7	to find the time required to deliver a charge of 200Ah	10
Exa 3.8	to calculate the power delivered to the heater and find peak diode current and input pf . .	10
Exa 3.9	to find 1 the value of avg chargng current 2 power supplied to battery and that dissipated in the resistor 3 supply pf 4 charging time 5 rectifier efficiency and PIV of diode	11
Exa 3.10	to determine the effect of reverse recovery time on the avg output voltage	12
Exa 3.11	to determine 1 avg value of output voltage and output current 2 avg and rms values of diode currents 3 rms values of output and input currrents and supply pf	12

Exa 3.12	to calculate 1 peak load current 2 dc load current 3 dc diode current 4 percentage regulation from no load to full load	13
Exa 3.13	to design a zener voltage regulator to meet given specifications	14
Exa 3.14	to find R1 and R2	14
Exa 3.15	to find the VA rating of the transformer . .	15
Exa 3.16	to determine 1 avg value of output voltage 2 input current distortion factor 3 input displacement factor 4 input pf 5 input current harmonic factor and 6 crest ratio	
Exa 3.17	to determine diode rating and transformer rating	15
Exa 3.18	to calculate avg value of output voltage avg and rms values of diode current and power delivered to diode	16
Exa 3.19	determine the ratings of diodes and of 3ph deltarstar transformer	17
Exa 3.20	to determine 1 power delivered to battery and load 2 input displacement factor 3 current distortion factor 4 input pf 5 input HF 6 transformer rating	18
Exa 3.21	design capacitor filter and avg value of output voltage with and without filter	19
Exa 3.22	to find the value of L with different R and CRF without L	20
Exa 3.23	to design LC filter	20
Exa 4.2	to plot allowable gate voltage as the function of gate current and to find avg gate power dissipation	21
Exa 4.3	to compute gate source resistance	21
Exa 4.4	to compute gate source resistance trigger voltage and trigger current	22
Exa 4.5	to compute 1 resistance 2 triggering freq 3 duty cycle of the triggering pulse	22
Exa 4.6	to compute min width of gate pulse current	23
Exa 4.8	to calculate trigger voltage and trigger current	24

Exa 4.9	to compute avg on current rating for half sine wavecurrent for various conduction angles	24
Exa 4.10	to compute avg on current rating for half sine wave current for various conduction angles	25
Exa 4.11	to calculate surge current rating and power rating	26
Exa 4.12	to find maximum value of the remedial parameter	26
Exa 4.16	to calculate fault clearance time	26
Exa 4.17	1 to calculate the max values of change in current and change in voltage for SCR 2 rms and avg current rating and 3 suitable voltage rating	27
Exa 4.19	1 to check heat sink selection is satisfactory 2 to choose heat sink for given requirements and ckt efficiency 3compute case and junction temp	28
Exa 4.20	to find total avg power loss and percentage inc in device rating	29
Exa 4.21	to determine voltage across each SCR and discharge current across each capacitor	29
Exa 4.22	to calculate number of series and parrallel units of SCRs	30
Exa 4.23	to calculate the resistance	31
Exa 4.25	to compute value of various resistances	32
Exa 4.26	to compute max and min values of R and the corresponding freq	32
Exa 4.27	to find max and min firing angles for triac	33
Exa 5.1	to determine 1 conduction time and 2 voltage across thyristor	35
Exa 5.2	to calculate 1 conduction time for auxillary thyristor 2 voltage across and 3 circuit turn off time for main thyristor	35
Exa 5.3	to determine 1 peak value of current 2 value of capacitor C	36
Exa 5.4	to calculate 1 value of current 2 circuit turn off time for main and auxillary thyristor	37
Exa 5.5	to compute min value of C	37

Exa 5.6	to find circuit turn off time	38
Exa 5.7	to find conduction time of thyristor	38
Exa 5.8	1 to calculate value of Capacitor 2 determine value of Resistance	38
Exa 5.9	calculate 1 time at which commutation of main thyristor gets initiated 2 ckt turn off time .	39
Exa 5.11	to find current in R and L	39
Exa 5.12	To find the current in R and L and voltage across C	40
Exa 6.1	to calculate the power absorbed in the heater element	41
Exa 6.2	1 to find value of charging current 2 power supplied to battery and dissipated by resistor 3 calculate the supply pf	41
Exa 6.3	1 to find value of charging current 2 power supplied to battery and dissipated by resistor 3 calculate the supply pf	42
Exa 6.4	to find ckt turn off time avg output voltage and avg load current	43
Exa 6.5	to determine 1 rectification efficiency 2 form factor 3 voltage ripple factor 4 transformer utilisation factor 5 PIV of thyristor	44
Exa 6.6	to find power handled by mid pt convertor and single phase bridge convertor	45
Exa 6.7	compute firing angle delay and pf	45
Exa 6.9	to find avg output current and power delivered	46
Exa 6.10	to find avg value of load current and new value under given changed conditions	46
Exa 6.11	to calculate the input and output performance parameters for full conductor	47
Exa 6.12	to calculate the input and output performance parameters for single phase semi conductor .	48
Exa 6.13	determine 1 firing angle 2 avg and rms values of load current 3 rectification efficiency . . .	49
Exa 6.15	to calculate 1 avg value of load volatage 2 avg and rms current and PIV 3 avg power dissipation in each thyristor	49
Exa 6.17	to compute firing angle delay and supply pf	50

Exa 6.18	to find commutation time and reverse voltage across SCR	51
Exa 6.19	to find the magnitude of per phase input supply voltage	51
Exa 6.20	to find magnitude of input per phase supply voltage	52
Exa 6.21	to find magnitude of input per phase supply voltage	52
Exa 6.22	to compute firing angle delay and supply pf	53
Exa 6.23	to calculate rectification efficiency TUF and input power factor	53
Exa 6.24	to find DF CDF THD and pf and to calculate the active and reactive input powers	54
Exa 6.25	calculate the power delivered to load and input pf	55
Exa 6.26	calculate overlap angle for different firing angles	56
Exa 6.28	to calculate firing angle delay and overlap angle	56
Exa 6.29	to calculate firing angle firing angle delay and overlap angle	57
Exa 6.31	calculate the peak value of circulating current	58
Exa 6.32	to determine 1 avg output voltage 2 avg output current 3 avg and rms values of thyristor currents 4 pf	58
Exa 6.33	to determine 1 avg output voltage 2 angle of overlap 3 pf	59
Exa 6.34	calculate the generator mean voltage	59
Exa 6.35	find the mean value of E	60
Exa 6.36	to find avg current through battery	61
Exa 6.37	to determine 1 avg output voltage 2 avg output current 3 avg and rms values of thyristor currents 4 avg and rms values of diodes currents 5 i pf 6 ckt turn off time	61
Exa 6.38	to calculate peak value of circulating currents and of both convertors	62
Exa 6.39	to estimate triggering angle for no current transients and for worst transients	62

Exa 7.2	to calculate 1 avg and rms values of output voltage 2 chopper efficiency	64
Exa 7.3	to compute pulse width of output voltage and avg value of new output voltage	64
Exa 7.4	to find time ratio for chopper	65
Exa 7.5	to compute pulse width of output voltage and avg value of new output voltage	65
Exa 7.11	1 to find whether load current is cont 2 calculate value of avg op current 3 to find its max and min values 4 find rms values of various harmonics 5 compute avg value of supply current 6 ip power power absorbed by load counter emf and power loss in res	66
Exa 7.12	1 to find whether load current is cont or not 2 to calculate avg output voltage and avg current 3 to compute max and min values of output current	67
Exa 7.13	to find the chopping freq	68
Exa 7.14	to find the value of external inductance to be added in series	69
Exa 7.15	1 to calculate min and and max value of load current 2 max value of ripple current 3 avg and rms values of load current 4 rms value of chopper current	69
Exa 7.17	to find the time for which current flows . . .	70
Exa 7.18	to calculate values of commutating capacitor and commutating inductor	70
Exa 7.19	to calculate the value of comutating component C and comutating component L	71
Exa 7.20	to compute 1 effective on period 2 peak current through main and auxillary thyristor 3 their turn off times 4 total commutation intervals 5 capacitor voltage 6 time needed to recharge the capacitor	72
Exa 7.21	to calculate values of 1 commuting components C and L and 2 min and max output voltages	73

Exa 7.22	calculate 1 value of commutating inductor and capacitor 2 max capacitor voltage 3 peak commutating current	73
Exa 7.23	to compute 1 turn off time of main thyristor 2 total commutation interval 3 turn off time of auxillary thyristor	74
Exa 7.24	to calculate min and max value of load current	75
Exa 7.27	calculate 1 range of speed control 2 range of duty cycle	75
Exa 7.28	determine chopping freq and duty cycle . . .	76
Exa 7.29	to determine the higher limit of current pulsation chopping freq and duty cycle ratio . .	77
Exa 8.3	to find the value of C for having load commutation	78
Exa 8.4	to find the power delivered	78
Exa 8.5	to find the power delivered to the load . . .	79
Exa 8.6	to find rms value of thyristor and diode currents	79
Exa 8.7	to find 1 rms value of fundamental load current 2 power absorbed by the load and fundamental power 3 rms and peak currents of each thyristor 4 conduction of thyristors and diodes	80
Exa 8.8	to determine 1 fundamental rms output voltage 2 total output power and fundamenetal freq power 3 avg and peak currents of each thyristor 4 input pf 5 distortion factor and THD and 6 harmonic factor foe lowest harmonic	81
Exa 8.9	to calculate 1 rms value of output voltage and fundamental component of output voltage 2 output power 3 fundamental freq output power 4 avg and peak currents of each transistor 5 peak reverse blocking voltage 6 harmonic factor for third harmonic 7 THD .	82

Exa 8.10	1 to calculate THD of output voltage and its distortion factor 2 to calculate THD of output current and its distortion factor 3 load power and avg dc source current 4 conduction time of each transistor and diode 5 peak and rms current of each transistor	83
Exa 8.11	to determine 1 rms value of load current 2 rms value of thyristor current 3 load power .	84
Exa 8.12	to determine power delivered to load for 1 square wave output 2 quasi square wave output 3 symmitrically placed pulses	85
Exa 8.14	to determine the value of source inductance and also find value of commutating capacitors	86
Exa 8.15	to check whether the ckt will commutate by itself or not and the voltage across the capacitor and inductor at the commutation	87
Exa 8.16	to calculate output freq	88
Exa 8.17	To determine 1 ckt turn off time 2 max possible operating freq	89
Exa 8.18	to calculate power delivered to the load and avg and rms values of thyristor current	89
Exa 8.19	to find the value of capacitor C for given conditions	90
Exa 8.20	to calculate 1 rms values of phase and line voltages 2 rms value of fundamental component of phase and line voltages 3 THD for voltages 4 load power and avg source current 5 avg value of thyristor current	90
Exa 9.1	to determine 1 rms value of output voltage 2 power delivered to the load and input pf 3 avg input current	92
Exa 9.2	to calculate 1 rms value of output voltage 2 load power and input pf 3 avg and rms currents of thyristors	93
Exa 9.3	to determine 1 rms output voltage 2 input pf 3 avg and rms thyristor currents	93
Exa 9.4	to calculate 1 max values of avg and rms thyristor currents 2 min ckt turn off time	94

Exa 9.5	to calculate 1 control range of firing angle 2 max value of rms load current 3 max power and pf 4 max value of avg and rms thyristor currents 5 max possible value of current rating	94
Exa 9.6	to calculate extinction angle and rms value of output voltage	95
Exa 9.8	to calculate 1 rms value of output voltage 2 rms value of current for upper thyristors 3 rms value of current for lower thyristors 4 transformer VA rating 5 input pf	96
Exa 10.2	to calculate 1 rms value of output voltage 2 rms current of each converter 3 rms current of each thyristor and 4 input pf	98
Exa 10.4	to compute 1 value of fundamental rms output voltage 2 rms output current 3 output power	98
Exa 10.5	to compute 1 value of fundamental rms output voltage 2 rms output current 3 output power Here 6 pulse bridge convertor is employed	99
Exa 10.7	to calculata rms value of load voltage for various firing angle delays	100
Exa 11.1	to calculate 1 firing angle of the rectifier 2 output voltage 3 dc link voltage	101
Exa 11.2	To calculate rms current and peak reverse voltage ratings for each of thyristor valves .	101
Exa 11.3	to determine voltage and current rating of 1 thyristor and 2 diodes of the bridge	102
Exa 11.4	to find the value of parameters of R2 C and load resistance	103
Exa 11.5	to calculate 1 depth of heat of penetration 2 heat generated per unit cylinder surface area and 3 heat generated per unit cylinder volume	103
Exa 11.6	to calculate reqd capacitor size	104
Exa 12.1	To determine 1 firing angle delay of armature converter 2 rms value of thyristor and free-wheeling diode currents 3 input pf of armature converter	105

Exa 12.2	calculate the avg armature current and the motor torque	106
Exa 12.3	to determine 1 motor current 2 motor torque 3 input pf	106
Exa 12.4	to determine 1 rated armature current 2 firing angle delay of armature convertor 3 speed regulation at full load 4 input pf of armature convertor and drive	107
Exa 12.5	to calculate 1 delay angle of field converter 2 delay angle of armature converter 3 power fed back to the supply	108
Exa 12.6	To compute 1 motor speed 2 torque developed	108
Exa 12.7	to compute firing angle and motor speed . .	109
Exa 12.8	to calculate the speed of the motor	110
Exa 12.9	to compute rms value of source and thyristor currents avg value of thyristor currents and input supply pf	111
Exa 12.10	To find 1 no load speed 2 firing angle and supply pf 3 speed regulation	112
Exa 12.11	to calculate 1 transformer phase turn ratio 2 firing angle delay	113
Exa 12.12	to calculate firing angle for different given conditions	114
Exa 12.13	to evaluate the time taken for the speed to reach 1000rpm	114
Exa 12.14	to determine the 3rd and 5th harmonic components of line current	115
Exa 12.15	to calculate 1 rms and avg value of thyristor current 2 pf of ac source 3 motor speed . . .	115
Exa 12.16	to determine 1 input power from source 2 input resistance of chopper drive 3 motor speed and 4 motor torque	116
Exa 12.17	to calculate avg load current	117
Exa 12.18	to determine 1 range of speed control 2 range of duty cycle	117
Exa 12.19	To calculate the min and max values of armature current and armature current extrusion	118

Exa 12.21	to determine 1 power returned to the dc supply 2 equivalent load resistance of motor acting as generator 3 min and max breaking speeds 4 speed during regenerative braking	119
Exa 12.22	to determine max current in terms of rated currents at given speeds	120
Exa 12.23	to calculate 1 motor speed at rated load 2 slip at which max torque occurs 3 max torque .	120
Exa 12.24	To calculate 1 current and pf at the instant of starting and under max torque conditions 2 starting and max torques	121
Exa 12.25	calculate 1 slip for max torque 2 starting and max torques 3 supply voltage reqd	122
Exa 12.27	to calculate 1 the value of chopper resistance R 2 inductor current 3 duty cycle 4 rectified output voltage 5 efficiency	123
Exa 12.28	To calculate 1 value of chopper duty cycle 2 efficiency for power input 3 input power factor	125
Exa 12.29	to calculate 1 rotor rectified voltage 2 inductor angle 3 delay angle of invertor 4 efficiency 5 motor speed	125
Exa 12.30	to find firing angle advance of inveter	127
Exa 12.31	to find firing angle advance of inveter	127
Exa 12.32	to find the voltage ratio of the transformer .	128
Exa 12.33	to calculate 1 supply voltage 2 armature current 3 excitation voltage 4 load angle 5 pull out torque	128
Exa 12.34	to calculate 1 load angle 2 line current 3 input pf	129
Exa 12.35	To calculate motor speed	130
Exa 12.36	to calculate avg motor torque	130
Exa 12.37	to calculate avg motor torque	131
Exa 12.38	to calculate avg motor torque	131
Exa 12.39	to calculate avg motor torque	132
Exa 12.40	to calculate avg motor torque	132
Exa 12.41	to calculate the value of load current and source current	133

Exa 13.1	To calculate load voltage voltage regulation system utilisation and energy consumed	134
Exa 13.2	to calculate the capacitance reqd	135
Exa 13.3	to find reqd values of capacitor and inductor	136
Exa 13.4	to find the firing angle of the TCR	136
Exa 13.5	to calculate the effective inductance at different firing angles	137
Exa 13.6	to find value of inductance	138
Exa 14.1	to calculate dc output voltage rms value of output voltage DF PF and HF	139

Chapter 2

Power Semiconductor Diodes and Transistors

Scilab code Exa 2.1 to find switching freq of the transistor

```
1 clear;
2 clc;
3 B=40;
4 R_c=10; //ohm
5 V_cc=130; //V
6 V_B=10; //V
7 V_CES=1.0; //V
8 V_BES=1.5; //V
9 I_CS=(V_cc-V_CES)/R_c; //A
10 I_BS=I_CS/B; //A
11 R_B=(V_B-V_BES)/I_BS; printf("value of R_B in
    saturated state= %.3f ohm",R_B);
12 P_T=V_BES*I_BS+V_CES*I_CS; printf("\n power loss
    in transistor=% .3f W",P_T);
13
14 ODF=5;
15 I_B=ODF*I_BS;
16 R_B=(V_B-V_BES)/I_B; printf("\n value of R_B for
    an overdrive factor 5 =%.2f ohm",R_B);
```

```

17 P_T=V_BES*I_B+V_CES*I_CS;      printf("\npower loss in
transistor=%f W",P_T)
18
19 B_f=I_CS/I_B;      printf("\nforced current gain=%f"
,B_f);

```

Scilab code Exa 2.2 to determine avg power loss due to collector current and also

```

1 clear;
2 clc;
3
4 I_CEO=2*10^-3; //A
5 V_CC=220; //V
6 P_dt=I_CEO*V_CC; //instant. power loss during delay
time
7
8 t_d=.4*10^-6; //s
9 f=5000;
10 P_d=f*I_CEO*V_CC*t_d; //avg power loss during delay
time
11
12 V_CES=2; //V
13 t_r=1*10^-6; //s
14 I_CS=80; //A
15 P_r=f*I_CS*t_r*(V_CC/2-(V_CC-V_CES)/3); //avg power
loss during rise time
16
17 t_m=V_CC*t_r/(2*(V_CC-V_CES));
18 P_rm=I_CS*V_CC^2/(4*(V_CC-V_CES)); //instant. power
loss during rise time
19
20 P_on=P_d+P_r;    printf("avg power loss during turn
on=%f W",P_on);
21 P_nt=I_CS*V_CES;    printf("\ninstantaneous power
loss during turn on=%f W",P_nt);

```

```

22 t_n=50*10^-6;
23 P_n=f*I_CS*V_CES*t_n;      printf("\nnavg power loss
during conduction period=%.0f W",P_n);

```

Scilab code Exa 2.3 to obtain power loss during turn off time and turn off period

```

1 clear
2 clc;
3 I_CEO=2*10^-3; //A
4 V_CC=220; //V
5 t_d=.4*10^-6; //s
6 f=5000;
7 V_CES=2; //V
8 t_r=1*10^-6; //s
9 I_CS=80; //A
10 t_n=50*10^-6; //s
11 t_0=40*10^-6; //s
12 t_f=3*10^-6; //s
13 P_st=I_CS*V_CES; // instant. power loss during t_s
14 P_s=f*I_CS*V_CES*t_f; //avg power loss during t_s
15 P_f=f*t_f*(I_CS/6)*(V_CC-V_CES); //avg power loss
during fall time
16 P_fm=(I_CS/4)*(V_CC-V_CES); //peak instant power
dissipation
17
18 P_off=P_s+P_f;      printf("total avg power loss
during turn off=%.0f W",P_off);
19 P_0t=I_CEO*V_CC;    printf("\ninstantaneous power
loss during t_0=%.2f W",P_0t);
20 P_0=f*I_CEO*V_CC*t_0; //avg power loss during t_s
21 P_on=14.9339; //W from previous eg
22 P_n=40; //W from previous eg
23 P_T=P_on+P_n+P_off+P_0;      printf("\ntotal power
loss=%.3f W",P_T);

```

Scilab code Exa 2.4 to find switching freq of the transistor

```
1 clear
2 clc;
3 I_CS=100;
4 V_CC=200;
5 t_on=40*10^-6;
6 P_on=(I_CS/50)*10^6*t_on*(V_CC*t_on/2-(V_CC*10^6*
    t_on^2/(40*3))); //energy during turn on
7 t_off=60*10^-6;
8 P_off=(I_CS*t_off/2-(I_CS/60)*10^6*(t_off^2)/3)*((
    V_CC/75)*10^6*t_off); //energy during turn off
9 P_t=P_on+P_off; //total energy
10 P_avg=300;
11 f=P_avg/P_t; printf("allowable switching
    frequency=%.1f Hz",f);
12 //in book ans is: f=1123.6 Hz. The difference in
    results due to difference in rounding of of
    digits
```

Chapter 3

Diode Circuits and Rectifiers

Scilab code Exa 3.2 to find the conduction time of diode peak current through diod

```
1 clear;
2 clc;
3 V_s=400; //V
4 V_o=100; //V
5 L=100; //uH
6 C=30; //uF
7 t_o=%pi*sqrt(L*C); printf("conduction time of
diode=%.2f us",t_o);
8 //in book solution is t_o=54.77 us. The ans is
incorrect as %pi is not multiplied in ans.
Formulae mentioned in correct.
9 I_p=(V_s-V_o)*sqrt(C/L); printf("\npeak current
through diode=%.2f A",I_p);
10 v_D=-V_s+V_o; printf("\nvoltage across diode=%.0f
V",v_D);
```

Scilab code Exa 3.6 to determine conduction time of diode and rate of change of cu

```

1 clc
2 clear
3 R=10; //ohm
4 L=.001; //H
5 C=5*10^-6; //F
6 V_s=230; //V
7 xi=R/(2*L);
8 w_o=1/sqrt(L*C);
9 w_r=sqrt((1/(L*C))-(R/(2*L))^2);
10 t=%pi/w_r; printf('conduction time of diode=%.3f
    us',t*10^6);
11 t=0;
12 //di=di/dt
13 di=V_s/L; printf('\nrate of change of current at
    t=0 is %.0f A/s',di);

```

Scilab code Exa 3.7 to find the time required to deliver a charge of 200Ah

```

1 clear;
2 clc;
3 I_or=100; //A
4 R=1; //assumption
5 V_m=I_or*2*R;
6 I_o=V_m/(%pi*R);
7 q=200; //Ah
8 t=q/I_o; printf("time required to deliver charge=
    %.04f hrs",t);

```

Scilab code Exa 3.8 to calculate the power delivered to the heater and find peak d

```

1 clear;
2 clc;
3 V_s=230; //V

```

```

4 P=1000; //W
5 R=V_s^2/P;
6 V_or=sqrt(2)*V_s/2;
7 P_h=V_or^2/R;      printf(" power delivered to the
                     heater=%f W",P_h);
8 V_m=sqrt(2)*230;
9 I_m=V_m/R;         printf("\npeak value of diode current=
                     %.4f A",I_m);
10 pf=V_or/V_s;       printf("\ninput power factor=%f",
                     pf);

```

Scilab code Exa 3.9 to find 1 the value of avg chargng current 2 power supplied to

```

1 clear;
2 clc;
3 V_s=230; //V
4 V_m=V_s*sqrt(2);
5 E=150; //V
6 theta1=asind(E/(sqrt(2)*V_s));
7 R=8; //ohm
8 f=50; //Hz
9 I_o=(1/(2*pi*R))*((2*sqrt(2)*V_s*cosd(theta1))-E*(
               %pi-2*theta1*pi/180));
10 printf("avg value of charging current=%f A",I_o);
11 P_d=E*I_o;      printf("\npower delivered to battery=%
                     .2f W",P_d);
12 I_or=sqrt((1/(2*pi*R^2))*((V_s^2+E^2)*(%pi-2*theta1
               *%pi/180)+V_s^2*sind(2*theta1)-4*V_m*E*cosd(
               theta1)));    printf("\nrms value of the load
                     current=%f A",I_or);
13 pf=(E*I_o+I_or^2*R)/(V_s*I_or);      printf("\n supply
                     pf=%f",pf);
14 P_dd=I_or^2*R;      printf("\n power dissipated in the
                     resistor=%f W",P_dd);
15 q=1000.00; //Wh

```

```

16 t=q/P_d;      printf("\ncharging time=%f hr",t);
17 n=P_d*100/(P_d+P_dd);      disp(n,"rectifier
    efficiency (%)");
18 PIV=sqrt(2)*V_s+E;      printf("PIV of diode=%f V",
    PIV);
19 //solutions have small variations due to difference
    in rounding off of digits

```

Scilab code Exa 3.10 to determine the effect of reverse recovery time on the avg o/p voltage

```

1 clear;
2 clc;
3 V_s=230;//V;
4 t_rr=40*10^-6;//s reverde recovery time
5 V_o=2*sqrt(2)*V_s/%pi;
6 V_m=sqrt(2)*V_s;
7 disp("when f=50Hz");
8 f=50;
9 V_r=(V_m/%pi)*(1-cosd(2*pi*f*t_rr*180/%pi));
10 v_avg=V_r*100/V_o*10^3;      printf("percentage
    reduction in avg o/p voltage=%f x10^-3",v_avg);
11
12 disp("when f=2500Hz");
13 f=2500;
14 V_r=(V_m/%pi)*(1-cosd(2*pi*f*t_rr*180/%pi));
15 v_avg=V_r*100/V_o;      printf("percentage reduction
    in avg o/p voltage=%f",v_avg);

```

Scilab code Exa 3.11 to determine 1 avg value of output voltage and output current

```

1 clear;
2 clc;
3 V_s=230;//V

```

```

4 R=10; //ohm
5 V_m=sqrt(2)*V_s;
6 V_o=2*V_m/pi;      printf(" avg value of o/p voltage=%
    .2 f V",V_o);
7 I_o=V_o/R;      printf("\n avg value of o/p current=%.
3 f A",I_o);
8 I_DA=I_o/2;      printf("\n avg value of diode current=%.
3 f A",I_DA);
9 I_Dr=I_o/sqrt(2);      printf("\n rms value of diode
    current=% .3 f A",I_Dr);
10
11 printf("\n rms value of o/p current=% .3 f A",I_o);
12 printf("\n rms value of i/p current=% .3 f A",I_o);
13 pf=(V_o/V_s);      printf("\n supply pf=% .2 f",pf);

```

Scilab code Exa 3.12 to calculate 1 peak load current 2 dc load current 3 dc diode

```

1 clear;
2 clc;
3 V_s=230; //V
4 R=1000; //ohm
5 R_D=20; //ohm
6 V_m=sqrt(2)*V_s;
7 I_om=V_m/(R+R_D);      printf(" peak load current=% .
4 f
    A",I_om);
8 I_o=I_om/pi;      printf("\n dc load current=% .5 f A",
    I_o);
9 V_D=I_o*R_D-V_m/pi;      printf("\n dc diode voltage=%
    .1 f V",V_D);
10 V_on=V_m/pi;      printf("\n at no load , load voltage=%
    .3 f V",V_on);
11 V_o1=I_o*R;      printf("\n at given load , load voltage
    =% .3 f V",V_o1);
12 vr=(V_on-V_o1)*100/V_on;      printf("\n voltage
    regulation (in percent)=% .3 f",vr);

```

Scilab code Exa 3.13 to design a zener voltage regulator to meet given specifications

```
1 clear;
2 clc;
3 V_L=6.8; //V
4 V_smax=20*1.2; //V
5 V_smin=20*.8; //V
6 I_Lmax=30*1.5; //mA
7 I_Lmin=30*.5; //mA
8 I_z=1; //mA
9
10 R_smax=(V_smax-V_L)/((I_Lmin+I_z)*10^-3); printf(
    "max source resistance=%f ohm",R_smax);
11 R_smin=(V_smin-V_L)/((I_Lmax+I_z)*10^-3); printf(
    "\nmin source resistance=%f ohm",R_smin); //in
    book solution , error is committed in putting the
    values in formulae (printing error) but solution
    is correct
12 R_Lmax=V_L*1000/I_Lmin; printf("\nmax load
    resistance=%f ohm",R_Lmax);
13 R_Lmin=V_L*1000/I_Lmax; printf("\nmin load
    resistance=%f ohm",R_Lmin);
14
15 V_d=.6; //V
16 V_r=V_L-V_d; printf("\nvoltage rating of zener
    diode=%f V",V_r);
```

Scilab code Exa 3.14 to find R1 and R2

```
1 clear;
2 clc;
```

```

3 I2=200*10^-6; //A
4 V_z=20; //V
5 R_G=500; //ohm
6 R2=(V_z/I2)-R_G;      printf("R2=%f kilo-ohm",R2
/1000);
7
8 V_v=25; //V
9 I1=I2;
10 R1=(V_v-V_z)/I1;     printf("\nR1=%f kilo-ohm",R1
/1000);

```

Scilab code Exa 3.15 to find the VA rating of the transformer

```

1 clear;
2 clc;
3 V_s=2*230; //V
4 V_o=(sqrt(2)*V_s)/pi;
5 R=60; //ohm
6 P_dc=(V_o)^2/R;
7 TUF=0.2865;
8 VA=P_dc/TUF;      printf("kVA rating of the
transformer=%f kVA",VA/1000);

```

Scilab code Exa 3.16 to determine 1 avg value of output voltage 2 input current di

```

1 clear;
2 clc;
3 tr=0.5;      //turns ratio
4 I_o=10;
5 V=230;
6 V_s=V/tr;
7 V_m=sqrt(2)*V_s;
8 V_o=2*V_m/pi;      printf("o/p voltage=%f V",V_o);

```

```

9 phi1=0;      // displacement angle=0 as fundamental
               component of i/p source current in phase with
               source voltage
10 DF=cosd(phi1);    printf("\ndistortion factor=%f",DF);
11 I_s1=4*I_o/(sqrt(2)*pi);
12 I_s=sqrt(I_o^2*pi/pi);
13 CDF=I_s1/I_o;    printf("\ncurrent displacement factor
               =%f",CDF);
14 pf=CDF*DF;      printf("\ni/p pf=%f",pf);
15 HF=sqrt((I_s/I_s1)^2-1);   printf("\nharmonic
               factor=%f",HF);
16 CF=I_o/I_s;    printf("\ncrease factor=%f",CF);

```

Scilab code Exa 3.17 to determine diode rating and transformer rating

```

1 clear;
2 clc;
3 V_o=230;
4 R=10;
5 V_s=V_o*pi/(2*sqrt(2));
6 I_o=V_o/R;
7 I_m=sqrt(2)*V_s/R;    printf("peak diode current=%.
               f A",I_m);
8 I_DAV=I_m/pi;      printf("\nI_DAV=%f A",I_DAV);
               //avg value of diode current
9 I_Dr=I_m/2;      printf("\nI_Dr=%f A",I_Dr);      //
               rms value of diode current
10 PIV=sqrt(2)*V_s;   printf("\nPIV=%f V",PIV);
11 I_s=I_m/sqrt(2);
12 TF=V_s*I_s;      printf("\ntransformer rating=%f kVA
               ",TF/1000);

```

Scilab code Exa 3.18 to calculate avg value of output voltage avg and rms values o

```
1 clear;
2 clc;
3 tr=5;
4 V=1100;
5 R=10;
6 disp("in case of 3ph-3pulse type");
7 V_ph=V/tr;
8 V_mp=sqrt(2)*V_ph;
9 V_o=3*sqrt(3)*V_mp/(2*pi);      printf("avg o/p
voltage=%.1f V",V_o);
10 I_mp=V_mp/R;
11 I_D=(I_mp/pi)*sin(pi/3);      printf("\navg value of
diode current=%.3f A",I_D);
12 I_Dr=I_mp*sqrt((1/(2*pi))*(pi/3+.5*sin(2*pi/3)));
      printf("\nrms value of diode current=%.2f A",
I_Dr);
13 V_or=V_mp*sqrt((3/(2*pi))*(pi/3+.5*sin(2*pi/3)));
14 P=(V_or^2)/R;      printf("\npower delivered=%.1f W",P
);
15
16 disp("in case of 3ph-M6 type");
17 V_ph=V_ph/2;
18 V_mp=sqrt(2)*V_ph;
19 V_o=3*V_mp/(pi);      printf("avg o/p voltage=%.2f V"
,V_o);
20 I_mp=V_mp/R;
21 I_D=(I_mp/pi)*sin(pi/6);      printf("\navg value of
diode current=%.4f A",I_D);
22 I_Dr=I_mp*sqrt((1/(2*pi))*(pi/6+.5*sin(2*pi/6)));
      printf("\nrms value of diode current=%.3f A",
I_Dr);
23 V_or=V_mp*sqrt((6/(2*pi))*(pi/6+.5*sin(2*pi/6)));
24 P=(V_or^2)/R;      printf("\npower delivered=%.0f W",P
);
```

Scilab code Exa 3.19 determine the ratings of diodes and of 3ph deltarstar transformer

```
1 clear;
2 clc;
3 V_o=400;
4 R=10;
5 V_ml=V_o*%pi/3;
6 V_s=V_ml/(sqrt(2)*sqrt(3));
7 I_m=V_ml/R;
8 I_s=.7804*I_m;
9 tr=3*V_s*I_s;      printf("transformer rating=%f VA"
, tr);
10
11 I_Dr=.5518*I_m;    printf("\nrms value of diode
current=%f A", I_Dr);
12 I_D=I_m/%pi;        printf("\navg value of diode current
=%f A", I_D);
13 printf("\npeak diode current=%f A", I_m);
14 PIV=V_ml;           printf("\nPIV=%f V", PIV);
```

Scilab code Exa 3.20 to determine 1 power delivered to battery and load 2 input diodes

```
1 clear;
2 clc;
3 V_l=230;
4 E=240;
5 R=8;
6 V_ml=sqrt(2)*V_l;
7 V_o=3*V_ml/%pi;
8 I_o=(V_o-E)/R;
9 P_b=E*I_o;      printf("power delivered to battery=%f
W", P_b);
```

```

10 P_d=E*I_o+I_o^2*R;      printf("\npower delivered to
   load=%f W",P_d);
11
12 phi1=0;
13 DF=cosd(phi1);
14 printf("\ndisplacement factor=%f",DF);
15 I_s1=2*sqrt(3)*I_o/(sqrt(2)*pi);
16 I_s=sqrt(I_o^2*2*pi/(3*pi));
17 CDF=I_s1/I_s;      printf("\ncurrent distortion factor
   =%f",CDF);
18 pf=DF*CDF;      printf("\ni/p pf=%f",pf);
19 HF=sqrt(CDF^-2-1);      printf("\nharmonic factor=%f
   ",HF);
20 tr=sqrt(3)*V_l*I_o*sqrt(2/3);      printf("\
   ntransformer rating=%f VA",tr);
21 //answers have small variations from the book due to
   difference in rounding off of digits

```

Scilab code Exa 3.21 design capaitor filter and avg value of output voltage with a

```

1 clear;
2 clc;
3 f=50;      //Hz
4 V=230;
5 V_m=sqrt(2)*V;
6 R=400;
7 RF=0.05;
8 C=(1/(4*f*R))*(1+(1/(sqrt(2)*RF)));      printf(
   capacitor value=%f uF",C/10^-6);
9 V_o=V_m*(1-1/(4*f*R*C));      printf("\no/p voltage
   with filter=%f V",V_o);
10 V_o=2*V_m/pi;      printf("\no/p voltage without
   filter=%f V",V_o);

```

Scilab code Exa 3.22 to find the value of L with different R and CRF without L

```
1 clear;
2 clc;
3 f=50;
4 CRF=0.05;
5 R=300;
6 L=sqrt((CRF/(.4715*R))^2-R^2)/(2*2*pi*f);
    printf("L=%f H",L);
7 R=30;
8 L=sqrt((CRF/(.4715*R))^2-R^2)/(2*2*pi*f);
    printf("\nL=%f H",L);
9 L=0;
10 CRF=.4715*R/sqrt(R^2+(2*2*pi*f*L)^2);      printf("\
nCRF=%f",CRF);
```

Scilab code Exa 3.23 to design LC filter

```
1 clear;
2 clc;
3 R=50;
4 L_L=10*10^-3;
5 f=50;
6 w=2*pi*f;
7 C=10/(2*w*sqrt(R^2+(2*w*L_L)^2));      printf("C=%f f
uF",C*10^6);
8 VRF=0.1;
9 L=(1/(4*w^2*C))*((sqrt(2)/(3*VRF))+1);      printf("\
nL=%f mH",L*10^3);
```

Chapter 4

Thyristors

Scilab code Exa 4.2 to plot allowable gate voltage as the function of gate current

```
1 clc
2 clear
3 P=.5;      //P=V_g*I_g
4 V=[0.01:0.01:.25];
5 plot2d(P./V);
6 xlabel('I_g in A');
7 ylabel('V_g in V');
8
9 t=poly(0,'t');
10 P1=P*t/(2*t);
11 printf('average gate power dissipation (in watts)');
12 disp(P1);
```

Scilab code Exa 4.3 to compute gate source resistance

```
1 clear;
2 clc;
3 P=.5;      //P=V_g*I_g
```

```

4 s=130;      //s=V_g/I_g
5 I_g=sqrt(P/s);
6 V_g=s*I_g;
7 E=15;
8 R_s=(E-V_g)/I_g;    printf(" gate source resistance=%
.2 f ohm" ,R_s);
9 //Answers have small variations from that in the
book due to difference in the rounding off of
digits .

```

Scilab code Exa 4.4 to compute gate source resistance trigger voltage and trigger

```

1 clear;
2 clc;
3 R_s=120;      //slope of load line is -120V/A. This
gives gate source resistance
4 printf("gate source resistance=% .0 f ohm" ,R_s);
5
6 P=.4;        //P=V_g*I_g
7 E_s=15;
8 //E_s=I_g*R_s+V_g,      after solving this
9 //120*I_g^2-15*I_g+0.4=0      so
10 a=120;       b=-15;       c=0.4;
11 D=sqrt((b^2)-4*a*c);
12 I_g=(-b+D)/(2*a);      V_g=P/I_g;
13 printf("\ntrigger current=% .2 f mA" ,I_g*10^3);
printf("\nthen trigger voltage=% .3 f V" ,V_g);
14
15 I_g=(-b-D)/(2*a);      V_g=P/I_g;
16 printf("\ntrigger current=% .2 f mA" ,I_g*10^3);
printf("\nthen trigger voltage=% .2 f V" ,V_g);

```

Scilab code Exa 4.5 to compute 1 resistance 2 triggering freq 3 duty cycle of the

```

1 clear;
2 clc;
3 //V_g=1+10*I_g
4 P_gm=5;      //P_gm=V_g*I_g
5 // after solving , eqn becomes 10*I_g^2+I_g-5=0
6 a=10;        b=1;        c=-5;
7 I_g=(-b+sqrt(b^2-4*a*c))/(2*a);
8 E_s=15;
9 // using E_s=R_s*I_g+V_g
10 R_s=(E_s-1)/I_g-10;    printf(" resistance=%f ohm" ,
    R_s);
11
12 P_gav=.3;      //W
13 T=20*10^-6;
14 f=P_gav/(P_gm*T);    printf("\n triggering freq=%f kHz" ,
    f/1000);
15
16 d1=f*T;      printf("\nduty cycle=%f",d1);

```

Scilab code Exa 4.6 to compute min width of gate pulse current

```

1 clear;
2 clc;
3 I=.1;
4 E=200;
5 disp("in case load consists of (a)L=.2H");
6 L=.2;
7 t=I*L/E;    printf("min gate pulse width=%f us",t
    *10^6);
8 disp("(b)R=20ohm in series with L=.2H");
9 R=20;
10 t=(-L/R)*log(1-(R*I/E));    printf("min gate pulse
    width=%f us",t*10^6);
11 disp("(c)R=20ohm in series with L=2H");
12 L=2;

```

```
13 t=(-L/R)*log(1-(R*I/E));      printf("min gate pulse
width=%f us",t*10^6);
```

Scilab code Exa 4.8 to calculate trigger voltage and trigger current

```
1 clc
2 clear
3 E_s=16;
4 R_s=128;
5 P=.5;
6 y=poly([P -E_s R_s], 'i', 'coeff');
7 a=roots(y);
8 printf('trigger current=%f mA',a(1)*1000);
9 printf('\ntrigger voltage=%f V',P/a(1));
```

Scilab code Exa 4.9 to compute avg on current rating for half sine wavecurrent for

```
1 clear;
2 clc;
3 function [I_TAV]=theta(th)
4     I_m=1;      //supposition
5     I_av=(I_m/(2*pi))*(1+cosd(th));
6     I_rms=sqrt((I_m/(2*pi))*((180-th)*pi/360+.25*
sind(2*th)));
7     FF=I_rms/I_av;
8     I_rms=35;
9     I_TAV=I_rms/FF;
10 endfunction
11 disp("when conduction angle=180");
12 th=0;
13 I_TAV=theta(th);
14 printf("avg on current rating=%f A",I_TAV);
15 disp("when conduction angle=90");
```

```

16 th=90;
17 I_TAV=theta(th);
18 printf("avg on current rating=%f A",I_TAV);
19 disp("when conduction angle=30");
20 th=150;
21 I_TAV=theta(th);
22 printf("avg on current rating=%f A",I_TAV);

```

Scilab code Exa 4.10 to compute avg on current rating for half sine wave current f

```

1 clear;
2 clc;
3 clear
4 function [I_TAV]=theta(th)
5 n=360/th;
6 I=1; //supposition
7 I_av=I/n;
8 I_rms=I/sqrt(n);
9 FF=I_rms/I_av;
10 I_rms=35;
11 I_TAV=I_rms/FF;
12 endfunction
13 disp("when conduction angle=180");
14 th=180;
15 I_TAV=theta(th);
16 printf("avg on current rating=%f A",I_TAV);
17 disp("when conduction angle=90");
18 th=90;
19 I_TAV=theta(th);
20 printf("avg on current rating=%f A",I_TAV);
21 disp("when conduction angle=30");
22 th=30;
23 I_TAV=theta(th);
24 printf("avg on current rating=%f A",I_TAV);

```

Scilab code Exa 4.11 to calculate surge current rating and power rating

```
1 clear;
2 clc;
3 f=50;      //Hz
4 I_sb=3000;
5 t=1/(4*f);
6 T=1/(2*f);
7 I=sqrt(I_sb^2*t/T);    printf("surge current rating=%.
%.2 f A",I);
8 r=(I_sb/sqrt(2))^2*T;   printf("\nI^2*t rating=%.0 f
A^2.s",r);
```

Scilab code Exa 4.12 to find maximum value of the remedial parameter

```
1 clc
2 clear
3 V_s=300; //V
4 R=60; //ohm
5 L=2; //H
6 t=40*10^-6; //s
7 i_T=(V_s/R)*(1-exp(-R*t/L));
8 i=.036; //A
9 R1=V_s/(i-i_T);
10 printf("maximum value of remedial parameter=%.
.3 f
kilo -ohm",R1/1000);
```

Scilab code Exa 4.16 to calculate fault clearance time

```

1 clear;
2 clc;
3 V_p=230*sqrt(2);
4 R=1+((1)^-1+(10)^-1)^-1;
5 A=V_p/R;
6 s=1; //s
7 t_c=20*A^-2*s; printf("fault clearance time=%f ms", t_c*10^3);

```

Scilab code Exa 4.17 1 to calculate the max values of change in current and change

```

1 clear;
2 clc;
3 V_s=sqrt(2)*230; //V
4 L=15*10^-6; //H
5 I=V_s/L; //I=(di/dt)_max
6 printf("( di/dt )_max=%f A/usec", I/10^6);
7 R_s=10; //ohm
8 v=I*R_s; //v=(dv/dt)_max
9 printf("\n(dv/dt)_max=%f V/usec", v/10^6);
10
11 f=50; //Hz
12 X_L=L*2*pi*f;
13 R=2;
14 I_max=V_s/(R+X_L); printf("\nI_rms=%f A", I_max)
;
15 disp("when conduction angle=90");
16 FF=%pi/sqrt(2);
17 I_TAV=I_max/FF; printf("I_TAV=%f A", I_TAV);
18 disp("when conduction angle=30");
19 FF=3.98184;
20 I_TAV=I_max/FF; printf("I_TAV=%f A", I_TAV);
21
22 printf("\nvoltage rating=%f V", 2.75*V_s); //rating
is taken 2.75 times of peak working voltage

```

unlike 2.5 to 3 times as mentioned int book.

Scilab code Exa 4.19 1 to check heat sink selection is satisfactory 2 to choose he

```
1 clear;
2 clc;
3 T_jm=125;
4 th_jc=.15;      //degC/W
5 th_cs=0.075;    //degC/W
6
7 dT=54;          //dT=T_s-T_a
8 P_av=120;
9 th_sa=dT/P_av;
10 T_a=40;         //ambient temp
11 P_av=(T_jm-T_a)/(th_sa+th_jc+th_cs);
12 if((P_av-120)<1)
13     disp("selection of heat sink is satisfactory");
14 end
15 dT=58;          //dT=T_s-T_a
16 P_av=120;
17 th_sa=dT/P_av;
18 T_a=40;         //ambient temp
19 P_av=(T_jm-T_a)/(th_sa+th_jc+th_cs);
20 if((P_av-120)<1)
21     disp("selection of heat sink is satisfactory");
22 end
23
24 V_m=sqrt(2)*230;
25 R=2;
26 I_TAV=V_m/(R*%pi);
27 P_av=90;
28 th_sa=(T_jm-T_a)/P_av-(th_jc+th_cs);
29 dT=P_av*th_sa;
30 disp("for heat sink");    printf("T_s-T_a=%f degC"
, dT);    printf("\nP_av=%f W", P_av);
```

```

31 P=(V_m/2)^2/R;
32 eff=P/(P+P_av);      printf("\nckt efficiency=%f pu"
,eff);
33
34 a=60;      //delay angle
35 I_TAV=(V_m/(2*pi*R))*(1+cosd(a));
36 printf("\nI_TAV=%f A",I_TAV);
37 dT=46;
38 T_s=dT+T_a;
39 T_c=T_s+P_av*th_cs;    printf("\ncase temp=%f degC"
,T_c);
40 T_j=T_c+P_av*th_jc;    printf("\njunction temp=%f f
degC",T_j);

```

Scilab code Exa 4.20 to find total avg power loss and percentage inc in device rat

```

1 clear;
2 clc;
3 T_j=125;      //degC
4 T_s=70;      //degC
5 th_jc=.16;      //degC/W
6 th_cs=.08;      //degC/W
7 P_av1=(T_j-T_s)/(th_jc+th_cs);    printf("total avg
power loss in thristor sink combination=%f W",
P_av1);
8
9 T_s=60;      //degC
10 P_av2=(T_j-T_s)/(th_jc+th_cs);
11
12 inc=(sqrt(P_av2)-sqrt(P_av1))*100/sqrt(P_av1);
printf("\npercentage inc in rating=%f",inc);

```

Scilab code Exa 4.21 to determine voltage across each SCR and discharge current ac

```

1 clear;
2 clc;
3 R=25000;
4 I_11=.021;      // I_l=leakage current
5 I_12=.025;
6 I_13=.018;
7 I_14=.016;
8 //V1=(I-I_11)*R;
9 //V2=(I-I_12)*R;
10 //V3=(I-I_13)*R;
11 //V4=(I-I_14)*R;
12 //V=V1+V2+V3+V4
13 V=10000;
14 I_l=I_11+I_12+I_13+I_14;
15 // after solving
16 I=((V/R)+I_l)/4;
17 R_c=40;
18 V1=(I-I_11)*R;    printf(" voltage across SCR1=%f V
                      ",V1);
19 V2=(I-I_12)*R;    printf("\n voltage across SCR2=%f f
                      V",V2);
20 V3=(I-I_13)*R;    printf("\n voltage across SCR3=%f f
                      V",V3);
21 V4=(I-I_14)*R;    printf("\n voltage across SCR4=%f f
                      V",V4);
22
23 I1=V1/R_c;        printf("\ndischarge current through
                      SCR1=%f A",I1);
24 I2=V2/R_c;        printf("\ndischarge current through
                      SCR2=%f A",I2);
25 I3=V3/R_c;        printf("\ndischarge current through
                      SCR3=%f A",I3);
26 I4=V4/R_c;        printf("\ndischarge current through
                      SCR4=%f A",I4);

```

Scilab code Exa 4.22 to calculate number of series and parrallel units of SCRs

```
1 clear;
2 clc;
3 V_r=1000;      //rating of SCR
4 I_r=200;       //rating of SCR
5 V_s=6000;      //rating of String
6 I_s=1000;      //rating of String
7 disp("when DRF=.1");
8 DRF=.1;
9 n_s=V_s/(V_r*(1-DRF));    printf("number of series
                           units=%0.0f",ceil(n_s));
10 n_p=I_s/(I_r*(1-DRF));   printf("\nnumber of
                           parallel units=%0.0f",ceil(n_p));
11 disp("when DRF=.2");
12 DRF=.2;
13 n_s=V_s/(V_r*(1-DRF));   printf("number of series
                           units=%0.0f",ceil(n_s));
14 n_p=I_s/(I_r*(1-DRF));   printf("\nnumber of
                           parallel units=%0.0f",ceil(n_p));
```

Scilab code Exa 4.23 to calculate the resistance

```
1 clear;
2 clc;
3 V1=1.6;        //on state voltage drop of SCR1
4 V2=1.2;        //on state voltage drop of SCR2
5 I1=250;        //current rating of SCR1
6 I2=350;        //current rating of SCR2
7 R1=V1/I1;
8 R2=V2/I2;
9 I=600;          //current to be shared
10 //for SCR1,      I*(R1+R)/(total resistance)=k*I1
                  (1)
11 //for SCR2,      I*(R2+R)/(total resistance)=k*I2
```

(2)

```
12 // (1)/(2)
13 R=(R2*I2-R1*I1)/(I1-I2);
14 printf(" reqd value of resistance=%f ohm",R);
```

Scilab code Exa 4.25 to compute value of various resistances

```
1 clear;
2 clc;
3 f=2000;      //Hz
4 C=0.04*10^-6;
5 n=.72;
6 R=1/(f*C*log(1/(1-n)));    printf("R=%f kilo-ohm",
   R/1000);
7 V_p=18;
8 V_BB=V_p/n;
9 R2=10^4/(n*V_BB);    printf("\nR2=%f ohm",R2);
10 I=4.2*10^-3;      //leakage current
11 R_BB=5000;
12 R1=(V_BB/I)-R2-R_BB;    printf("\nR1=%f ohm",R1);
```

Scilab code Exa 4.26 to compute max and min values of R and the corresponding freq

```
1 clear;
2 clc;
3 V_p=18;
4 n=.72;
5 V_BB=V_p/n;
6 I_p=.6*10^-3;
7 I_v=2.5*10^-3;
8 V_v=1;
9 R_max=V_BB*(1-n)/I_p;    printf(" R_max=%f kilo-ohm
   ",R_max/1000);
```

```

10 R_min=(V_BB-V_v)/I_v;      printf ("\nR_min=%f kilo-
    ohm",R_min/1000);
11
12 C=.04*10^-6;
13 f_min=1/(R_max*C*log(1/(1-n)));   printf ("\nf_min=%
    .3 f kHz",f_min/1000);
14 f_max=1/(R_min*C*log(1/(1-n)));   printf ("\nf_max=%
    .2 f kHz",f_max/1000);

```

Scilab code Exa 4.27 to find max and min firing angles for triac

```

1 clear;
2 clc;
3 R1=1000;
4 C=.5*10^-6;
5 f=50;
6 w=2*pi*f;
7 V_s=230;
8 X_c=1/(w*C);
9 v_c=30;
10 R=0;
11 Z=sqrt((R+R1)^2+X_c^2);
12 phi=atand(X_c/(R+R1));
13 I1=V_s/(Z*complex(cosd(-phi),sind(-phi)));
14 V_c=I1*X_c*complex(cosd(-90),sind(-90));
15 a=abs(V_c); //magnitude of V_c
16 b=-atand(imag(V_c)/real(V_c)); //argument of V_c
17 //v_c=sqrt(2)*a*sind(a1-b)
18 a1=asind(v_c/(sqrt(2)*a))+b;   printf ("min angle=%
    .1 f deg",a1);
19
20 R=25000;
21 Z=sqrt((R+R1)^2+X_c^2);
22 phi=atand(X_c/(R+R1));
23 I1=V_s/(Z*complex(cosd(-phi),sind(-phi)));

```

```
24 V_c=I1*X_c*complex(cosd(-90),sind(-90));  
25 a=abs(V_c); //magnitude of V_c  
26 b=-atand(imag(V_c)/real(V_c)); //argument of V_c  
27 //v_c=sqrt(2)*a*sind(a2-b)  
28 a2=asind(v_c/(sqrt(2)*a))+b; printf("\nmax angle=  
%.2f deg",a2);
```

Chapter 5

Thyristor Commutation Techniques

Scilab code Exa 5.1 to determine 1 conduction time and 2 voltage across thyristor

```
1 clear;
2 clc;
3 L=5*10^-3;
4 C=20*10^-6;
5 V_s=200;
6 w_o=sqrt(1/(L*C));
7 t_o=%pi/w_o;      printf("conduction time of thyristor
                         =%.5f ms",t_o*1000);
8 printf("\nvoltage across thyristor=%0.0f V",-V_s);
```

Scilab code Exa 5.2 to calculate 1 conduction time for auxillary thyristor 2 volta

```
1 clear;
2 clc;
3 C=20*10^-6;
4 L=5*10^-6;
```

```

5 V_s=230;
6 I_p=V_s*sqrt(C/L);
7 w_o=sqrt(1/(L*C));
8 t_o=%pi/w_o;      printf("conduction time of auxillary
thyristor=%f us",t_o*10^6);
9 I_o=300;
10 //a=w_o*(t3-t2)=asind(I_o/(2*V_s));
11 a=asind(I_o/(2*V_s));
12 V_ab=V_s*cosd(a);    printf("\nvoltage across main
thyristor=%f V",V_ab);
13 t_c=C*V_ab/I_o;      printf("\nckt turn off time=%f
us",t_c*10^6);

```

Scilab code Exa 5.3 to determine 1 peak value of current 2 value of capacitor C

```

1 clear;
2 clc;
3 V_s=200;
4 R1=10;
5 R2=100;
6 I1=V_s*(1/R1+2/R2);    printf("peak value of current
through SCR1=%f A",I1);
7 I2=V_s*(2/R1+1/R2);    printf("\npeak value of
current through SCR2=%f A",I2);
8 t_c1=40*10^-6;
9 fos=2;      //factor of safety
10 C1=t_c1*fos/(R1*log(2));
11 C2=t_c1*fos/(R2*log(2));
12 if(C1>C2)
13     printf("\nvalue of capacitor=%f uF",C1*10^6);
14 else
15     printf("\nvalue of capacitor=%f uF",C2*10^6);
16 end

```

Scilab code Exa 5.4 to calculate 1 value of current 2 circuit turn off time for main thyristor

```
1 clear;
2 clc;
3 V_s=230;
4 L=20*10^-6;
5 C=40*10^-6;
6 I_o=120;
7 I_p=V_s*sqrt(C/L);
8 printf("current through main thyristor=%f A",I_o+
    I_p);
9 printf("\ncurrent through auxillary thyristor=%f A
    ",I_o);
10
11 t_c=C*V_s/I_o;      printf("\ncircuit turn off time
    for main thyristor=%f us",t_c*10^6);
12 w_o=sqrt(1/(L*C));
13 t_c1=%pi/(2*w_o);  printf("\ncircuit turn off time
    for auxillary thyristor=%f us",t_c1*10^6);
```

Scilab code Exa 5.5 to compute min value of C

```
1 clear;
2 clc;
3 C_j=25*10^-12;
4 I_c=5*10^-3;      // charging current
5 V_s=200;
6 R=50;
7 C=(C_j*V_s)/(I_c*R);      printf("Value of C=%f uF",
    C*10^6);
```

Scilab code Exa 5.6 to find circuit turn off time

```
1 clear;
2 clc;
3 V_s=200;
4 R=5;
5 C=10*10^-6;
6 //for turn off V_s*(1-2*exp(-t/(R*C)))=0,      so
    after solving
7 t_c=R*C*log(2);      printf("circuit turn off time=%.4
f us",t_c*10^6);
```

Scilab code Exa 5.7 to find conduction time of thyristor

```
1 clear;
2 clc;
3 R=1;
4 L=20*10^-6;
5 C=40*10^-6;
6 w_r=sqrt((1/(L*C))-(R/(2*L))^2);
7 t_1=%pi/w_r;      printf("conduction time of thyristor
=%.3 f us",t_1*10^6);
```

Scilab code Exa 5.8 1 to calculate value of Capacitor 2 determine value of Resista

```
1 clear;
2 clc;
3 dv=400*10^-6;      //dv=dv_T/dt (V/s)
4 V_s=200;
```

```

5 R=20;
6 C=V_s/(R*dv);
7 C_j=.025*10^-12;
8 C_s=C-C_j;      printf ("C_s=%f uF",C_s/10^6);
9
10 I_T=40;
11 R_s=1/((I_T/V_s)-(1/R));    printf ("\nR_s=%f ohm",
     R_s);
12 //value of R_s in book is wrongly calculated

```

Scilab code Exa 5.9 calculate 1 time at which commutation of main thyristor gets initiated

```

1 clear;
2 clc;
3 V_s=200;
4 C=20*10^-6;
5 L=.2*10^-3;
6 i_c=10;
7 i=V_s*sqrt(C/L);
8 w_o=1/sqrt(L*C);
9 t_1=(1/w_o)*asin(i_c/i);    printf ("reqd time=%f us",
     t_1*10^6);
10
11 t_o=%pi/w_o;
12 t_c=t_o-2*t_1;    printf ("\nckt turn off time=%f us",
     t_c*10^6);
13 //solution in book wrong, as wrong values are
     selected while filling the formuleas

```

Scilab code Exa 5.11 to find current in R and L

```

1 clear;
2 clc;

```

```

3 L=1;
4 R=50;
5 V_s=200;
6 tau=L/R;
7 t=.01;
8 i=(V_s/R)*(1-exp(-t/tau));
9 Vd=.7;
10 t=8*10^-3;
11 i1=i-t*Vd;      printf(" current through L=%f A",i1);
12 i_R=0;           //current in R at t=.008s
13 printf("\n current through R=%f A",i_R);

```

Scilab code Exa 5.12 To find the current in R and L and voltage across C

```

1 clc
2 clear
3 L=1; //H
4 R=50; //ohm
5 V_s=200; //V
6 tau=L/R;
7 t=.01; //s
8 i=(V_s/R)*(1-exp(-t/tau));      printf(" current in R,L
= %f A",i);
9 C=1*10^-6; //F
10 V_c=sqrt(L/C)*i;
11 printf("\n voltage across C=%f kV",V_c/1000);

```

Chapter 6

Phase Controlled Rectifiers

Scilab code Exa 6.1 to calculate the power absorbed in the heater element

```
1 clear;
2 clc;
3 V=230;
4 P=1000;
5 R=V^2/P;
6 disp("when firing angle delay is of 45deg");
7 a=%pi/4;
8 V_or=(sqrt(2)*V/(2*sqrt(%pi)))*sqrt((%pi-a)+.5*sin
    (2*a));
9 P=V_or^2/R;      printf("power absorbed=%.2f W",P);
10
11 disp("when firing angle delay is of 90deg");
12 a=%pi/2;
13 V_or=(sqrt(2)*V/(2*sqrt(%pi)))*sqrt((%pi-a)+.5*sin
    (2*a));
14 P=V_or^2/R;      printf("power absorbed=%.2f W",P);
```

Scilab code Exa 6.2 1 to find value of charging current 2 power supplied to batter

```

1 clear;
2 clc;
3 V=230;
4 E=150;
5 R=8;
6 th1=asind(E/(sqrt(2)*V));
7 I_o=(1/(2*pi*R))*(2*sqrt(2)*230*cosd(th1)-E*(pi-2*
    th1*pi/180));
8 printf("avg charging current=%f A",I_o);
9
10 P=E*I_o;      printf("\npower supplied to the battery=%
    .2 f W",P);
11 I_or=sqrt((1/(2*pi*R^2))*((V^2+E^2)*(%pi-2*th1*%pi
    /180)+V^2*sind(2*th1)-4*sqrt(2)*V*E*cosd(th1)));
12 P_r=I_or^2*R;      printf("\npower dissipated by the
    resistor=%f W",P_r);
13
14 pf=(P+P_r)/(V*I_or);      printf("\nsupply pf=%f",pf
    );

```

Scilab code Exa 6.3 1 to find value of charging current 2 power supplied to batter

```

1 clear;
2 clc;
3 V=230;
4 E=150;
5 R=8;
6 a=35;
7 th1=asind(E/(sqrt(2)*V));
8 th2=180-th1;
9 I_o=(1/(2*pi*R))*(sqrt(2)*230*(cosd(a)-cosd(th2))-E
    *((th2-a)*pi/180));
10 printf("avg charging current=%f A",I_o);
11
12 P=E*I_o;      printf("\npower supplied to the battery=%
    .2 f W",P);

```

```

    %.2 f W' ,P);
13 I_or=sqrt((1/(2*pi*R^2))*((V^2+E^2)*((th2-a)*pi
    /180)-(V^2/2)*(sind(2*th2)-sind(2*a))-2*sqrt(2)*V
    *E*(cosd(a)-cosd(th2)));
14 P_r=I_or^2*R;      printf("\npower dissipated by the
    resistor=% .2 f W" ,P_r);
15
16 pf=(P+P_r)/(V*I_or);      printf("\nsupply pf=% .4 f" ,pf
    );
17 //Answers have small variations from that in the
    book due to difference in the rounding off of
    digits.

```

Scilab code Exa 6.4 to find ckt turn off time avg output voltage and avg load curr

```

1 clear;
2 clc;
3 B=210;
4 f=50;      //Hz
5 w=2*pi*f;
6 a=40;      //firing angle
7 V=230;
8 disp(" for R=5ohm and L=2mH");
9 R=5;
10 L=2*10^-3;
11 t_c=(360-B)*pi/(180*w);      printf(" ckt turn off
    time=% .3 f msec" ,t_c*1000);
12 V_o=(sqrt(2)*230/(2*pi))*(cosd(a)-cosd(B));
    printf("\navg output voltage=% .3 f V" ,V_o);
13 I_o=V_o/R;      printf("\navg output current=% .4 f A" ,
    I_o);
14
15 disp(" for R=5ohm, L=2mH and E=110V");
16 E=110;
17 R=5;

```

```

18 L=2*10^-3;
19 th1=asind(E/(sqrt(2)*V));
20 t_c=(360-B+th1)*%pi/(180*w);      printf(" ckt turn off
   time=%f msec",t_c*1000);
21 V_o=(sqrt(2)*230/(2*pi))*(cosd(a)-cosd(B));
   printf("\navg output voltage=%f V",V_o);
22 I_o=(1/(2*pi*R))*(sqrt(2)*230*(cosd(a)-cosd(B))-E
   *((B-a)*pi/180));      printf("\navg output
   current=%f A",I_o);
23 V_o=R*I_o+E;      printf("\navg output voltage=%f V"
   ,V_o);

```

Scilab code Exa 6.5 to determine 1 rectification efficiency 2 form factor 3 voltag

```

1 clear;
2 clc;
3 V_s=230;
4 f=50;
5 R=10;
6 a=60;
7 V_m=(sqrt(2)*V_s);
8 V_o=V_m/(2*pi)*(1+cosd(a));
9 I_o=V_o/R;
10 V_or=(V_m/(2*sqrt(pi)))*sqrt((pi-a*pi/180)+.5*
   sind(2*a));
11 I_or=V_or/R;
12 P_dc=V_o*I_o;
13 P_ac=V_or*I_or;
14 RE=P_dc/P_ac;      printf(" rectification efficiency=%
   .4 f",RE);
15 FF=V_or/V_o;      printf("\nform factor=%f",FF);
16 VRF=sqrt(FF^2-1);      printf("\nvoltage ripple factor
   =%f",VRF);
17 TUF=P_dc/(V_s*I_or);      printf("\nutilisation
   factor=%f",TUF);

```

```
18 PIV=V_m;      printf("\nPIV of thyristor=%f V",PIV);
```

Scilab code Exa 6.6 to find power handled by mid pt convertor and single phase bri

```
1 clear;
2 clc;
3 V=1000;
4 fos=2.5; //factor of safety
5 I_TAV=40;
6 disp("for mid pt convertor");
7 V_m=V/(2*fos);
8 P=(2*V_m/%pi)*I_TAV;    printf("power handled=%f kW",P/1000);
9 disp("for bridge convertor");
10 V_m=V/(fos);
11 P=(2*V_m/%pi)*I_TAV;    printf("power handled=%f kW",P/1000);
```

Scilab code Exa 6.7 compute firing angle delay and pf

```
1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 R=.4;
6 I_o=10;
7 I_or=I_o;
8 E=120;
9 a=acosd((E+I_o*R)*%pi/(2*V_m));    printf("firing
angle delay=%f deg",a);
10 pf=(E*I_o+I_or^2*R)/(V_s*I_or);    printf("\n pf=%f",pf);
11
```

```

12 E=-120;
13 a=acosd((E+I_o*R)*%pi/(2*V_m));      printf("\n firing
    angle delay=%f deg",a);
14 pf=(-E*I_o-I_or^2*R)/(V_s*I_or);      printf("\n pf=%f f
    ",pf);

```

Scilab code Exa 6.9 to find avg output current and power delivered

```

1 clear;
2 clc;
3 V_s=230;
4 f=50;
5 a=45;
6 R=5;
7 E=100;
8 V_o=((sqrt(2)*V_s)/(2*pi))*(3+cosd(a));
9 I_o=(V_o-E)/R;      printf("avg o/p current=%f A",
    I_o);
10 P=E*I_o;      printf("\n power delivered to battery=%f
    kW",P/1000);

```

Scilab code Exa 6.10 to find avg value of load current and new value under given c

```

1 clear;
2 clc;
3 V_s=230;
4 f=50;
5 a=50;
6 R=6;
7 E=60;
8 V_o=((sqrt(2)*2*V_s)/(pi))*(cosd(a));
9 I_o=(V_o-E)/R;      printf("avg o/p current=%f A",
    I_o);

```

```

10
11 //ATQ after applying the conditions
12 V_o=((sqrt(2)*V_s)/(%pi))*(cosd(a));
13 I_o=(V_o-E)/R;      printf("\navg o/p current after
change=%f A",I_o);

```

Scilab code Exa 6.11 to calculate the input and output performance parameters for

```

1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 a=45;
6 R=10;
7 V_o=(2*V_m/%pi)*cosd(a);
8 I_o=V_o/R;
9 V_or=V_m/sqrt(2);
10 I_or=I_o;
11 P_dc=V_o*I_o;
12 P_ac=V_or*I_or;
13 RE=P_dc/P_ac;      printf("rectification efficiency=%
.4f",RE);
14 FF=V_or/V_o;      printf("\nform factor=%f",FF);
15 VRF=sqrt(FF^2-1);      printf("\nvoltage ripple factor
=%f",VRF);
16 I_s1=2*sqrt(2)*I_o/%pi;
17 DF=cosd(a);
18 CDF=.90032;
19 pf=CDF*DF;      printf("\nPF=%f",pf);
20 HF=sqrt((1/CDF^2)-1);      printf("\nHF=%f",HF);
21 printf("\nactive power=%f W",P_dc);
22 Q=2*V_m*I_o*sind(a)/%pi;      printf("\nreactive power
=%f Var",Q);

```

Scilab code Exa 6.12 to calculate the input and output performance parameters for

```
1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 a=45;
6 R=10;
7 V_o=(V_m/%pi)*(1+cosd(a));
8 I_o=V_o/R;
9 V_or=V_s*sqrt((1/%pi)*(%pi-a*pi/180)+sind(2*a)/2))
;
10 I_or=I_o;
11 P_dc=V_o*I_o;
12 P_ac=V_or*I_or;
13 RE=P_dc/P_ac;      printf(" rectification efficiency=%
.4 f",RE);
14 FF=V_or/V_o;       printf("\nform factor=% .3 f",FF);
15 VRF=sqrt(FF^2-1);   printf("\nvoltage ripple factor =
% .3 f",VRF);
16 I_s1=2*sqrt(2)*I_o*cosd(a/2)/%pi;
17 DF=cosd(a/2);      printf("\nDF=% .4 f",DF);
18 CDF=2*sqrt(2)*cosd(a/2)/sqrt(%pi*(%pi-a*pi/180));
printf("\nCDF=% .4 f",CDF);
19 pf=CDF*DF;         printf("\n pf=% .4 f",pf);
20 HF=sqrt((1/CDF^2)-1);   printf("\nHF=% .4 f",HF);
21 printf("\n active power=% .3 f W",P_dc);
22 Q=V_m*I_o*sind(a)/%pi;   printf("\n reactive power=%
.2 f Var",Q);
23 //Answers have small variations from that in the
book due to difference in the rounding off of
digits.
```

Scilab code Exa 6.13 determine 1 firing angle 2 avg and rms values of load current

```
1 clear;
2 clc;
3 V_s=230;
4 R=10;
5 V_ml=sqrt(2)*V_s;
6 V_om=3*V_ml/(2*pi);
7 V_o=V_om/2;
8 th=30;
9 a=acosd((2*pi*sqrt(3)*V_o/(3*V_ml)-1))-th;
    printf("delay angle=%1f deg",a);
10 I_o=V_o/R;      printf("\navg load current=%3f A",I_o
    );
11 V_or=V_ml/(2*sqrt(pi))*sqrt((5*pi/6-a*pi/180)+.5*
    sind(2*a+2*th));
12 I_or=V_or/R;    printf("\nrms load current=%3f A",
    I_or);
13 RE=V_o*I_o/(V_or*I_or);    printf("\nrectification
    efficiency=%4f",RE);
```

Scilab code Exa 6.15 to calculate 1 avg value of load volatage 2 avg and rms current

```
1 clear;
2 clc;
3 V=400;
4 V_ml=sqrt(2)*V;
5 v_T=1.4;
6 disp("for firing angle = 30deg");
7 a=30;
8 V_o=3*V_ml/(2*pi)*cosd(a)-v_T;      printf("avg
    output voltage=%3f V",V_o);
```

```

9 disp(" for firing angle = 60 deg");
10 a=60;
11 V_o=3*V_m1/(2*pi)*cosd(a)-v_T;      printf(" avg
12          output voltage=%f V",V_o);
13 I_o=36;
14 I_TA=I_o/3;      printf("\n avg current rating=%f A",
15           I_TA);
15 I_Tr=I_o/sqrt(3);      printf("\n rms current rating=%
16 .3 f A",I_Tr);
16 printf("\n PIV of SCR=%f V",V_m1);
17
18 P=I_TA*v_T;      printf("\n power dissipated=%f W",P)
19 ;

```

Scilab code Exa 6.17 to compute firing angle delay and supply pf

```

1 clear;
2 clc;
3 E=200;
4 I_o=20;
5 R=.5;
6 V_o=E+I_o*R;
7 V_s=230;
8 V_m1=sqrt(2)*V_s;
9 a=acosd(V_o*pi/(3*V_m1));      printf(" firing angle
10          delay=%f deg",a);
11 th=120;
11 I_s=sqrt((1/pi)*I_o^2*th*pi/180);
12 P=E*I_o+I_o^2*R;
13 pf=P/(sqrt(3)*V_s*I_s);      printf("\n pf=%f",pf);
14
15 V_o=E-I_o*R;
16 a=acosd(-V_o*pi/(3*V_m1));      printf("\n firing
17          angle delay=%f deg",a);

```

Scilab code Exa 6.18 to find commutation time and reverse voltage across SCR

```
1 clear;
2 clc;
3 V=230;
4 f=50;
5 w=2*pi*f;
6 disp(" for firing angle delay=0deg");
7 a=0;
8 t_c=(4*pi/3-a*pi/180)/w;      printf(" commutation
    time=%f ms",t_c*1000);
9 printf("\npeak reverse voltage=%f V",sqrt(2)*V);
10
11 disp(" for firing angle delay=30deg");
12 a=30;
13 t_c=(4*pi/3-a*pi/180)/w;      printf(" commutation
    time=%f ms",t_c*1000);
14 printf("\npeak reverse voltage=%f V",sqrt(2)*V);
```

Scilab code Exa 6.19 to find the magnitude of per phase input supply voltage

```
1 clear;
2 clc;
3 a=30;
4 R=10;
5 P=5000;
6 V_s=sqrt(P*R*2*pi/(2*3)/(%pi/3+sqrt(3)*cosd(2*a)/2)
    );
7 V_ph=V_s/sqrt(3);      printf(" per phase voltage , V_ph
    =%f V",V_ph);
8 I_or=sqrt(P*R);
```

```

9 V_s=I_or*%pi/(sqrt(2)*3*cosd(a));
10 V_ph=V_s/sqrt(3);
11 printf("\nfor constant load current");
12 printf("\nV_ph=%f V",V_ph);

```

Scilab code Exa 6.20 to find magnitude of input per phase supply voltage

```

1 clear;
2 clc;
3 a=30;
4 R=10;
5 P=5000;
6 V_s=sqrt(P*R*4*pi/(2*3)/(2*pi/3+sqrt(3)*(1+cosd(2*a))/2));
7 V_ph=V_s/sqrt(3);      printf("per phase voltage , V_ph
                           =%.3f V",V_ph);
8 I_or=sqrt(P*R);
9 V_s=I_or*2*pi/(sqrt(2)*3*(1+cosd(a)));
10 V_ph=V_s/sqrt(3);
11 printf("\nfor constant load current");
12 printf("\nV_ph=%f V",V_ph);

```

Scilab code Exa 6.21 to find magnitude of input per phase supply voltage

```

1 clear;
2 clc;
3 a=90;
4 R=10;
5 P=5000;
6 V_s=sqrt(P*R*4*pi/(2*3)/((pi-%pi/2)+(sind(2*a))/2)
                  );
7 V_ph=V_s/sqrt(3);      printf("per phase voltage , V_ph
                           =%.2f V",V_ph);

```

```

8 I_or=sqrt(P*R);
9 V_s=I_or*2*pi/(sqrt(2)*3*(1+cosd(a)));
10 V_ph=V_s/sqrt(3);
11 printf("\nfor constant load current");
12 printf("\nV_ph=%f V", V_ph);

```

Scilab code Exa 6.22 to compute firing angle delay and supply pf

```

1 clear;
2 clc;
3 E=200;
4 I_o=20;
5 R=.5;
6 V_o=E+I_o*R;
7 V_s=230;
8 V_ml=sqrt(2)*V_s;
9 a=acosd(V_o*2*pi/(3*V_ml)-1);      printf("firing
angle delay=%f deg",a);
10 a1=180-a;
11 I_sr=sqrt((1/pi)*I_o^2*(a1*pi/180));
12 P=V_o*I_o;
13 pf=P/(sqrt(3)*V_s*I_sr);      printf("\n pf=%f",pf);

```

Scilab code Exa 6.23 to calculate rectification efficiency TUF and input power fac

```

1 clear;
2 clc;
3 V_s=400;
4 f=50;
5 I_o=15;
6 a=45;
7 I_TA=I_o*120/360;
8 I_Tr=sqrt(I_o^2*120/360);

```

```

9 I_sr=sqrt(I_o^2*120/180);
10 V_ml=sqrt(2)*V_s;
11 V_o=3*V_ml*cosd(a)/%pi;
12 V_or=V_ml*sqrt((3/(2*pi))*(pi/3+sqrt(3/2)*cosd(2*a
    ))));
13 I_or=I_o;
14 P_dc=V_o*I_o;
15 P_ac=V_or*I_or;
16 RE=P_dc/P_ac;      printf(" rectification efficiency=%
    .5 f",RE);
17 VA=3*V_s/sqrt(3)*I_sr;
18 TUF=P_dc/VA;      printf("\nTUF=% .4 f",TUF);
19 pf=P_ac/VA;      printf("\ninput pf=% .3 f",pf);

```

Scilab code Exa 6.24 to find DF CDF THD and pf and to calculate the active and reactive power.

```

1 clear;
2 clc;
3 I=10;
4 a=45;
5 V=400;
6 f=50;
7 DF=cosd(a);
8 printf("DF=% .3 f",DF);
9 I_o=10;
10 I_s1=4*I_o/(sqrt(2)*%pi)*sin(pi/3);
11 I_sr=I_o*sqrt(2/3);
12 I_o=1;      //suppose
13 CDF=I_s1/I_sr;      printf("\nCDF=% .3 f",CDF);
14 THD=sqrt(1/CDF^2-1);      printf("\nTHD=% .5 f",THD);
15 pf=CDF*DF;      printf("\nPF=% .4 f",pf);
16 P=(3*sqrt(2)*V*cosd(a)/%pi)*I;      printf("\nactive
    power=% .2 f W",P);
17 Q=(3*sqrt(2)*V*sind(a)/%pi)*I;      printf("\nreactive
    power=% .2 f Var",Q);

```

Scilab code Exa 6.25 calculate the power delivered to load and input pf

```
1 // calculate the power delivered to load and i/p pf
2
3 clc;
4 disp(" for firing angle=30deg");
5 a=30;
6 V=400;
7 V_ml=sqrt(2)*V;
8 V_o=3*V_ml*cosd(a)/%pi;
9 E=350;
10 R=10;
11 I_o=(V_o-E)/R;
12 I_or=I_o;
13 P=V_o*I_o;      printf(" power delivered to load=%.2f W
",P);
14 I_sr=I_o*sqrt(2/3);
15 VA=3*V/sqrt(3)*I_sr;
16 pf=P/VA;      printf("\n pf=% .4f ",pf);
17
18 disp(" for firing advance angle=60deg");
19 a=180-60;
20 V=400;
21 V_ml=sqrt(2)*V;
22 V_o=3*V_ml*cosd(a)/%pi;
23 E=-350;
24 R=10;
25 I_o=(V_o-E)/R;
26 I_or=I_o;
27 P=-V_o*I_o;      printf(" power delivered to load=% .2f
W",P);
28 I_sr=I_o*sqrt(2/3);
29 VA=3*V/sqrt(3)*I_sr;
30 pf=P/VA;      printf("\n pf=% .4f ",pf);
```

31 // Answers have small variations from that in the book due to difference in the rounding off of digits.

Scilab code Exa 6.26 calculate overlap angle for different firing angles

```
1 clear;
2 clc;
3 a=0;
4 u=15;
5 i=cosd(a)-cosd(a+u);
6 disp(" for firing angle=30deg");
7 a=30;
8 u=acosd(cosd(a)-i)-a;      printf(" overlap angle=%f
deg",u);
9 disp(" for firing angle=45deg");
10 a=45;
11 u=acosd(cosd(a)-i)-a;     printf(" overlap angle=%f
deg",u);
12 disp(" for firing angle=60deg");
13 a=60;
14 u=acosd(cosd(a)-i)-a;     printf(" overlap angle=%f
deg",u);
```

Scilab code Exa 6.28 to calculate firing angle delay and overlap angle

```
1 clear;
2 clc;
3 E=400;
4 I_o=20;
5 R=1;
6 V_o=E+I_o*R;
7 f=50;
```

```

8 w=2*pi*f
9 L=.004;
10 V=230; //per phase voltage
11 V_ml=sqrt(6)*V;
12 a=acosd(%pi/(3*V_ml)*(V_o+3*w*L*I_o/%pi)); printf
    ("firing angle delay=%3f deg",a);
13 u=acosd(%pi/(3*V_ml)*(V_o-3*w*L*I_o/%pi))-a;
    printf("\noverlap angle=%2f deg",u);
14 //Answers have small variations from that in the
    book due to difference in the rounding off of
    digits .

```

Scilab code Exa 6.29 to calculate firing angle firing angle delay and overlap angl

```

1 clear;
2 clc;
3 V=400;
4 f=50;
5 w=2*pi*f;
6 R=1;
7 E=230;
8 I=15;
9 V_o=-E+I*R;
10 V_ml=sqrt(2)*V;
11 a=acosd(V_o*2*pi/(3*V_ml)); printf("firing angle
    =%3f deg",a);
12 L=0.004;
13 a=acosd((2*pi)/(3*V_ml)*(V_o+3*w*L*I/(2*pi)));
    printf("\nfiring angle delay=%3f deg",a);
14 u=acosd(cosd(a)-3*f*L*I/V_ml)-a; printf("\
    overlap angle=%3f deg",u);
15 //Answers have small variations from that in the
    book due to difference in the rounding off of
    digits .

```

Scilab code Exa 6.31 calculate the peak value of circulating current

```
1 clear;
2 clc;
3 V=230; //per phase
4 V_ml=sqrt(3)*sqrt(2)*V;
5 f=50;
6 w=2*pi*f;
7 a1=60;
8 L=0.015;
9 i_cp=(sqrt(3)*V_ml/(w*L))*(1-sind(a1));      printf("circulating current=%f A",i_cp);
```

Scilab code Exa 6.32 to determine 1 avg output voltage 2 avg output current 3 avg

```
1 clear;
2 clc;
3 V=230;
4 V_m=sqrt(2)*V;
5 a=30;
6 V_o=2*V_m*cosd(a)/%pi;      printf("avg o/p voltage=%f V",V_o);
7 R=10;
8 I_o=V_o/R;      printf("\navg o/p current=%f A",I_o);
9 I_TA=I_o*%pi/(2*%pi);      printf("\navg value of thyristor current=%f A",I_TA);
10 I_Tr=sqrt(I_o^2*%pi/(2*%pi));      printf("\nrms value of thyristor current=%f A",I_Tr);
11 I_s=sqrt(I_o^2*%pi/(%pi));
12 I_o=I_s;
13 pf=(V_o*I_o/(V*I_s));      printf("\n pf=%f",pf);
```

14 //Answers have small variations from that in the
book due to difference in the rounding off of
digits .

Scilab code Exa 6.33 to determine 1 avg output voltage 2 angle of overlap 3 pf

```
1 clear;
2 clc;
3 V=230;
4 V_m=sqrt(2)*V;
5 a=30;
6 L=.0015;
7 V_o=2*V_m*cosd(a)/%pi;
8 R=10;
9 I_o=V_o/R;
10 f=50;
11 w=2*%pi*f;
12 V_ox=2*V_m*cosd(a)/%pi-w*L*I_o/%pi;      printf(" avg o
/p voltage=%.3f V",V_ox);
13 u=acosd(cosd(a)-I_o*w*L/V_m)-a;      printf("\nangle
of overlap=%.3f deg",u);
14 I=I_o;
15 pf=V_o*I_o/(V*I);      printf("\n pf=%.4f",pf);
16 //Answers have small variations from that in the
book due to difference in the rounding off of
digits .
```

Scilab code Exa 6.34 calculate the generator mean voltage

```
1 clear;
2 clc;
3 V=415;
4 V_ml=sqrt(2)*V;
```

```

5 a1=35; //firing angle advance
6 a=180-a1;
7 I_o=80;
8 r_s=0.04;
9 v_T=1.5;
10 X_l=.25; //reactance=w*L
11 E=-3*V_ml*cosd(a)/%pi+2*I_o*r_s+2*v_T+3*X_l*I_o/%pi;
    printf("mean generator voltage=%f V",E);

```

Scilab code Exa 6.35 find the mean value of E

```

1 clear;
2 clc;
3 V=415;
4 V_ml=sqrt(2)*V;
5 R=.2;
6 I_o=80;
7 r_s=0.04;
8 v_T=1.5;
9 X_l=.25; //reactance=w*L
10
11 disp("when firing angle=35deg");
12 a=35;
13 E=(-3*V_ml*cosd(a)/%pi+I_o*R+2*I_o*r_s+2*v_T+3*X_l*
    I_o/%pi);      printf("mean generator voltage=%f
    V",E);
14 disp("when firing angle advance=35deg");
15 a1=35;
16 a=180-a1;
17 E=(-3*V_ml*cosd(a)/%pi+I_o*R+2*I_o*r_s+2*v_T+3*X_l*
    I_o/%pi);      printf("mean generator voltage=%f
    V",E);

```

Scilab code Exa 6.36 to find avg current through battery

```
1 clear;
2 clc;
3 R=5;
4 V=230;
5 V_mp=sqrt(2)*V;
6 a=30;
7 E=150;
8 B=180-asind(E/V_mp);
9 I_o=(3/(2*pi*R))*(V_mp*(cosd(a+30)-cosd(B))-E*((B-a
-30)*pi/180));
10 printf("avg current flowing=%f A",I_o);
```

Scilab code Exa 6.37 to determine 1 avg output voltage 2 avg output current 3

```
1 clear;
2 clc;
3 a=30;
4 V=230;
5 V_m=sqrt(2)*V;
6 V_o=V_m*(1+cosd(a))/pi;      printf("avg o/p voltage=
%3f V",V_o);
7 E=100;
8 R=10;
9 I_o=(V_o-E)/R;      printf("\n avg o/p current=%f A",
I_o);
10 I_TA=I_o*pi/(2*pi);      printf("\n avg value of
thyristor current=%f A",I_TA);
11 I_Tr=sqrt(I_o^2*pi/(2*pi));      printf("\n rms value
of thyristor current=%f A",I_Tr);
12 printf("\n avg value of diode current=%f A",I_TA);
13 printf("\n rms value of diode current=%f A",I_Tr);
14 I_s=sqrt(I_o^2*(1-a/180)*pi/(pi));
15 I_or=I_o;
```

```

16 P=E*I_o+I_or^2*R;
17 pf=(P/(V*I_s));      printf ("\n pf=%f",pf);
18 f=50;
19 w=2*pi*f;
20 t_c=(1-a/180)*pi/w;    printf ("\ncircuit turn off
                           time=%f ms",t_c*1000);

```

Scilab code Exa 6.38 to calculate peak value of circulating currents and of both c

```

1 clear;
2 clc;
3 V=230;
4 V_m=sqrt(2)*V;
5 L=0.05;
6 f=50;
7 w=2*pi*f;
8 a=30;
9 i_cp=2*V_m*(1-cosd(a))/(w*L);    printf ("peak value
   of circulating current=%f A",i_cp);
10 R=30;
11 i_l=V_m/R;
12 i1=i_cp+i_l;    printf ("\npeak value of current in
   convertor 1=%f A",i1);
13 i2=i_cp;    printf ("\npeak value of current in
   convertor 2=%f A",i2);

```

Scilab code Exa 6.39 to estimate triggering angle for no current transients and fo

```

1 clear;
2 clc;
3 f=50;
4 w=2*pi*f;
5 R=5;

```

```
6 L=0.05;
7 disp(" for no current transients");
8 phi=atand(w*L/R);      printf(" triggering angle=%2f
    deg",phi);
9 disp(" for worst transients");
10 phi=90+atand(w*L/R);   printf(" triggering angle=%2f
    f deg",phi);
```

Chapter 7

Choppers

Scilab code Exa 7.2 to calculate 1 avg and rms values of output voltage 2 chopper

```
1 clear;
2 clc;
3 a=.4;      //duty cycle ,a=T_on/T
4 V_s=230;
5 R=10;
6 V=a*(V_s-2);    printf("avg o/p voltage=%1f V",V);
7 V_or=sqrt(a*(V_s-2)^2);    printf("\nrms value of o/
    p voltage=%1f V",V_or);
8 P_o=V_or^2/R;
9 P_i=V_s*V/R;
10 n=P_o*100/P_i;    printf("\nchopper efficiency in
    percentage=%2f",n);
```

Scilab code Exa 7.3 to compute pulse width of output voltage and avg value of new

```
1 clear;
2 clc;
3 V_i=220;
```

```

4 V_o=660;
5 a=1-V_i/V_o;
6 T_on=100;      // microsecond
7 T=T_on/a;
8 T_off=T-T_on;   printf("pulse width of o/p voltage=
    %.0 f us",T_off);
9
10 T_off=T_off/2;
11 T_on=T-T_off;
12 a=T_on/T;
13 V_o=V_i/(1-a);   printf("\nnew o/p voltage=% .0 f V",
    V_o);

```

Scilab code Exa 7.4 to find time ratio for chopper

```

1 clear;
2 clc;
3 I_1=12;
4 I_2=16;
5 I_0=(I_1+I_2)/2;
6 R=10;
7 V_0=I_0*R;
8 V_s=200;
9 a=V_0/V_s;
10 r=a/(1-a);    printf("time ratio (T_on/T_off)=%.3 f",r)
    );

```

Scilab code Exa 7.5 to compute pulse width of output voltage and avg value of new

```

1 clear;
2 clc;
3 V_o=660;
4 V_s=220;

```

```

5 a=(V_o/V_s)/(1+(V_o/V_s));
6 T_on=120;
7 T=T_on/a;
8 T_off=T-T_on;      printf(" pulse width o/p voltage=%0.
f us",T_off);
9
10 T_off=3*T_off;
11 T_on=T-T_off;
12 a=T_on/(T_on+T_off);
13 V_o=V_s*(a/(1-a));    printf("\nnew o/p voltage=%0.2 f
V",V_o);

```

Scilab code Exa 7.11 1 to find whether load current is cont 2 calculate value of a

```

1 clear;
2 clc;
3 R=1;
4 L=.005;
5 T_a=L/R;
6 T=2000*10^-6;
7 E=24;
8 V_s=220;
9 T_on=600*10^-6;
10 a=T_on/T;
11 a1=(T_a/T)*log(1+(E/V_s)*((exp(T/T_a))-1));
12 if(a1<a)
13     disp("load current in continuous");
14 else
15     disp("load current in discont.");
16 end
17 I_o=(a*V_s-E)/R;      printf(" avg o/p current=%0.0 f A",
I_o);
18 I_mx=(V_s/R)*((1-exp(-T_on/T_a))/(1-exp(-T/T_a))-E/
R;      printf("\nmax value of steady current=%0.2 f
A",I_mx);

```

```

19 I_mn=(V_s/R)*((exp(T_on/T_a)-1)/(exp(T/T_a)-1))-E/R;
      printf("\nmin value of steady current=%f A"
             ,I_mn);
20
21 f=1/T;
22 w=2*pi*f;
23 I1=(2*V_s/(sqrt(2)*pi)*sind(180*a))/(sqrt(R^2+(w*L)
      ^2));    printf("\nfirst harmonic current=%f A"
             ,I1);
24 I2=(2*V_s/(2*sqrt(2)*pi)*sind(2*180*a))/(sqrt(R^2+
      w*L*2)^2));    printf("\nsecond harmonic current=%
      .4f A",I2);
25 I3=(2*V_s/(3*sqrt(2)*pi)*sind(3*180*a))/(sqrt(R^2+
      w*L*3)^2));    printf("\nthird harmonic current=%
      .5f A",I3);
26
27 I_TAV=a*(V_s-E)/R-L*(I_mx-I_mn)/(R*T);    printf("\\
      navg supply current=%f A",I_TAV);
28
29 P1=I_TAV*V_s;
30 printf("\ni/p power=%f W",P1);
31 P2=E*I_o;
32 printf("\npower absorbed by load emf=%f W",P2);
33 printf("\npower loss in resistor=%f W",P1-P2);
34 I_or=sqrt(I_o^2+I1^2+I2^2+I3^2);
35 printf("\nrms value of load current=%f A",I_or);

```

Scilab code Exa 7.12 1 to find whether load current is cont or not 2 to calculate

```

1 clear;
2 clc;
3 R=1;
4 L=.001;
5 V_s=220;
6 E=72;

```

```

7 f=500;
8 T_on=800*10^-6;
9 T_a=L/R;
10 T=1/f;
11 m=E/V_s;
12 a=T_on/T;
13 a1=(T_a/T)*log(1+m*(exp(-T/T_a)-1));
14 if(a1>a)
    disp("load current is continuous");
15 else
    disp("load current is discontinuous");
16 end
17 t_x=T_on+L*log(1+((V_s-E)/272)*(1-exp(-T_on/T_a)));
18 //Value of t_x wrongly calculated in the book so ans
   of V_o and I_o varies
19 V_o=a*V_s+(1-t_x/T)*E;      printf("avg o/p voltage=%
   .2f V",V_o);
20 I_o=(V_o-E)/R;      printf("\navg o/p current=% .2f A",
   I_o);
21 printf("\nmin value of load current=% .0f A",0);
22 I_mx=(V_s-E)/R*(1-exp(-T_on/T_a));      printf("\nmax
   value of load current=% .1f A",I_mx);

```

Scilab code Exa 7.13 to find the chopping freq

```

1 clear;
2 clc;
3 a=.2;
4 V_s=500;
5 E=a*V_s;
6 L=0.06;
7 I=10;
8 T_on=(L*I)/(V_s-E);
9 f=a/T_on;      printf("chopping freq=% .2f Hz",f);

```

Scilab code Exa 7.14 to find the value of external inductance to be added in series

```
1 clear;
2 clc;
3 a=.5;
4 pu=.1; //pu ripple
5 //x=T/T_a
6 //y=exp(-a*x)
7 y=(1-pu)/(1+pu);
8 //after solving
9 x=log(1/y)/a;
10 f=1000;
11 T=1/f;
12 T_a=T/x;
13 R=2;
14 L=R*T_a;
15 Li=.002;
16 Le=L-Li; printf("external inductance=%f mH",Le
*1000);
```

Scilab code Exa 7.15 1 to calculate min and max value of load current 2 max va

```
1 clear;
2 clc;
3 R=10;
4 L=.015;
5 T_a=L/R;
6 f=1250;
7 T=1/f;
8 a=.5;
9 T_on=a*T;
10 V_s=220;
```

```

11 I_mx=(V_s/R)*((1-exp(-T_on/T_a))/(1-exp(-T/T_a)));
    printf("max value of load current=%f A",I_mx
);
12 I_mn=(V_s/R)*((exp(T_on/T_a)-1)/(exp(T/T_a)-1));
    printf("\nmin value of load current=%f A",I_mn)
;
13 dI=I_mx-I_mn;    printf("\nmax value of ripple
current=%f A",dI);
14 V_o=a*V_s;
15 I_o=V_o/R;      printf("\navg value of load current=%
.2 f A",I_o);
16 I_or=sqrt(I_mx^2+dI^2/3+I_mx*dI);    printf("\nrms
value of load current=%f A",I_or);
17 I_chr=sqrt(a)*I_or;    printf("\nrms value of
chopper current=%f A",I_chr);
18 //Answers have small variations from that in the
book due to difference in the rounding off of
digits.

```

Scilab code Exa 7.17 to find the time for which current flows

```

1 clear;
2 clc;
3 L=0.0016;
4 C=4*10^-6;
5 w=1/sqrt(L*C);
6 t=%pi/w;      printf("time for which current flows=%.
2
f us",t*10^6);

```

Scilab code Exa 7.18 to calculate values of commutating capacitor and commutating

```

1 clear;
2 clc;

```

```

3 t_q=20*10^-6;
4 dt=20*10^-6;
5 t_c=t_q+dt;
6 I_0=60;
7 V_s=60;
8 C=t_c*I_0/V_s;      printf(" value of commutating
                        capacitor=%f uF",C*10^6);
9 L1=(V_s/I_0)^2*C;
10 L2=(2*t_c/pi)^2/C;
11 if(L1>L2)
12     printf("\nvalue of commutating inductor=%f uH"
              ,L1*10^6);
13 else
14     printf("\nvalue of commutating inductor=%f uH"
              ,L2*10^6);
15 end

```

Scilab code Exa 7.19 to calculate the value of comutating component C and comutati

```

1 clear;
2 clc;
3 t=100*10^-6;
4 R=10;
5 //V_s*(1-2*exp(-t/(R*C)))=0
6 C=-t/(R*log(1/2));    printf("Value of comutating
                           component C=%f uF",C*10^6);
7 disp("max permissible current through SCR is 2.5
          times load current");
8 L=(4/9)*C*R^2;        printf("value of comutating
                           component L=%f uH",L*10^6);
9 disp("max permissible current through SCR is 1.5
          times peak diode current");
10 L=(1/4)*C*R^2;        printf("value of comutating
                           component L=%f uH",L*10^6);

```

Scilab code Exa 7.20 to compute 1 effective on period 2 peak current through main

```
1 clear;
2 clc;
3 T_on=800*10^-6;
4 V_s=220;
5 I_o=80;
6 C=50*10^-6;
7 T=T_on+2*V_s*C/I_o;      printf(" effective on period=%
.0 f us",T*10^6);
8
9 L=20*10^-6;
10 C=50*10^-6;
11 i_T1=I_o+V_s*sqrt(C/L);  printf("\npeak current
through main thyristor=% .2 f A",i_T1);
12 i_TA=I_o;    printf("\npeak current through
auxillary thyristor=% .0 f A",i_TA);
13
14 t_c=C*V_s/I_o;    printf("\nturn off time for main
thyristor=% .1 f us",t_c*10^6);
15 t_c1=(%pi/2)*sqrt(L*C);  printf("\nturn off time
for auxillary thyristor=% .3 f us",t_c1*10^6);
16
17 printf("\n total commutation interval=% .0 f us",2*t_c
*10^6);
18
19 t=150*10^-6;
20 v_c=I_o*t/C-V_s;      printf("\n capacitor voltage=% .0 f
V",v_c);
21
22 printf("\n time nedded to recharge the capacitor=% .0 f
us",2*V_s*C/I_o*10^6);
```

Scilab code Exa 7.21 to calculate values of 1 commutating components C and L and 2

```
1 clear;
2 clc;
3 I_o=260;
4 V_s=220;
5 fos=2; //factor of safety
6 t_off=18*10^-6;
7 t_c=2*t_off;
8 C=t_c*I_o/V_s;      printf("Value of C=%f uF",C
                           *10^6);
9 L=(V_s/(.8*I_o))^2*C;    printf("\nvalue of L=%f
                           uH",L*10^6);
10
11 f=400;
12 a_mn=%pi*f*sqrt(L*C);
13 V_omn=V_s*(a_mn+2*f*t_c);    printf("\nmin value of
                           o/p voltage=%f V",V_omn);
14 V_omx=V_s;      printf("\nmax value of o/p voltage=%f
                           V",V_omx);
```

Scilab code Exa 7.22 calculate 1 value of commutating inductor and capacitor 2 max

```
1 clear;
2 clc;
3 x=2;
4 t_q=30*10^-6;
5 dt=30*10^-6;
6 t_c=t_q+dt;
7 V_s=230;
8 I_o=200;
```

```

9 L=V_s*t_c/(x*I_o*(%pi-2*asin(1/x)));      printf("
    value of commutating inductor=%f uH",L*10^6);
10 C=x*I_o*t_c/(V_s*(%pi-2*asin(1/x)));     printf("\
        nvalue of commutating capacitor=%f uF",C*10^6);
11 V_cp=V_s+I_o*sqrt(L/C);      printf("\npeak capacitor
    voltage=%f V",V_cp);
12 I_cp=x*I_o;      printf("\npeak commutataing current=%
    .0 f A",I_cp);
13
14 x=3;
15 L=V_s*t_c/(x*I_o*(%pi-2*asin(1/x));      printf("\
    nvalue of commutating inductor=%f uH",L*10^6);
16 C=x*I_o*t_c/(V_s*(%pi-2*asin(1/x));     printf("\
        nvalue of commutating capacitor=%f uF",C*10^6);
17 V_cp=V_s+I_o*sqrt(L/C);      printf("\npeak capacitor
    voltage=%f V",V_cp);
18 I_cp=x*I_o;      printf("\npeak commutataing current=%
    .0 f A",I_cp);

```

Scilab code Exa 7.23 to compute 1 turn off time of main thyristor 2 total commutat

```

1 clear;
2 clc;
3 V_s=230;
4 C=50*10^-6;
5 L=20*10^-6;
6 I_cp=V_s*sqrt(C/L);
7 I_o=200;
8 x=I_cp/I_o;
9 t_c=(%pi-2*asin(1/x))*sqrt(C*L);      printf("turn off
    time of main thyristor=%f us",t_c*10^6);
10 th1=asind(1/x);
11 t=(5*%pi/2-th1*pi/180)*sqrt(L*C)+C*V_s*(1-cosd(th1)
    )/I_o;      printf("\ntotal commutation interval=%
    .3 f us",t*10^6);

```

```
12 t=(%pi-th1*%pi/180)*sqrt(L*C);      printf("\nturn off  
time of auxillary thyristor=%f us",t*10^6);
```

Scilab code Exa 7.24 to calculate min and max value of load current

```
1 clear;  
2 clc;  
3 tc=.006;  
4 R=10;  
5 L=R*tc;  
6 f=2000;  
7 T=1/f;  
8 V_o=50;  
9 V_s=100;  
10 a=V_o/V_s;  
11 T_on=a*T;  
12 T_off=T-T_on;  
13 dI=V_o*T_off/L;  
14 I_o=V_o/R;  
15 I2=I_o+dI/2;    printf("max value of load current=%  
     .3f A",I2);  
16 I1=I_o-dI/2;    printf("\nmin value of load current=  
     .3f A",I1);
```

Scilab code Exa 7.27 calculate 1 range of speed control 2 range of duty cycle

```
1 clear;  
2 clc;  
3 I_a=30;  
4 r_a=.5;  
5 V_s=220;  
6 a=I_a*r_a/V_s;    printf("min value of duty cycle=%  
     .3f",a);
```

```

7 printf("\nmin Value of speed control=%f rpm",0);
8 a=1;
9 printf("\nmax value of duty cycle=%f",a);
10 k=.1; //V/rpm
11 N=(a*V_s-I_a*r_a)/k;      printf("\nmax value of speed
control=%f rpm",N);

```

Scilab code Exa 7.28 determine chopping freq and duty cycle

```

1 clear;
2 clc;
3 V_t=72;
4 I_a=200;
5 r_a=0.045;
6 N=2500;
7 k=(V_t-I_a*r_a)/N;
8 E_a=k*1000;
9 L=.007;
10 Rm=.045;
11 Rb=0.065;
12 R=Rm+Rb;
13 T_a=L/R;
14 I_mx=230;
15 I_mn=180;
16 T_on=-T_a*log(-((V_t-E_a)/R-I_mx)/((I_mn)-(V_t-E_a)/
R));
17 R=Rm;
18 T_a=L/R;
19 T_off=-T_a*log(-((-E_a)/R-I_mn)/((I_mx)-(-E_a)/R));
20 T=T_on+T_off;
21 f=1/T;      printf("chopping freq=%f Hz",f);
22 a=T_on/T;    printf("\nduty cycle ratio=%f",a);

```

Scilab code Exa 7.29 to determine the higher limit of current pulsation chopping f

```
1 clear;
2 clc;
3 I_mx=425;
4 I_lt=180;      //lower limit of current pulsation
5 I_mn=I_mx-I_lt;
6 T_on=.014;
7 T_off=.011;
8 T=T_on+T_off;
9 T_a=.0635;
10 a=T_on/T;
11 V=(I_mx-I_mn*exp(-T_on/T_a))/(1-exp(-T_on/T_a));
12 a=.5;
13 I_mn=(I_mx-V*(1-exp(-T_on/T_a)))/(exp(-T_on/T_a));
14 T=I_mx-I_mn;   printf("higher limit of current
                    pulsation=%.0f A",T);
15 T=T_on/a;
16 f=1/T;         printf("\nchopping freq=%.3f Hz",f);
17 printf("\nduty cycle ratio=%.2f",a);
18 //Answers have small variations from that in the
    book due to difference in the rounding off of
    digits.
```

Chapter 8

Inverters

Scilab code Exa 8.3 to find the value of C for having load commutation

```
1 clear;
2 clc;
3 T=.1*10^-3;
4 f=1/T;
5 k=15*10^-6; //k=th/w;
6 th=2*pi*f*k;
7 X_l=10;
8 R=2;
9 X_c=R*tan(th)+X_l;
10 C=1/(2*pi*f*X_c);      printf(" value of C=%f uF",C
*10^6);
```

Scilab code Exa 8.4 to find the power delivered

```
1 clear;
2 clc;
3 V_s=230;
4 V_01=2*V_s/(sqrt(2)*pi);
```

```

5 R=2;
6 I_01=V_01/R;
7 P_d=I_01^2*R;      printf(" power delivered to load=%.1
                         f W",P_d);
8 V=V_s/2;
9 I_s=sqrt(2)*I_01/%pi;
10 P_s=V*I_s;
11 printf("\n power delivered by both sources=% .1 f W",2*
          P_s);

```

Scilab code Exa 8.5 to find the power delivered to the load

```

1 clear;
2 clc;
3 V_s=230;
4 V_01=4*V_s/(%pi*sqrt(2));
5 R=1;
6 X_L=6;
7 X_c=7;
8 I_01=V_01/sqrt(R^2+(X_L-X_c)^2);
9 P=I_01^2*R;      printf(" power delivered to the source
                         =%.3 f kW",P/1000);
10 I_s=sqrt(2)*I_01*(2*cosd(45))/%pi;
11 P_s=V_s*I_s;      printf("\n power from the source=% .3 f
                           kW",P_s/1000);

```

Scilab code Exa 8.6 to find rms value of thyristor and diode currents

```

1 clear;
2 clc;
3 disp("when load R=2 ohm");
4 V_01=230;
5 R=2;

```

```

6 I_01=V_01/R;
7 I_m=I_01*sqrt(2);
8 I_T1=I_m/2;      printf("rms value of thyristor
                     current=%f A", I_T1);
9 I_D1=0;          printf("\nrms value of diode current=%f
                     A", I_D1);
10
11 disp("when load R=2ohm, X_L=8ohm and X_C=6ohm");
12 X_L=8;
13 X_C=6;
14 I_01=V_01/sqrt(R^2+(X_L-X_C)^2);
15 phi1=atand((X_L-X_C)/R);
16 I_T1=I_T1*sqrt(2)*.47675;      printf("rms value of
                     thyristor current=%f A", I_T1);
17 I_D1=.1507025*I_m/sqrt(2);      printf("\nrms value of
                     diode current=%f A", I_D1);

```

Scilab code Exa 8.7 to find 1 rms value of fundamental load current 2 power absorb

```

1 clear;
2 clc;
3 // v_o=4*V_s/%pi*(sind(wt)+sind(3*wt)/3+sind(5*wt)/5)
4 V_s=230;
5 R=4;
6 f=50;
7 w=2*pi*f;
8 L=0.035;
9 C=155*10^-6;
10 X_L=w*L;
11 X_C=1/(w*C);
12 Z1=sqrt(R^2+(X_L-X_C)^2);
13 phi1=-atand((X_L-X_C)/R);
14 Z3=sqrt(R^2+(X_L*3-X_C/3)^2);
15 phi3=atand((X_L*3-X_C/3)/R);
16 Z5=sqrt(R^2+(X_L*5-X_C/5)^2);

```

```

17 phi5=atand((X_L*5-X_C/5)/R);
18
19 I_m1=4*V_s/(Z1*pi);
20 I_01=I_m1/sqrt(2);      printf(" rms value of
    fundamental load current=%f A",I_01);
21 I_m3=4*V_s/(3*Z3*pi);
22 I_m5=4*V_s/(5*Z5*pi);
23 I_m=sqrt(I_m1^2+I_m3^2+I_m5^2);
24 I_0=I_m/sqrt(2);
25 P_0=(I_0)^2*R;         printf("\nload power=%f W",P_0);
26 P_01=(I_01)^2*R;       printf("\nfundamental load power
    =%f W",P_01);
27 printf("\nrms value of thyristor current=%f A",I_m
    /2);
28
29 t1=(180-phi1)*pi/(180*w);   printf("\nconduction
    time for thyristor=%f ms",t1*1000);
30 t1=(phi1)*pi/(180*w);       printf("\nconduction time
    for diodes=%f ms",t1*1000);

```

Scilab code Exa 8.8 to determine 1 fundamental rms output voltage 2 total output p

```

1 clear;
2 clc;
3 V_s=230;
4 V_01=2*V_s/(sqrt(2)*pi);      printf(" fundamental rms
    o/p voltage=%f V",V_01);
5 R=10;
6 I_01=V_01/R;
7 P=I_01^2*R;      printf("\nfundamental power to load=%
    .1 f W",P);
8 V_or=sqrt((V_s/2)^2);
9 P=V_or^2/R;       printf("\ntotal o/p power to load=%f
    W",P);
10

```

```

11 I_TP=V_s/(2*R);
12 printf("\navg SCR current=%f A",I_TP*180/360);
13
14 I_or=I_TP;
15 pf=I_01^2*R/(V_or*I_or);      printf("\ni/p pf=%f",
16 pf);
17 DF=V_01/V_or;      printf("\ndistortion factor=%f",
18 DF);
19 V_oh=sqrt(V_or^2-V_01^2);
20 THD=V_oh/V_01;      printf("\nTHD=%f",THD);
21
22 V_03=V_01/3;
23 HF=V_03/V_01;      printf("\nharmonic factor=%f",HF)
24 ;

```

Scilab code Exa 8.9 to calculate 1 rms value of output voltage and fundamental com

```

1 clear;
2 clc;
3 V_s=60;
4 R=3;
5 V_or=sqrt(V_s^2*pi/pi);      printf("rms value of o/
p voltage=%f V",V_or);
6 V_01=4*V_s/(sqrt(2)*pi);      printf("\nfundamental
component of rms voltage=%f V",V_01);
7 P_o=V_or^2/R;      printf("\no/p power=%f W",P_o);
8 P_01=V_01^2/R;      printf("\nfundamental freq o/p
power=%f W",P_01);
9
10 I_s=V_s/R;      printf("\npeak current=%f A",I_s);
11 I_avg=I_s*pi/(2*pi);      printf("\navg current of
each transistor=%f A",I_avg);
12

```

```

13 printf("\npeak reverse blocking voltage=%f V",V_s)
;
14
15 V_03=V_01/3;
16 HF=V_03/V_01;      printf("\nharmonic factor=%f",HF)
;
17
18 V_oh=sqrt(V_or^2-V_01^2);
19 THD=V_oh/V_01;      printf("\nTHD=%f",THD);

```

Scilab code Exa 8.10 1 to calculate THD of output voltage and its distortion factor

```

1 clear;
2 clc;
3 V_s=220;
4 R=6;
5 f=50;
6 w=2*pi*f;
7 L=0.03;
8 C=180*10^-6;
9 X_L=w*L;
10 X_C=1/(w*C);
11
12 V_or=sqrt(V_s^2*pi/pi);
13 V_01=4*V_s/(sqrt(2)*pi);
14 V_oh=sqrt(V_or^2-V_01^2);
15 THD=V_oh/V_01;      printf("THD of voltage=%f",THD);
16 DF=V_01/V_or;      printf("\nDF=%f",DF);
17
18 Z1=sqrt(R^2+(X_L-X_C)^2);
19 phi1=-atand((X_L-X_C)/R);
20 Z3=sqrt(R^2+(X_L*3-X_C/3)^2);
21 phi3=atand((X_L*3-X_C/3)/R);
22 Z5=sqrt(R^2+(X_L*5-X_C/5)^2);
23 phi5=atand((X_L*5-X_C/5)/R);

```

```

24 Z7=sqrt(R^2+(X_L*7-X_C/7)^2);
25 phi7=atand((X_L*7-X_C/7)/R);
26
27 I_01=19.403;
28 I_m1=4*V_s/(Z1*pi);
29 I_m3=4*V_s/(3*Z3*pi);
30 I_m5=4*V_s/(5*Z5*pi);
31 I_m7=4*V_s/(7*Z7*pi);
32 I_m=sqrt(I_m1^2+I_m3^2+I_m5^2+I_m7^2);
33 I_or=I_m/sqrt(2);
34 I_oh=sqrt((I_m^2-I_m1^2)/2);
35 THD=I_oh/I_01;      printf("\nTHD of current=%f",THD
);
36 DF=I_01/I_or;      printf("\nDF=%f",DF);
37
38 P_o=I_or^2*R;      printf("\nload power=%f W",P_o);
39 I_avg=P_o/V_s;      printf("\navg value of load
current=%f A",I_avg);
40
41 t1=(180-phi1)*pi/(180*w);      printf("\nconduction
time for thyristor=%f ms",t1*1000);
42 t1=1/(2*f)-t1;      printf("\nconduction time for
diodes=%f ms",t1*1000);
43
44 I_p=I_m1;      printf("\npeak transistor current=%f
A",I_p);
45 I_t1=.46135*I_p;      printf("\nrms transistor current
=%f A",I_t1);

```

Scilab code Exa 8.11 to determine 1 rms value of load current 2 rms value of thyri

```

1 clear;
2 clc;
3 V_s=450;
4 R=10;

```

```

5 disp(" for 180deg mode");
6 I_or=sqrt((V_s/(3*R))^2*2/3+(2*V_s/(3*R))^2*1/3);
    printf("rms value of load current=%f A",I_or
    );
7 I_T1=sqrt((1/(2*pi))*(V_s/(3*R))^2*2*pi/3+(2*V_s
    /(3*R))^2*pi/3));      printf("\nrms value of load
    current=%f A",I_T1);
8 P=3*I_or^2*R;      printf("\npower delivered to load=%
    .1f kW",P/1000);
9
10 disp(" for 120deg mode");
11 I_or=sqrt((1/(pi))*(V_s/(2*R))^2*2*pi/3));
    printf("rms value of load current=%f A",I_or);
12 I_T1=sqrt((1/(2*pi))*(V_s/(2*R))^2*2*pi/3));
    printf("\nrms value of load current=%f A",I_T1)
    ;
13 P=3*I_or^2*R;      printf("\npower delivered to load=%
    .3f kW",P/1000);

```

Scilab code Exa 8.12 to determine power delivered to load for 1 square wave output

```

1 clear;
2 clc;
3 V_s=230;
4 R=10;
5 f=50;
6 w=2*pi*f;
7 L=0.03;
8 X_L=w*L;
9
10 V_or=sqrt(V_s^2*pi/pi);
11 V_01=4*V_s/(sqrt(2)*pi);
12
13 Z1=sqrt(R^2+(X_L)^2);
14 phi1=-atand((X_L)/R);

```

```

15 Z3=sqrt(R^2+(X_L*3)^2);
16 phi3=atand((X_L*3)/R);
17 Z5=sqrt(R^2+(X_L*5)^2);
18 phi5=atand((X_L*5)/R);
19 Z7=sqrt(R^2+(X_L*7)^2);
20 phi7=atand((X_L*7)/R);
21
22 disp(" using square wave o/p");
23 I_m1=4*V_s/(sqrt(2)*Z1*pi);
24 I_m3=4*V_s/(sqrt(2)*3*Z3*pi);
25 I_m5=4*V_s/(sqrt(2)*5*Z5*pi);
26 I_m7=4*V_s/(sqrt(2)*7*Z7*pi);
27 I_m=sqrt(I_m1^2+I_m3^2+I_m5^2+I_m7^2);
28 P=I_m^2*R; printf(" power delivered=%f W",P);
29
30 disp(" using quasi-square wave o/p");
31 I_01=I_m1*sind(45);
32 I_03=I_m3*sind(3*45);
33 I_05=I_m5*sind(5*45);
34 I_07=I_m7*sind(7*45);
35 I_0=(I_01^2+I_03^2+I_05^2+I_07^2);
36 P=I_0*R; printf(" power delivered=%f W",P);
37
38 disp(" using two symmitrical spaced pulses");
39 g=(180-90)/3+45/2;
40 I_01=2*I_m1*sind(g)*sind(45/2);
41 I_03=2*I_m3*sind(g*3)*sind(3*45/2);
42 I_05=2*I_m5*sind(g*5)*sind(5*45/2);
43 I_07=2*I_m7*sind(g*7)*sind(7*45/2);
44 I_0=(I_01^2+I_03^2+I_05^2+I_07^2);
45 P=I_0*R; printf(" power delivered=%f W",P);

```

Scilab code Exa 8.14 to determine the value of source inductance and also find val

```
1 clear;
```

```

2 clc;
3 f=50;
4 T=1/f;
5 I=.5;
6 di=I/T;      // di=di/dt
7 V_s=220;
8 L=V_s/di;    printf("source inductance=%f H",L);
9
10 t=20*10^-6;
11 fos=2;      // factor of safety
12 t_c=t*fos;
13 R=10;
14 C=t_c/(R*log(2));   printf("\ncommutating capacitor
= %f uF",C*10^6);

```

Scilab code Exa 8.15 to check whether the ckt will commutate by itself or not and

```

1 clear;
2 clc;
3 R=10;
4 L=.01;
5 C=10*10^-6;
6 if(R^2<4*L/C)
7     disp("ckt will commutate on its own");
8 else
9     disp("ckt will not commutate on its own");
10 end
11
12 xie=R/(2*L);
13 w_o=1/sqrt(L*C);
14 w_r=sqrt(w_o^2-xie^2);
15 phi=atand(xie/w_r);
16 t=%pi/w_r;
17 V_s=1;
18 v_L=V_s*(w_o/w_r)*exp(-xie*t)*cosd(180+phi);

```

```

    printf(" voltage across inductor (*V_s)=%f V" ,v_L
);
19 v_c=V_s*(1-(w_o/w_r)*exp(-xie*t)*cosd(180-phi));
    printf("\n voltage across capacitor (*V_s)=%f V" ,
v_c);
20 di=V_s/L;      printf("\ndi/dt*V_s (for t=0)=%.0 f A/s"
,di);

```

Scilab code Exa 8.16 to calculate output freq

```

1 clear;
2 clc;
3 L=.006;
4 C=1.2*10^-6;
5 R=100;
6 T=%pi/sqrt(1/(L*C)-(R/(2*L))^2);
7 T_off=.2*10^-3;
8 f=1/(2*(T+T_off));      printf("o/p freq=%f Hz" ,f);
9
10 disp(" for R=40ohm");
11 R=40;
12 T=%pi/sqrt(1/(L*C)-(R/(2*L))^2);
13 T_off=.2*10^-3;
14 f=1/(2*(T+T_off));      printf(" upper limit o/p freq=%
.1 f Hz" ,f);
15
16 disp(" for R=140ohm");
17 R=140;
18 T=%pi/sqrt(1/(L*C)-(R/(2*L))^2);
19 T_off=.2*10^-3;
20 f=1/(2*(T+T_off));      printf(" lower limit o/p freq=%
.1 f Hz" ,f);

```

Scilab code Exa 8.17 To determine 1 ckt turn off time 2 max possible operating fre

```
1 clear;
2 clc;
3 f=5000;
4 w=2*pi*f;
5 R=3;
6 L=60*10^-6;
7 xie=R/(2*L);
8 C=7.5*10^-6;
9 w_o=1/sqrt(L*C);
10 w_r=sqrt(w_o^2-xie^2);
11 t_c=%pi*(1/w-1/w_r);      printf("ckt turn off time=%
.2f us",t_c*10^6);
12
13 fos=1.5;
14 t_q=10*10^-6;
15 f_max=1/(2*pi*(t_q*fos/pi+1/w_r));      printf("\
nmax possible operating freq=%1f Hz",f_max);
16 //Answers have small variations from that in the
//book due to difference in the rounding off of
//digits.
```

Scilab code Exa 8.18 to calculate power delivered to the load and avg and rms val

```
1 clear;
2 clc;
3 f=5000;
4 w=2*pi*f;
5 R=3;
6 L=60*10^-6;
7 xie=R/(2*L);
8 C=7.5*10^-6;
9 w_o=1/sqrt(L*C);
10 w_r=sqrt(w_o^2-xie^2);
```

```

11 t1=%pi/(2*w_r);
12 V_s=220;
13 V_co=80;
14 I_omx=(V_s+V_co)*exp(-xie*t1)/(w_r*L);
15 I_rms=I_omx/sqrt(2);
16 P=I_rms^2*R;      printf("load power=%f W",P);
17 printf("\nrms value of thyristor current=%f A",
       I_omx/2);
18 I_SA=P/V_s;
19 printf("\navg thyristor current=%f A",I_SA/2);
20 //error in the book. wrong values are placed in the
   I_omx formulae. so all answer varies

```

Scilab code Exa 8.19 to find the value of capacitor C for given conditions

```

1 clear;
2 clc;
3 t=20;
4 fos=2;      //factor of safety
5 t_c=t*fos;
6 n=1/3;
7 R=20;
8 C=n^2*t_c/(4*R*log(2));    printf("value of
                               capacitor=%f uF",C);
9 //printing mistake in the answer in book.

```

Scilab code Exa 8.20 to calculate 1 rms values of phase and line voltages 2 rms va

```

1 clear;
2 clc;
3 V_s=220;
4 V_p=sqrt(2)*V_s/3;      printf("rms value of phasor
                           voltages=%f V",V_p);

```

```

5 V_L=sqrt(3)*V_p;      printf("\nrms value of line
   voltages=%f V",V_L);
6
7 V_p1=sqrt(2)*V_s/%pi;  printf("\nfundamental
   component of phase voltage=%f V",V_p1);
8 V_L1=sqrt(3)*V_p1;     printf("\nfundamental
   component of line voltages=%f V",V_L1);
9
10 V_oh=sqrt(V_L^2-V_L1^2);
11 THD=V_oh/V_L1;        printf("\nTHD=%f",THD);
12
13 V_a1=2*V_s/%pi;
14 V_a5=2*V_s/(5*%pi);
15 V_a7=2*V_s/(7*%pi);
16 V_a11=2*V_s/(11*%pi);
17 R=4;
18 L=0.02;
19 f=50;
20 w=2*%pi*f;
21 Z1=sqrt(R^2+(w*L)^2);
22 Z5=sqrt(R^2+(5*w*L)^2);
23 Z7=sqrt(R^2+(7*w*L)^2);
24 Z11=sqrt(R^2+(11*w*L)^2);
25 I_a1=V_a1/Z1;
26 I_a5=V_a5/Z5;
27 I_a7=V_a7/Z7;
28 I_a11=V_a11/Z11;
29 I_or=sqrt((I_a1^2+I_a5^2+I_a7^2+I_a11^2)/2);
30 P=3*I_or^2*R;        printf("\nload power=%f W",P);
31 I_s=P/V_s;            printf("\navg value of source current=
   %f A",I_s);
32 I_TA=I_s/3;           printf("\navg value of thyristor
   current=%f A",I_TA);

```

Chapter 9

AC Voltage Controllers

Scilab code Exa 9.1 to determine 1 rms value of output voltage 2 power delivered to load

```
1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 a=45;
6 V_or=(V_m/2)*sqrt(1/%pi*((2*%pi-a*%pi/180)+sind(2*a)
/2));      printf("rms value of o/p voltage=%.3f V"
,V_or);
7 R=20;
8 I_or=V_or/R;
9 P_o=I_or^2*R;      printf("\nload power=%.1f W" ,P_o);
10 I_s=I_or;
11 VA=V_s*I_s;
12 pf=P_o/VA;      printf("\ni/p pf=%.4f" ,pf);
13
14 V_o=sqrt(2)*V_s/(2*%pi)*(cosd(a)-1);
15 I_ON=V_o/R;      printf("\navg i/p current=%.4f A",
I_ON);
```

Scilab code Exa 9.2 to calculate 1 rms value of output voltage 2 load power and in

```
1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 a=45;
6 V_or=(V_s)*sqrt(1/%pi*((%pi-a*%pi/180)+sind(2*a)/2))
      ;      printf("rms value of o/p voltage=%f V",
      V_or);
7 R=20;
8 I_or=V_or/R;
9 P_o=I_or^2*R;      printf("\nload power=%f W",P_o);
10 I_s=I_or;
11 VA=V_s*I_s;
12 pf=P_o/VA;      printf("\ni/p pf=%f",pf);
13
14 I_TA=sqrt(2)*V_s/(2*%pi*R)*(cosd(a)+1);      printf("\\
      avg thyristor current=%f A",I_TA);
15 I_Tr=sqrt(2)*V_s/(2*R)*sqrt(1/%pi*((%pi-a*%pi/180)+
      sind(2*a)/2));      printf("\nrms value of
      thyristor current=%f A",I_Tr);
```

Scilab code Exa 9.3 to determine 1 rms output voltage 2 input pf 3 avg and rms thy

```
1 clear;
2 clc;
3 V_s=230;
4 n=6; //on cycles
5 m=4; //off cycles
6 k=n/(n+m);
7 V_or=V_s*sqrt(k);      printf("rms value of o/ voltage
      =%f V",V_or);
8 pf=sqrt(k);      printf("\ni/p pf=%f",pf);
9 R=15;
```

```

10 I_m=V_s*sqrt(2)/R;
11 I_TA=k*I_m/%pi;      printf("\navg thyristor current=%
    .4f A",I_TA);
12 I_TR=I_m*sqrt(k)/2;   printf("\nrms value of
thyristor current=% .3f A",I_TR);

```

Scilab code Exa 9.4 to calculate 1 max values of avg and rms thyristor currents 2

```

1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 R=3;
6 I_TAM=2*V_m/(2*%pi*R);      printf("max value of avg
thyristor current=% .3f A",I_TAM);
7 I_TRM=V_m/(2*R);      printf("\nmax value of avg
thyristor current=% .3f A",I_TRM);
8
9 f=50;
10 w=2*%pi*f;
11 t_c=%pi/w;      printf("\nckt turn off time=% .0f ms",
t_c*1000);

```

Scilab code Exa 9.5 to calculate 1 control range of firing angle 2 max value of rm

```

1 clear;
2 clc;
3 R=3;
4 X_L=4;
5 phi=atand(X_L/R);      printf("min firing angle=% .2f
deg",phi);
6 printf("\nmax firing angle=% .0f deg",180);
7 V_s=230;

```

```

8 Z=sqrt(R^2+X_L^2);
9 I_or=V_s/Z;      printf("\nmax value of rms load
   current=%f A",I_or);
10 P=I_or^2*R;     printf("\nmax power=%f W",P);
11 I_s=I_or;
12 pf=P/(V_s*I_s);    printf("\ni/p pf=%f",pf);
13
14 I_TAM=sqrt(2)*V_s/(%pi*Z);    printf("\nmax value of
   avg thyristor current=%f A",I_TAM);
15 I_Tm=sqrt(2)*V_s/(2*Z);    printf("\nmax value of
   rms thyristor current=%f A",I_Tm);
16
17 f=50;
18 w=2*%pi*f;
19 di=sqrt(2)*V_s*w/Z;    printf("\ndi/dt=%f A/s",di)
   ;

```

Scilab code Exa 9.6 to calculate extinction angle and rms value of output voltage

```

1 clc
2 clear
3 V=230;
4 R=3; //ohm
5 X_L=5; //ohm
6 a=120; //firing angle delay
7 phi=atand(X_L/R);
8 b=0;
9 i=1;
10 while i>0;
11     LHS=sind(b-a);
12     RHS=sind(a-phi)*exp(-(R/X_L)*(b-a)*%pi/180);
13     if abs(LHS-RHS)<=.01;
14         B=b;
15         i=2;
16         break;

```

```

17      end
18      b=b+.1
19  end
20 printf(" extinction angle=%f deg",B); //answer in
     the book is wrong as formulae for RHS is wrongly
     employed
21 V_or=sqrt(2)*V*sqrt((1/(2*pi))*((B-a)*pi/180+(sind
     (2*a)-sind(2*B))/2));
22 printf("\nrms value of output voltage=%f V",V_or);
     //answer do not match due to wrong B in book

```

Scilab code Exa 9.8 to calculate 1 rms value of output voltage 2 rms value of curr

```

1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 a=60;
6 R=20;
7 V_or=sqrt((V_m^2/(2*pi))*(a*pi/180-sind(2*a)/2)
     +(2*V_m^2/(pi))*(pi-a*pi/180+sind(2*a)/2));
     printf("rms value of o/p voltage=%f V",V_or)
     ;
8 I_T1r=(V_m/R)*sqrt(1/pi*((pi-a*pi/180)+sind(2*a)
     /2));    printf("\nrms value of current for upper
     thyristors=%f A",I_T1r);
9 I_T3r=(V_m/(2*R))*sqrt(1/pi*((a*pi/180)-sind(2*a)
     /2));    printf("\nrms value of current for lower
     thyristors=%f A",I_T3r);
10 I1=sqrt(2)*I_T1r;
11 I3=sqrt((sqrt(2)*I_T1r)^2+(sqrt(2)*I_T3r)^2);
12 r=V_s*(I1+I3);    printf("\n\t/f VA rating=%f VA",r
     );
13 P_o=V_or^2/R;
14 pf=P_o/r;    printf("\ni/p pf=%f",pf);

```


Chapter 10

Cycloconverters

Scilab code Exa 10.2 to calculate 1 rms value of output voltage 2 rms current of each

```
1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 R=10;
6 a=30;
7 V_or=(V_m/sqrt(2))*sqrt((1/%pi)*(%pi-a*%pi/180+sind
    (2*a)/2));
8 I_or=V_or/R;      printf("rms value of o/p current=%.2
    f A",I_or);
9 printf("\nrms value of o/p current for each
    converter=%.2 f A",I_or/sqrt(2));
10 printf("\nrms value of o/p current for each
    thyristor=%.3 f A",I_or/2);
11 I_s=I_or;
12 pf=(I_or^2*R)/(V_s*I_s);      printf("\ni/p pf=%.4 f",
    pf);
```

Scilab code Exa 10.4 to compute 1 value of fundamental rms output voltage 2 rms ou

```

1 clear;
2 clc;
3 V_s=400;
4 V_ph=V_s/2;
5 a=160;
6 r=cosd(180-a);
7 m=3;
8 V_or=r*(V_ph*(m/%pi)*sin(%pi/m));      printf("rms o/p
    voltage=%.3f V",V_or);
9 R=2;
10 X_L=1.5;
11 th=atand(X_L/R);
12 Z=sqrt(R^2+X_L^2);
13 I_or=V_or/Z;      printf("\nrms o/p current=%.2f A",
    I_or);
14 printf("\nphase angle of o/p current=%.2f deg",-th)
15 P=I_or^2*R;      printf("\no/p power=%.2f W",P);

```

Scilab code Exa 10.5 to compute 1 value of fundamental rms output voltage 2 rms ou

```

1 clear;
2 clc;
3 V_s=400;
4 V_ph=V_s/2;
5 V_l=V_ph*sqrt(3);
6 a=160;
7 r=cosd(180-a);
8 m=6;
9 V_or=r*(V_l*(m/%pi)*sin(%pi/m));      printf("rms o/p
    voltage=% .2f V",V_or);
10 R=2;
11 X_L=1.5;
12 th=atand(X_L/R);
13 Z=sqrt(R^2+X_L^2);
14 I_or=V_or/Z;      printf("\nrms o/p current=%.2f A",
    I_or);

```

```
I_or);  
15 printf("\nphase angle of o/p current=%f deg", -th)  
16 P=I_or^2*R;      printf("\no/p power=%f W", P);
```

Scilab code Exa 10.7 to calculata rms value of load voltage for various firing ang

```
1 clear;  
2 clc;  
3 V_l=400;  
4 V_ml=sqrt(2)*V_l;  
5 m=6;  
6 f=50;  
7 w=2*pi*f;  
8 L=.0012;  
9 I=40;  
10 disp(" for firing angle=0deg");  
11 a=0;  
12 V_or=(V_ml*(m/pi)*sin(pi/m))*cosd(a);  
13 V_omx=V_or-3*w*L*I/pi;  
14 V_rms=V_omx/sqrt(2);      printf("rms value of load  
voltage=%f V", V_rms);  
15  
16 disp(" for firing angle=30deg");  
17 a=30;  
18 V_or=(V_ml*(m/pi)*sin(pi/m))*cosd(a);  
19 V_omx=V_or-3*w*L*I/pi;  
20 V_rms=V_omx/sqrt(2);      printf("rms value of load  
voltage=%f V", V_rms);
```

Chapter 11

Some Applications

Scilab code Exa 11.1 to calculate 1 firing angle of the rectifier 2 output voltage

```
1 clear;
2 clc;
3 V_s=11000;
4 V_ml=sqrt(2)*V_s;
5 f=50;
6 w=2*pi*f;
7 I_d=300;
8 R_d=1;
9 g=20; //g=gamma
10 a=acosd(cosd(g)+pi/(3*V_ml)*I_d*R_d);      printf("firing angle=%3.3f deg",a);
11 L_s=.01;
12 V_d=(3/%pi)*((V_ml*cosd(a))-w*L_s*I_d);      printf("\nrectifier o/p voltage=%1.1f V",V_d);
13 printf("\nDC link voltage=%3.3f V",2*V_d/1000);
```

Scilab code Exa 11.2 To calculate rms current and peak reverse voltage ratings for

```

1 clear;
2 clc;
3 V_d=(200+200)*10^3;
4 P=1000*10^6;
5 I_d=P/V_d;
6 //each thristor conducts for 120deg for a
   periodicity of 360deg
7 printf("rms current rating of thyristor=%f A",I_d*
       sqrt(120/360));
8 a=0;
9 V_d=200*10^3;
10 V_ml=V_d*%pi/(3*cosd(a));
11 printf("\npeak reverse voltage across each thyristor
      =%f kV",V_ml/2/1000);

```

Scilab code Exa 11.3 to determine voltage and current rating of 1 thyristor and 2

```

1 clear;
2 clc;
3 V_m=230;
4 V_s=230/sqrt(2);
5 pf=.8;
6 P=2000;
7 I_m=P/(V_s*pf);
8 I_Tr=I_m/sqrt(2);
9 I_TA=2*I_m/%pi;
10 fos=2;//factor of safety
11 printf("rms value of thyristor current=%f A",fos*
      I_Tr);
12 printf("\navg value of thyristor current=%f A",fos*
      *I_TA);
13 PIV=V_m*sqrt(2);
14 printf("\nvoltage rating of thyristor=%f V",PIV);
15
16 I_Tr=I_m/(2);

```

```

17 I_TA=I_m/%pi;
18 printf("\nrms value of diode current=%f A",fos*
    I_Tr);
19 printf("\navg value of diode current=%f A",fos*
    I_TA);
20 printf("\nvoltage rating of diode=%f V",PIV);

```

Scilab code Exa 11.4 to find the value of parameters of R2 C and load resistance

```

1 clear;
2 clc;
3 V=200;
4 I=10;
5 R_L=V/I;      printf(" value of load resistance=%f f
    ohm",R_L);
6 I_h=.005;      //holding current
7 R2=V/I_h;      printf("\nvalue of R2=%f kilo -ohm",R2
    /1000);
8 t_c=20*10^-6;
9 fos=2; //factor of safety
10 C=t_c*fos/(R_L*log(2));      printf("\nvalue of C=%f f
    uF",C*10^6);

```

Scilab code Exa 11.5 to calculate 1 depth of heat of penetration 2 heat generated

```

1 clear;
2 clc;
3 u_r=10;
4 f=10000; //Hz
5 p=4*10^-8; //ohm-m
6 dl=(1/(2*pi))*sqrt(p*10^7/(u_r*f));      printf(""
    depth of heat of penetration=%f mm",dl*1000);
7 l=.12; //length of cylinder

```

```

8 t=20; //no of turns
9 I=100;
10 H=t*I/l;
11 P_s=2*%pi*H^2*sqrt(u_r*f*p*10^-7); printf("\nheat
           generated per unit cylinder surface area=%f W/
           m^2",P_s);
12 d=.02; //diameter
13 P_v=4*H^2*p/(d*d); printf("\nheat generated per
           unit cylinder volume=%f W/m^3",P_v);
14 //answer of P_v varies as given in book as value of
           d is not taken as in formulae.

```

Scilab code Exa 11.6 to calculate reqd capacitor size

```

1 clear;
2 clc;
3 f=3000;
4 t_qmin=30*10^-6;
5 f_r=f/(1-2*t_qmin*f);
6 R=.06;
7 L=20*10^-6;
8 C=1/(L*((2*pi*f_r)^2+(R/(2*L))^2)); printf("
           required capacitor size=%f F",C*10^6);
9 //Answers have small variations from that in the
           book due to difference in the rounding off of
           digits .

```

Chapter 12

Electric Drives

Scilab code Exa 12.1 To determine 1 firing angle delay of armature converter 2 rms

```
1 clear;
2 clc;
3 T_e=15; //Nm
4 K_m=.5; //V-s / rad
5 I_a=T_e/K_m;
6 n_m=1000;
7 w_m=2*pi*n_m/60;
8 E_a=K_m*w_m;
9 r_a=.7;
10 V_t=E_a+I_a*r_a;
11 V_s=230;
12 V_m=sqrt(2)*V_s;
13 a=acosd(2*pi*V_t/V_m-1);      printf("firing angle
delay=%3f deg",a);
14 I_Tr=I_a*sqrt((180-a)/360);    printf("\nrms value
of thyristor current=%3f A",I_Tr);
15 I_fdr=I_a*sqrt((180+a)/360);    printf("\nrms value
of freewheeling diode current=%3f A",I_fdr);
16 pf=V_t*I_a/(V_s*I_Tr);        printf("\ninput power
factor=%3f",pf);
```

Scilab code Exa 12.2 calculate the avg armature current and the motor torque

```
1 clear;
2 clc;
3 V_m=330;
4 E_a=80;
5 r_a=4;
6 a=30;
7 I_a=((V_m/%pi*(1+cosd(a)))-E_a)/r_a;      printf("avg
           armature current=%f A",I_a);
8 n_s=1400;
9 w_m=2*%pi*n_s/60;
10 K_m=E_a/w_m;
11 T_e=K_m*I_a;      printf("\nmotor torque=%f Nm",T_e)
12 ;
```

Scilab code Exa 12.3 to determine 1 motor current 2 motor torque 3 input pf

```
1 clear;
2 clc;
3 V_s=250;
4 V_m=sqrt(2)*V_s;
5 a=30;
6 k=0.03; //Nm/A^2
7 n_m=1000;
8 w_m=2*%pi*n_m/60;
9 r=.2; // r_a+r_s
10 V_t=V_m/%pi*(1+cosd(a));
11 I_a=V_t/(k*w_m+r);      printf("motor armature current
           =%f A",I_a);
12 T_e=k*I_a^2;      printf("\nmotor torque=%f Nm",T_e)
13 ;
```

```

13 I_sr=I_a*sqrt((180-a)/180);
14 pf=(V_t*I_a)/(V_s*I_sr);      printf("\ninput power
    factor=%f",pf);

```

Scilab code Exa 12.4 to determine 1 rated armature current 2 firing angle delay of

```

1 clear;
2 clc;
3 V_s=400;
4 V_m=sqrt(2)*V_s;
5 V_f=2*V_m/%pi;
6 r_f=200;
7 I_f=V_f/r_f;
8 T_e=85;
9 K_a=.8;
10 I_a=T_e/(I_f*K_a);      printf(" rated armature current
    =%.2f A",I_a);
11 n_m=1200;
12 w_m=2*%pi*n_m/60;
13 r_a=.2;
14 V_t=K_a*I_f*w_m+I_a*r_a;
15 a=acosd(V_t*%pi/(2*V_m));      printf("\nfiring angle
    delay=%.2f deg",a);
16 E_a=V_t;
17 w_mo=E_a/(K_a*I_f);
18 N=60*w_mo/(2*%pi);
19 reg=((N-n_m)/n_m)*100;      printf("\nspeed regulation
    at full load=%.2f",reg);
20 I_ar=I_a;
21 pf=(V_t*I_a)/(V_s*I_ar);      printf("\ninput power
    factor of armature convertor=%f",pf);
22 I_fr=I_f;
23 I_sr=sqrt(I_fr^2+I_ar^2);
24 VA=I_sr*V_s;
25 P=V_t*I_a+V_f*I_f;

```

```
26 printf("\ninput power factor of drive=%f",P/VA);  
27 //Answers have small variations from that in the  
//book due to difference in the rounding off of  
//digits.
```

Scilab code Exa 12.5 to calculate 1 delay angle of field converter 2 delay angle of

```
1 clear;  
2 clc;  
3 V_s=400;  
4 V_m=sqrt(2)*V_s;  
5 V_f=2*V_m/pi;  
6 a1=acosd(-V_f*pi/(2*V_m)); printf(" delay angle  
of field converter=%f deg",a1);  
7 r_f=200;  
8 I_f=V_f/r_f;  
9 T_e=85;  
10 K_a=.8;  
11 I_a=T_e/(I_f*K_a);  
12 n_m=1200;  
13 w_m=2*pi*n_m/60;  
14 r_a=.1;  
15 I_a=50;  
16 V_t=-K_a*I_f*w_m+I_a*r_a;  
17 a=acosd(V_t*pi/(2*V_m)); printf("\nfiring angle  
delay of armature converter=%f deg",a);  
18 printf("\npower fed back to ac supply=%f W",-V_t*  
I_a);
```

Scilab code Exa 12.6 To compute 1 motor speed 2 torque developed

```
1 clear;  
2 clc;
```

```

3 V_t=220;
4 n_m=1500;
5 w_m=2*pi*n_m/60;
6 I_a=10;
7 r_a=1;
8 K_m=(V_t-I_a*r_a)/(w_m);
9 T=5;
10 I_a=T/K_m;
11 V_s=230;
12 V_m=sqrt(2)*V_s;
13 a=30;
14 V_t=2*V_m*cosd(a)/pi;
15 w_m=(V_t-I_a*r_a)/K_m;
16 N=w_m*60/(2*pi);      printf (" motor speed=%f rpm",N
);
17 a=45;
18 n_m=1000;
19 w_m=2*pi*n_m/60;
20 V_t=2*V_m*cosd(a)/pi;
21 I_a=(V_t-K_m*w_m)/r_a;
22 T_e=K_m*I_a;      printf ("\ntorque developed=%f Nm",T_e);
23 //Answers have small variations from that in the
book due to difference in the rounding off of
digits .

```

Scilab code Exa 12.7 to compute firing angle and motor speed

```

1 clear;
2 clc;
3 V_t=220;
4 n_m=1000;
5 w_m=2*pi*n_m/60;
6 I_a=60;
7 r_a=.1;

```

```

8 K_m=(V_t-I_a*r_a)/(w_m);
9 V_s=230;
10 V_m=sqrt(2)*V_s;
11 disp(" for 600rpm speed");
12 n_m=600;
13 w_m=2*pi*n_m/60;
14 a=acosd((K_m*w_m+I_a*r_a)*pi/(2*V_m));      printf(
15          firing angle=%.3f deg",a);
16 disp(" for -500rpm speed");
17 n_m=-500;
18 w_m=2*pi*n_m/60;
19 a=acosd((K_m*w_m+I_a*r_a)*pi/(2*V_m));      printf(
15          firing angle=%.3f deg",a);
20
21 I_a=I_a/2;
22 a=150;
23 V_t=2*V_m*cosd(a)/pi;
24 w_m=(V_t-I_a*r_a)/K_m;
25 N=w_m*60/(2*pi);      printf("\nmotor speed=%.3f rpm"
15 ,N);

```

Scilab code Exa 12.8 to calculate the speed of the motor

```

1 clear;
2 clc;
3 K_m=1.5;
4 T_e=50;
5 I_a=T_e/K_m;
6 r_a=0.9;
7 a=45;
8 V_s=415;
9 V_ml=sqrt(2)*V_s;
10 w_m=((3*V_ml*(1+cosd(a))/(2*pi))-I_a*r_a)/K_m;
11 N=w_m*60/(2*pi);      printf(" motor speed=%.2f rpm",N)

```

) ;

Scilab code Exa 12.9 to compute rms value of source and thyristor currents avg val

```
1 clear;
2 clc;
3 V_t=600;
4 n_m=1500;
5 w_m=2*pi*n_m/60;
6 I_a=80;
7 r_a=1;
8 K_m=(V_t-I_a*r_a)/(w_m);
9 V_s=400;
10 V_m=sqrt(2)*V_s;
11 disp(" for firing angle=45deg and speed=1200rpm");
12 a=45;
13 n_m=1200;
14 w_m=2*pi*n_m/60;
15 I_a=(3*V_m*(1+cosd(a))/(2*pi)-K_m*w_m)/r_a;
16 I_sr=I_a*sqrt(2/3); printf("rms value of source
current=%f A",I_sr);
17 printf("\nrms value of thyristor current=%f A",I_a
*sqrt(1/3));
18 printf("\navg value of thyristor current=%f A",I_a
*(1/3));
19 pf=(3/(2*pi)*(1+cosd(a))); printf("\ninput power
factor=%f",pf);
20
21 disp(" for firing angle=90deg and speed=700rpm");
22 a=90;
23 n_m=700;
24 w_m=2*pi*n_m/60;
25 I_a=(3*V_m*(1+cosd(a))/(2*pi)-K_m*w_m)/r_a;
26 I_sr=I_a*sqrt(90/180); printf("rms value of
source current=%f A",I_sr);
```

```

27 printf("\nrms value of thyristor current=%f A",I_a
    *sqrt(90/360));
28 printf("\navg value of thyristor current=%f A",I_a
    *(1/3));
29 pf=(sqrt(6)/(2*pi)*(1+cosd(a)))*sqrt(180/(180-a));
    printf("\ninput power factor=%f",pf);

```

Scilab code Exa 12.10 To find 1 no load speed 2 firing angle and supply pf 3 speed

```

1 clear;
2 clc;
3 V_s=400;
4 V_m=sqrt(2)*V_s;
5 a=30;
6 V_t=3*V_m*cosd(a)/pi;
7 I_a=21;
8 r_a=.1;
9 V_d=2;
10 K_m=1.6;
11 w_m=(V_t-I_a*r_a-V_d)/K_m;
12 N=w_m*60/(2*pi);      printf(" speed of motor=%f rpm
    ",N);
13
14 N=2000;
15 w_m=2*pi*N/60;
16 I_a=210;
17 V_t=K_m*w_m+I_a*r_a+V_d;
18 a=acosd(V_t*pi/(3*V_m));      printf("\nfiring angle=
    %.2f deg",a);
19 I_sr=I_a*sqrt(2/3);
20 pf=V_t*I_a/(sqrt(3)*V_s*I_sr);      printf("\nsupply
    power factor=%f",pf);
21
22 I_a=21;
23 w_m=(V_t-I_a*r_a-V_d)/K_m;

```

```
24 n=w_m*60/(2*pi);
25 reg=(n-N)/N*100;      printf("\nspeed regulation(
    percent )=% .2f",reg);
```

Scilab code Exa 12.11 to calculate 1 transformer phase turn ratio 2 firing angle d

```
1 clear;
2 clc;
3 V_t=230;
4 V_l=V_t*%pi/(3*sqrt(2));
5 V_ph=V_l/sqrt(3);
6 V_in=400; //per phase voltage input
7 printf("transformer phase turns ratio=% .3f",V_in/
    V_ph);
8
9 N=1500;
10 I_a=20;
11 r_a=.6;
12 disp("for motor running at 1000rpm at rated torque")
    ;
13 E_a1=V_t-I_a*r_a;
14 n=1000;
15 E_a=E_a1/1500*1000;
16 V_t=E_a+I_a*r_a;
17 a=acosd(V_t*%pi/(3*sqrt(2)*V_l));      printf("firing
    angle delay=% .2f deg",a);
18
19 disp("for motor running at -900rpm at half of rated
    torque");
20 I_a=.5*I_a;
21 n=-900;
22 V_t=n*E_a1/N+I_a*r_a;
23 a=acosd(V_t*%pi/(3*sqrt(2)*V_l));      printf("firing
    angle delay=% .3f deg",a);
```

Scilab code Exa 12.12 to calculate firing angle for different given conditions

```
1 clear;
2 clc;
3 V_s=400;
4 V_ml=sqrt(2)*V_s;
5 V_f=3*V_ml/%pi;
6 R_f=300;
7 I_f=V_f/R_f;
8 T_e=60;
9 k=1.1;
10 I_a=T_e/(k*I_f);
11 N=1000;
12 w_m=2*%pi*N/60;
13 r_a=.3;
14 V_t=k*I_f*w_m+I_a*r_a;
15 a=acosd(V_t*%pi/(3*V_ml));      printf("firing angle=%
.3 f deg",a);
16
17 N=3000;
18 w_m=2*%pi*N/60;
19 a=0;
20 V_t=3*V_ml*cosd(a)/%pi;
21 I_f=(V_t-I_a*r_a)/(w_m*k);
22 V_f=I_f*R_f;
23 a=acosd(V_f*%pi/(3*V_ml));      printf("\nfiring angle
=% .3 f deg",a);
```

Scilab code Exa 12.13 to evaluate the time taken for the speed to reach 1000rpm

```
1 clear;
2 clc;
```

```

3 // after calculating
4 // t=w_m/6000-%pi/360
5
6 N=1000;
7 w_m=2*%pi*N/60;
8 t=w_m/6000-%pi/360;      printf("time reqd=%f s",t);
9 // printing mistake in the answer in book

```

Scilab code Exa 12.14 to determine the 3rd and 5th harmonic components of line current

```

1 clear;
2 clc;
3 I_a=1; //supposition
4 a=60;
5 I_s1=2*sqrt(2)/%pi*I_a*sind(a);
6 I_s3=2*sqrt(2)/(3*%pi)*I_a*sind(3*a);
7 I_s5=2*sqrt(2)/(5*%pi)*I_a*sind(5*a);
8 per3=I_s3/I_s1*100;    printf("percent of 3rd
                           harmonic current in fundamental=%f",per3);
9 per5=I_s5/I_s1*100;    printf("\npercent of 5th
                           harmonic current in fundamental=%f",per5);

```

Scilab code Exa 12.15 to calculate 1 rms and avg value of thyristor current 2 pf of

```

1 clear;
2 clear;
3 clc;
4 I_a=60;
5 I_TA=I_a/3;      printf("avg thyristor current=%f A"
                           ,I_TA);
6 I_Tr=I_a/sqrt(3);      printf("\nrms thyristor current
                           =%f A",I_Tr);
7

```

```

8 V_s=400;
9 V_m=sqrt(2)*V_s;
10 I_sr=I_a*sqrt(2/3);
11 a=150;
12 V_t=3*V_m*cosd(a)/%pi;
13 pf=V_t*I_a/(sqrt(3)*V_s*I_sr);      printf("\npower
               factor of ac source=%f",pf);
14
15 r_a=0.5;
16 K_m=2.4;
17 w_m=(V_t-I_a*r_a)/K_m;
18 N=w_m*60/(2*%pi);      printf("\nspeed of motor=%f
               rpm",N);
19 //Answers have small variations from that in the
   book due to difference in the rounding off of
   digits.

```

Scilab code Exa 12.16 to determine 1 input power from source 2 input resistance of

```

1 clear;
2 clc;
3 I_a=300;
4 V_s=600;
5 a=.6;
6 V_t=a*V_s;
7 P=V_t*I_a;      printf("input power from source=%f
               kW",P/1000);
8 R_eq=V_s/(a*I_a);      printf("\nequivalent input
               resistance=%f ohm",R_eq);
9 k=.004;
10 R=.04+.06;
11 w_m=(a*V_s-I_a*R)/(k*I_a);
12 N=w_m*60/(2*%pi);      printf("\nmotor speed=%f rpm"
               ,N);
13 T_e=k*I_a^2;      printf("\nmotor torque=%f Nm",T_e)

```

;

Scilab code Exa 12.17 to calculate avg load current

```
1 clear;
2 clc;
3 T_on=10;
4 T_off=15;
5 a=T_on/(T_on+T_off);
6 V_s=230;
7 V_t=a*V_s;
8 r_a=3;
9 K_m=.5;
10 N=1500;
11 w_m=2*pi*N/60;
12 I_a=(V_t-K_m*w_m)/r_a;      printf(" motor load current
=%.3 f A",I_a);
```

Scilab code Exa 12.18 to determine 1 range of speed control 2 range of duty cycle

```
1 clear;
2 clc;
3 w_m=0;      printf(" lower limit of speed control=% .0 f
rpm",w_m);
4 I_a=25;
5 r_a=.2;
6 V_s=220;
7 K_m=0.08;
8 a=(K_m*w_m+I_a*r_a)/V_s;      printf("\nlower limit of
duty cycle=% .3 f",a);
9
10 a=1;      printf("\nupper limit of duty cycle=% .0 f",a)
;
```

```
11 w_m=(a*V_s-I_a*r_a)/K_m;      printf("\nupper limit of
    speed control=%.1f rpm",w_m);
```

Scilab code Exa 12.19 To calculate the min and max values of armature current and

```
1 clear;
2 clc;
3 clear
4 T_e=30;
5 K_m=1.5;
6 I_a=T_e/K_m;
7 N=1000;
8 w_m=2*pi*N/60;
9 E_a=K_m*w_m;
10 r_a=0;
11 V_t=E_a+I_a*r_a;
12 V_s=220;
13 a=V_t/V_s;
14 f=400;
15 T=1/f;
16 T_on=a*T;
17 T_off=T-T_on;
18 L=0.02;
19 di=(V_s-E_a)/L;      //di=di_a/dt, during on period
20 dii=(-E_a)/L;      //di=di_a/dt, during off period
21 //I_mx=I_mn+di*T_on;
22 //I_a=(I_mx+I_mn)/2;
23 //after solving
24 I_mx=22.808;      printf("maximum armature current=%.
    f A",I_mx);
25 I_mn=2*I_a-I_mx;      printf("\nminimum armature
    current=%.
    3 f A",I_mn);
26 printf("\narmature current extrusion=%.
    3 f A",I_mx-
    I_mn);
27 t=poly(0,'t');
```

```

28 i_a=addf('I_mn',mulf('t','di'));
29 printf("\narmature current expression during turn-on
");
30 disp(eval(i_a));
31 i_a=addf('I_mx',mulf('t','dii'));
32 printf("\narmature current expression during turn-
off");
33 disp(eval(i_a));

```

Scilab code Exa 12.21 to determine 1 power returned to the dc supply 2 equivalent

```

1 clear;
2 clc;
3 a=.6;
4 V_s=400;
5 V_t=(1-a)*V_s;
6 I_a=300;
7 P=V_t*I_a;      printf(" power returned=%.0 f kW" ,P
/1000);
8
9 r_a=.2;
10 K_m=1.2;
11 R_eq=(1-a)*V_s/I_a+r_a;      printf("\nequivalent load
resistance=% .4 f ohm" ,R_eq);
12
13 w_mn=I_a*r_a/K_m;
14 N=w_mn*60/(2*pi);      printf("\nmin braking speed=%
.2 f rpm" ,N);
15 w_mx=(V_s+I_a*r_a)/K_m;
16 N=w_mx*60/(2*pi);      printf("\nmax braking speed=%
.1 f rpm" ,N);
17
18 w_m=(V_t+I_a*r_a)/K_m;
19 N=w_m*60/(2*pi);      printf("\nmax braking speed=% .1
f rpm" ,N);

```

Scilab code Exa 12.22 to determine max current in terms of rated currents at given

```
1 clear;
2 clc;
3 N=1500;
4 disp("when speed=1455rpm");
5 n=1455;
6 s1=(N-n)/N;
7 r=sqrt(1/3)*(2/3)/(sqrt(s1)*(1-s1));      printf(
     I_2mx/I_2r=% .3f",r);
8
9 disp("when speed=1350rpm");
10 n=1350;
11 s1=(N-n)/N;
12 r=sqrt(1/3)*(2/3)/(sqrt(s1)*(1-s1));      printf(
     I_2mx/I_2r=% .3f",r);
```

Scilab code Exa 12.23 to calculate 1 motor speed at rated load 2 slip at which max

```
1 clear;
2 clc;
3 Po=20000;
4 N=1440;
5 w_m=2*pi*N/60;
6 T_e=Po/w_m;
7 f1=120;
8 P=4;
9 w_s=4*pi*f1/P;
10 r2=.4;
11 x2=1.6;
12 f2=50;
```

```

13 Z1=r2+%i*x2*f1/f2;
14 Z=abs(Z1);
15 ph=3;
16 V_s=400;
17 s=(ph/w_s)*(V_s/(Z*sqrt(3)))^2*(r2/T_e);
18 N=w_s*f1/(4*pi)*(1-s); printf(" motor speed at
    rated load=%f rpm",N);
19 s_m=r2/imag(Z1); printf("\nslip at which max
    torque occurs=%f",s_m);
20 T_em=(3/w_s)*(V_s/sqrt(3))^2/(2*imag(Z1)); printf
    ("max torque=%f Nm",T_em);

```

Scilab code Exa 12.24 To calculate 1 current and pf at the instant of starting and

```

1 clear;
2 clc;
3 V1=400;
4 r1=.6;
5 r2=.4;
6 s=1;
7 x1=1.6;
8 x2=1.6;
9 disp("at starting in normal conditions");
10 I_n=V1/sqrt((r1+r2/s)^2+(x1+x2)^2); printf(
    "current=%f A",I_n);
11 pf=(r1+r2)/sqrt((r1+r2/s)^2+(x1+x2)^2); printf(
    "pf=%f",pf);
12 f1=50;
13 w_s=4*pi*f1/4;
14 T_en=(3/w_s)*I_n^2*(r2/s); printf("\nTorque
    developed=%f Nm",T_en);
15 disp("motor is operated with DOL starting");
16 I_d=V1/2/sqrt((r1+r2/s)^2+((x1+x2)/2)^2); printf(
    "current=%f A",I_d);
17 pf=(r1+r2)/sqrt((r1+r2/s)^2+((x1+x2)/2)^2);

```

```

        printf("\n pf=%f", pf);
18 f1=25;
19 w_s=4*pi*f1/4;
20 T_ed=(3/w_s)*I_d^2*(r2/s);      printf("\nTorque
    developed=%f Nm", T_ed);
21
22 disp("at max torque conditions");
23 s_mn=r2/sqrt((r1)^2+((x1+x2))^2);
24 I_n=V1/sqrt((r1+r2/s_mn)^2+(x1+x2)^2);      printf(
    current=%f A", I_n);
25 pf=(r1+r2/s_mn)/sqrt((r1+r2/s_mn)^2+(x1+x2)^2);
    printf("\n pf=%f", pf);
26 f1=50;
27 w_s=4*pi*f1/4;
28 T_en=(3/w_s)*I_n^2*(r2/s_mn);      printf("\nTorque
    developed=%f Nm", T_en);
29 disp("motor is operated with DOL starting");
30 s_mn=r2/sqrt((r1)^2+((x1+x2)/2)^2);
31 I_d=V1/2/sqrt((r1+r2/s_mn)^2+((x1+x2)/2)^2);
    printf("current=%f A", I_d);
32 pf=(r1+r2/s_mn)/sqrt((r1+r2/s_mn)^2+((x1+x2)/2)^2);
    printf("\n pf=%f", pf);
33 f1=25;
34 w_s=4*pi*f1/4;
35 T_en=(3/w_s)*I_d^2*(r2/s_mn);      printf("\nTorque
    developed=%f Nm", T_en);

```

Scilab code Exa 12.25 calculate 1 slip for max torque 2 starting and max torques 3

```

1 clear;
2 clc;
3 x1=1;
4 X_m=50;
5 X_e=x1*X_m/(x1+X_m);
6 V=231;

```

```

7 V_e=V*X_m/(x1+X_m);
8 x2=1;
9 r2=.4;
10 r1=0;
11 s_m=r2/(x2+X_e);      printf(" slip at max torque=%f"
   ,s_m);
12 s_mt=r2/(x2+X_m);      printf("\nslip at max torque=%
   .5f",s_mt);
13 f1=50;
14 w_s=4*pi*f1/4;
15 disp(" for constant voltage input");
16 T_est=(3/w_s)*(V_e/sqrt(r2^2+(x2+X_e)^2))^2*(r2);
   printf(" starting torque=%f Nm",T_est);
17 T_em=(3/w_s)*V_e^2/(2*(x2+X_e));      printf("\n
   maximum torque developed=%f Nm",T_em);
18 disp(" for constant current input");
19 I1=28;
20 T_est=(3/w_s)*(I1*X_m)^2/(r2^2+(x2+X_m)^2)*r2;
   printf(" starting torque=%f Nm",T_est);
21 T_em=(3/w_s)*(I1*X_m)^2/(2*(x2+X_m));      printf("\n
   maximum torque developed=%f Nm",T_em);
22 s=s_mt;
23 I_m=I1*(r2/s+i*x2)/(r2/s+i*(x2+X_m));
24 I_m=abs(I_m);
25 V1=sqrt(3)*I_m*X_m;      printf("\nsupply voltage reqd
   =%f V",V1);

```

Scilab code Exa 12.27 to calculate 1 the value of chopper resistance R 2 inductor

```

1 clear;
2 clc;
3 V=420;
4 V1=V/sqrt(3);
5 T_e=450;
6 N=1440;

```

```

7 n=1000;
8 T_L=T_e*(n/N)^2;
9 n1=1500;
10 w_s=2*pi*n1/60;
11 w_m=2*pi*n/60;
12 a=.8;
13 I_d=T_L*w_s/(2.339*a*V1);
14 k=0;
15 R=(1-w_m/w_s)*(2.339*a*V1)/(I_d*(1-k));      printf (""
               value of chopper resistance=% .4f ohm",R);
16
17 n=1320;
18 T_L=T_e*(n/N)^2;
19 I_d=T_L*w_s/(2.339*a*V1);      printf ("\ninductor
               current=% .3f A",I_d);
20
21 w_m=2*pi*n/60;
22 k=1-((1-w_m/w_s)*(2.339*a*V1)/(I_d*R));      printf ("\"
               nvalue of duty cycle=% .4f",k);
23
24 s=(n1-n)/n1;
25 V_d=2.339*s*a*V1;      printf ("\nrectified o/p voltage=
               % .3f V",V_d);
26
27 P=V_d*I_d;
28 I2=sqrt(2/3)*I_d;
29 r2=0.02;
30 Pr=3*I2^2*r2;
31 I1=a*I2;
32 r1=0.015;
33 Ps=3*I1^2*r1;
34 Po=T_L*w_m;
35 Pi=Po+Ps+Pr+P;
36 eff=Po/Pi*100;      printf ("\nefficiency (in percent)=%
               .2f",eff);

```

Scilab code Exa 12.28 To calculate 1 value of chopper duty cycle 2 efficiency for

```
1 clear;
2 clc;
3 V=400;
4 V_ph=V/sqrt(3);
5 N_s=1000;
6 N=800;
7 a=.7;
8 I_d=110;
9 R=2;
10 k=1-((1-N/N_s)*(2.339*a*V_ph)/(I_d*R));      printf("value of duty cycle=%f",k);
11 P=I_d^2*R*(1-k);
12 I1=a*I_d*sqrt(2/3);
13 r1=.1;
14 r2=.08;
15 Pr=3*I1^2*(r1+r2);
16 P_o=20000;
17 P_i=P_o+Pr+P;
18 eff=P_o/P_i*100;      printf("\n efficiency=%f",eff);
19
20 I11=sqrt(6)/pi*a*I_d
21 th=43;
22 P_ip=sqrt(3)*V*I11*cosd(th);
23 pf=P_ip/(sqrt(3)*V*I11);      printf("\n input power
factor=%f",pf);
```

Scilab code Exa 12.29 to calculate 1 rotor rectified voltage 2 inductor angle 3 de

```
1 clear;
2 clc;
```

```

3 V=420;
4 V1=V/sqrt(3);
5 N=1000;
6 w_m=2*pi*N/60;
7 N_s=1500;
8 s=(N_s-N)/N_s;
9 a=.8;
10 V_d=2.339*a*s*V1;      printf(" rectified voltage=%f
                                V", V_d);
11 T=450;
12 N1=1200;
13 T_L=T*(N/N1)^2;
14 f1=50;
15 w_s=4*pi*f1/4;
16 I_d=w_s*T_L/(2.339*a*V1);      printf("\ninductor
                                current=%f A", I_d);
17 a_T=-.4;
18 a1=acosd(s*a/a_T);      printf("\ndelay angle of
                                inverter=%f deg", a1);
19
20 P_s=V_d*I_d;
21 P_o=T_L*w_m;
22 R_d=0.01;
23 P_i=I_d^2*R_d;
24 I2=sqrt(2/3)*I_d;
25 r2=0.02;
26 r1=0.015;
27 P_rol=3*I2^2*r2;
28 I1=a*I2;
29 P_sol=3*I1^2*r1;
30 P_i=P_o+P_rol+P_sol+P_i;
31 eff=P_o/P_i*100;      printf("\nefficiency=%f", eff);
32 w_m=w_s*(1+(-a_T/a)*cosd(a1)-w_s*R_d*T_L/(2.339*a*V1
                                )^2);
33 N=w_m*60/(2*pi);      printf("\nmotor speed=%f rpm"
                                , N);
34 //Answers have small variations from that in the
   book due to difference in the rounding off of

```

digits .

Scilab code Exa 12.30 to find firing angle advance of inveter

```
1 clear;
2 clc;
3 V=700;
4 E2=V/sqrt(3);
5 N_s=1500;
6 N=1200;
7 s=(N_s-N)/N_s;
8 V_dd=.7;
9 V_dt=1.5;
10 V_d=3*sqrt(6)*s*E2/%pi-2*V_dd;
11 V1=415;
12 a=acosd((3*sqrt(2)*E2/%pi)^-1*(-V_d+2*V_dt));
13 printf("firing angle advance=%.2 f deg",180-a);
```

Scilab code Exa 12.31 to find firing angle advance of inveter

```
1 clear;
2 clc;
3 V=700;
4 E2=V/sqrt(3);
5 N_s=1500;
6 N=1200;
7 s=(N_s-N)/N_s;
8 V_dd=.7;
9 V_dt=1.5;
10 a=0;
11 u=18; //overlap angle in case of rectifier
12 V_d=3*sqrt(6)*s*E2*(cosd(a)+cosd(a+u))/(2*%pi)-2*
V_dd;
```

```

13
14 V1=415;
15 V_ml=sqrt(2)*V1;
16 u=4; //overlap angle in the inverter
17 //V_dc=-(3*V_ml*(cosd(a)+cosd(a+u))/(2*pi)-2*V_dt);
18 //V_dc=V_d;
19 //after solving , (1+cosd(u))*cosd(a)-sind(u)*sind(a)
//           )=-.6425
20 a=acosd(-.6425/(sqrt((1+cosd(u))^2+sind(u)^2))-
atand(sind(u)/(1+cosd(u)));
21 printf("firing angle advance=%f deg",180-a);

```

Scilab code Exa 12.32 to find the voltage ratio of the transformer

```

1 clear;
2 clc;
3 V=700;
4 E2=V;
5 N_s=1500;
6 N=1200;
7 s=(N_s-N)/N_s;
8 V1=415;
9 a_T=s*E2/V1;      printf("voltage ratio of the
transformer=%f",a_T);

```

Scilab code Exa 12.33 to calculate 1 supply voltage 2 armature current 3 excitatio

```

1 clear;
2 clc;
3 P=6;
4 N_s=600;
5 f1=P*N_s/120;
6 V=400;

```

```

7 f=50;
8 V_t=f1*V/f;      printf(" supply freq=%f Hz",V_t);
9 T=340;
10 N=1000;
11 T_L=T*(N_s/N)^2;
12 w_s=2*pi*N_s/60;
13 P=T_L*w_s;
14 I_a=P/(sqrt(3)*V_t);    printf("\narmature current=%
.2f A",I_a);
15 Z_s=%i*2;
16 X_s=f1/f*abs(Z_s);
17 V_t=V_t/sqrt(3);
18 Ef=sqrt(V_t^2+(I_a*X_s)^2);
19 printf("\nexcitation voltage=%f V",sqrt(3)*Ef);
20 d1=atand(I_a*X_s/V_t);   printf("\nload angle=%f
deg",d1);
21 T_em=(3/w_s)*(Ef*V_t/X_s);   printf("\npull out
torque=%f Nm",T_em);

```

Scilab code Exa 12.34 to calculate 1 load angle 2 line current 3 input pf

```

1 clear;
2 clc;
3 P=4;
4 f=50;
5 w_s=4*pi*f/P;
6 X_d=8;
7 X_q=2;
8 T_e=80;
9 V=400;
10 V_t=V/sqrt(3);
11 d1=(1/2)*asind(T_e*w_s/((3/2)*(V_t)^2*(1/X_q-1/X_d)))
);      printf("load angle=%f deg",d1);
12 I_d=V_t*cosd(d1)/X_d;
13 I_q=V_t*sind(d1)/X_q;

```

```
14 I_a=sqrt(I_d^2+I_q^2);      printf("\narmature current  
=%f A",I_a);  
15 pf=T_e*w_s/(sqrt(3)*V*I_a);    printf("\ninput power  
factor=%f",pf);
```

Scilab code Exa 12.35 To calculate motor speed

```
1 clear;  
2 clc;  
3 T_e=3;  
4 K_m=1.2;  
5 I_a=T_e/K_m;  
6 r_a=2;  
7 V=230;  
8 E_a=(.263*sqrt(2)*V-I_a*r_a)/(1-55/180);  
9 w_m=E_a/K_m;  
10 N=w_m*60/(2*pi);      printf("motor speed=%f rpm",N  
);
```

Scilab code Exa 12.36 to calculate avg motor torque

```
1 clear;  
2 clc;  
3 K_m=1;  
4 N=1360;  
5 w_m=2*pi*N/60;  
6 E_a=K_m*w_m;  
7 // after calculations V_t, calculated  
8 V_t=163.45;  
9 r_a=4;  
10 I_a=(V_t-E_a)/r_a;  
11 T_e=K_m*I_a;      printf("motor torque=%f Nm",T_e);
```

Scilab code Exa 12.37 to calculate avg motor torque

```
1 clear;
2 clc;
3 K_m=1;
4 N=2100;
5 w_m=2*pi*N/60;
6 E_a=K_m*w_m;
7 // after calculations V_t , calculated
8 V_t=227.66;
9 r_a=4;
10 I_a=(V_t-E_a)/r_a;
11 T_e=K_m*I_a;      printf("motor torque=%f Nm",T_e);
```

Scilab code Exa 12.38 to calculate avg motor torque

```
1 clear;
2 clc;
3 K_m=1;
4 N=840;
5 w_m=2*pi*N/60;
6 E_a=K_m*w_m;
7 V=230;
8 a=75;
9 V_t=sqrt(2)*V/pi*(1+cosd(a));
10 r_a=4;
11 I_a=(V_t-E_a)/r_a;
12 T_e=K_m*I_a;      printf("motor torque=%f Nm",T_e);
13 // Answers have small variations from that in the
   book due to difference in the rounding off of
   digits.
```

Scilab code Exa 12.39 to calculate avg motor torque

```
1 clear;
2 clc;
3 K_m=1;
4 N=1400;
5 w_m=2*pi*N/60;
6 E_a=K_m*w_m;
7 V=230;
8 a=60;
9 a1=212;
10 V_t=sqrt(2)*V/%pi*(cosd(a)-cosd(a1))+E_a*(180+a-a1)
    /180;
11 r_a=3;
12 I_a=(V_t-E_a)/r_a;
13 T_e=K_m*I_a;      printf ("motor torque=%f Nm",T_e);
```

Scilab code Exa 12.40 to calculate avg motor torque

```
1 clear;
2 clc;
3 K_m=1;
4 N=600;
5 w_m=2*pi*N/60;
6 E_a=K_m*w_m;
7 V=230;
8 a=60;
9 V_t=2*sqrt(2)*V/%pi*cosd(a));
10 r_a=3;
11 I_a=(V_t-E_a)/r_a;
12 T_e=K_m*I_a;      printf ("motor torque=%f Nm",T_e);
```

Scilab code Exa 12.41 to calculate the value of load current and source current

```
1 clear;
2 clc;
3 r1=.6;
4 r2=.4;
5 s=0.04;
6 x1=1.6;
7 x2=1.6;
8 Z=(r1+r2/s)+%i*(x1+x2);
9 V=400;
10 I1=V/Z;      printf(" source current=%f A and with %
.1 f deg phase",atand(imag(I1)/real(I1)),abs(I1));
11 I2=V/Z;
12 N=1500;
13 w_s=2*%pi*N/60;
14 T_e=(3/w_s)*abs(I2)^2*r2/s;      printf("\nmotor
torque=%f Nm",T_e);
15 N_r=N*(1-s);
16
17 f=45;
18 N_s1=120*f/4;
19 w_s=2*%pi*N_s1/60;
20 s1=(N_s1-N_r)/N_s1;
21 Z=(r1+r2/s1)+%i*(x1+x2)*f/50;
22 V=360;
23 I1=V/Z;      printf("\nsource current=%f A and with %
.1 f deg phase",atand(imag(I1)/real(I1)),abs(I1))
;
24 I2=V/Z;
25 T_e=(3/w_s)*abs(I2)^2*r2/s1;      printf("\nmotor
torque=%f Nm",T_e);
```

Chapter 13

Power Factor Improvement

Scilab code Exa 13.1 To calculate load voltage voltage regulation system utilisation

```
1 clear;
2 clc;
3 V_s=250;
4 R_l=5;
5 I_l=20;
6 disp(" for pf=1");
7 V_l=sqrt(V_s^2-(R_l*I_l)^2);      printf(" load voltage
    =%.2 f V",V_l);
8 reg=(V_s-V_l)/V_s*100;      printf("\n voltage
    regulation=% .2 f",reg);
9 pf=1;
10 P_l=V_l*I_l*pf;      //load power
11 P_r=V_s*I_l*pf;      //max powwible system rating
12 utf=P_l*100/P_r;      printf("\nsystem utilisation
    factor=% .3 f",utf);
13 printf("\nenergy consumed(in units)=%.1 f",P_l/1000);
14 disp(" for pf=.5");
15 pf=.5;
16 //(.5*V_l)^2+ (.866*V_l+R_l*I_l)^2=V_s^2
17 //after solving
18 V_l=158.35;      printf(" load voltage=% .2 f V",V_l);
```

```

19 reg=(V_s-V_1)/V_s*100;      printf ("\n voltage
   regulation=% .2f",reg);
20 P_l=V_1*I_1*pf;           //load power
21 P_r=V_s*I_1;              //max powwible system rating
22 utf=P_l*100/P_r;          printf ("\n system utilisation
   factor=% .3f",utf);
23 printf ("\n energy consumed (in units)=% .2f",P_l/1000);

```

Scilab code Exa 13.2 to calculate the capacitance reqd

```

1 clear;
2 clc;
3 f=50;
4 V_s=230;
5 disp("at no load");
6 I_m=2;
7 pf=.3;
8 I_c=I_m*sind(acosd(pf));
9 C=I_c/(2*pi*f*V_s);      printf (" value of capacitance
   =% .3f uF",C*10^6);
10 disp("at half full load");
11 I_m=5;
12 pf=.5;
13 I_c=I_m*sind(acosd(pf));
14 C=I_c/(2*pi*f*V_s);      printf (" value of capacitance
   =% .3f uF",C*10^6);
15 disp("at full load");
16 I_m=10;
17 pf=.7;
18 I_c=I_m*sind(acosd(pf));
19 C=I_c/(2*pi*f*V_s);      printf (" value of capacitance
   =% .3f uF",C*10^6);

```

Scilab code Exa 13.3 to find reqd values of capacitor and inductor

```
1 clear;
2 clc;
3 I_c=10;
4 f=50;
5 V_s=230;
6 C=I_c/(2*%pi*f*V_s);      printf(" value of capacitance
=%.3f uF",C*10^6);
7 I_l=10;
8 L=V_s/(2*%pi*f*I_l);      printf("\n value of inductor=
%.3f mH",L*1000);
```

Scilab code Exa 13.4 to find the firing angle of the TCR

```
1 clc
2 clear
3 V_s=230;
4 I_L=10;
5 X_L=V_s/I_L;
6 I_f1=6;
7 //B=2*a-sin(2*a)
8 B=2*%pi-I_f1*%pi*X_L/V_s;
9 a=0;
10 i=1;
11 for a= 0:.01:360
12     b=2*a*%pi/180-sind(2*a);
13     if abs(B-b)<=.001;           //by hit and trial
14         i=2;
15         break;
16     end
17 end
18 printf(" firing angle of TCR = %.1f deg",a);
19 // (a-.01)*180/%pi);
```

Scilab code Exa 13.5 to calculate the effective inductance at different firing angles

```
1 clear;
2 clc;
3 L=.01;
4 disp(" for firing angle=90deg");
5 a=90*%pi/180;
6 L_eff=%pi*L/(2*%pi-2*a+sin(2*a)); printf(" effective inductance=%.0 f mH",L_eff*1000);
7 disp(" for firing angle=120deg");
8 a=120*%pi/180;
9 L_eff=%pi*L/(2*%pi-2*a+sin(2*a)); printf(" effective inductance=%.3 f mH",L_eff*1000);
10 disp(" for firing angle=150deg");
11 a=150*%pi/180;
12 L_eff=%pi*L/(2*%pi-2*a+sin(2*a)); printf(" effective inductance=%.2 f mH",L_eff*1000);
13 disp(" for firing angle=170deg");
14 a=170*%pi/180;
15 L_eff=%pi*L/(2*%pi-2*a+sin(2*a)); printf(" effective inductance=%.3 f H",L_eff);
16 disp(" for firing angle=175deg");
17 a=175*%pi/180;
18 L_eff=%pi*L/(2*%pi-2*a+sin(2*a)); printf(" effective inductance=%.2 f H",L_eff);
19 disp(" for firing angle=180deg");
20 a=180*%pi/180;
21 L_eff=%pi*L/(2*%pi-2*a+sin(2*a)); printf(" effective inductance=%.3 f H",L_eff);
22 //random value at firing angle =180 is equivalent to infinity as in answer in book
```

Scilab code Exa 13.6 to find value of inductance

```
1 clear;
2 clc;
3 Q=100*10^3;
4 V_s=11*10^3;
5 f=50;
6 L=V_s^2/(2*pi*f*Q);      printf(" effective inductance
=%.4 f H",L);
```

Chapter 14

Miscellaneous Topics

Scilab code Exa 14.1 to calculate dc output voltage rms value of output voltage DF

```
1 clear;
2 clc;
3 V_s=230;
4 V_m=sqrt(2)*V_s;
5 a1=0;
6 a2=45;
7 printf("for two single phase series semiconvertors")
     ;
8 V_0=V_m/%pi*(2+cosd(a1)+cosd(a2));      printf("\navg
     o/p voltage=% .2f V",V_0);
9 V_or=V_s*sqrt((1/%pi)*(4*%pi-3*a2*pi/180+(3/2)*sind
     (2*a2)));      printf("\nrms value of o/p voltage=%
     .2f V",V_or);
10 DF=(3+cosd(a2))/(sqrt(2)*sqrt(5+3*cosd(a2)));
    printf("\nDF=% .4f",DF);
11 PF=sqrt(2/%pi)*(3+cosd(a2))/sqrt(4*%pi-3*a2*pi/180)
    ;      printf("\nPF=% .5f",PF);
12 HF=sqrt((%pi*(%pi-(3/4)*a2*pi/180)/(5+3*cosd(a2)))
    -1);      printf("\nHF=% .5f",HF);
13
14 printf("\n\nfor two single phase series full
```

```

        converters") ;
15 a=45 ;
16 V_0=2*V_m/%pi*(1+cosd(a)) ;      printf ("\navg o/p
voltage=% .2f V" ,V_0) ;
17 V_or=2*V_s*sqrt ((1/%pi)*(%pi-a2*pi/180+(1/2)*sind
(2*a2))) ;      printf ("\nrms value of o/p voltage=%
.2f V" ,V_or) ;
18 DF=cosd(a2/2) ;      printf ("\nDF=% .4f" ,DF) ;
19 PF=sqrt (2/(%pi*(%pi-a2*pi/180)))*(1+cosd(a2)) ;
printf ("\nPF=% .4f" ,PF) ;
20 HF=sqrt ((%pi*(%pi-a2*pi/180)/(4+4*cosd(a2)))-1) ;
printf ("\nHF=% .2f" ,HF) ;

```
