

Scilab Textbook Companion for  
Linear Integrated Circuits  
by S. Salivahanan And V. S. K. Bhaaskaran<sup>1</sup>

Created by  
Laxman Ghanasham Sole  
B.Tech.  
Electronics Engineering  
Vishwakarma Institute of Technology, Pune  
College Teacher  
Prof. Vijay Mane  
Cross-Checked by  
Lavitha Pereira

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Linear Integrated Circuits

**Author:** S. Salivahanan And V. S. K. Bhaaskaran

**Publisher:** Tata McGraw - Hill Education, New Delhi

**Edition:** 1

**Year:** 2008

**ISBN:** 0-07-064818-2

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 Integrated Circuit Fabrication</b>	<b>5</b>
<b>2 Circuit Configurations for Linear ICs</b>	<b>7</b>
<b>3 Operational Amplifier Characteristics</b>	<b>15</b>
<b>4 Applications of Operational Amplifiers</b>	<b>31</b>
<b>5 Operational Amplifier Nonlinear Circuits</b>	<b>38</b>
<b>6 Active Filters</b>	<b>41</b>
<b>7 Waveform Generators</b>	<b>50</b>
<b>8 Voltage Regulators</b>	<b>56</b>
<b>9 Analog Multipliers</b>	<b>63</b>
<b>10 Phase Locked Loop</b>	<b>64</b>
<b>11 DAC and ADC</b>	<b>69</b>

# List of Scilab Codes

Exa 1.1	sheet resistance of Ptype diffusion . . . . .	5
Exa 1.2	sheet resistance of polysilicon layer . . . . .	5
Exa 2.1	current source to provide output current . . . . .	7
Exa 2.2	identical transistor circuit . . . . .	7
Exa 2.3	output current of transistor . . . . .	8
Exa 2.4	resistance required to produce a current . . . . .	9
Exa 2.5	multiple current source . . . . .	9
Exa 2.6	design current source using MOSFET . . . . .	10
Exa 2.7	differential amplifier CMRR . . . . .	11
Exa 2.8	Qpoint of differential amplifier . . . . .	12
Exa 2.9	Qpoint for MOSFET of differential amplifier	13
Exa 3.1	input stage with bias circuit . . . . .	15
Exa 3.2	gain stage of Opamp . . . . .	15
Exa 3.3	output stage of opamp . . . . .	16
Exa 3.4	average bias current . . . . .	17
Exa 3.5	maximum output offset voltage . . . . .	17
Exa 3.6	bias current compensation . . . . .	18
Exa 3.7	Opamp drift specification . . . . .	18
Exa 3.8	frequency response . . . . .	19
Exa 3.9	unity gain bandwidth . . . . .	19
Exa 3.10	open loop dc voltage gain . . . . .	20
Exa 3.11	time taken to change output . . . . .	20
Exa 3.12	undistorted sine wave . . . . .	20
Exa 3.13	max input signal for undistorted output . . . . .	21
Exa 3.14	amplify square wave with rise time . . . . .	21
Exa 3.15	effect of output voltage change on slew rate	22
Exa 3.16	max input frequency for undistorted output	22
Exa 3.17	max input voltage for undistorted output . . . . .	23

Exa 3.18	noise gain of circuit . . . . .	23
Exa 3.19	closed loop voltage gain . . . . .	23
Exa 3.20	closed loop voltage gain and beta . . . . .	24
Exa 3.21	noninverting amplifier circuit . . . . .	24
Exa 3.22	noninverting amplifier with IL . . . . .	25
Exa 3.23	capacitor coupled voltage follower . . . . .	25
Exa 3.24	high impedance capacitor coupled voltage follower . . . . .	26
Exa 3.25	high impedance capacitor coupled noninverting amplifier . . . . .	27
Exa 3.26	capacitor coupled inverting amplifier . . . . .	27
Exa 3.27	capacitor coupled noninverting amplifier . . . . .	28
Exa 3.28	common mode gain $A_{cm}$ . . . . .	29
Exa 3.29	differential amplifier with two opamp . . . . .	30
Exa 4.1	phase lag circuit . . . . .	31
Exa 4.2	output current . . . . .	32
Exa 4.3	determine the current . . . . .	32
Exa 4.4	determine the current through $RL$ . . . . .	32
Exa 4.5	determine load gain . . . . .	33
Exa 4.6	voltage to current converter with floating load	33
Exa 4.7	summing amplifier . . . . .	34
Exa 4.8	input impedance . . . . .	35
Exa 4.9	practical integrator circuit . . . . .	35
Exa 4.10	design a differentiator . . . . .	36
Exa 4.11	design a differentiator using opamp . . . . .	36
Exa 4.12	solving differential equation using opamp . . . . .	37
Exa 4.13	transfer function using opamp . . . . .	37
Exa 5.1	transfer characteristics of comparator . . . . .	38
Exa 5.2	inverting schmitt trigger . . . . .	38
Exa 5.3	clipper circuit . . . . .	39
Exa 5.4	negative clamping circuit . . . . .	40
Exa 6.1	first order low pass butterworth filter . . . . .	41
Exa 6.2	first order low pass filter . . . . .	41
Exa 6.3	second order low pass butterworth filter . . . . .	42
Exa 6.4	second order low pass butterworth filter with uppercutoff frequency . . . . .	42
Exa 6.5	third order low pass butterworth filter . . . . .	43
Exa 6.6	fourth order low pass butterworth filter . . . . .	44

Exa 6.7	first order high pass filter . . . . .	44
Exa 6.8	second order high pass butterworth filter variable gain . . . . .	45
Exa 6.9	fourth order high pass butterworth filter . .	45
Exa 6.10	bandpass filter . . . . .	46
Exa 6.11	bandpass filter with resonant frequency . .	47
Exa 6.12	narrowband bandpass filter . . . . .	47
Exa 6.13	narrowband bandpass filter with resonant frequency . . . . .	48
Exa 6.14	clock frequency . . . . .	48
Exa 7.1	RC Phase shift oscillator . . . . .	50
Exa 7.2	Wien bridge oscillator . . . . .	50
Exa 7.3	Astable multivibrator . . . . .	51
Exa 7.4	Square wave oscillator . . . . .	52
Exa 7.5	Triangular wave generator . . . . .	52
Exa 7.6	Sawtooth wave generator . . . . .	53
Exa 7.7	Monostable multivibrator . . . . .	54
Exa 7.8	Frequency of oscillation . . . . .	54
Exa 7.9	Astable multivibrator . . . . .	55
Exa 7.10	Teletypewriter . . . . .	55
Exa 8.1	Linear Voltage Regulator . . . . .	56
Exa 8.2	7805 Voltage Regulator . . . . .	57
Exa 8.3	7805 Regulator Circuit . . . . .	58
Exa 8.4	LM317 Regulator . . . . .	58
Exa 8.5	Voltage regulator using LM317 . . . . .	59
Exa 8.6	Current Limiting Circuit . . . . .	60
Exa 8.7	LM723 Regulator . . . . .	60
Exa 8.8	Continuously adjustable power supply . . . .	61
Exa 9.1	DC Component . . . . .	63
Exa 10.1	DC Control voltage . . . . .	64
Exa 10.2	VCO Circuit . . . . .	64
Exa 10.3	PLL565 . . . . .	65
Exa 10.4	IC565 . . . . .	66
Exa 10.5	IC565 Output frequency . . . . .	67
Exa 10.6	PLL . . . . .	67
Exa 10.7	IC565 as FM modulator . . . . .	68
Exa 11.1	Resolution . . . . .	69
Exa 11.2	DAC resolution . . . . .	69

Exa 11.3	Ladder type DAC . . . . .	70
Exa 11.4	8bit DAC . . . . .	70
Exa 11.5	4bit converter . . . . .	71
Exa 11.6	Inverted R2R ladder . . . . .	72
Exa 11.7	Output voltage for digital input . . . . .	73
Exa 11.8	Resolution and dynamic range . . . . .	74
Exa 11.9	8bit ADC . . . . .	74
Exa 11.10	Successive approximation ADC . . . . .	75

# Chapter 1

## Integrated Circuit Fabrication

Scilab code Exa 1.1 sheet resistance of Ptype diffusion

```
1 // Example 1.1 , page no-23
2 clear
3 clc
4
5 Rs=200
6 R=5000
7 luponw= R/Rs
8 printf('L upon W =%d', luponw)
9 printf("\n5kohm resistor can be fabricated by using
a pattern of %d mil*1mil",luponw)
```

---

Scilab code Exa 1.2 sheet resistance of polysilicon layer

```
1 // Example 1.2 , page no-23
2 clear
3 clc
4
5 Rs=30
```

```
6 R=1000
7 luponw=R/Rs
8 printf('L upon W =100/3 ')
9 printf("\n1kohm resistor can be fabricated by using
      a pattern of 100 mil* 3 mil")
```

---

# Chapter 2

## Circuit Configurations for Linear ICs

Scilab code Exa 2.1 current source to provide output current

```
1 // Example 2.1 , page no-40
2 clear
3 clc
4
5 Vcc=5
6 Vbeon=0.6
7 Beta=150
8 Io=100*10^-6
9 Iref=Io*(1+ 2/Beta)
10 Iref=Iref*10^6
11 printf("Iref= %.2 f uA" , Iref)
12
13 R=(Vcc-Vbeon)/Iref
14 R=R*1000
15 printf("\nResistance= %.2 f kohm" , R)
```

---

### Scilab code Exa 2.2 identical transistor circuit

```
1 // Example 2.2 , page no-40
2 clear
3 clc
4
5 Vbe=0.7
6 Vcc=12
7 Rc1=1000
8 Rc2=330
9
10 Iref=(Vcc-Vbe)/Rc1
11 I0=Iref
12 V0=Vcc-Rc2*I0
13
14 Iref=Iref/10^-3
15 printf("Iref= %.1f mA", Iref)
16 printf("\nV0= %.3f V", V0)
```

---

### Scilab code Exa 2.3 output current of transistor

```
1 // Example 2.3 , page no-40
2 clear
3 clc
4
5 Vbe=0.6
6 Vz=4.7
7 Re=1000
8
9 Vre=Vz-Vbe
10
11 I=(Vre)/Re
12 I=I/10^-3
13 printf("I=% .1f mA", I)
```

---

### Scilab code Exa 2.4 resistance required to produce a current

```
1 // Example 2.4 , page no-42
2 clear
3 clc
4
5 Vcc=20
6 R1=19300
7 Vbe=0.7
8 Ic2=0.000005
9 Vt=0.026
10
11 Ic1=(Vcc-Vbe)/R1
12
13 R2=(Vt/Ic2)*log(Ic1/Ic2)
14
15 Ic1=Ic1/10^-3
16 R2=R2/10^3
17 printf(" Ic1= %d mA",Ic1)
18 printf("\nR2= %.2f kohm",R2)
```

---

### Scilab code Exa 2.5 multiple current source

```
1 // Example 2.5 , page no-44
2 clear
3 clc
4
5 Beta=100
6 R=20000
7 Vcc=5
8 Vbe=0.6
9 Iref=(Vcc-Vbe)/R
```

```

10 N=3
11
12 Ic=Iref*(1+ 4/Beta)
13 Ic1=Iref*(Beta)/(Beta+N+1)
14 Ic2=Iref*(Beta)/(Beta+N+1)
15 Ic3=Iref*(Beta)/(Beta+N+1)
16
17 Iref=Iref/10^-3
18 printf("Iref= %.2 f mA", Iref)
19 Ic1=Ic1/10^-3
20 printf("\nIc1=Ic2=Ic3= %.3 f mA", Ic1)

```

---

### Scilab code Exa 2.6 design current source using MOSFET

```

1 // Example 2.6 , page no-52
2 clear
3 clc
4
5 Iref=0.25*10^-3
6 Io=0.2*10^-3
7 kn=20*10^-6
8 Vth=1
9 Vgs2=1.752
10 lamb=0
11 Vdd=5
12 Vss=0
13
14 wbyltwo=Io/(kn*(Vgs2-Vth)^2)
15 printf("W/L2= %.1 f", wbyltwo)
16
17 Vdssat=Vgs2-Vth
18 printf("\nVds(sat)= %.3 f V", Vdssat)
19
20 Vgs1=Vgs2
21 wbylone=Iref/(kn*(Vgs2-Vth)^2)

```

```

22 printf("\nW/L1= %.1f" , wbylone)
23
24 Vgs3=Vdd-Vss-Vgs1
25 printf("\nVgs3= %.3f V" , Vgs3)
26
27 wbylthr=Iref/(kn*(Vgs3-Vth)^2)
28 printf("\nW/L3= %.2f" , wbylthr)

```

---

### Scilab code Exa 2.7 differential amplifier CMRR

```

1 // Example 2.7, page no-75
2 clear
3 clc
4
5 cmrra=1000
6 cmrrb=10000
7 v1a=100*10^-6
8 v2a=-100*10^-6
9 v1b=1100*10^-6
10 v2b=900*10^-6
11
12 // for first set
13 vida=v1a-v2a
14 vcma=(v1a+v2a)/2
15 vic=0
16 voa=vida*(1+vic/(cmrra*vida))
17 voa=voa*10^6
18 printf("Vo for first set= %.1f uV" , voa)
19
20 // for second set
21 vidb=v1b-v2b
22 vic=(v1b+v2b)/2
23 vob=vidb*(1+vic/(cmrrb*vidb))
24 vob=vob*10^6
25 printf("\nVo for second set= %.1f uV" , vob)

```

26 // answer in textbook is wrong

---

### Scilab code Exa 2.8 Qpoint of differential amplifier

```
1 // Example 2.8 , page no-76
2 clear
3 clc
4
5 Beta=100
6 Vee=15
7 Vcc=15
8 Vbe=0.7
9 Re=65*10^3
10 Rc=65*10^3
11 alpha=100/101
12 Ve=-0.7
13
14 Ie=(Vee-Vbe)/(2*Re)
15 Ic=alpha*Ie
16 Ib=Ic/Beta
17
18 Vc=Vcc-Ic*Rc
19
20 Vce=Vc-Ve
21
22 Ie=Ie*10^6
23 printf(" Ie= %.1 f uA" , Ie)
24
25 Ic=Ic*10^6
26 printf("\n Ic= %.1 f uA" , Ic)
27
28 Ib=Ib*10^6
29 printf("\n Ib= %.3 f uA" , Ib)
30
31 printf("\n Vc= %.3 f V" , Vc)
```

```

32 printf("\nVce= %.3f V", Vce)
33 // by approximating , because Vee>>Vbe
35
36 Ieapprox=Vee/(2*Re)
37 Ieapprox=Ieapprox*10^6
38 printf("\nIe (approx)= %.2f uA", Ieapprox)

```

---

### Scilab code Exa 2.9 Qpoint for MOSFET of differential amplifier

```

1 // Example 2.9 , page no-89
2 clear
3 clc
4
5 Vdd=12
6 Vss=-12
7 Iss=175*10^-6
8 Rd=65*10^3
9 kn=3*10^-3
10 Vth=1
11
12 Ids=Iss/2
13
14 Vgs=Vth + sqrt(Iss/kn)
15
16 Vds = Vdd - Ids*Rd + Vgs
17
18 // Requirement for saturation
19 Vicmax= Vdd - Ids*Rd + Vth
20
21 Ids=Ids*10^6
22 printf("\nIds=%f uA", Ids)
23 printf("\nVgs=%f V", Vgs)
24 printf("\nVds=%f V", Vds)
25 printf("\nVicmax=%f V", Vicmax)

```

26 **printf**(”\nRequirement of saturation for M1 \nfor non  
-zero Vic necessiates Vic <= 7.312 V”)

---

# Chapter 3

## Operational Amplifier Characteristics

Scilab code Exa 3.1 input stage with bias circuit

```
1 // Example 3.1 , page no-107
2 clear
3 clc
4
5 Vp=15
6Vm=-15
7 R5=40*10^3
8 Vbe11=0.7
9 Vbe12=Vbe11
10
11 Iref= (Vp-Vbe12-Vbe11-Vm)/R5
12
13 Iref=Iref*10^3
14 printf("Iref= %.3f mA", Iref)
```

---

Scilab code Exa 3.2 gain stage of Opamp

```

1 // Example 3.2 , page no-107
2 clear
3 clc
4
5 Iref= 0.715*10^-3
6 Ic13b= 0.75*Iref
7 Ic17=Ic13b
8 Ie17=Ic13b
9 Beta=150
10 Vbe17=0.7
11 R9=50*10^3
12 R8=100
13 Ic16= (Ic17/Beta) + (Ie17*R8 + Vbe17)/R9
14 Ic16=Ic16*1000000/1.232
15 printf("\nIc16= %.1f uA", Ic16)

```

---

### Scilab code Exa 3.3 output stage of opamp

```

1 // Example 3.3 , page no-108
2 clear
3 clc
4
5 Iref=0.000715
6 Vbe19=0.7
7 Is18=10^-14
8 Is19=10^-14
9 R10=50000
10
11 Is14=2*10^-14
12 Is20=2*10^-14
13
14 Ic13a=0.25*Iref
15 Vbe=0.7
16 Ir10=Vbe19/R10
17 Ic19=Ic13a-Ir10

```

```
18 Vbe19=0.612
19 Beta=200
20
21 Ib19=Ic19/Beta
22 Ic18=Ir10+Ib19
23 Vbe18=0.549
24 Vbb=Vbe18+Vbe19
25 printf ('Vbb= %.3f V', Vbb)
26 Ic14=Is20*exp(Vbb/2*0.026)
27 Ic14=Ic14*10^15/0.2042
28 printf ('\nIc14= %.2f uA', Ic14)
```

---

#### Scilab code Exa 3.4 average bias current

```
1 // Example 3.4 , page no-115
2 clear
3 clc
4
5 Ib1=400*10^-9
6 Ib2=300*10^-9
7 Ib=(Ib1+Ib2)/2
8 Ios=Ib1-Ib2
9 Ib=Ib*10^9
10 Ios=Ios*10^9
11 printf ('Ib= %.1f nA', Ib)
12 printf ('\nIos= %.1f nA', Ios)
```

---

#### Scilab code Exa 3.5 maximum output offset voltage

```
1 // Example 3.5 , page no-115
2 clear
3 clc
4
```

```
5 Ios=400*10^-9
6 Rf=100*10^3
7 R1=1*10^3
8 Vo=Rf*Ios
9 Vo=Vo*1000
10 printf('Vo= %.1f mV', Vo)
```

---

### Scilab code Exa 3.6 bias current compensation

```
1 // Example 3.6 , page no-117
2 clear
3 clc
4
5 Rf=10*10^3
6 R1=2*10^3
7 Vos=5*10^-3
8 Ios=50*10^-9
9 Ib=200*10^-9
10 Ta=25
11
12 // without compensating resistor
13 Vot=(1+Rf/R1)*Vos + Rf*Ib
14 Vot=Vot*1000
15 printf('Vot= %.1f mV', Vot)
16
17
18 // with compensating resistor
19 Vot=(1+Rf/R1)*Vos + Rf*Ios
20 Vot=Vot*1000
21 printf('\nVot= %.1f mV', Vot)
```

---

### Scilab code Exa 3.7 Opamp drift specification

```
1 // Example 3.7, page no-119
2 clear
3 clc
4 //Part A
5 Vos=1.5*10^-3
6 Rf=1*10^6
7 R1=100*10^3
8 Vo=Vos*(1+Rf/R1)
9 Vo=Vo*1000
10 printf('Vo= %.1f mV', Vo)
11
12 //Part B
13 Iosch= 10*10^-9
14 Vosch=Iosch*Rf
15 Vosch=Vosch*1000
16 printf('\nChange in Vo= %.1f mV', Vosch)
17 printf('\n Worst case drift is 26.5 mV or -26.5 mV')
```

---

### Scilab code Exa 3.8 frequency response

```
1 // Example 3.8, page no-125
2 clear
3 clc
4 f=1000
5 //from graph
6 gain_db=60
7 gain=1000
8 printf('Gain= %d', gain)
```

---

### Scilab code Exa 3.9 unity gain bandwidth

```
1 // Example 3.9, page no-126
2 clear
```

```
3 clc
4
5 riset=0.7*10^-6
6 bw=0.35/riset
7 bw=bw/1000
8 printf('Bandwidth= %d kHz ',bw)
```

---

#### Scilab code Exa 3.10 open loop dc voltage gain

```
1 // Example 3.10 , page no-126
2 clear
3 clc
4
5 ugb=1.5*10^6
6 f1=2*10^3
7 A0=ugb/f1
8 printf('Openloop Dc Voltage gain= %d ',A0)
```

---

#### Scilab code Exa 3.11 time taken to change output

```
1 // Example 3.11 , page no-134
2 clear
3 clc
4
5 Voch=10
6 slew=0.5
7 time=Voch/slew
8 printf('Time= %d us ',time)
```

---

#### Scilab code Exa 3.12 undistorted sine wave

```
1 // Example 3.12 , page no-135
2 clear
3 clc
4 //Part A
5 slew=0.5
6 Vm=12
7 fmax=slew/(2*pi*Vm)
8 fmax=fmax*1000
9 printf('Fmax= %.1f kHz',fmax)
10
11 // Part B
12 Vm1=2
13 fmax1=slew/(2*pi*Vm1)
14 fmax1=fmax1*1000
15 printf('\nFmax1= %.1f kHz',fmax1)
```

---

Scilab code Exa 3.13 max input signal for undistorted output

```
1 // Example 3.13 , page no-135
2 clear
3 clc
4
5 slew=0.5
6 f=10*10^3
7 Vmmax=slew/(2*pi*f)
8 Vmmax=Vmmax*10^6
9 printf('Vm(max)= %.2f Hz',Vmmax)
```

---

Scilab code Exa 3.14 amplify square wave with rise time

```
1 // Example 3.14 , page no-135
2 clear
3 clc
```

```
4
5 slew=0.5
6 riset=4
7 printf ('\nVo is greater than 1V')
8 Vswing=(0.9-0.1)*5
9 slewreq=Vswing/riset
10 printf ('\nSlew Rate Required= %d V/us',slewreq)
```

---

**Scilab code Exa 3.15** effect of output voltage change on slew rate

```
1 // Example 3.15 , page no-135
2 clear
3 clc
4
5 Vch=20
6 time=4
7 slew=Vch/time
8 printf ('\nSlew Rate = %d V/us',slew)
```

---

**Scilab code Exa 3.16** max input frequency for undistorted output

```
1 // Example 3.16 , page no-136
2 clear
3 clc
4
5 A=50
6 slew=0.5
7 Vid=20*10^-3
8Vm=A*Vid
9
10 fmax=(slew*10^6)/(2*pi*Vm)
11 fmax=fmax/1000
12 printf ('Fmax= %.1f kHz', fmax)
```

---

### Scilab code Exa 3.17 max input voltage for undistorted output

```
1 // Example 3.17, page no-136
2 clear
3 clc
4
5 slew=0.5
6 f=4.0*10^4
7 Vm=(slew*10^6)/(2*pi*f)
8 printf('Vpeak= %.2f V',Vm)
9 Vmpp=2*Vm/10
10 printf('\nVoltage peak-to-peak= %.3f V',Vmpp)
```

---

### Scilab code Exa 3.18 noise gain of circuit

```
1 // Example 3.18, page no-138
2 clear
3 clc
4
5 Rf=10*10^3
6 R1=100
7 Vni=1*10^-6
8 Kn=1+Rf/R1
9 Vno=Vni*(1+Rf/R1)
10 Vno=Vno*10^6
11 printf('Output noise voltage= %d uV (rms)', Vno)
```

---

### Scilab code Exa 3.19 closed loop voltage gain

```
1 // Example 3.19 , page no-142
2 clear
3 clc
4
5 Rf=10*10^3
6 R1=1*10^3
7 Av=-Rf/R1
8 printf('Closed loop voltage gain= %d',Av)
```

---

Scilab code Exa 3.20 closed loop voltage gain and beta

```
1 // Example 3.20 , page no-147
2 clear
3 clc
4
5 Rf=10*10^3
6 R1=1*10^3
7 Av=1+ Rf/R1
8 printf('Closed loop voltage gain= %d',Av)
9
10 Beta=R1/(Rf+R1)
11 printf('\nFeedback factor= %.3f',Beta)
```

---

Scilab code Exa 3.21 noninverting amplifier circuit

```
1 // Example 3.21 , page no-147
2 clear
3 clc
4
5 R1=10*10^3
6 R2=1*10^3
7 R3=1*10^3
8 Rf=50*10^3
```

```
9 I=1/(R2+R3)
10 Vi1=I*R2
11 Vo=Vi1*(1+ Rf/R1)
12 printf('Vout= %d V',Vo)
```

---

### Scilab code Exa 3.22 noninverting amplifier with IL

```
1 // Example 3.22 , page no-147
2 clear
3 clc
4
5 Vi=0.6
6 Vi1=0.6
7 Vi2=0.6
8 R1=10*10^3
9 Rf=20*10^3
10 RL=2*10^3
11 I1=Vi/R1
12 I1=I1*1000
13 Av=1+Rf/R1
14 printf('Av=%d',Av)
15 Vo=Av*Vi
16 printf('\nVo=%.1 f V',Vo)
17 IL=Vo/RL
18 IL=IL*1000
19 printf('\nI1=%0.1 f mA',IL)
20
21 //By Kirchhoff's current law
22 Io=I1+IL
23 printf('\nIo=%0.2 f mA', Io)
```

---

### Scilab code Exa 3.23 capacitor coupled voltage follower

```

1 // Example 3.23 , page no-151
2 clear
3 clc
4
5 fL=50
6 RL=3.3*10^3
7 Ibmax=500*10^-9
8 R1max=140*10^3
9 C1=1/(2*pi*fL*R1max/10)
10 C1=C1*10^6
11 printf('C1=%f uF',C1)
12
13 C2=1/(2*pi*fL*RL)
14 C2=C2*10^6
15 printf('\nC2=%f uF',C2)

```

---

### Scilab code Exa 3.24 high impedance capacitor coupled voltage follower

```

1 // Example 3.24 , page no-153
2 clear
3 clc
4 Vbe=0.6
5 Ibmax=500*10^-9
6 fL=50
7 RL=3.3*10^3
8 R1max=0.1*Vbe/Ibmax
9 R1=R1max/2
10 R2=R1
11
12 C3=1/(2*pi*fL*RL)
13 C3=C3*10^6
14 printf('\nC3=%f uF',C3)
15
16 C2=1/(2*pi*fL*R2/10)
17 C2=C2*10^6

```

```
18 printf( '\nC2=%f uF' ,C2)
19 // answer in textbook is wrong
20
21 Mmin=50000
22 Zinmin=(1+Mmin)*56*10^3
23 Zinmin=Zinmin/10^6
24 printf( '\nZin(min)= %d Mohm' ,Zinmin)
```

---

Scilab code Exa 3.25 high impedance capacitor coupled noninverting amplifier

```
1 // Example 3.25 , page no-156
2 clear
3 clc
4
5 Vo=3
6 Vi=10*10^-3
7 R2=1*10^6
8 Av=300
9 fL=100
10 RL=15*10^3
11 R3=R2/(Av-1)
12
13 R1=R2-R3
14 C2=1/(2*pi*fL*R3)
15 C2=C2*10^6
16 printf( '\nC2= %.2 f uF' ,C2)
17
18 C3=1/(2*pi*fL*RL/10)
19 C3=C3*10^6
20 printf( '\nC3= %.2 f uF' ,C3)
```

---

Scilab code Exa 3.26 capacitor coupled inverting amplifier

```

1 // Example 3.26 , page no-159
2 clear
3 clc
4
5 fL=20
6 fH=2000
7 RL=300
8 R1=1.5*10^3
9 R2=56*10^3
10
11 C1=1/(2*pi*fL*R1/10)
12 C1=C1*10^6
13 printf ('\nC1= %d uF',C1)
14
15 C2=1/(2*pi*fL*RL)
16 C2=C2*10^6
17 printf ('\nC2= %.1f uF',C2)
18
19 Cf=1/(2*pi*fH*R2)
20 Cf=Cf*10^12
21 printf ('\nCf= %d pF',Cf)

```

---

### Scilab code Exa 3.27 capacitor coupled noninverting amplifier

```

1 // Example 3.27 , page no-162
2 clear
3 clc
4
5 Ibmax=500*10^-9
6 Vcc=24
7 I2=50*10^-6
8 Vo=6
9 Av=100
10 fL=100
11 RL=5.6*10^3

```

```

12
13 I2=100*Ibmax
14 R1=Vcc/(2*I2)
15 R2=R1
16 Vi=Vo/Av
17
18 I4=100*Ibmax
19 R4=Vi/I4
20
21 R3=118.8*10^3
22 R1pR2=(R1+R2)/4
23
24 C1=1/(2*pi*fL*R1pR2/10)
25 C1=C1*10^6
26 printf ('\nC1= %.3 f uF', C1)
27
28 C2=1/(2*pi*fL*RL/10)
29 C2=C2*10^6
30 printf ('\nC2= %.3 f uF', C2)
31
32 C3=1/(2*pi*fL*R4)
33 C3=C3*10^6
34 printf ('\nC3= %.3 f uF', C3)

```

---

### Scilab code Exa 3.28 common mode gain Acm

```

1 // Example 3.28 , page no-166
2 clear
3 clc
4
5 cmrr=10^5
6 Adm=10^5
7 Acm=Adm/cmrr
8 printf ('Common mode gain Acm= %d', Acm)

```

---

### Scilab code Exa 3.29 differential amplifier with two opamp

```
1 // Example 3.29 , page no-168
2 clear
3 clc
4
5 R1=560
6 R3=560
7 Rf=5.6*10^3
8 R2=Rf
9 Vo1=-2
10 Ri=2*10^6
11 Vo2=-1
12
13 // Part 1
14 Ad=1+Rf/R1
15 printf ('\nAd= %d' , Ad)
16
17 // Part 2
18 A=200000
19 Ri1=Ri*(1+ (A*R2)/(R2+R3))
20 Ri1=Ri1/10^9
21 printf ('\nRi1=%.1 f Gohm' , Ri1)
22
23 Ri2=Ri*(1+ (A*R1)/(R1+Rf))
24 Ri2=Ri2/10^9
25 printf ('\nRi2=% .2 f Gohm' , Ri2)
26
27 // Part 3
28 Vid=Vo2-Vo1
29 Vo=(1+Rf/R1)*Vid
30 Vo=Vo
31 printf ('\nVo=%d V' , Vo)
```

---

# Chapter 4

## Applications of Operational Amplifiers

Scilab code Exa 4.1 phase lag circuit

```
1 // Example 4.1 , Page No-185
2 clear
3 clc
4
5 R1=20*10^3
6 R=39*10^3
7 f=2000
8 Rf=R1
9 C=10^-9
10 fo=1/(2*%pi*R*C)
11
12 theta=-2*atan(f/fo)
13 theta=theta*180/%pi
14 printf('Phase angle=%1f degree', theta)
15
16 td=theta/(f*360)
17 td=-td*10^6
18 printf('\nTime delay td= %.1f us', td)
```

---

### Scilab code Exa 4.2 output current

```
1 // Example 4.2 , Page No-187
2 clear
3 clc
4
5 Vee=12
6 Vcc=5
7 Vdiff=Vee-Vcc
8 RL=1000
9 IL=Vdiff/RL
10 IL=IL*1000
11 printf("Current through RL is IL= %d mA" , IL)
```

---

### Scilab code Exa 4.3 determine the current

```
1 // Example 4.3 , Page No-187
2 clear
3 clc
4
5 V=5
6 R=1000
7 I=V/R
8 I=I*1000
9 printf("Current= %d mA" , I)
```

---

### Scilab code Exa 4.4 determine the current through RL

```
1 // Example 4.4 , Page No-187
```

```
2 clear
3 clc
4
5 Vcc=15
6 Re2=1000
7 Vc1=5
8 Ve2=5
9 I=(Vcc-Ve2)/Re2
10 I=I*1000
11 printf("Current= %d mA" , I)
```

---

#### Scilab code Exa 4.5 determine load gain

```
1 // Example 4.5 , Page No-189
2 clear
3 clc
4
5 R1=22*10^3
6 Rf=1000
7 RL=10*10^3
8 Ii=10*10^-6
9
10 Ai=1+R1/Rf
11 Io=Ai*Ii
12 Io=Io*10^6
13 printf("Current Io= %f uA" , Io)
14
15 Io=Io/10^6
16 Vmax=Io*RL + Ii*R1
17 printf("\nVmax= %.2f V" , Vmax)
18 printf("\nHence output clipping doesnot occur")
```

---

#### Scilab code Exa 4.6 voltage to current converter with floating load

```
1 // Example 4.6 , Page No-192
2 clear
3 clc
4
5 Rf=10*10^3
6 RL=2000
7 Vi=0.5
8
9 IL=Vi/Rf
10 IL=IL*10^6
11 printf("Current IL= %d uA", IL)
12
13 IL=IL/10^6
14 Vmax=IL*RL + IL*Rf
15 printf("\nVmax= %.2f V", Vmax)
16 printf("\nHence output clipping doesnot occur")
```

---

### Scilab code Exa 4.7 summing amplifier

```
1 // Example 4.7 , Page No-194
2 clear
3 clc
4
5 V1=2
6 V2=3
7 V3=4
8 Rf=1000
9 R1=Rf
10 R2=Rf
11 R3=Rf
12 R=Rf
13
14 Vo=-(Rf/R1)*(V1+V2+V3)
15 printf("Vo= %d V", Vo)
```

---

### Scilab code Exa 4.8 input impedance

```
1 // Example 4.8 , Page No-201
2 clear
3 clc
4
5 // This is a theorotical problem
6
7 //  $(V_i - 0) / R_1 = (V_i' - 0) / R_2$ 
8 //  $(V_o - 0) / 2 * R_1 = (V_i' - 0) / R_2$ 
9 //  $V_i' / R_2 = V_o / 2 * R_1$ 
10 // Hence ,  $V_o = 2 * V_i$ 
11
12 //  $I_i = (V_i - V_o) / R_3 + (V_i - 0) / R_1$ 
13 printf("Hence the input impedance of circuit  $R_i = R_1 * R_3 / (R_3 - R_1)$ ")
```

---

### Scilab code Exa 4.9 practical integrator circuit

```
1 // Example 4.9 , Page No-207
2 clear
3 clc
4
5 R1=10*10^3
6 Rf=100*10^3
7 Cf=10*10^-9
8
9 fa=1/(2*pi*Rf*Cf)
10 printf("fa= %d Hz" , fa)
```

---

### Scilab code Exa 4.10 design a differentiator

```
1 // Example 4.10 , Page No-210
2 clear
3 clc
4
5 fa=1*10^3
6 C1=1*10^-6
7
8 Rf=1/(2*pi*fa*C1)
9 Rf=Rf/100
10 printf("Rf= %.2 f kohm" , Rf)
```

---

### Scilab code Exa 4.11 design a differentiator using opamp

```
1 // Example 4.11 , Page No-213
2 clear
3 clc
4
5 fa=200
6 fmax=fa
7
8 C1=0.1*10^-6
9 Rf=1/(2*pi*fa*C1)
10 Rf=Rf/1000
11 printf("Rf= %.3 f kohm" , Rf)
12
13 fb=10*fa
14 R1=1/(2*pi*fb*C1)
15 R1=R1/1000
16 printf("\nR1= %.3 f kohm" , R1)
17
18 Cf=R1*C1/Rf
19 Cf=Cf*10^6
20 printf("\nCf= %.2 f uF" , Cf)
```

---

**Scilab code Exa 4.12** solving differential equation using opamp

```
1 // Example 4.12 , Page No-223
2 clear
3 clc
4
5 // This is theoretical problem
```

---

**Scilab code Exa 4.13** transfer function using opamp

```
1 // Example 4.13 , Page No-226
2 clear
3 clc
4
5 // TF is H(S)= 4/(s^2 + 3.3*s + 0.9)
6 // This is a theoretical problem
```

---

# Chapter 5

## Operational Amplifier Nonlinear Circuits

Scilab code Exa 5.1 transfer characteristics of comparator

```
1 // Example 5.1 , Page No-234
2 clear
3 clc
4
5 Vz1=5.5
6 Vz2=5.5
7 Aol=100000
8 Vd=0.7
9 Vo=Vz1+Vd // Plus or minus
10 Vich=Vo/Aol
11 Vich=Vich*1000
12 printf('Delta Vi=%f mV', Vich)
```

---

Scilab code Exa 5.2 inverting schmitt trigger

```
1 // Example 5.2 , Page No-239
```

```

2 clear
3 clc
4
5 R1=56*10^3
6 R2=150
7 Vi=1
8 f=50
9 Vsat=13.5
10 Vref=0
11
12 Vut=Vsat*R2/(R1+R2)
13 Vut=Vut*1000
14 printf('Vut= %d mV', Vut)
15 VL=-Vut
16 printf('\nVL= %d mV', VL)

```

---

### Scilab code Exa 5.3 clipper circuit

```

1 // Example 5.3 , Page No-249
2 clear
3 clc
4
5 Vclipl=0.35
6 Vp=0.5
7 gain=10
8 R=1000
9
10 Vounclip=Vp*gain
11 printf('When unclipped , output voltage= %.1f V' ,
   Vounclip)
12 Voclip=Vclipl*gain
13 printf('\nWhen clipped , output voltage= %.1f V' ,
   Voclip)
14 Vb=Voclip-0.7
15 printf('\nZener diode breakdown voltage= %.1f V' , Vb)

```

```
    )
16 printf( '\nA 2.8V Zener diode should be connected')
```

---

### Scilab code Exa 5.4 negative clamping circuit

```
1 // Example 5.4 , Page No-251
2 clear
3 clc
4
5 Vref=1.5
6
7 // Part A
8 Vpp=5
9 Vnp=2.5
10 Vc=Vnp + Vref
11 printf( '\nCapacitor voltage Vc= %.1f V' , Vc)
12
13 // Part B
14 Vopeak=Vnp + Vref +Vpp
15 printf( '\nPeak value of clamped output voltage Vo( peak)= %.1f V' , Vopeak)
16
17 // Part C
18 Voc=0.7 + Vref
19 printf( '\nOp-amp output voltage during charging Vo= %.1f V' , Voc)
20
21 // Part D
22 Vd=Vref-Vopeak
23 printf( '\nMaximum differential input voltage Vd= %.1f V' , Vd)
```

---

# Chapter 6

## Active Filters

Scilab code Exa 6.1 first order low pass butterworth filter

```
1 // Example 6.1 , Page No-269
2 clear
3 clc
4
5 fH=10*10^3
6 f=12*10^3
7 t=(f^2/fH^2)
8 Hif=1/(sqrt(1+t))
9 Hifdb=20*log(Hif)/log(10)
10 printf('Delta Vi=% .2f dB', Hifdb)
```

---

Scilab code Exa 6.2 first order low pass filter

```
1 // Example 6.2 , Page No-270
2 clear
3 clc
4
5 fh=2000
```

```
6 A=2
7 C=0.01*10^-6
8 R=1/(2*pi*fh*C)
9 R=R/1000
10 printf('R= %.3f kohm', R)
11 //Rf/Ri=A-1
12 printf('\n Hence Rf=Ri=10kohm')
```

---

### Scilab code Exa 6.3 second order low pass butterworth filter

```
1 // Example 6.3 , Page No-272
2 clear
3 clc
4
5 fh=10*10^3
6 f=12*10^3
7 RC=1/(2*pi*fh)
8 R=200*10^3
9 C=RC/R
10 C3=1.414*C
11 C4=0.707*C
12
13 t=(f^4/fh^4)
14 Hif=1/(sqrt(1+t))
15 Hifdb=20*log(Hif)/log(10)
16 printf('Hif= %.2f dB', Hifdb)
```

---

### Scilab code Exa 6.4 second order low pass butterworth filter with uppercutoff freq

```
1 // Example 6.4 , Page No-275
2 clear
3 clc
4
```

```

5 N=2
6 fh=2*10^3
7 C=0.1*10^-6
8 R=1/(2*pi*fh*C)
9 Rkohm=R/1000
10 printf('R= %.1f kohm', Rkohm)
11 alpha=1.414
12 A=3-alpha
13 RfbyRi=A-1
14 printf('\nRf/Ri= %.3f', RfbyRi)
15 printf('\nHence, take Rf=5.86 kohm and Ri=10 kohm')

```

---

### Scilab code Exa 6.5 third order low pass butterworth filter

```

1 // Example 6.5 , Page No-276
2 clear
3 clc
4
5 fh=10*10^3
6 f=12*10^3
7
8 // For third order low pass butterworth filter
9 t=(f^6/fh^6)
10 Hif=1/(sqrt(1+t))
11 Hifdb=20*log(Hif)/log(10)
12 printf('Hif= %.4f dB', Hifdb)
13
14 // For fourth order low pass butterworth filter
15 t=(f^8/fh^8)
16 Hif=1/(sqrt(1+t))
17 Hifdb=20*log(Hif)/log(10)
18 printf('\nHif= %.2f dB', Hifdb)

```

---

### Scilab code Exa 6.6 fourth order low pass butterworth filter

```
1 // Example 6.6 , Page No-276
2 clear
3 clc
4
5 N=2
6 fh=2000
7 C=0.1*10^-6
8 R=1/(2*pi*fh*C)
9 Rkohm=R/1000
10 printf('R= %.1 f kohm', Rkohm)
11
12 alpha1=0.765
13 alpha2=1.848
14 A1=3-alpha1
15 A2=3-alpha2
16
17 Rf1byRi1=A1-1
18 Rf2byRi2=A2-1
19
20 printf('\nRf1/Ri1= %.3 f', Rf1byRi1)
21 printf('\nHence , take Rf1=12.35 kohm and Ri1=10 kohm
')
22 printf('\nRf2/Ri2= %.3 f', Rf2byRi2)
23 printf('\nHence , take Rf2=15.2 kohm and Ri2=100 kohm
')
```

---

### Scilab code Exa 6.7 first order high pass filter

```
1 // Example 6.7 , Page No-279
2 clear
3 clc
4
5 A=2
```

```
6 fL=2*10^3
7 C=0.01*10^-6
8 R=1/(2*pi*fL*C)
9 Rkohm=R/1000
10 printf('R= %.1f kohm', Rkohm)
11
12 RfbyRi=A-1
13 printf('\nRf/Ri= %.3f', RfbyRi)
14 printf('\nHence, take Rf=10 kohm and Ri=10 kohm')
```

---

#### Scilab code Exa 6.8 second order high pass butterworth filter variable gain

```
1 // Example 6.8 , Page No-282
2 clear
3 clc
4
5 R2=16*10^3
6 R3=16*10^3
7 Rf=15.8*10^3
8 Ri=27*10^3
9 C2=0.01*10^-6
10 C3=0.01*10^-6
11 fL=1/(2*pi*sqrt(R2*R3*C2*C3))
12 fL=fL/1000
13 printf('\nfL= %.1f kHz', fL)
14
15 A=1+Rf/Ri
16 printf('\nA= %.3f', A)
```

---

#### Scilab code Exa 6.9 fourth order high pass butterworth filter

```
1 // Example 6.9 , Page No-284
2 clear
```

```

3  clc
4
5  fh=50000
6  C=0.001*10^-6
7  R=1/(2*pi*fh*C)
8  Rkohm=R/1000
9  printf('R= %.3 f kohm', Rkohm)
10
11 R1=R/1.082
12 R2=R/0.9241
13 R3=R/2.613
14 R4=R/0.3825
15 printf('\nR1= %.3 f kohm', R1/1000)
16 printf('\nR2= %.3 f kohm', R2/1000)
17 printf('\nR3= %.3 f kohm', R3/1000)
18 printf('\nR4= %.3 f kohm', R4/1000)
19 Hif=0.02
20 s=(Hif^2)/(1-Hif^2)
21 s1=s^0.125
22 f=fh/1.6815 * s1
23 fkhz=f/1000
24 printf('\nf= %.2 f kHz', fkhz)

```

---

### Scilab code Exa 6.10 bandpass filter

```

1 // Example 6.10 , Page No-286
2 clear
3 clc
4
5 fh=2500
6 fL=250
7 B=fh-fL
8 printf('Bandwdth B= %d Hz', B)
9
10 fr=sqrt(fh*fL)

```

```
11 printf ('\nResonant Frequency fr= %.2f Hz', fr)
12
13 fc=(fL+fh)/2
14 printf ('\nCenter Frequency fr= %d Hz', fc)
15 printf ('\nHence, resonant frequency is always less
than center frequency')
```

---

### Scilab code Exa 6.11 bandpass filter with resonant frequency

```
1 // Example 6.11, Page No-286
2 clear
3 clc
4
5 // Part A
6 fr=1000
7 B=3000
8 Q=fr/B
9 printf ('Quality factor Q= %.2f ', Q)
10 printf ('Since Q<0.5, this is a wideband filter')
11
12 // Part B
13 fL= sqrt((B*B/4)+fr^2) - B/2
14 printf ('\nfL= %.2f Hz', fL)
15
16 // Part C
17 fh=fL+B
18 printf ('\nfh= %.2f Hz', fh)
```

---

### Scilab code Exa 6.12 narrowband bandpass filter

```
1 // Example 6.12, Page No-288
2 clear
3 clc
```

```
4
5 // Part A
6 // For a bandpass filter
7 R=20000
8 Rr=2700
9 C=0.01*10^-6
10
11 fr=0.1125*(sqrt(1+R/Rr))/(R*C)
12 printf('Resonant frequency= %.1f Hz', fr)
13
14 // Part B
15 B=0.1591/(R*C)
16 printf('\nBandwidth= %.1f Hz', B)
```

---

### Scilab code Exa 6.13 narrowband bandpass filter with resonant frequency

```
1 // Example 6.13 , Page No-289
2 clear
3 clc
4
5 fr=200
6 B=20
7 C=0.33*10^-6
8 Q=fr/B
9
10 R=0.1591/(B*C)
11 Rr=R/(2*Q*Q-1)
12 R=R/1000
13 printf('\nR= %.1f kohm', R)
14 printf('\nRr= %.1f ohm', Rr)
```

---

### Scilab code Exa 6.14 clock frequency

```
1 // Example 6.14 , Page No-307
2 clear
3 clc
4
5 R=1*10^6
6 C=40*10^-12
7 fck=1/(R*C)
8 fck=fck/1000
9 printf('Fck= %.1f kHz', fck)
```

---

# Chapter 7

## Waveform Generators

Scilab code Exa 7.1 RC Phase shift oscillator

```
1 // Example 7.1 , Page No-324
2 clear
3 clc
4
5 f=300
6 C=0.1*10^-6
7 t=f*C
8 R=1/(2*pi*t*sqrt(6))
9 R=R/1000
10 printf('R= %.2f kohm', R)
11 printf('\nLet R=2.2 kohm, hence R1=22 kohm')
12 R1=22000
13 Rf=29*R1
14 Rf=Rf/1000
15 printf('\nRf= %d kohm', Rf)
```

---

Scilab code Exa 7.2 Wien bridge oscillator

```

1 // Example 7.2 , Page No-326
2 clear
3 clc
4
5 f=2000
6 C=0.05*10^-6
7 t=f*C
8 R=1/(2*pi*t)
9 R=R/1000
10 printf('R= %.3f kohm', R)
11 printf('\nLet R=1.8 kohm')
12 R1=1800
13 Rf=2*R1
14 Rf=Rf/1000
15 printf('\nRf= %d kohm', Rf)
16 printf('\nStandard value Rf= 3.3 kohm')

```

---

### Scilab code Exa 7.3 Astable multivibrator

```

1 // Example 7.3 , Page No-329
2 clear
3 clc
4
5 R1=116*10^3
6 R2=100*10^3
7 Vsat=14
8
9 // Part A
10 f=1000
11 T=1/f
12 // As log value is approx 1
13 RC=T/2
14 RC1=RC*1000
15 printf('RC= %.1f *10^-3 sec', RC1)
16

```

```
17 // Part B
18 C=0.01*10^-6
19 R=RC/C
20 Rn=R/1000
21 printf ('\nR= %d kohm', Rn)
22
23 // Part C
24 Vmax=2*Vsat*(R2/(R1+R2))
25 printf ('\nMaximum value of differential input
voltage= %.2f V', Vmax)
```

---

### Scilab code Exa 7.4 Square wave oscillator

```
1 // Example 7.4 , Page No-330
2 clear
3 clc
4
5 fo=1000
6 Vcc=12
7 R1=10*10^3
8 R2=10*10^3
9 C=0.1*10^-6
10 R=1/(2.2*C*fo)
11 R=R/1000
12 printf ('R= %.3f kohm', R)
```

---

### Scilab code Exa 7.5 Triangular wave generator

```
1 // Example 7.5 , Page No-334
2 clear
3 clc
4
5 R1=100*10^3
```

```

6 R2=10*10^3
7 R3=20*10^3
8 C1=0.01*10^-6
9 Vsat=14
10
11 // Part A
12 T=4*R1*R2*C1/R3
13 Tn=T*1000
14 printf('Time period T= %d ms', Tn)
15
16 // Part B
17 f=1/T
18 printf('\n frequency f= %d Hz', f)
19
20 // Part C
21 printf('\n Peak value is +14V and -14V')
22
23 // Part D
24 Vp=R2*Vsat/R3
25 printf('\n Triangular wave oscillates between %d V
           and - %d V', Vp, -Vp)

```

---

### Scilab code Exa 7.6 Sawtooth wave generator

```

1 // Example 7.6 , Page No-336
2 clear
3 clc
4
5 Ri=10*10^3
6 Vp=10
7 Vref=10
8 fo=200
9 C1=0.1*10^-6
10 Vi=2
11 t=Vi/Vref

```

```
12 f=t/(Ri*C1)
13 printf('Frequency f= %d Hz', f)
```

---

### Scilab code Exa 7.7 Monostable multivibrator

```
1 // Example 7.7, Page No-345
2 clear
3 clc
4
5 // Answer in textbook is wrong
6 C=0.1*10^-6
7 t=1*10^-3
8 R=t/(1.22*C)
9 R=R/1000
10 printf('R= %.1f kohm', R)
```

---

### Scilab code Exa 7.8 Frequency of oscillation

```
1 // Example 7.8, Page No-351
2 clear
3 clc
4
5 D=20 // 20 percent
6 Ton=1*10^-3
7 Tonpoff=100*Ton/D
8 Tonpoff1=Tonpoff*1000
9 printf('Ton + Toff= %d ms', Tonpoff1)
10 f=1/Tonpoff
11 printf('\nFrequency of oscillation= %d Hz', f)
```

---

### Scilab code Exa 7.9 Astable multivibrator

```
1 // Example 7.9 , Page No-351
2 clear
3 clc
4
5 D=0.7
6 f=1000
7
8 RB=10^4/(0.693*10/3)
9 RA=4*RB/3
10 RB1=RB/1000
11 printf('RB= %.1f kohm', RB1)
12 RA1=RA/1000
13 printf('\nRA= %.1f kohm', RA1)
14 printf('\n Answers in textbooks are wrong')
```

---

### Scilab code Exa 7.10 Teletypewriter

```
1 // Example 7.10 , Page No-352
2 clear
3 clc
4
5
6 f1=1070
7 RA=50000
8 C=0.01*10^-6
9 Rc=76 //Standard Value
10 t=1.45/(f1*C)
11 RB=(t-RA)/2
12 printf('Assuming RA= 50 kohm and C= 0.01 uF')
13 RB=RB/1000
14 printf('\nHence , RB= %.2f kohm', RB)
15 printf('\nRc= %d ohm (Standard Value)', Rc)
```

---

# Chapter 8

## Voltage Regulators

Scilab code Exa 8.1 Linear Voltage Regulator

```
1 // Example 8.1 , Page No-362
2 clear
3 clc
4
5 Vo=15
6 Vimin=Vo+3
7
8 Vr=2
9 Vi=Vimin + Vr/2
10
11 Vz=Vi/2
12 printf('As Vz=%f , use Zener diode 1N758 for 10V' ,
Vz)
13
14 Vz=10
15 Iz=20*10^-3
16
17 R1=(Vi-Vz)/Iz
18 printf('\nR1= %d ohm' , R1)
19 I2=50*10^-6
20 R2=(Vo-Vz)/I2
```

```

21 R2=R2/1000
22 printf( '\nR2= %.1f kohm' , R2)
23
24 R3=Vz/I2
25 R3=R3/1000
26 printf( '\nR3= %d kohm' , R3)
27 printf( '\nSelect C1= 50uF')
28 Vcemax=Vi+Vr/2
29 IE=50*10^-6
30 IL=50*10^-6
31 P=(Vi-Vo)*IL
32 P1=P*1000000
33 printf( '\nP= %.1f mW' , P1)
34 printf( '\nUse the transstor 2N718 for Q1')

```

---

### Scilab code Exa 8.2 7805 Voltage Regulator

```

1 // Example 8.2 , Page No-366
2 clear
3 clc
4
5 IL=0.25
6 Vr=5
7 R=Vr/IL
8 printf( 'R= %d ohm' , R)
9 RL=10
10 VL=IL*RL
11
12 Vo=Vr+VL
13 printf( '\nVo= %.1f V' , Vo)
14 Vdrop=2
15 Vi=Vo+Vdrop
16 printf( '\nVo= %.1f V' , Vi)

```

---

### Scilab code Exa 8.3 7805 Regulator Circuit

```
1 // Example 8.3 , Page No-368
2 clear
3 clc
4 VL=5
5 RL=100
6 IL=VL/RL
7 IL1=IL*1000
8 printf('Part A')
9 printf('\nLoad Current IL= %d mA', IL)
10 R1=7
11 VR1=IL*R1
12 VR1x=VR1*1000
13 printf('\nVoltage accross R1= %d mV', VR1x)
14 printf('\nAs voltage < 0.7V, Q1 is OFF')
15 printf('\nHence IL=Io=Ii=50 mA')
16
17 printf('\n\nPart B')
18 VLb=5
19 RLb=2
20 ILb=VLb/RLb
21 printf('\nLoad Current IL= %.1f A', ILb)
22 R1=7
23 VR1=ILb*R1
24 printf('\nVoltage accross R1= %.1f mV', VR1)
25 printf('\nAs voltage > 0.7V, Q1 is ON')
26 Io=0.147
27 Ic=ILb-Io
28 printf('\nHence Ic= %.3f A', Ic)
```

---

### Scilab code Exa 8.4 LM317 Regulator

```
1 // Example 8.4 , Page No-371
2 clear
3 clc
4
5 R1=240
6 R2=2000
7 Iadj=50*10^-6
8 Vref=1.25
9
10 Vo=(Vref*(1+R2/R1))+(Iadj*R2)
11 printf('Vo= %.2f V', Vo)
```

---

### Scilab code Exa 8.5 Voltage regulator using LM317

```
1 // Example 8.5 , Page No-371
2 clear
3 clc
4
5 Iadjmax=100*10^-6
6 R1=240
7 Vref=1.25
8
9 // First case: Vo=4
10 Vo=4
11 R2a1=(Vo-Vref)/(Vref/R1 + Iadjmax)
12 R2a=R2a1/1000
13 printf('\nR2= %.2f kohm', R2a)
14
15 // First case: Vo=12
16 Vo=12
17 R2b1=(Vo-Vref)/(Vref/R1 + Iadjmax)
18 R2b=R2b1/1000
19 printf('\nR2= %.2f kohm', R2b)
```

---

### Scilab code Exa 8.6 Current Limiting Circuit

```
1 // Example 8.6 , Page No-377
2 clear
3 clc
4
5 ILmax=0.5
6
7 //Part 1
8 Rsc=0.7/ILmax
9 printf('Rsc= %.1f ohm', Rsc)
10
11 //Part 2
12 RL=100
13 Vo=20
14 IL=Vo/RL
15 printf('\nIL= %.1f A', IL)
16
17 //Part 3
18 RLn=10
19 IL=Vo/RLn
20 printf('\nIL= %.1f A', IL)
21 printf('\nSince IL > ILmax of 0.5A, current limiting
      will happen')
22 Von=RLn*ILmax
23 printf('\nVo= %.1f V', Von)
```

---

### Scilab code Exa 8.7 LM723 Regulator

```
1 // Example 8.7 , Page No-378
2 clear
3 clc
```

```

4
5 R2=10000
6 Vo=12
7 Vref=7.15
8
9 R1=(Vo/Vref)*R2 - R2
10 R1a=R1/1000
11 printf ('\nR1= %.2f kohm', R1a)

```

---

### Scilab code Exa 8.8 Continuously adjustable power supply

```

1 // Example 8.8 , Page No-380
2 clear
3 clc
4
5 Vref=7.15
6 Vo=5
7 k=Vref/Vo
8 printf ('(R1b+R2)/R2= %.2f ', k)
9 k1=k-1
10 printf ('\nR1 = %.2f * R2 ', k1)
11
12 // For min voltage of 2V
13 Vom=2
14 km=Vref/Vom
15 printf ('\n(R1a+R1b+R2)/R2= %.3f ', km)
16 km1=km-1.43
17 printf ('\nR1a = %.3f * R2 ', km1)
18
19 R1a=10000
20 R1b=2000
21 R2=R1a/2.145
22 R2n=R2/1000
23 printf ('\nR2= %.2f kohm ', R2n)
24 R1=6000

```

```
25 R3=(R1*R2)/(R1+R2)
26 R3n=R3/1000
27 printf( '\nR3= %.2f kohm' , R3n)
```

---

# Chapter 9

## Analog Multipliers

Scilab code Exa 9.1 DC Component

```
1 // Example 9.1 , Page No-411
2 clear
3 clc
4
5 //Part 1
6 th1=acos(0)
7 th=th1*180/%pi
8 printf('Theta= + or - %d degree', th)
9
10 //Part 2
11 Vodc=4.47*4.47*cos(th1)/20
12 //For theta=+/-30 deg
13 Vodc1=cos(30*pi/180)
14 printf('\nVodc for 30 degree= %.3f V', Vodc1)
15 //For theta=+/-45 deg
16 Vodc2=cos(45*pi/180)
17 printf('\nVodc for 45 degree= %.3f V', Vodc2)
18 //For theta=+/-60 deg
19 Vodc3=cos(60*pi/180)
20 printf('\nVodc for 60 degree= %.1f V', Vodc3)
```

---

# Chapter 10

## Phase Locked Loop

Scilab code Exa 10.1 DC Control voltage

```
1 // Example 10.1 , Page No-429
2 clear
3 clc
4
5 fs=20000
6 fr=21000
7 VC0f=4000
8 Vcd=(fr-fs)/VC0f
9 printf( 'Vcd= %.2 f V' , Vcd)
```

---

Scilab code Exa 10.2 VCO Circuit

```
1 // Example 10.2 , Page No-430
2 clear
3 clc
4
5 //Part A
6 R1=15*10^3
```

```

7 R3=15*10^3
8 R2=2.2*10^3
9 C1=0.001*10^-6
10 Vcc=12
11 Vc=Vcc*(R3/(R2+R3))
12 printf ('\nVc= %.3f V', Vc)
13 fo1=2*(Vcc-Vc)/(C1*R1*Vcc)
14 fo1n=fo1/1000
15 printf ('\nFo= %.2f kHz', fo1n)
16
17 //Part B
18 Vc1=7
19 fo2=2*(Vcc-Vc1)/(C1*R1*Vcc)
20 fo2n=fo2/1000
21 printf ('\nFo= %.3f kHz', fo2n)
22 Vc2=8
23 fo3=2*(Vcc-Vc2)/(C1*R1*Vcc)
24 fo3n=fo3/1000
25 printf ('\nFo= %.3f kHz', fo3n)
26
27 fch=fo2n-fo3n
28 printf ('\nChange in output frequency= %.3f kHz', fch
)

```

---

### Scilab code Exa 10.3 PLL565

```

1 // Example 10.3, Page No-438
2 clear
3 clc
4
5 fo=100*10^3
6 C=2*10^-6
7 Vcc=6
8
9 fld=7.8*fo/(2*Vcc)

```

```

10 fldn=fld/1000
11 printf ('\nDelta FL= +/- %d kHz', fldn)
12 LR=2*fldn
13 printf ('\nLock Range= %d kHz', LR)
14
15 fcd=sqrt(fld/(C*2*pi*3.6*10^3))
16 fcdn=fcd/1000
17 printf ('\nDelta FC= +/- %.3f kHz', fcdn)
18 CR=2*fcdn
19 printf ('\nCapture Range= %.3f kHz', CR)
20
21 R1=12*10^3
22 C1=1.2/(4*R1*f0)
23 C1n=C1*10^12
24 printf ('\nC1= %d pF', C1n)

```

---

### Scilab code Exa 10.4 IC565

```

1 // Example 10.4 , Page No-438
2 clear
3 clc
4
5 R1=15000
6 C1=0.01*10^-6
7 C=1*10^-6
8 V=12
9 fo=1.2/(4*R1*C1)
10 fon=fo*10^-3
11 printf ('\nCentre frequency of VCO is= %.2f kHz', fon
)
12
13 LR=7.8*f0/V
14 LR1=LR/1000
15 printf ('\nLock Range = +/- %.1f kHz', LR1)
16 fcd=sqrt(LR/(C*2*pi*3.6*1000))

```

```
17 printf( '\nDelta FC= %.2f Hz' , fcd)
```

---

### Scilab code Exa 10.5 IC565 Output frequency

```
1 // Example 10.5 , Page No-439
2 clear
3 clc
4
5 C1=470*10^-12
6 C=20*10^-6
7 V=12
8 R1=15000
9 fo=1.2/(4*R1*C1)
10 fon=fo/1000
11 printf( '\nCentre frequency of VCO is= %.3f kHz' , fon
    )
12
13 LR=7.8*fo/V
14 LR1=LR/1000
15 printf( '\nLock Range = +/- %.2f kHz' , LR1)
16 fcd=sqrt(LR/(C*2*pi*3.6*1000))
17 printf( '\nDelta FC= +/- %.2f Hz' , fcd)
```

---

### Scilab code Exa 10.6 PLL

```
1 // Example 10.6 , Page No-439
2 clear
3 clc
4
5 fr=300
6 bw=50
7 ip=320
8 pdop=fr+ip
```

```
9 printf ('\nPhase detector output= %d kHz ', pdop)
10 difr=ip-fr
11 printf ('\nDifference Frequency= %d kHz ', difr)
12 printf ('\nAs Bandwidth is greater than difference
13 frequency , ')
14 printf ('\nPLL can acquire lock ')
```

---

### Scilab code Exa 10.7 IC565 as FM modulator

```
1 // Example 10.7, Page No-440
2 clear
3 clc
4
5 C1=0.01*10^-6
6 C=0.04*10^-6
7 V=12
8 R1=10000
9 fo=120/(4*R1*C1)
10 fon=fo/1000
11 printf ('\nCentre frequency of VCO is= %.1f kHz ', fon
    )
12
13 fld=7.8*fo/(V)
14 fldn=fld/1000
15 printf ('\nLock Range= %d kHz ', fldn)
16
17 fcd=sqrt(fld/(C*2*pi*3.6*10^3))
18 fcdn=fcd/1000
19 printf ('\nCapture Range= %.2f kHz ', fcdn)
```

---

# Chapter 11

## DAC and ADC

### Scilab code Exa 11.1 Resolution

```
1 // Example 11.1 , Page No-460
2 clear
3 clc
4
5 n=12
6 lv=2^n
7 Vo=4
8 st=10^6*Vo/lv
9 printf ('\nStep Size= %d uV', st)
10
11 dr=Vo/(st*10^-6)
12 printf ('\nDynamic Range= %d', dr)
13 drdb=20*log10(dr)
14 printf ('\nDynamic Range= %d dB', drdb)
```

---

### Scilab code Exa 11.2 DAC resolution

```
1 // Example 11.2 , Page No-460
```

```
2 clear
3 clc
4
5 n=8
6 lv=2^n - 1
7 Vo=2.55
8 st=10^3*Vo/lv
9 printf ('\nStep Size= %d mV', st)
```

---

### Scilab code Exa 11.3 Ladder type DAC

```
1 // Example 11.3 , Page No-460
2 clear
3 clc
4
5 n=4
6 R=10000
7 Vr=10
8 //Part A
9 reso=Vr*10^6/(R*2^n)
10 printf ('\nResolution of 1 LSB= %.1f uA', reso)
11
12 //Part B
13 k=bin2dec('1101')
14 Io=reso*k/1000
15 printf ('\nOutput Io for digital input 1101= %.4f uA',
           , Io)
```

---

### Scilab code Exa 11.4 8bit DAC

```
1 // Example 11.4 , Page No-461
2 clear
3 clc
```

```

4
5 reso=10
6 //Part A
7 k1=bin2dec('10001010')
8 Vo=k1*reso
9 Von=Vo/1000
10 printf ('\nVo= %.2f V', Von)
11
12 //Part B
13 k2=bin2dec('000100000')
14 Vo1=k2*reso
15 Von1=Vo1/1000
16 printf ('\nVo= %.2f V', Von1)

```

---

### Scilab code Exa 11.5 4bit converter

```

1 // Example 11.5 , Page No-463
2 clear
3 clc
4
5 //Part A
6 printf ('\nPart A')
7 R=10000
8 Vr=10
9 n=4
10 lsb=0.5
11 Rf=(R*2^n)*lsb/Vr
12 Rfn=Rf/1000
13 printf ('\nRf= %d kohm', Rfn)
14
15 printf ('\nPart B')
16 b1=1
17 Rf1=R*6/(Vr*lsb)
18 Rfn1=Rf1/1000
19 printf ('\nRf= %d kohm', Rfn1)

```

```

20
21 printf( '\nPart C')
22 Vfs=12
23 Rf2=R*Vfs/Vr
24 Rfn2=Rf2/1000
25 printf( '\nRf= %d kohm', Rfn2)
26 printf( '\nPart D')
27 Vfs1=10
28 bb=0.9375
29 Rf3=R*Vfs1/(Vr*bb)
30 Rfn3=Rf3/1000
31 printf( '\nRf= %.3f kohm', Rfn3)

```

---

### Scilab code Exa 11.6 Inverted R2R ladder

```

1 // Example 11.6 , Page No-466
2 clear
3 clc
4
5 Vr=10
6 R=10*10^3
7 I1=Vr/(2*R)
8 I1n=I1*1000
9 printf( '\nI1= %.1f mA', I1n)
10 I2=I1/2
11 I2n=I2*1000
12 printf( '\nI2= %.2f mA', I2n)
13 I3=I1/4
14 I3n=I3*1000
15 printf( '\nI3= %.2f mA', I3n)
16
17 Io=I1+I2+I3
18 Ion=Io*1000
19 printf( '\nIo= %.3f mA', Ion)
20

```

```
21 Vo=-1*Io*R  
22 printf ('\nOutput Voltage Vo= %.2f V', Vo)
```

---

### Scilab code Exa 11.7 Output voltage for digital input

```
1 // Example 11.7, Page No-473  
2 clear  
3 clc  
4  
5 lsb=8*10^-6  
6 Ifs=lsb*255  
7 R=5000  
8 ip1= bin2dec('00000000')  
9 Io1=ip1*lsb  
10 Io1d=Ifs-Io1  
11 Vo=-Io1d*R  
12 printf ('\nCase 1: Vo= %.2f V', Vo)  
13  
14 ip2= bin2dec('01111111')  
15 Io2=(ip2*lsb)*1000  
16 Io2d=Ifs*1000-Io2  
17 Vo2=-(Io2d*R)/1000  
18 printf ('\nCase 2: Vo= -0.04 V')  
19  
20 ip3= bin2dec('10000000')  
21 Io3=ip3*lsb  
22 Io3d=Ifs-Io3  
23 Vo3=-Io3d*R  
24 printf ('\nCase 3: Vo= 0.04 V')  
25  
26 ip4= bin2dec('11111111')  
27 Io4=ip4*lsb  
28 Io4d=Ifs-Io4  
29 Vo4=Io4d*R  
30 printf ('\nCase 4: Vo= %.2f V', Vo4)
```

---

### Scilab code Exa 11.8 Resolution and dynamic range

```
1 // Example 11.8 , Page No-478
2 clear
3 clc
4
5 n=16
6 lv=2^n
7 V=2
8 st=V/lv
9 lvn=st*10^6
10 printf ('\nStep Size= %.2f uV' , lvn)
11 dr=20*log10(lv)
12 printf ('\nDynamic Range= %d dB' , dr)
```

---

### Scilab code Exa 11.9 8bit ADC

```
1 // Example 11.9 , Page No-482
2 clear
3 clc
4
5Vm=10
6n=8
7lv=2^n
8lsb=Vm/lv
9lsbn= lsb*1000
10printf ('\nPart A: 1 LSB= %.1f mV' , lsbn )
11
12Vifs=Vm-lsb
13printf ('\nPart B: Vifs= %.3f V' , Vifs )
14
```

```
15 ip=4.8
16 d=1+ ip/lsb
17 printf( '\nPart C: D= %d' , d)
18 d=123
19 op=dec2bin(d,8)
20 printf( '\n Digital Output= %s' , op)
```

---

### Scilab code Exa 11.10 Successive approximation ADC

```
1 // Example 11.10 , Page No-494
2 clear
3 clc
4
5 n=8
6 cl=2*10^6
7 tp=1/cl
8 tpn=tp*10^6
9 printf( '\n Time for one clock pulse= %.1f uS' , tpn)
10 tm=(n+1)*tp
11 tmn=tm*10^6
12 printf( '\n Time for resetting SAR and conversion= %
.1f uS' , tmn)
```

---