

Scilab Textbook Companion for  
Electronic Circuit Analysis And Design  
by D. A. Neamen<sup>1</sup>

Created by  
Priya Apte  
Electrical  
Electrical Engineering  
Indian Institute of Technology Patna  
College Teacher  
NA  
Cross-Checked by  
Ganesh R

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Electronic Circuit Analysis And Design

**Author:** D. A. Neamen

**Publisher:** McGraw-Hill Education

**Edition:** 2

**Year:** 2001

**ISBN:** 0256119198

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 Semiconductor materials and diodes</b>	<b>5</b>
<b>2 Diode Circuits</b>	<b>12</b>
<b>3 The Bipolar Junction Transistor</b>	<b>17</b>
<b>4 Basic BJT Amplifiers</b>	<b>29</b>
<b>5 The Field Effect Transistor</b>	<b>36</b>
<b>6 Basic FET Amplifier</b>	<b>46</b>
<b>7 Frequency Response</b>	<b>58</b>
<b>8 Ouput Stages and Power Amplifier</b>	<b>72</b>
<b>9 The Ideal Operational Amplifier</b>	<b>78</b>
<b>10 Integrated Circuit Biasing and Active Loads</b>	<b>80</b>
<b>11 Differential and Multistage Amplifier</b>	<b>88</b>
<b>12 Feedback and Stability</b>	<b>98</b>

<b>13 Operational Amplifier Circuits</b>	<b>105</b>
<b>14 Nonideal Effects in Operational Amplifier Circuits</b>	<b>116</b>
<b>15 Applications and Design of Integrated Circuits</b>	<b>121</b>
<b>16 MOSFET Digital Circuits</b>	<b>126</b>
<b>17 Bipolar Digital Circuits</b>	<b>132</b>

# List of Scilab Codes

Exa 1.1	Calculate intrinsic carrier concentration in silicon . . . . .	5
Exa 1.2	Calculate thermal equilibrium electron and hole concentrations . . . . .	5
Exa 1.3	Calculate the built in potential barrier of a pn junction . . . . .	6
Exa 1.4	Calculate the junction capacitance of a pn junction . . . . .	6
Exa 1.5	Determine the diode current in pn junction . . . . .	7
Exa 1.6	Determine the diode voltage and current . . . . .	8
Exa 1.7	Determine the diode voltage and current . . . . .	9
Exa 1.9	Analysing the circuit . . . . .	9
Exa 1.10	Calculate currents in a circuit . . . . .	10
Exa 1.11	Design the value of resistance required to limit the current in given circuit . . . . .	10
Exa 2.1	Compare voltages and the transformer turns ratio in two full wave rectifier circuits . . . . .	12
Exa 2.2	Determine the capacitance required to yield a particular ripple voltage . . . . .	13
Exa 2.3	Design a full wave rectifier . . . . .	14
Exa 2.5	Determine the percent regulation of a voltage regulator . . . . .	14
Exa 2.8	Determine the output voltage and diode currents . . . . .	15
Exa 2.10	Calculate the photocurrent generated in a photodiode . . . . .	16
Exa 2.11	Determine the value of R required to limit the current in circuit . . . . .	16

Exa 3.1	Calculate the collector and emitter currents	17
Exa 3.2	Calculate the breakdown voltage of a transistor . . . . .	17
Exa 3.3	Calculate the base collector and emitter currents and ce voltage for common emitter circuit . . . . .	18
Exa 3.4	Analyse the common emitter circuit with pnp transistor . . . . .	18
Exa 3.5	Calculate the currents and voltages in a circuit	19
Exa 3.6	Calculate the characteristics of a circuit containing an emitter resistor . . . . .	20
Exa 3.7	Calculate the characteristics of a circuit . . . . .	21
Exa 3.9	Calculate the characteristics of an npn bipolar circuit . . . . .	22
Exa 3.10	Calculate the currents output voltage and power dissipation . . . . .	23
Exa 3.13	Design the circuit . . . . .	24
Exa 3.14	Analyze a circuit using voltage divider bias circuit and determine the change in Q point	24
Exa 3.15	Design a bias stable circuit . . . . .	25
Exa 3.16	Determine the currents in a two transistor current source . . . . .	26
Exa 3.17	Calculate the dc voltages at each node and the dc currents through the elements in multistage circuit . . . . .	27
Exa 4.1	Calculate the small signal voltage gain of a bipolar transistor . . . . .	29
Exa 4.2	Determine the small signal voltage gain . . . . .	30
Exa 4.4	Determine the small signal voltage gain . . . . .	30
Exa 4.5	Determine the small signal voltage gain of a common emitter circuit . . . . .	31
Exa 4.7	Determine the small signal voltage gain of a common emitter circuit . . . . .	32
Exa 4.8	Determine the dc and ac load lines . . . . .	33
Exa 4.9	Determine the maximum symmetrical swing	33
Exa 4.10	Calculate the small signal voltage gain of an emitter circuit . . . . .	34

Exa 5.1	Calculate the current in an n channel MOSFET . . . . .	36
Exa 5.2	Determine the source to drain voltage required to bias p channel MOSFET . . . . .	36
Exa 5.3	Calculate the drain current and drain to source voltage of circuit . . . . .	37
Exa 5.4	Calculate the drain current and drain to source voltage of circuit . . . . .	37
Exa 5.6	Design the dc bias of a MOSFET circuit to produce specified drain current . . . . .	38
Exa 5.7	Design a MOSFET circuit biased with a constant current source . . . . .	39
Exa 5.8	Calculate the characteristics of a circuit containing an enhancement load device . . . . .	39
Exa 5.10	Calculate the characteristics of a circuit containing a depletion load device . . . . .	40
Exa 5.11	Determine the dc transistor currents and voltages in a circuit containing a depletion load device . . . . .	41
Exa 5.13	Determine the currents and voltages in a MOSFET constant current source . . . . .	41
Exa 5.14	Design the size of a power MOSFET to meet the specification of particular switch application . . . . .	42
Exa 5.16	Calculate Id and Vds in an n channel pn JFET	43
Exa 5.17	Design the dc bias of a JFET circuit . . . . .	43
Exa 5.19	Calculate the quiscent current and voltage values . . . . .	44
Exa 5.20	Design a circuit with an enhancement mode MESFET . . . . .	44
Exa 6.1	Calculate the transconductance of an n channel MOSFET . . . . .	46
Exa 6.2	Determine the small signal voltage gain of a MOSFET . . . . .	46
Exa 6.3	Determine the small signal voltage gain and input and output resistance of a common source amplifier . . . . .	47

Exa 6.4	Design the bias of a MOSFET such that the Q point is in the middle of saturation . . . . .	48
Exa 6.6	Determine the small signal voltage gain of a circuit . . . . .	49
Exa 6.7	Determine the small signal voltage gain of a circuit . . . . .	50
Exa 6.9	Calculate the output resistance of a source follower circuit . . . . .	51
Exa 6.11	Design the small signal voltage gain of an NMOS amplifier . . . . .	51
Exa 6.12	Determine the small signal voltage gain of a circuit . . . . .	52
Exa 6.13	Determine the small signal voltage gain of a circuit . . . . .	52
Exa 6.14	Design the biasing of a multistage MOSFET	53
Exa 6.15	Design the biasing of cascade circuit . . . . .	54
Exa 6.17	Determine the small signal voltage gain of a circuit . . . . .	55
Exa 6.18	Determine the small signal voltage gain of a circuit . . . . .	56
Exa 6.19	Design a JFET source follower . . . . .	57
Exa 7.1	Determine the corner frequencies and maximum magnitude asymptotes . . . . .	58
Exa 7.2	Determine the corner frequencies and bandwidth . . . . .	59
Exa 7.3	Determine the corner frequencies and maximum gain . . . . .	59
Exa 7.4	Design the circuit . . . . .	60
Exa 7.5	Determine 3dB frequency . . . . .	61
Exa 7.6	Determine the corner frequencies and maximum gain . . . . .	62
Exa 7.7	Determine the mid gain corner frequencies and bandwidth of a circuit . . . . .	62
Exa 7.8	Determine the corner frequencies and limiting horizontal asymptotes . . . . .	64
Exa 7.9	Determine 3dB frequency . . . . .	65
Exa 7.10	Calculate bandwidth and capacitance . . . . .	65
Exa 7.12	Determine the unity gain bandwidth . . . . .	66

Exa 7.13	Determine the Miller capacitance and cutoff frequency . . . . .	66
Exa 7.14	Determine the upper corner frequency and midband gain . . . . .	66
Exa 7.15	Determine the upper corner frequency and midband gain . . . . .	67
Exa 7.16	Determine the upper corner frequency and midband gain . . . . .	69
Exa 7.17	Determine the frequency of a zero and a pole . . . . .	70
Exa 8.2	Determine the maximum power dissipation . . . . .	72
Exa 8.3	Determine the maximum safe power dissipation . . . . .	73
Exa 8.7	Determine the required biasing in MOSFET class AB . . . . .	73
Exa 8.8	Design a transformer coupled emitter follower amplifier . . . . .	74
Exa 8.9	Design the class AB output stage . . . . .	75
Exa 8.11	Determine the currents and the current gain . . . . .	76
Exa 9.5	Determine a load current in a voltage to current converter . . . . .	78
Exa 9.9	Determine the time constant . . . . .	79
Exa 10.1	Design a two transistor current source . . . . .	80
Exa 10.2	Determine the change in load current . . . . .	80
Exa 10.4	Design a Widlar current source . . . . .	81
Exa 10.5	Determine the change in load current . . . . .	82
Exa 10.6	Design a generalized current mirror . . . . .	83
Exa 10.7	Design a MOSFET current source . . . . .	83
Exa 10.8	Compare the output resistances . . . . .	84
Exa 10.9	Determine the currents and voltages . . . . .	84
Exa 10.10	Calculate the open circuit voltage gain . . . . .	85
Exa 10.11	Calculate the small signal voltage gain . . . . .	86
Exa 10.12	Calculate the small signal voltage gain . . . . .	86
Exa 11.1	Determine the quiescent collector current and collector emitter voltage . . . . .	88
Exa 11.3	Determine the differential and common mode gains . . . . .	89
Exa 11.7	Determine the CMRR of a differential amplifier . . . . .	89

Exa 11.8	Design a bipolar source . . . . .	90
Exa 11.9	Determine the differential and common mode input resistance . . . . .	90
Exa 11.10	Calculate the dc characteristics of a MOS-FET diff amp . . . . .	91
Exa 11.11	Compare the forward transconductance . .	92
Exa 11.12	Determine the differential mode voltage gain common mode voltage gain CMRR . . . .	92
Exa 11.13	Determine the differential mode voltage gain . .	93
Exa 11.15	Determine the differential mode voltage gain . .	93
Exa 11.16	Calculate the input resistance and the small signal voltage gain . . . . .	94
Exa 11.17	Calculate the output resistance . . . . .	95
Exa 11.19	Determine the differential mode voltage gain . .	96
Exa 11.20	Determine the zero and pole frequencies . .	97
Exa 12.1	Calculate the feedback transfer function . .	98
Exa 12.2	Calculate the percent change in the closed loop gain $A_f$ . . . . .	98
Exa 12.3	Determine the bandwidth of a feedback amplifier . . . . .	99
Exa 12.5	Determine the input resistance and output resistance . . . . .	99
Exa 12.6	Determine the input resistance and output resistance . . . . .	100
Exa 12.7	Determine the expected input resistance . .	100
Exa 12.11	Determine the transconductance gain of a transistor feedback circuit . . . . .	101
Exa 12.16	Determine the loop gain . . . . .	102
Exa 12.19	Determine the stability of an amplifier . .	102
Exa 12.22	Determine the shift in the 3dB frequency . .	103
Exa 12.23	Determine the shift in the 3dB frequency . .	103
Exa 13.1	Calculate the dc currents . . . . .	105
Exa 13.2	Calculate the bias currents . . . . .	106
Exa 13.3	Calculate the bias currents . . . . .	106
Exa 13.4	Determine the small signal differential voltage gain . . . . .	107
Exa 13.5	Determine the small signal voltage gain . .	109
Exa 13.6	Calculate the output resistance . . . . .	110

Exa 13.7	Determine the dominant pole frequency of the 741 op amp . . . . .	111
Exa 13.9	Determine the small signal voltage gain . . . . .	111
Exa 13.10	Determine the differential mode voltage gain . . . . .	112
Exa 13.12	Determine the small signal voltage gain . . . . .	113
Exa 13.13	Determine the small signal voltage gain . . . . .	114
Exa 13.14	Determine the dominant pole frequency and unity gain bandwidth . . . . .	114
Exa 14.2	Determine the closed loop input resistance . . . . .	116
Exa 14.3	Determine the closed loop input resistance . . . . .	116
Exa 14.5	Determine the unity gain bandwidth and the closed loop gain . . . . .	117
Exa 14.6	Calculate the slew rate of the 741 op amp . . . . .	117
Exa 14.7	Determine the small signal bandwidth of an amplifier and full power bandwidth . . . . .	118
Exa 14.8	Calculate the offset voltage in bipolar diff amp . . . . .	118
Exa 14.10	Calculate the offset voltage in MOSFET diff amp . . . . .	118
Exa 14.11	Determine the range of voltage produced by an offset voltage compensation network . . . . .	119
Exa 14.13	Determine the bias current effect . . . . .	119
Exa 15.2	Determine the clock frequency . . . . .	121
Exa 15.3	Design a one pole low pass switched capacitor filter . . . . .	121
Exa 15.4	Determine the oscillation frequency and required amplifier gain . . . . .	122
Exa 15.6	Determine the hysteresis width of a particular Schmitt trigger . . . . .	122
Exa 15.7	Design a Schmitt trigger circuit . . . . .	123
Exa 15.10	Design the 555IC as a monostable multivibrator . . . . .	123
Exa 15.13	Design the supply voltage . . . . .	123
Exa 15.14	Determine the output resistance and load regulation . . . . .	124
Exa 15.15	Determine the output resistance and variation in output voltage . . . . .	124

Exa 15.16	Determine the bias current temperature compensated reference voltage and required resistor . . . . .	125
Exa 16.3	Design the aspect ratio and determine the power dissipation . . . . .	126
Exa 16.4	Design the aspect ratio and determine the power dissipation . . . . .	127
Exa 16.5	Determine the noise margin of an inverter with enhancement load . . . . .	127
Exa 16.9	Determine the critical voltage on the voltage transfer curve of a CMOS inverter . . . . .	128
Exa 16.10	Calculate the power dissipation in CMOS inverter . . . . .	129
Exa 16.11	Determine the noise margins of a CMOS inverter . . . . .	129
Exa 16.15	Determine the currents voltages and power dissipation in two NMOS SPAM cells . . . . .	130
Exa 17.1	Calculate the currents and voltages in the basic differential amplifier circuit used as digital circuit . . . . .	132
Exa 17.2	Calculate the currents resistors and logic 0 values in the basic ECL logic gate . . . . .	133
Exa 17.3	Design the reference position of the ECL circuit . . . . .	134
Exa 17.4	Calculate the power dissipated in the ECL logic circuit . . . . .	135
Exa 17.5	Calculate minimum fanout of ECL logic gate . . . . .	135
Exa 17.7	Analyze the modified ECL logic gate . . . . .	136
Exa 17.9	Calculate the currents and voltages for the basic TTL NAND circuit . . . . .	137
Exa 17.11	Determine the currents in a Schottky transistor . . . . .	138
Exa 17.12	Calculate the power dissipation in a low power Schottky TTL circuit . . . . .	139

# Chapter 1

## Semiconductor materials and diodes

Scilab code Exa 1.1 Calculate intrinsic carrier concentration in silicon

```
1 clear;
2 clc;
3 //Example 1.1
4 T=300; //(( K )temperature)
5 //for silicon
6 B=5.23*10^(15); //Constant ( per centimeter cube
degree kelvin)
7 Eg=1.1; //bandgap energy in electrovolt(eV)
8 k=86*10^(-6); //Boltzmann's constant(eV per degree
kelvin)
9 n_i=B*T^(3/2)*exp(-Eg/(2*k*T)); //intrinsic carrier
concentration
10 printf('intrinsic carrier concentration=%f cm^-3',
n_i);
```

---

Scilab code Exa 1.2 Calculate thermal equilibrium electron and hole concentrations

```

1 clear;
2 clc;
3 //Example 1.2
4 T=300; //( K ) Given Temperature
5 Nd=10^16; //(cm^-3) Donor concentration
6 n_i=1.5*10^10; //(cm^-3) intrinsic carrier
    concentration
7 //since Nd>>n_i
8 n_o=10^16; //(cm^-3) electron concentration
9 //by using formula :: n_i^2=n_o*p_o
10 p_o=(n_i)^2/Nd; //hole concentration
11 printf ('\nelectron concentration=%e cm^-3',n_o);
12 printf ('\n hole concentration =%e cm^-3',p_o);

```

---

**Scilab code Exa 1.3** Calculate the built in potential barrier of a pn junction

```

1 clear;
2 clc;
3 //Example1.3
4 T=300; //( K ) Given Temperature
5 Na=10^16; //(cm^-3) Acceptor concentration in p region
6 Nd=10^17; //(cm^-3) Donor concentration in n region
7 n_i=1.5*10^10; //(cm^-3) intrinsic carrier
    concentration
8 V_T=0.026; //(Volt) terminal voltage
9 //built-in potential
10 V_bi=V_T*log(Na*Nd/(n_i)^2);
11 printf ('\nthe built-in potential=%f V',V_bi)

```

---

**Scilab code Exa 1.4** Calculate the junction capacitance of a pn junction

```

1 clear;
2 clc;

```

```

3 //Example 1.4
4 T=300; //( K ) Given Temperature
5 Na=10^16; //(cm^-3) Acceptor concentration in p region
6 Nd=10^15; //(cm^-3) Donor concentration in n region
7 n_i=1.5*10^10; //(cm^-3) intrinsic carrier
    concentration
8 C_jo=0.5; //(pF) junction capacitance at zero applied
    voltage
9 V_T=0.026; //(Volt) terminal voltage
10 //built-in potential
11 V_bi=V_T*log(Na*Nd/(n_i)^2);
12 disp(V_bi,"the built-in potential(V)")
13 //the junction capacitance for
14 V_R=1; //(V) reverse bias voltage
15 Cj=C_jo*(1+V_R/V_bi)^(-1/2);
16 printf('\nthe junction capacitance for V_R=1V=%f pF\
    ',Cj)
17 V_R=5; //(V) reverse bias voltage
18 Cj=C_jo*(1+V_R/V_bi)^(-1/2);
19 printf('\nthe junction capacitance for V_R=5V =%f pF
    ',Cj)

```

---

**Scilab code Exa 1.5 Determine the diode current in pn junction**

```

1 clear;
2 clc;
3 //Example 1.5
4 T=300; //( K ) Given Temperature
5 V_T=0.026; //(Volt) terminal voltage
6 Is=10^-11; //(mA) reverse bias saturation current
7 n=1; //emission coefficient
8 v_D=+0.7; //(V) applied voltage
9 //pn junction is forward biased
10 i_D=Is*(exp(v_D/V_T)-1); //diode current
11 printf('\ndiode current=%f mA\n',i_D)

```

```

12 v_D=-0.7; // (V) pn junction is reverse biased
13 Is=10^-14 //A;
14 i_D=Is*(exp(v_D/V_T)-1); // diode current
15 printf ('\n diode current=%e A', i_D)

```

---

**Scilab code Exa 1.6 Determine the diode voltage and current**

```

1 clear;
2 clc;
3 //Example 1.6
4 Is=10^-13; // (A) reverse saturation current
5 V_PS=5; // (V) applied voltage
6 R=2; // (KOhm) Resistance in circuit
7 V_T=0.026; // (Volt) terminal voltage
8 //V_PS=Is*R*(exp(V_D/V_T)-1)+V_D
9 //5=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
10 // let right side of equation be x=(10^-13)*(2000)*(
    exp(V_D/V_T)-1)+V_D
11 V_D=0.6; // (V)
12 x=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
13 // so the equation is not balanced
14 V_D=0.65; // (V)
15 x=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
16 // again equation is not balanced . solution for V_D
    is between 0.6V and 0.65V
17 V_D=0.619; // (V)
18 x=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
19 // essentially equal to the value of the left side of
    the equation i.e 5V
20 printf ('\n diode voltage=%f V', V_D)
21 I_D=(V_PS-V_D)/R; // (A) diode current
22 printf ('\n the diode current=%f mA', I_D)

```

---

### Scilab code Exa 1.7 Determine the diode voltage and current

```
1 clear;
2 clc;
3 //Example 1.7
4 //piecewise linear diode parameters
5 V_Y=0.6; //(V)
6 r_f=0.010; //(KOhm)
7 V_PS=5; //(V) applied voltage
8 R=2; //(KOhm) Resistance in circuit
9 I_D=(V_PS-V_Y)/(R+r_f); //(A) diode current
10 printf ('\nthe diode current=%f mA\n', I_D)
11 V_D=V_Y+I_D*r_f; //(V) diode voltage
12 printf ('\ndiode voltage=%f V', V_D)
```

---

### Scilab code Exa 1.9 Analysing the circuit

```
1 clear;
2 clc;
3 //Example 1.9
4 //circuit and diode parameters
5 V_PS=5; //(V)
6 R=5; //(KOhm)
7 V_Y=0.6; //(V)
8 V_T=0.026; //(Volt) terminal voltage
9 v_i=0.1/*sin (wt) Volt
10 //dc analysis
11 I_DQ=(V_PS-V_Y)/R;
12 printf ('\ndc quiescent current=%f mA\n', I_DQ)
13 V_O=I_DQ*R;
14 printf ('\ndc output voltage=%f V\n', V_O)
15 //ac analysis
16 V_PS=0;
17 //Kirchhoff voltage law equation becomes
18 //v_i=i_d*r_d+i_d*R
```

```

19 r_d=V_T/I_DQ // (Ohm) small signal diode diffusion
   resistance
20 i_d=v_i/(r_d+R); // ac diode current
21 printf ('\nac diode current=%fsin(wt) A\n',i_d)
22
23 v_o=i_d*R; // ac output voltage
24 printf ('\nac output voltage=%fsin(wt) V',v_o)

```

---

### Scilab code Exa 1.10 Calculate currents in a circuit

```

1 clear;
2 clc;
3 //Example 1.10
4 V_Y=0.7; // (V) cut in voltage for pn junction
5 r_f=0;
6 V_PS=4; // (V)
7 R1=4,R2=4 // (KOhm) from given circuit
8 I1=(V_PS-V_Y)/R1;
9 printf ('\ncurrent through pn junction diode=%.3f mA\n',
          I1)
10 V_Y=0.3; // (V) cut in voltage for Schottky diode
11 I2=(V_PS-V_Y)/R2;
12 printf ('\ncurrent through Schottky diode=%.3f mA\n',
          I2)

```

---

### Scilab code Exa 1.11 Design the value of resistance required to limit the current

```

1 clear;
2 clc;
3 //Example 1.11
4 V_Z=5.6; // (V) Zener diode breakdown voltage
5 r_z=0; // (Ohm) Zener resistance
6 I=3; // (mA) current in the diode

```

```
7 V_PS=10; // (V)
8 // I=(V_PS-V_Z)/R
9 R=(V_PS-V_Z)/I;
10 printf ('\\n resistance=%.3f KOhm\\n ',R)
```

---

# Chapter 2

## Diode Circuits

Scilab code Exa 2.1 Compare voltages and the transformer turns ratio in two full w

```
1 clear;
2 clc;
3 //Example 2.1
4 v_I=120; //(V)rms primary input
5 v_o=9; //(V)peak output voltage
6 V_Y=0.7; //(V)diode cut in voltage
7 //for center-tapped transformer circuit in fig.2.6(a)
    )
8 v_S=v_o+V_Y//(V)peak value of secondary voltage
9 printf ('\npeak value of secondary voltage=%f V\n', v_S)
10 v_S_rms=v_S/sqrt(2)//for a sinusoidal signal rms
    value of v_S
11 printf ('\nrms value of v_S=%f V\n', v_S_rms)
12 //let turns ratio of the primary to secondary
    winding be x=N1/N2
13 x=v_I/v_S_rms;
14 printf ('\nturns ratio=%f \n', x)
15 //for the bridge circuit in fig.2.7(a)
16 v_Sb=v_o+2*V_Y;//(V)peak value of secondary voltage
17 printf ('\npeak value of secondary voltage=%f V\n',
```

```

    v_Sb)
18 v_S_rms=v_Sb/sqrt(2); //for a sinusoidal signal rms
    value of v_S
19 printf ('\nrms value of v_S=%f V\n',v_S_rms)
20 //let turns ratio of the primary to secondary
    winding be x=N1/N2
21 x=v_I/v_S_rms;
22 printf ('\nturns ratio=%f\n',x)
23 //for center tapped rectifier
24 PIV=2*v_S-V_Y;
25 printf ('\npeak inverse voltage of a diode=%f V\n',
    PIV)
26 //for the bridge rectifier peak inverse voltage of a
    diode
27 PIV=v_Sb-V_Y;
28 printf ('\npeak inverse voltage of a diode=%.2f V\n',
    PIV)
29 //advantage of bridge rectifier over center tapped
    rectifier is it requies only half of the turns

```

---

**Scilab code Exa 2.2** Determine the capacitance required to yield a particular ripple

```

1 clear;
2 clc;
3 //Example 2.2
4 //full wave rectifier circuit with 60Hz input signal
5 V_M=10; //(V) peak output voltage
6 R=0.01; //(MOhm) output load resistance
7 f=60; //Hz
8 V_r=0.2; //(V) ripple voltage
9 C=V_M/(2*f*R*V_r); //capacitance
10 printf ('\ncapacitance=%f microF\n',C)

```

---

### Scilab code Exa 2.3 Design a full wave rectifier

```
1 clear;
2 clc;
3 //Example 2.3
4 V_0=12; // (V) peak output voltage
5 I_L=0.12; // (A) current delivered to the load
6 R=V_0/I_L;
7 printf ('\n effective load resistance=%f Ohm\n',R)
8 V_Y=0.7; // (V) diode cut in voltage
9 v_S=V_0+2*V_Y;
10 printf ('\n peak value of v_S=%f V\n',v_S)
11 v_Srms=v_S/sqrt(2);
12 printf ('\n rms voltage=%f V\n',v_Srms)
13 //let x=N1/N2
14 Vin=120; // (V) input line voltage
15 x=Vin/v_Srms;
16 printf ('\n turns ratio=%f \n',x)
17 VM=12; // (V)
18 Vr=5/100*VM;
19 printf ('\n ripple voltage=%f V\n',Vr)
20 f=60; // (Hz) input frequency
21 C=VM/(2*R*Vr*f);
22 printf ('\n filter capacitance=%f F\n',C)
23 i_Dmax=(VM/R)*(1+2*pi*sqrt(VM/(2*Vr)));
24 printf ('\n peak diode current=%f A\n',i_Dmax)
25 R=0.1; //Kohm
26 i_Davg=(1/(2*pi))*sqrt(2*Vr/VM)*((VM/R)*(1+pi*sqrt
    (VM/(2*Vr))));
27 printf ('\n average diode current=%f mA\n',i_Davg)
28 PIV=v_S-V_Y;
29 printf ('\n peak inverse voltage=%f V\n',PIV)
```

---

### Scilab code Exa 2.5 Determine the percent regulation of a voltage regulator

```

1 clear;
2 clc;
3 //Example 2.5
4 rZ=4; //(Ohm) Zener resistance
5 V_Lnom=9; //(V) nominal output voltage
6 Izmax=0.3; //(A) maximum zener diode current
7 Izmin=0.03; //(A) minimum zener diode current
8 V_Lmax=V_Lnom+Izmax*rZ
9 V_Lmin=V_Lnom+Izmin*rZ
10 //percent regulation R
11 R=((V_Lmax-V_Lmin)/V_Lnom)*100;
12 printf ('\npercent regulation=%0.1f \n',R)

```

---

**Scilab code Exa 2.8 Determine the output voltage and diode currents**

```

1 clear;
2 clc;
3 //Example 2.8
4 R1=5; R2=10; //(KOhm)
5 V_Y=0.7; //(V) diode cut in voltage
6 V1=5; V2=-5; //(V)
7 vt=0; //(V)
8 //asssuming initially diode D1 is off
9 //iR1=iD2=iR2=V1-V2-V_Y/(R1+R2)
10 iD2=(V1-V2-V_Y)/(R1+R2);
11 printf ('\n diode current=%0.2f mA\n', iD2)
12 iR1=iD2;
13 vo=V1-iR1*R1;
14 printf ('\n output voltage=%0.2f V\n', vo)
15 v=vo-V_Y; //v=v'
16 printf ('\n Voltage=%0.1f V\n', v)
17 vt=4; //(V) fig .2.33
18 //both D1 and D2 are on
19 vo==vt;
20 vo=4;

```

```

21 iD2=(V1-vo)/R1;
22 printf ('\n diode current=%f mA\n', iD2)
23 iR1==iD2;
24 v=vo-V_Y;
25 printf ('\n V=%f V\n', v)
26 iR2=(v-V2)/R2;
27 printf ('\n iR2=%f mA\n', iR2)
28 iD1=iR2-iD2;
29 printf ('\n current through D1=%f mA\n', iD1)

```

---

**Scilab code Exa 2.10** Calculate the photocurrent generated in a photodiode

```

1 clear;
2 clc;
3 //Example 2.10
4 n=1; //quantum efficiency
5 A=10^-2; //cm^2 junction area
6 p=5*10^17; // (cm^-2-s^-1) incident photon flux
7 e=1.6*10^-16; //charge of an electron
8 Iph=n*e*p*A;
9 printf ('\n photocurrent=%0.1 f mA\n', Iph)

```

---

**Scilab code Exa 2.11** Determine the value of R required to limit the current in circuit

```

1 clear;
2 clc;
3 //Example 2.11
4 I=0.01; //(A) diode current
5 V_Y=1.7; //(V) forward bias voltage drop
6 Vt=0.2; //(V)
7 R=(5-V_Y-Vt)/I;
8 printf ('\n resistance=%0.1 f Ohm', R)

```

---

# Chapter 3

## The Bipolar Junction Transistor

Scilab code Exa 3.1 Calculate the collector and emitter currents

```
1 clear;
2 clc;
3 //Example 3.1
4 //let beta be "b"
5 b=150; //common emitter current gain
6 iB=15*10^-3; //(mA) base current
7 //assume transistor biased in forward active mode
8 iC=b*iB;
9 printf ('\ncollector current=%.2f mA\n',iC)
10 iE=(1+b)*iB;
11 printf ('\nemitter current=% .2f mA\n',iE)
12 a=b/(1+b);
13 printf ('\ncommon base current gain=% .3f \n',a)
```

---

Scilab code Exa 3.2 Calculate the breakdown voltage of a transistor

```

1 clear;
2 clc;
3 //Example 3.2
4 b=100; //common emitter current gain
5 BVcbo=120; //(V) break down voltage of the B-C
    junction
6 n=3; //empirical constant
7 BVceo=BVcbo/(b)^(1/n);
8 printf ('\nbreakdown voltage=%f V\n',BVceo)

```

---

**Scilab code Exa 3.3 Calculate the base collector and emitter currents and ce voltage**

```

1 clear;
2 clc;
3 //Example 3.3
4 Vbb=4; //(V)
5 Rb=220 /(KOhm) ;
6 Rc=2; /(KOhm)
7 Vcc=10; /(V)
8 Vbe=0.7; /(V)
9 b=200;
10 //from fig .3.19(b)
11 Ib=(Vbb-Vbe)/Rb;
12 printf ('\nbase current=%f mA\n',Ib)
13 Ic=b*Ib;
14 printf ('\ncollector current=%f mA\n',Ic)
15 Ie=(1+b)*Ib;
16 printf ('\nemitter current=%f mA\n',Ie)
17 Vce=Vcc-Ic*Rc;
18 printf ('\ncollector emitter voltage=%f V\n',Vce)

```

---

**Scilab code Exa 3.4 Analyse the common emitter circuit with pnp transistor**

```

1 clear;
2 clc;
3 //Example 3.4
4 Vbb=1.5; //(V)
5 Rb=580; // (KOhm)
6 Veb=0.6; //(V)
7 Vcc=5; //(V)
8 b=100;
9 // writing Kirchhoff voltage law equation around E-B
   loop
10 Ib=(Vcc-Veb-Vbb)/Rb;
11 printf ('\nbase current=%f mA\n', Ib)
12 Ic=b*Ib;
13 printf ('\ncollector current=%f mA\n', Ic)
14 Ie=(1+b)*Ib;
15 printf ('\nemitter current=%f mA\n', Ie)
16 Vec=(1/2)*Vcc;
17 printf ('\nce voltage=%f V\n', Vec)
18 Rc=(Vcc-Vec)/Ic;
19 printf ('\ncollector resistance=%f KOhm\n', Rc)

```

---

Scilab code Exa 3.5 Calculate the currents and voltages in a circuit

```

1 clear;
2 clc;
3 //Example 3.5
4 b=100;
5 Vbe=0.7; //(V)
6 Vce=0.2; //(V)
7 Vbb=8; //(v)
8 Rb=220; // (KOhm)
9 Ib=(Vbb-Vbe)/Rb
10 printf ('\nbase current=%f mA\n', Ib)
11 //transistor in active region
12 Ic=b*Ib;

```

```

13 printf ('\n collector current=%f mA\n', Ic)
14 Vcc=10; // (V)
15 Rc=4; // (KOhm)
16 Vce=Vcc-Ic*Rc;
17 printf ('\n collector emitter voltage=%f V\n', Vce)
18 //saturation
19 Vce=0.2; // (V)
20 Ic=(Vcc-Vce)/Rc;
21 printf ('\n saturation collector current=%f mA\n', Ic
    )
22 x=Ic/Ib
23 //which is <b
24 Ie=Ic+Ib;
25 printf ('\n emitter current=%f mA\n', Ie)

```

---

Scilab code Exa 3.6 Calculate the characteristics of a circuit containing an emitter

```

1 clear;
2 clc;
3 //Example 3.6
4 Vbe=0.7;
5 b=75;
6 //Q point values::
7 //using KVL eq around the B-E loop
8 //Vbb=Ib*Re+Vbe+Ie*Re
9 //assuming transistor is in forward biased mode we
   can write Ie=(1+b)*Ib
10 Vbb=6;
11 Rb=25; //KOhm
12 Re=0.6; //KOhm
13 Ib=(Vbb-Vbe)/(Rb+(1+b)*Re);
14 printf ('\n base current=%f mA\n', Ib)
15 Ic=b*Ib;
16 printf ('\n collector current=%f mA\n', Ic)
17 Ie=(1+b)*Ib;

```

```

18 printf ('\n emitter current=%0.2f mA\n', Ie)
19 Vcc=12;
20 Rc=0.4;
21 Vce=Vcc-Ic*Rc-Ie*Re;
22 printf ('\n collector emitter voltage=%0.2f V\n', Vce)
23 //load line::
24 //using KVL law around C-E loop
25 //Vce=Vcc-(Ic*(Rc+((1+B)/B)*Re));
26 Ic=[0,12,5.63]
27 Vce=12-Ic*1;
28 xset ('window',1)
29 plot2d(Vce,Ic,style=3)
30 title("load line")
31 xlabel("Vce")
32 ylabel("Ic")

```

---

### Scilab code Exa 3.7 Calculate the characteristics of a circuit

```

1 clear;
2 clc;
3 //Example 3.7
4 Vbe=0.65;
5 Vcc=5;
6 Rc=0.5; //KOhm
7 b=100;
8 V1=-5;
9 Re=1; //KOhm
10 // Q-point values :: writing KVL eq around B-E loop
11 Ie=(-V1-Vbe)/Re;
12 printf ('\n emitter current=%0.2f mA\n', Ie)
13 Ib=(Ie/(1+b));
14 printf ('\n base current=%0.2f mA\n', Ib)
15 Ic=(b/(1+b))*Ie;
16 printf ('\n collector current=%0.2f mA\n', Ic)
17 Vce=Vcc-Ic*Rc-Ie*Re-V1;

```

```

18 printf ('\n collector emitter voltage=%f V\n',Vce)
19 //load line :: 
20 //Vce=Vcc-V1-(Ic*(Rc+((1+B)/B)*Re));
21 Vce=[0,2,,3.5,4,6,8,10]
22 Ic=(10-Vce)/1.51;
23 xset ('window ',1)
24 plot2d(Vce,Ic,style=3,rect=[0,0,10,8])
25 title("load line")
26 xlabel("Vce")
27 ylabel("Ic")

```

---

**Scilab code Exa 3.9 Calculate the characteristics of an npn bipolar circuit**

```

1 clear;
2 clc;
3 //Example 3.9
4 b=100;
5 Vbe=0.7;
6 V1=-5;
7 V2=12;
8 Rb=10;
9 Re=5;
10 Rc=5;
11 Rl=5;
12 //Q point values:: using KVL eq around B-E loop
13 Ib=-(V1+Vbe)/(Rb+(1+b)*Re);
14 printf ('\nbbase current=%f mA\n',Ib)
15 Ic=b*Ib;
16 printf ('\n collector current=%f mA\n',Ic)
17 Ie=(1+b)*Ib;
18 printf ('\n emitter current=%f mA\n',Ie)
19 //at collector node we can write Ic=(V2-Vo)/Rc-Vo/Rl
20 Vo=(V2/Rc-Ic)*Rc*Rl/(Rc+Rl);
21 printf ('\n output voltage=%0.3f V\n',Vo)
22 Vce=Vo-Ie*Re-V1;

```

```

23 printf ('\ncollector emitter voltage=%f V\n',Vce)
24 //load line::
25 Rth=Rl*Rc/(Rl+Rc);
26 printf ('\nThevenin rquivalent resistance=%f KOhm\n',
27 Rth)
27 Vth=(Rl/(Rl+Rc))*V2;
28 printf ('\nThevenin equivalent voltage=%f V\n',Vth)
29 // fig .3.36(c) KVL law
30 //Vce=6-V1-Ic*Rth-Ie*Re;
31 Vce=[0,2,4.7,3.5,4,6,8,10]
32 Ic=(11-Vce)/7.5;
33 xset ('window',1)
34 plot2d(Vce,Ic,style=3,rect=[0,0,12,2])
35 title("load line")
36 xlabel("Vce")
37 ylabel("Ic")

```

---

**Scilab code Exa 3.10** Calculate the currents output voltage and power dissipation

```

1 clear;
2 clc;
3 //Example 3.10
4 Rb=0.24;
5 Vcc=12;
6 Vbe=0.7;
7 Vce=0.1;
8 b=75;
9 Rc=5; //Ohm
10 //for Vt=0 ,transistor is cut off , Ib=Ic=0,Vo=Vcc=12
11 //V, power dissipation is zero
11 Vt=12; //(V)
12 Ib=(Vt-Vbe)/Rb;
13 printf ('\nbase current=%0.3f mA\n',Ib)
14 Ic=(Vcc-Vce)/Rc;
15 printf ('\ncollector current=%0.2f A\n',Ic)

```

```

16 Ib=0.0471; //A
17 x=Ic/Ib
18 //since Ic/Ib<b transistor is in saturation
19 //Vo==Vcc;
20 Vo=0.1;
21 printf( '\noutput voltage=%0.2f V\n' ,Vo)
22 P=Ic*Vce+Ib*Vbe;
23 printf( '\npower dissipation=%0.3f W\n' ,P)

```

---

### Scilab code Exa 3.13 Design the circuit

```

1 clear;
2 clc;
3 //Example 3.13
4 b=100;
5 Vcc=12;
6 Vbe=0.7;
7 Icq=1; //mA
8 Vceq=6;
9 Rc=(Vcc-Vceq)/Icq;
10 printf( '\ncollector resistance=%.3f KOhms\n' ,Rc)
11 Ibq=Icq/b;
12 printf( '\nbase current=%0.3f mA\n' ,Ibq)
13 Rb=(Vcc-Vbe)/Ibq;
14 printf( '\nbase resistance=%.3f KOhms\n' ,Rb)

```

---

### Scilab code Exa 3.14 Analyze a circuit using voltage divider bias circuit and determine

```

1 clear;
2 clc;
3 //Example 3.14
4 R1=56;
5 R2=12.2;

```

```

6  Rc=2;
7  Re=.4;
8  Vcc=10;
9  Vbe=0.7;
10 b=100;
11 // fig .3.53(b)
12 Rth=R2*R1/(R1+R2);
13 printf ('\nThevenin rquivalent resistance=%0.1f KOhm\
n',Rth)
14 Vth=(R2/(R1+R2))*Vcc;
15 printf ('\nThevenin equivalent voltage=%0.2f V\n',Vth
)
16 Ibq=(Vth-Vbe)/(Rth+(1+b)*Re);
17 printf ('\nbase current=%f mA\n',Ibq)
18 Icq=b*Ibq;
19 printf ('\ncollector current=%f mA\n',Icq)
20 Ieq=(1+b)*Ibq;
21 printf ('\nemitter current=%f mA\n',Ieq)
22 Vceq=Vcc-Icq*Rc-Ieq*Re;
23 printf ('\ncollector emitter voltage=%f V\n',Vceq)
24 b=[50,100,150]
25 for x=b
26 Ibq=(Vth-Vbe)/(Rth+(1+x)*Re);
27 disp("Ibeq ,Iceq ,Ieq ,Vceq")
28 disp(Ibq)
29 Icq=x*Ibq;
30 disp(Icq)
31 Ieq=(1+x)*Ibq;
32 disp(Ieq)
33 Vceq=Vcc-Icq*Rc-Ieq*Re;
34 disp(Vceq)
35 disp(""))
36 end

```

---

Scilab code Exa 3.15 Design a bias stable circuit

```

1 clear;
2 clc;
3 //Example 3.15
4 Vcc=5;
5 Rc=1; //KOhm
6 Vbe=0.7;
7 b=120;
8 Vceq=3;
9 Re=.510;
10 Icq=(Vcc-Vceq)/(Rc+Re);
11 printf ('\n collector current=%.3f mA\n', Icq)
12 Ibq=Icq/b;
13 printf ('\n base current=%0.3f mA\n', Ibq)
14 //for bias stable circuit
15 Rth=0.1*(1+b)*Re;
16 printf ('\n Thevenin equivalent resistance=%.1f KOhm\n
', Rth)
17 //Ibq=(Vth-Vbe)/(Rth+(1+b)*Re)
18 Vth=Ibq*(Rth+(1+b)*Re)+Vbe;
19 printf ('\n Thevenin equivalent voltage=%.2f V\n', Vth)
20 //Vth=(R2/(R1+R2))*Vcc
21 // let x=(R2/(R1+R2))
22 x=Vth/Vcc
23 //Rth=6050=R1*x
24 R1=6.05/x;
25 printf ('\n R1=%.1f KOhms\n', R1)
26 R2=x*R1/(1-x);
27 printf ('\n R2=%0.1f KOhms\n', R2)

```

---

**Scilab code Exa 3.16 Determine the currents in a two transistor current source**

```

1 clear;
2 clc;
3 //Example 3.16
4 R1=10;

```

```

5 b=50;
6 Vbe=0.7;
7 V1=-5;
8 I1=-(V1+Vbe)/R1;
9 printf ('\nreference current=%f mA\n',I1)
10 Iq=I1/(1+2/b);
11 printf ('\nbias current=%f mA\n',Iq)
12 // Ib=Ib1=Ib2
13 Ib=Iq/b;
14 printf ('\nbase current=%f mA\n',Ib)

```

---

**Scilab code Exa 3.17** Calculate the dc voltages at each node and the dc currents th

```

1 clear;
2 clc;
3 //Example 3.17
4 Vbe=0.7;
5 Vcc=10;
6 V2=5;
7 b=100;
8 R1=100;
9 R2=50;
10 Re1=2;
11 Rth=R2*R1/(R1+R2);
12 printf ('\nThevenin equivalent resistance=%f KOhm\n',Rth)
13 Vth=(R2/(R1+R2))*Vcc-V2;
14 printf ('\nThevenin equivalent voltage=%f V\n',Vth)
15 //Vth=Ib1*Rth+Vbe+Ie1*Re1-5 and Ie1=(1+b)*Ib1
16 Ib1=(Vth+5-Vbe)/(Rth+(1+b)*Re1);
17 printf ('\nIb1=%f mA\n',Ib1)
18 Ic1=b*Ib1;
19 printf ('\nIc1=%f mA\n',Ic1)
20 Ie1=(1+b)*Ib1;
21 printf ('\nIe1=%f mA\n',Ie1)

```

```

22 //summing the currents at the collector of Q1, Ir1+
23 Ib2=Ic1
24 //(5-Vc1)/Rc1+Ib2=Ic1
25 // also Ib2=Ie2/(1+b)=(5-(Vc1+0.7))/(1+b)*Re2
26 Rc1=5;
27 Re1=2;
28 Re2=2;
29 Rc2=1.5;
30 Vc1=Rc1*(1+b)*Re2*((5/Rc1)+(4.3/((1+b)*Re2))-Ic1)
   /(((1+b)*Re2)+Rc1);
31 printf ('\nVc1=%f V\n',Vc1)
32 Ir1=(5-Vc1)/Rc1;
33 Ve2=Vc1+Vbe;
34 printf ('\nVe2=%f V\n',Ve2)
35 Ie2=(5-Ve2)/Re1;
36 printf ('\nIe2=%f mA\n',Ie2)
37 Ic2=Ie2*b/(1+b);
38 printf ('\nIc2=%f mA\n',Ic2)
39 Ib2=Ie2/(1+b);
40 printf ('\nIb2=%f mA\n',Ib2)
41 Ve1=Ie1*Re1-5;
42 printf ('\nVe1=%f V\n',Ve1)
43 Vc2=Ic2*Rc2-5;
44 printf ('\nVc2=%f V\n',Vc2)
45 Vce1=Vc1-Ve1;
46 printf ('\nVce1=%f V\n',Vce1)
47 Vec2=Ve2-Vc2;
48 printf ('\nVec2=%f V\n',Vec2)

```

---

# Chapter 4

## Basic BJT Amplifiers

Scilab code Exa 4.1 Calculate the small signal voltage gain of a bipolar transistor

```
1 clear;
2 clc;
3 //Example 4.1
4 b=100;
5 Vcc=12;
6 Vbe=0.7;
7 Rc=6;
8 Rb=50;
9 Vbb=1.2;
10 //dc solution
11 Ibq=(Vbb-Vbe)/Rb;
12 printf ('\nbase current=%f mA\n',Ibq)
13 Icq=b*Ibq;
14 printf ('\ncollector current=%f mA\n',Icq)
15 Vceq=Vcc-Icq*Rc;
16 printf ('\ncollector emitter voltage=%f V\n',Vceq)
17 //transistor is forward biased
18 //ac solution
19 V_T=0.026; //(V)
20 //small signal hybrid pi parameters
21 r_pi=b*V_T/Icq;
```

```

22 printf ('\nsmall signal resistance=%f KOhm\n', r_pi)
23 g_m=Icq/V_T;
24 printf ('\ntransconductance=%f mA/V\n', g_m)
25 //Av=Vo/Vs=-(g_m*Rc)*r_pi/(r_pi+Rb)
26 Av=-(g_m*Rc)*r_pi/(r_pi+Rb);
27 printf ('\nsmall signal voltage gain=%f\n', Av)

```

---

### Scilab code Exa 4.2 Determine the small signal voltage gain

```

1 clear;
2 clc;
3 //Example 4.2
4 V_pi=50; //(V)
5 Icq=1; //(mA)
6 ro=V_pi/Icq;
7 printf ('\nsmall signal output resistance=%f KOhm\n
      ', ro)
8 Rc=6;
9 g_m=38.5;
10 r_pi=2.6;
11 Rb=50;
12 Av=-(g_m)*(Rc*ro/(Rc+ro))*r_pi/(r_pi+Rb);
13 printf ('\nsmall signal voltage gain=%f \n', Av)

```

---

### Scilab code Exa 4.4 Determine the small signal voltage gain

```

1 clear;
2 clc;
3 //Example 4.4
4 b=100;
5 Vbe=0.7;
6 Va=100;
7 V_T=0.026; //(V)

```

```

8 //from dc analysis
9 Icq=0.95;
10 Vceq=6.31;
11 //ac analysis
12 r_pi=b*V_T/Icq;
13 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)
14 g_m=Icq/V_T;
15 printf ('\ntransconductance=%f mA/V\n',g_m)
16 Rs=0.5;
17 Rc=6;
18 ro=Va/Icq;
19 printf ('\nro=%f KOhm\n',ro)
20 Av=-g_m*(5.9*r_pi/(5.9+r_pi))/((5.9*r_pi/(r_pi+5.9))
   +Rs)*ro*Rc/(ro+Rc);
21 printf ('\nsmall signal voltage gain=%f \n',Av)
22 Ri=5.9*r_pi/(r_pi+5.9);
23 printf ('\ninput resistance=%f KOhm\n',Ri)
24 Ro=ro*Rc/(ro+Rc);
25 printf ('\noutput resistance=%f KOhm\n',Ro)

```

---

**Scilab code Exa 4.5** Determine the small signal voltage gain of a common emitter ci

```

1 clear;
2 clc;
3 //Example 4.5
4 b=100;
5 Vbe=0.7;
6 Rc=2;
7 Rs=0.5;
8 Icq=2.16;
9 V_T=0.026; //(V)
10 Vceq=4.8
11 //ac solution
12 r_pi=b*V_T/Icq;
13 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)

```

```

14 g_m=Icq/V_T;
15 printf ('\ntransconductance=%3f mA/V\n',g_m)
16 //since Va=infinity ,ro=Va/Icq is also infinity
17 Re=0.4;
18 Rib=r_pi+(1+b)*Re;
19 printf ('\ninput resistance to the base=%2f KOhm\n',
          Rib)
20 //Ri=R1||R2||Rib
21 Ri=10*Rib/(10+Rib);
22 printf ('\ninput resistance to the amplifier=%3f
          KOhm\n',Ri)
23 Av=-(1/(r_pi+(1+b)*Re))*b*Rc*Ri/(Ri+Rs);
24 printf ('\nsmall signal voltage gain=%2f \n',Av)
25 //by approximate expression
26 Av=-Rc/Re;
27 printf ('\nsmall signal voltage gain=%3f \n',Av)

```

---

**Scilab code Exa 4.7** Determine the small signal voltage gain of a common emitter ci

```

1 clear;
2 clc;
3 //Example 4.7
4 Iq=0.5;
5 b=120;
6 Va=80;
7 V_T=0.026; //(V)
8 rc=120; //small signal collector resistance (KOhm)
9 //Icq=Iq
10 Icq=0.5;
11 g_m=Icq/V_T;
12 printf ('\ntransconductance=%3f mA/V\n',g_m)
13 ro=Va/Icq;
14 printf ('\nsmall signal output resistance=%2f KOhm\n',
          ',ro)
15 Av=-g_m*ro*rc/(ro+rc);

```

```
16 printf( '\nsmall signal voltage gain=%f \n' ,Av)
```

---

### Scilab code Exa 4.8 Determine the dc and ac load lines

```
1 clear;
2 clc;
3 //Example 4.8
4 b=150;Veb=0.7;
5 //dc solution
6 V2=10;
7 V1=-10;
8 V_T=0.026; // (V)
9 Rc=5;
10 Rb=50;
11 Re=10;
12 Ibq=(V2-Veb)/(Rb+(1+b)*Re);
13 printf( '\nbase current=%f mA\n' ,Ibq)
14 Icq=b*Ibq;
15 printf( '\ncollector current=%f mA\n' ,Icq)
16 Ieq=(1+b)*Ibq;
17 printf( '\nemitter current=%f mA\n' ,Ieq)
18 Vecq=V2-V1-Icq*Rc-Ieq*Re;
19 printf( '\nemitter collector voltage=%f V\n' ,Vecq)
20 //ac solution
21 r_pi=b*V_T/Icq;
22 printf( '\nsmall signal resistance=%f KOhm\n' ,r_pi)
23 g_m=Icq/V_T;
24 printf( '\ntransconductance =%fmA/V\n' ,g_m)
25 //since Va=infinity ,ro=Va/Icq is also infinity
```

---

### Scilab code Exa 4.9 Determine the maximum symmetrical swing

```
1 clear;
```

```

2 clc;
3 //Example 4.9
4 Ic=0.894;
5 i_C=2*Ic;
6 printf ('\nmaximum possible symmetrical peak to peak
    ac collector current=%f mA\n',i_C)
7 Rc=5;
8 Rl=2;
9 vo=i_C*Rc*Rl/(Rc+Rl);
10 printf ('\nmaximum possible symmetrical peak to peak
    output voltage=%f V\n',vo)
11 iC=Ic+i_C*1/2;
12 printf ('\nmaximum instantaneous collector current=%
    .3 f mA\n',iC)

```

---

Scilab code Exa 4.10 Calculate the small signal voltage gain of an emitter circuit

```

1 clear;
2 clc;
3 //Example 4.10
4 b=100;
5 Vbe=0.7;
6 V_T=0.026; //(V)
7 Re=2;
8 R1=50;
9 R2=50;
10 Rs=0.5;
11 Va=80;
12 //by dc analysis
13 Icq=0.793;
14 Vceq=3.4;
15 r_pi=b*V_T/Icq;
16 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)
17 g_m=Icq/V_T;
18 printf ('\ntransconductance=%f mA/V\n',g_m)

```

```
19 ro=Va/Icq;
20 printf ('\nsmall signal output resistance=%f KOhm\n',
21 ,ro)
21 Rib=r_pi+(1+b)*Re*ro/(ro+Re);
22 printf ('\ninput resistance to the base=%f KOhm\n',
23 Rib)
23 //Ri=R1||R2||Rib
24 x=R1*R2/(R1+R2);
25 Ri=x*Rib/(x+Rib);
26 printf ('\nRi=%f KOhm\n',Ri)
27 y=ro*Re/(ro+Re);
28 Av=(1/(r_pi+(1+b)*y))*(1+b)*y*Ri/(Ri+Rs);
29 printf ('\nsmall signal voltage gain=%f \n',Av)
```

---

# Chapter 5

## The Field Effect Transistor

Scilab code Exa 5.1 Calculate the current in an n channel MOSFET

```
1 clear;
2 clc;
3 //Example 5.1
4 Vtn=0.75; //(V)
5 W=40*10^-6; //(cm)
6 L=4*10^-6; //(cm)
7 u=650; //(cm)
8 Iox=450*10^-11;
9 e=3.9*8.86*10^-14;
10 Kn=W*u*e/(2*L*Iox);
11 printf ('\nconduction parameter=%f mA/V^2\n',Kn)
12 Vgs=2*Vtn;
13 i_D=Kn*(Vgs-Vtn)^2;
14 printf ('\ndrain current=%f mA\n',i_D)
```

---

Scilab code Exa 5.2 Determine the source to drain voltage required to bias p channel

```
1 clear;
```

```

2 clc;
3 //Example 5.2
4 Kp=0.2; // (mA/V^2)
5 Vtp=0.5;
6 iD=0.5;
7 Vsg=sqrt(iD/Kp)-Vtp;
8 printf ('\nVgs=%f V\n',Vsg)
9 //to bias in p channel MOSFET
10 Vsd=Vsg+Vtp;
11 printf ('\nVsd=%f V\n',Vsd)

```

---

**Scilab code Exa 5.3** Calculate the drain current and drain to source voltage of cir

```

1 clear;
2 clc;
3 //Example 5.3
4 R1=30;
5 R2=20;
6 RD=20;
7 Vdd=5;
8 Vtn=1;
9 Kn=0.1;
10 Vgs=R2*Vdd/(R1+R2);
11 printf ('\nVgs=%0.2 f V\n',Vgs)
12 I_D=Kn*(Vgs-Vtn)^2;
13 printf ('\nthe drain current=%0.1 f mA\n',I_D)
14 Vds=Vdd-I_D*RD;
15 printf ('\ndrain to source voltage=%0.1 f V\n',Vds)

```

---

**Scilab code Exa 5.4** Calculate the drain current and drain to source voltage of cir

```

1 clear;
2 clc;

```

```

3 //Example 5.4
4 R1=50;
5 R2=50;
6 RD=7.5;
7 Vdd=5;
8 Vtp=-0.8;
9 Vg=2.5;
10 Kp=0.2;
11 Vo=R2*Vdd/(R1+R2);
12 printf ('\nVo=%.2f V\n',Vo)
13 Vsg=Vdd-Vg;
14 printf ('\nsource to gate voltage=% .2f V\n',Vsg)
15 I_D=Kp*(Vsg+Vtp)^2;
16 printf ('\nthe drain current=% .3f mA\n',I_D)
17 Vsd=Vdd-I_D*RD;
18 printf ('\nsource to drain voltage=% .3f V\n',Vsd)

```

---

**Scilab code Exa 5.6** Design the dc bias of a MOSFET circuit to produce specified drain current.

```

1 clear;
2 clc;
3 //Example 5.6
4 Vtn=2;
5 Kn=80*10^-3;
6 //x=W/L
7 x=4;
8 I_D=0.5;
9 //I_D=Kn*x*((Vgs-Vtn)^2)/2;
10 Vgs=sqrt(I_D*2/(Kn*x))+2;
11 printf ('\nVgs=% .2f V\n',Vgs)
12 //y=R1+R2
13 Rs=2;
14 y=10/0.05;
15 printf ('\nR1+R2=% .2f Kohm\n',y)
16 //Vgs=Vg-Vs=(R2/(R1+R2)*10-5)-I_D*Rs+5

```

---

```

17 R2=(y/10)*(Vgs+I_D*Rs);
18 printf ('\nR2=%f KOhm\n',R2)
19 R1=y-R2;
20 printf ('\nR1=%f KOhm\n',R1)

```

---

**Scilab code Exa 5.7** Design a MOSFET circuit biased with a constant current source

```

1 clear;
2 clc;
3 //Example 5.7
4 Vtn=0.8;
5 Kn=80;
6 //x=W/L
7 x=3;
8 I_D=250;
9 Vd=2.5;
10 //I_D=Kn/2*x*(Vgs-Vtn)^2
11 Vgs=sqrt(I_D*2/(Kn*x))+Vtn;
12 printf ('\nVgs=%f V\n',Vgs)
13 Vs=-Vgs
14 //I_D=(5-Vd)/Rd
15 Rd=(5-Vd)/I_D;
16 printf ('\nRd=%f KOhm\n',Rd)
17 Vds=Vd-Vs;
18 printf ('\nVds=%f V\n',Vds)
19 Vdssat=Vgs-Vtn
20 //since Vds>Vdssat transistor is biased in
   saturation region

```

---

**Scilab code Exa 5.8** Calculate the characteristics of a circuit containing an enhan

```

1 clear;
2 clc;

```

```

3 //Example 5.8
4 Vtn=0.8;
5 Kn=0.05;
6 //I_D=Kn*(Vgs-Vtn)^2
7 //Vds=Vgs=5-I_D*Rs
8 //combining these two equations we obtain 0.5(Vgs)
     ^2+0.2Vgs-4.68
9 Vgs=poly(0,'Vgs')
10 p=poly([-4.68 0.2 0.5],'Vgs','c')
11 printf('\npossible solutions ::%.3f V\n',roots(p))
12 //assuming transistor is conducting ,Vgs must be
     greater than threshold voltage
13 Vgs=2.87;
14 I_D=Kn*(Vgs-Vtn)^2;
15 printf ('\ndrain current=% .3f mA\n',I_D)

```

---

**Scilab code Exa 5.10 Calculate the characteristics of a circuit containing a deple**

```

1 clear;
2 clc;
3 //Example 5.10
4 Vtn=-2;
5 Kn=0.1;
6 Vdd=5;
7 Rs=5;
8 Vgs=0;
9 I_D=Kn*(Vgs-Vtn)^2;
10 printf ('\ndrain current=% .3f mA\n',I_D)
11 Vds=Vdd-I_D*Rs;
12 printf ('\ndrain to source voltage=% .2f V\n',Vds)
13 Vdssat=Vgs-Vtn
14 //since Vds>Vdssat transisitor is biased in
     saturation region

```

---

**Scilab code Exa 5.11** Determine the dc transistor currents and voltages in a circuit

```
1 clear;
2 clc;
3 //Example 5.11
4 Vtnd=1;
5 Vtnl=-2;
6 Knd=50;
7 Knl=10;
8 Vt=5;
9 Vo=poly(0, 'Vo')
10 p=poly([4 -40 5], 'Vo', 'c')
11 printf ('\npossible solutions ::%.2f V\n', roots(p))
12 //since output voltage cannot be greater than supply
    voltage 5V
13 Vo=0.1; //(V)
14 I_D=Knl*(-Vtnl)^2;
15 printf ('\ndrain current=%.3f microA\n', I_D)
```

---

**Scilab code Exa 5.13** Determine the currents and voltages in a MOSFET constant curr

```
1 clear;
2 clc;
3 //Example 5.13
4 Kn1=0.2;
5 Kn2=0.1;
6 Kn3=0.1;
7 Kn4=0.1;
8 Vtn1=1;
9 Vtn2=1;
10 Vtn3=1;
11 Vtn4=1;
```

```

12 V2=-5;
13 Vgs3=(sqrt(Kn4/Kn3)*(-V2-Vtn4)+Vtn3)/(1+sqrt(Kn4/Kn3));
14 printf ('\nVgs3=%f\n',Vgs3)
15 Iq=Kn3*(Vgs3-Vtn3)^2;
16 printf ('\nbias current=%f mA\n',Iq)
17 Vgs1=sqrt(Iq/Kn1)+Vtn1;
18 printf ('\ngate to source voltage on M1=%f V\n',
19 Vgs1)
20 Vds2=-V2-Vgs1;
21 printf ('\ndrain to source voltage on M2=%f V\n',
22 Vds2)
23 //since Vds2>Vdssat M2 is biased in saturation
region

```

---

**Scilab code Exa 5.14** Design the size of a power MOSFET to meet the specification of

```

1 clear;
2 clc;
3 //Example 5.14
4 I_D=0.5;
5 Vds=6;
6 Kn=80*10^-6;
7 Vgs=5;
8 Vtn=1;
9 //x=W/L
10 x=I_D*2/(Kn*(Vgs-Vtn)^2);
11 disp(x,"W/L ")
12 //maximum power dissipation in transistor
13 Pmax=Vds*I_D;
14 printf ('\nmaximum power dissipation in transistor=%
.3 f W\n',Pmax)

```

---

**Scilab code Exa 5.16** Calculate  $I_D$  and  $V_{ds}$  in an n channel pn JFET

```
1 clear;
2 clc;
3 //Example 5.16
4 Idss=2; // (mA) saturation current
5 Vp=-3.5; // (V) pinch off voltage
6 Vgs=[0 Vp/4 Vp/2]
7 I_D=Idss*(1-Vgs/Vp)^2;
8 disp(I_D,"I_D (A)")
9 Vds=Vgs-Vp;
10 disp(Vds,"Vdssat (V)")
```

---

**Scilab code Exa 5.17** Design the dc bias of a JFET circuit

```
1 clear;
2 clc;
3 //Example 5.17
4 Idss=5; //mA
5 Vp=-4;
6 Vdd=10;
7 I_D=2;
8 Vds=6;
9 //I_D=Idss*(1-Vgs/Vp)^2
10 Vgs=(1-sqrt(I_D/Idss))*Vp;
11 printf ('\nVgs=%f V\n',Vgs)
12 Rs=-Vgs/I_D;
13 printf ('\nRs=%f KOhm\n',Rs)
14 Rd=(Vdd-Vds-I_D*Rs)/I_D;
15 printf ('\nRd=%f KOhm\n',Rd)
16 Vgs-Vp
17 //since Vds>Vgs-Vp JFET is biased in saturation
```

---

**Scilab code Exa 5.19** Calculate the quiscent current and voltage values

```
1 clear;
2 clc;
3 //Example 5.19
4 Idss=2.5;
5 Vp=2.5;
6 I_D=0.8;
7 //I_D=Iq=0.8*10^-3=(Vd-(-9))/Rd
8 Vd=0.8*4-9;
9 printf ('\nVd =%.2fV\n',Vd)
10 //I_D=Idss*(1-Vgs/Vp)^2;
11 Vgs=(1-sqrt(I_D/Idss))*Vp;
12 printf ('\nVgs =%.2fV\n',Vgs)
13 Vs=1-Vgs;
14 printf ('\nVs=% .2 f V\n',Vs)
15 Vsd=Vs-Vd;
16 printf ('\nVsd=% .2 f V\n',Vsd)
17 Vp-Vgs
18 //since Vsd>Vp-Vgs JFET is biased in saturation
```

---

**Scilab code Exa 5.20** Design a circuit with an enhancement mode MESFET

```
1 clear;
2 clc;
3 //Example 5.20
4 Vtn=0.24;
5 Kn=1.1;
6 //x=R1+R2=50000
7 x=50;
8 Vgs=0.5;
```

```

9 Vds=2.5;
10 Vdd=4;
11 Rd=6.7;
12 I_D=Kn*(Vgs-Vtn)^2;
13 printf ('\ndrain current=%.3f mA\n', I_D)
14 Vd=Vdd-I_D*Rd;
15 printf ('\nvoltage at drain=%0.2f V\n', Vd)
16 Vs=Vd-Vds;
17 printf ('\nvoltage at source =%0.2fV\n', Vs)
18 Rs=Vs/I_D;
19 printf ('\nsource resistance =%.2fKOhm\n', Rs)
20 Vg=Vgs+Vs;
21 printf ('\nvoltage at the gate=%0.2f V\n', Vg)
22 //Vg=R2*Vdd/(R2+R1)
23 R2=Vg*x/Vdd;
24 printf ('\nR2=%0.3f KOhm\n', R2)
25 R1=x-R2;
26 printf ('\nR1=%0.3f KOhm\n', R1)
27 Vgs-Vtn
28 //since Vds>Vgs-Vtn transistor is biased in
   saturation

```

---

# Chapter 6

## Basic FET Amplifier

Scilab code Exa 6.1 Calculate the transconductance of an n channel MOSFET

```
1 clear;
2 clc;
3 //Example 6.1
4 Vtn=1;
5 //let x= u_n*Cox*1/2
6 x=20*10^-3;
7 //let y=W/L
8 y=40;
9 I_D=1;
10 Kn=x*y;
11 printf('nconduction parameter=%.3f mA/V^2\n',Kn)
12 g_m=2*sqrt(Kn*I_D);
13 printf('ntransconductance=%.3f mA/V\n',g_m)
```

---

Scilab code Exa 6.2 Determine the small signal voltage gain of a MOSFET

```
1 clear;
2 clc;
```

```

3 //Example 6.2
4 Vgsq=2.12;
5 Vdd=5;
6 Rd=2.5;
7 Vtn=1;
8 Kn=0.8;
9 //let lambda=y
10 y=0.02; //V^-1
11 Idq=Kn*(Vgsq-Vtn)^2;
12 printf ('\n drain current=%.3f mA\n', Idq)
13 Vdsq=Vdd-Idq*Rd;
14 printf ('\n drain to source voltage=% .3f V\n', Vdsq)
15 Vgs=1.82;
16 Vgs-Vtn
17 //since Vdsq>Vgs-Vtn transistor is biased in
   saturation
18 g_m=2*Kn*(Vgsq-Vtn);
19 printf ('\n transconductance=% .3f mA/V\n', g_m)
20 ro=(y*Idq)^-1;
21 printf ('\n output resistance=% .2f KOhm\n', ro)
22 Av=-g_m*ro*Rd/(ro+Rd);
23 printf ('\n small signal voltage gain=% .2f \n', Av)

```

---

**Scilab code Exa 6.3** Determine the small signal voltage gain and input and output resistance.

```

1 clear;
2 clc;
3 //Example 6.3
4 Vdd=10;
5 R1=70.9; // (Kohm)
6 R2=29.1; // (Kohm)
7 Rd=5; // (Kohm)
8 Vtn=1.5;
9 Kn=0.5; // (mA/V^2)
10 //lambda=y

```

```

11 y=0.01; //V^-1
12 Rsi=4; // (Kohm)
13 Vgsq=Vdd*R2/(R1+R2);
14 printf ('\ngate to source voltage=%f V\n',Vgsq)
15 Idq=Kn*(Vgsq-Vtn)^2;
16 printf ('\ndrain current=%f mA\n', Idq)
17 Vdsq=Vdd-Idq*Rd;
18 printf ('\ndrain to source voltage=%f V\n',Vdsq)
19 g_m=2*Kn*(Vgsq-Vtn);
20 printf ('\ntransconductance=%f mA/V\n',g_m)
21 ro=(y*Idq)^-1;
22 printf ('\noutput resistance=%f KOhm\n',ro)
23 Ri=R1*R2/(R1+R2);
24 printf ('\namplifier input resistance=%f Kohm\n',Ri
)
25 Av=-g_m*(ro*Rd/(ro+Rd))*Ri/(Ri+Rsi);
26 printf ('\nsmall signal voltage gain=%f\n',Av)
27 printf ('\namplifier input resistance=%f Kohm\n',Ri
)
28 Ro=Rd*ro/(Rd+ro);
29 printf ('\namplifier output resistance=%f Kohm\n',
Ro)

```

---

**Scilab code Exa 6.4** Design the bias of a MOSFET such that the Q point is in the mi

```

1 clear;
2 clc;
3 //Example 6.4
4 Vtn=1;
5 Kn=1; //(mA/V^2)
6 //lambda=y
7 y=0.015; //V^-1
8 Ri=100; // (Kohm)
9 Idq=2; //(mA)
10 Idt=4; //(mA)

```

```

11 // Idt=4=Kn*( Vgst-Vtn ) ^2
12 Vgst=sqrt( Idt/Kn)+Vtn;
13 printf( '\nVgst=%f V\n' ,Vgst)
14 Vdst=Vgst-Vtn;
15 printf( '\nVdst=%f V\n' ,Vdst)
16 Vdd=12;
17 Vdsq=7;
18 Rd=(Vdd-Vdsq)/Idq;
19 printf( '\nRd =%f Kohm\n' ,Rd)
20 Vgsq=sqrt( Idq/Kn)+Vtn;
21 printf( '\nVgsq=%f V\n' ,Vgsq)
22 R1=Ri*Vdd/Vgsq;
23 printf( '\nR1=%f Kohm\n' ,R1)
24 R2=Ri*R1/(R1-Ri);
25 printf( '\nR2=%f Kohm\n' ,R2)
26 g_m=2*Kn*(Vgsq-Vtn);
27 printf( '\ntransconductance=%f mA/V\n' ,g_m)
28 ro=(y*Idq)^-1;
29 printf( '\noutput resistance=%f Kohm\n' ,ro)
30 Av=-g_m*(ro*Rd/(ro+Rd));
31 printf( '\nsmall signal voltage gain=%f\n' ,Av)

```

---

**Scilab code Exa 6.6** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.6
4 Vtn=0.8;
5 Kn=1; //(mA/V^2)
6 Idq=0.5;
7 Vdd=5;
8 Rd=7; //(Kohm)
9 Vgsq=sqrt( Idq/Kn)+Vtn;
10 printf( '\nVgsq=%f V\n' ,Vgsq)
11 Vs=-Vgsq

```

```

12 Vdsq=Vdd-Idq*Rd-Vs;
13 printf ('\nVdsq=%f V\n',Vdsq)
14 g_m=2*Kn*(Vgsq-Vtn);
15 printf ('\ntransconductance=%f mA/V\n',g_m)
16 Av=-g_m*Rd;
17 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

**Scilab code Exa 6.7 Determine the small signal voltage gain of a circuit**

```

1 clear;
2 clc;
3 //Example 6.7
4 Vdd=12;
5 R1=162;
6 R2=463;
7 Rs=0.75;
8 Kn=4;
9 Vtn=1.5;
10 //lambda=y
11 y=0.01;
12 Rsi=4;
13 Idq=7.97;
14 Vgsq=2.91;
15 g_m=2*Kn*(Vgsq-Vtn);
16 printf ('\ntransconductance=%f mA/V\n',g_m)
17 ro=(y*Idq)^-1;
18 printf ('\noutput resistance=%f KOhm\n',ro)
19 Ri=R1*R2/(R1+R2);
20 printf ('\namplifier input resistance=%f Kohm\n',Ri
)
21 x=Rs*ro/(Rs+ro);
22 Av=g_m*x*(Ri/(Ri+Rsi))/(1+g_m*x);
23 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

**Scilab code Exa 6.9** Calculate the output resistance of a source follower circuit

```
1 clear;
2 clc;
3 //Example 6.9
4 Rs=750; //Ohm
5 ro=12500;
6 g_m=11.3*10^-3;
7 x=1/g_m;
8 y=x*Rs/(x+Rs);
9 Ro=y*ro/(y+ro);
10 printf ('\noutput resistance=%.3f ohm\n',Ro)
```

---

**Scilab code Exa 6.11** Design the small signal voltage gain of an NMOS amplifier

```
1 clear;
2 clc;
3 //Example 6.11
4 Vtnd=1;
5 Vtnl=1;
6 Kn=30;
7 // let W/L=x
8 xl=1;
9 Vdd=5;
10 Av=10;
11 //Av=sqrt (xd/xl)
12 xd=(Av)^2*xl;
13 printf ('\nwidth to length ratio of driver transistor
           =%.2f\n',xd)
14 Knd=xd*Kn*0.001/2;
15 Knl=xl*Kn*0.001/2;
```

```

16 printf( '\nconduction parameter Knd=%f mA/V^2\n' ,
      Knd)
17 printf( '\nconduction parameter Knl=%f mA/V^2\n' ,
      Knl)
18 //Vgsd-Vtnd=(Vdd-Vtnl)-sqrt (Knd/Knl)*(Vgsd-Vtnd)
19 y=sqrt(Knd/Knl);
20 Vgsd=(y+5)/(1+y);
21 printf( '\nVgsd=%f V\n' ,Vgsd)
22 Vdsd=Vgsd-1;
23 printf( '\nVdsd=%f V\n' ,Vdsd)

```

---

**Scilab code Exa 6.12** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.12
4 Vtnd=0.8;
5 Vtnl=-1.5;
6 Knd=1;
7 Knl=0.2;
8 //lambda=y
9 yd=0.01;
10 yl=0.01;
11 Idq=0.2;
12 gmd=2*sqrt(Knd*Idq);
13 printf( '\ntransconductance of the driver=%f mA/V\n' ,
      ,gmd)
14 roD=1/(yd*Idq);
15 printf( '\noutput resistances=%f Kohm\n' ,roD)
16 Av=-gmd*roD/2;
17 printf( '\nsmall signal voltage gain=%f \n' ,Av)

```

---

**Scilab code Exa 6.13** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.13
4 Vtn=0.8;
5 Vtp=-0.8;
6 Kn=80*10^-3;
7 Kp=40*10^-3;
8 //x=W/L
9 xn=15;
10 xp=10;
11 //lambda=y
12 yn=0.01;
13 yp=0.01;
14 Ibias=0.2;
15 gm=2*sqrt(Kn*xn*Ibias/2);
16 printf ('\ntransconductance of the NMOS driver=%f
mA/V^2\n',gm)
17 ron=1/(yn*Ibias);
18 printf ('\noutput resistances=%f Kohm\n',ron)
19 Av=-gm*ron/2;
20 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

**Scilab code Exa 6.14 Design the biasing of a multistage MOSFET**

```

1 clear;
2 clc;
3 //Example 6.14
4 Kn1=500*10^-3;
5 Kn2=200*10^-3;
6 Vtn1=1.2;
7 Vtn2=Vtn1;
8 Idq1=0.2;
9 Idq2=0.5;
10 Vdsq1=6;
11 Vdsq2=6;

```

```

12 Ri=100;
13 Rsi=4;
14 Rs2=(10-Vdsq2)/Idq2;
15 printf ('\nRs2=%f KOhm\n',Rs2)
16 Vgs2=sqrt(Idq2/Kn2)+Vtn2;
17 printf ('\ngate to source voltage for M2=%f V\n',
          Vgs2)
18 Vs2=-1;
19 Vg2=Vs2+Vgs2;
20 printf ('\ngate voltage of M2=%f V\n',Vg2)
21 Vg1=Vg2;
22 Rd1=(5-Vg1)/Idq1;
23 printf ('\nresistor Rd1=%f KOhm\n',Rd1)
24 Vs1=Vg1-Vdsq1;
25 printf ('\nsource voltage of M1=%f KOhm\n',Vs1)
26 Rs1=(Vs1+5)/Idq1;
27 printf ('\nresistor Rs1=%f KOhm\n',Rs1)
28 Vgs1=sqrt(Idq1/Kn1)+Vtn1;
29 printf ('\ngate to source voltage for M1=%f V\n',
          Vgs1)
30 R1=Ri*10/(Vgs1+Idq1*Rs1);
31 printf ('\nR1=%f KOhm\n',R1)
32 //Ri=R1*R2/(R1+R2)
33 R2=Ri*R1/(R1-Ri);
34 printf ('\nR2=%f KOhm\n',R2)

```

---

### Scilab code Exa 6.15 Design the biasing of cascade circuit

```

1 clear;
2 clc;
3 //Example 6.15
4 Vtn1=1.2;
5 Vtn2=1.2;
6 Kn1=0.8;
7 Kn2=0.8;

```

```

8 //x=R1+R2+R3=300
9 x=300;
10 Rs=10;
11 Idq=0.4;
12 Vdsq1=2.5;
13 Vdsq2=2.5;
14 Vs1=Idq*Rs-5;
15 printf ('\n dc voltage at source of M1=%f V\n',Vs1)
16 Vgs=sqrt(Idq/Kn1)+Vtn1;
17 printf ('\n gate to source voltage=%f V\n',Vgs)
18 R3=(Vgs+Vs1)*x/5;
19 printf ('\n R3=%f KOhm\n',R3)
20 Vs2=Vdsq2+Vs1;
21 printf ('\n voltage at source of M2=%f V\n',Vs2)
22 //y=R2+R3
23 y=(Vgs+Vs2)*x/5;
24 printf ('\n R2+R3=%f KOhm\n',y)
25 R2=150;
26 R1=x-y;
27 printf ('\n R1=%f KOhm\n',R1)
28 R3=y-R2;
29 printf ('\n R3=%f KOhm\n',R3)
30 Vd2=Vdsq2+Vs2;
31 printf ('\n voltage at drain of M2 =%f V\n',Vd2)
32 Rd=(5-Vd2)/Idq;
33 printf ('\n drain resistance=%f KOhm\n',Rd)

```

---

**Scilab code Exa 6.17** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.17
4 Kn=0.8;
5 Vtn=1.2;
6 Vgs=1.91;

```

```

7 Rd=2.5;
8 gm=2*Kn*(Vgs-Vtn);
9 printf ('\ntransconductance=%f mA/V\n',gm)
10 Av=-gm*Rd;
11 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

**Scilab code Exa 6.18** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.18
4 //Determine the small signal voltage gain of a
   circuit in fig.6.55
5 Idss=12;
6 Vp=-4;
7 //lambda=y
8 y=0.008;
9 Vgssq=poly(0, 'Vgssq');
10 p=poly([26.4 17.2 2.025], 'Vgssq', 'c')
11 printf ('\nroots=%fV\n',roots(p))
12 Vgssq=-2.01
13 Idq=Idss*(1-Vgssq/Vp)^2;
14 printf ('\nquiescent drain current=%f mA\n',Idq)
15 gm=(-2*Idss/Vp)*(1-Vgssq/Vp);
16 printf ('\ntransconductance=%f mA/V\n',gm)
17 ro=(1/(y*Idq));
18 printf ('\noutput resistance=%f KOhm\n',ro)
19 Rd=2.7;
20 Rl=4;
21 x=Rd*Rl/(Rd+Rl);
22 Av=-gm*ro*x/(ro+x);
23 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

### Scilab code Exa 6.19 Design a JFET source follower

```
1 clear;
2 clc;
3 //Example 6.19
4 Idss=12;
5 Vp=-4;
6 Rl=10;
7 //lambda=y
8 y=0.01;
9 Av=0.9;
10 //gm=(-2*Idss/Vp)*(1-Vgs/Vp)
11 gm=2;
12 Vgs=(1+gm*Vp/(2*Idss))*Vp;
13 printf ('\ngate to source voltage=%f V\n',Vgs)
14 Idq=Idss*(1-Vgs/Vp)^2;
15 printf ('\nquiescent drain current=%f mA\n',Idq)
16 Rs=(-Vgs+10)/Idq;
17 printf ('\nRs=%f KOhm\n',Rs)
18 ro=(1/(y*Idq));
19 printf ('\noutput resistance=%f KOhm\n',ro)
20 x=Rl*ro/(Rl+ro);
21 t=x*Rs/(x+Rs);
22 Av=gm*t/(1+gm*t);
23 printf ('\nsmall signal voltage gain=%f \n',Av)
```

---

# Chapter 7

## Frequency Response

Scilab code Exa 7.1 Determine the corner frequencies and maximum magnitude asymptotic approximation

```
1 clear;
2 clc;
3 //Example 7.1
4 Rs=1000;
5 Rp=10000;
6 Cs=1*10^-6;
7 Cp=3*10^-12;
8 Ts=(Rs+Rp)*Cs;
9 printf('ntime constant=%f s\n',Ts)
10 f=1/(2*pi*Ts);
11 printf('ncorner frequency=%f Hz\n',f)
12 x=20*log10(Rp/(Rp+Rs));
13 printf('\nmaximum magnitude =%f dB\n',x)
14 Rp=10; //KOhm
15 Rs=1; //Kohm
16 Cp=3; //pF
17 Tp=Cp*Rs*Rp/(Rs+Rp);
18 printf('ntime constant=%f ns\n',Tp)
19 Tp=2.73*10^-3; //micro sec
20 f=1/(2*pi*Tp);
21 printf('ncorner frequency =%f MHz\n',f)
```

---

**Scilab code Exa 7.2 Determine the corner frequencies and bandwidth**

```
1 clear;
2 clc;
3 //Example 7.2
4 Rs=1000;
5 Rp=10000;
6 Cs=1*10^-6;
7 Cp=3*10^-12;
8 Ts=(Rs+Rp)*Cs;
9 printf ('\nopen circuit time constant=%.3f s\n',Ts)
10 Rs=1; //KOhm
11 Rp=10; //KOhm
12 Cp=3; //pF
13 Tp=Cp*Rs*Rp/(Rs+Rp);
14 printf ('\nshort circuit time constant=%.3f ns\n',Tp)
15 fL=1/(2*pi*Ts);
16 printf ('\ncorner frequency fL=%.2f Hz\n',fL)
17 Tp=2.73*10^-3; //microsec
18 fH=1/(2*pi*Tp);
19 printf ('\ncorner frequency fH=%.3f MHz\n',fH)
20 fL=14.5*10^-6; //MHz
21 fbw=fH-fL;
22 printf ('\nbandwidth =%.3fMHz\n',fbw)
```

---

**Scilab code Exa 7.3 Determine the corner frequencies and maximum gain**

```
1 clear;
2 clc;
3 //Example 7.3
4 R1=51.2;
```

```

5 R2=9.6;
6 Rc=2;
7 Re=.4;
8 Rsi=.1;
9 Vt=0.026;
10 Cc=1;
11 Vcc=10;
12 Vbe=0.7;
13 b=100;
14 Rb=8.08;
15 Icq=1.81;
16 gm=Icq/Vt;
17 printf ('\ntransconductance=%f mA/V\n',gm)
18 r=b*Vt/Icq;
19 printf ('\ndiffusion resistance=%f KOhm\n',r)
20 x=r+(1+b)*Re;
21 y=x*R2/(x+R2);
22 Ri=y*R1/(R1+y);
23 printf ('\ninput resistance=%f KOhm\n',Ri)
24 Ts=(Rsi+Ri)*Cc;
25 printf ('\ntime constant=%f ms\n',Ts)
26 Ts=6.87*10^-3; //Sec
27 fL=1/(2*pi*Ts);
28 printf ('\ncorner frequency fL=%f Hz\n',fL)
29 Rib=r+(1+b)*Re;
30 printf ('\nRib=%f KOhm\n',Rib)
31 Av=(gm*r*Rc/(Rsi+Ri))*Rb/(Rb+Rib);
32 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

### Scilab code Exa 7.4 Design the circuit

```

1 clear;
2 clc;
3 //Example 7.4
4 fL=20*10^-3; //KHz

```

```

5 Rd=6.7;
6 Rl=10;
7 Ts=1/(2*pi*fL);
8 printf ('\ntime constant=%f ms\n',Ts)
9 Cc=Ts/(Rd+Rl);
10 printf ('\ncoupling capacitance=%f microF\n',Cc)

```

---

### Scilab code Exa 7.5 Determine 3dB frequency

```

1 clear;
2 clc;
3 //Example 7.5
4 b=100;
5 Vbe=0.7;
6 Rs=500;
7 Rb=100000;
8 Re=10000;
9 Rl=10000;
10 Va=120;
11 Ccc2=1*10^-6;
12 Icq=0.838*0.001;
13 r=3100; //small signal parameter
14 gm=32.2*0.001;
15 ro=143000;
16 x=(r+Rs*Rb/(Rs+Rb))/(1+b);
17 y=ro*x/(ro+x);
18 Ro=Re*y/(Re+y);
19 printf ('\noutput resistance of emitter=%f Ohm\n',
Ro)
20 Ts=(Ro+Rl)*Ccc2;
21 printf ('\ntime constant=%f s\n',Ts)
22 fL=1/(2*pi*Ts);
23 printf ('\n3dB frequency=%f Hz\n',fL)

```

---

**Scilab code Exa 7.6** Determine the corner frequencies and maximum gain

```
1 clear;
2 clc;
3 //Example 7.6
4 Rs=3.2;
5 Rd=10;
6 Rl=20;
7 Cl=10;
8 Vtp=-2;
9 Kp=0.25;
10 Idq=0.5;
11 Vsgq=3.41;
12 Vsdq=3.41;
13 gm=2*Kp*(Vsgq+Vtp);
14 printf ('\ntransconductance =%.3fmA/V\n',gm)
15 Tp=Cl*Rd*Rl/(Rd+Rl);
16 printf ('\ntime constant=%.3f ns\n',Tp)
17 Tp=66.7*10^-3; //micro sec
18 fH=1/(2*pi*Tp);
19 printf ('\ncorner frequency=%.2f MHz\n',fH)
20 Av=(gm*Rd*Rl/(Rd+Rl))/(1+gm*Rs);
21 printf ('\nmaximum small signal voltage gain=%.2f\n',
Av)
```

---

**Scilab code Exa 7.7** Determine the mid gain corner frequencies and bandwidth of a c

```
1 clear;
2 clc;
3 //Example 7.7
4 Vbe=0.7;
5 b=100;
```

```

6 Re=.5;
7 Rc=5;
8 Rl=10;
9 R1=40;
10 Cc=10;
11 R2=5.7;
12 Rs=.1;
13 Vt=0.026;
14 Icq=0.99;
15 gm=Icq/Vt;
16 printf ('\ntransconductance=%f mA/V\n',gm)
17 r=b*Vt/Icq;
18 printf ('\ndiffusion resistance=%f KOhm\n',r)
19 Ri=r+(1+b)*Re;
20 printf ('\ninput resistance=%f KOhm\n',Ri)
21 x=Rc*Rl/(Rc+Rl);
22 y=R1*R2/(R1+R2);
23 t=y*Ri/(y+Ri);
24 Av=gm*r*x*(y/(y+Ri))*(1/(Rs+t));
25 printf ('\nmaximum small signal voltage gain=%f\n',
           Av)
26 Ts=(Rs+t)*Cc;
27 printf ('\ntime constant=%f ms\n',Ts)
28 Ts=46.6*0.001; //sec
29 Cl=15;
30 Tp=x*Cl;
31 printf ('\ntime constant=%f ns\n',Tp)
32 fL=1/(2*pi*Ts);
33 printf ('\nlower corner frequency=%f Hz\n',fL)
34 Tp=50*10^-3; //micro sec
35 fH=1/(2*pi*Tp);
36 printf ('\nupper corner frequency=%f MHz\n',fH)
37 fL=3.4*10^-6; //MHz
38 fbw=fH-fL;
39 printf ('\nbandwidth =%f MHz\n',fbw)

```

---

### Scilab code Exa 7.8 Determine the corner frequencies and limiting horizontal asymptotes

```
1 clear;
2 clc;
3 //Example 7.8
4 Re=4;
5 Rc=2;
6 Rs=0.5;
7 Vt=0.026;
8 Ce=1*10^-3;
9 V1=5;
10 Icq=1.06;
11 V2=-5;
12 b=100;
13 Vbe=0.7;
14 gm=Icq/Vt;
15 printf ('\ntransconductance =%.2fmA/V\n',gm)
16 r=b*Vt/Icq;
17 printf ('\ndiffusion resistance=%.2f KOhm\n',r)
18 Ta=Re*Ce;
19 printf ('\ntime constant Ta=%ef s\n',Ta)
20 Tb=(Re*Ce*(Rs+r))/(Rs+r+(1+b)*Re);
21 printf ('\ntime constant Tb=%e s\n',Tb)
22 fA=1/(2*pi*Ta);
23 printf ('\ncorner frequency =%.2fHz\n',fA)
24 Tb=2.9*0.01; //msec
25 fB=1/(2*pi*Tb);
26 printf ('\ncorner frequency =%.2fkHz\n',fB)
27 Av=(gm*r*Rc)/(Rs+r+(1+b)*Re);
28 printf ('\nlimiting low frequency horizontal
           asymptote=%.2f\n',Av)
29 Av=gm*r*Rc/(Rs+r);
30 printf ('\nnlimiting high frequency horizontal
           asymptote=%.2f\n',Av)
```

---

### Scilab code Exa 7.9 Determine 3dB frequency

```
1 clear;
2 clc;
3 //Example 7.9
4 r=2600;
5 C1=2*10^-6;
6 C2=0.1*10^-6;
7 fB=1/(2*pi*r*(C1+C2));
8 printf('n3dB frequency=%f MHz\n',fB)
```

---

### Scilab code Exa 7.10 Calculate bandwidth and capacitance

```
1 clear;
2 clc;
3 //Example 7.10
4 fT=500;
5 Ic=1;
6 b=100;
7 Vt=0.026;
8 C2=0.3*10^-12;
9 fB=fT/b;
10 printf('nbandwidth=%f MHz\n',fB)
11 gm=Ic/Vt;
12 printf('ntransconductance=%f mA/V\n',gm)
13 fT=500000000;
14 gm=38.5*0.001;
15 C1=gm/(fT*2*pi)-C2;
16 printf('ncapacitance =%f eF\n',C1)
```

---

**Scilab code Exa 7.12** Determine the unity gain bandwidth

```
1 clear;
2 clc;
3 //Example 7.12
4 Kn=0.25;
5 Vtn=1;
6 Cgd=0.04*10^-3;
7 Cgs=0.2*10^-3;
8 Vgs=3;
9 gm=2*Kn*(Vgs-Vtn);
10 printf ('\ntransconductance =%.3fmA/V\n',gm)
11 fT=gm/(2*pi*(Cgd+Cgs));
12 printf ('\nunity gain bandwidth=%.f MHz\n',fT)
```

---

**Scilab code Exa 7.13** Determine the Miller capacitance and cutoff frequency

```
1 clear;
2 clc;
3 //Example 7.13
4 gm=1;
5 Cgd=0.04;
6 Rl=10;
7 Cgs=0.2;
8 Cm=Cgd*(1+gm*Rl);
9 printf ('\nMiller capacitance=%f pF\n',Cm)
10 Cm=0.44*0.001; //nF
11 Cgs=0.2*0.001; //nF
12 fT=gm/(2*pi*(Cgs+Cm));
13 printf ('\ncutoff frequency=%f MHz\n',fT)
```

---

**Scilab code Exa 7.14** Determine the upper corner frequency and midband gain

```

1 clear;
2 clc;
3 //Example 7.14
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 Rb=40;
8 R2=5.72;
9 Re=0.5;
10 Rc=5;
11 Rl=10;
12 b=150;
13 Vbe=0.7;
14 C1=35*10^-3;
15 C2=4;
16 Vt=0.026;
17 Icq=1.02;
18 r=b*Vt/Icq;
19 printf ('\nsmall signal parameter=%f KOhm\n',r)
20 gm=Icq/Vt;
21 printf ('\ntransconductance=%f mA/V\n',gm)
22 Cm=C2*(1+gm*Rc*Rl/(Rc+Rl));
23 printf ('\nMiller capacitance=%f pF\n',Cm)
24 Cm=527*10^-3;
25 x=Rb*Rs/(Rb+Rs);
26 y=r*x/(r+x);
27 fH=1/(2*pi*y*(C1+Cm));
28 printf ('\nupper corner frequency =%f MHz\n',fH)
29 t=Rb*r/(Rb+r);
30 p=Rc*Rl/(Rc+Rl);
31 Av=gm*p*t/(t+Rs);
32 printf ('\nmidband gain=%f\n',Av)

```

---

**Scilab code Exa 7.15** Determine the upper corner frequency and midband gain

```

1 clear;
2 clc;
3 //Example 7.15
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 R1=40;
8 R2=5.72;
9 Re=0.5;
10 Rc=5;
11 Rl=10;
12 b=150;
13 Vbe=0.7;
14 C1=35;
15 C2=4;
16 Vt=0.026;
17 Icq=1.02;
18 gm=39.2;
19 r=3.82;
20 x=Re*Rs/(Re+Rs);
21 t=r/(1+b);
22 y=t*x/(t+x);
23 Tp=y*C1;
24 printf ('\n time constant=%f ns\n',Tp)
25 Tp=0.679*10^-3; //micro sec
26 f=1/(2*pi*Tp);
27 printf ('\n upper frequency =%f MHz\n',f)
28 T=C2*Rc*Rl/(Rc+Rl);
29 printf ('\n time constant=%f ns\n',T)
30 T=13.3*10^-3; //micro sec
31 f=1/(2*pi*T);
32 printf ('\n upper frequency=%f MHz\n',f)
33 x=Rc*Rl/(Rc+Rl);
34 y=Re*t/(Re+t);
35 Av=gm*x*(y/(y+Rs));
36 printf ('\n midband voltage gain=%f \n',Av)

```

---

Scilab code Exa 7.16 Determine the upper corner frequency and midband gain

```
1 clear;
2 clc;
3 //Example 7.16
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 R1=42.5;
8 R2=20.5;
9 R3=28.3;
10 Re=5.4;
11 Rc=5;
12 Rl=10;
13 b=150;
14 Vbe=0.7;
15 C1=35;
16 C2=4;
17 Vt=0.026;
18 Icq=1.02;
19 gm=39.2;
20 r=3.820;
21 Rb=R2*R3/(R2+R3);
22 x=Rb*r/(Rb+r);
23 y=Rs*x/(x+Rs);
24 Tp=y*(C1+2*C2);
25 printf ('\n time constant=%.3f ns\n',Tp)
26 Tp=Tp*10^-3; //micro sec
27 f=1/(2*pi*Tp);
28 printf ('\n 3dB frequency =%0.3fMHz\n',f)
29 T=C2*Rc*Rl/(Rc+Rl);
30 printf ('\n time constant=%.2f ns\n',T)
31 T=T*0.001; //micro sec
32 f=1/(2*pi*T);
```

```

33 printf ('\nupper frequency=%f MHz\n', f)
34 x=Rc*Rl/(Rc+Rl);
35 y=Rb*r/(Rb+r);
36 Av=gm*x*(y/(y+Rs));
37 printf ('\nmidband voltage gain=%f \n', Av)

```

---

**Scilab code Exa 7.17** Determine the frequency of a zero and a pole

```

1 clear;
2 clc;
3 //Example 7.17
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 R1=40;
8 R2=5.720;
9 Re=0.5;
10 Rc=5;
11 Rl=10;
12 b=150;
13 Vbe=0.7;
14 C1=35;
15 C2=4;
16 Vt=0.026;
17 Icq=1.02;
18 gm=39.2;
19 r=3.820;
20 t=r/(1+b);
21 t=t*0.001;
22 f=1/(2*pi*C1*t);
23 printf ('\nthe zero occurs at this frequency=%f MHz
          \n', f)
24 x=1+gm*Re*Rl/(Re+Rl);
25 Rb=R1*R2/(R1+R2)
26 d=x*r;

```

```
27 y=d*Rb/(d+Rb);
28 t=y*Rs/(y+Rs);
29 Tp=t*(C2+C1/x);
30 printf( '\n time constant=%f ns\n' ,Tp)
31 Tp=Tp*10^-3; //micro sec
32 f=1/(2*pi*Tp);
33 printf( '\n 3dB frequency=%f MHz\n' ,f)
```

---

# Chapter 8

## Ouput Stages and Power Amplifier

Scilab code Exa 8.2 Determine the maximum power dissipation

```
1 clear;
2 clc;
3 //Example 8.1
4 //let thermal resistance parameters be R
5 Rdcase=1.75; //degree celsius per watt
6 Rcsnk=1; //degree celsius per watt
7 Rsamb=5; //degree celsius per watt
8 Rcamb=50; //degree celsius per watt
9 Tamb=30; //ambient temperature
10 Tjmax=150; //maximum junction temperature
11 Tdev=150; //device temperature
12 //when no heat sink is used
13 P=(Tjmax-Tamb)/(Rdcase+Rcamb);
14 printf ('\nmaximum power dissipation=%f W\n',P)
15 //when heat sink is used
16 P=(Tjmax-Tamb)/(Rdcase+Rcsnk+Rsamb);
17 printf ('\nmaximum power dissipation=%f W\n',P)
```

---

**Scilab code Exa 8.3 Determine the maximum safe power dissipation**

```
1 clear;
2 clc;
3 //Example 8.3
4 Rcsnk=1;//degree celsius per watt
5 Rsamb=5;//degree celsius per watt
6 Tjmax=175;//maximum junction temperature
7 Toc=25;
8 Tamb=25;
9 Pr=20;//rated power W
10 Rdcase=(Tjmax-Toc)/Pr;
11 printf ('\ndevice to case thermal resistance=%f C
/W\n',Rdcase)
12 P=(Tjmax-Tamb)/(Rdcase+Rcsnk+Rsamb);
13 printf ('\nmaximum power dissipation=%f W\n',P)
```

---

**Scilab code Exa 8.7 Determine the required biasing in MOSFET class AB**

```
1 clear;
2 clc;
3 //Example 8.7
4 Vdd=10;
5 Rl=20;
6 K=0.2;
7 Vt=1;
8 vo=5;
9 iL=vo/20;
10 printf ('\niL=%f A\n',iL)
11 Idq=0.05;
12 //Idq=K*(Vbb/2-Vt)
13 Vbb=(sqrt(Idq/K)+1)*2;
```

```

14 printf( '\nVbb=%f V\n' ,Vbb)
15 iD=iL;
16 Vgsn=sqrt(iD/K)+Vt;
17 printf( '\nVgsn=%f V\n' ,Vgsn)
18 Vsgp=Vbb-Vgsn;
19 printf( '\nVsgp=%f V\n' ,Vsgp)
20 vi=vo+Vgsn-Vbb/2;
21 printf( '\ninput voltage=%f V\n' ,vi)

```

---

### Scilab code Exa 8.8 Design a transformer coupled emitter follower amplifier

```

1 clear;
2 clc;
3 //Example 8.8
4 Vcc=24;
5 Rl=8;
6 P=5;
7 Vbe=0.7;
8 b=100;
9 Vp=sqrt(2*Rl*P);
10 printf( '\npeak output voltage=%f V\n' ,Vp)
11 Ip=Vp/Rl;
12 printf( '\npeak output current =%f mA\n' ,Ip)
13 a=0.9*Vcc/Vp;
14 printf( '\nalpha=%f\n' ,a)
15 Icq=Ip/(0.9*a);
16 printf( '\nIcq=%f A\n' ,Icq)
17 Pq=Vcc*Icq;
18 printf( '\nmaximum power dissipated in the transistor
    =%f W\n' ,Pq)
19 Ibq=Icq/b;
20 Ibq=Ibq*1000; //mA
21 printf( '\nbase current Ibq=%f mA\n' ,Ibq)
22 Rth=2.500;
23 //Vth=Vcc*Rth/R1 and Vth=Ibq*Rth+Vbe

```

```

24 R1=Vcc*Rth/(Ibq*Rth+Vbe);
25 printf ('\nR1=%f KOhm\n',R1)
26 R2=Rth*R1/(R1-Rth);
27 printf ('\nR2=%f KOhm\n',R2)

```

---

### Scilab code Exa 8.9 Design the class AB output stage

```

1 clear;
2 clc;
3 //Example 8.9
4 Iso=3*10^-14;
5 Isq=10^-13;
6 b=75;
7 Vt=0.026;
8 Rl=8;
9 P=5;
10 Vp=sqrt(2*Rl*P);
11 printf ('\npeak voltage Vp=%f V\n',Vp)
12 Vcc=Vp/0.8;
13 printf ('\nsupply voltage=%f V\n',Vcc)
14 Ien=Vp/Rl;
15 printf ('\nemitter current=%f A\n',Ien)
16 Ibn=Ien/(1+b);
17 Ibn=Ibn*1000; //mA
18 printf ('\nbase current=%f mA\n',Ibn)
19 iD=0.020;
20 Vbb=2*Vt*log(iD/Iso);
21 printf ('\nVbb=%f V\n',Vbb)
22 Icq=Isq*exp((Vbb/2)/Vt);
23 Icq=Icq*1000; //mA
24 printf ('\nquiescent collector current=%f mA\n',Icq
    )
25 Ibias=20; //mA
26 iD=Ibias-Ibn;
27 printf ('\ndrain current=%f mA\n',iD)

```

```

28 iD=iD*0.001; //A
29 Vbb=2*Vt*log(iD/Iso);
30 printf ('\nVbb=%f V\n',Vbb)
31 Icn=1.12;
32 Vben=Vt*log(Icn/Isq);
33 printf ('\nB-E voltage of Qn=%f V\n',Vben)
34 Vebp=Vbb-Vben;
35 printf ('\nemitter base voltage of Qp=%f V\n',Vebp)
36 Icp=Isq*exp(Vebp/Vt);
37 Icp=Icp*1000; //mA
38 printf ('\nIcp=%f mA\n',Icp)

```

---

**Scilab code Exa 8.11 Determine the currents and the current gain**

```

1 clear;
2 clc;
3 //Example 8.11
4 R1=2; //KOhm
5 R2=R1;
6 Rl=.1; //KOhm
7 b=60;
8 Vbe=0.6;
9 Veb=0.6;
10 V1=15;
11 V2=V1;
12 iR1=(V1-Vbe)/R1;
13 //iR1=iR2=iE1=iE2
14 printf ('\niR1=%f mA\n',iR1)
15 vo=10;
16 io=vo/Rl;
17 printf ('\noutput current=%f mA\n',io)
18 iB3=100/61;
19 printf ('\niB3=%f mA\n',iB3)
20 iR1=(V1-(10+Vbe))/R1;
21 printf ('\ncurrent in R1=%f mA\n',iR1)

```

```
22 iE1=iR1-iB3;
23 printf ('\niE1=%f mA\n',iE1)
24 iB1=iE1/(1+b);
25 iB1=iB1*1000; //micro A
26 printf ('\niB1=%f microA\n',iB1)
27 iE2=(10-0.6+15)/R1;
28 printf ('\niE2=%f mA\n',iE2)
29 iB2=iE2/(1+b);
30 iB2=iB2*1000;
31 printf ('\niB2=%f microA\n',iB2)
32 Ii=iB2-iB1;
33 printf ('\ninput current=%f microA\n',Ii)
34 Ii=Ii*0.001; //mA
35 Ai=io/Ii;
36 printf ('\ncurrent gain=%f\n',Ai)
37 Ai=(1+b)*R1/(2*R1);
38 printf ('\npredicted current gain=%f\n',Ai)
```

---

# Chapter 9

## The Ideal Operational Amplifier

Scilab code Exa 9.5 Determine a load current in a voltage to current converter

```
1 clear;
2 clc;
3 //Example 9.5
4 Zl=0.1;
5 R1=10;
6 R2=1;
7 R3=1;
8 Rf=10;
9 Vt=-5;
10 iL=-Vt/R2;
11 printf ('\nload current=%.3f mA\n',iL)
12 vL=iL*Zl;
13 printf ('\nvoltage across the load=%.2f V\n',vL)
14 i4=vL/R2;
15 printf ('\ni4=%.3f mA\n',i4)
16 i3=i4+iL;
17 printf ('\ni3=%.3f mA\n',i3)
18 Vo=i3*R3+vL;
19 printf ('\noutput voltage=%.2f V\n',Vo)
```

```
20 i1=Vt/R1;
21 i2=i1;
22 printf( '\ni1=%f mA\n', i1)
23 printf( '\ni2=%f mA\n', i2)
```

---

### Scilab code Exa 9.9 Determine the time constant

```
1 clear;
2 clc;
3 //Example 9.9
4 //Vo=(-1/R1*C2)*integrate((-1)dt)
5 x=integrate('(-1)', 't', 0, 1)
6 Vo=10;
7 // let y=R1*C2
8 y=-x/Vo;
9 printf( '\nR1C2=%f ms\n', y)
```

---

# Chapter 10

## Integrated Circuit Biasing and Active Loads

Scilab code Exa 10.1 Design a two transistor current source

```
1 clear;
2 clc;
3 //Example 10.1
4 Vbe=0.6; //(V)
5 b=100;
6 V1=5;
7 Io=200; //micro A
8 Iref=Io*(1+2/b);
9 printf ('\nreference current=%.2f microA\n',Iref)
10 Iref=Iref*0.001; //mA
11 R1=(V1-Vbe)/Iref;
12 printf ('\nR1=% .2f KOhm\n',R1)
```

---

Scilab code Exa 10.2 Determine the change in load current

```
1 clear;
```

```

2  clc;
3 //Example 10.2
4 V1=5;
5 V2=-5;
6 R1=9.3;
7 b=50;
8 Vbe=0.7;
9 Va=80;
10 Iref=(V1-Vbe-V2)/R1;
11 printf ('\nreference current =%.3fmA\n',Iref)
12 Io=Iref/(1+2/b);
13 printf ('\noutput current=%f fmA\n',Io)
14 ro=Va/Io;
15 printf ('\nsmall signal output resistance=%f KOhm\n',
           ,ro)
16 //dIo=dVce2/ro
17 Vce2=0.7;
18 dIo=(V1-Vce2)/ro;
19 printf ('\nchange in load current=%f mA\n',dIo)
20 x=dIo/Io;
21 x=x*100;
22 printf ('\npercent change in output current=%f \n',
           x)

```

---

#### Scilab code Exa 10.4 Design a Widlar current source

```

1 clear;
2 clc;
3 //Example 10.4
4 Iref=1;
5 Io=12*10^-3;
6 V1=5;
7 V2=-5;
8 Vt=0.026;
9 Vbe=0.7;

```

```

10 R1=(V1-Vbe-V2)/Iref;
11 printf ('\nResistance R1 =%.2fKOhm\n',R1)
12 Re=(Vt/Io)*log(Iref/Io);
13 printf ('\nResistance Re =%.2fKOhm\n',Re)
14 Vbe=Io*Re;
15 printf ('\ndifference between two B-E voltages=% .2f V
    \n',Vbe)

```

---

### Scilab code Exa 10.5 Determine the change in load current

```

1 clear;
2 clc;
3 //Example 10.5
4 V1=5;
5 V2=-5;
6 R1=9.3;
7 Re=9.580;
8 Vt=0.026;
9 b=100;
10 Vbe=0.7;
11 Va=80;
12 Io=12;
13 ro2=Va/Io;
14 printf ('\nsmall signal collector resistance=% .2f
    MOhm\n',ro2)
15 Io=12*0.001; //mA
16 gm2=Io/Vt;
17 printf ('\ntransconductance=% .3f mA/V\n',gm2)
18 r=b*Vt/Io;
19 printf ('\nResistance=% .2f KOhm\n',r)
20 Ro=ro2*(1+gm2*Re*r/(Re+r));
21 printf ('\noutput resistance=% .2f MOhm\n',Ro)
22 dVc2=4;
23 dIo=dVc2/Ro;
24 printf ('\nchange in load current=% .3f microA\n',dIo)

```

```
25 Io=12; //micro A
26 x=dIo/Io;
27 x=x*100;
28 printf ('\npercent change in output current =%.4f\n', x)
```

---

#### Scilab code Exa 10.6 Design a generalized current mirror

```
1 clear;
2 clc;
3 //Example 10.6
4 V1=5;
5 V2=-5;
6 Vbe=0.6;
7 Veb=0.6;
8 Iq2=400*10^-3; //mA
9 Iref=200*10^-3; //mA
10 Iq1=Iref;
11 Iq3=Iq1;
12 Iq4=600*10^-6;
13 R1=(V1-Veb-Vbe-V2)/Iref;
14 printf ('\nResistance R1=%f KOhm\n', R1)
```

---

#### Scilab code Exa 10.7 Design a MOSFET current source

```
1 clear;
2 clc;
3 //Example 10.7
4 //uox*Cox/2=x
5 x=20*10^-6; //A/V^2
6 Vtn=1;
7 V1=5;
8 V2=0;
```

```

9 Iref=0.25*10^-3;
10 Io=0.1*10^-3;
11 Vgs2=1.85;
12 // let y=W/L
13 y2=Io/(x*(Vgs2-Vtn)^2);
14 printf ('\nwidth per length 2=%f\n',y2)
15 y1=Iref/(x*(Vgs2-Vtn)^2);
16 printf ('\nwidth per length 1=%f\n',y1)
17 Vgs1=Vgs2;
18 Vgs3=V1-V2-Vgs1;
19 printf ('\nVgs3=%f V\n',Vgs3)
20 y3=Iref/(x*(Vgs3-Vtn)^2);
21 printf ('\nwidth per length 3=%f\n',y3)

```

---

**Scilab code Exa 10.8** Compare the output resistances

```

1 clear;
2 clc;
3 //Example 10.8
4 Iref=100;
5 Io=Iref;
6 //lambda=y
7 y=0.01;
8 gm=0.5*10^3;
9 ro=1/(y*Iref);
10 printf ('\noutput resistance=%f MOhm\n',ro)
11 ro2=1;
12 ro4=1;
13 Ro=ro4+ro2*(1+gm*ro4);
14 printf ('\noutput resistance of cascode circuit=%f
MOhm\n',Ro)

```

---

**Scilab code Exa 10.9** Determine the currents and voltages

```

1 clear;
2 clc;
3 //Example 10.9
4 Idss1=2;
5 Idss2=1;
6 Vp1=-1.5;
7 Vp2=Vp1;
8 //lambda=y
9 y1=0.05;
10 y2=y1;
11 V2=-5;
12 Vds=1.5;
13 Vsmin=Vds+V2;
14 printf ('\nminimum value of Vs=%f V\n',Vsmin)
15 Io=Idss2*(1+y1*Vds);
16 printf ('\noutput current=%f mA\n',Io)
17 Vgs1=(1-sqrt(Io/Idss1))*Vp1;
18 printf ('\ngate to source voltage of Q1=%f V\n',
Vgs1)
19 V1=Vgs1+Vsmin;
20 printf ('\nV1=%f V\n',V1)

```

---

**Scilab code Exa 10.10 Calculate the open circuit voltage gain**

```

1 clear;
2 clc;
3 //Example 10.10
4 Vt=0.026;
5 Van=120;
6 Vap=80;
7 Av=-(1/Vt)/(1/Van+1/Vap);
8 printf ('\nsmall signal open circuit voltage gain=%f\n',Av)

```

---

**Scilab code Exa 10.11** Calculate the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 10.11
4 Van=120;
5 Vap=80;
6 Vt=0.026;
7 Ico=0.001;
8 //Rl=infinity
9 Av=-(1/Vt)/(1/Van+1/Vap);
10 printf ('\nsmall signal open circuit voltage gain=%.\n2
           f\n',Av)
11 Rl=100;
12 Av1=-(1/Vt)/(1/Van+1/Vap+1/Rl);
13 printf ('\nsmall signal open circuit voltage gain=%.\n2
           f\n',Av1)
14 Rl=10;
15 Av2=-(1/Vt)/(1/Van+1/Vap+1/Rl);
16 printf ('\nsmall signal open circuit voltage gain=%.\n2
           f\n',Av2)
```

---

**Scilab code Exa 10.12** Calculate the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 10.12
4 //lambda=y
5 yn=0.01;
6 yp=0.01;
7 Vtn=1;
8 Kn=1;
```

```
9 Iref=0.5;
10 gm=2*sqrt(Kn*Iref);
11 printf ('\ntransconductance =%.2fmA/V\n',gm)
12 go=yn*Iref;
13 printf ('\nsmall signal transistor conductance=%f
mA/V\n',go)
14 go2=go;
15 // for Rl=infinity
16 Av=-gm/(go+go2);
17 printf ('\nvoltage gain=%f \n',Av)
18 Rl=100; //Kohm
19 gl=0.01;
20 Av=-gm/(go+gl+go2);
21 printf ('\nvoltage gain=%f \n',Av)
```

---

# Chapter 11

## Differential and Multistage Amplifier

Scilab code Exa 11.1 Determine the quiescent collector current and collector emitt

```
1 clear;
2 clc;
3 //Example 11.1
4 V1=10;
5 V2=-10;
6 Iq=1;
7 Rc=10;
8 Vbe=0.7;
9 iC1=Iq/2;
10 iC2=iC1;
11 printf ('\ncollector currents =%.2fmA\n',iC1)
12 Vc1=V1-iC1*Rc;
13 Vc2=Vc1;
14 printf ('\ncollector voltages =%.2fV\n',Vc1)
15 Vcm=0;
16 Ve=Vcm-Vbe;
17 Vce1=Vc1-Ve;
18 printf ('\ncollector emitter voltage=%f V\n',Vce1)
19 Vcm=-5;
```

```

20 Ve=Vcm-Vbe;
21 Vce1=Vc1-Ve;
22 printf ('\ncollector emitter voltage =%.2fV\n',Vce1)
23 Vcm=5;
24 Ve=Vcm-Vbe;
25 Vce1=Vc1-Ve;
26 printf ('\ncollector emitter voltage=% .2f V\n',Vce1)

```

---

**Scilab code Exa 11.3** Determine the differential and common mode gains

```

1 clear;
2 clc;
3 //Example 11.3
4 V1=10;
5 V2=-10;
6 Iq=0.8*10^-3;
7 Rc=12000;
8 Ro=25000;
9 b=100;
10 Vt=0.026;
11 Ad=Iq*Rc/(4*Vt);
12 printf ('\n differential gain=% .3f\n',Ad)
13 Acm=-(Iq*Rc/(2*Vt))/(1+(1+b)*Iq*Ro/(Vt*b));
14 printf ('\ncommon mode gain=% .3f\n',Acm)

```

---

**Scilab code Exa 11.7** Determine the CMRR of a differential amplifier

```

1 clear;
2 clc;
3 //Example 11.7
4 Ad=92.3;
5 Acm=0.237; //mod of Acm
6 CMRR=Ad/Acm;

```

```
7 printf ('\ncommon mode rejection ratio=%f\n',CMRR)
8 CMRRdB=20*log10(CMRR);
9 printf ('\nCMRR in decibels=%f dB\n',CMRRdB)
```

---

### Scilab code Exa 11.8 Design a bipolar source

```
1 clear;
2 clc;
3 //Example 11.8
4 CMRRdB=90; //dB
5 CMRR=3.16*10^4;
6 b=100;
7 Vt=0.026;
8 Iq=0.8;
9 Ro=(2*CMRR-1)*Vt*b/((1+b)*Iq);
10 Ro=Ro*10^-3; //Mohm
11 disp(Ro,"output resistance (MOhm)")
```

---

### Scilab code Exa 11.9 Determine the differential and common mode input resistance

```
1 clear;
2 clc;
3 //Example 11.9
4 b=100;
5 Vbe=0.7;
6 Va=100;
7 Vt=0.026;
8 Iref=0.5;
9 Iq=Iref;
10 I1=Iq/2
11 Icq=I1;
12 r=b*Vt/Icq;
13 printf ('\nsmall signal parameter=%f KOhm\n',r)
```

```

14 ro=Va/Icq;
15 printf ('\nro=%f KOhm\n',ro)
16 Ro=Va/Iq;
17 printf ('\noutput resistance of Q=%f KOhm\n',Ro)
18 Rid=2*r;
19 printf ('\ndifferential mode input resistance =%f
      fKOhm\n',Rid)
20 Ricm=(1+b)*(Ro*ro/2)/(Ro+ro/2);
21 Ricm=Ricm*0.001; //Mohm
22 printf ('\ncommon mode input resistance=%f MOhm\n',
      Ricm)

```

---

**Scilab code Exa 11.10** Calculate the dc characteristics of a MOSFET diff amp

```

1 clear;
2 clc;
3 //Example 11.10
4 Kn1=0.1;
5 Kn2=Kn1;
6 Kn3=0.1;
7 Kn4=Kn3;
8 R1=30;
9 Vtn=1;
10 Rd=16;
11 // I1=(20-Vgs4)/R1 and I1=Kn3*(Vgs4-Vtn)^2
12 Vgs4=poly(0,'Vgs4')
13 p=poly([-1 -17 9],'Vgs4','c')
14 printf ('\nroots=%fV\n',roots(p))
15 Vgs4=2.40;
16 I1=(20-Vgs4)/R1;
17 printf ('\nI1=%f mA\n',I1)
18 Iq=I1;
19 Id1=Iq/2;
20 printf ('\nId1 and Id2 =%fmA\n',Id1)
21 Vgs1=sqrt(Id1/Kn1)+Vtn;

```

```

22 printf( '\nVgs1 and Vgs2 =%.2fV\n' ,Vgs1)
23 vo1=10-Id1*Rd;
24 printf( '\nvo1 and vo2=% .2f V\n' ,vo1)
25 Vds1=Vgs1-Vtn;
26 printf( '\nVds1=Vds2=Vds1( sat )=% .2f V\n' ,Vds1)
27 Vcm=vo1-Vds1+Vgs1;
28 printf( '\nVcm max=% .2f V\n' ,Vcm)
29 Vds4=Vgs4-Vtn;
30 printf( '\nVds4=% .2f V\n' ,Vds4)
31 Vcm2=Vgs1+Vds4-10;
32 printf( '\nVcm min=% .2fV\n' ,Vcm2)

```

---

**Scilab code Exa 11.11** Compare the forward transconductance

```

1 clear;
2 clc;
3 //Example 11.11
4 Kn=0.5;
5 Iq=1;
6 Vt=0.026;
7 //transconductance of the MOSFET
8 gm=2*sqrt(Kn*Iq/2);
9 printf( '\ntransconductance=% .3f mA/V\n' ,gm)
10 //transconductance of the bipolar transistor
11 gm=Iq/(2*Vt);
12 printf( '\ntransconductance=% .3f mA/V\n' ,gm)

```

---

**Scilab code Exa 11.12** Determine the differential mode voltage gain common mode vol

```

1 clear;
2 clc;
3 //Example 11.12
4 Iq=0.587;

```

```

5 Kn=1;
6 Rd=16;
7 //lambda=y
8 y=0.01;
9 Ro=1/(y*Iq);
10 printf ('\noutput resistance =%.2fKOhm\n',Ro)
11 Ad=sqrt(Kn*Iq/2)*Rd;
12 printf ('\ndifferential mode voltage gain=% .2f \n',Ad
        )
13 Acm=-sqrt(2*Kn*Iq)*Rd/(1+2*sqrt(2*Kn*Iq)*Ro);
14 printf ('\ncommon mode voltage gain=% .2f \n',Acm)
15 CMRR=20*log10(-Ad/Acm);
16 printf ('\ncommon mode rejection ratio=% .2f dB\n',
        CMRR)

```

---

**Scilab code Exa 11.13 Determine the differential mode voltage gain**

```

1 clear;
2 clc;
3 //Example 11.13
4 Iq=0.2;
5 Va=100;
6 Va2=Va;
7 Va4=Va;
8 Rl=100;
9 Vt=0.026;
10 Ad=(1/Vt)/(1/Va2+1/Va4);
11 printf ('\nopen circuit voltage gain=% .2f \n',Ad)
12 Ad=(Iq/(2*Vt))/(Iq/(2*Va2)+Iq/(2*Va4)+1/Rl);
13 printf ('\nvoltage gain=% .2f \n',Ad)

```

---

**Scilab code Exa 11.15 Determine the differential mode voltage gain**

```

1 clear;
2 clc;
3 //Example 11.15
4 Kn=0.2;
5 Idq=0.1;
6 ro4=1000; //Kohm
7 ro6=1000; //KOhm
8 ro2=ro4;
9 //lambda=y
10 y=0.01;
11 gm=2*sqrt(Kn*Idq);
12 printf ('\ntransconductance=%f mA/V\n',gm)
13 ro=1/(y*Idq);
14 printf ('\noutput resistance=%f f KOhm\n',ro)
15 Ro=ro4+ro6*(1+gm*ro);
16 Ro=Ro*0.001; //Mohm
17 printf ('\noutput resistance of the cascode active
load=%f fMohm\n',Ro)
18 Ro=Ro*1000; //KOhm
19 Ad=gm*ro2*Ro/(ro4+Ro);
20 printf ('\ndifferential mode voltage gain=%f\n',Ad)

```

---

**Scilab code Exa 11.16** Calculate the input resistance and the small signal voltage

```

1 clear;
2 clc;
3 //Example 11.16
4 Iq=0.2;
5 Ic1=Iq;
6 Icb=1;
7 R4=10;
8 R3=0.2;
9 b=100;
10 Va=100;
11 Vt=0.026;

```

```

12 Ri=2*(1+b)*b*Vt/Iq;
13 Ri=Ri*0.001; //MOhm
14 printf ('\ninput resistance=%f MOhm\n',Ri)
15 R11=b*Vt/Iq;
16 printf ('\nresistance R11=%f KOhm\n',R11)
17 Re=R11*R3/(R11+R3);
18 printf ('\nRe=%f KOhm\n',Re)
19 gm11=Iq/Vt;
20 printf ('\ngm11=%f mA/V\n',gm11)
21 ro11=Va/Iq;
22 printf ('\nro11 =%f fKOhm\n',ro11)
23 Rc11=ro11*(1+gm11*Re);
24 Rc11=Rc11*0.001; //MOhm
25 printf ('\nRc11=%f MOhm\n',Rc11)
26 r8=b*Vt/Icb;
27 printf ('\nresistance=%f fKOhm\n',r8)
28 //answer of following given in the book is wrong
29 Rb8=r8+(1+b)*R4;
30 Rb8=Rb8*0.001; //MOhm
31 printf ('\nRb8 =%f fMOhm\n',Rb8)
32 R17=Rc11*Rb8/(Rc11+Rb8);
33 printf ('\nR17=%f MOhm\n',R17)
34 Av=Iq*R17/(2*Vt);
35 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

### Scilab code Exa 11.17 Calculate the output resistance

```

1 clear;
2 clc;
3 //Example 11.17
4 Va=100;
5 R4=10;
6 b=100;
7 Rc11=1.26*10^3;
8 r8=2.6;

```

```

9 Iq=0.2;
10 Rc7=Va/Iq;
11 printf( '\nRc7=%f KOhm\n' ,Rc7)
12 Z=Rc11*Rc7/(Rc11+Rc7);
13 printf( '\nZ=%f KOhm\n' ,Z)
14 x=(r8+Z)/(1+b);
15 Ro=R4*x/(R4+x);
16 printf( '\noutput resistance=%f KOhm\n' ,Ro)

```

---

**Scilab code Exa 11.19** Determine the differential mode voltage gain

```

1 clear;
2 clc;
3 //Example 11.19
4 b=100;
5 Vt=0.026;
6 Rc=20;
7 Ir4=0.4;
8 Iq=Ir4;
9 Ir6=Ir4;
10 r4=b*Vt/Ir4;
11 printf( '\nr4=%f KOhm\n' ,r4)
12 r3=b^2*Vt/Ir4;
13 printf( '\nr3=%f KOhm\n' ,r3)
14 Ri2=r3+(1+b)*r4;
15 printf( '\ninput resistance=%f KOhm\n' ,Ri2)
16 gm=Iq/(2*Vt);
17 printf( '\ntransconductance=%f mA/V\n' ,gm)
18 Ad1=gm*Rc*Ri2/(2*(Rc+Ri2));
19 printf( '\ngain of differential amplifier stage=%f\n' ,Ad1)
20 r5=b*Vt/Ir6;
21 printf( '\nr5 =%f KOhm\n' ,r5)
22 Ir7=2;
23 r6=b*Vt/Ir7;

```

```

24 printf( '\nr6=%f KOhm\n',r6)
25 R6=16.5;
26 R7=5;
27 Ri3=r5+(1+b)*(R6+r6+(1+b)*R7);
28 Ri3=Ri3*0.001; //MOhm
29 printf( '\nRi3=%f MOhm\n',Ri3)
30 Rs=5;
31 A2=Ir4*Rs/(2*Vt);
32 printf( '\nvoltage gain A2=%f\n',A2)
33 A3=1; //vo/vo3
34 Ad=Ad1*A2*A3;
35 printf( '\nsmall signal voltage gain=%f\n',Ad)

```

---

**Scilab code Exa 11.20** Determine the zero and pole frequencies

```

1 clear;
2 clc;
3 //Example 11.20
4 Ro=10000000;
5 Co=1*10^-12;
6 Rb=500;
7 r=10000;
8 b=100;
9 f=1/(2*pi*Ro*Co);
10 f=f*0.001; //KHz
11 printf( '\nfrequency of the zero=%f KHz\n',f)
12 Req=Ro*(1+Rb/r)/(1+Rb/r+2*(1+b)*Ro/r);
13 printf( '\nReq=%f Ohm\n',Req)
14 f=1/(2*pi*Req*Co);
15 f=f*10^-9; //GHz
16 printf( '\nfrequency of the pole=%f GHz\n',f)

```

---

# Chapter 12

## Feedback and Stability

Scilab code Exa 12.1 Calculate the feedback transfer function

```
1 clear;
2 clc;
3 //Example 12.1
4 A=10^5; //open loop gain
5 Af=50; //closed loop gain
6 b=(A/Af-1)/A;
7 printf ('\nfeedback transfer function=%f\n',b)
8 A=-10^5;
9 Af=-50;
10 b=(A/Af-1)/A;
11 printf ('\nfeedback transfer function=%f\n',b)
```

---

Scilab code Exa 12.2 Calculate the percent change in the closed loop gain Af

```
1 clear;
2 clc;
3 //Example 12.2
4 A=10^5;
```

```

5 Af=50;
6 b=0.019999;
7 dA=10^4;
8 dAf=Af*dA/(A*(1+b*A));
9 printf ('\n dAf=%e\n',dAf)
10 //x=dAf/Af
11 x=dAf/Af;
12 x=x*100;
13 printf ('\n percent change dAf/Af=%f\n',x)

```

---

### Scilab code Exa 12.3 Determine the bandwidth of a feedback amplifier

```

1 clear;
2 clc;
3 //Example 12.3
4 Ao=10^4;
5 wh=2*pi*100; // rad/s
6 Af=50;
7 //x=(1+bAo)
8 x=Ao/Af;
9 printf ('\n(1+bAo)=%f\n',x)
10 wfh=wh*x;
11 printf ('\n closed loop bandwidth=%f\n',wfh)

```

---

### Scilab code Exa 12.5 Determine the input resistance and output resistance

```

1 clear;
2 clc;
3 //Example 12.5
4 Av=10^5;
5 Avf=50;
6 Rf=10; //Kohm
7 Ro=20000; //Ohm

```

```

8 //x=(1+bvAv)
9 x=Av/Avf;
10 printf( '\n(1+bvAv)=%e\n' ,x)
11 Rif=Rf*x;
12 Rif=Rif*0.001; //MOhm
13 printf( '\ninput resistance=%.2 f MOhm\n' ,Rif)
14 Rof=Ro/x;
15 printf( '\noutput resistance=%.2 f Ohm\n' ,Rof)

```

---

**Scilab code Exa 12.6** Determine the input resistance and output resistance

```

1 clear;
2 clc;
3 //Example 12.6
4 Af=10^5;
5 Aif=50;
6 Rf=10000;
7 Ro=20;
8 //x=(1+biAi)
9 x=Af/Aif;
10 printf( '\n(1+biAi)=%e\n' ,x)
11 Rif=Rf/x;
12 printf( '\ninput resistance =%.2 fOhm\n' ,Rif)
13 Rof=Ro*x;
14 Rof=Rof*0.001; //Mohm
15 printf( '\noutput resistance=%.2 f MOhm\n' ,Rof)

```

---

**Scilab code Exa 12.7** Determine the expected input resistance

```

1 clear;
2 clc;
3 //Example 12.7
4 Ri=50;

```

```

5 R1=10;
6 R2=90;
7 Av=10^4;
8 bv=1/(1+R2/R1);
9 printf ('\nfeedback transfer function=%f\n',bv)
10 Rif=Ri*(1+bv*Av);
11 Rif=Rif*0.001; //Mohm
12 printf ('\ninput resistance=%f MOhm\n',Rif)

```

---

### Scilab code Exa 12.11 Determine the transconductance gain of a transistor feedback

```

1 clear;
2 clc;
3 //Example 12.11
4 hFE=100;//transistor parameter
5 Vbe=0.7;
6 Vcc=10;
7 R1=55;
8 R2=12;
9 Re=1;
10 Rc=4;
11 Rl=4;
12 Icq=0.983;
13 Vceq=5.08;
14 Vt=0.026;
15 r=hFE*Vt/Icq;
16 printf ('\nsmall signal parameter resistance=%f
          KOhm\n',r)
17 gm=Icq/Vt;
18 printf ('\ntransconductance=%f mA/V\n',gm)
19 Agf=-gm*(Rc/(Rc+Rl))/(1+Re*(gm+1/r));
20 printf ('\ntransconductance transfer function=%f mA
          /V\n',Agf)
21 //as first approximation
22 Agf2=-1/Re;

```

```
23 printf( '\nAgf=%f mA/V\n' , Agf2)
24 Avf=Agf*R1;
25 printf( '\nvoltage gain=%f\n' , Avf)
```

---

### Scilab code Exa 12.16 Determine the loop gain

```
1 clear;
2 clc;
3 //Example 12.15
4 //Determine the loop gain fig12.45(a)
5 hFE=100;
6 Vbe=0.7;
7 Icq=0.492;
8 r=5.28;
9 gm=18.9;
10 Rs=10;
11 R1=51;
12 R2=5.5;
13 Re=0.500;
14 Rc=10;
15 Rf=82;
16 x=r*R2/(r+R2);
17 y=R1*x/(x+R1);
18 t=Rs*y/(y+Rs);
19 Req=t;
20 printf( '\nequivalent resistance=%f KOhm\n' ,t)
21 T=gm*Rc*Req/(Rc+Rf+Req);
22 printf( '\nthe loop gain=%f\n' ,T)
```

---

### Scilab code Exa 12.19 Determine the stability of an amplifier

```
1 clear;
2 clc;
```

```

3 //Example 12.19
4 //T=b*100/(sqrt(1+(f/10^5)^2)) angle=-3tan^-1(f/10^5)
5 //stable at f180 at which phase becomes -180 degrees
6 //-3*atan(f180/10^5)=-180
7 f180=tand(180/3)*10^5;
8 printf ('\n frequency at -180 degree=%ef Hz\n',f180)
9 b=0.2;
10 T=b*100/(sqrt(1+(f180/10^5)^2))^3;
11 printf ('\n magnitude of the loop gain=% .2f\n',T)
12 b=0.02;
13 T=b*100/(sqrt(1+(f180/10^5)^2))^3;
14 printf ('\n magnitude of the loop gain=% .2f\n',T)

```

---

**Scilab code Exa 12.22** Determine the shift in the 3dB frequency

```

1 clear;
2 clc;
3 //Example 12.22
4 Ao=10^6;
5 fPD=0.010; //KHz
6 b=0.01;
7 Af=Ao/(1+b*Ao);
8 printf ('\n low frequency closed loop gain=% .2f\n',Af)
9 fc=fPD*(1+b*Ao);
10 printf ('\n closed loop 3dB frequency=% .2f KHz\n',fc)

```

---

**Scilab code Exa 12.23** Determine the shift in the 3dB frequency

```

1 clear;
2 clc;
3 //Example 12.23
4 A=10^3;
5 Cf=30*10^-12; // feedback capacitor (F)

```

```
6 R2=5*10^5;
7 Cm=Cf*(1+A);
8 printf ('\nMiller capacitance=%e F\n',Cm)
9 fp=1/(2*pi*R2*Cm);
10 printf ('\ndominant pole frequency =%.2 fHz\n',fp)
```

---

# Chapter 13

## Operational Amplifier Circuits

Scilab code Exa 13.1 Calculate the dc currents

```
1 clear;
2 clc;
3 //Example 13.1
4 V1=15; //positive supply voltage
5 V2=-15; //negative supply voltage
6 Veb12=0.6;
7 Vbe11=0.6;
8 Rs=40;
9 Iref=(V1-V2-Veb12-Vbe11)/Rs;
10 printf ('\nreference current=%.2f mA\n',Iref)
11 Ic10=19;
12 Ic1=Ic10/2;
13 printf ('\nIc1=Ic2=Ic3=Ic4= %.3f microA \n',Ic1)
14 Ic1=Ic1*0.001; //mA
15 Vbe7=0.6;
16 Vbe6=0.6;
17 Ic6=Ic1;
18 R2=1;
19 Vc6=Vbe7+Vbe6+Ic6*R2+V2;
20 printf ('\nvoltage at collector of Q6=%.2f V\n',Vc6)
```

---

### Scilab code Exa 13.2 Calculate the bias currents

```
1 clear;
2 clc;
3 //Example 13.2
4 Iref=0.72;
5 Ic17=0.75*Iref;
6 printf ('\ncollector currents in Q17=%f mA\n',Ic17)
7 b=200;
8 Ib17=Ic17/b;
9 Ie17=Ic17;
10 R8=0.100;
11 Vbe17=0.6;
12 R9=50;
13 Ic16=Ib17+(Ie17*R8+Vbe17)/R9;
14 Ic16=Ic16*1000;
15 printf ('\ncollector current in Q16=%f microA\n',
           Ic16)
```

---

### Scilab code Exa 13.3 Calculate the bias currents

```
1 clear;
2 clc;
3 //Example 13.3
4 Is1=10^-14; //reverse saturation currents for Q18 Q19
5 Is2=3*10^-14; //reverse saturation currents for Q14
                 Q20
6 Iref=0.72;
7 Vt=0.026;
8 Ic13a=0.25*Iref;
9 printf ('\nIc13a=%f mA\n',Ic13a)
10 Vbe19=0.6;
```

```

11 R10=50;
12 Ir1o=Vbe19/R10;
13 printf ('\ncurrent in Ro=%f mA\n',Ir1o)
14 Ic19=Ic13a-Ir1o;
15 printf ('\ncurrent in Q19 =%.3fmA\n',Ic19)
16 Ic19=Ic19*0.001; //A
17 Vbe19=Vt*log(Ic19/Is1);
18 printf ('\nB-E voltage of Q19=%f V\n',Vbe19)
19 b=200;
20 Ic19=Ic19*10^6; //micro A
21 Iv19=Ic19*1000;
22 Ib18=Ic19/b;
23 Ir1o=Ir1o*1000;
24 printf ('\nbase current in Q18=%f microA\n',Ib18)
25 Ic18=Ir1o+Ib18;
26 printf ('\n currents in Q18=%f microA\n',Ic18)
27 Ic18=Ic18*10^-6;
28 Vbe18=Vt*log(Ic18/Is1);
29 printf ('\nB-E voltage of Q18=%f V\n',Vbe18)
30 Vbb=Vbe18+Vbe19;
31 printf ('\nvoltage difference Vbb=%f V\n',Vbb)
32 Ic14=Is2*exp(Vbb/(2*Vt));
33 Ic14=Ic14*10^6; //micro A
34 printf ('\n quiescent currents in Q14 and Q20 =%.
fmicroA\n',Ic14)

```

---

**Scilab code Exa 13.4** Determine the small signal differential voltage gain

```

1 clear;
2 clc;
3 //Example 13.4
4 b=200;
5 Va=50
6 Vt=0.026;
7 R2=1;

```

```

8 Ic6=0.0095;
9 Ic4=Ic6;
10 Ic16=0.0158;
11 Ic17=0.54;
12 r17=b*Vt/Ic17;
13 printf ('\ninput resistance to gain stage=%.2 f KOhm\n',
14 ,r17)
15 R9=50;
16 R8=0.100;
17 x=r17+(1+b)*R8;
18 Re=x*R9/(x+R9);
19 printf ('\nRe=%0.3 f KOhm\n',Re)
20 r16=b*Vt/Ic16;
21 r16=(1+b)*Re;
22 Ri2=r16+R16;
23 printf ('\nRi2=%0.2 f KOhm\n',Ri2)
24 r6=b*Vt/Ic6;
25 printf ('\nresistance of the active load=%0.2 f KOhm\n',
26 ,r6)
27 gm=Ic6/Vt;
28 printf ('\ntransconductance =%.3 fmA/V\n',gm)
29 ro6=Va/Ic6;
30 ro6=ro6*0.001; //MOhm
31 printf ('\nro6=%0.2 f MOhm\n',ro6)
32 R=ro6*(1+gm*R2*r6/(R2+r6));
33 printf ('\nactive load=%0.2 f
34 MOhm\n',R)
35 ro4=Va/Ic4;
36 ro4=ro4*0.001; //Mohm
37 printf ('\nResistance ro4=%0.2 f KOhm\n',ro4)
38 Icq=9.5;
39 x=Ri2*R/(R+Ri2);
40 y=ro4*x/(ro4+x);
41 Ad=-y*Icq/Vt;
42 printf ('\nsmall signal differential voltage gain=%0.2
43 f\n',Ad)

```

---

**Scilab code Exa 13.5 Determine the small signal voltage gain**

```
1 clear;
2 clc;
3 //Example 13.5
4 bp=50;
5 bn=200;
6 Va=50;
7 R9=50;
8 R8=0.100;
9 Rl=2;
10 Vt=0.026;
11 Ri2=4070;
12 Ic20=0.138;
13 r20=bp*Vt/Ic20;
14 printf ('\n r20=%f KOhm\n',r20)
15 R20=r20+(1+bp)*Rl;
16 printf ('\n R20=%f KOhm\n',R20)
17 Ic13A=0.18;
18 R19=Va/Ic13A;
19 printf ('\n R19=%f KOhm\n',R19)
20 r22=bp*Vt/Ic13A;
21 printf ('\n r22=%f KOhm\n',r22)
22 Ri3=r22+(1+bp)*R19*R20/(R19+R20);
23 Ri3=Ri3*0.001; //MOhm
24 printf ('\n input resistance to the output stage=%f
    MOhm\n',Ri3)
25 Ic13B=0.54;
26 R=Va/Ic13B;
27 printf ('\n effective resistance of the active load=%
    .2 f KOhm\n',R)
28 Ic17=Ic13B;
29 R17=Va/Ic17;
30 printf ('\n output resistance Ro17 =%f KOhm\n',R17)
```

```

31 Ri3=Ri3*1000; //KOhm
32 r17=9.63;
33 x=R17*Ri3/(Ri3+R17);
34 y=x*R/(R+x);
35 A=-bn*R9*(1+bn)*y/(Ri2*(R9+r17+(1+bn)*R8));
36 printf ('\nsmall signal voltage gain=%f\n',A)

```

---

### Scilab code Exa 13.6 Calculate the output resistance

```

1 clear;
2 clc;
3 //Example 13.6
4 Ic20=2;
5 bn=200;
6 bp=50;
7 Va=50;
8 r17=9.63;
9 r22=7.22;
10 R20=0.260;
11 gm17=20.8;
12 ro17=92.6;
13 Ro13B=92.6;
14 R8=0.100;
15 Rc17=ro17*(1+gm17*R8*r17/(R8+r17));
16 printf ('\nRc17=%f KOhm\n',Rc17)
17 Rc22=(r22+Rc17*Ro13B/(Rc17+Ro13B))/(1+bp);
18 printf ('\nRc22=%f KOhm\n',Rc22)
19 Ic13A=0.18;
20 Rc19=Va/Ic13A;
21 printf ('\nRc19=%f KOhm\n',Rc19)
22 Rc20=(R20+Rc22*Rc19/(Rc22+Rc19))/(1+bp);
23 printf ('\nRc20=%f KOhm\n',Rc20)
24 Rc20=Rc20*1000; //Ohm
25 R3=22;
26 Ro=R3+Rc20;

```

```
27 printf ('\noutput resistance=%f Ohm\n', Ro)
```

---

Scilab code Exa 13.7 Determine the dominant pole frequency of the 741 op amp

```
1 clear;
2 clc;
3 //Example 13.7
4 Av2=285;
5 C1=30;
6 Ci=C1*(1+Av2);
7 printf ('\ninput capacitance=%f pF\n', Ci)
8 Ri2=4.07;
9 Ract=7.18;
10 ro4=5.26;
11 Ro1=Ract*ro4/(Ract+ro4);
12 printf ('\ngate stage input resistance=%fMOhm \n',
Ro1)
13 Req=Ro1*Ri2/(Ri2+Ro1);
14 printf ('\nequivalent resistance=%f MOhm\n', Req)
15 Req=Req*10^6; //Ohm
16 Ci=Ci*10^-12; //F
17 fPD=1/(2*pi*Req*Ci);
18 printf ('\ndominant pole frequency =%fHz\n', fPD)
```

---

Scilab code Exa 13.9 Determine the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 13.9
4 //lambda=y
5 y=0.02;
6 //W/L=x and u*Cox/2=t
7 x=12.5;
```

```

8 t=10;
9 Kp1=x*t;
10 printf ('\nconduction parameters of M1 and M2=%.
           fmicroA/V^2\n',Kp1)
11 Kp1=Kp1*0.001; //mA/V^2
12 Id=0.0199;
13 ro2=1/(y*Id);
14 ro2=ro2*0.001; //Mohm
15 printf ('\noutput resistance=%.2f MOhm\n',ro2)
16 Iq=0.0397;
17 ro2=ro2*1000; //Kohm
18 ro4=ro2;
19 Ad=sqrt(2*Kp1*Iq)*ro2*ro4/(ro2+ro4);
20 printf ('\nthe gain of input stage=%.2f \n',Ad)
21 Kn7=0.250;
22 Id7=Iq;
23 gm7=2*sqrt(Kn7*Id7)
24 printf ('\ntransconductance of M7=% .2f mA/V\n',gm7)
25 ro7=1/(y*Id7);
26 ro7=ro7*0.001;
27 printf ('\noutput resistance of M7 and M8 =%.2fMOhm\n
           ',ro7)
28 ro7=ro7*1000; //Kohm
29 ro8=ro7;
30 Av2=gm7*ro7*ro8/(ro7+ro8);
31 printf ('\ngain of the second stage=% .2f\n',Av2)
32 Av=Ad*Av2;
33 printf ('\noverall voltage gain=% .2f\n',Av)

```

---

**Scilab code Exa 13.10 Determine the differential mode voltage gain**

```

1 clear;
2 clc;
3 //Example 13.10
4 Iref=100;

```

```

5 Kn=80;
6 Kp=40;
7 //W/L=x
8 x=25;
9 //lambda=y
10 y=0.02;
11 Id=Iref/2;
12 gm1=2*sqrt(Kp*x*Id/2);
13 printf ('\ntransconductance gm1=gm8=%f microA/V\n', gm1)
14 gm6=2*sqrt(Kn*x*Id/2);
15 printf ('\ntransconductance=%f microA/V\n', gm6)
16 ro1=1/(y*Id);
17 ro8=ro1;
18 ro6=ro1;
19 ro10=ro1;
20 printf ('\noutput resistance ro1=ro8=ro6=ro10=%f
MOhm\n', ro1)
21 Id4=Iref;
22 ro4=1/(y*Id4);
23 printf ('\nro4=%f MOhm\n', ro4)
24 Ro8=gm1*ro8*ro10;
25 printf ('\ncomposite output resistances =%f MOhm\n',
Ro8)
26 Ro6=gm6*ro6*ro4*ro1/(ro4+ro1);
27 printf ('\ncomposite output resistances=%f MOhm\n',
Ro6)
28 Ad=gm1*Ro6*Ro8/(Ro6+Ro8);
29 printf ('\ndifferential voltage gain=%f\n', Ad)

```

---

**Scilab code Exa 13.12 Determine the small signal voltage gain**

```

1 clear;
2 clc;
3 //Example 13.12

```

```

4 Kp=0.6;
5 bn=200;
6 Va=50;
7 Vt=0.026;
8 Ic13=0.20;
9 Ri2=bn*Vt/Ic13;
10 printf ('\ninput resistance to the gain stage=%f
           KOhm\n',Ri2)
11 Iq5=Ic13;
12 Ad=sqrt(2*Kp*Iq5)*Ri2;
13 printf ('\nsmall signal voltage gain=%f\n',Ad)

```

---

Scilab code Exa 13.13 Determine the small signal voltage gain

```

1 clear;
2 clc;
3 //Example 13.13
4 Va=150;
5 Vt=0.026;
6 Ic13=0.2;
7 gm13=Ic13/Vt;
8 printf ('\ntransconductance=%f mA/V\n',gm13)
9 ro13=Va/Ic13;
10 printf ('\noutput resistance=%f f KOhm\n',ro13)
11 Av2=gm13*ro13;
12 printf ('\nvoltage gain=%f \n',Av2)

```

---

Scilab code Exa 13.14 Determine the dominant pole frequency and unity gain bandwidth

```

1 clear;
2 clc;
3 //Example 13.14
4 Av2=5768;

```

```
5 C1=12;
6 Ci=C1*(1+Av2);
7 printf ('\n effective input capacitance=%f pF\n',Ci)
8 Ri2=26000; //gain stage input resistance (Ohm)
9 Ci=Ci*10^-12; //F
10 fPD=1/(2*pi*Ri2*Ci);
11 printf ('\n dominant pole frequency=%f Hz\n',fPD)
12 Av=73254;
13 fT=fPD*Av;
14 fT=fT*10^-6; //MHz
15 printf ('\n unity gain bandwidth=%f MHz\n',fT)
```

---

# Chapter 14

## Nonideal Effects in Operational Amplifier Circuits

Scilab code Exa 14.2 Determine the closed loop input resistance

```
1 clear;
2 clc;
3 //Example 14.2
4 R2=10000;
5 Ri=10000;
6 Aol=10^5;
7 Rif=1/(1/Ri+(1+Aol)/R2);
8 printf ('\nclosed loop input resistance =%.2fOhm\n',Rif)
```

---

Scilab code Exa 14.3 Determine the closed loop input resistance

```
1 clear;
2 clc;
3 //Example 14.3
4 Aol=10^5;
```

```
5 Ri=10;
6 R1=10;
7 R2=R1;
8 Rif=(Ri*(1+Ao1)+R2*(1+Ri/R1))/(1+R2/R1);
9 Rif=Rif*0.001; //Mohm
10 printf ('\ninput resistance =%.fMOhm\n',Rif)
```

---

**Scilab code Exa 14.5** Determine the unity gain bandwidth and the closed loop gain

```
1 clear;
2 clc;
3 //Example 14.5
4 Ao=2*10^5;
5 fPD=5;
6 fT=fPD*Ao;
7 printf ('\nunity gain bandwidth=%e Hz\n',fT)
8 f3dB=20*10^3;
9 Acl=fT/f3dB;
10 printf ('\nclosed loop gain=%.2f\n',Acl)
```

---

**Scilab code Exa 14.6** Calculate the slew rate of the 741 op amp

```
1 clear;
2 clc;
3 //Example 14.6
4 Iq=19*10^-6;
5 C1=30*10^-12;
6 SR=Iq/C1;
7 SR=SR*10^-6;
8 printf ('\nslew rate=%.2f V/micros\n',SR)
```

---

**Scilab code Exa 14.7** Determine the small signal bandwidth of an amplifier and full

```
1 clear;
2 clc;
3 //Example 14.7
4 fT=1000; //KHz
5 Aclo=10;
6 SR=1*10^3;
7 Vpo=10;
8 f3dB=fT/Aclo;
9 printf ('\nsmall signal closed loop bandwidth=%f f
          KHz\n',f3dB)
10 fmax=SR/(2*pi*Vpo);
11 printf ('\nfull power bandwidth=%f f KHz\n',fmax)
```

---

**Scilab code Exa 14.8** Calculate the offset voltage in bipolar diff amp

```
1 clear;
2 clc;
3 //Example 14.8
4 Is1=10^-14;
5 Is2=1.05*10^-14;
6 Vt=0.026;
7 Vos=Vt*log(Is2/Is1);
8 printf ('\nthe offset voltage =%fV\n',Vos)
```

---

**Scilab code Exa 14.10** Calculate the offset voltage in MOSFET diff amp

```
1 clear;
2 clc;
3 //Example 14.10
4 Kn1=105;
5 Kn2=100;
```

```

6 Iq=200;
7 dKn=Kn1-Kn2;
8 printf ('\n difference in conduction parameter=%.2f
      microA/V^2\n',dKn)
9 Kn=(Kn1+Kn2)/2;
10 printf ('\naverage of the conduction parameter=%.2f
      microA/V^2\n',Kn)
11 Vos=sqrt(Iq/(2*Kn))*dKn/(2*Kn);
12 printf ('\noffset voltage=%f V\n',Vos)

```

---

**Scilab code Exa 14.11** Determine the range of voltage produced by an offset voltage

```

1 clear;
2 clc;
3 //Example 14.11
4 Rs=100;
5 R4=100000;
6 R3=100000;
7 V1=15;
8 V2=-15;
9 Vy=Rs*V1/(Rs+R4);
10 Vy=Vy*1000; //mV
11 printf ('\nVoltage Vy =%.2fmV\n',Vy)

```

---

**Scilab code Exa 14.13** Determine the bias current effect

```

1 clear;
2 clc;
3 //Example 14.13
4 R1=10;
5 R2=100;
6 Ib1=1.1*10^-3;
7 Ib2=1*10^-3;

```

```
8 vo=Ib1*R2;
9 printf ('\noutput voltage =%.2fV\n',vo)
10 R3=R1*R2/(R1+R2);
11 printf ('\nR3=% .2f KOhm\n',R3)
12 vo=R2*(Ib1-Ib2);
13 printf ('\noutput voltage=% .2f V\n',vo)
```

---

# Chapter 15

## Applications and Design of Integrated Circuits

Scilab code Exa 15.2 Determine the clock frequency

```
1 clear;
2 clc;
3 //Example 15.2
4 C=20*10^-6;
5 Req=1000;
6 fC=1/(C*Req);
7 printf ('\nclock frequency =%.2fkHz\n',fC)
```

---

Scilab code Exa 15.3 Design a one pole low pass switched capacitor filter

```
1 clear;
2 clc;
3 //Example 15.3
4 fC=10000;
5 f3dB=1000;
6 //x=C2/C1
```

```
7 x=2*pi*f3dB/fC;
8 printf ('\\n capacitances C2/C1=% .3f \\n ',x)
```

---

Scilab code Exa 15.4 Determine the oscillation frequency and required amplifier gain

```
1 clear;
2 clc;
3 //Example 15.4
4 C=0.1*10^-6;
5 R=1000;
6 fo=1/(2*pi*R*C*sqrt(3));
7 printf ('\\n the oscillation frequency =%.2f Hz\\n ',fo)
8 //minimum amplifier gain=8
9 R=1; //KOhm
10 R2=8*R;
11 printf ('\\n R2=% .f KOhm\\n ',R2)
```

---

Scilab code Exa 15.6 Determine the hysteresis width of a particular Schmitt trigger

```
1 clear;
2 clc;
3 //Example 15.6
4 R1=10000;
5 R2=90000;
6 Vh=10;
7 Vl=-10;
8 Vth=R1*Vh/(R1+R2);
9 printf ('\\n upper crossover voltage=% .f V\\n ',Vth)
10 Vtl=R1*Vl/(R1+R2);
11 printf ('\\n lower crossover voltage=% .f V\\n ',Vtl)
12 x=Vth-Vtl;
13 printf ('\\n hysteresis width =% .f V\\n ',x)
```

---

**Scilab code Exa 15.7 Design a Schmitt trigger circuit**

```
1 clear;
2 clc;
3 //Example 15.7
4 Vs=2;
5 Vh=15;
6 Vl=-15;
7 // hysteresis width=x
8 x=60*0.001; //(V)
9 //Vth-Vt1=(R1/(R1+R2))*(Vh-Vl)
10 //R2/R=y
11 y=(Vh-Vl)/x-1;
12 printf ('\nR2/R1=%f \n',y)
13 Vref=(1+1/y)*Vs;
14 printf ('\nreference voltage=%f V\n',Vref)
```

---

**Scilab code Exa 15.10 Design the 555IC as a monostable multivibrator**

```
1 clear;
2 clc;
3 //Example 15.10
4 C=15*10^-9;
5 T=100*10^-6; //(s) time
6 R=T/(1.1*C);
7 R=R*0.001; //Kohm
8 printf ('\nResistance R=%f f KOhm\n',R)
```

---

**Scilab code Exa 15.13 Design the supply voltage**

```

1 clear;
2 clc;
3 //Example 15.13
4 Rl=10; //load resistance
5 P1=20; //power delivered to the load
6 Ps=20; //(W)
7 Vp=sqrt(2*Rl*P1);
8 printf ('\npeak output voltage=%f V\n',Vp)
9 Ip=Vp/Rl;
10 printf ('\npeak load current =%.2fA\n',Ip)
11 Vs=%pi*Rl*Ps/Vp;
12 printf ('\nrequired supply voltage=%f V\n',Vs)

```

---

**Scilab code Exa 15.14** Determine the output resistance and load regulation

```

1 clear;
2 clc;
3 //Example 15.14
4 Vonl=5;
5 Vofl=4.96;
6 I1=0.005;
7 I2=1.5;
8 dVo=Vonl-Vofl;
9 dIo=I1-I2;
10 Rvf=-dVo/dIo;
11 printf ('\noutput resistance=%f Ohm\n',Rvf)
12 LR=100*(Vonl-Vofl)/Vonl;
13 printf ('\nload regulation =%.2f\n',LR)

```

---

**Scilab code Exa 15.15** Determine the output resistance and variation in output volt

```

1 clear;
2 clc;

```

```

3 //Example 15.15
4 Aol=1000;
5 Vref=5;
6 Vo=10;
7 Io=0.1*0.001;
8 Vt=0.026;
9 Rof=2*Vt*Vo/(Io*Vref*Aol);
10 printf ('\noutput resistance=%f mOhm\n',Rof)
11 //dVo/Vo=V and dIo/Io=I
12 //V=-I*2*Vt/(Vref*Aol)
13 //V/I=x
14 x=-2*Vt/(Vref*Aol);
15 printf ('\npercent change=%e\n',x)

```

---

**Scilab code Exa 15.16** Determine the bias current temperature compensated reference

```

1 clear;
2 clc;
3 //Example 15.16
4 Vz=6.3;
5 Vbe=0.6;
6 Veb=0.6;
7 Vo=8;
8 R1=3.9;
9 R2=3.4;
10 R3=0.576;
11 Ic3=(Vz-3*Vbe)/(R1+R2+R3);
12 printf ('\nbias current =%f mA\n',Ic3)
13 Vb7=Ic3*R1+2*Vbe;
14 printf ('\ntemperature compensated reference voltage=%f V\n',Vb7)
15 R13=2.23;
16 R12=R13*Vo/Vb7-R13;
17 printf ('\nR12=%f KOhm\n',R12)

```

---

# Chapter 16

## MOSFET Digital Circuits

Scilab code Exa 16.3 Design the aspect ratio and determine the power dissipation

```
1 clear;
2 clc;
3 //Example 16.3
4 Vdd=5;
5 Vtnd=0.8;
6 Vtnl=0.8;
7 Kn=35;
8 Vo=0.1;
9 Vi=4.2;
10 //W/L=Y
11 yl=0.5;
12 //Kd/Kl=x
13 x=(Vdd-Vo-Vtnl)^2/(2*Vo*(Vi-Vtnd)-Vo^2);
14 printf ('\nKd/Kl=%f\n',x)
15 //Kd/Kl=yd/yl
16 yd=12.6
17 yl=0.5
18 iD=Kn*yl*(Vdd-Vo-Vtnl)^2/2;
19 printf ('\ndrain current =%.2f microA\n',iD)
20 P=iD*Vdd;
21 printf ('\npower dissipation=%.2f microW\n',P)
```

---

**Scilab code Exa 16.4** Design the aspect ratio and determine the power dissipation

```
1 clear;
2 clc;
3 //Example 16.4
4 Vdd=5;
5 Vtnd=0.8;
6 Vtnl=-2;
7 Kn=35;
8 Vo=0.1;
9 Vi=5;
10 //W/L=Y
11 yl=0.5;
12 //Kd/Kl=x
13 x=(-Vtnl)^2/(2*Vo*(Vi-Vtnd)-Vo^2);
14 printf ('\nKd/Kl=%f\n',x)
15 //Kd/Kl=yd/yl
16 yd=2.41
17 yl=0.5
18 iD=Kn*yl*(-Vtnl)^2/2;
19 printf ('\n drain current=%f microA\n',iD)
20 P=iD*Vdd;
21 printf ('\n power dissipation =%f microW\n',P)
```

---

**Scilab code Exa 16.5** Determine the noise margin of an inverter with enhancement lo

```
1 clear;
2 clc;
3 //Example 16.5
4 Voh=4.2;
5 Vol=0.1;
```

```

6 //x=Kd/Kl
7 x=25.1;
8 Vdd=5;
9 Vtnl=0.8;
10 Vohu=4.2;
11 Vil=0.8;
12 Vtnd=0.8;
13 Vih=Vtnd+(Vdd-Vtnl)/x*((1+2*x)/sqrt(1+3*x)-1);
14 printf ('\nVih=%f V\n',Vih)
15 Volu=(Vdd-Vtnl+x*(Vih-Vtnd))/(1+2*x);
16 printf ('\noutput voltage corresponding to Vih=%f V
          \n',Volu)
17 NMl=Vil-Volu;
18 printf ('\nnoise margin=%f V\n',NMl)
19 NMh=Vohu-Vih;
20 printf ('\nnoise margin=%f V\n',NMh)

```

---

**Scilab code Exa 16.9** Determine the critical voltage on the voltage transfer curve

```

1 clear;
2 clc;
3 //Example 16.9
4 Vdd=5;
5 Vtn=1;
6 Vtp=-1;
7 //Kn=Kp hence Kn/Kp=x=1;
8 x=1;
9 Vit=(Vdd+Vtp+sqrt(x)*Vtn)/(1+sqrt(x));
10 printf ('\ninput voltage=%f V\n',Vit)
11 Vipt=Vit;
12 Vopt=Vipt-Vtp;
13 printf ('\noutput voltage at the transition point for
          PMOS =%fV\n',Vopt)
14 Vint=Vit;
15 Vont=Vint-Vtn;

```

```

16 printf ('\noutput voltage at the transition point for
    NMOS=% .2f V\n',Vont)
17 Vdd=10;
18 Vit=(Vdd+Vtp+sqrt(x)*Vtn)/(1+sqrt(x));
19 printf ('\ninput voltage =% .2fV\n',Vit)
20 Vipt=Vit;
21 Vint=Vit;
22 Vopt=Vipt-Vtp;
23 printf ('\noutput voltage at the transition point for
    PMOS =% .2fV\n',Vopt)
24 Vont=Vint-Vtn;
25 printf ('\noutput voltage at the transition point for
    NMOS =% .2fV\n',Vont)

```

---

**Scilab code Exa 16.10** Calculate the power dissipation in CMOS inverter

```

1 clear;
2 clc;
3 //Example 16.10
4 C1=2*10^-6;
5 Vdd=5;
6 f=100000;
7 P=f*C1*Vdd^2;
8 printf ('\npower dissipation in the CMOS inverter=% .3
    f microW\n',P)

```

---

**Scilab code Exa 16.11** Determine the noise margins of a CMOS inverter

```

1 clear;
2 clc;
3 //Example 16.11
4 Vtn=1;
5 Vtp=-1;

```

```

6 Vdd=5;
7 Vth=1;
8 Vil=Vtn+3*(Vdd+Vtp-Vth)/8;
9 printf ('\ninput voltage at the transition points Vil
    =%.3f V\n',Vil)
10 Vih=Vtn+5*(Vdd+Vtp-Vtn)/8;
11 printf ('\ninput voltage at the transition points Vih
    =%.3fV\n',Vih)
12 Vohu=1*(2*Vil+Vdd-Vtn-Vtp)/2;
13 printf ('\noutput voltage =%.3f V\n',Vohu)
14 Volu=1*(2*Vih-Vdd-Vtn-Vtp)/2;
15 printf ('\noutput voltage =%.2f V\n',Volu)
16 NML=Vil-Volu;
17 printf ('\nnoise margin =%.3f V\n',NML)
18 NMH=Vohu-Vih;
19 printf ('\nnoise margin=% .3f V\n',NML)

```

---

**Scilab code Exa 16.15** Determine the currents voltages and power dissipation in two

```

1 clear;
2 clc;
3 //Example 16.15
4 Vdd=3;
5 Kn=60;
6 Vtnd=0.5;
7 //W/L=x
8 xd=2;
9 Vtnl=-1;
10 xl=0.5;
11 R=2; //(MOhm)
12 Vgsl=0;
13 //solution with Depletion load
14 iD=Kn*xl*(Vgsl-Vtnl)^2/2;
15 printf ('\nfrain currents in M1 and M3 =%.fmicroA\n',
        iD)

```

```

16 P=iD*Vdd;
17 printf ('\n power dissipation in the circuit =%.f
           microW\n',P)
18 // iD=Kn/2*x*(2*Vgsd-Vtnd)Vdsd-Vdsd^2
19 Q=poly(0,'Q');
20 p=poly([0.25 -5 1],'Q','c');
21 roots(p)
22 disp("Q=50.5 (mV)")
23 // solution with Resistor load
24 // (Vdd-Q)/R=Kn/2*xd*(2*Vgsd-Vtnd)Q-Q^2
25 Q=poly(0,'Q');
26 p=poly([3 -599 120],'Q','c');
27 roots(p)
28 Q=0.005;
29 disp("Q=5 (mV)")
30 iD=(Vdd-Q)/R;
31 printf ('\n drain current =%.2f microA\n',iD)
32 P=iD*Vdd;
33 printf ('\n power dissipation in the circuit =%.2f
           microW\n',P)

```

---

# Chapter 17

## Bipolar Digital Circuits

Scilab code Exa 17.1 Calculate the currents and voltages in the basic differential

```
1 clear;
2 clc;
3 //Example 17.1
4 V1=5;
5 V2=-5;
6 Rc1=1;
7 Rc2=Rc1;
8 Rc=Rc1;
9 Re=2.150;
10 v2=0;
11 //for v1=0
12 vE=-0.7;
13 iE=(vE-V2)/Re;
14 printf ('\nemitter current=%.3f mA\n',iE)
15 iC=1;
16 Vcc=5;
17 vo1=Vcc-iC*Rc;
18 printf ('\nvo1=vo2=%f V\n',vo1)
19 //for v2=-1
20 vE=-0.7;
21 iE=2;
```

```

22 iC2=2;
23 vo1=5;
24 vo2=Vcc-iC2*Rc;
25 printf ('\nvo2=%.2f V\n',vo2)
26 v1=1;
27 Vbe=0.7;
28 vE=v1-Vbe;
29 iE=(vE-V2)/Re;
30 printf ('\nemitter current =%.3f mA\n',iE)
31 iC1=iE;
32 vo1=Vcc-iC1*Rc;
33 printf ('\nvo1=% .2f V\n',vo1)
34 vo2=Vcc

```

---

**Scilab code Exa 17.2** Calculate the currents resistors and logic 0 values in the base

```

1 clear;
2 clc;
3 //Example 17.2
4 Vx=-0.7;
5 Vy=Vx;
6 Vbe=0.7;
7 V2=-5.2;
8 Re=1.180;
9 vE=Vx-Vbe;
10 printf ('\nemitter voltage =%.2f V\n',vE)
11 iE=(vE-V2)/Re;
12 printf ('\nemitter current=% .2f mA\n',iE)
13 Icxy=iE;
14 vo1=-0.7;
15 Rc1=-vo1/Icxy;
16 printf ('\nRc1=% .2f KOhm\n',Rc1)
17 Vnor=vo1-Vbe;
18 printf ('\nNOR output logic 0 value=% .2f V\n',Vnor)
19 Vr=(vo1+Vnor)/2;

```

```

20 vE=Vr-Vbe;
21 printf( '\nVE=%f V\n', vE)
22 iE=(vE-V2)/Re;
23 printf( '\niE=%f mA\n', iE)
24 vo2=-0.7;
25 iC2=iE;
26 Rc2=-vo2/iC2;
27 printf( '\nRc2=%f KOhm\n', Rc2)
28 Vor=vo2-Vbe;
29 printf( '\nOR logic 0 value is=%f V\n', Vor)

```

---

**Scilab code Exa 17.3 Design the reference position of the ECL circuit**

```

1 clear;
2 clc;
3 //Example 17.3
4 Vr=-1.05;
5 Vbe=0.7;
6 Vb5=Vr+Vbe;
7 printf( '\nVb5 =%fV\n', Vb5)
8 R1=0.250;
9 i1=-Vb5/R1;
10 printf( '\ni1=%f mA\n', i1)
11 Vy=0.7;
12 V2=-5.2;
13 // let R1+R2=x
14 x=(-2*Vy-V2)/i1;
15 R2=x-R1;
16 printf( '\nR2=%f KOhm\n', R2)
17 iS=i1;
18 Rs=(Vr-V2)/iS;
19 printf( '\nRs=%f KOhm\n', Rs)

```

---

**Scilab code Exa 17.4** Calculate the power dissipated in the ECL logic circuit

```
1 clear;
2 clc;
3 //Example 17.4
4 Vx=-0.7;
5 Vy=-0.7;
6 iCxy=3.22; // (mA)
7 iCR=0;
8 i5=1.40;
9 i1=1.40;
10 Vor=-0.7;
11 R4=1.500;
12 Vnor=-1.4;
13 V2=-5.2;
14 R3=1.500;
15 i3=(Vor-V2)/R3;
16 printf ('\n current i3=%f mA\n',i3)
17 i4=(Vnor-V2)/R4;
18 printf ('\n current i4 =%fmA\n',i4)
19 P=(iCxy+iCR+i5+i1+i3+i4)*(0-V2);
20 printf ('\n power dissipation=%f mW\n',P)
```

---

**Scilab code Exa 17.5** Calculate minimum fanout of ECL logic gate

```
1 clear;
2 clc;
3 //Example 17.5
4 b=50;
5 V2=-5.2;
6 Vbe=0.7;
7 Rc2=0.240;
8 Vor=-0.75;
9 Re=1.180;
10 iE=(Vor-Vbe-V2)/Re;
```

```

11 printf ('\nemitter current=%f mA\n', iE)
12 iB=iE/(1+b);
13 iB=iB*1000; //micro A
14 printf ('\ninput base current=%f microA\n', iB)
15 R3=1.500;
16 i3=(Vor-V2)/R3;
17 printf ('\ni3=%f mA\n', i3)
18 iB=iB*0.001; //mA
19 N=(-(Vor+Vbe)*(1+b)/(Rc2)-i3)/iB;
20 printf ('\nN=%f\n', N)

```

---

**Scilab code Exa 17.7 Analyze the modified ECL logic gate**

```

1 clear;
2 clc;
3 //Example 17.7
4 Vcc=1.7;
5 Re=0.008; //mohm
6 Rc=0.008; //mohm
7 Vy=0.4;
8 Vbe=0.7;
9 Vor=Vcc //logic 1
10 Vor=Vcc-Vy //logic 0
11 Vr=1.5;
12 iE=(Vr-Vbe)/Re;
13 printf ('\nemitter current=%f microA\n', iE)
14 iR=Vy/Rc;
15 printf ('\nmaximum current in Rc =%f microA\n', iR)
16 iD=iE-iR;
17 printf ('\ncurrent through the diode=%f microA\n',
18 iD)
19 P=iE*Vcc;
20 printf ('\npower dissipation=%f microW\n', P)
21 Vv=1.7;
22 iE=(Vv-Vbe)/Re;

```

```

22 printf( '\niE =%.2f microA\n' , iE)
23 P=iE*Vcc;
24 printf( '\npower dissipation =%.2f microW\n' , P)

```

---

**Scilab code Exa 17.9** Calculate the currents and voltages for the basic TTL NAND ci

```

1 clear;
2 clc;
3 //Example 17.9
4 bf=25;
5 b=bf;
6 br=0.1;
7 Vcc=5;
8 R1=4;
9 Vbc=0.7;
10 Vy=0.1;
11 Vx=0.1;
12 R2=1.6;
13 Vbe=0.8;
14 Rc=4;
15 Vce=0.1;
16 vB2=Vx+Vce;
17 printf( '\nvB2=% .2 f V\n' , vB2)
18 vB1=Vx+Vbe;
19 printf( '\nbase voltage=% .2 f V\n' , vB1)
20 i1=(Vcc-vB1)/R1;
21 printf( '\ncurrent i1=% .2 f mA\n' , i1)
22 vB1=Vbe+Vbe+Vbc;
23 printf( '\nvB1=% .2 f V\n' , vB1)
24 vC2=Vbe+Vce;
25 printf( '\ncollector voltage=% .2 f V\n' , vC2)
26 i1=(Vcc-vB1)/R1;
27 printf( '\ncurrent i1 =% .2 fmA\n' , i1)
28 iB2=(1+2*br)*i1;
29 printf( '\niB2=% .2 f mA\n' , iB2)

```

```

30 i2=(Vcc-vC2)/R2;
31 printf ('\ni2 =%.2fmA\n',i2)
32 iE2=i2+iB2;
33 printf ('\niE2=%.2f mA\n',iE2)
34 Rb=1;
35 i4=Vbe/Rb;
36 printf ('\ncurrent in the pull down resistor=%.2f mA\
n',i4)
37 iBo=iE2-i4;
38 printf ('\nbias drive to the output transistor=%.2f
mA\n',iBo)
39 i1=(Vcc-Vce)/Rc;
40 printf ('\ni1=%.2f mA\n',i1)

```

---

**Scilab code Exa 17.11** Determine the currents in a Schottky transistor

```

1 clear;
2 clc;
3 //Example 17.11
4 b=25;
5 iB=1;
6 iC=2;
7 ic=(iB+iC)/(1+1/b);
8 printf ('\nnormal collector current=%.3f mA\n',ic)
9 ib=ic/b;
10 printf ('\nnormal base current =%.3fmA\n',ib)
11 iD=iB-ib;
12 printf ('\nSchottky diode current=%.3f mA\n',iD)
13 iC=20;
14 ic=(iB+iC)/(1+1/b);
15 printf ('\nnormal collector current=%.3f mA\n',ic)
16 ib=ic/b;
17 printf ('\nnormal base current =%.3fmA\n',ib)
18 iD=iB-ib;
19 printf ('\nSchottky diode current=%.3f mA\n',iD)

```

---

**Scilab code Exa 17.12** Calculate the power dissipation in a low power Schottky TTL

```
1 clear;
2 clc;
3 //Example 17.12
4 Vy=0.3;
5 Vbe=0.7;
6 vx=0.4;
7 R2=8;
8 Vce=0.4;
9 Vcc=5;
10 b=25;
11 Vce=0.4;
12 Vbe1=0.7;
13 Vbe2=0.7;
14 Vcc=5;
15 R1=20;
16 v1=Vce+Vy;
17 i1=(Vcc-v1)/R1;
18 printf ('\ni1=%f mA\n',i1)
19 P1=i1*(Vcc-vx);
20 printf ('\npower dissipation=%f mW\n',P1)
21 v1=Vbe1+Vbe2;
22 printf ('\nv1=%f V\n',v1)
23 vC2=Vbe1+Vce;
24 printf ('\nvoltage vC2 =%fV\n',vC2)
25 i1=(Vcc-v1)/R1;
26 printf ('\ncurrent i1 =%.3fmA\n',i1)
27 i2=(Vcc-vC2)/R2;
28 printf ('\ncurrent i2 =%.3fmA\n',i2)
29 P=(i1+i2)*Vcc;
30 printf ('\npower dissipation for high input condition
=%.3f mW\n',P)
```

---