

Scilab Textbook Companion for  
Electrical Measurements And Measuring  
Instruments  
by N. V. Suryanarayana<sup>1</sup>

Created by  
Abishek Nimal  
Measurement  
Instrumentation Engineering  
Thapar University patiala  
College Teacher  
Dr. Sunil Kumar Singla  
Cross-Checked by  
Ganesh R

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Electrical Measurements And Measuring Instruments

**Author:** N. V. Suryanarayana

**Publisher:** S. Chand And Co. Ltd., New Delhi

**Edition:** 1

**Year:** 2001

**ISBN:** 81-219-2011-6

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 Standards units and dimensions</b>	<b>5</b>
<b>2 Calculation of capacitance and inductance</b>	<b>9</b>
<b>3 Principles of electrical measurements and measuring instruments</b>	<b>11</b>
<b>4 Measurement of resistance</b>	<b>16</b>
<b>5 Potentiometer</b>	<b>20</b>
<b>6 Location of the faults</b>	<b>23</b>
<b>7 Measurement of Capacitance and Inductance</b>	<b>26</b>
<b>8 Measurement of power</b>	<b>31</b>
<b>9 Instrument Transformers</b>	<b>33</b>
<b>10 Magnetic Measurements</b>	<b>37</b>
<b>12 Basic Transducers</b>	<b>39</b>

14 Cathode Ray Oscilloscope	42
16 Polyphase systems	44

# List of Scilab Codes

Exa 1.17	Find the various parameters of measurement	5
Exa 1.18	Find the precision of the 8th reading . . . . .	5
Exa 1.19	Find the value and limiting error of Resistance	6
Exa 1.20	Find the resistance and uncertainty in resistance . . . . .	6
Exa 1.21	Find the least square line . . . . .	7
Exa 1.22	Using the chi square test estimate the probability that the coin is unweighted . . . . .	7
Exa 1.23	Find the assigned value and uncertainty associated with measurement . . . . .	8
Exa 2.1	Calculate the self inductance of the coil . . . .	9
Exa 2.2	Calculate stored charge and potential gradient	9
Exa 2.3	Calculate the capacitance of the cable . . . .	10
Exa 3.1	Calculate deflection for spring controlled and gravity control instruments . . . . .	11
Exa 3.2	Calculate the shunt resistance . . . . .	11
Exa 3.3	Calculate the value of total resistance . . . . .	12
Exa 3.4	Calculate the current . . . . .	12
Exa 3.5	Calculate the expected error and per cent error	13
Exa 3.6	Calculate the resistance and maximum possible error . . . . .	13
Exa 3.7	Calculate the resistance and maximum possible error . . . . .	14
Exa 3.8	Calculate current in the voltage coil . . . . .	14
Exa 3.9	Calculate the correction required . . . . .	14
Exa 3.10	Calculate the meter constant and power factor	15
Exa 3.11	Calculate the percentage error at full load . .	15
Exa 4.1	Calculate the Insulation resistance . . . . .	16

Exa 4.2	Calculate the Insulation resistance . . . . .	16
Exa 4.3	Calculate the Insulation resistance . . . . .	17
Exa 4.4	Calculate the value of X . . . . .	17
Exa 4.5	Calculate Resistance of the field coil . . . . .	17
Exa 4.6	Calculate Unknown resistance . . . . .	18
Exa 4.7	Calculate Resistance between positive earth and negative earth . . . . .	18
Exa 4.8	Calculate Unknown resistance X . . . . .	19
Exa 5.1	Calculate Distance PX . . . . .	20
Exa 5.2	Calculate Voltage of dry cell . . . . .	20
Exa 5.3	Calculate Length of PQ . . . . .	21
Exa 5.4	Calculate Length of wire and Ratio of resistances . . . . .	21
Exa 5.5	Calculate emf of the cell and Percentage error of the voltmeter . . . . .	21
Exa 6.1	Find the position of fault . . . . .	23
Exa 6.2	Find the position of fault . . . . .	23
Exa 6.3	Find the resistance of the armature and percentage error . . . . .	24
Exa 6.4	Find the position of fault . . . . .	24
Exa 6.5	Calculate the distance to the fault . . . . .	24
Exa 7.1	Calculate the resistance and inductance of the coil . . . . .	26
Exa 7.2	Calculate the parameters of the cable . . . . .	27
Exa 7.3	Calculate the power factor and equivalent series resistance . . . . .	27
Exa 7.4	Calculate the capacitance and resistance . . . . .	28
Exa 7.5	Calculate the inductance and resistance of the impedance . . . . .	28
Exa 7.6	Calculate the inductance and resistance . . . . .	28
Exa 7.7	Calculate the inductance and resistance of the impedance . . . . .	29
Exa 7.8	Calculate the capacitance and loss resistance of the capacitor . . . . .	29
Exa 7.9	Calculate the resistance and inductance of the coil . . . . .	30
Exa 8.1	Calculate the parameters of the load . . . . .	31

Exa 8.2	Calculate the parameters of the load and circuit . . . . .	31
Exa 9.1	Calculate ratio error and phase angle . . . . .	33
Exa 9.2	Calculate secondary voltage and current . . . . .	33
Exa 9.3	Calculate secondary voltage and current in line . . . . .	34
Exa 9.4	Calculate the ratio error . . . . .	34
Exa 9.5	Calculate phase angle error at no load . . . . .	35
Exa 9.6	Calculate the ratio error . . . . .	35
Exa 10.1	Calculate relative permeability . . . . .	37
Exa 10.2	Calculate galvanometer constant . . . . .	37
Exa 12.1	Calculate change in resistance . . . . .	39
Exa 12.2	Calculate change in length . . . . .	39
Exa 12.3	Calculate capacitance . . . . .	40
Exa 12.4	Calculate the displacement . . . . .	40
Exa 12.5	Calculate the acceleration in g and natural frequency . . . . .	40
Exa 14.1	Calculate the rms value of current . . . . .	42
Exa 14.2	Calculate the frequency of the voltage applied . . . . .	42
Exa 14.3	Calculate the time constant capacitance and maximum frequency . . . . .	43
Exa 16.1	Calculate Line and phase current . . . . .	44
Exa 16.2	Calculate line current and total power . . . . .	44
Exa 16.3	Calculate the resistance and inductive reactance of the load . . . . .	45
Exa 16.4	Calculate phase voltage and total power . . . . .	45
Exa 16.5	Calculate current in each generator and motor phase . . . . .	46
Exa 16.6	Calculate the circuit parameters . . . . .	46
Exa 16.7	Calculate the reduction in power . . . . .	47
Exa 16.8	Calculate the circuit parameters . . . . .	47
Exa 16.9	Calculate the circuit parameters . . . . .	48
Exa 16.10	Calculate the current in each line and value of each resistance . . . . .	48
Exa 16.11	Calculate circuit constants of load per phase . . . . .	49
Exa 16.12	Calculate the readings of watt meters . . . . .	49
Exa 16.13	Calculate the value of power and power factor . . . . .	50
Exa 16.14	Calculate the readings of watt meters . . . . .	50

# Chapter 1

## Standards units and dimensions

Scilab code Exa 1.17 Find the various parameters of measurement

```
1 // 1.17
2 clc;
3 Y=90;
4 X=89;
5 Error_absolute=Y-X;
6 disp(Error_absolute, 'absolute Error')
7 Error_relative=(Y-X)*100/Y;
8 disp(Error_relative, 'relative Error ( percent )=')
9 Accuracy_relative=1>Error_relative;
10 disp(Accuracy_relative, 'Accuracy relative=')
11 Accuracy_percentage=100*Accuracy_relative;
12 disp(Accuracy_percentage, 'Accuracy( percentage )=')
```

---

Scilab code Exa 1.18 Find the precision of the 8th reading

```
1 // 1.18
2 clc;
3 S=98+100+102+98+100+100+104+104+105+97;
```

```
4 n=10;
5 Avg=S/n;
6 P=1-abs((104-Avg)/Avg);
7 printf(" Precision for the 8th reading=% .2f",P)
```

---

Scilab code Exa 1.19 Find the value and limiting error of Resistance

```
1 // 1.19
2 clc;
3 V=10;
4 I=20*10^-3;
5 RI=50;
6 R=(V/I)-RI;
7 printf("The value of Resistance=% .0f ohm",R)
8 dV=0.2;
9 dI=1*10^-3;
10 dRI=5;
11 dR=(dV/I)+(V*dI/I^2)+(dRI)
12 printf("\nLimiting error of resistance=% .0f ohm",dR)
```

---

Scilab code Exa 1.20 Find the resistance and uncertainty in resistance

```
1 // 1.20
2 clc;
3 R0=5;
4 a=0.004;
5 T=30;
6 R=R0*(1+a*(T-20));
7 printf("Resistance of the wire=% .1f ohm",R)
8 // Let (dR/dR0)=b ; (dR/da)=c ; (dR/dT)=d
9 b=(1+a*(T-20));
10 c=R0*(T-20);
11 d=R0*a;
```

```
12 ur0=5*0.003;
13 ua=0.004*0.01;
14 ut=1;
15 uR=(b^2*ur0^2+c^2*ua^2+d^2*ut^2)^0.5;
16 printf(" Uncertanity in resistance=% .2 f ohm" ,uR)
```

---

Scilab code Exa 1.21 Find the least square line

```
1 // 1.21
2 clc;
3 X_mean=(15+20+25+30+35+45)/6;
4 printf("The sample mean of the temperature=% .2 f
degree C" ,X_mean)
5 Y_mean
    =(1.9+1.93+1.97+2+2.01+2.01+1.94+1.95+1.97+2.02+2.02+2.04)
    /12*10^-6;
6 printf("\nThe sample mean of the failure=% .6 f
failures/hour" ,Y_mean)
7 disp('from these values we get')
8 a=1.80*10^-6;
9 b=0.00226;
10 disp('Y=1.80+0.00226x      is the required least
square line')
```

---

Scilab code Exa 1.22 Using the chi square test estimate the probability that the c

```
1 // 1.22
2 clc;
3 n=2;
4 k=1;
5 dof=n-k;
6 chi_square=(3-5)^2/5+(7-5)^2/5;
7 disp(chi_square , 'Chi square value=')
```

```
8 disp('From the dof and chi square value we find P  
=0.22')  
9 disp('Hence there are 22% chance that the  
distribution is just the result of random  
fluctuations and the coin may be unweighted')
```

---

**Scilab code Exa 1.23** Find the assigned value and uncertainty associated with measu

```
1 // 1.23  
2 clc;  
3 X_mean=501*1/5;  
4 printf("\nAssigned Value=%f V",X_mean)  
5 sigma={(1/(5-1))*((100.2-X_mean)^2+(100.3-X_mean)  
^2+(100.2-X_mean)^2+(100.2-X_mean)^2+(100.1-  
X_mean)^2)}^0.5;  
6 //disp('For 95% confidance level student factor t is  
2.78')  
7 t=2.78;  
8 n=5;  
9 Ur=t*sigma/(n^0.5);  
10 printf("\nUncertainty=%f V",Ur)
```

---

# Chapter 2

## Calculation of capacitance and inductance

Scilab code Exa 2.1 Calculate the self inductance of the coil

```
1 // 2.1
2 clc;
3 N=400;
4 a=4*10^-4;
5 MUo=4*pi*10^-7;
6 MUr=800;
7 l=0.3;
8 L=(MUo*MUr*a*N^2)/l;
9 printf("Self inductance of the coil=%f H",L)
```

---

Scilab code Exa 2.2 Calculate stored charge and potential gradient

```
1 // 2.2
2 clc;
3 P0=8.854*10^-12;
4 Pr1=5.5;
```

```

5 d1=10^-3;
6 b1=d1/Pr1;
7 Pr2=2.2;
8 d2=10^-3;
9 b2=d2/Pr2;
10 Pr3=1.5;
11 d3=10^-3;
12 b3=d3/Pr3;
13 A=100*10^-4;
14 C=P0*A/(b1+b2+b3);
15 V=5000;
16 Q=C*V*10^6;
17 printf("stored charge in the capacitor=%f coulombs
      ",Q)
18 D=Q/A;
19 D=146*10^-6;
20 g1=D*10^-3/(P0*Pr1);
21 printf("\n potential gradient g1=%f kV/m",g1)
22 g2=D*10^-3/(P0*Pr2);
23 printf("\n potential gradient g2=%f kV/m",g2)
24 g3=D*10^-3/(P0*Pr3);
25 printf("\n potential gradient g3=%f kV/m",g3)

```

---

**Scilab code Exa 2.3 Calculate the capacitance of the cable**

```

1 // 2.3
2 clc;
3 a=0.5/2;
4 b=0.25+0.4;
5 Pr=4.5;
6 C=(0.024*Pr)/(log10(b/a))
7 C_total=300*C
8 printf("\ncapacitance of the cable=%f uF",C_total)

```

---

# Chapter 3

## Principles of electrical measurements and measuring instruments

Scilab code Exa 3.1 Calculate deflection for spring controlled and gravity controlled

```
1 // 3.1
2 clc;
3 disp('For spring controlled Tc is proportional to
      theta')
4 theta=90*(3/5)^2;
5 printf("Deflection for spring controlled instrument=
      %.2f degree",theta)
6 disp('For gravity controlled Tc is proportional to
      sin(theta)')
7 theta=asin((3/5)^2);
8 printf("\nDeflection for gravity controlled
      instrument=% .2f degree",theta)
```

---

Scilab code Exa 3.2 Calculate the shunt resistance

```
1 // 3.2
2 clc;
3 I=1000;
4 Ia=50*10^-3;
5 Is=I-Ia;
6 Ra=10;
7 Va=Ia*Ra;
8 Rs=10*Va/Is;
9 printf("The shunt resistance=%f ohm",Rs)
```

---

### Scilab code Exa 3.3 Calculate the value of total resistance

```
1 // 3.3
2 clc;
3 Is=150*10^-6;
4 I=50*10^-6;
5 R=4*10^3;
6 Rt=R*I/Is;
7 printf("\nthe value of total resistance=%f ohm",Rt)
)
```

---

### Scilab code Exa 3.4 Calculate the current

```
1 // 3.4
2 clc;
3 V=1;
4 R=2*10^3;
5 I=(V/R)*1000;
6 printf("Actual current=%f mA",I)
7 Rm=1000;
8 Rt=R+Rm;
9 I=(V/Rt)*1000;
10 printf("\nCurrent when Rm is 1000 ohm =%f mA",I)
```

```
11 Rm=100;
12 Rt=R+Rm;
13 I=(V/Rt)*1000;
14 printf("\nCurrent when Rm is 100 ohm =%.2f mA",I)
```

---

**Scilab code Exa 3.5** Calculate the expected error and per cent error

```
1 // 3.5
2 clc;
3 I=20;
4 E_expected=2.5*I/100;
5 printf("Expected error=+/-%.2f mA",E_expected)
6 disp('Actual reading for 5mA indication will be 4.5
     mA to 5.5mA')
7 disp('Actual reading for 15mA indication will be
     14.5mA to 15.5mA')
8 E_5mA=(0.5/5)*100;
9 printf("Error for 5mA reading=% .2f percent",E_5mA)
10 E_15mA=(0.5/15)*100;
11 printf("\nError for 15mA reading=% .2f percent",
     E_15mA)
```

---

**Scilab code Exa 3.6** Calculate the resistance and maximum possible error

```
1 // 3.6
2 clc;
3 V=20;
4 A=20*10^-6;
5 Ra=25*10^3;
6 Rx=((V/A)-Ra)*10^-3;
7 printf("The resistance=% .0f Kohm",Rx)
8 E_voltmeter=(2/(100*20))*20*100;
9 E_current=(2/(100*20))*50*100;
```

```
10 E_total=E_voltmeter+E_current;
11 printf("\nMaximum possible error=%f percent",
E_total)
```

---

**Scilab code Exa 3.7** Calculate the resistance and maximum possible error

```
1 //3.7
2 clc;
3 V=20;
4 A=20*10^-3;
5 Rv=10*10^3*20;
6 Rx=(V/(A-(V/Rv)))/1000;
7 printf("The resistance=%f Kohm",Rx)
8 E_total=2.5+2.5;
9 printf("Maximum possible error=%f percent",E_total
)
```

---

**Scilab code Exa 3.8** Calculate current in the voltage coil

```
1 //3.8
2 clc;
3 Sp_constant=10.5*10^-6*pi/180;
4 deflection=83;
5 Td=Sp_constant*deflection;
6 I1=10;
7 K=0.078;
8 I2=(Td/(K*I1))*10^6;
9 printf("Current in the voltage coil=%f uA",I2)
```

---

**Scilab code Exa 3.9** Calculate the correction required

```
1 // 3.9
2 clc;
3 AH=5*1/2;
4 printf("AH passed in 30 minuties=%f percent",AH)
5 V_assumed=0.51*1000/AH;
6 V_actual=200;
7 Error=V_actual-V_assumed;
8 Correction=-Error;
9 Cor=Correction*100/V_actual;
10 printf("\nCorrection required=%f percent",Cor)
```

---

**Scilab code Exa 3.10** Calculate the meter constant and power factor

```
1 // 3.10
2 clc;
3 E_unity_pf=230*6*4*1/1000;
4 M_constant=2208/E_unity_pf;
5 printf("Meter constant=%f rev/kWh",M_constant)
6 E_consumed=1472/M_constant;
7 pf=(E_consumed/(230*5*4))*1000;
8 printf("\npower factor=%f",pf)
```

---

**Scilab code Exa 3.11** Calculate the percentage error at full load

```
1 // 3.11
2 clc;
3 phi=acosd(0.8);
4 alpha_actual=85-phi;
5 alpha_true=90-phi;
6 er=(alpha_true-alpha_actual)/(alpha_true)*100;
7 printf("percentage error at full load=%f",er)
```

---

# Chapter 4

## Measurement of resistance

Scilab code Exa 4.1 Calculate the Insulation resistance

```
1 // 4.1
2 clc;
3 t=20;
4 C=8*10^-10;
5 E=200;
6 e=150;
7 a=log10(E/e)
8 R=(0.4343*t)/(C*a)*10^-6;
9 printf("Insulation resistance=%f mega-ohm",R)
```

---

Scilab code Exa 4.2 Calculate the Insulation resistance

```
1 // 4.2
2 clc;
3 t=600;
4 C=2.5*10^-12;
5 E=500;
6 e=300;
```

```
7 a=log10(E/e)
8 R=(0.4343*t)/(C*a);
9 printf("Insulation resistance=%f mega-ohm",R)
```

---

#### Scilab code Exa 4.3 Calculate the Insulation resistance

```
1 // 4.3
2 clc;
3 //V=Eexp(-t/tc) where tc= RC=Time constant
4 t=30;
5 V=125;
6 E=200;
7 tc=-30/log(V/E);
8 R=(7/15)*tc-7;
9 printf("Insulation resistance=%f mega-ohm",R)
```

---

#### Scilab code Exa 4.4 Calculate the value of X

```
1 // 4.4
2 clc;
3 Q=3000;
4 S=0.1;
5 M=2000;
6 X=Q*S/M;
7 printf("The value of X=%f ohm",X)
```

---

#### Scilab code Exa 4.5 Calculate Resistance of the field coil

```
1 // 4.5
2 clc;
```

```
3 lx=55;
4 ly=100-lx;
5 Y=100;
6 X=Y*(lx/ly);
7 printf("Resistance of the field coil=%f ohm",X)
```

---

#### Scilab code Exa 4.6 Calculate Unknown resistance

```
1 // 4.6
2 clc;
3 p=200.7;
4 q=400;
5 S=200.05*10^-6;
6 P=200.5;
7 Q=400;
8 r=1400*10^-6;
9 X=((P*S/Q)+((q*r)/(p+q)))*((P/Q)-(p/q))*10^6;
10 printf("Unknown resistance=%f micro-ohm",X)
```

---

#### Scilab code Exa 4.7 Calculate Resistance between positive earth and negative earth

```
1 // 4.7
2 clc;
3 E=230;
4 V1=60;
5 V2=40;
6 Rv=50000;
7 R1=((E-(V1+V2))/V2)*Rv*10^-3;
8 printf("Resistance between positive and earth=%f Kohm",R1)
9 R2=((E-(V1+V2))/V1)*Rv*10^-3;
10 printf("\nResistance between -ve and earth=%f Kohm",R2)
```

---

### Scilab code Exa 4.8 Calculate Unknown resistance X

```
1 // 4.8
2 clc;
3 Q=100.5;
4 M=300;
5 q=100.6;
6 m=300.25;
7 r=0.1;
8 S=0.0045;
9 X=((M*S/Q)+((r)/(r+m*q))*((M*q/Q)-(m)))*10^6;
10 printf("Unknown resistance=%f micro-ohm",X)
```

---

# Chapter 5

## Potentiometer

Scilab code Exa 5.1 Calculate Distance PX

```
1 // 5.1
2 clc;
3 Ipq=4/(3+4) ;
4 Vpq=Ipq*3;
5 Vpq_per_cm=Vpq/100;
6 Dpx=1.0186/Vpq_per_cm;
7 printf("Distance PX=%f cm",Dpx)
```

---

Scilab code Exa 5.2 Calculate Voltage of dry cell

```
1 // 5.2
2 clc;
3 V_per_cm=1.0186/60;
4 //When S is replaced by a dry cell we get PK=85 cm
   for null deflection
5 Dpk=85;
6 V_dry_cell=Dpk*V_per_cm;
7 printf("Voltage of dry cell=%f V",V_dry_cell)
```

---

### Scilab code Exa 5.3 Calculate Length of PQ

```
1 // 5.3
2 clc;
3 Vpq=(1.02*5/2500)*1000;
4 Lpq=1.2*100/Vpq;
5 printf("Length of PQ=%f m",Lpq)
```

---

### Scilab code Exa 5.4 Calculate Length of wire and Ratio of resistances

```
1 // 5.4
2 clc;
3 l2=(10/3)*(1.5/1.5)*(9/15)^2;
4 printf("Length of wire=%f m",l2)
5 a1=0.0004;
6 a2=0.0003;
7 R2=1;
8 R1=1.5*R2;
9 T=100;
10 Rp=R1*(1+a1*T);
11 Rq=R2*(1+a2*T);
12 R=Rp/Rq;
13 printf("Ratio of resistances=%f",R)
```

---

### Scilab code Exa 5.5 Calculate emf of the cell and Percentage error of the voltmeter

```
1 // 5.5
2 clc;
3 emf_std_cell=1.0183;
```

```
4 emf_cell=70/50*emf_std_cell;
5 printf("e.m. f. of the cell=%.2f V",emf_cell)
6 V_read=1.35;
7 V_cal=1.32379;
8 error_voltmeter_percent=((V_read-V_cal)/V_cal)*100;
9 printf("\nPercentage error of the voltmeter=% .2f",
       error_voltmeter_percent)
```

---

# Chapter 6

## Location of the faults

**Scilab code Exa 6.1** Find the position of fault

```
1 // 6.1
2 clc;
3 r=250;
4 s=1000;
5 l=1000;
6 x=r*l/s;
7 printf("Position of the fault=%0.1fm" ,x)
```

---

**Scilab code Exa 6.2** Find the position of fault

```
1 // 6.2
2 clc;
3 r=600;
4 s=1000;
5 El=500*30/50;
6 l=450+El;
7 x=r*l/s;
8 printf("Position of the fault=%0.1f m" ,x)
```

---

**Scilab code Exa 6.3** Find the resistance of the armature and percentage error

```
1 // 6.3
2 clc;
3 R_armature=0.256/16;
4 printf("Armature Resistance=%f ohm",R_armature)
5 R_armature_true=0.256/(16-(0.256/10));
6 Error=R_armature-R_armature_true;
7 Error_percentage=Error*100/R_armature_true;
8 printf("\nPercentage Error=%f",Error_percentage)
```

---

**Scilab code Exa 6.4** Find the position of fault

```
1 // 6.4
2 clc;
3 R1=45;
4 R2=100-R1;
5 l=500;
6 x=2*l*R1/(R1+R2);
7 printf("Position of the fault from the test end=%f
m",x)
```

---

**Scilab code Exa 6.5** Calculate the distance to the fault

```
1 clc;
2 // 5.6
3 r3=300;
4 r2=1500;
5 r1=15;
```

```
6 R=(r3/r2)*r1;
7 l=4000;
8 r3=180;
9 d=(2*l/R)*(R*r2-r3*r1)/(r1+r2);
10 printf("Distance of the fault=% .2fm" ,d)
```

---

# Chapter 7

## Measurement of Capacitance and Inductance

Scilab code Exa 7.1 Calculate the resistance and inductance of the coil

```
1 // 7.1
2 clc;
3 //The coil has resistance of R ohm and inductance L2
4 //ZKL=25+j (2*pi*f)*0.05;
5 ZLM=100;
6 //ZKN=(R+2)+j (2*pi*f)*L2;
7 ZNM=100;
8 //Now (ZKL/ZLM)=(ZKN/ZNM)
9 //((25+j (2*pi*f)*0.05)/100)=((R+2)+j (2*pi*f)*L2
10 //Equating Real and imaginary parts
11 //we have 25=R+2
12 //2*pi*f)*0.05=2*pi*f)*L2
13 R=23;
14 L2=50;
15 printf("Resistance=%f ohm",R)
16 printf("\nInductance=%f mH",L2)
```

---

**Scilab code Exa 7.2 Calculate the parameters of the cable**

```
1 // 7.2
2 clc;
3 C1=50*10^-12;
4 r2=1500/%pi;
5 r3=120;
6 Cs=C1*r2/r3*10^12;
7 printf("Cable capacitance=%f pF",Cs)
8 C2=0.95*10^-6;
9 rs=C2*r3/(C1*10^6);
10 printf("\nParallel loss resistance=%f Mega-ohm",rs
    )
11 w=314;
12 Loss_angle=atand(rs*w*Cs);
13 printf("\nLoss angle=%f degree",Loss_angle)
```

---

**Scilab code Exa 7.3 Calculate the power factor and equivalent series resistance**

```
1 // 7.3
2 clc;
3 C3=106*10^-12;
4 C1=0.35*10^-6;
5 R1=318;
6 R2=130;
7 C2=C3*R1/R2;
8 Rx=R2*C1/C3;
9 printf("Series Resistance=%f ohm",Rx)
10 wr=314;
11 pf=wr*Rx*C2;
12 printf("\nPower factor=%f",pf)
```

---

**Scilab code Exa 7.4 Calculate the capacitance and resistance**

```
1 // 7.4
2 clc;
3 Q=10;
4 Cs=0.2;
5 P=2;
6 Cx=Q*Cs/P;
7 printf("Capacitance=%f uF",Cx)
8 S=5;
9 rx=P*S/Q;
10 printf("\nResistance=%f Kohm",rx)
```

---

**Scilab code Exa 7.5 Calculate the inductance and resistance of the impedance**

```
1 // 7.5
2 clc;
3 S=900;
4 P=1.5*10^3;
5 Q=2*10^3;
6 Cs=0.2*10^-6;
7 rx=S*P/Q;
8 printf("Resistance=%f ohm",rx)
9 Lx=P*Cs*S;
10 printf("\nInductance=%f H",Lx)
```

---

**Scilab code Exa 7.6 Calculate the inductance and resistance**

```
1 // 7.6
```

```
2 clc;
3 R1=2;
4 R2=1;
5 R4=500;
6 L4=0.1
7 R3=R1*R4/R2;
8 printf(" Resistance=%f ohm" ,R3)
9 L3=R1*L4/R2;
10 printf("\n Inductance=%f H" ,L3)
```

---

**Scilab code Exa 7.7** Calculate the inductance and resistance of the impedance

```
1 // 7.7
2 clc;
3 S=0.875;
4 P=1.35*10^3;
5 Q=1*10^3;
6 Cs=0.1*10^-6;
7 rx=S*P/Q;
8 printf(" Resistance=%f ohm" ,rx)
9 Lx=P*Cs*S*10^3;
10 printf("\n Inductance=%f mH" ,Lx)
```

---

**Scilab code Exa 7.8** Calculate the capacitance and loss resistance of the capacitor

```
1 // 7.8
2 clc;
3 r1=250;
4 r4=1200;
5 r2=10^6;
6 C4=4*10^-5;
7 r3=r1*r4/r2;
8 printf(" Resistance=%f ohm" ,r3)
```

```
9 C3=r2*C4/r1;
10 printf("\nCapacitance=%f uF", C3)
```

---

Scilab code Exa 7.9 Calculate the resistance and inductance of the coil

```
1 // 7.9
2 clc;
3 R2=1000;
4 R4=833;
5 f=50;
6 w=2*pi*f;
7 C=0.38*10^-6;
8 R3=16800;
9 R1=(R2*R3*R4*w^2*C^2)/(1+w^2*R4^2*C^2);
10 printf("Resistance=%f ohm", R1)
11 L=R2*R3*C/(1+w^2*R4^2*C^2);
12 printf("Inductance=%f H", L)
```

---

# Chapter 8

## Measurement of power

**Scilab code Exa 8.1** Calculate the parameters of the load

```
1 // 8.1
2 clc;
3 ZL=220/2;
4 printf("Load impedance=%f ohm",ZL)
5 Z_total=220/4;
6 printf("\nImpedance of the combination=%f ohm",
      Z_total)
7 I1=2;
8 I2=2.5;
9 I3=4;
10 P=(Z_total/2)*(I3^2-I1^2-I2^2);
11 printf("\nPower absorbed by load=%f W",P)
12 pf=P/(220*2^2);
13 printf("\nPower factor of load=%f",pf)
```

---

**Scilab code Exa 8.2** Calculate the parameters of the load and circuit

```
1 // 8.2
```

```
2 clc;
3 I=125/10;
4 ZL=50/I;
5 printf("Load impedance=%f ohm",ZL)
6 Z_total=150/I;
7 printf("\nImpedance of the combination=%f ohm",
       Z_total)
8 I1=125;
9 I2=50;
10 I3=150;
11 P=(1/(2*10))*(I3^2-I1^2-I2^2);
12 printf("\nPower absorbed by load=%f W",P)
13 Pr=I^2*10;
14 printf("\nPower consumed by the resistor=%f W",Pr)
15 pf=P/(50*I);
16 printf("\nPower factor of load=%f",pf)
```

---

# Chapter 9

## Instrument Transformers

Scilab code Exa 9.1 Calculate ratio error and phase angle

```
1 // 9.1
2 clc;
3 n=300/1;
4 Z2=complex(1.5,1);
5 a=polar(Z2);
6 I2=5;
7 E2=I2*a;
8 E1=E2/n;
9 alpha=atand(1/1.5)
10 Io=complex(100,40)
11 delta=atand(40/100);
12 b=polar(Io)
13 sigma=-(b*sind(alpha+delta))*100/(n*I2);
14 printf("Ratio error=% .2f percent",sigma)
15 bet=(b*cosd(alpha+delta))/(n*I2);
16 printf("\nPhase angle=% .2f degree",bet)
```

---

Scilab code Exa 9.2 Calculate secondary voltage and current

```
1 // 9.2
2 clc;
3 I_ratio=500/5;
4 n=1/100;
5 I2=300/100;
6 printf("Secondary current=%f A",I2)
7 V2=I2*1.5;
8 printf("\nSecondary voltage=%f V",V2)
```

---

Scilab code Exa 9.3 Calculate secondary voltage and current in line

```
1 // 9.3
2 clc;
3 V_line=200*33000/220;
4 printf("Voltage on line=%f V",V_line)
5 I_line=4*100/5;
6 printf("Current in line=%f A",I_line)
```

---

Scilab code Exa 9.4 Calculate the ratio error

```
1 // 9.4
2 clc;
3 n=1000/5;
4 Ie=0.7*1000/100;
5 Tp=1;
6 n=200;
7 Ts=200;
8 R_actual=Ts+(7/5);
9 Error_ratio=(200-R_actual)*100/R_actual;
10 printf("Ratio error=%f percent",Error_ratio)
11 Ts=200-(0.5*200/100);
12 n=199/1;
13 R_actual=Ts+(7/5);
```

```
14 Error_ratio=(200-R_actual)*100/R_actual;
15 printf("\nRatio error=% .2f percent",Error_ratio)
```

---

**Scilab code Exa 9.5 Calculate phase angle error at no load**

```
1 //9.5
2 clc;
3 Vp=1000;
4 Vs=100;
5 n=Vp/Vs;
6 pf_no_load=0.4;
7 sina=0.4;
8 cosa= (1-sina^2)^0.5;
9 tana=sina/cosa;
10 Im=0.02;
11 Ie=Im*tana;
12 xp=66.2;
13 rp=94.5;
14 //At no load Is=0 so
15 theta=((Ie*xp)-(Im*rp))/(n*Vs);
16 printf("Phase angle error at no load=% .4f",theta)
```

---

**Scilab code Exa 9.6 Calculate the ratio error**

```
1 //9.6
2 clc;
3 E2=((1.8+5*0.16)^2+(2.4+5*0.195)^2)^0.5;
4 pf2=2.6/E2;
5 AT_sec=600;
6 sina=3.375/E2;
7 AT_pri=600+10.1*pf2+13.4*sina;
8 I1=AT_pri/40;
9 Ratio_error=(15-I1)*100/I1;
```

```
10 printf("Ratio error=% .2f percent",Ratio_error)
```

---

# Chapter 10

## Magnetic Measurements

Scilab code Exa 10.1 Calculate relative permeability

```
1 // 10.1
2 clc;
3 K=0.1*10^-3;
4 d=60;
5 N2=200;
6 phi2=K*d/(2*N2);
7 a2=25*10^-6;
8 B=phi2/a2;
9 N=300;
10 I=10;
11 l=0.1;
12 H=N*I/l;
13 Permeability_absolute=4*pi*10^-7;
14 Permeability_relative=B/(Permeability_absolute*H)
15 printf("Relative permeability of iron=%.2f",
    Permeability_relative)
```

---

Scilab code Exa 10.2 Calculate galvanometer constant

```
1 // 10.2
2 clc;
3 N1=2500;
4 I1=2;
5 l1=1;
6 a2=3*10^-4;
7 Permeability_absolute=4*pi*10^-7;
8 phi2=Permeability_absolute*N1*I1*a2/(l1);
9 N2=50;
10 theta=1;
11 l=10;
12 K=2*N2*phi2/(theta*l);
13 a=60*pi*10^-7;
14 printf("Galvanometer Constant=%f Wb turns/division
",K)
```

---

# Chapter 12

## Basic Transducers

Scilab code Exa 12.1 Calculate change in resistance

```
1 // 12.1
2 clc;
3 K=4;
4 strain=1*10^-6;
5 R=150;
6 dR=K*strain*R*10^6;
7 printf("Change in resistance=%f micro-ohm",dR)
```

---

Scilab code Exa 12.2 Calculate change in length

```
1 // 12.2
2 clc;
3 d=0.03;
4 a=%pi*d^2/4;
5 f=40000;
6 l=0.5;
7 E=3*10^10;
8 dl=f*l/(E*a);
9 printf("Change in length=%f m",dl)
```

---

### Scilab code Exa 12.3 Calculate capacitance

```
1 // 12.3
2 clc;
3 d=10^-4;
4 A=6*10^-3;
5 permitivity_absolute=8.854*10^-12;
6 permitivity_relative=1
7 C=permitivity_absolute*permitivity_relative*A*10^12/
    d;
8 printf("capacitance=%f pF",C)
```

---

### Scilab code Exa 12.4 Calculate the displacement

```
1 // 12.4
2 clc;
3 disp('1.5 cm core displacement produces 6V so ')
4 d_15=6;
5 d_18=1.8*d_15/1.5
6 printf("1.8 cm core displacement produces=%f V",
    d_18);
7 d_08=(-0.8)*(-d_15)/(-1.5);
8 printf("\n-0.8 cm core displacement produces=%f V"
    ,d_08);
9 d_06=(-0.6)*(-d_15)/(-1.5);
10 printf("\n-0.6 cm core displacement produces=%f V"
    ,d_06);
```

---

### Scilab code Exa 12.5 Calculate the acceleration in g and natural frequency

```
1 // 12.5
2 clc;
3 k=4*10^3;
4 dx=0.04;
5 m=0.1;
6 acc=k*dx/m;
7 accg=acc/9.8;
8 printf(" acceleration=%f g" ,accg)
9 fn=(1/2*pi)*(k/m)^0.5;
10 printf("\nNatural Frequency=%f Hz" ,fn)
```

---

# Chapter 14

## Cathode Ray Oscilloscope

**Scilab code Exa 14.1** Calculate the rms value of current

```
1 // 14.1
2 clc;
3 R=3;
4 V_pp =10*6;
5 Vrms=V_pp/(2*2^0.5);
6 Irms=Vrms/R;
7 printf("R.M.S. value of current=%f A",Irms)
```

---

**Scilab code Exa 14.2** Calculate the frequency of the voltage applied

```
1 // 14.2;
2 clc;
3 T=3*10^-3;
4 f=1/T;
5 printf("frequency of the voltage applied=%f m",f)
```

---

**Scilab code Exa 14.3** Calculate the time constant capacitance and maximum frequency

```
1 // 14.3
2 clc;
3 tc=2*2.5;
4 printf("time constant=%.6 f ms" , tc)
5 R=5*10^3;
6 C=(tc*10^-3/R)*10^6;
7 printf("\nCapacitance=% .2 f uF" , C)
8 Tmax=10*R*C*10^-6;
9 fmax=1/Tmax;
10 printf("\nMaximum frequency=% .2 f m" , fmax)
```

---

# Chapter 16

## Polyphase systems

Scilab code Exa 16.1 Calculate Line and phase current

```
1 // 16.1
2 clc;
3 disp('For star connected load')
4 I1=50000/((3^0.5)*440*0.85);
5 printf("\nLine current=%f A",I1)
6 Iph=I1;
7 printf("\nPhase current=%f A",Iph)
8 disp('For Delta connected load')
9 I1=50000/((3^0.5)*440*0.85);
10 printf("\nLine current=%f A",I1)
11 Iph=I1/(3^0.5);
12 printf("\nPhase current=%f A",Iph)
```

---

Scilab code Exa 16.2 2Calculate line current and total power

```
1 // 16.2
2 clc;
3 disp('For star connection')
```

```

4 Zph=(12^2+5^2)^0.5;
5 Eph=440/(3^0.5);
6 Iph=Eph/Zph;
7 I1=Iph;
8 printf("\nLine current=%f A",I1)
9 P_total=(3^0.5)*440*I1*12/(Zph*1000);
10 printf("\nTotal Power=%f kW",P_total)
11
12 disp('For Delta connection')
13 Zph=(12^2+5^2)^0.5;
14 Eph=440;
15 Iph=Eph/Zph;
16 I1=Iph*(3^0.5);
17 printf("\nLine current=%f A",I1)
18 P_total=(3^0.5)*440*I1*12/(Zph*1000);
19 printf("\nTotal Power=%f kW",P_total)

```

---

**Scilab code Exa 16.3 Calculate the resistance and inductive reactance of the load**

```

1 // 16.3
2 clc;
3 pf=(1.8*1000)/(1100*(3^0.5));
4 Z=1100/100;
5 R=Z*pf;
6 printf("\nResistance of the load=%f ohm",R)
7 Xl=(121-108)^0.5;
8 L=Xl/314;
9 printf("\nInductive reactance of the load=%f H",L)

```

---

**Scilab code Exa 16.4 Calculate phase voltage and total power**

```

1 // 16.4
2 clc;

```

---

```

3 Eph=400/(3^0.5);
4 printf("\nPhase voltage=%f V",Eph)
5 P_total=(3^0.5)*400*30*cosd(30)/1000;
6 printf("\nTotal power=%f kW",P_total)

```

---

**Scilab code Exa 16.5 Calculate current in each generator and motor phase**

---

```

1 // 16.5
2 clc;
3 Out_motor=80*735.5;
4 Input_motor=Out_motor/0.8;
5 I_alternator_phase=120.64;
6 I_motor_phase= I_alternator_phase/(3^0.5);
7 printf("\nCurrent in each motor phase=%f A",
       I_motor_phase)
8 printf("\nCurrent in each generator phase=%f A",
       I_alternator_phase)

```

---

**Scilab code Exa 16.6 Calculate the circuit parameters**

---

```

1 // 16.6
2 clc;
3 El=400;
4 Eph=El;
5 Impedance_per_phase= (10^2+15^2)^0.5;
6 Iph= 400/Impedance_per_phase;
7 printf("\nPhase current=%f A",Iph)
8 I1=Iph*3^0.5;
9 printf("\nLine current=%f A",I1)
10 pf=10/Impedance_per_phase;
11 printf("\nPower factor=%f ",pf)
12 P_total=(3^0.5)*El*I1*pf/1000;
13 printf("\nTotal Power=%f kW",P_total)

```

---

```
14 VAR=(3^0.5)*E1*I1*15/(Impedance_per_phase*1000);  
15 printf("\nReactive volt ampers=%f KVAR",VAR)  
16 VA=(3^0.5)*E1*I1/1000;  
17 printf("\nTotal Volt ampers=%f kVA",VA)
```

---

### Scilab code Exa 16.7 Calculate the reduction in power

```
1 // 16.7  
2 clc;  
3 disp('Star connections')  
4 R=20;  
5 Iph=440/(3^0.5*R);  
6 P_total=3*Iph^2*R;  
7 disp('when one of the resistor get disconnected')  
8 Iph=440/(2*20);  
9 P_total_new=2*Iph^2*R;  
10 P_reduction=(P_total-P_total_new)*100/P_total;  
11 printf("\nReduction in Power=%f percent",  
       P_reduction)  
12 disp('Delta connections')  
13 R=20;  
14 Iph=440/(R);  
15 P_total=3*Iph^2*R;  
16 disp('when one of the resistor get disconnected')  
17 Iph=440/(20);  
18 P_total_new=2*Iph^2*R;  
19 P_reduction=(P_total-P_total_new)*100/P_total;  
20 printf("\nReduction in Power=%f percent",  
       P_reduction)
```

---

### Scilab code Exa 16.8 Calculate the circuit parameters

```
1 // 16.8
```

```

2 clc;
3 R=3;
4 XL=4;
5 Z=(R^2+XL^2)^0.5;
6 Iph1=440/(3^0.5*Z);
7 IL1=Iph1;
8 printf("\nLine current=%f A",IL1)
9 P=3*Iph1^2*R;
10 printf("\nPower=%f W",P)
11 pf1=R/Z;
12 printf("\nPower factor=%f (lag)",pf1)
13 IL2=IL1*(4/5);
14 Iph2=IL2/3^0.5;
15 XL2=440/Iph2;
16 C2=1*10^6/(2*50*28.755);
17 printf("\nCapacitance=%f uF",C2)

```

---

**Scilab code Exa 16.9 Calculate the circuit parameters**

```

1 // 16.9
2 clc;
3 IL=11000;
4 Eph=IL/3^0.5;
5 printf("\nLine to neutral voltage=%f V",Eph)
6 E_Each_phase=Eph;
7 printf("\nVoltage induced in Each phase winding=%f f
V",E_Each_phase)
8 T=(242/360)*(1/50)*1000;
9 printf("\nTime interval=%f ms",T)
10 IL_peak=(2^0.5)*IL;
11 printf("\nPeak line voltage=%f V",IL_peak)

```

---

**Scilab code Exa 16.10 Calculate the current in each line and value of each resista**

```
1 // 16.10
2 clc;
3 P_consumed=3000/3;
4 E_per_phase=440/(3^0.5);
5 IL=P_consumed/E_per_phase;
6 printf("\nCurrent in each line=%f A",IL)
7 R=E_per_phase/IL;
8 printf("\nResistance of resistor=%f ohm",R)
```

---

Scilab code Exa 16.11 Calculate circuit constants of load per phase

```
1 // 16.11
2 clc;
3 VL=1100;
4 IL=100;
5 pf=150*1000/(3^0.5*VL*IL);
6 E_per_phase=VL/3^0.5;
7 Zph=E_per_phase/100;
8 Rph=pf*Zph;
9 Xc=(Zph^2-Rph^2)^0.5;
10 C=10^6/(2*pi*50*Xc);
11 disp('Circuit Constants are')
12 printf("\nR=%f ohm",Rph)
13 printf("\nC=%f uF",C)
```

---

Scilab code Exa 16.12 Calculate the readings of watt meters

```
1 // 16.12
2 clc;
3 // P_input=W1+W2=15000.....( i )
4 pf=0.4
5 phi=acosd(0.4);
6 a=tand(phi);
```

```

7 //tand( phi)=(3^0.5)*(W1-W2) /(W1+W2)
8 //on solving W1-W2=3464.2 .....( ii )
9 //From ( i ) and ( ii ) we can calculate
10 W1=9.232;
11 W2=5.768;
12 printf("\nW1=%f kW" ,W1)
13 printf("\nW2=%f kW " ,W2)

```

---

**Scilab code Exa 16.13** Calculate the value of power and power factor

```

1 // 16.13
2 clc;
3 W1=10;
4 W2=-1.2;
5 P_absorbed=W1+W2;
6 printf("\nPower=%f kW" ,P_absorbed)
7 phi=atand((3^0.5)*(W1-W2)/(W1+W2));
8 pf=cosd(phi);
9 printf("\nPower Factor=%f " ,pf)

```

---

**Scilab code Exa 16.14** Calculate the readings of watt meters

```

1 // 16.14
2 clc;
3 P_input=10*735.5/0.82;
4 // P_input=W1+W2=8974.....( i )
5 pf=0.4
6 phi=acosd(0.83);
7 a=tand(phi);
8 //tand( phi)=(3^0.5)*(W1-W2) /(W1+W2)
9 //on solving W1-W2=3482 .....( ii )
10 //From ( i ) and ( ii ) we can calculate
11 W1=6.228;

```

```
12 W2=2.746;  
13 printf("\nW1=%f kW",W1)  
14 printf("\nW2=%f kW",W2)
```

---