

Scilab Textbook Companion for
Basics Of Electrical Engineering
by S. Sharma¹

Created by
Arundhati Yadava
B.Tech
Electrical Engineering
School of Engineering, JRE Group of Institutions
College Teacher
Mr. Abrar Ahmad
Cross-Checked by

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Basics Of Electrical Engineering

Author: S. Sharma

Publisher: I. K. International Publishing House, New Delhi

Edition: 2

Year: 2008

ISBN: 978-81-906942-5-4

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 DC Circuit Analysis and Network Theorems	5
2 Steady State Analysis of Single Phase AC Circuit	73
3 Three Phase AC Circuits	140
4 Measuring Instruments	158
6 Magnetic Circuits	169
7 Single Phase Transformer	179
8 Direct Current Machines	248
10 Three Phase Induction Machines	293
11 Single Phase Induction Motor	317

List of Scilab Codes

Exa 1.1	Independent loop equations	5
Exa 1.2	Resistance between A and B	6
Exa 1.3	Resistance between A and B	7
Exa 1.4	Values of Rab Rcd and Rde	8
Exa 1.5	Rac and Rbd	10
Exa 1.6	Finding value of current by mesh analysis .	11
Exa 1.7	Source transformation	12
Exa 1.8	Source transformation and mesh analysis .	14
Exa 1.9	Equivalent resistance	15
Exa 1.10	Current through R3 using nodal analysis .	16
Exa 1.11	Current through R3 using mesh analysis .	17
Exa 1.12	Current through R3 using superposition theorem	18
Exa 1.13	Current through R3 using Thevenin theorem	19
Exa 1.14	Current through R3 using Norton theorem .	20
Exa 1.15	To find Vx by mesh analysis	21
Exa 1.16	To find Vx by nodal analysis	22
Exa 1.17	To find Vx by Superposition theorem	23
Exa 1.18	To find Vx by Thevenin theorem	24
Exa 1.19	To find Vx by Norton theorem	25
Exa 1.20	To find I using Norton theorem	27
Exa 1.21	To find I using Thevenin theorem	28
Exa 1.22	To find I using mesh analysis	29
Exa 1.23	To find I using nodal analysis	30
Exa 1.24	To find I using Superposition theorem . . .	32
Exa 1.25	To find I using mesh analysis	33
Exa 1.26	To find I using nodal analysis	34
Exa 1.27	To find I using Thevenin theorem	34

Exa 1.28	To find I using Norton theorem	35
Exa 1.29	To find I using Superposition theorem	36
Exa 1.30	Source transformation and mesh and nodal methods	37
Exa 1.31	Delta to star transformation	39
Exa 1.32	To find I through 1 ohm by mesh analysis .	40
Exa 1.33	To find I through 1 ohm R by nodal analysis	41
Exa 1.34	To find I through 1 ohm R by Superposition theorem	43
Exa 1.35	To find I through 1 ohm by Thevenin theorem	45
Exa 1.36	To find I through 1 ohm R by Norton theorem	46
Exa 1.37	To calculate Vab by Thevenin and Norton theorem	47
Exa 1.38	Thevenin and Norton equivalent	49
Exa 1.39	Delta to star transformation to find I	50
Exa 1.40	Currents in different branches	51
Exa 1.41	Current when resistance is connected across AB	52
Exa 1.42	Thevenin and Nodal analysis	53
Exa 1.43	Superposition theorem	55
Exa 1.44	Determination of voltage	56
Exa 1.45	value of resistance	56
Exa 1.46	Resistance of metal filament lamp	57
Exa 1.47	Copper wire and platinum silver wire . . .	58
Exa 1.48	Cells B1 and b2	59
Exa 1.49	Values of R1 and R2	60
Exa 1.50	Currents i1 and i2	61
Exa 1.51	Currents in all branches	62
Exa 1.52	Thevenin theorem and Norton theorem . .	63
Exa 1.53	Thevenin equivalent circuit	65
Exa 1.54	Thevenin theorem	66
Exa 1.55	Nodal analysis	67
Exa 1.56	Delta values	68
Exa 1.57	Superposition theorem to find I	69
Exa 1.58	Thevenin or Norton theorem	70
Exa 1.59	Mesh analysis	71
Exa 2.1	Form factor of sine wave	73
Exa 2.3	Average and rms value	74

Exa 2.4	Vav and Vrms	74
Exa 2.5	Fluorescent lamp	75
Exa 2.6	Single phase motor	76
Exa 2.7	Apparent power of 300 kVA	77
Exa 2.8	Two element series circuit	78
Exa 2.9	120 V 100 W lamp	79
Exa 2.10	Current and power drawn	80
Exa 2.11	To calculate parameters of coil and power factor	81
Exa 2.13	Current in load in rectangular form	82
Exa 2.14	To find frequency and current elements	83
Exa 2.15	Choke coil takes current of 2 Amperes	85
Exa 2.16	Two coils of 5 ohm and 10 ohm connected in parallel	86
Exa 2.17	AC voltage applied to series RC circuit	89
Exa 2.18	Non inductive resistance of 10 ohm	91
Exa 2.19	Admittance in each parallel branch	92
Exa 2.20	Resonant frequency and band width	94
Exa 2.22	Series RLC circuit	95
Exa 2.23	An alternating current of frequency of 50 Hertz	97
Exa 2.24	RMS value average value and form factor	98
Exa 2.25	50 Hz sinusoidal voltage wave shape	99
Exa 2.26	Sinusoidal alternating current of frequency 25 Hz	100
Exa 2.27	Impedance resistance reactance and power factor of the circuit	101
Exa 2.28	Total impedance current drawn from the supply	103
Exa 2.29	An alternating current of frequency of 60 Hertz	105
Exa 2.30	An alternating current with RMS value of 20 A	106
Exa 2.31	Significance of RMS and average values of wave	107
Exa 2.32	Average value effective value and form factor	108
Exa 2.33	Three coils of resistances	109
Exa 2.34	To draw the vector diagram	110
Exa 2.35	Total impedance and total current	111
Exa 2.36	Total current taken from supply	113

Exa 2.37	Current taken by each branch	114
Exa 2.38	To solve example 27 by j method	116
Exa 2.39	To draw the complete vector diagram	116
Exa 2.40	Power factor and average power delivered to the circuit	118
Exa 2.41	100 V 60 W lamp	119
Exa 2.42	Three sinusoidaly alternating currents	121
Exa 2.43	Resultant current wave made up of two com- ponents	122
Exa 2.44	To find power consumed by the circuit	123
Exa 2.45	Quality factor and bandwidth	124
Exa 2.46	To find power consumed and reactive power	125
Exa 2.47	RL series circuit	127
Exa 2.48	Power factor of the combination	128
Exa 2.49	kVA and kW in each branch circuit and in the main circuit	130
Exa 2.50	Current in each branch when total current is 20 A	132
Exa 2.51	Admittance and impedance of the circuit	133
Exa 2.52	Total impedance and current in each branch	134
Exa 2.53	Total impedance and power taken	137
Exa 2.54	Q factor at resonance	138
Exa 3.1	Identical impedances each consisting of 15 ohm in series	140
Exa 3.2	Resistance and reactance values of each impedance	141
Exa 3.3	Three similar coils each of 30 ohms	142
Exa 3.4	Line and phase current when phase sequence is positive	144
Exa 3.5	Power measurement by 2 wattmeter method	146
Exa 3.6	3300 V synchronous alternator	147
Exa 3.7	Three phase star connected system	149
Exa 3.8	Balanced delta connection	150
Exa 3.9	400 V 50 Hz three phase supply	151
Exa 3.11	Balanced load of 20kVA	153
Exa 3.12	Three identical impedances each having a re- sistance R	156
Exa 4.1	Deflecting torque exerted on a coil	158
Exa 4.2	Current through galvanometer	159

Exa 4.3	Resistance of wire	159
Exa 4.4	Resistance required to read current and voltage	160
Exa 4.5	Number of revolutions made by energy meter and percentage error	161
Exa 4.6	Series resistance to measure 500 V on full scale	162
Exa 4.7	Percentage error of energy meter	163
Exa 4.8	Resistance required to read current and voltage	164
Exa 4.9	Percentage error of meter	164
Exa 4.10	Readings of two voltmeters	165
Exa 4.11	Readings of two voltmeters with different internal resistances	166
Exa 4.12	Total current carried by two ammeters	167
Exa 6.1	Magnetic circuit having two air gaps	169
Exa 6.2	Steel ring of 25 cm mean diameter	171
Exa 6.3	Magnetic circuit with cast steel core	173
Exa 6.4	Iron ring made of round iron rod	174
Exa 6.5	Ring made of composite material	176
Exa 7.1	To calculate magnetizing component of no load current	179
Exa 7.2	To calculate the primary current	180
Exa 7.3	To find the voltage regulation	182
Exa 7.4	10 kVA transformer	184
Exa 7.5	Transformer with 350 primary and 1050 secondary turns	186
Exa 7.6	Primary current and power factor	187
Exa 7.8	Efficiency of transformer	188
Exa 7.9	Core loss current of distribution transformer	191
Exa 7.10	Number of turns on HT and LT sides	192
Exa 7.11	To calculate primary and full load currents .	193
Exa 7.12	Magnetising component of no load current .	194
Exa 7.13	Current taken by primary	196
Exa 7.14	To calculate total resistance and reactance referred to primary	197
Exa 7.15	To calculate percent regulation at full load .	199
Exa 7.16	Maximum value of percent regulation	200

Exa 7.17	200 kVA transformer with 1000 W iron loss and 2000 W copper loss at full load	202
Exa 7.18	To calculate all day efficiency	203
Exa 7.19	Open circuit and short circuit test	205
Exa 7.20	4kVA 200 400 V transformer	207
Exa 7.21	To determine the regulation while supplying full load	209
Exa 7.22	Total equivalent resistance referred to primary and secondary	210
Exa 7.23	33 kVA 2200 220 V 50 Hz transformer	211
Exa 7.24	To calculate secondary terminal voltage	214
Exa 7.25	15 kVA 2200 110 V transformer	216
Exa 7.26	Open circuit and short circuit test	219
Exa 7.27	Open and short circuit test	221
Exa 7.28	Open and short circuit test	223
Exa 7.29	200 kVA 4000 1000 V transformer	227
Exa 7.30	Secondary terminal voltage at full load	229
Exa 7.31	To calculate the value of maximum flux density in the core and the emf	230
Exa 7.32	To calculate total copper loss	231
Exa 7.33	No load and short circuit results of transformer	233
Exa 7.34	50 kVA transformer of 5 is to 1 ratio of turns	235
Exa 7.35	No load and short circuit results of transformer	237
Exa 7.36	Value of load for maximum efficiency	238
Exa 7.37	To calculate regulation at full load	240
Exa 7.38	Total no load loss	242
Exa 7.39	Percentage of hysteresis and copperloss	243
Exa 7.40	To draw the phasor diagram	245
Exa 7.41	Star connected auto transformer	246
Exa 8.1	Generated emf	248
Exa 8.2	Ratio of speed	249
Exa 8.3	Armature induced emf and developed torque and efficiency	250
Exa 8.4	Armature resistance and load current at maximum efficiency	251
Exa 8.5	BHP of prime mover	252
Exa 8.6	20 HP 230 V 1150 rpm shunt motor	254
Exa 8.7	New operating speed	255

Exa 8.8	250 V DC shunt machine	256
Exa 8.9	Torque developed in the motor	258
Exa 8.10	6 pole DC machine with 400 conductors . .	259
Exa 8.11	Total emf generated in the armature	261
Exa 8.12	Terminal voltage of the machine	262
Exa 8.13	Current in each conductor and emf generated	263
Exa 8.14	Armature resistance and load current at maximum efficiency	264
Exa 8.15	Full load speed	265
Exa 8.16	250 V 4 pole shunt motor	266
Exa 8.17	200 V DC shunt motor	267
Exa 8.18	Value of inserted resistance	269
Exa 8.19	New speed of motor on inserting a 250 ohm resistance	270
Exa 8.20	Reduction of main flux to raise the speed by 50 percent	271
Exa 8.21	10 kW 6 pole DC generator	272
Exa 8.22	Shunt wound motor running at 600 rpm from a 230 V supply	274
Exa 8.23	Value of inserted resistance in field circuit for increasing the speed	275
Exa 8.24	New speed of motor on inserting a 250 ohm resistance in the field circuit	276
Exa 8.25	24 slot 2 pole DC machine	277
Exa 8.27	Counter emf of motor and power developed in armature	279
Exa 8.28	Voltage between far end of feeder and bus bar	280
Exa 8.29	Speed of motor when connected in series with 5 ohm resistance	280
Exa 8.30	Value of starting torque	281
Exa 8.31	Value of speed when flux is increased by 20 percent	282
Exa 8.32	250 V series motor with 20 A current and 1000 rpm	283
Exa 8.33	Resistance to be added to obtain rated torque at starting and at 1000 rpm	285
Exa 8.34	Total emf and armature current	286
Exa 8.35	Armature current and induced emf	287

Exa 8.36	Constant losses and full load efficiency	288
Exa 8.37	Hysteresis and eddy current losses	290
Exa 8.38	Speed of motor when flux per pole is increased by 10 percent	291
Exa 10.2	6 pole wound rotor induction motor	293
Exa 10.3	3 phase induction motor running at 1140 rpm	296
Exa 10.4	3 phase squirrel cage motor	298
Exa 10.5	Speed of motor	299
Exa 10.6	Speed of 4 pole induction motor	300
Exa 10.7	4 pole 3 phase induction motor	301
Exa 10.8	3 phase induction motor with synchronous speed 1200 rpm	302
Exa 10.9	150 kW 6 pole star connected induction motor	304
Exa 10.10	6 pole 60 Hz induction motor	305
Exa 10.11	4 pole induction motor	306
Exa 10.12	3 phase 440 V distribution	307
Exa 10.13	3 phase 50 Hz induction motor	309
Exa 10.14	10 kW 400 V delta connected induction motor	311
Exa 10.15	4 pole 3 phase SRIM	313
Exa 10.16	3 phase induction motor	314
Exa 11.1	Shaft torque	317
Exa 11.2	Slip and resistance in forward and backward direction	318

Chapter 1

DC Circuit Analysis and Network Theorems

Scilab code Exa 1.1 Independent loop equations

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 1  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 1");  
7  
8 //VARIABLE INITIALIZATION  
9 b=14; //number of branches  
10 n=8; //number of nodes  
11  
12 //SOLUTION  
13 m=b-n+1; //number of loop  
equations  
14 disp(sprintf("The total number of independent loop  
equations are %d",m));  
15  
16 //END
```

Scilab code Exa 1.2 Resistance between A and B

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 2  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 2");  
7  
8 //VARIABLE INITIALIZATION  
9 // star values ra , rc and rd  
10 ra=2; //in Ohms  
11 rc=4; //in Ohms  
12 rd=3; //in Ohms  
13 r1=5; //in Ohms  
14 r2=4; //in Ohms  
15 r3=6; //in Ohms  
16  
17 //SOLUTION  
18 //converting star with points A, C and D into delta  
ACD  
19 r=(ra*rc)+(rc*rd)+(rd*ra); // 'r' is the  
resistance that appears in the numerator of the  
equation of star-delta conversion  
20  
21 //delta values rac , rcd and rad  
22 rac=r/rd;  
23 rcd=r/ra;  
24 rad=r/rc;  
25 req1=(r1*rad)/(r1+rad); // equivalent  
resistance between A and D  
26 req2=(r2*rcd)/(r2+rcd); // equivalent  
resistance between C and D
```

```

27 req3=req1+req2;           // series combination
    of resistors
28 req4=(req3*rac)/(req3+rac); // parallel
    combination of resistors
29 req5=req4+r3;
30 req6=(req5*7)/(req5+7);
31 disp(sprintf("The equivalent resistance between
    points A and B is %f ",req6));
32
33 //END

```

Scilab code Exa 1.3 Resistance between A and B

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 3
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 r1=4.6;                      // in Ohms
10 r2=7.6;                     // in Ohms
11
12
13 // star values
14 rc=3;
15 rd=7;
16 re=5;
17
18 //SOLUTION
19 //converting star with points C, D and E to delta
    CDE
20 r=(rc*rd)+(rd*re)+(re*rc);   // 'r' is the

```

```

        resistance that appears in the numerator of the
        equation of star-delta conversion
21
22 //delta values rcd , rde and rec
23 rcd=r/re;
24 rde=r/rc;
25 rec=r/rd;
26 req1=(8*rec)/(8+rec);           // equivalent
        resistance between C and E
27 req2=(6*rde)/(6+rde);         // equivalent
        resistance between D and E
28 req3=(4*rcd)/(4+rcd);         // equivalent
        resistance between C and D
29 req4=req2+req3;
30 req5=(req1*req4)/(req1+req4); // parallel
        combination of resistors
31 req6=req5+r1;                // series combination
        of resistors
32 req7=(req6*r2)/(req6+r2);
33 disp(sprintf("The equivalent resistance between
        points A and B is %f    ",req7));
34
35 //END

```

Scilab code Exa 1.4 Values of Rab Rcd and Rde

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 4
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION

```

```

9 r1=1;                                //LHS resistance in
                                         Ohms
10 r2=2;                                 //in Ohms
11 r3=3;                                 //in Ohms
12 r4=4;                                 //in Ohms
13 r5=5;                                 //in Ohms
14 r6=6;                                 //in Ohms
15 r7=7;                                 //in Ohms
16 r8=8;                                 //RHS resistance in
                                         Ohms
17
18 //SOLUTION
19
20 //To find resistance between a and b
21 req1=r1+r2;                           //series combination
                                         of resistors
22 req2=(req1*r3)/(req1+r3);           //parallel combination
                                         of resistors
23 req3=req2+(r4+r5);
24 req4=(req3*r6)/(req3+r6);
25 req5=req4+r7;
26 req6=(req5*r8)/(req5+r8);
27 disp(sprintf("The equivalent resistance between
                  points a and b is %f    ",req6));
28
29 //To find resistance between c and d
30 req7=r7+r8;
31 req8=(req7*r6)/(req7+r6);
32 req9=req2+r5+req8;
33 req10=(req9*r4)/(req9+r4);
34 disp(sprintf("The equivalent resistance between
                  points c and d is %f    ",req10));
35
36 //To find resistance between d and e
37 req11=req2+r4+r5;
38 req12=(req11*r6)/(req11+r6);
39 req13=(req12*req7)/(req12+req7);
40 disp(sprintf("The equivalent resistance between

```

```
    points d and e is %f    ",req13));  
41  
42 //END
```

Scilab code Exa 1.5 Rac and Rbd

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 5  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 5");  
7  
8 //VARIABLE INITIALIZATION  
9 r1=2;                                //in Ohms  
10 r2=4;                                 //in Ohms  
11 r3=8;                                 //in Ohms  
12 r4=8;                                 //in Ohms  
13 r5=2;                                 //middle resistance in  
                                         Ohms  
14  
15 //SOLUTION  
16  
17 //To find resistance between a and c  
18 req1=r1+r2;  
19 req2=r1+r4;  
20 req3=(req1*r1)/(req1+r1);  
21 rac=(req3*req2)/(req3+req2);  
22 disp(sprintf("The equivalent resistance between  
points a and c is %f    ",rac));  
23  
24 //To find resistance between b and d  
25 //converting delta abc into star with points a, b  
                                         and c
```

```

26 //delta values
27 rab=r1;
28 rbc=r2;
29 rac=6;
30 //star values
31 r=rab+rbc+rac;           // 'r' is the resistance
                            that appears in the denominator of the equation
                            of delta-star conversion
32 ra=(rab*rbc)/r;
33 rb=(rab*rac)/r;
34 rc=(rbc*rac)/r;
35 req5=rb+rac;
36 req6=rc+8;
37 rbd=ra+((req5*req6)/(req5+req6));
38 disp(sprintf("The equivalent resistance between
points b and d is %f ",rbd));
39
40 //END

```

Scilab code Exa 1.6 Finding value of current by mesh analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
THEOREMS
2 //Example 6
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 n=4;                                //number of
nodes
10 b=6;                                 //number of
branches
11

```

```

12 //SOLUTION
13 m=b-n+1;                                     // number of
   mesh equations
14 disp(sprintf("Number of mesh equations are %d",m));
15 nd=n-1;                                       //number of
   node equations
16 disp(sprintf("Number of node equations are %d",nd));
17
18 // (5/2) I1+(-2)I2+(-1/2)I3 = 4.....eq (1)
19 // (0) I1+(0) I2+(1) I3 = -2 .....eq (2)
20 // (-2) I1+(10/3) I2+(-1/3) I3 =0....eq (3)
21 //using matrix method to solve the set of equations
22 A=[5/2 -2 -1/2;-2 10/3 -1/3;0 0 1];
23 b=[4;0;-2];
24 x=inv(A)*b;
25 I=x(1,:);                                     //to access
   the 1st element of 3X1 matrix
26 disp(sprintf("The current from the source Vs is %d A
   ",I));
27
28 //END

```

Scilab code Exa 1.7 Source transformation

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 7
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 I1=1;                                         // current source in
   Amperes

```

```

10 v1=4;                                // voltage source in
   Volts
11 v2=3;                                // voltage source in
   Volts
12 v3=6;                                // voltage source in
   Volts
13 r1=2;                                // resistance in Ohms
14 r2=2;                                // resistance in Ohms
15 r3=1;                                // resistance in Ohms
16 r4=3;                                // resistance in Ohms
17
18 //SOLUTION
19 //converting all the voltage sources into current
   sources
20 I2=v1/r1;
21 I3=v2/r3;
22 I4=v3/r4;
23 disp(sprintf("The four current sources are %d A, %d
   A, %d A and %d A",I1,I2,I3,I4));
24
25 req1=(r1*r2)/(r1+r2);                // parallel
   combination of resistors
26 req2=(r3*r4)/(r3+r4);
27 v2=(I1+I4)*req1;
28 v3=(I3-I2)*req2;
29 req=req1+req2;
30 v=v2+v3;
31 I=v/req;
32 disp("VOLTAGE EQUIVALENT CIRCUIT:");
33 disp(sprintf("    Voltage source= %f V",v));
34 disp(sprintf("    Equivalent resistance(in series)=
   %f ",req));
35 disp("CURRENT EQUIVALENT CIRCUIT:");
36 disp(sprintf("    Current source= %f A",I));
37 disp(sprintf("    Equivalent resistance(in parallel)=
   %f ",req));
38
39 //END

```

Scilab code Exa 1.8 Source transformation and mesh analysis

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 8  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 8");  
7  
8 //VARIABLE INITIALIZATION  
9 I=2;                                // current source  
    in Amperes  
10 r1=1/2;                               //in Ohms  
11 r2=1/2;                               //in Ohms  
12  
13 //SOLUTION  
14 //the current source of 2A is converted into two 1V  
    sources  
15 v1=I*r1;  
16 v2=I*r2;  
17 disp(sprintf("The voltage sources after conversion  
    are %d V and %d V",v1,v2));  
18 //(5/2)I1+(-1)I2 = 0.....eq (1) // applying KVL in  
    mesh 1  
19 //(-1)I1+(7/2)I2 = 2.....eq (2) // applying KVL in  
    mesh 2  
20 //using matrix method to solve the set of equations  
21 A=[5/2 -1;-1 7/2];  
22 b=[2;2];  
23 x=inv(A)*b;  
24 x=x(2,:);  
25 disp(sprintf("The current in 2 resistor is %f A",x  
));
```

26
27 //END

Scilab code Exa 1.9 Equivalent resistance

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
  THEOREMS
2 //Example 9
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 r1=1;                                //in Ohms
10 r2=2;                                 //in Ohms
11 r3=3;                                 //in Ohms
12 r4=1;                                 //in Ohms
13
14 //SOLUTION
15
16 //delta values
17 rab=r1;                               //between points a
  and b
18 rac=r2;                               //between points a
  and c
19 rbc=r3;                               //between points b
  and c
20 //converting delta abc into star with points a, b and
  c
21 //star values ra, rb and rc
22 r=rab+rbc+rac;                      // 'r' is the
  resistance that appears in the denominator of the
  equation of delta-star conversion
23 ra=(rab*rac)/r;
```

```

24 rb=(rab*rbc)/r;
25 rc=(rbc*rac)/r;
26 req1=r1+r4;
27 req2=rb+r2;
28 req3=(req1*req2)/(req1+req2);
29 req4=ra+req3;
30 disp(sprintf("The equivalent input resistance is %f
                 ",req4));
31
32 //END

```

Scilab code Exa 1.10 Current through R3 using nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
      THEOREMS
2 //Example 10
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 v=10;                                // voltage source in
                                         Volts
10 I=5;                                  // current source in
                                         Amperes
11 r1=2;                                 // in Ohms
12 r2=2;                                 // in Ohms
13 r3=4;                                 // in Ohms
14
15 //SOLUTION
16 res=I+(v/r1);
17 v1=res/((1/r1)+(1/r2)+(1/r3));
18 I1=v1/r3;
19 disp(sprintf("By Nodal analysis , the current through

```

```
    resistor R3 is %d A",I1));  
20  
21 //END
```

Scilab code Exa 1.11 Current through R3 using mesh analysis

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 11  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 11");  
7  
8 //VARIABLE INITIALIZATION  
9 I3=-5;                                //direction of  
    I3 is opposite to the current which flows from  
    the current source  
10  
11 //SOLUTION  
12  
13 // using mesh analysis , the following equations are  
    obtained  
14 // (4) I1+(-2)I2 = 10..... eq (1)  
15 // (-2)I1+(6)I2 = -20..... eq (2)  
16 // solving the two equations using matrix method  
17 A=[4 -2; -2 6];  
18 b=[10; -20];  
19 x=inv(A)*b;  
20 I1=x(1,:);                            //to access 1st  
    element of 2X1 matrix  
21 I2=x(2,:);                            //to access 2nd  
    element of 2X1 matrix  
22 I=I2-I3;  
23 disp(sprintf("By mesh analysis , the current through
```

```
    resistor R3 is %d A" ,I));  
24  
25 //END
```

Scilab code Exa 1.12 Current through R3 using superposition theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 12  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 12");  
7  
8 //VARIABLE INITIALIZATION  
9 v=10;                                //voltage source  
   in Volts  
10 I=5;                                  //current source  
   in Amperes  
11 r1=2;                                 //in Ohms  
12 r2=2;                                 //in Ohms  
13 r3=4;                                 //in Ohms  
14  
15 //SOLUTION  
16  
17 //deactivating current source  
18 v1=(v/r1)/((1/r1)+(1/r2)+(1/r3));  //using nodal  
   analysis  
19 I1=v1/r3;  
20  
21 //deactivating voltage source  
22 v2=I/((1/r1)+(1/r2)+(1/r3));        //using nodal  
   analysis  
23 I2=v2/r3;  
24 I_tot=I1+I2;                          //applying
```

```

25
26 Superposition Theorem (I1 and I2 are in same
27 direction)
28 disp(sprintf("By Superposition Theorem, the current
   through resistor R3 is %d A",I_tot));
29 //END

```

Scilab code Exa 1.13 Current through R3 using Thevenin theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 13
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 13");
7
8 //VARIABLE INITIALIZATION
9 v=10;                                // voltage source in
   Volts
10 I=5;                                 // current source in
   Amperes
11 r1=2;                                // in Ohms
12 r2=2;                                // in Ohms
13 r3=4;                                // in Ohms
14
15 //SOLUTION
16 //solving by nodal analysis
17 res=I+(v/r1);                         // 'res' is used to
   make the calculation easy
18 vth=res/((1/r1)+(1/r2));             // Thevenin voltage
19 rth=(r1*r2)/(r1+r2);                 // Thevenin resistance
20 Ith=vth/(rth+r3);                   // Thevenin current
21 disp(sprintf("By Thevenin Theorem, the current

```

```
through resistor R3 is %d A",Ith));  
22  
23 //END
```

Scilab code Exa 1.14 Current through R3 using Norton theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 14  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 14");  
7  
8 //VARIABLE INITIALIZATION  
9 v=10; // voltage source in  
Volts  
10 I3=-5; // current source in  
Amperes  
11 r1=2; // in Ohms  
12 r2=2; // in Ohms  
13 r3=4; // in Ohms  
14  
15 //SOLUTION  
16 //by loop analysis  
17 //(1) I1+(-1)I2 = 0..... eq (1)  
18 //(4) I1+(-2)I2 = 10..... eq (2)  
19 //solving the equations by matrix method  
20 A=[1 -1;4 -2];  
21 b=[0;10];  
22 x=inv(A)*b;  
23 I1=x(1,:); // to access 1st  
element of 2X1 matrix  
24 I2=x(2,:); // to access 2nd  
element of 2X1 matrix
```

```

25 In=I2-I3;
26 rn=(r1*r2)/(r1+r2);
27 I=(rn*In)/(rn+r3);
28 disp(sprintf("By Norton Theorem , the current through
    resistor R3 is %d A",I));
29
30 //END

```

Scilab code Exa 1.15 To find Vx by mesh analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 15
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 v=7;                                // voltage source in
    Volts
10 I=7;                                 // current source in
    Amperes
11 r3=1;                                // in Ohms
12
13 //SOLUTION
14 //(1) I1+(-4)I2+(4)I3 = 7..... eq (1)
15 //(-1)I1+(6)I2+(-3)I3 = 0..... eq (2)
16 //(1)I1+(0)I2+(-1)I3 = 7..... eq (3)
17 //solving the equations by matrix method
18 A=[1 -4 4;-1 6 -3;1 0 -1];
19 b=[7;0;7];
20 x=inv(A)*b;
21 I1=x(1,:);                           //to access the 1st
    element of 3X1 matrix

```

```

22 I2=x(2,:);                                //to access the 2nd
      element of 3X1 matrix
23 I3=x(3,:);                                //to access the 3rd
      element of 3X1 matrix
24 vx=-(I3*r3);
25 disp(sprintf("By Mesh analysis , the value of Vx is
      %d V",vx));
26
27 //END

```

Scilab code Exa 1.16 To find Vx by nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 16
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 16");
7
8 //VARIABLE INITIALIZATION
9 v=7;                                         // voltage source in
   Volts
10 I=7;                                         // current source in
    Amperes
11 r1=1;                                         //in Ohms
12 r2=2;                                         //in Ohms
13 r3=1;                                         //in Ohms
14 r4=2;                                         //in Ohms
15 r5=3;                                         //in Ohms
16
17 //SOLUTION
18 //(4)vb+(-1)vc = 0 ..... eq (1)
19 //(-2)vb+(11)vc = 21 ..... eq (2)
20 //solving the equations by matrix method

```

```

21 A=[4 -1;-2 11];
22 b=[0;21];
23 x=inv(A)*b;
24 vb=x(1,:); //to access the 1st
   element of 2X1 matrix
25 vc=x(2,:); //to access the 2nd
   element of 2X1 matrix
26 vx=-vc;
27 disp(sprintf("By Nodal analysis , the value of Vx is
    %d V",vx));
28
29 //END

```

Scilab code Exa 1.17 To find V_x by Superposition theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 17
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 17");
7
8 //VARIABLE INITIALIZATION
9 v=7; // voltage source in
   Volts
10 I=7; // current source in
   Amperes
11 r1=1; //in Ohms
12 r2=2; //in Ohms
13 r3=1; //in Ohms
14 r4=2; //in Ohms
15 r5=3; //in Ohms
16
17 //SOLUTION

```

```

18
19 //deactivating the current source
20 res=(v/4)+(v/2);
21 vc=res/((1/4)+(1/r1)+(1/r2));
22 vx1=-vc;
23
24 //deactivating voltage source
25 //(4)va+(-1)vb = -21.....eq (1)
26 //(2)va+(-11)vb = 0.....eq (2)
27 //solving the equations by matrix method
28 A=[4 -1;2 -11];
29 b=[-21;0];
30 x=inv(A)*b;
31 va=x(1,:);                                //to access 1st
32 vb=x(2,:);                                //to access 2nd
33 vx2=-vb;
34 vx=vx1+vx2;
35 disp(sprintf("By Superposition Theorem, the value of
   Vx is %d V",vx));
36
37 //END

```

Scilab code Exa 1.18 To find Vx by Thevenin theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 18
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 18");
7
8 //VARIABLE INITIALIZATION

```

```

9 v=7;                                // voltage source in
   Volts
10 I=7;                                // current source in
   Amperes
11 r1=1;                                //in Ohms
12 r2=2;                                //in Ohms
13 r3=1;                                //in Ohms
14 r4=2;                                //in Ohms
15 r5=3;                                //in Ohms
16
17 //SOLUTION
18 //solving by mesh analysis
19 I2=0;                                 //since mesh 2 is
   open
20 I1=I-I2;
21 I3=I1/6;                             //from the equation
   of mesh 3
22 vth=-(r2*I3)+v;                     //Thevenin voltage
23 r=r1+r5;                            //series combination
   of resistors
24 rth=(r*r4)/(r+r4);                  //parallel
   combination of resistors (Thevenin resistance)
25 I=vth/(rth+r3);                    //Thevenin current
26 vx=-I*r3;
27 disp(sprintf("By Thevenin Theorem , the value of Vx
   is %d V",vx));
28
29 //END

```

Scilab code Exa 1.19 To find V_x by Norton theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 19
3

```

```

4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 19");
7
8 //VARIABLE INITIALIZATION
9 v=7; // voltage source in
      Volts
10 I=7; // current source in
       Amperes
11 r1=1; //in Ohms
12 r2=2; //in Ohms
13 r3=1; //in Ohms
14 r4=2; //in Ohms
15 r5=3; //in Ohms
16
17 //SOLUTION
18 //by using mesh analysis , the following equations
   are obtained
19 // (1) I1+(-4)I2+(3)In = 7..... eq (1)
20 // (-1)I1+(6)I1+(-3)In = 0..... eq (2)
21 // (0)I1+(1)I2+(-1)In = 0..... eq (3)
22 // solving the equations by matrix method
23 A=[1 -4 3;-1 6 -3;0 1 -1];
24 b=[7;0;0];
25 x=inv(A)*b;
26 I1=x(1,:); //to access the 1st
   element of 3X1 matrix
27 I2=x(2,:); //to access the 2nd
   element of 3X1 matrix
28 IN=x(3,:); //to access the 3rd
   element of 3X1 matrix; IN is Norton current
29 r=r1+r5; //series combination
   of resistors
30 rN=(r*r4)/(r+r4); // parallel
   combination of resistors (Norton resistance)
31 I=(rN*IN)/(rN+r3);
32 vx=-I*r3;
33 disp(sprintf("By Norton Theorem , the value of Vx is

```

```
    %d V" ,vx));  
34  
35 //END
```

Scilab code Exa 1.20 To find I using Norton theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 20  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 20");  
7  
8 //VARIABLE INITIALIZATION  
9 I=20;                                // current source  
    in Amperes  
10 v1=10;                                 // voltage source  
    in Volts  
11 v2=40;                                 // voltage source  
    in Volts  
12 r1=8;                                  // in Ohms  
13 r2=5;                                  // in Ohms  
14 r3=4;                                  // in Ohms  
15 r4=12;                                 // in Ohms  
16  
17 //SOLUTION  
18 req=r1+r2;  
19 rn=(req*r3)/(req+r3);  
20 //finding In by mesh analysis  
21 //(17)I2+(-4)I3 = 110.....eq (1)  
22 //(1)I2+(-1)I3 = -10.....eq (2)  
23 //solving the equations by matrix method  
24 A=[17 -4;1 -1];  
25 b=[110;-10];
```

```

26 x=inv(A)*b;
27 I2=x(1,:);                                //to access the 1
     st element of 2X1 matrix
28 I3=x(2,:);                                //to access the 2
     nd element of 2X1 matrix
29 In=I3;
30 I=(rn*In)/(rn+r4);
31 disp(sprintf("By Norton Theorem, the value of I is
   %f A",I));
32
33 //END

```

Scilab code Exa 1.21 To find I using Thevenin theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 21
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 21");
7
8 //VARIABLE INITIALIZATION
9 I=20;                                         // current source
   in Amperes
10 v1=10;                                         // voltage source
    in Volts
11 v2=40;                                         // voltage source
    in Volts
12 r1=8;                                          // in Ohms
13 r2=5;                                          // in Ohms
14 r3=4;                                          // in Ohms
15 r4=12;                                         // in Ohms
16
17 //SOLUTION

```

```

18
19 req=r1+r2; // series
   combination of resistors
20 rth=(req*r3)/(req+r3); // parallel
   connection of resistors (Thevenin resistance)
21
22 //by using nodal analysis , the following equations
   are obtained
23 // (13)v1+(-8)v2=750.....eq (1)
24 // (-4)v1+(9)v2=200.....eq (2)
25 // solving the equations by matrix method
26
27 A=[13 -8;-4 9];
28 b=[750;200];
29 x=inv(A)*b;
30 v1=x(1,:); //to access the 1
   st element of 2X1 matrix
31 v2=x(2,:); //to access the 2
   nd element of 2X1 matrix
32 vth=v2; //Thevenin voltage
33 I=vth/(rth+r4); //Thevenin current
34 disp(sprintf("By Thevenin Theorem , the value of I is
   %f A",I));
35
36 //END

```

Scilab code Exa 1.22 To find I using mesh analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 22
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 22");

```

```

7
8 //VARIABLE INITIALIZATION
9 I1=20;                                // current source
10 v1=10;                                 // voltage source
11 v2=40;                                 // voltage source
12 r1=8;                                  // in Ohms
13 r2=5;                                  // in Ohms
14 r3=4;                                  // in Ohms
15 r4=12;                                 // in Ohms
16
17 //SOLUTION
18
19 //by using mesh analysis the following equations are
   obtained
20 // (17) I2+(-4)I3 = 110.....eq (1)
21 // (-1)I2+(4)I3 = 10.....eq (2)
22 //solving the equations by matrix method
23 A=[17 -4;-1 4];
24 b=[110;10];
25 x=inv(A)*b;
26 I2=x(1,:);                           //to access the 1
   st element of 2X1 matrix
27 I3=x(2,:);                           //to access the 2
   nd element of 2X1 matrix
28 I=I3;
29 disp(sprintf("By mesh analysis , the value of I is %f
   A",I));
30
31 //END

```

Scilab code Exa 1.23 To find I using nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 23
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 23");
7
8 //VARIABLE INITIALIZATION
9 I1=20;                                // current source
   in Amperes
10 v1=10;                                 // voltage source
    in Volts
11 v2=40;                                 // voltage source
    in Volts
12 r1=8;                                  // in Ohms
13 r2=5;                                  // in Ohms
14 r3=4;                                  // in Ohms
15 r4=12;                                 // in Ohms
16
17 //SOLUTION
18 // (17) I2+(-4)I3 = 110..... eq (1)
19 // (-4)v1+(16)I3 = 40..... eq (2)
20 // solving the equations by matrix method
21 A=[17 -4;-4 16];
22 b=[110;40];
23 x=inv(A)*b;
24 I2=x(1,:);                            //to access the 1
   st element of 2X1 matrix
25 I3=x(2,:);                            //to access the 2
   nd element of 2X1 matrix
26 disp(sprintf("By Nodal analysis , the value of I is
   %f A",I3));
27
28 //END

```

Scilab code Exa 1.24 To find I using Superposition theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 24  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 24");  
7  
8 //VARIABLE INITIALIZATION  
9 I=20;                                // current source  
    in Amperes  
10 v1=10;                                // voltage source  
     in Volt  
11 v2=40;                                // voltage source  
     in Volts  
12 r1=8;                                  // in Ohms  
13 r2=5;                                  // in Ohms  
14 r3=4;                                  // in Ohms  
15 r4=12;                                 // in Ohms  
16  
17 //SOLUTION  
18  
19 // activating 20A current source  
20 r=r2+((r3*r4)/(r3+r4));  
21 I1=(r*I)/(r+r1);  
22 I_20=(r3*I1)/(r3+r4);  
23  
24 // activating 10V battery source  
25 req=r1+r2;  
26 v_10=(-v1/req)/((1/req)+(1/r3)+(1/r4));  
27 I_10=v_10/r4;  
28
```

```

29 // activating 40V battery source
30 v_40=(v2/r3)/((1/req)+(1/r3)+(1/r4));
31 I_40=v_40/r4;
32 I_tot=I_20+I_10+I_40;
33 disp(sprintf("By Superposition Theorem, the value of
   I is %f A", I_tot));
34
35 //END

```

Scilab code Exa 1.25 To find I using mesh analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 // Example 25
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 25");
7
8 //SOLUTION
9 // (1) I1+(0) I2+(0) I3 = 5 . . . . . . . . . . eq (1)
10 // (-20) I1+(50) I2+(-20) I3 = 0 . . . . . . . . . eq (2)
11 // (0) I1+(1) I2+(-1) I3 = 5 . . . . . . . . . . eq (3)
12 // solving the equations by matrix method
13 A=[1 0 0;-20 50 -20;0 1 -1];
14 b=[5;0;5];
15 x=inv(A)*b;
16 I1=x(1,:);                                //to access the 1
   st element of 3X1 matrix
17 I2=x(2,:);                                //to access the 2
   nd element of 3X1 matrix
18 I3=x(3,:);                                //to access the 3
   rd element of 3X1 matrix
19 I=I2;
20 disp(sprintf("By Mesh analysis, the value of I is %d

```

```
    A" , I));  
21  
22 //END
```

Scilab code Exa 1.26 To find I using nodal analysis

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 26  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 26");  
7  
8 //VARIABLE INITIALIZATION  
9 I1=5;                                // current source in  
                                         Ampères  
10 v2=100;                               // voltage source in  
                                         Volts  
11 r1=20;                                // in Ohms  
12 r2=10;                                // in Ohms  
13 r3=20;                                // in Ohms  
14  
15 //SOLUTION  
16 v1=(I1+(v2/r2))/((1/r1)+(1/r2));  
17 I=(v1-v2)/r2;  
18 disp(sprintf("By Nodal analysis , the value of I is  
%d A" ,I));  
19  
20 //END
```

Scilab code Exa 1.27 To find I using Thevenin theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 27
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 27");
7
8 //VARIABLE INITIALIZATION
9 I1=5;                                // current source in
    Ampères
10 vb=100;                               // voltage source in
    Volts
11 r1=20;                                // in Ohms
12 r2=10;                                // in Ohms
13 r3=20;                                // in Ohms
14
15 //SOLUTION
16 va=I1*r1;                            // by applying node
    analysis at point 'a'
17 vth=va-vb;                            // Thevenin voltage
    vth=vab
18 rth=r1+((r3*0)/(r3+0));             // Thevenin resistance
19 I=vth/(rth+r2);
20 disp(sprintf("By Thevenin Theorem , the value of I is
    %d A",I));
21
22 //END

```

Scilab code Exa 1.28 To find I using Norton theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 28
3

```

```

4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 28");
7
8 //VARIABLE INITIALIZATION
9 I1=5;                                // current source in
                                         Ampères
10 va=100;                               // voltage source in
                                         Volts
11 r1=20;                                // in Ohms
12 r2=10;                                // in Ohms
13 r3=20;                                // in Ohms
14
15 //SOLUTION
16 IN=I1-(va/r1);                      // using nodal
                                         analysis at point 'a'
17 rN=r1+((r3*0)/(r3+0));
18 I=(rN*IN)/(rN+r2);
19 disp(sprintf("By Norton Theorem, the value of I is
%d A",I));
20
21 //END

```

Scilab code Exa 1.29 To find I using Superposition theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
THEOREMS
2 //Example 29
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 29");
7
8 //VARIABLE INITIALIZATION
9 I=5;                                // current source in

```

```

    Ampères
10 v=100;                                // voltage source in
    Volts
11 r1=20;                                 // in Ohms
12 r2=10;                                 // in Ohms
13 r3=20;                                 // in Ohms
14
15 //SOLUTION
16
17 // activating current source
18 I1=(I*r1)/(r1+r2);                  //by current divider
    law
19
20 // activating voltage source
21 I2=-(v/(r1+r2));
22
23 I_tot=I1+I2;
24 disp(sprintf("By Superposition Theorem, the value of
    I is %d A",I_tot));
25
26 //END

```

Scilab code Exa 1.30 Source transformation and mesh and nodal methods

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 30
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 30");
7
8 //VARIABLE INITIALIZATION
9 I1=25;                                // current source
    in Ampères

```

```

10 I2=20;                                // current source
    in Amperes
11 v=20;                                 // voltage source
    in Volts
12 r1=4;                                  //LHS resistance
    in Ohms
13 r2=10;                                 //in Ohms
14 r3=2;                                  //in Ohms
15 r4=1;                                  //in Ohms
16 r5=10;                                 //RHS resistance
    in Ohms
17
18 //SOLUTION
19
20 //source transformation
21 v1=I1*r1;                               // current source
    I1 is converted to voltage source v1
22 v2=I2*r3;                               //current source
    I2 is converted to voltage source v2
23
24 //using mesh analysis
25 // (8)IA+(-1)IB = 30..... eq (1)
26 // (-2)IA+(3)IB = 20..... eq (2)
27 // solving the equations by matrix method
28 A=[8 -1;-2 3];
29 b=[30;20];
30 x=inv(A)*b;
31 IA=x(1,:);                            //to access the 1
    st element of 2X1 matrix
32 IB=x(2,:);                            //to access the 2
    nd element of 2X1 matrix
33 disp(sprintf("By Mesh analysis I_A= %d A and I_B= %d
    A",IA,IB));
34
35 // using nodal analysis
36 req=r1+r2;
37 res=(v1/req)+(v2/r3)+(v/r4);
38 v3=res/((1/req)+(1/r3)+(1/r4));

```

```

39 I3=(v1-v3)/req;
40 I4=(v2-v)/r3; //since here ((v2-
    v)/r3)=((v3-v)/r4) (this is only done for
    convinient calculation)
41 disp(sprintf("By Nodal analysis I_1= %d A and I_2=
    %d A",I3,I4));
42
43 //END

```

Scilab code Exa 1.31 Delta to star transformation

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 // Example 31
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 31");
7
8 //VARIABLE INITIALIZATION
9 r1=6; //in Ohms
10 r2=4; //in Ohms
11 r3=4; //in Ohms
12 r4=4; //in Ohms
13 r5=6; //in Ohms
14 r6=6; //in Ohms
15 r7=6; //in Ohms
16 r8=8; //in Ohms
17 r9=4; //in Ohms
18 r10=10; //in Ohms
19 r11=10; //middle resistance
    in Ohms
20
21 //SOLUTION
22 //converting delta cde in a star

```

```

23 req1=r5+r6+r7;
24 req2=(r6*r7)/req1;
25 req3=(r5*r6)/req1;
26 req4=(r5*r7)/req1;
27
28 req5=r1+r2+r3;                                //on LHS of middle
     resistance
29 req6=r4+req2;                                //top LHS
30 req7=req4+r11;                               //equivalent middle
     resistance
31 req8=req3+r8+r9+r10;                          //top RHS
32
33 req9=(req7*req8)/(req7+req8);                //parallel
     combination of resistors
34 req10=req9+req6;                             //series combination
     of resistors
35 req11=(req5*req10)/(req5+req10);
36
37 disp(sprintf("The equivalent resistance between A
     and B is %d ",req11));
38
39 //END

```

Scilab code Exa 1.32 To find I through 1 ohm by mesh analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 32
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 32");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                         // current source in

```

```

    Ampères
10 v=10;                                // voltage source in
    Volts
11 r1=4;                                 //top resistance in
    Ohms
12 r1=4;                                 //right resistance
    in Ohms
13 r3=4;                                 //bottom resistance
    in Ohms
14 r4=6;                                 //left resistance in
    Ohms
15 r5=1;                                 //in Ohms
16
17 //SOLUTION
18 //without converting the current source into voltage
    source
19 // (10)I1+(-4)I2+(0)I3 = 50..... eq (1)
20 // (-4)I1+(9)I2+(-4)I3 = 0..... eq (2)
21 // (0)I1+(-4)I2+(8)I3 = 10..... eq (3)
22 //solving the equations by matrix method
23 A=[10 -4 0;-4 9 -4;0 -4 8];
24 b=[50;0;10];
25 x=inv(A)*b;
26 I2=x(2,:);                           //to access the 2nd
    element of 3X1 matrix
27 disp(sprintf("By Mesh analysis , the current through
    1 resistor is %f A",I2));
28
29 //END

```

Scilab code Exa 1.33 To find I through 1 ohm R by nodal analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 33

```

```

3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 33");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                // current source in
   Ampères
10 v=10;                                 // voltage source in
    Volts
11 r1=4;                                //top resistance in
   Ohms
12 r1=4;                                //right resistance
   in Ohms
13 r3=4;                                //bottom resistance
   in Ohms
14 r4=6;                                //left resistance in
   Ohms
15 r5=1;                                //in Ohms
16
17 //SOLUTION
18
19 //by applying nodal analysis at node 1, the
   following equations are obtained:
20 // (17)v1+(-12)v2=150.....eq (1)
21 // (-4)v1+(6)v2=10.....eq (2)
22 // solving the equations by matrix method
23
24 A=[17 -12;-4 6];
25 b=[150;10];
26 x=inv(A)*b;
27 v1=x(1,:);                           //to access the 1st
   element of 2X1 matrix
28 v2=x(2,:);                           //to access the 1st
   element of 2X1 matrix
29 if(v1>v2) then
30 I=(v1-v2)/r5;
31 disp(sprintf("By nodal analysis , the current through

```

```

1      resistor is %f A",I));
32 else
33 I=(v2-v1)/r5;
34 disp(sprintf("By nodal analysis , the current through
1      resistor is %f A",I));
35 end;
36
37 //END

```

Scilab code Exa 1.34 To find I through 1 ohm R by Superposition theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
THEOREMS
2 // Example 34
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 34");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                // current source in
                                         Ampères
10 v=10;                                 // voltage source in
                                         Volts
11 r1=4;                                 //top resistance in
                                         Ohms
12 r1=4;                                 // right resistance
                                         in Ohms
13 r3=4;                                 //bottom resistance
                                         in Ohms
14 r4=6;                                 //left resistance in
                                         Ohms
15 r5=1;                                 //in Ohms
16
17 //SOLUTION

```

```

18
19 // activating the current source
20 //  $(17)v_1 + (-12)v_2 = 120$  ..... eq (1)
21 //  $(-4)v_1 + (6)v_2 = 0$  ..... eq (2)
22 // solving the equations by matrix method
23 A=[17 -12;-4 6];
24 b=[120;0];
25 x=inv(A)*b;
26 v1=x(1,:); // to access the 1st
   element of 2X1 matrix
27 v2=x(2,:); // to access the 1st
   element of 2X1 matrix
28 if(v1>v2) then
29 I1=(v1-v2)/r5;
30 else
31 I1=(v2-v1)/r5;
32 end;
33
34 // activating the voltage source
35 //  $(17)v_1 + (-12)v_2 = 30$  ..... eq (1)
36 //  $(-4)v_1 + (6)v_2 = 10$  ..... eq (2)
37 // solving the equations by matrix method
38 A=[17 -12;-4 6];
39 b=[30;10];
40 x=inv(A)*b;
41 v3=x(1,:); // to access the 1st
   element of 2X1 matrix
42 v4=x(2,:); // to access the 1st
   element of 2X1 matrix
43 if(v3>v4) then
44 I2=(v3-v4)/r5;
45 else
46 I2=(v4-v3)/r5;
47 end;
48
49 I_tot=I1+I2;
50 disp(sprintf("By Superposition Theorem, the current
   through 1 resistor is %f A",I_tot));

```

```
51
52 //END
```

Scilab code Exa 1.35 To find I through 1 ohm by Thevenin theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 35
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 35");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                // current source in
   Ampères
10 v=10;                                 // voltage source in
    Volts
11 r1=4;                                // top resistance in
   Ohms
12 r2=4;                                // right resistance
   in Ohms
13 r3=4;                                // bottom resistance
   in Ohms
14 r4=6;                                // left resistance in
   Ohms
15 r5=1;                                // in Ohms
16
17 //SOLUTION
18 res=I+(v/r1);                         // 'res' is used to
   make calucations easy
19 va=res/((1/r4)+(1/r1));                // applying nodal
   analysis at node 1
20 vb=(v/r2)/((1/r2)+(1/r3));            // applying nodal
   analysis at node 2
```

```

21 vth=va-vb;
22 req1=(r1*r4)/(r1+r4);
23 req2=(r2*r3)/(r2+r3);
24 rth=req1+req2;
25 Ith=vth/(rth+r5);
26 disp(sprintf("By Thevenins Theorem, the current
through the 1 resistor is %f A",Ith));
27
28 //END

```

Scilab code Exa 1.36 To find I through 1 ohm R by Norton theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
THEOREMS
2 //Example 36
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 36");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                //current source
   in Amperes
10 v=10;                                 //voltage source
    in Volts
11 r1=4;                                  //top resistance
    in Ohms
12 r2=4;                                  //right
    resistance in Ohms
13 r3=4;                                  //bottom
    resistance in Ohms
14 r4=6;                                  //left resistance
    in Ohms
15 r5=1;                                  //in Ohms
16

```

```

17 //SOLUTION
18 // (1) v1+(12/5)In = 30 ..... eq (1)
19 // (2) v1+(-4)In = 10 ..... eq (2)
20 A=[1 12/5;2 -4];
21 b=[30;10];
22 x=inv(A)*b;
23 v1=x(1,:); //to access the
               1st element of 2X1 matrix
24 In=x(2,:); //to access the
               2nd element of 2X1 matrix
25 req1=(r1*r4)/(r1+r4);
26 req2=(r2*r3)/(r2+r3);
27 rn=req1+req2;
28 I1=(rn*In)/(rn+r5);
29 disp(sprintf("By Norton Theorem , the current through
               1 resistor is %f A",I1));
30
31 //END

```

Scilab code Exa 1.37 To calculate Vab by Thevenin and Norton theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 37
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 37");
7
8 //VARIABLE INITIALIZATION
9 v1=90; //voltage source
         in Volts
10 r1=8; //in Ohms
11 r2=6; //in Ohms
12 r3=5; //in Ohms

```

```

13 r4=4; // in Ohms
14 r5=8; // diagonal
15 r6=8; // in Ohms
16
17 //SOLUTION
18
19 //solution (i): using Thevenin's Theorem
20 // (3)v1+(-2)v2 = 90..... eq (1) // applying nodal
   analysis at node 1
21 // (-2)v1+(4)v2 = -90..... eq (2) // applying nodal
   analysis at node 2
22 A=[3 -2;-2 4];
23 b=[90;-90];
24 x=inv(A)*b;
25 v1=x(1,:);
26 v2=x(2,:);
27 vth=v1;
28 req1=(r1*r5)/(r1+r5);
29 req2=req1+r4;
30 req3=(req2*r6)/(req2+r6);
31 rth=req3+r2;
32 vab1=(vth*r3)/(rth+r3);
33 disp(sprintf("By Thevenins Theorem, the value of Vab
   is %f V",vab1));
34
35 //solution (ii): using Norton's Theorem
36 // (13)v1+(-7)v2 = 270..... eq (1) // applying nodal
   analysis at node 1
37 // (7)v1+(-13)v2 = 0..... eq (2) // applying nodal
   analysis at node 2
38 A=[13 -7;7 -13];
39 b=[270;0];
40 x=inv(A)*b;
41 v1=x(1,:);
42 v2=x(2,:);
43 req1=(r1*r5)/(r1+r5);
44 req2=req1+r4;

```

```

45 req3=(req2*r6)/(req2+r6);
46 rN=req3+r2;
47 if(v1>v2) then
48 IN=(v1-v2)/r2;
49 else
50 IN=(v2-v1)/r2;
51 end;
52 vab2=(r3*IN)*(rN/(rth+r3));
53 disp(sprintf("By Nortons Theorem, the value of Vab
      is %f V",vab2));
54
55 //END

```

Scilab code Exa 1.38 Thevenin and Norton equivalent

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 38
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 38");
7
8 //VARIABLE INITIALIZATION
9 I=2;                                // current source in
   Amperes
10 r1=2;                                 // in Ohms
11 r2=1;                                 // in Ohms
12 r3=1;                                 // in Ohms
13 r4=2;                                 // in Ohms
14
15 //SOLUTION
16
17 //Thevenin Equivalent circuit
18 I1=1;                                // since there is

```

```

            equal resistance of 3 , hence , current=1A
19 vth=(I1*r2)+(-I1*r4);
20 req1=r1+r2;
21 req2=r3+r4;
22 rth=(req1*req2)/(req1+req2);
23 disp("THEVENIN EQUIVALENT CIRCUIT IS-");
24 disp(sprintf("      Thevenin voltage= %d V",vth));
25 disp(sprintf("      Thevenin resistance= %f      ",rth)
   );
26
27 //Norton Equivalent circuit
28 v1=I/((1/r2)+(1/r4));
29 v2=-I/((1/r3)+(1/r1));
30 req1=r1+r2;
31 req2=r3+r4;
32 rn=(req1*req2)/(req1+req2);
33 Isc=(v1/r4)+v2;
34 disp("NORTON EQUIVALENT CIRCUIT IS-");
35 disp(sprintf("      Norton current= %f A",Isc));
36 disp(sprintf("      Norton resistance= %f      ",rn));
37
38 //END

```

Scilab code Exa 1.39 Delta to star transformation to find I

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 39
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 39");
7
8 //VARIABLE INITIALIZATION
9 v=2;                                // in Volts

```

```

10 r=2;                                // in Ohms
11
12 //SOLUTION
13 z_star=r/3;
14 req1=(r/3)+r;
15 req2=(r/3)+r;
16 req3=(req1*req2)/(req1+req2);
17 req4=(r/3)+req3;
18 req5=(req4*r)/(req4+r);
19 I=v/req5;
20 disp(sprintf("The value of I is %d A",I));
21
22 //END

```

Scilab code Exa 1.40 Currents in different branches

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 40
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 40");
7
8 //VARIABLE INITIALIZATION
9 v1=20;                                // in Volts
10 v2=10;                                 // in Volts
11 r1=5;                                  // top resistance in
   Ohms
12 r2=10;                                 // bottom resistance in
   Ohms
13 r3=5;                                  // in Ohms
14 r4=5;                                  // in Ohms
15 r5=10;                                 // in Ohms
16

```

```

17 //SOLUTION
18 // (5) I1+(10)I3+(-10)I4 = 20 ..... eq (1)
19 // (0) I1+(10)I3+(10)I4 = -50 ..... eq (2)
20 // (5) I1+(20)I3+(0)I4 = -30 ..... eq (3) (eq(1) +
   eq(2))
21 // Since the determinant of matrix A is 0, hence , the
   set of these equations cannot be solved by
   matrix method
22 //So, solving them directly ,
23
24 I3=-15/25;
25 I1=-3-(3/5);
26 I4=-5-(-3/5);
27 I=I1+3+5;
28 disp("The currents (in Amperes) flowing in different
   branches are :");
29 disp(I1);
30 disp(I3);
31 disp(I4);
32 disp(sprintf("The total current is %f A",I));
33
34 //END

```

Scilab code Exa 1.41 Current when resistance is connected across AB

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 41
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 41");
7
8 //VARIABLE INITIALIZATION
9 vs=6;                                // in Volts

```

```

10 Is=4;                                // in Amperes
11 r1=5;                                 // in Ohms
12 r2=2;                                 // in Ohms
13 r3=2;                                 // in Ohms
14 r=2/3;                                // in Ohms
15 r4=3;                                 // in Ohms
16 r5=1;                                 // in Ohms
17 r6=2;                                 // in Ohms
18
19 //SOLUTION
20 req1=(r2*r3)/(r2+r3);
21 req2=req1+r1;                         // resistance across
   vs
22 va=vs/req2;                           // voltage divider law
23 rth1=(req1*r1)/(req1+r1);
24 I1=Is*(r2/req2);                     // current divider law
25 vb=I1*r4;
26 rth2=(r4*r4)/(r4+r4);
27 I=(vb-va)/(rth1+r+rth2);
28 disp(sprintf("The value of the current is %d A",I));
29
30 //END

```

Scilab code Exa 1.42 Thevenin and Nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 42
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 42");
7
8 //VARIABLE INITIALIZATION
9 v=10;                                  // in Volts

```

```

10 I=0.5; // in Amperes
11 r1=4; //top LHS
    resistance in Ohms
12 r2=2; //top RHS
    resistance in Ohms
13 r3=2; //first
    resistance in Ohms
14 r4=2; //second
    resistance in Ohms
15
16 //SOLUTION
17
18 //using Thevenin's theorem
19 rth=(r1*r3)/(r1+r3);
20 vth=v*(r3/(r1+r3)); //Thevenin
    voltage
21 R=(40-(56*I))/(24*I); //solving for R
    directly
22 disp(sprintf("(i) By Thevenins Theorem, the value of
    R is %d ",R));
23
24 //v1=(10R+4)/(3R+4).....eq(1) //using nodal
    analysis at node 1
25 //v1=1+R.....eq(2) //using nodal
    analysis at node 2
26 //the following the quadratic equation is formed
    when both the equations are compared
27 //(3)R^2+(-3)R+(0)=0
28 //solving the quadratic equation
29 a=3;
30 b=-3;
31 c=0;
32 D=(b^2)-(4*a*c); //discriminant
33 R1=(-b+sqrt(D))/(2*a);
34 R2=(-b-sqrt(D))/(2*a);
35 if(R1==1) then
36 disp(sprintf("(ii) By Nodal analysis, the value of R
    is %d ",R1));

```

```

37 else
38 disp(sprintf("( ii ) By Nodal analysis , the value of R
            is %d      ",R1));
39 end;
40
41 //END

```

Scilab code Exa 1.43 Superposition theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 43
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 43");
7
8 //VARIABLE INITIALIZATION
9 Is1=2;                                // first current
   source in Amperes
10 Is2=4;                                 // second current
    source in Amperes
11 v=2;                                    //in Volts
12 r1=200;                                 //in Ohms
13 r2=100;                                 //in Ohms
14 r3=4;                                   //in Ohms
15
16 //SOLUTION
17 req1=34;
18 Ia=Is2*(r3/req1);
19 req2=24;
20 Iab=Is1*(req2/req1);
21 I=Ia+Iab;
22 vab=I*10;
23 disp(sprintf("By Superposition Theorem the voltage

```

```
24 Vab = %f V" ,vab));  
25 //END
```

Scilab code Exa 1.44 Determination of voltage

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 44  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 44");  
7  
8 //VARIABLE INITIALIZATION  
9 I=40; //in Amperes  
10 r=5; //in Ohms  
11  
12 //SOLUTION  
13 v=I*r; //Ohm's Law  
14 disp(sprintf("The voltage required is %d V" ,v));  
15  
16 //END
```

Scilab code Exa 1.45 value of resistance

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 45  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 45");
```

```

7
8 //VARIABLE INITIALIZATION
9 w=5*1000;                                //power consumed by
   coil in Watts
10 v=200;                                    //applied voltage in
    Volts
11
12 //SOLUTION
13 r=(v^2)/w;                                //since w=(v^2) / r
14 disp(sprintf("Value of resistance is %d ",r));
15
16 //END

```

Scilab code Exa 1.46 Resistance of metal filament lamp

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 46
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 46");
7
8 //VARIABLE INITIALIZATION
9 v=240;                                     //in Volts
10
11 //SOLUTION
12 //case1: p=60W
13 p1=60;                                       //in Watts
14 r1=(v^2)/p1;
15 disp(sprintf("Resistance of the metal filament lamp
   is %d ",r1));
16
17 //case2: p=100W
18 p2=100;                                      //in Watts

```

```

19 r2=(v^2)/p2;
20
21 if(r1>r2) then
22 disp(sprintf("Resistance of %d W lamp will be
     greater",p1));
23 else
24 disp(sprintf("Resistance of %d W lamp will be
     greater",p2));
25 end;
26
27 //END

```

Scilab code Exa 1.47 Copper wire and platinum silver wire

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 // Example 47
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 47");
7
8 //VARIABLE INITIALIZATION
9 lc=20;                                //length of copper
   wire in m
10 dc=0.015/100;                          //diameter of copper
    wire in m
11 rhoc=1.7;                             // specific resistance
   for copper
12 lp=15;                                 //length of platinum
   silver wire in m
13 dp=0.015/100;                          //diameter of
   platinum silver wire in m
14 rhop=2.43;                            // specific resistance
   for platinum silver

```

```

15
16 //SOLUTION
17
18 //for copper wire
19 sc=(%pi/4)*(dc^2); // area
20 rc=rhoc*(lc/sc);
21
22 //for platinum silver
23 sp=(%pi/4)*(dp^2); // area
24 rp=rhop*(lp/sp);
25
26
27 if(rc>rp) then
28 disp("Copper wire has greater resistance");
29 else
30 disp("Platinum silver wire has greater resistance");
31 end;
32
33 //END

```

Scilab code Exa 1.48 Cells B1 and b2

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 48
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 48");
7
8 //VARIABLE INITIALIZATION
9 v1=2.05; //1st cell in
    Volts
10 v2=2.15; //2nd cell in
    Volts

```

```

11 r1=0.05;                                //in Ohms
12 r2=0.04;                                //in Ohms
13 r3=1;                                   //in Ohms
14
15 //SOLUTION
16 // (r3+r1) I1+(r3) I2=v1 ..... eq (1)
17 // (r3) I1+(r3+r2) I2=v2 ..... eq (2)
18 req1=r3+r1;
19 req2=r3+r2;
20 A=[req1 r3;r3 req2];
21 b=[v1;v2];
22 x=inv(A)*b;
23 I1=x(1,:);                           //to access the
                                         1st element of 2X1 matrix
24 I2=x(2,:);                           //to access the
                                         2nd element of 2X1 matrix
25 I=I1+I2;
26 pd=I*r3;
27 disp(sprintf("Current through B1 is %f A",I1));
28 disp(sprintf("Current through B2 is %f A",I2));
29 disp(sprintf("Potential difference across AC is %f V
",pd));
30
31 //END

```

Scilab code Exa 1.49 Values of R1 and R2

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 49
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 49");
7

```

```

8 //VARIABLE INITIALIZATION
9 v1=110;                                // voltage source in
   Volts
10 v2=80;                                 // voltage source in
    Volts
11 v3=50;                                 // voltage source in
    Volts
12 r=2;                                    // in Ohms
13
14 //SOLUTION
15
16 //solution (a)
17 I1=4;                                    // charging
18 I2=6;                                    // charging
19 r1=((v1-v2)-((I1+I2)*r))/I1;
20 r2=((v1-v3)-((I1+I2)*r))/I2;
21 disp(sprintf("(a) R1= %f ",r1));
22 disp(sprintf("      R2= %f ",r2));
23
24 //solution (b)
25 I1=2;                                    // discharging
26 I2=20;                                   // charging
27 r1=((v1-v2)-((I2-I1)*r))/(-I1);
28 r2=((v1-v3)-((I2-I1)*r))/I2;
29 disp(sprintf("(b) R1= %f ",r1));
30 disp(sprintf("      R2= %f ",r2));
31
32 //solution (c)
33 I1=0;
34 I2=(v1-v2)/r;
35 r2=((v1-v3)-(I2*r))/I2;
36 disp(sprintf("(c) I1=0 when R2= %d ",r2));
37
38 //END

```

Scilab code Exa 1.50 Currents i1 and i2

```
1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 // Example 50  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 50");  
7  
8 //SOLUTION  
9 // (5) I1+(-3)I2 = 10..... eq (1)  
10 // (-3)I1+(34)I2 = 40..... eq (2)  
11 A=[5 -3;-3 34];  
12 b=[10;40];  
13 x=inv(A)*b;  
14 I1=x(1,:); //to access the 1st  
element of 2X1 matrix  
15 I2=x(2,:); //to access the 2nd  
element of 2X1 matrix  
16 I=I2-I1;  
17 disp(sprintf("Current i1 is %f A (loop EFAB)",I1));  
18 disp(sprintf("Current i2 is %f A (loop BCDE)",abs(I)) );  
19  
20 //END
```

Scilab code Exa 1.51 Currents in all branches

```
1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 // Example 51  
3  
4 clc;  
5 disp("CHAPTER 1");
```

```

6 disp("EXAMPLE 51");
7
8 //SOLUTION
9 // (9) I1+(-5)I2+(-3)I3 = 5 ..... eq (1)
10 // (-5)I1+(8)I2+(-1)I3 = 5 ..... eq (2)
11 // (-3)I1+(-1)I2+(6)I3 = 3 ..... eq (3)
12 A=[9 -5 -3;-5 8 -1;-3 -1 6];
13 b=[5;5;3];
14 x=inv(A)*b;
15 I1=x(1,:); //to access the 1st
   element of 3X1 matrix
16 I2=x(2,:); //to access the 2nd
   element of 3X1 matrix
17 I3=x(3,:); //to access the 3rd
   element of 3X1 matrix
18 disp(sprintf("Current i1 is %f A (loop ABGH)",I1));
19 disp(sprintf("Current i2 is %f A (loop BCDH)",I2));
20 disp(sprintf("Current i3 is %f A (loop GDEF)",I3));
21
22 //END

```

Scilab code Exa 1.52 Thevenin theorem and Norton theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 52
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 52");
7
8 //VARIABLE INITIALIZATION
9 v1=20; //LHS voltage source
   in Volts
10 v2=12; //RHS voltage source

```

```

    in Volts
11 r1=5;                                //LHS resistance in
    Ohms
12 r2=2;                                //in Ohms
13 r3=8;                                //in Ohms
14 r4=10;                               //RHS resistance in
    Ohms
15
16 //SOLUTION
17
18 //by Thevenin's Theorem
19 rth=r3+((r1*r2)/(r1+r2));           //Thevenin
    resistance
20 v=v1*(r2/(r1+r2));                  //voltage divider
    law
21 vab=-v2+(r3*0)+(rth*0)+v;
22 It=vab/(rth+r4);                   //current obtained
    by applying Thevenin's Theorem
23 Isc=vab/rth;
24 disp(sprintf("By Thevenins Theorem , current in the
    10 resistor is %f A",It));
25
26 //verification by Norton's Theorem
27 //(7)I1+(2)I2 = 20.....eq (1)
28 /(2)I1+(10)I2 = 12.....eq (2)
29 //solving the equations using matrix method
30 A=[7 2;2 10];
31 b=[20;12];
32 x=inv(A)*b;
33 x1=x(1,:);                          //to access 1st
    element of 2X1 matrix
34 x2=x(2,:);                          //to access 2nd
    element of 2X1 matrix and Isc=-x2
35 Isc=-x2;                            //Isc is negative
    because its direction is opposite to I2
36 I=Isc*(rth/(rth+r4));            //current obtained
    by applying Norton's Theorem
37 if(It==I)

```

```

38 disp(sprintf("By Nortons Theorem , current in the 10
            resistor is %f A",I));
39 disp(sprintf("Hence , answer is confirmed by Norton
            Theorem"));
40 else
41 disp(sprintf("The answer is not confirmed by Norton
            Theorem"));
42 end;
43
44 //END

```

Scilab code Exa 1.53 Thevenin equivalent circuit

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 53
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 53");
7
8 //VARIABLE INITIALIZATION
9 v1=10;                                //LHS voltage source
   in Volts
10 v2=4;                                 //RHS voltage source
    in Volts
11 r1=2;                                  //LHS resistance in
   Ohms
12 r2=3;                                  //in Ohms
13 r3=10;                                 //in Ohms
14 r4=3;                                  //in Ohms
15 r5=1;                                  //RHS resistance in
   Ohms
16
17 //SOLUTION

```

```

18 van=v1*(r2/(r1+r2));           // voltage divider
   law
19 vbn=-v2*(r4/(r5+r4));           // voltage divider
   law
20 ran=(r1*r2)/(r1+r2);
21 rbn=(r4*r5)/(r4+r5);
22 vab=(ran*0)+van-vbn+(rbn*0);    // current is zero as
   AB is open circuited when Thevenin's Theorem is
   applied
23 disp(sprintf("The Thevenin voltage is %d V",vab));
24
25 //END

```

Scilab code Exa 1.54 Thevenin theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 54
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 54");
7
8 //VARIABLE INITIALIZATION
9 v=5;                           // voltage source in
   Volts
10 r1=1;                          //LHS resistance in
   Ohms
11 r2=5;                          //in Ohms
12 r3=1;                          //in Ohms
13 r4=1;                          //RHS resistance in
   Ohms
14 I=10;                          // current source in
   Amperes
15

```

```

16 //SOLUTION
17
18 req1=r1+r3+r4;                                //on deactivating
      the current source , current I1 flows in the
      circuit
19 I1=v/req1;
20 vab1=v-(I1*r1);                            //(I1*r1) is voltage
      drop across 1    resistance
21 I2=I/req1;
22 vab2=vab1+(I2*r1);                            //(I2*r1) is voltage
      drop across 1    resistance
23 req=r1+((r3*r4)/(r3+r4));                  //'req' is the same
      as 'Rth' mentioned in the book
24 I=vab2/(req+r2);
25 RTh=(6/5)+(3/4);
26 req2=10+2;
27 I3=9/12;
28 disp(sprintf("The value of the current is %f A",I3))
      ;
29
30 //END

```

Scilab code Exa 1.55 Nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
      THEOREMS
2 //Example 55
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 55");
7
8 //VARIABLE INITIALIZATION
9 vcd=50;                                //voltage source in
      Volts

```

```

10 v=100;                                // voltage source in
   Volts
11 r1=40;                                 //in Ohms
12 r2=50;                                 //in Ohms
13 r3=20;                                 //in Ohms
14 r4=10;                                 //in Ohms
15
16 //SOLUTION
17 res=(vcd/r2)-(v/r3);                  // 'res' (short for
   result) is used to make calculations easy
18 vp=res/((1/r2)+(1/r3)+(1/r4));
19 vba=vp+v;
20 disp(sprintf("The voltage between A and B is %f V" ,
   vba));
21
22 //END

```

Scilab code Exa 1.56 Delta values

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 56
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 56");
7
8 //VARIABLE INITIALIZATION
9 r=1;                                     // this is an
   assumption
10 r1=r*1;                                  //in Ohms
11 r2=r*2;                                  //in Ohms
12 r3=r*3;                                  //in Ohms
13
14 //SOLUTION

```

```

15 req=(r1*r2)+(r2*r3)+(r3*r1);      // 'req' is the
   equivalent resistance that appears in the
   numerator of the equation of star-delta
   conversion
16 ra=req/r3;
17 rb=req/r1;
18 rc=req/r2;
19 disp(sprintf("The equivalent delta values are ra=(%
    %f x r) , rb=( %f x r) and rc=( %f x r) " ,
    ra,rb,rc));
20
21 //END

```

Scilab code Exa 1.57 Superposition theorem to find I

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 57
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 57");
7
8 //VARIABLE INITIALIZATION
9 v=10;                      // voltage source in
   Ohms
10 r1=2;                      //RHS resistance in
   Ohms
11 r2=2;                      //in Ohms
12 r3=4;                      //in Ohms
13 r4=4;                      //in Ohms
14 I=20;                      //current source in
   Amperes
15
16 //SOLUTION

```

```

17
18 r=r1+r2;
19 //deactivating voltage source of 10
20 v1=-I/((1/r)+(1/r3)+(1/r4)); //from equation
21 I1=v1/r3;
22
23 //deactivating current source of 20A
24 v2=(v/r)/((1/r)+(1/r3)+(1/r4));
25 I2=v2/r3;
26
27 I_tot=I1+I2;
28 if(I_tot>0)
29 disp(sprintf("The value of I is %f A (upward)", I_tot
    ));
30 else
31 disp(sprintf("The value of I is %f A (downward)", -I_tot));
32
33 //END

```

Scilab code Exa 1.58 Thevenin or Norton theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 58
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 58");
7
8 //VARIABLE INITIALIZATION
9 v1=20; //LHS voltage source in
      Volts
10 v2=5; //RHS voltage source in
       Volts

```

```

11 r1=100; //LHS resistance in
           Ohms
12 r2=2;   //in Ohms
13 r3=1;   //in Ohms
14 r4=4;   //in Ohms
15 r5=1;   //RHS resistance in
           Ohms
16
17 //SOLUTION
18
19 //applying Thevenin's Theorem
20 //Thevenin's equivalent resistance , r_th is same as
   r_AB
21 r_th=((r3+r5)*r2)/((r3+r5)+r2);
22 v_th=(v1-v2)/2; //from the equation
23 I1=v_th/(r4+r_th);
24 v1=I1*r4;
25 disp(sprintf("By Thevenin Theorem , the value of V is
   %d V",v1));
26
27 //applying Norton's Theorem
28 //Norton's equivalent resistance , r_n is same as
   r_AB
29 r_n=((r3+r5)*r2)/((r3+r5)+r2);
30 I_n=(v1-v2)/r2; //since v_A=0
31 I2=r_n*(I_n/(r4+r_n));
32 v2=I2*r4;
33 disp(sprintf("By Norton Theorem , the value of V is
   %d V",v2));
34
35 //END

```

Scilab code Exa 1.59 Mesh analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 59
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 59");
7
8 //SOLUTION
9
10 //I1+I2 = 20 . . . . . . . . . . . . . . . . eq (1)
11 //−I1+I2 = 10 . . . . . . . . . . . . . . . . eq (2)
12 //solving the simultaneous equations by matrix
   method
13
14 A=[1 1;-1 1];
15 b=[20;10];
16 I=inv(A)*b;
17 I1=I(1,:);           //to access 1st element of
   2X1 matrix
18 I2=I(2,:);           //to access 2nd element of
   2X1 matrix
19 disp(sprintf("Current I1= %d A",I1));
20 disp(sprintf("Current I2= %d A",I2));
21
22 //END

```

Chapter 2

Steady State Analysis of Single Phase AC Circuit

Scilab code Exa 2.1 Form factor of sine wave

```
1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
     .C. CIRCUIT
2 //Example 1
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 1");
7
8 //SOLUTION
9
10 //average value
11 v_av=(integrate('sin(x)', 'x', 0, %pi))/(2*%pi);
12
13 //rms value
14 v_rms=(integrate('sin(x)^2', 'x', 0, %pi))/(2*%pi);
15 v_rms=sqrt(v_rms);
16
17 ff=v_rms/v_av;
18 disp(sprintf("The form factor is %f", ff));
```

```
19
20 //END
```

Scilab code Exa 2.3 Average and rms value

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 3
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 v_m=5;                                //peak value of
    voltage in Volts
10
11 //SOLUTION
12 v_av=(integrate('v_m*sin(x)', 'x', 0, %pi)) / (%pi);
13 v_rms=(integrate('(v_m*sin(x))^2', 'x', 0, %pi)) / (%pi);
14 v_rms=sqrt(v_rms);
15 disp(sprintf("Average value of full wave rectifier
    sine wave is %f V", v_av));
16 disp(sprintf("Effective value of full wave rectifier
    sine wave is %f V", v_rms));
17
18 //END
```

Scilab code Exa 2.4 Vav and Vrms

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 4
```

```

3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 v_m=10;                                //peak value of
   voltage in Volts
10 angle=60*(%pi/180);                   //delay angle in
   radians
11
12 //SOLUTION
13 v_av=(integrate('v_m*sin(x)', 'x', angle, %pi)) / (%pi);
14 v_rms=(integrate(' (v_m*sin(x))^2 ', 'x', angle, %pi)) / (
   %pi);
15 v_rms=sqrt(v_rms);
16 disp(sprintf("Average value of full wave rectifier
   sine wave is %f V", v_av));
17 disp(sprintf("Effective value of full wave rectifier
   sine wave is %f V", v_rms));
18
19 //END

```

Scilab code Exa 2.5 Fluorescent lamp

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 5
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 I1=0.75;                                // in Amperes

```

```

10 v=240; //in Volts
11 f=50; //in Hertz
12 p=80; //in Watts
13
14 //SOLUTION
15 res=p/v;
16 pf1=res/I1; //1st power factor =
    cos( 1 )
17 phi1=acos(pf1);
18 res1=tan(phi1); //result1 = tan( 1 )
19 w=2*pi*f;
20
21 //solution (a)
22 res2=0; //result2 = tan( 2 )
23 Ic1=res*(res1-res2);
24 c1=Ic1/(v*w);
25 disp(sprintf("(a) When power factor is unity , the
    value of capacitance is %f F ",c1*(10^6)));
26
27 //solution (b)
28 pf2=0.95; //given
29 phi2=acos(pf2);
30 res2=tan(phi2);
31 Ic2=res*(res1-res2);
32 c2=Ic2/(v*w);
33 disp(sprintf("(b) When power factor is 0.95(lagging)
    , the value of capacitance is %f F ",c2*(10^6)))
    ;
34
35 //END

```

Scilab code Exa 2.6 Single phase motor

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT

```

```

2 //Example 6
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 f=50;                                //in Hertz
10 I1=20;                                 //in Amperes
11 pf1=0.75;                             //power factor
12 v=230;                                 //in Volts
13 pf2=0.9;                               //power factor(
    lagging)
14
15 //SOLUTION
16 phi1=acos(pf1);
17 res1=tan(phi1);                      //result1 = tan( 1
    )
18 phi2=acos(pf2);
19 res2=tan(phi2);                      //result2 = tan( 2
    )
20 Ic=I1*pf1*(res1-res2);
21 w=2*pi*f;
22 c=Ic/(v*w);
23 disp(sprintf("The value of capacitance is %f F ",c
    *(10^6)));
24 Qc=v*Ic;
25 disp(sprintf("The reactive power is %f kVAR",Qc
    /(10^3)));
26 I2=I1*(pf1/pf2);
27 disp(sprintf("The new supply current is %f A",I2));
28
29 //END

```

Scilab code Exa 2.7 Apparent power of 300 kVA

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
. C. CIRCUIT
2 //Example 7
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 s1=300; // apparent power in
           kVA
10 pf1=0.65; // power factor(
               lagging)
11 pf2=0.85; // power factor(
               lagging)
12
13 //SOLUTION
14
15 // solution (a)
16 p=s1*pf1; // active power
17 q1=sqrt((s1^2)-(p^2));
18 disp(sprintf("(a) To bring the power factor to unity
               , the capacitor bank should have a capacity of %f
               kVAR",q1));
19
20 //solution (b)
21 s2=p/pf2;
22 q2=sqrt((s2^2)-(p^2));
23 disp(sprintf("(b) To bring the power factor to 85%
               lagging , the capacitor bank should have a
               capacity of %f kVAR",q2));
24
25 //END

```

Scilab code Exa 2.8 Two element series circuit

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 8
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 v=300/sqrt(2);                                //in Volts
10 angle_v=110;                                  //in degrees
11 I=15/sqrt(2);                                //in Amperes
12 angle_I=80;                                   //in degrees
13
14 //SOLUTION
15 Z=v/I;
16 angle_Z=angle_v-angle_I;
17 disp(sprintf("The circuit impedance is %d ",Z));
18 disp(sprintf("The phase angle is %d degrees",angle_Z
));
19 p_av=v*I*cos(angle_Z*(pi/180)); //to convert
angle_z from degrees to radians
20 disp(sprintf("The average power drawn is %f W",p_av
));
21
22 //END

```

Scilab code Exa 2.9 120 V 100 W lamp

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 9
3
4 clc;
5 disp("CHAPTER 2");

```

```

6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 v1=120;                                // voltage of lamp in
   Volts
10 p=100;                                  //in Watts
11 v2=220;                                //supply voltage in
   Volts
12 f=50;                                   //in Hertz
13
14 //SOLUTION
15 v1=sqrt((v2^2)-(v1^2));
16 x1=(v1*v1)/p;
17 L=x1/(2*pi*f);
18 disp(sprintf("The pure inductance should have a
   value of %f H",L));
19
20 //END

```

Scilab code Exa 2.10 Current and power drawn

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 10
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 v=230;                                    // in Volts
10 z1=3+(%i*4);                            //impedance in
   rectangular form in Ohms
11 z2=6+(%i*8);                            //impedance in
   rectangular form in Ohms

```

```

12
13 //SOLUTION
14 function [z,angle]=rect2pol(x,y);
15 z=sqrt((x^2)+(y^2)); //z is impedance &
16 the resultant of x and y
17 angle=atan(y/x)*(180/%pi); //to convert the
18 angle from radians to degrees
19 endfunction;
20
21 [z1,angle1]=rect2pol(3,4);
22 [z2,angle2]=rect2pol(6,8);
23
24 z=(z1*z2)/(z1+z2);
25 I=v/z;
26 angle=-angle1; //as angle1=angle2
27 p=v*I*cos(angle*%pi/180); //to convert the
28 angle from degrees to radians
29 disp(sprintf("The power drawn from the source is %f
30 kW",p/1000));
31
32 //END

```

Scilab code Exa 2.11 To calculate parameters of coil and power factor

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
2 .C. CIRCUIT
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 11");
7
8 //VARIABLE INITIALIZATION
9 vdc=100; //DC voltage in Volts
10 vac=100; //AC voltage in Volts

```

```

11 f=50;                                //in Hertz
12 I1=10;                               //in Amperes
13 I2=5;                                //in Amperes
14
15 //SOLUTION
16 r=vdc/I1;
17 z=vac/I2;
18 xl=sqrt((z^2)-(r^2));
19 L=xl/(2*pi*f);
20 pf=r/z;
21 disp(sprintf("The inductance of the coil is %f H",L))
   );
22 disp(sprintf("The power factor of the coil is %f (%
   lagging)",pf));
23
24 //END

```

Scilab code Exa 2.13 Current in load in rectangular form

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 13
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 13");
7
8 //VARIABLE INITIALIZATION
9 z=1+(%i*1);                           //load impedance
   in rectangular form in Ohms
10 v=20*sqrt(2);                         //amplitude of
   rms value of voltage in Volts
11
12 //SOLUTION
13 function [zp,angle]=rect2pol(x,y); //function '

```

```

rect2pol()' converts impedance in rectangular
form to polar form
14 zp=sqrt((x^2)+(y^2)); //z= (x) + j(y)=
(1)+ j(1); 'zp' is in polar form
15 angle=atan(y/x)*(180/%pi); //to convert the
angle from radians to degrees
16 endfunction;
17
18 //solution (i)
19 [zp,angle]=rect2pol(1,1); //since x=1 and y
=1
20 v=v/sqrt(2);
21 angle_v=100; //v=(20/sqrt(2))*sin( t +100)
22 I=v/zp; //RMS value of
current
23 angle_I=angle_v-angle;
24 Im=I*sqrt(2);
25 disp(sprintf("(i) The current in load is i = %d sin(
t +%d) A",Im,angle_I));
26
27 //solution (ii)
28 p=(v/sqrt(2))*(I*sqrt(2))*cos(angle*(%pi/180));
29 disp(sprintf("(ii) The real power is %f W",p));
30
31 //solution (iii)
32 pa=(v/sqrt(2))*(I*sqrt(2));
33 disp(sprintf("(ii) The apparent power is %f VAR",pa));
34
35 //END

```

Scilab code Exa 2.14 To find frequency and current elements

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 14
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 14");
7
8 //VARIABLE INITIALIZATION
9 v=100;                                // amplitude of rms
    value of voltage in Volts
10 I=20;                                  // amplitude of rms
    value of current in Amperes
11
12 //SOLUTION
13
14 //solution(i)
15 w=314;                                 // angular frequency
    in radian/sec
16 f=w/(2*pi);                           // as w=2*(pi)*f
17 f=ceil(f);
18 disp(sprintf("(i) The frequency is %d Hz",f));
19
20 //solution (ii)
21 E=v/sqrt(2);                          // in degrees
22 angle_E=-45;
23 I=I/sqrt(2);                          // in degrees
24 angle_I=-90;
25 z=E/I;
26 angle=angle_E-angle_I;
27 disp(sprintf("(ii) The impedance is %d , %d
    degrees",z,angle));
28
29 function [x,y]=pol2rect(mag,angle1);
30 x=mag*cos(angle1*(pi/180));        //to convert the
    angle from degrees to radian
31 y=mag*sin(angle1*(pi/180));
32 endfunction;

```

```

33 [r,x]=pol2rect(z,angle);
34 L=x/(2*pi*f);
35 disp(sprintf(" The inductance is %f H",L));
36
37 //END

```

Scilab code Exa 2.15 Choke coil takes current of 2 Amperes

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 15
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 I=2;                                //in Amperes
10 angle_I=60;                          //in degrees
11 v1=200;                             //in Volts
12 f1=50;                              //in Hertz
13 v2=100;                             //in Volts
14 f2=25;                              //in Hertz
15
16 //SOLUTION
17
18 //solution (i): when supply is 200V and frequency is
     50 Hz
19 z1=v1/I;
20 disp(sprintf("(i) When the supply is 200V and
     frequency is 50 Hz:"));
21 disp(sprintf("The impedance is %d , %d degrees",z1
     ,angle_I));
22 function [x,y]=pol2rect(mag,angle); //function '
     pol2rect()' converts impedance in polar form to

```

```

    rectangular form
23 x=mag*cos(angle*(%pi/180));           //to convert
      the angle from degrees to radians
24 y=mag*sin(angle*(%pi/180));
25 endfunction;
26 [r,x1]=pol2rect(z1,angle_I);
27 disp(sprintf("The resistance is %d ",r));
28 L=x1/(2*pi*f1);
29 disp(sprintf("The inductance is %f H",L));
30
31 //solution (ii): when supply is 100V and frequency
      is 25 Hz
32 x2=2*pi*f2*L;
33 z2=sqrt((r^2)+(x2^2));
34 angle=atan(x2/r);
35 I1=v2/z2;
36 p=v2*I1*cos(-angle);
37 disp(sprintf("(ii) When supply is 100V and frequency
      is 25 Hz:"));
38 disp(sprintf("The power consumed is %f W",p));
39
40 //Answer may be slightly different due to precision
      of floating point numbers
41
42 //END

```

Scilab code Exa 2.16 Two coils of 5 ohm and 10 ohm connected in parallel

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 16
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 16");

```

```

7
8 //VARIABLE INITIALIZATION
9 r1=5;                                //in Ohms
10 r2=10;                               //in Ohms
11 L1=0.04;                             //in Henry
12 L2=0.05;                             //in Henry
13 v=200;                               //in Volts
14 f=50;                                //in Hertz
15
16 //SOLUTION
17
18 //solution (i)
19 x11=L1*(2*pi*f);
20 x12=L2*(2*pi*f);
21 z1=r1+(%i*x11);
22 z2=r2+(%i*x12);
23 function [z,angle]=rect2pol(x,y);    //function '
    rect2pol() ' converts impedance in rectangular
    form to polar form
24 z=sqrt((x^2)+(y^2));                  //z=(x) + j(y)
    where 'x' represents resistance and 'y'
    represents inductive reactance
25 angle=atan(y/x)*(180/%pi);           //to convert
    the angle from radians to degrees
26 endfunction;
27 [z1,angle1]=rect2pol(r1,x11);
28 [z2,angle2]=rect2pol(r2,x12);
29 Y1=1/z1;                                //admittance
30 Y2=1/z2;
31 function [x,y]=pol2rect(mag,angle);   //function '
    pol2rect() ' converts admittance in polar form to
    rectangular form
32 x=mag*cos(angle*(%pi/180));          //to convert
    the angle from degrees to radians
33 y=mag*sin(angle*(%pi/180));
34 endfunction;
35 [G1,B1]=pol2rect(Y1,angle1);
36 [G2,B2]=pol2rect(Y2,angle2);

```

```

37 disp(".....");
38 disp("SOLUTION (i)");
39 disp(sprintf("Conductance of 1st coil is %f S",G1));
40 disp(sprintf("Conductance of 2nd coil is %f S",G2));
41 disp(" ");
42 disp(sprintf("Susceptance of 1st coil is %f S",B1));
43 disp(sprintf("Susceptance of 2nd coil is %f S",B2));
44 disp(" ");
45 disp(sprintf("Admittance of 1st coil is %f S",Y1));
46 disp(sprintf("Admittance of 2nd coil is %f S",Y2));
47 disp(".....");
48
49 //solution (ii)
50 G=G1+G2;
51 B=B1+B2;
52 [Y,angle]=rect2pol(G,B);
53 I=v*Y;
54 pf=cos((angle)*(pi/180));
55 disp("SOLUTION (ii)");
56 disp(sprintf("Total current drawn by the circuit is
%f A, %f degrees",I,-angle));
57 disp(sprintf("Power factor of the circuit is %f (
lagging)",pf));
58 disp(".....");
59
60 //solution (iii)
61 p=v*I*pf;
62 disp("SOLUTION (iii)");
63 disp(sprintf("Power absorbed by the circuit is %f kW
",p/1000));
64 disp(".....");
65
66 //solution (iv)
67 z=v/I;
68 function [x,y]=pol2rect(mag,angle);
69 x=mag*cos(angle*(pi/180)); //to convert the
angle from degrees to radians
70 y=mag*sin(angle*(pi/180));

```

```

71 endfunction;
72 [r,x]=pol2rect(z,angle);
73 L=x/(2*pi*f);
74 disp("SOLUTION (iv)");
75 disp(sprintf("Resitance of single coil is %f ",r))
    ;
76 disp(sprintf("Inductance of single coil is %f H",L))
    ;
77 disp(".....");
78
79 //END

```

Scilab code Exa 2.17 AC voltage applied to series RC circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
      .C. CIRCUIT
2 //Example 17
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 17");
7
8 //VARIABLE INITIALIZATION
9 e=141.4;                                     // amplitude of
      e(t) in Volts
10 E=141.4/sqrt(2);                           //RMS value of
      e(t) in Volts
11 angle_E=0;                                    //in degrees
12 //i(t)=(14.14<0)+(7.07<120)
13 i1=14.14;                                     //in Amperes
14 angle_i1=0;                                    //in degrees
15 i2=7.07;                                      //in Amperes
16 angle_i2=120;                                 //in degrees
17
18 //SOLUTION

```

```

19 function [x,y]=pol2rect(mag,angle); //function
    pol2rect() converts current in polar form to
    rectangular form
20 x=mag*cos(angle*(%pi/180));           //to convert
    the angle from degrees to radians
21 y=mag*sin(angle*(%pi/180));
22 endfunction;
23 //the given current i(t) is composed of two currents
    i1(t) and i2(t)
24 //i1(t) and i2(t) are not mentioned in the book but
    are considered for the sake of convenience
25 [i1_x,i1_y]=pol2rect(i1,angle_i1); //i1(t)= 14.14
    sin(120t)
26 [i2_x,i2_y]=pol2rect(i2,angle_i2); //i2(t)=7.07
    cos(120t+30)
27 i=(i1_x+i2_x)+(%i*(i1_y+i2_y));
28 function [mag,angle]=rect2pol(x,y); //function
    rect2pol() converts current in rectangular form
    to polar form
29 mag=sqrt((x^2)+(y^2));
30 angle=atan(y/x)*(180/%pi);           //to convert
    the angle from radians to degrees
31 endfunction;
32 [I,angle_I]=rect2pol((i1_x+i2_x),(i1_y+i2_y));
33 I=I/sqrt(2);
34
35 //solution (i)
36 z=E/I;
37 angle_z=angle_E-angle_I;
38 [r,xc]=pol2rect(z,angle_z);
39 f=50;
40 c=1/(2*pi*f*(-xc));
41 disp(sprintf("(i) The value of resistance is %f ", r));
42 disp(sprintf("The value of capacitance is %f F ", c*10^6));
43
44 //solution (ii)

```

```

45 pf=cos(angle_z*(%pi/180));
46 disp(sprintf("( ii ) The power factor is %f ",pf));
47
48 //solution ( iii )
49 p=E*I*pf;
50 disp(sprintf("( iii ) The power absorbed by the source
      is %f W",p));
51
52 //END

```

Scilab code Exa 2.18 Non inductive resistance of 10 ohm

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
     .C. CIRCUIT
2 //Example 18
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 18");
7
8 //VARIABLE INITIALIZATION
9 r=10;                                //in Ohms
10 v=200;                               //in Volts
11 f=50;                                 //in Hertz
12 I=10;                                 //in Amperes
13 rc=2;                                 //resistance of
     coil in Ohms
14
15 //SOLUTION
16
17 //solution ( i )
18 z=v/I;
19 xl=sqrt((z^2)-((r+rc)^2));
20 L=xl/(2*%pi*f);
21 disp(sprintf("( i ) The inductance of the coil is %f H

```

```

" ,L));
22
23 //solution ( ii )
24 pf=(r+rc)/z;
25 disp(sprintf("( ii ) The power factor is %f",pf));
26
27 //solution ( iii )
28 v1=I*(rc+(%i*x1));
29 function [mag,angle]=rect2pol(x,y); //function
    rect2pol() converts voltage in rectangular form
    to polar form
30 mag=sqrt((x^2)+(y^2));
31 angle=atan(y/x)*(180/%pi); //to convert the
    angle from radians to degrees
32 endfunction;
33 [v1,angle_v1]=rect2pol(real(v1),imag(v1));
34 disp(sprintf("( iii ) The voltage across the coil is
    %f V, %f degrees",v1,angle_v1));
35
36 //END

```

Scilab code Exa 2.19 Admittance in each parallel branch

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 19
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 19");
7
8 //VARIABLE INITIALIZATION
9 z1=4+(%i*3); //impedance in
    rectangular form in Ohms
10 z2=6-(%i*8); //impedance in

```

```

    rectangular form in Ohms
11 z3=1.6+(%i*7.2);                                //impedance in
    rectangular form in Ohms
12 v=100                                              //in volts
13 //SOLUTION
14
15 //SOLUTION ( i )
16
17 //Y1 and Y2 are admittances of each parallel branch
18 Y1=1/z1;
19 Y2=1/z2;
20 disp("SOLUTION ( i )");
21 disp(sprintf("Admittance parallel branch 1 is %3f
%3fj S", real(Y1), imag(Y1)));
22 disp(sprintf("Admittance parallel branch 2 is %3f+
%3fj S", real(Y2), imag(Y2)));
23 disp(" ");
24
25 //SOLUTION ( ii )
26
27 z=z3+(z2*z1)/(z1+z2)                                //series and
    parallel combination of impedances
28 disp("SOLUTION ( ii )");
29 disp(sprintf("Total circuit impedance is %3f %3fj S"
, real(z), imag(z)));
30 //solution given in the book is wrong as j
    (7.2+0.798) cannot be equal to j11.598
31
32 //SOLUTION ( iii )
33
34 I=v/z;
35 function [Z,angle]=rect2pol(x,y); //function '
    rect2pol()' converts impedance in rectangular
    form to polar form
36 Z=sqrt((x^2)+(y^2));                                //z is impedance &
    the resultant of x and y
37 angle=atan(y/x)*(180/%pi);                          //to convert the
    angle from radians to degrees

```

```

38 endfunction;
39 [Z, angle]=rect2pol(real(I), imag(I));
40 //disp(sprintf("%f, %f",z,angle));
41 //disp(sprintf("%f, %f",real(I), imag(I)));
42 pf=cos(angle*%pi/180);
43 disp("SOLUTION (iii)");
44 disp(sprintf("The power factor is %f",pf));
45
46 //SOLUTION (iv)
47
48 P=v*real(I)*pf; //power supplied
    by source is either (VI cos ) or (I^2 . R)
49 disp("SOLUTION (iv)");
50 disp(sprintf("The power supplied by source is %f
    watt",P));
51 //END

```

Scilab code Exa 2.20 Resonant frequency and band width

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 20 // read it as example 19 in the book on
    page 2.72
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 20");
7
8 //VARIABLE INITIALIZATION
9 L=0.5 //in Henry
10 C=5 //in mf, multiply by
    10^-6 to convert to f
11 R=25 //in ohms
12 //SOLUTION
13

```

```

14 //solution (i)
15 //Resonance frequency f = (1/2) sqrt ((1/LC)-R^2/L
16 ^2)
17 fr=(1/(2*pi))*sqrt((1/(L*C*10^-6))-(R^2)/(L^2));
18 disp("SOLUTION ( i )");
19 disp(sprintf("For parallel circuit , Resonant frquency
20 is %3f Hz", fr));
21 disp(" ");
22 //solution ( ii )
23 //Total circuit impedance at resonance is Z=L/RC
24 z=L/(R*C*10^-6);
25 disp("SOLUTION ( ii )");
26 disp(sprintf("Total impedance at resonance is %3f
27 k ", z/1000));
28 //
29 //solution ( iii )
30 //Bandwidth (f2-f1)=R/(2. .L)
31 bw=R/(2*pi*L);
32 disp("SOLUTION ( iii )");
33 disp(sprintf("Bandwidth is %3f Hz", bw));
34 //
35 //solution ( iv )
36 //Quality factor Q=1/R. sqrt (L/C)
37 Q=(1/R)*sqrt(L/(C*10^-6));
38 disp("SOLUTION ( iv )");
39 disp(sprintf("Quality Factor is %3f", Q));
40 //solution in the book is wrong as there is a total
41 //mistake in imaginary part 7.2+0.798=11.598
42 //
43 //END

```

Scilab code Exa 2.22 Series RLC circuit

```
1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
```

```

.C. CIRCUIT
2 //Example 22 (mentioned as 'example 21' in the book)
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 22");
7
8 //VARIABLE INITIALIZATION
9 L=0.1                                //in Henry
10 C=8*10^-6                             //in Farad
11 R=10                                  //in Ohms
12 //SOLUTION
13
14 //solution (i)
15 fr=1/(2*pi*sqrt(L*C));                //resonant frequency
16 disp("SOLUTION (i)");
17 disp(sprintf("For series circuit , resonant frquency
           is %3f Hz", fr));
18 disp(" ");
19
20 //solution (ii)
21 w=2*pi*fr;
22 Q=w*L/R;
23 disp("SOLUTION (ii)");
24 disp(sprintf("The Q-factor at resonance is %3f k ", Q));
25
26 //solution (iii)
27 bw=R/(2*pi*L);
28 f1=fr+bw/2;
29 disp("SOLUTION (iii)");
30 disp(sprintf("Half power frequencies are %3f Hz and
           %3f Hz", f1, fr));
31
32 //END

```

Scilab code Exa 2.23 An alternating current of frequency of 50 Hertz

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 22 (mentioned as 'example 22' in the book)
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 23");
7
8 //VARIABLE INITIALIZATION
9 A=100                         //amplitude in
                                  Amperes
10 f=50                           //frequency in Hz
11 t1=1/600                        //time in seconds
                                  after wave becomes zero again
12 a1=86.6                         //amplitude in
                                  Amperes at some time 't' after start
13
14 //SOLUTION
15
16 //solution (a)
17 //Amplitude at 1/600 second after it becomes zero
18 w=f*2*pi;                      //angular speed
19 hp=1/(2*f);                   //half period , the
                                  point where sine becomes zero again after origin
20 t=hp+t1;
21 a2=A*sin(w*t);
22 disp("SOLUTION (a)");
23 disp(sprintf("Amplitude after 1/600 sec is %3f A",
               a2));
24 disp(" ");
25 //solution (b)
26 //since A=A0.sinwt , t=asin(A/A0)/w
```

```

27 t2=(asin(a1/A))/w;
28 disp("SOLUTION (b)");
29 disp(sprintf("The time at which amp would be %f is
    %3f sec", a1, t2));
30
31 //END

```

Scilab code Exa 2.24 RMS value average value and form factor

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 22 // read it as example 23 in the book on
   page 2.77
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 24");
7
8 //VARIABLE INITIALIZATION
9 V=200                         // Amplitude in Volts
10 w=314                           // angular spped
11 R=20                            // in ohms
12 //SOLUTION
13
14 //solution
15 //comparing with standard equation
16 Im=V/R;                         // in Amps
17 rms=Im/2;
18 Iav=Im/%pi;                     // average current
19 ff=rms/Iav;
20 disp("SOLUTION");
21 disp(sprintf("RMS value of current is %3f A", rms))
   ;
22 disp(sprintf("Average value of current is %3f A",
   Iav));

```

```

23 disp(sprintf("Form Factor of current is %3f A", ff)
   );
24 disp("");
25
26 //END

```

Scilab code Exa 2.25 50 Hz sinusoidal voltage wave shape

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 25 // read it as example 24 in the book on
page 2.78
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 25");
7
8 //VARIABLE INITIALIZATION
9 V=350                                //Amplitude in Volts
10 f=50                                   //frequency in Hz
11 t1=0.005                               //sec after wave
   becomes zero again
12 t2=0.008                               //sec after waves
   passes through 0 in -ve direction
13 //SOLUTION
14 //e=Esinwt
15 //solution (a)
16 //RAmplitude at 1/600 second after it becomes zero
17 w=f*2*pi;                             //angular speed
18 v1=V*sin(w*t1);
19 disp("SOLUTION (a)");
20 disp(sprintf("Voltage after %f sec is %3f A", t1, v1
));
21 disp("");
22 //solution (b)

```

```

23 // since wave will pass in -ve direction after half
   period
24 hp=1/(2*f);                                // half period , the
   point where sine becomes zero again after origin
25 t=hp+t2;
26 v2=V*sin(w*t);
27 disp("SOLUTION (b)");
28 disp(sprintf("The voltage would be %f V %3f sec",
   v2,t));
29 //
30 //END

```

Scilab code Exa 2.26 Sinusoidal alternating current of frequency 25 Hz

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 26 // read it as example 25 in the book on
   page 2.79
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 26");
7
8 //VARIABLE INITIALIZATION
9 A=100                                         // Amplitude in Amps
10 f=25                                           // frquency in Hz
11 a1=20                                         // svalue in Amps to
   be achieved in certain time
12 a2=100                                         //in Amps
13
14 //SOLUTION
15 //i=Isinwt
16 //solution (a)
17 //RAmplitude at 1/600 second after it becomes zero
18 w=f*2*pi;                                     //angular speed

```

```

19 t1=(asin(a1/A))/w;
20 disp("SOLUTION (a)");
21 disp(sprintf("The time to reach value %f A is %3f
sec", a1,t1));
22 disp("");
23 //solution (b)
24 //since wave will pass in -ve direction after half
period
25 t2=(asin(a2/A))/w;
26 disp("SOLUTION (a)");
27 disp(sprintf("The time to reach value %f A is %3f
sec", a2,t2));
28 disp("");
29 //
30 //END

```

Scilab code Exa 2.27 Impedance resistance reactance and power factor of the circuit

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 27 // read it as example 26 in the book on
page 2.79
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 27");
7
8 //VARIABLE INITIALIZATION
9 V=250; //Amplitude in
          Volts
10 w=314; //angular spped
11 p= -10; //phase angle in
          degrees
12 I=10; //Amplitude in Amps
13 pi=50 //phase angle in

```

```

    degrees
14
15 //SOLUTION
16 //v=Vsin(wt+pv)
17 //i=Isin(wt+pi)
18 //solution
19 //representing V in polar format as V=V0/sqrt(2) <
   , we get
20 v1=V/sqrt(2);
21 i1=I/sqrt(2);
22 //converting polar to rect
23 function [x,y]=pol2rect(mag,angle);
24 x=mag*cos(angle*pi/180);           // angle convert in
   radians
25 y=mag*sin(angle*pi/180);
26 endfunction;
27 [x,y]=pol2rect(v1,pv);
28 V=x+y*i;
29 [x,y]=pol2rect(i1,pi);
30 I=x+y*i;
31 Z=V/I;
32 //convert back into angles in deg
33 function [mag,angle]=rect2pol(x,y);
34 mag=sqrt((x^2)+(y^2));           //z is impedance &
   the resultant of x and y
35 angle=atan(y/x)*(180/pi);       //to convert the
   angle from radians to degrees
36 endfunction;
37 [mag,angle]=rect2pol(real(Z),imag(Z));
38 disp("SOLUTION (a)");
39 disp(sprintf("The impedance is %f < %3f Deg", mag
   ,angle));
40 //disp("");
41 //power factor=cos(angle)
42 pf=cos(-1*angle*pi/180);         //convert to radians
   and change sign
43 disp(sprintf("The power factor is %f", pf));
44 //Z=R-jXc by comparing real and imag parts we get

```

```

45 disp(sprintf("The resistance is %f and Reactance
    is %3f ", real(Z), imag(Z)));
46 disp("");
47 //
48 //END

```

Scilab code Exa 2.28 Total impedance current drawn from the supply

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 28 // read it as example 27 in the book on
page 2.80
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 28");
7
8 //VARIABLE INITIALIZATION
9 z1=2+(%i*3);                                //impedance in
    rectangular form in Ohms
10 z2=1-(%i*5);                                //impedance in
    rectangular form in Ohms
11 z3=4+(%i*2);                                //impedance in
    rectangular form in Ohms
12 v=10;                                         //in volts
13 //SOLUTION
14
15 //solution (a)
16 //Total impedance
17 //Total circuit impedance Z=(Z1 || Z2)+Z3
18 z=z1+(z2*z3)/(z2+z3);
19 disp("SOLUTION ( i )");
20 disp(sprintf("Total circuit impedance is %3f %3fj S"
    , real(z), imag(z)));
21 //Total supply current I=V/Z

```

```

22 //solution (b)
23 i=v/z;
24 function [mag ,angle]=rect2pol(x,y);
25 mag=sqrt((x^2)+(y^2));           //z is impedance &
26 the resultant of x and y
27 angle=atan(y/x)*(180/%pi);      //to convert the
28 angle from radians to degrees
29 endfunction;
30 [mag , angle]=rect2pol(real(i) , imag(i));
31 disp("SOLUTION (b)");
32 disp(sprintf("Total current is %f<%f Amp",mag ,angle));
33 //solution (c)
34 //Vbc=I . Zbc where Zbc=(z2*z3)/(z2+z3)
35 Vbc=i*((z2*z3)/(z2+z3));
36 [mag1 , angle1]=rect2pol(real(Vbc) , imag(Vbc));
37 disp("SOLUTION (c)");
38 disp(sprintf("The voltage across the || circuit is
39 %f<%f",mag1 , angle1));
40 disp(sprintf("The voltage Vbc lags circuit by %f Deg
41 ",angle-angle1));
42 //solution (d)
43 //i2=Vbc/z2 , i3=Vbc/z3
44 i2=Vbc/z2;
45 i3=Vbc/z3;
46 [mag2 , angle2]=rect2pol(real(i2) , imag(i2));
47 [mag3 , angle3]=rect2pol(real(i3) , imag(i3));
48 disp(sprintf("The current across fist branch of ||
49 circuit is %f<%f",mag2 , angle2));
50 disp(sprintf("The current across second branch of ||
51 circuit is %f<%f",mag3 , angle3));
52 //solution (e)
53 pf=cos(-1*angle*%pi/180);
54 disp("SOLUTION (e)");
55 disp(sprintf("The power factor is %f",pf));
56 //solution (iv)
57 //Apparent power s=VI, True Power , tp I^2R, Reactive
58 Power , rp=I^2X or VISSin(angle)

```

```

52 s=v*mag;
53 tp=mag*mag*real(z);
54 rp=v*mag*sin(-1*angle*pi/180);
55 disp("SOLUTION ( f )");
56 disp(sprintf("The Apparent power is %f VA, True
      power is %f W , Reactive power is %f vars",s,tp,
      rp));
57 disp(" ");
58 //END

```

Scilab code Exa 2.29 An alternating current of frequency of 60 Hertz

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
     .C. CIRCUIT
2 //Example 29 // read it as example 28 in the book on
     page 2.83
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 29");
7
8 //VARIABLE INITIALIZATION
9 I=120;                                // Amplitude in Amps
10 f=60;                                  //Hz
11 t1=1/360;                             //in sec time to
     find amplitude
12 i2=96;                                // in Amps ,2 to
     find time taken to reach this
13 //SOLUTION
14 //i=Isin(wt)
15 //solution (a)
16 w=2*pi*f;
17 i=I*sin(w*t1);
18 disp("SOLUTION ( a )");
19 disp(sprintf("The amplitude at time %f sec is %f Amp

```

```

    " , t1,i));
20 //solution (b)
21 t2=(asin(i2/I))/w;
22 disp("SOLUTION (b)");
23 disp(sprintf("The time taken to reach %f Amp is %f
    Sec", i2,t2));
24 disp("");
25 //
26 //END

```

Scilab code Exa 2.30 An alternating current with RMS value of 20 A

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 30 // read it as example 29 in the book on
     page 2.83
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 30");
7
8 //VARIABLE INITIALIZATION
9 f=50;                                //Hz
10 rms=20;                               //in Amp
11 t1=0.0025;                            //in sec time to
     find amplitude
12 t2=0.0125;                            //in sec , to
     find amp after passing through +ve maximum
13 i3=14.14;                             //in Amps, to
     find time when will it occur after passing
     through +ve maxima
14 //SOLUTION
15 //i=Isin(wt)
16 //solution (a)
17 w=2*pi*f;

```

```

18 Im=rms*sqrt(2);
19 disp(sprintf("The equation would be i=%f. sin(%f.t)"
    , Im,w));
20 t0=(asin(1)/w);                                //time to reach
    maxima in +ve direction
21 i=Im*sin(w*t1);
22 disp("SOLUTION (a)");
23 disp(sprintf("The amplitude at time %f sec is %f Amp"
    , t1,i));
24 //solution (b)
25 tx=t0+t2;
26 i2=Im*sin(w*tx);
27 disp("SOLUTION (b)");
28 disp(sprintf("The amplitude at time %f sec is %f Amp"
    , t2,i2));
29 //solution (c)
30 ty=(asin(i3/Im))/w;
31 t3=t0-ty;                                     //since ty is
    the time starting from 0, the origin needs to be
    shifted to maxima
32 disp("SOLUTION (c)");
33 disp(sprintf("The amplitude of %f Amp would be
    reached in %f Sec", i3,t3));
34 disp("");
35 //
36 //END

```

Scilab code Exa 2.31 Significance of RMS and average values of wave

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 31 // read it as example 30 in the book on
page 2.84
3
4 clc;

```

```

5 disp("CHAPTER 2");
6 disp("EXAMPLE 31");
7
8 //VARIABLE INITIALIZATION
9 //function of the waveform is deduced to be y=10+10.
10 //SOLUTION
11 //Yav=(1/T).Integral(ydt) from 0 to T
12 //say
13 T=1;                                     // 1 sec
14 Yav=(1/T)*integrate('(10+10*t/T)', 't', 0, 1);
15 disp(sprintf("The average value of waveform is %f",
16 Yav));
16 //RMS value Yrms=(1/T).Integral(y^2.dt) from 0 to T
17 Yms=(1/T)*integrate('(10+10*t/T)^2', 't', 0, 1);
18 disp(sprintf("The RMS value of waveform is %f",
19 sqrt(Yms)));
20 disp("");
21 //
22 //END

```

Scilab code Exa 2.32 Average value effective value and form factor

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 32 // read it as example 31 in the book on
 page 2.85
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 32");
7
8 //VARIABLE INITIALIZATION
9 //function of the waveform is deduced to be i=Im.
 sin

```

```

10 //SOLUTION
11 //Iav=(1/2. ) . Integral( yd ) from 0 to , and
12 //      to 2. is zero , interval is 2.
12 //
13 //say
14 Im=1;                                // in Amp
15 Iav=(1/(2*pi))*integrate('((Im*sin(th))', 'th', 0,
16 %pi);
16 //disp(sprintf("The average value of waveform is %f
17 //      ", Iav));
17 //RMS mean square value (1/ ). Integral(y^2. d )
18 //from 0 to
18 Ims=(1/(2*pi))*integrate('((Im*sin(th))^2', 'th', 0,
19 %pi);
19 //disp(sprintf("The RMS value of waveform is %f",
20 //      sqrt(Ims)));
20 ff=sqrt(Ims)/Iav;
21 disp(sprintf("The form factor of waveform is %f", ff)
22 );
22 disp("");
23 //
24 //END

```

Scilab code Exa 2.33 Three coils of resistances

```

1 //CHAPTER 2— STEADY-STATE ANALYSIS OF SINGLE-PHASE A
2 .C. CIRCUIT
2 //Example 33 // read it as example 32 in the book on
3 // page 2.86
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 33");
7
8 //VARIABLE INITIALIZATION

```

```

9 r1=20; //in
10 r2=30;
11 r3=40;
12 l1=0.5; //in Henry
13 l2=0.3;
14 l3=0.2;
15 V=230; //volts
16 f=50; //Hz
17 //coils connected in series
18 //
19 //SOLUTION
20 R=r1+r2+r3;
21 L=l1+l2+l3;
22 XL=2*pi*f*L;
23 //impedence Z=sqrt(R^2 +XL^2)
24 Z=sqrt(R^2 +XL^2);
25 I=V/Z;
26 pf=R/Z;
27 pc=V*I*pf;
28 disp(sprintf("The total current is %f Amp", I));
29 disp(sprintf("The Power Factor is %f lagging", pf))
;
30 disp(sprintf("The Power consumed in the circuit is
%f W", pc));
31 disp("");
32 //
33 //END

```

Scilab code Exa 2.34 To draw the vector diagram

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
.C. CIRCUIT
2 //Example 34 // read it as example 33 in the book on
page 2.87
3

```

```

4  clc;
5  disp("CHAPTER 2");
6  disp("EXAMPLE 34");
7
8 //VARIABLE INITIALIZATION
9 r=100;                                //in
10 c=40*10^(-6);                         //
11 V=400;                                 // volts
12 f=50;                                  //Hz
13 //
14 //SOLUTION
15 XC=1/(2*pi*f*c);
16 //impedance Z=sqrt(R^2 +XL^2)
17 Z=sqrt(r^2 +XC^2);
18 I=V/Z;
19 pf=r/Z;
20 pc=V*I*pf;
21 disp(sprintf("The total current is %f Amp", I));
22 disp(sprintf("The Power Factor is %f leading", pf))
;
23 disp(sprintf("The Power consumed in the circuit is
    %f W", pc));
24 disp("");
25 //
26 //END

```

Scilab code Exa 2.35 Total impedance and total current

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 35 // read it as example 34 in the book on
     page 2.88
3
4 clc;
5 disp("CHAPTER 2");

```

```

6 disp("EXAMPLE 35");
7
8 //VARIABLE INITIALIZATION
9 R=100; //in
10 L=0.2; //in Henry
11 C=20*10^(-6); //farads
12 V=240; // volts
13 f=50; //Hz
14 //
15 //SOLUTION
16 //Solution (a)
17 XL=2*pi*f*L;
18 XC=1/(2*pi*f*C);
19 //impedence Z=sqrt(R^2 +XL^2)
20 X=XL-XC;
21 Z=sqrt(R^2 +X^2);
22 disp("SOLUTION (a)");
23 disp(sprintf("The total impedance is %f ", z));
24 I=V/Z;
25 disp("SOLUTION (b)");
26 disp(sprintf("The total current is %f Amp", I));
27 Vr=I*R;
28 Vi=I*XL;
29 Vc=I*XC;
30 disp("SOLUTION (c)");
31 disp(sprintf("The voltage across resistance is %f V"
    ,Vr));
32 disp(sprintf("The voltage across inductance is %f V"
    ,Vi));
33 disp(sprintf("The voltage across capacitance is %f V"
    ,Vc));
34 pf=R/Z;
35 pc=V*I*pf;
36 disp("SOLUTION (d)");
37 disp(sprintf("The Power Factor is %f leading", pf))
    ;
38 disp("SOLUTION (e)");
39 disp(sprintf("The Power consumed in the circuit is

```

```

        %f W' ,pc));
40 //XL=XC
41 f0=1/(2*pi*sqrt(L*C));
42 disp("SOLUTION ( f )");
43 disp(sprintf("Resonance will occur at %f Hz",f0));
44 disp(" ");
45 //
46 //END

```

Scilab code Exa 2.36 Total current taken from supply

```

1 //CHAPTER 2— STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 36 // read it as example 35 in the book on
page 2.90
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 36");
7
8 //VARIABLE INITIALIZATION
9 R1=10;                                //in
10 XL=15;                                 //in
11 R2=12;                                 //
12 C=20;                                  //capacitative
13 V=230;                                 // volts
14 f=50;                                   //Hz
15 //
16 //SOLUTION
17 //Solution (a)
18 //conductance g, susceptance b
19 Z12=(R1^2 +XL^2);                     //squared impedance
20 Z^2 for branch 1
21 Z22=(R1^2 +C^2);                      //squared impedance

```

```

        Z^2 for branch 2
21 g1=R1/Z12;
22 g2=R2/Z22;
23 b1=-XL/Z12;
24 b2=C/Z22;
25 g=g1+g2;
26 b=b1+b2;
27 Y=sqrt(g^2+b^2);
28 I=V*Y;
29 disp("SOLUTION (a)");
30 disp(sprintf("The total current is %f Amp", I));
31 pf=g/Y;
32
33 disp("SOLUTION (b)");
34 disp(sprintf("The power factor is %f", pf));
35 disp("");
36 //
37 //END

```

Scilab code Exa 2.37 Current taken by each branch

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 37 // read it as example 36 in the book on
     page 2.93
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 37");
7
8 //VARIABLE INITIALIZATION
9 R1=20;                                //
10 XL=15;                                // in ohms
11 R2=0;                                  // assumed
12 C=50;                                  // in ohms

```

```

        capacitative reactance
13 V=200;
14 f=60;                                //Hz
15 //
16 //SOLUTION
17 //Solution (a)
18 //conductance g, susceptance b
19 Z1=sqrt(R1^2 +XL^2);                  //squared
    impedance Z^2 for branch 1
20 Z2=sqrt(R2^2 +C^2);                  //squared
    impedance Z^2 for branch 2
21 i1=V/Z1;
22 i2=V/Z2;
23 disp("SOLUTION (a)");
24 disp(sprintf("The current in Branch 1 is %f Amp", i1));
25 disp(sprintf("The current in Branch 2 is %f Amp", i2));
26 phi1=atan(XL/R1);
27 phi2=%pi/2;                           //atan(C/R2);
                                         //R2=0, output is infinity
28 Icos=i1*cos(phi1)+i2*cos(phi2);      // phi in
    radians
29 Isin=-i1*sin(phi1)+i2*sin(phi2);     // phi in
    radians
30 I=sqrt(Icos^2+Isin^2);
31 //
32 disp("SOLUTION (b)");
33 disp(sprintf("The total current is %f Amp", I));
34 //
35 pf=Icos/I;
36 disp("SOLUTION (c)");
37 disp(sprintf("The power factor is %f ", pf));
38 disp(" ");
39 //
40 //END

```

Scilab code Exa 2.38 To solve example 27 by j method

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 38 // read it as example 37 in the book on
page 2.93
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 38");
7
8 //VARIABLE INITIALIZATION
9 z1=10+15*i;
10 z2=12-20*i;
11 V=230;
12 //invZ=1/z1+1/z2 ;
13 Z=z1*z2/(z1+z2);
14 magZ=sqrt(real(Z)^2+imag(Z)^2);
15 I=V/magZ;
16 pf=real(Z)/magZ;
17 disp("SOLUTION (a)");
18 disp(sprintf("The current is %f Amp", I));
19 //
20 disp("SOLUTION (b)");
21 disp(sprintf("The Power factor is %f", pf));
22 disp(" ");
23 //
24 //END
```

Scilab code Exa 2.39 To draw the complete vector diagram

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 39 // read it as example 38 in the book on
    page 2.94
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 39");
7
8 //VARIABLE INITIALIZATION
9 z1=2.5+1.5*i;
10 z2=4+3*i;
11 z3=3-4*i;
12 V=200;
13 f=50;
14 E=V+0*i;                                // representing
    as a vector
15 //invZ=1/z1+1/z2;
16 Z23=z2*z3/(z2+z3);
17 Z=z1+Z23;
18 I=E/Z;
19 magI=sqrt(real(I)^2+imag(I)^2);          //total current
20 phi=atan(-imag(I)/real(I));                //total phase
21 //
22 //Voltages across the branches
23 e12=I*z1;                                 //voltage across
    series branch
24 mage12=sqrt(real(e12)^2+imag(e12)^2);
25 phi12=atan(imag(e12)/real(e12));
26 //
27 e23=E-e12;                                //voltage across
    parallel branch
28 mage23=sqrt(real(e23)^2+imag(e23)^2);
29 phi23=atan(-imag(e23)/real(e23));
30 //
31 //current in branch 1 upper
32 i1=e23/z2;
33 magi1=sqrt(real(i1)^2+imag(i1)^2);

```

```

34 phii1=atan(-imag(i1)/real(i1));
35 //
36 //current in branch 2 lower
37 i2=e23/z3;
38 magi2=sqrt(real(i2)^2+imag(i2)^2);
39 phii2=atan(imag(i2)/real(i2));
40 disp("SOLUTION (b)");
41 disp(sprintf("The current in Upper branch is %f
Amp",magI1));
42 disp(sprintf("The current in Lower branch is %f
Amp",magI2));
43 disp(sprintf("The Total current is %f Amp",magI));
44 ;
45 //
46 pf=cos(phi); //%
47 disp("SOLUTION (c)");
48 disp(sprintf("The Power factor is %f", pf));
49 //
50 disp("SOLUTION (d)");
51 disp(sprintf("The voltage across series branch is
%f V", mage12));
52 disp(sprintf("The voltage across parallel branch is
%f V", mage23));
53 //
54 tp=V*magI*pf;
55 disp("SOLUTION (e)");
56 disp(sprintf("The total power absorbed in circuit
is %f W", tp));
57 //
58 //END

```

Scilab code Exa 2.40 Power factor and average power delivered to the circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 40 // read it as example 39 in the book on
page 2.98
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 40");
7
8 //VARIABLE INITIALIZATION
9 V=100; // max amplitude
10 w=314; //angular speed
11 phiV=5; //phase angle
12 in degrees
13 I=5; //max current
14 amplitude
15 phiI=-40; //phase angle in
current in deg
16
17 //SOLUTION
18 phi=phiI-phiV;
19 pf=cos(phi*pi/180); //convert to
radians
20 p=(V/sqrt(2))*(I/sqrt(2))*pf;
21 //disp(sprintf("The Power factor is %f lagging", pf));
22 disp(sprintf("The Power delivered is %f W", p));
23 disp("");
24 //
25 //END

```

Scilab code Exa 2.41 100 V 60 W lamp

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 41 // read it as example 40 in the book on
    page 2.99
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 41");
7
8 //VARIABLE INITIALIZATION
9 lampV=100;                                //Volts
10 lampW=60;                                 //watts
11 V=250;
12 f=50;
13 //
14 //SOLUTION
15 lampI=lampW/lampV;
16 lampR=lampW/lampI^2;                      //W=I ^ 2.R
17 //
18 disp("SOLUTION (a)");
19 disp(sprintf("The resistance of the lamp is t is %f
    Ohms", lampR));
20 //
21 //in purely resistive / non inductive circuit ,V=IR
    applies , and R=lampR+R
22 R=V/lampI-lampR;
23 disp(sprintf("The value value of resistor to be
    placed in series with the lamp is %f Ohms", R));
24 //
25 //in case of inductance
26 //XL=2*pi*f*L;
27 //V=Z.I where Z^2=R^2+XL^2
28 //L=sqrt((V^2/I^2-R^2)/2*pi*f)
29 L=sqrt((V/lampI)^2-lampR^2)/(2*pi*f);
30 disp(sprintf("The inductive resistance to be placed
    is %f H", L));
31 disp("");
32 //

```

33 //END

Scilab code Exa 2.42 Three sinusoidally alternating currents

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 42 // read it as example 41 in the book on
 page 2.100
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 42");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                // max
   amplitude of wave in Amp
10 rms1=5;
11 rms2=7.5;
12 rms3=10;
13 phi1=30;
14 phi2=-60;
15 phi3=45;
16 f=50;                                 //Hz
17 w=2*pi*f;
18 //
19 //SOLUTION
20 av1=rms1/1.11;
21 av2=rms2/1.11;
22 av3=rms3/1.11;
23 disp("SOLUTION ( i )");
24 disp(sprintf("The average value of 1st current is
 %f Amp", av1));
25 disp(sprintf("The average value of 2nd current is
 %f Amp", av2));
26 disp(sprintf("The average value of 3rd current is
```

```

        %f Amp" , av3));
27 // 
28 disp("SOLUTION ( i i )");
29 disp(sprintf("The instantaneous value of 1st
    current is %f sin(%f*t+%f) Amp" , rms1*sqrt(2) , w ,
    phi1));
30 disp(sprintf("The instantaneous value of 2nd
    current is %f sin(%f*t%f) Amp" , rms2*sqrt(2) , w ,
    phi2));
31 disp(sprintf("The instantaneous value of 3rd
    current is %f sin(%f*t+%f) Amp" , rms3*sqrt(2) , w ,
    phi3));
32 // 
33 //instantaneous values of current at t=100msec=0.1
    sec
34 t=0.1;
35 i1=(rms1*sqrt(2))*(sin(w*t+phi1*pi/180));
36 i2=(rms2*sqrt(2))*(sin(w*t+phi2*pi/180));
37 i3=(rms3*sqrt(2))*(sin(w*t+phi3*pi/180));
38 disp("SOLUTION ( iv )");
39 disp(sprintf("The instantaneous value of 1st
    current is %f Amp at %f Sec" , i1 , t));
40 disp(sprintf("The instantaneous value of 2nd
    current is %f Amp at %f Sec" , i2 , t));
41 disp(sprintf("The instantaneous value of 3rd
    current is %f Amp at %f Sec" , i3 , t));
42 disp(" ");
43 // 
44 //END
```

Scilab code Exa 2.43 Resultant current wave made up of two components

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 43 // read it as example 42 in the book on
```

```

page 2.102
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 43");
7
8 //VARIABLE INITIALIZATION
9 I=5;                                // max amplitude
   of wave in Amp
10 f=50;                                 //Hz
11 //wave for is to be obtained by adding the two waves
12 //i=5+5.sin(wt)=5+5.sin(theta)
13 //
14 //SOLUTION
15 Iav=(1/(2*pi))*integrate('5+5*sin(theta)', 'theta', 0, 2*
   %pi);
16 ImS=(1/(2*pi))*integrate('(5+5*sin(theta))^2', 'theta',
   0, 2*pi);
17 //
18 disp(sprintf("The average value of resultant
   current is %f Amp", Iav));
19 disp(sprintf("The RMS value of resultant current is
   %f Amp", sqrt(ImS)));
20 disp("");
21 //
22 //END

```

Scilab code Exa 2.44 To find power consumed by the circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 44
3
4 clc;
5 disp("CHAPTER 2");

```

```

6 disp("EXAMPLE 44");
7
8 //VARIABLE INITIALIZATION
9 r=20; // in Ohms
10
11 //SOLUTION
12 p0=(4^2)*r;
13 p1=((5/sqrt(2))^2)*r;
14 p2=((3/sqrt(2))^2)*r;
15 p=p0+p1+p2;
16 I=sqrt(p/r);
17 disp(sprintf("The power consumed by the resistor is
    %d W",p));
18 disp(sprintf("The effective value of current is %f A
    ",I));
19
20 //END

```

Scilab code Exa 2.45 Quality factor and bandwidth

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 45
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 45");
7
8 //VARIABLE INITIALIZATION
9 L=1.405; //in Henry
10 r=40; //in Ohms
11 c=20/(10^6); //in Farad
12 v=100; //in Volts
13
14 //SOLUTION

```

```

15 f0=1/(2*pi*sqrt(L*c));
16 disp(sprintf("The frequency at which the circuit
    resonates is %d Hz",f0));
17
18 I0=v/r;
19 disp(sprintf("The current drawn from the supply is
    %f A",I0));
20
21 x10=2*pi*f0*L;
22 z0=sqrt((r^2)+(x10^2));
23 v10=I0*z0;
24 disp(sprintf("The voltage across the coil is %f V",
    v10));
25
26 xc0=1/(2*pi*f0*c);
27 disp(sprintf("The capacitative reactance is %f      ",
    xc0));
28
29 Q0=(2*pi*f0*L)/r;
30 disp(sprintf("The quality factor is %f", Q0));
31
32 bw=r/L;
33 disp(sprintf("The bandwidth is %f Hz", bw));
34
35 //END

```

Scilab code Exa 2.46 To find power consumed and reactive power

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 46
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 46");

```

```

7
8 //VARIABLE INITIALIZATION
9 I=120-(%i*(50));                                //in Amperes
10 v=8+(%i*(2));                                  //in Volts
11
12 //SOLUTION
13
14 //function to convert from rectangular form to polar
   form
15 function [mag,angle]=rect2pol(x,y);
16 mag=sqrt((x^2)+(y^2));
17 angle=atan(y/x)*(180/%pi);          //to convert the
   angle from radians to degrees
18 endfunction;
19 [v,angle_v]=rect2pol(real(v),imag(v));
20 [I,angle_I]=rect2pol(real(I),imag(I));
21
22 //solution (i)
23 z=v/I;
24 angle_z=angle_v-angle_I;
25 disp(sprintf("(i) The impedance is %f , %f degrees
   ",z,angle_z));
26
27 //solution (ii)
28 phi=angle_z;
29 pf=cos(phi* (%pi/180));
30 disp(sprintf("(ii) The power factor is %f (lagging)"
   ,pf));
31
32 //solution (iii)
33 s=v*I;
34 angle_s=angle_v-angle_I;
35 //function to convert from polar form to rectangular
   form
36 function [x,y]=pol2rect(mag,angle);
37 x=mag*cos(angle* (%pi/180));    //to convert the angle
   from degrees to radians
38 y=mag*sin(angle* (%pi/180));

```

```

39 endfunction;
40 [p,q]=pol2rect(s,angle_s);
41 disp(sprintf("(iii) The power consumed is %f W",p));
42 disp(sprintf("          The reactive power is %f VAR",q)
   );
43
44 //END

```

Scilab code Exa 2.47 RL series circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 47
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 47");
7
8 //VARIABLE INITIALIZATION
9 r=10;                                // in Ohms
10 xl=8.66;                             // in Ohms
11 I=5-(%i*10);                          // in Amperes
12
13 //SOLUTION
14 z=r+(%i*(xl));
15 // function to convert from rectangular form to polar
   form
16 function [mag,angle]=rect2pol(x,y);
17 mag=sqrt((x^2)+(y^2));
18 angle=atan(y/x)*(180/%pi);           //to convert the
   angle from radians to degrees
19 endfunction;
20 [z,angle_z]=rect2pol(real(z),imag(z));
21 [I,angle_I]=rect2pol(real(I),imag(I));
22

```

```

23 //solution (i)
24 v=I*z;
25 angle_v=angle_I+angle_z;
26 disp(sprintf("(i) The applied voltage is %f V, %f
degrees",v,angle_v));
27
28 //solution (ii)
29 phi=angle_I-angle_v;
30 pf=cos(phi*(%pi/180));
31 disp(sprintf("(ii) The power factor is %f (lagging)"
,pf));
32
33 //solution (iii)
34 s=v*I;
35 angle_s=angle_v-angle_I;
36 //function to convert from polar form to rectangular
form
37 function [x,y]=pol2rect(mag,angle);
38 x=mag*cos(angle*(%pi/180)); //to convert the angle
from degrees to radians
39 y=mag*sin(angle*(%pi/180));
40 endfunction;
41 [p,q]=pol2rect(s,angle_s);
42 disp(sprintf("(iii) The active power is %f W",p));
43 disp(sprintf("The reactive power is %f VAR",q));
44
45 //END

```

Scilab code Exa 2.48 Power factor of the combination

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 48
3

```

```

4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 48");
7
8 //VARIABLE INITIALIZATION
9 pf1=0.8;                                //power factor of 1st
    circuit
10 pf2=0.6;                                //power factor of 2nd
    circuit
11 z=1;                                     //this is an
    assumption
12
13 //SOLUTION
14 angle1=acos(pf1)*(180/%pi);           //in degrees
15 angle2=acos(pf2)*(180/%pi);           //in degrees
16 //function to convert from polar form to rectangular
    form
17 function [x,y]=pol2rect(mag,angle);
18 x=mag*cos(angle*(%pi/180));          //to convert the
    angle from degrees to radians
19 y=mag*sin(angle*(%pi/180));
20 endfunction;
21 [z1_x,z1_y]=pol2rect(z,angle1);
22 [z2_x,z2_y]=pol2rect(z,angle2);
23 nr=angle1+angle2;                      //numerator
24 z_x=z1_x+z2_x;
25 z_y=z1_y+z2_y;
26
27 //function to convert from rectangular form to polar
    form
28 function [z,angle]=rect2pol(x,y);
29 I=sqrt((x^2)+(y^2));
30 angle=atan(y/x)*(180/%pi);           //to convert the
    angle from radians to degrees
31 endfunction;
32 [z,angle]=rect2pol(z_x,z_y);
33 angle_z=nr-angle;
34 pf=cos(angle_z*(%pi/180));

```

```

35 disp(sprintf("The power factor of the combination is
36 %f",pf));
37 //END

```

Scilab code Exa 2.49 kVA and kW in each branch circuit and in the main circuit

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
2 .C. CIRCUIT
3 //Example 49
4
5 clc;
6 disp("CHAPTER 2");
7 disp("EXAMPLE 49");
8 //VARIABLE INITIALIZATION
9 v=200;                                //in Volts
10 angle_v=30;                            //in degrees
11 I1=20;                                 //in Amperes
12 angle_I1=60;                           //in degrees
13 I2=40;                                 //in Amperes
14 angle_I2=-30;                          //in degrees
15
16 //SOLUTION
17 //function to convert from polar form to rectangular
18 //form
19 function [x,y]=pol2rect(mag,angle);
20 x=mag*cos(angle*(%pi/180));           //to convert the
21 y=mag*sin(angle*(%pi/180));
22 endfunction;
23 [v_x,v_y]=pol2rect(v,angle_v);
24 [I1_x,I1_y]=pol2rect(I1,angle_I1);
25 [I2_x,I2_y]=pol2rect(I2,angle_I2);
26 s1=v*I1;

```

```

26 angle_s1=-angle_v+angle_I1;
27 disp(sprintf("The apparent power in 1st branch is %d
kVA",s1/1000));
28 [s1_x,s1_y]=pol2rect(s1,angle_s1);
29 disp(sprintf("The true power in 1st branch is %f kW"
,s1_x/1000));
30
31 disp("");
32
33 s2=v*I2;
34 angle_s2=angle_v-angle_I2;
35 disp(sprintf("The apparent power in 2nd branch is %d
kVA",s2/1000));
36 [s2_x,s2_y]=pol2rect(s2,angle_s2);
37 disp(sprintf("The true power in 2nd branch is %d kW"
,s2_x/1000));
38 I=(I1_x+I2_x)+(%i*(I1_y+I2_y)); disp(I);
39
40 //function to convert from rectangular form to polar
form
41 function [I,angle]=rect2pol(x,y);
42 I=sqrt((x^2)+(y^2));
43 angle=atan(y/x)*(180/%pi); //to convert the
angle from radians to degrees
44 endfunction;
45 [I,angle]=rect2pol(real(I),imag(I));
46 disp(I);
47 s=v*I;
48 angle_s=angle_v-angle;
49 disp(sprintf("The apparent power in the main circuit
is %f kVA",s/1000));
50 [p,q]=pol2rect(s,angle_s);
51 disp(sprintf("The true power in the main circuit is
%f kW",p/1000));
52
53 //END

```

Scilab code Exa 2.50 Current in each branch when total current is 20 A

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 50
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 50");
7
8 //VARIABLE INITIALIZATION
9 z1=6+(%i*5);                                //impedance in Ohms
10 z2=8-(%i*6);                               //impedance in Ohms
11 z3=8+(%i*10);                             //impedance in Ohms
12 I=20;                                         //in Amperes
13
14 //SOLUTION
15 Y1=1/z1;
16 Y2=1/z2;
17 Y3=1/z3;
18 Y=Y1+Y2+Y3;
19 //function to convert from rectangular form to polar
   form
20 function [Y,angle]=rect2pol(x,y);
21 Y=sqrt((x^2)+(y^2));
22 angle=atan(y/x)*(180/%pi);           //to convert the
   angle from radians to degrees
23 endfunction;
24 [Y_tot,angle]=rect2pol(real(Y),imag(Y));
25 v=I/Y_tot;
26 angle_v=-angle;
27 [z1,angle1]=rect2pol(real(z1),imag(z1));
28 [z2,angle2]=rect2pol(real(z2),imag(z2));
29 [z3,angle3]=rect2pol(real(z3),imag(z3));
```

```

30 I1=v/z1;
31 angle_I1=angle_v-angle1;
32 I2=v/z2;
33 angle_I2=angle_v-angle2;
34 I3=v/z3;
35 angle_I3=angle_v-angle3;
36 disp("The current in each branch in polar form is-")
    ;
37 disp(sprintf("%f A, %f degrees",I1,angle_I1));
38 disp(sprintf("%f A, %f degrees",I2,angle_I2));
39 disp(sprintf("%f A, %f degrees",I3,angle_I3));
40
41 //END

```

Scilab code Exa 2.51 Admittance and impedance of the circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 51
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 51");
7
8 //VARIABLE INITIALIZATION
9 Y1=0.4+(%i*0.6);           // admittance of 1st
     branch in Siemens
10 Y2=0.1+(%i*0.4);          // admittance of 2nd
     branch in Siemens
11 Y3=0.06+(%i*0.23);        // admittance of 3rd
     branch in Siemens
12
13 //SOLUTION
14 Y=Y1+Y2+Y3;
15 //function to convert from rectangular form to polar

```

```

        form
16 function [Y,angle]=rect2pol(x,y);
17 Y=sqrt((x^2)+(y^2));
18 angle=atan(y/x)*(180/%pi);      //to convert the
        angle from radians to degrees
19 endfunction;
20 [Y1,angle]=rect2pol(real(Y),imag(Y));
21 disp(sprintf("The total admittance of the circuit is
        %f S, %f degrees",Y1,angle));
22 z=1/Y1;
23 disp(sprintf("The impedance of the circuit is %f ,
        %f degrees",z,-angle));
24
25 //END

```

Scilab code Exa 2.52 Total impedance and current in each branch

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
        .C. CIRCUIT
2 //Example 52
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 52");
7
8 //VARIABLE INITIALIZATION
9 r1=7;                                //in Ohms
10 L1=0.015;                             //in Henry
11 r2=12;                                //in Ohms
12 c2=180*(10^(-6));                   //in Farad
13 r3=5;                                 //in Ohms
14 L3=0.01;                              //in Henry
15 v=230;                                //in Volts
16 f=50;                                 //in Hertz
17

```

```

18 //SOLUTION
19
20 // solution (a)
21 x11=2*%pi*f*L1;
22 xc2=1/(2*%pi*f*c2);
23 x13=2*%pi*f*L3;
24 Z1=r1+x11*%i; //complex
   representations
25 Z2=r2-xc2*%i;
26 Z3=r3+x13*%i;
27 //function to convert from rectangular form to polar
   form
28 function [z,angle]=rect2pol(r,x);
29 z=sqrt((r^2)+(x^2));
30 angle=atan(x/r)*(180/%pi); //to convert the angle
   from radians to degrees
31 endfunction;
32 [z1,angle1]=rect2pol(r1,x11);
33 [z2,angle2]=rect2pol(r2,xc2);
34 [z3,angle3]=rect2pol(r3,x13);
35 //to obtain rectangular form of (Z1+Z2)
36 req1=r1+r2;
37 xeq1=x11-xc2;
38 //to obtain polar form of (Z1+Z2)
39 [zeq1,angle_eq1]=rect2pol(req1,-xeq1);
40 zp=(z1*z2)/(zeq1);
41 angle_p=(angle1-angle2)+angle_eq1;
42 //function to convert from polar form to rectangular
   form
43 function [r,x]=pol2rect(z,angle);
44 r=z*cos(angle*(%pi/180)); //to convert the angle
   from degrees to radians
45 x=z*sin(angle*(%pi/180));
46 endfunction;
47 [rp,xp]=pol2rect(zp,angle_p);
48 [req,xeq]=pol2rect(z3,angle3);
49 r_tot=req+rp;
50 x_tot=xeq+xp;

```

```

51 [z_tot,angle_tot]=rect2pol(r_tot,x_tot);
52 Z=r_tot+x_tot*j; //complex
      representation
53 disp(sprintf("(a) The total impedance is %f , %f
      degrees",z_tot,angle_tot));
54
55 //solution (b)
56 I=v/Z; //complex division
57 angle_I=-angle_tot;
58 [I_x,I_y]=pol2rect(I,angle_I);
59 disp(sprintf("(b) The total current is (%f-j%f) A",
      real(I),imag(I)));
60
61 //solution (c)
62 //Voltage drop across Z3
63 Vab=I*Z3;
64 disp(sprintf("      The Voltage between AB is (%f-j%f)
      A",real(Vab),imag(Vab)));
65 //since we know that V=Vab+Vbc
66 Vbc=v-Vab;
67 disp(sprintf("      The Voltage between BC is (%f-j%f)
      A",real(Vbc),imag(Vbc)));
68 I1=Vbc/Z1; //Branch 1 current
69 I2=Vbc/Z2; //branch 2 current
70 //I3=I, main branch current
71 [mag1,angle1]=rect2pol(real(I1),imag(I1));
72 [mag2,angle2]=rect2pol(real(I2),imag(I2));
73 disp(sprintf("(c) Current in branch 1 is %f A, %f
      degrees",mag1,angle1));
74 disp(sprintf("      The current in branch 1 is (%f-
      j%f) A",real(I1),imag(I1)));
75 disp(sprintf("      The current in branch 2 is %f A,
      %f degrees",mag2,angle2));
76 disp(sprintf("      The current in branch 2 is (%f-
      j%f) A",real(I2),imag(I2)));
77 //END

```

Scilab code Exa 2.53 Total impedance and power taken

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
. C. CIRCUIT
2 //Example 53 Read Example 52 of the Text Book
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 53");
7
8 //VARIABLE INITIALIZATION
9 v=230;                                //in Volts
10 angle_v=30;                            //in degrees
11 I1=20;                                 //in Amperes
12 angle_I1=60;                           //in degrees
13 I2=40;                                 //in Amperes
14 angle_I2=-30;                          //in degrees
15
16 //SOLUTION
17 //function to convert from polar form to rectangular
   form
18 function [x,y]=pol2rect(mag,angle);
19 x=mag*cos(angle*(%pi/180));           //to convert the
   angle from degrees to radians
20 y=mag*sin(angle*(%pi/180));
21 endfunction;
22 [x1,y1]=pol2rect(I1,angle_I1);
23 [x2,y2]=pol2rect(I2,angle_I2);
24 X=x1+x2;
25 Y=y1+y2;
26
27 //function to convert from rectangular form to polar
   form
28 function [I,angle]=rect2pol(x,y);
```

```

29 I=sqrt((x^2)+(y^2));
30 angle=atan(y/x)*(180/%pi); //to convert the
   angle from radians to degrees
31 endfunction;
32 [I,angle]=rect2pol(X,Y);
33
34 //solution (i)
35 z=v/I;
36 angle_z=angle_v-angle;
37 disp(sprintf("(i) The total impedance of the circuit
   is %f , %f degrees",z,angle_z));
38
39 //solution (ii)
40 //disp(sprintf("The value of I is %f and angle is %f
   ",I, angle_z));
41 pf=cos(angle_z*(%pi/180));
42 p=v*I*pf;
43 disp(sprintf("(ii) The power taken is %f W",p));
44 //END

```

Scilab code Exa 2.54 Q factor at resonance

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 54 Read example 53 of the Book
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 54");
7
8 //VARIABLE INITIALIZATION
9 C=2.5/(10^6); //capacitance in
   Farads
10 R=15; //in Ohms
11 L=260/1000; //in Henry

```

```

12
13 //SOLUTION
14
15 //solution ( i )
16 f_r=(1/(2*pi))*sqrt((1/(L*C)-(R^2/L^2)));
17 f_r=round(f_r);                                //to round off the
18 disp(sprintf("( i ) The resonant frequency is %d Hz" ,
19 f_r));
20 //solution ( ii )
21 q_factor=(2*pi*f_r*L)/R;
22 disp(sprintf("( ii ) The Q-factor of the circuit is %f
23 " ,q_factor));
24 //solution ( iii )
25 Z_r=L/(C*R);
26 disp(sprintf("( iii ) The dynamic impedance of the
27 circuit is %f " ,Z_r));
28 //END

```

Chapter 3

Three Phase AC Circuits

Scilab code Exa 3.1 Identical impedances each consisting of 15 ohm in series

```
1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 1
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 v_l=400;                                // line voltage in
                                              Volts
10 r=15;                                     // resistance in
                                              Ohms
11 xc=10;                                    // capacitive
                                              reactance in Ohms
12
13 //SOLUTION
14
15 //solution (i)
16 v_ph=v_l/sqrt(3);                         // phase voltage=(
                                              line voltage)/sqrt(3) for star connection
17 disp(sprintf("(i) The phase voltage is %f V",v_ph));
```

```

18
19 //solution (ii)
20 z_ph=sqrt((r^2)+(xc^2));
21 I_l=v_ph/z_ph; //phase current =
    line current for star connection
22 disp(sprintf("(ii) The line current is %f A",I_l));
23
24 //solution (iii)
25 disp(sprintf("(iii) The phase current is %f A",I_l))
    ;
26
27 //solution (iv)
28 pow_fact=r/z_ph;
29 disp(sprintf("(iv) The power factor of the circuit
    is %f (leading)",pow_fact));
30
31 //solution (v)
32 p=sqrt(3)*v_l*I_l*pow_fact;
33 disp(sprintf("(v) The total power absorbed is %f W",
    p));
34
35 //solution (vi)
36 va=sqrt(3)*v_l*I_l;
37 disp(sprintf("(vi) The apparent power is %f VA",va))
    ;
38 var=sqrt((va^2)-(p^2));
39 disp(sprintf("The reactive power is %f VAR",var));
40
41 //Answers (v) and (vi) are different due to
    precision of floating point numbers
42
43 //END

```

Scilab code Exa 3.2 Resistance and reactance values of each impedance

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 2
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 v_l=400;                                //line voltage in
                                              Volts
10 I_l=30;                                  //line current in
                                              Amperes
11 p=12*1000;                               //power absorbed
                                              in Watts
12
13 //SOLUTION
14 v_ph=v_l/sqrt(3);                      //phase voltage =
                                              (line voltage)/sqrt(3)
15 z_ph=v_ph/I_l;                          //phase current =
                                              line current for star connection
16 pow_fact=p/(sqrt(3)*v_l*I_l);        //three-phase
                                              power = sqrt(3)*v_l*I_l*pow_fact
17 r_ph=z_ph*pow_fact;                    //from impedance
                                              triangle
18 disp(sprintf("The resistance of each impedance is %f
                                              ",r_ph));
19 x_ph=sqrt((z_ph^2)-(r_ph^2));
20 disp(sprintf("The reactance of each impedance is %f
                                              ",x_ph));
21
22 //END

```

Scilab code Exa 3.3 Three similar coils each of 30 ohms

```
1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
```

```

2 //Example 3
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 r_ph=30;                                // resistance of coils
   in Ohms
10 l=0.07;                                  // inductance of coils
    in Henry
11 v_l=400;                                 //line voltage in Volts
12 f=50;                                    //frequency in Hertz
13
14 //SOLUTION
15
16 //solution (a)
17 x_ph=2*(%pi)*f*l;                      //inductive reactance
18 z_ph=sqrt((r_ph^2)+(x_ph^2));
19 I_ph=v_l/z_ph;                          //phase voltage = line
   voltage for delta connection
20 disp(sprintf("(a) The phase current is %f A",I_ph));
21
22 //solution (b)
23 I_l=sqrt(3)*I_ph;                      //phase current = (line
   current)/sqrt(3) for delta connection
24 disp(sprintf("(b) The line current is %f A",I_l));
25
26 //solution (c)
27 pow_fact=r_ph/z_ph;
28 disp(sprintf("(c) The power factor is %f (lagging)",pow_fact));
29
30 //solution (d)
31 p=sqrt(3)*v_l*I_l*pow_fact;
32 disp(sprintf("(d) The power absorbed is %f W",p));
33
34 //Answer is different due to precision of floating

```

```
    point numbers  
35  
36 //END
```

Scilab code Exa 3.4 Line and phase current when phase sequence is positive

```
1 //CHAPTER 3– THREE-PHASE A.C. CIRCUITS  
2 //Example 4  
3  
4 clc;  
5 disp("CHAPTER 3");  
6 disp("EXAMPLE 4");  
7  
8 //VARIABLE INITIALIZATION  
9 v_l=866;                                //line voltage  
    in Volts  
10 z_delta=177-(%i*246);                  //impedance of  
    delta connected load in Ohms  
11 z_wire=1+(%i*2);                      //impedance of  
    each wire of the line in Ohms  
12  
13 //SOLUTION  
14 v_ph=v_l/sqrt(3);                     //phase  
    current = (line current)/sqrt(3) for star  
    connection  
15 z_star=z_delta/3;  
16 z=z_wire + z_star;  
17 I=v_ph/z;                            //I_na in  
    rectangular form  
18 //I_na, I_nb and I_nc are same in magnitude and are  
    the line currents for delta connection or vice-  
    versa  
19 //function is not used to covert quantities in  
    rectangular form to polar form  
20 //I_na
```

```

21 I_na=sqrt((real(I))^2+(imag(I))^2); //I_na from
    rectangular to polar form
22 a=atan(imag(I)/real(I)); //angle in
    radians
23 a=a*(180/%pi); //radians to
    degrees
24 //I_nb
25 I_na=sqrt((real(I))^2+(imag(I))^2);
26 b=a-120; //lags by 120
    degrees
27 //I_nc
28 I_na=sqrt((real(I))^2+(imag(I))^2);
29 c=a-240; // lags by
    another 120 degrees ie.,240 degrees
30 disp(sprintf("The line currents are %f A (%f degrees
    ), %f A (%f degrees) and %f A (%f degrees)" ,I_na ,
    a,I_na,b,I_na,c));
31
32
33 //line current lags phase current by 30 degrees ,
    hence (-30)
34 //I_AB
35 I_AB=I_na/sqrt(3);
36 a1=a-(-30);
37 //I_BC
38 I_BC=I_na/sqrt(3);
39 b1=b-(-30);
40 //I_AC
41 I_AC=I_na/sqrt(3);
42 c1=c-(-30);
43 disp(sprintf("The phase currents are %f A (%f
    degrees) , %f A (%f degrees) and %f A (%f degrees)
    " ,I_AB ,a1 ,I_BC ,b1 ,I_AC ,c1));
44
45 //converting z_delta from polar form to rectangular
    form
46 z=sqrt((real(z_delta))^2+(imag(z_delta))^2);
47 angle=atan(imag(z_delta)/real(z_delta));

```

```

48 angle=angle*(180/%pi);
49
50 //line voltages for load or phase voltages for the
   delta load-
51 //v_AB
52 v_AB=I_AB*z;
53 a2=a1+angle;
54 //v_B
55 v_BC=I_BC*z;
56 b2=b1+angle;
57 //v_AC
58 v_AC=I_AC*z;
59 c2=c1+angle;
60 disp(sprintf("The phase voltages for the delta load
   are %f A (%f degrees), %f A (%f degrees) and %f
   A (%f degrees)",v_AB,a2,v_BC,b2,v_AC,c2));
61
62 p_AB=(I_AB^2)*real(z_delta);
63 p_load=3*p_AB;
64 disp(sprintf("The power absorbed by the load is %f W
   ",p_load));
65 p_l=3*(I_na^2)*real(z_wire);
66 disp(sprintf("The power dissipated by the line is %f
   W",p_l));
67 p=p_load+p_l;
68 disp(sprintf("The total power supplied by 3-
   source is %f W",p));
69
70 //Answers may be slightly different due to precision
   of floating point numbers
71
72 //END

```

Scilab code Exa 3.5 Power measurement by 2 wattmeter method

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 5
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 w1=5000;                                // reading of 1st
   wattmeter in Watts
10 w2=-1000;                                // reading of 2nd
    wattmeter in Watts
11
12 //SOLUTION
13
14 //solution (a)
15 p1=w1+w2;
16 disp(sprintf("(a) The total power is %d W",p1));
17
18 //solution (b)
19 p2=w1-w2;
20 phi=atan((sqrt(3)*p2)/p1);      //this equation comes
   from two-wattmeter method
21 pow_fact=cos(phi);
22 disp(sprintf("(b) The power factor of the load is %f",
   , pow_fact));
23
24 //END

```

Scilab code Exa 3.6 3300 V synchronous alternator

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 6
3
4 clc;

```

```

5 disp("CHAPTER 3");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 v_l=3300;                                //line voltage in
   Volts
10 p_out=1500*735.5;                      //output power in
   Watts (1 metric horsepower= 735.498W)
11 eff=0.85;
12 pow_fact=0.81;
13
14 //SOLUTION
15
16 // solution (a)
17 p_in=p_out/eff;
18 disp(sprintf("(a) The motor input is %f kW",p_in
   /1000));
19
20 // solution (b)
21 I=p_in/(sqrt(3)*v_l*pow_fact); //phase current = line
   current for star connection
22 disp(sprintf("(b) The line and phase current of the
   alternator is %f A",I));
23
24 // solution (c)
25 I_l=I;
26 I_ph=I_l/sqrt(3);                      //phase current = (
   line current)/sqrt(3) for delta connection
27 disp(sprintf("(c) The line current of the motor is
   %f A",I_l));
28 disp(sprintf("The phase current of the motor is %f A
   ",I_ph));
29
30 //Answers may be different due to precision of
   floating point numbers
31
32 //END

```

Scilab code Exa 3.7 Three phase star connected system

```
1 //CHAPTER 3– THREE-PHASE A.C. CIRCUITS
2 //Example 7
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 v_ph=200;                                //phase voltage
   in Volts
10 r1=5;                                     //in Ohms
11 r2=8;                                     //in Ohms
12 r3=10;                                    //in Ohms
13
14 //SOLUTION
15 I1=v_ph/r1;
16 I2=v_ph/r2;
17 I3=v_ph/r3;
18 disp(sprintf("The current in the three phases are %d
   A, %d A and %d A",I1,I2,I3));
19
20 I_x=0+I2*(sqrt(3)/2)-I3*(sqrt(3)/2); //x-component
   of the three currents =>I_x = I1*cos(90) + I2*cos
   (30) + I3*cos(30)
21 I_y=I1-(I2*0.5)-(I3*0.5);              //y-component
   of the three currents =>I_y = I1*sin(90) + I2*sin
   (30) + I3*sin(30)
22 I=sqrt((I_x^2)+(I_y^2));
23 disp(sprintf("The neutral current is %f A",I));
24
25 p1=v_ph*I1;                            //power
   consumed in 1st phase
```

```

26 p2=v_ph*I2;                                // power
      consumed in 2nd phase
27 p3=v_ph*I3;                                // power
      consumed in 3rd phase
28 disp(sprintf("The power consumed in the three phases
      are %d W, %d W and %d W",p1,p2,p3));
29
30 p=p1+p2+p3;
31 disp(sprintf("The total power is %d W",p));
32
33 //END

```

Scilab code Exa 3.8 Balanced delta connection

```

1 //CHAPTER 3– THREE-PHASE A.C. CIRCUITS
2 //Example 8
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 v_ph=230;                                     //in Volts
      and in polar form
10 z=8+(%i*6);                                  //in Ohms
      and in rectangular form
11
12 //SOLUTION
13 //converting z from rectangular form to polar form
14 z_mag=sqrt(real(z)^2+imag(z)^2);
15 phi=atan(imag(z)/real(z));                  // atan()
      gives output in radians
16
17 I_ph=v_ph/z_mag;
18 I_l=sqrt(3)*I_ph;

```

```

19 disp(sprintf("The line current is %f A", I_1));
20
21 pow_fact=cos(phi);
22 disp(sprintf("The power factor is %f", pow_fact));
23
24 p=sqrt(3)*v_ph*I_1*pow_fact; //phase volt=
    line volt in delta connection(v_l=v_ph)
25 disp(sprintf("The power is %f W", p));
26
27 var=sqrt(3)*v_ph*I_1*sin(phi);
28 var=var/1000; //from VAR to
    kVAR
29 disp(sprintf("The reactive power is %f kVAR", var));
30
31 va=sqrt(3)*v_ph*I_1;
32 va=va/1000; //from VA to
    kVA
33 disp(sprintf("The total volt amperes is %f kVA", va))
    ;
34
35 //END

```

Scilab code Exa 3.9 400 V 50 Hz three phase supply

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 9
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 v_ab=400; //in Volts
10 v_bc=400; //in Volts
11 v_ac=400; //in Volts

```

```

12 z_ab=100; //in Ohms
13 z_bc=100; //in Ohms
14 z_ac=100; //in Ohms
15
16 //solution (a)
17
18 //function to convert from polar to rectangular form
19 function [x,y]=pol2rect(mag,angle);
20 x=mag*cos(angle);
21 y=mag*sin(angle);
22 endfunction;
23
24 I_AB=v_ab/z_ab;
25 mag1=abs(real(I_AB)); //I_AB is represented as
26 ang1=0; m a g 1 angl
27 I_BC=v_bc/z_bc;
28 ang2=-210*(%pi/180); //I_BC is represented
29 I_AC=v_ac/z_ac;
30 ang3=210*(%pi/180); //I_AC is represented
31 [x1,y1]=pol2rect(I_AB,ang1);
32 [x2,y2]=pol2rect(I_BC,ang2);
33 [x3,y3]=pol2rect(I_AC,ang3);
34 //let us consider values X1, Y1, X2, Y2, X3 and Y3
35 //for the ease of calculation (these are not
36 //mentioned in the book)
37 X1=x1-x3;
38 Y1=y1-y3;
39 X2=x2-x1;
40 Y2=y2-y1;
41 X3=x3-x2;
42 Y3=y3-y2;
43 I_A=X1+(%i*Y1);
44 I_B=X2+(%i*Y2);
45 I_C=X3+(%i*Y3);
46

```

```

45 //function to convert from rectangular to polar form
46 function [z,angle]=rect2pol(x,y);
47 z=sqrt((x^2)+(y^2)); //z is impedance &
    the resultant of x and y
48 if(x==0 & y>0) then angle=90; //in case atan=
49 elseif(x==0 & y<0) then angle=-90 //in case atan=-
50 else
51 angle=atan(y/x)*(180/%pi); //to convert the
    angle from radians to degrees
52 end;
53 endfunction;
54
55 [mag4 ,ang4]=rect2pol(X1 ,Y1 );
56 [mag5 ,ang5]=rect2pol(X2 ,Y2 );
57 [mag6 ,ang6]=rect2pol(X3 ,Y3 );
58 disp(sprintf("(a) The line current I_A is %f %f A"
    ,mag4 ,ang4));
59 disp(sprintf("The line current I_B is %f %f A",
    mag5 ,(180+ang5)));
60 disp(sprintf("The line current I_C is %f %f A",
    mag6 ,ang6));
61
62 //solution (b)
63 //since power is consumed only by 100 resistance
    in the arm AB
64 r1=100;
65 p1=(I_AB^2)*r1;
66 p2=160000;
67 r2=p2/p1;
68 disp(sprintf("(b) The star connected balanced
    resistance is %d ",r2));
69
70 //END

```

Scilab code Exa 3.11 Balanced load of 20kVA

```
1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 11
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 11");
7
8 //SOLUTION
9 function power_sum=p1(phi);
10 power_sum=20*cos(phi); //power_sum=
    p1+p2=20*cos(phi) and in KiloWatts
11 endfunction;
12 function power_diff=p2(phi);
13 power_diff=(20*sin(phi))/sqrt(3); //power_diff=
    p1-p2=(20*sin(phi))/sqrt(3) and in KiloWatts
14 endfunction;
15
16 //solution (a): when phi=0
17 power_sum=20*cos(0); //eq(i)
18 power_diff=(20*sin(0))/sqrt(3); //eq(ii)
19 //solving eq(i) and eq(ii) to get values of p1 and
    p2
20 A=[1 1;1 -1];
21 b=[power_sum;power_diff];
22 x=inv(A)*b;
23 x1=x(1,:); //to access
    the 1st row of 2X1 matrix
24 x2=x(2,:); //to access
    the 2nd row of 2X1 matrix
25 disp("Solution (a)");
26 disp(sprintf("P1 + P2 = %d kW",power_sum));
27 disp(sprintf("P1 - P2 = %d kW",power_diff));
28 disp(sprintf("The two wattmeter readings are %d kW
    and %d kW",x1,x2));
29
30 //solution (b): when phi=30 or %pi/6 (lagging)
```

```

31 power_sum=20*cos(%pi/6);
32 power_diff=(20*sin(%pi/6))/sqrt(3);
33 A=[1 1;1 -1];
34 b=[power_sum;power_diff];
35 x=inv(A)*b;
36 x1=x(1,:);
37 x2=x(2,:);
38 disp("Solution (b)");
39 disp(sprintf("P1 + P2 = %f kW",power_sum));
40 disp(sprintf("P1 - P2 = %f kW",power_diff));
41 disp(sprintf("The two wattmeter readings are %f kW
        and %f kW",x1,x2));
42
43 //solution (c): when phi=60 or %pi/3
44 power_sum=20*cos(%pi/3);
45 power_diff=(20*sin(-(pi/3)))/sqrt(3); //leading
46 A=[1 1;1 -1];
47 b=[power_sum;power_diff];
48 x=inv(A)*b;
49 x1=x(1,:);
50 x2=x(2,:);
51 disp("Solution (c)");
52 disp(sprintf("P1 + P2 = %f kW",power_sum));
53 disp(sprintf("P1 - P2 = %f kW",power_diff));
54 disp(sprintf("The two wattmeter readings are %f kW
        and %f kW",x1,x2));
55
56 //solution (d): when phi=90 or %pi/2
57 power_sum=20*cos(%pi/2);
58 power_diff=(20*sin(%pi/2))/sqrt(3); //leading
59 A=[1 1;1 -1];
60 b=[power_sum;power_diff];
61 x=inv(A)*b;
62 x1=x(1,:);
63 x2=x(2,:);
64 disp("Solution (d)");
65 disp(sprintf("P1 + P2 = %f kW",power_sum));
66 disp(sprintf("P1 - P2 = %f kW",power_diff));

```

```

67 disp(sprintf("The two wattmeter readings are %f kW
    and %f kW",x1,x2));
68
69 //END

```

Scilab code Exa 3.12 Three identical impedances each having a resistance R

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 12
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION
9 v_l=400;                                //in Volts
10 f=50;                                    //in Hertz
11 w1=2000;                                 //in Watts
12 w2=800;                                  //in Watts
13
14 //SOLUTION
15 //solution (a)
16 p1=w1+w2;
17 p2=w1-w2;
18 phi=atan((sqrt(3)*p2)/p1);   // this equation comes
      from two-wattmeter method
19 pow_fact=cos(phi);
20 disp(sprintf("(a) The power factor of the circuit is
    %f (leading)",pow_fact));
21
22 //solution (b)
23 I_l=p1/(sqrt(3)*v_l*pow_fact);
24 disp(sprintf("(b) The line current is %f A",I_l));
25
26 //solution (c)

```

```
27 v_ph=v_l/sqrt(3);
28 z_ph=v_ph/I_l; //phase current = line
    current for delta connection
29 r_ph=z_ph*pow_fact;
30 disp(sprintf("(c) The resistance of each phase is %f
    ",r_ph));
31 xc=sqrt((z_ph^2)-(r_ph^2));
32 c=1/(2*pi*f*xc);
33 disp(sprintf("The capacitance of each phase is %E F"
    ,c));
34
35 //END
```

Chapter 4

Measuring Instruments

Scilab code Exa 4.1 Deflecting torque exerted on a coil

```
1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 1
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 N=10;           //number of turns
10 I=5;           //in amperes
11 B=500;          //flux density in Wb/m^2
12 ar=15/10000;    //area in m^2
13
14 //SOLUTION
15 T_d=N*B*I*ar;
16 disp(sprintf("The deflecting torque exerted on the
   coil is %f N-m",T_d));
17
18 //END
```

Scilab code Exa 4.2 Current through galvanometer

```
1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 2
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 G=10;           //galvanometer resistance in Ohms
10 S=1;           //shunt resistance in Ohms
11 r=12;          //total resistance in Ohms
12 emf=2;         //emf of cell in Volts
13
14 //SOLUTION
15 I=emf/r;       //current in the circuit
16 I_g=(S*I)/(S+G);
17 disp(sprintf("The current through the galvanometer
18           is %f A",I_g));
19 //END
```

Scilab code Exa 4.3 Resistance of wire

```
1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 3
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 3");
7
```

```

8 //VARIABLE INITIALIZATION
9 I=1;                      //in Amperes (I=1 is an
   assumption)
10 I_g=I/100;                //in Amperes
11 G=2970;                  //in Ohms
12
13 //SOLUTION
14 S=(G*I_g)/(I-I_g); //since I_g=(S*I)/(S+G);
15
16 disp(sprintf("The wire should have a resistance of
   %f    ",S));
17
18 //END

```

Scilab code Exa 4.4 Resistance required to read current and voltage

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 4
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 r_A=10;                      //in Ohms
10 I_A=15/1000;                 //from mA to A
11 I=100;                       //in A
12 V=500;                       //in Volts
13
14 //SOLUTION
15
16 //solution (a)
17 R_sh=r_A/((I/I_A)-1); //((I/I_A) is the
   multiplying factor of the shunt
18

```

```

19 disp(sprintf("The required shunt resistance is %f
",R_sh));
20
21 //solutuion (b)
22 r=V/I_A;                                // total resistance
23 R_se=r-r_A;
24 disp(sprintf("The required resistance to be added in
series is %f ",R_se));
25
26 //END

```

Scilab code Exa 4.5 Number of revolutions made by energy meter and percentage error

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 5
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 m_c=100;                                //meter constant in rev/
kWh
10 I=20;                                    //load current in Amperes
11 v=230;                                    //supply voltage in Volts
12 pow_fact=0.8;
13 rev_act=360;                                //actual number of
revolutions
14
15 //SOLUTION
16 E=(v*I*pow_fact)/1000;      // 'E' is energy consumed
in one hour in kWh
17 rev=m_c*E;                                //number of revolutions
for true energy

```

```

18 disp(sprintf("The number of revolutions made by the
    meter is %f",rev));
19 err=(rev_act-rev)/rev;           //error
20 err=err*100;                  //percentage error
21 disp(sprintf("The percentage error is %f %%",err));
22 if(err<0) then
23 disp("The negative sign indicates that the meter
    will run slow");
24 end
25
26 //END

```

Scilab code Exa 4.6 Series resistance to measure 500 V on full scale

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 6
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 I_m=20/1000;           //full scale deflection in
    Ampères
10 v_m=50/1000;          //applied potential difference
    in Volts
11 v=500;                //in Volts
12
13 //SOLUTION
14 r_m=v_m/I_m;          //resistance of moving-coil
    instrument
15 r_s=(v/I_m)-r_m;
16 disp(sprintf("The series resistance to measure 500 V
    on full scale is %f    ",r_s));
17

```

18 //END

Scilab code Exa 4.7 Percentage error of energy meter

```
1 //CHAPTER 4- MEASURING INSTRUMENTS
2 //Example 7
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 m_c=100;           //meter constant in rev/kwh
10 I=20;             //in Amperes
11 v=210;            //in Volts
12 pow_fact=0.8;     //leading
13 rev_act=350;      //actual revolution
14
15 //SOLUTION
16 E=(v*I*pow_fact)/1000; //from Wh to kWh
17 rev_true=m_c*E;
18 disp(sprintf("The number of revolutions made by the
    meter is %f",rev_true));
19 err=(rev_act-rev_true)/rev_true;
20 err=err*100;        //percentage error
21 disp(sprintf("The percentage error is %f %%",err));
22 if(err<0) then
23 disp("The negative sign indicates that the meter
    will run slow");
24 end
25
26 //END
```

Scilab code Exa 4.8 Resistance required to read current and voltage

```
1 //CHAPTER 4- MEASURING INSTRUMENTS
2 //Example 8
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 I_m=15/1000;           //from mA to A
10 r_m=5;                //in Ohms
11 I=2;                  //in Amperes
12 v=30;                 //in Volts
13
14 //SOLUTION
15 R_sh=(I_m*r_m)/I;     //I_m=I*(R_sh/(R_sh+r_m)) if
   R_sh<<5 , then I_m=I*(R_sh/r_m) neglecting R_sh
   in the denominator
16 disp(sprintf("In order to read upto 2A, a shunt of
   %f      has to be connected in parallel",R_sh));
17
18 R_se=(v-(I_m*r_m))/I_m;
19 disp(sprintf("In order to read upto 30V, a
   resistance of %f      has to be connected in series
   ",R_se));
20
21 //END
```

Scilab code Exa 4.9 Percentage error of meter

```
1 //CHAPTER 4- MEASURING INSTRUMENTS
2 //Example 9
3
4 clc;
```

```

5 disp("CHAPTER 4");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 I=50;                                //in Amperes
10 v=230;                                 //in Volts
11 rev=61;                                //revolutions
12 t=37/3600;                            //from seconds to hours
13 m_c=500;                               //meter constant in rev/
   kwh
14 pow_fact=1;                           //since load is purely
   resistive
15
16 //SOLUTION
17 E1=(v*I*t*pow_fact)/1000; //energy consumed in 37
   seconds in kWh
18 E2=rev/m_c;                          //energy consumption
   registered by meter
19 err=(E2-E1)/E1;
20 err=err*100;                         //percentage error
21 disp(sprintf("The percentage error is %f %%",err));
22 if(err<0) then
23 disp("The negative sign indicates that the meter
   will run slow");
24 end
25
26 //END

```

Scilab code Exa 4.10 Readings of two voltmeters

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 10
3
4 clc;
5 disp("CHAPTER 4");

```

```

6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 r1=2;                      //in Ohms (r1=2 is an
   assumption)
10 r2=2;                      //in Ohms (since r1=r2)
11 v=100;                     //in Volts
12
13 //SOLUTION
14 v1=(v*r1)/(r1+r2);        //voltage divider law
15 v2=(v*r2)/(r1+r2);        //voltage divider law
16 disp(sprintf("Reading of the 1st voltmeter is %d V",
   v1));
17 disp(sprintf("Reading of the 2nd voltmeter is %d V",
   v2));
18
19 //END

```

Scilab code Exa 4.11 Readings of two voltmeters with different internal resistance

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 11
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 11");
7
8 //VARIABLE INITIALIZATION
9 r1=30000;                  //in Ohms
10 r2=20000;                  //in Ohms
11 v=600;                     //in Volts
12
13 //SOLUTION
14 v1=(r1*v)/(r1+r2);        //voltage divider law
15 v2=(r2*v)/(r1+r2);        //voltage divider law

```

```

16 disp(sprintf("Reading of the 1st voltmeter is %d V",
17 v1));
17 disp(sprintf("Reading of the 2nd voltmeter is %d V",
18 v2));
19 //END

```

Scilab code Exa 4.12 Total current carried by two ammeters

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 12
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION
9 I1=1; // full scale current in 1st
       ammeter in mA
10 I2=10; // full scale current in 2nd
        ammeter in mA
11 r1=100; //internal resistance of 1st
        ammeter in Ohms
12 r2=25; //internal resistance of 2nd
        ammeter in Ohms
13
14 //SOLUTION
15 R1=r2/(r1+r2); //resistance for 1st ammeter
16 R2=r1/(r1+r2); //resistance for 2nd ammeter
17 I=I1/R1; //by current divider law I1=(I*
             r2)/(r1+r2) =>I1=I*R1 =>I=I1/R1
18 A2=I*R2; //A2=reading of second ammeter
19 disp(sprintf("The total current that the two
       ammeters can carry is %d mA",I));
20

```

21 //END

Chapter 6

Magnetic Circuits

Scilab code Exa 6.1 Magnetic circuit having two air gaps

```
1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 1
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 lA=17/100;           //length of A in meters (lA is
                      calculated in the solution in the book; here it
                      is initialised directly for the sake of
                      convinience)
10 l=3/100;             //in meters
11 lg=2/1000;           //width of air-gap in meters
12 N=1000;              //number of turns
13 AB=10/100;            //in meters
14 BC=20/100;            //in meters
15 CD=10/100;            //in meters
16 I=1;                  //exciting current in Amperes
17 murA=1000;            //relative permeability of part A
18 murB=1200;            //relative permeability of part B
```

```

19 mu0=4*%pi*10^(-7); // absolute permeability in Henry/
    meters
20
21 //SOLUTION
22
23 //solution (i)
24 ar=l*l; //area of cross-section
25 rA=lA/(mu0*murA*ar);
26 disp(sprintf("(i) Reluctance of part A is %E AT/Wb" ,
    rA));
27 lB=(AB-(1/2))+(BC-1)+(CD-(1/2));
28 rB=lB/(mu0*murB*ar);
29 disp(sprintf("Reluctance of part B is %E AT/Wb" ,rB))
    ;
30
31 //solution (ii)
32 lg=2*lg;
33 murg=1;
34 rg=lg/(mu0*murg*ar);
35 disp(sprintf("(ii) Reluctance of the two air gaps is
    %E AT/Wb" ,rg));
36
37 //solution (iii)
38 rT=rA+rB+rg;
39 disp(sprintf("(iii) Total reluctance is %E AT/Wb" ,rT
    ));
40
41 //solution (iv)
42 mmf=N*I;
43 disp(sprintf("(iv) MMF is %d AT" ,mmf));
44
45 //solution (v)
46 totFlux=mmf/rT;
47 disp(sprintf("(v) Total flux is %E Wb" ,totFlux));
48
49
50 //solution (vi)
51 b=totFlux/ar;

```

```

52 disp(sprintf("( vi) Flux density is %f Wb/m^2" ,b));
53
54 //Answers of (v) and (vi) do not match due to
55 // calculation mistake in the book
56 //END

```

Scilab code Exa 6.2 Steel ring of 25 cm mean diameter

```

1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 2
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 dr=25/100;                                //diameter of steel
10 ds=3/100;                                  //diameter of
11 lg=1.5/1000;                               //length of air-gap
12 N=700;                                     //number of turns
13 mu0=4*pi*10^(-7);                         //absolute
14 I=2;                                       //in Amperes
15
16 //SOLUTION
17
18 //solution ( i )
19 mmf=N*I;
20 disp(sprintf("( i) MMF is %d AT" , mmf));
21
22 //solution ( ii )

```

```

23 netMMF=(mmf-(0.35*mmf));           //mmf taken by iron
     path is 35% of total mmf
24 b=(mu0*netMMF)/lg;                 // phi=b*area , r=lg
     /(mu0*area) & mmf=phi*r => mmf=(b*lg)/mu0 => b=(
     mmf*mu0)/lg
25 disp(sprintf("( ii ) The flux density of the air gap
     is %E Wb/m^2" , b));
26
27 //solution ( iii )
28 ar=%pi*((ds/2)^2);                // area of cross-
     section of circular section
29 phi=ar*b;
30 disp(sprintf("( iii ) The magnetic flux is %E Wb" ,phi))
     );
31
32 //solution ( iv )
33 rt=mmf/phi;
34 disp(sprintf("( iv ) The total reluctance is %E AT/wb"
     ,rt));
35
36 //solution ( v )
37 rg=lg/(mu0*ar);                  // reluctance of air
     gap
38 rs=rt-rg;                        // reluctance of
     steel
39 lr=%pi*dr;                      // circumference of
     ring
40 mur=lr/(mu0*rs*ar);
41 disp(sprintf("( v ) The relative permeability of the
     steel ring is %E" ,mur));
42
43 //solution ( vi )
44 disp(sprintf("( vi ) Reluctance of steel is %E AT/Wb" ,
     rs));
45
46 //END

```

Scilab code Exa 6.3 Magnetic circuit with cast steel core

```
1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 3
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 lg1=0.025/100;                                //length of 1st air-
   gap in m
10 a1=(1*1)/10000;                                //in m^2
11 lg2=0.02/100;                                 //length of 2nd air-
   gap in m
12 a2=(1*1)/10000;                                //in m^2
13 lg3=0.02/100;                                 //length of 3rd air-
   gap in m
14 a3=(2*1)/10000;                                //in m^2
15 phi=0.75/1000;                                 //flux in Wb
16 lc1=0.5;                                       //length through outer
   limb in m
17 lc2=0.5;                                       //length through outer
   limb in m
18 lc3=0.2;                                       //length through
   central limb in m
19 mu0=4*pi*10^(-7);                            //absolute
   permeability in Henry/m
20
21 //SOLUTION
22
23 //solution (a): when mur=infinity i.e., no mmf drops
   in any member of the core
24 rg1=lg1/(mu0*a1);                            //reluctance of 1st
```

```

        air-gap
25 rg2=lg2/(mu0*a2);           // reluctance of 2nd
        air-gap
26 rg3=lg3/(mu0*a3);           // reluctance of 3rd
        air-gap
27 rgeq=(rg1*rg2)/(rg1+rg2);   // parallel combination
        of resistors
28 mmf1=phi*(rg1+rg3);
29 mmf1=round(mmf1);           // to round off the
        value
30 disp(sprintf("(a) MMF of the exciting coil when
        permeability is infinity is %d AT",mmf1));
31
32 // solution (b): when mur=5000 i.e., reluctance of
        magnetic core must be considered
33 mur=5000;
34 rc1=lc1/(mu0*mur*a1);       // reluctance of first
        path in the core
35 rc2=lc2/(mu0*mur*a2);       // reluctance of second
        path in the core
36 rc3=lc3/(mu0*mur*a3);       // reluctance of third
        path in the core
37 r1=rg1+rc1;
38 r2=rg2+rc2;
39 r3=rg3+rc3;
40 req=(r1*r2)/(r1+r2);
41 totr=req+r3;                // total resistance
42 mmf2=phi*totr;
43 mmf2=round(mmf2);
44 disp(sprintf("(b) MMF of the exciting coil when
        permeability is 5000 is %d AT",mmf2));
45
46 //END

```

Scilab code Exa 6.4 Iron ring made of round iron rod

```

1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 4
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 di=10;                                //diameter of iron
10 dr=1.5;                               //diameter of iron
11 mui=900;                             //relative permeability of rod
12 mu0=4*pi*10^(-7);                   //absolute permeability in Henry/m
13 lg=5/10;                            //length of air-gap
14 N=400;                               //number of turns
15 I=3.4;                               //current through the winding in Amperes
16
17 //SOLUTION
18 li=(di*pi)-lg;                      //length of iron path
19 area=((dr^2)*pi)/4;                  //area of iron cross section
20
21 //solution (a)
22 mmf=(4*pi*N*I)/10;                 //in gilberts , since
23 1 AT=(4*pi)/10
23 mmf=round(mmf);                     //to round off the value
24 disp(sprintf("(a) MMF is %d Gilberts",mmf));
25
26 //solution (b)
27 //tot reluctance = iron reluctance + air gap
      reluctance(mur=1 for air)

```

```

28 totR=(li/(area*mu0*mui))+(lg/(area*mu0*1));
29 disp(sprintf("(b) The total reluctance is %E
    Gilberts/Maxwell",totR));
30
31 //solution (c)
32 phi=mmf/totR;
33 disp(sprintf("(c) The flux in the circuit is %f
    Maxwell",phi));
34
35 //solution (d)
36 b=phi/area;
37 disp(sprintf("(d) The flux density in the circuit is
    %f Gauss",b));
38
39 //Answers of (b), (c) & (d) are different because
    absolute permeability is not included in (b)
40
41 //END

```

Scilab code Exa 6.5 Ring made of composite material

```

1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 5
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 li=100/100;                                //length of iron part
    in m
10 ls=200/100;                                //length of steel
    part in m
11 lg=1/100;                                   //length of air gap
    in m

```

```

12 ai=20/10000; //cross-sectional
    area of iron in m^2
13 as=10/10000; //cross-sectional
    area of steel in m^2
14 ag=20/10000; //cross-sectional
    area of air-gap in m^2
15 muRi=300; //relative
    permeability of iron
16 muRs=900; //relative
    permeability of steel
17 muRg=1; //relative
    permeability of air
18 N=170; //number of turns
19 phi=9000*10^(-8); //flux in Wb (1 line
    = 10^(-8) Wb)
20 lkg=1.2; //leakage coefficient
21 mu0=4*pi*10^(-7); //absolute
    permeability in Henry/m
22
23 //SOLUTION
24 rg=lg/(mu0*muRg*ag);
25 mg=rg*phi;
26 mg=round(mg); //to round off the
    value
27 disp(sprintf("MMF of the air gap is %d AT",mg));
28
29 ri=li/(mu0*muRi*ai); //reluctance of iron
    paths
30 mi=lkg*ri*phi; //MMF for iron path
31 mi=round(mi);
32 disp(sprintf("MMF of iron is %d AT",mi));
33
34 rs=ls/(mu0*muRs*as); //reluctance of steel
    paths
35 ms=lkg*rs*phi; //MMF for steel path
36 ms=round(ms);
37 disp(sprintf("MMF of cast steel is %d AT",ms));
38

```

```
39 totMMF=mg+mi+ms;
40 I=totMMF/N;
41 disp(sprintf("Current through the coil is %f A",I));
42
43 //END
```

Chapter 7

Single Phase Transformer

Scilab code Exa 7.1 To calculate magnetizing component of no load current

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 1
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 I_0=10;                                //no load current in
                                           Ampères
10 pf=0.25;                                //power factor
11 v1=400;                                  //in Volts
12 f=50;                                    //in Hertz
13
14 //SOLUTION
15
16 //solution (a)
17 //magnetizing component
18 //Iphi=I0 . sin theta
19 theta=acos(pf);                         //taking value of
                                           theta from the given power factor
```

```

20 I_phi=I_0*sin(theta);
21 disp(sprintf("(a) The magnetizing component of no
      load current is %.2f A",I_phi));
22
23 //solution (b)
24 //iron loss
25 //Pc=V1.Ic
26 //Ic=I0.cos theta & also Ic=I0.pf as pf=cos theta
27 p_c=v1*I_0*pf;
28 disp(sprintf("(b) The iron loss is %d W",p_c));
29
30 //solution (c)
31 N1=500;                                // number of turns in
      primary given
32 phi_m=v1/(sqrt(2)*pi*f*N1);
33 disp(sprintf("(c) The maximum value of flux in the
      core is %.2f mWb",phi_m*1000));
34
35 //END

```

Scilab code Exa 7.2 To calculate the primary current

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 2
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 2");
7 //
8 //400/200V transformer
9 //VARIABLE INITIALIZATION
10 v1=400;                                //primary voltage in
      Volts
11 v2=200;                                //secondary voltage
      in Volts

```

```

12 I0=1;                                //in Amperes
13 pf1=0.4;                             //power factor in
   degrees on no load
14 I2=50;                               //secondary current
   in Amperes
15 pf2=0.8;                             //secondary supplies
   lagging power factor in degrees
16
17 //SOLUTION
18 //primary current is given by
19 //I1=I0+I2
20 //function to convert from polar to rectangular form
21 function [x,y]=pol2rect(mag,angle1);
22 x=mag*cos(angle1);
23 y=mag*sin(angle1);
24 endfunction;
25 //
26 phi_0=acos(pf1);                     // cosine inverse of
   the power factor which is given
27 phi=acos(pf2);                      // cosine inverse of
   the power factor which is given
28 I2_dash=(v2*I2)/v1;                  //v1.i1=v2.i2
29 //I0=1 < phi_0 in polar format
30 [x0,y0]=pol2rect(I0,-phi_0);
31 [x2_dash,y2_dash]=pol2rect(I2_dash,-phi);
32 I1_x=x0+x2_dash;                    //x-component of I1
33 I1_y=y0+y2_dash;                   //y-component of I1
34 disp(sprintf("The primary current in reactangular
   form is (%.3f-j%.2f) A",I1_x,-I1_y));
35 //
36 //function to convert from rectangular form to polar
   form
37 function [I,angle]=rect2pol(x,y);
38 I=sqrt((x^2)+(y^2));
39 angle=atan(y/x)*(180/%pi);        //to convert the
   angle from radians to degrees
40 endfunction;
41 [I,angle]=rect2pol(I1_x,I1_y);      // converting

```

```

        current from rectangular to polar form
42 disp(sprintf("The primary current in polar form is (
    %.3 f <% .2 f) A", I, angle));
43 //END

```

Scilab code Exa 7.3 To find the voltage regulation

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 3
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 3");
7 //
8 //2300/230 V 50 Hz transformer
9 //VARIABLE INITIALIZATION
10 v1=2300;                                //primary
     voltage in Volts
11 v2=230;                                  //secondary
     voltage in Volts
12 f=50;
13 R1=0.286;
14 X1=0.73;
15 R_dash_2=0.319;
16 X_dash_2=0.73;
17 Rc=250;
18 Xphi=1250;
19 Z1=0.387+0.29*i;
20 //
21 //SOLUTION
22 Z_e1=(R1+R_dash_2)+(X1+X_dash_2)*%i;
23 Z_dash_1=(v1/v2)^2*Z1;
24 //
25 I_dash_1=v1/(Z_dash_1+Z_e1);
26 // [mag, angle]=rect2pol( real(I_dash_1), imag(I_dash_1))

```

```

);
27 // disp( sprintf(" The current is %f <%f A" ,mag ,angle
));
28 // impedance of shunt branch
29 Zm=Rc*(Xphi*%i)/(Rc+Xphi*%i);
30 // [mag ,angle]=rect2pol( real(Zm) ,imag(Zm) );
31 // disp( sprintf(" The Zm is %f <%f A" ,mag ,angle));
32 I0=v1/Zm;
33 // [mag ,angle]=rect2pol( real(I0) ,imag(I0) );
34 // disp( sprintf(" The I0 is %f <%f A" ,mag ,angle));
35 //
36 // primary current
37 I1=I0+I_dash_1;
38 function [mag ,angle]=rect2pol(x,y);
39 mag=sqrt((x^2)+(y^2)); //z is impedance &
the resultant of x and y
40 angle=atan(y/x)*(180/%pi); //to convert the
angle from radians to degrees
41 endfunction;
42 [mag ,angle]=rect2pol(real(I1) ,imag(I1));
43 theta1=angle;
44 disp("SOLUTION ( i )");
45 disp(sprintf("The primay current in rectangulr form
is %.3 f -j%.2 f A" ,real(I1) ,-imag(I1)));
46 disp(sprintf("The primay current in polar form is %
.3 f <%.2 f A" ,mag ,angle));
47 //
48 //input power
49 Pin=v1*I1; //=I1 . cos(
theta1)
50 // disp( sprintf(" The input power is %.3 f kW" ,Pin
/1000));
51 //output power
52 V_dash_2=I_dash_1*Z_dash_1;
53 [mag ,angle]=rect2pol( real(V_dash_2) ,imag(V_dash_2));
54 theta2=angle;
55 // disp( sprintf(" The V_dash_2 is %.2 f <%d f A" ,mag ,
angle));

```

```

56 //  

57 Pout= V_dash_2*I_dash_1; // I_dash_1 .  

58 //disp(sprintf("The output power is %.3f kW",real(  

59 // Efficiency  

60 disp("SOLUTION (ii)");  

61 disp(sprintf("The Efficiency is %.2f kW",Pout*100/  

62 // Losses  

63 Pc=v1*I0; // core loss  

64 loss=Pin-Pout;  

65 Pcu=loss-Pc; // copper  

66 loss  

67 disp(sprintf("The core loss is %.2f kW",Pc/1000));  

68 //text book answer is 0.8 kW  

69 disp(sprintf("The copper loss is %.2f kW",Pcu/1000))  

70 //text book answer is 1.38 kW  

71 //efficiency  

72 //eff=Pout*100/Pin;  

73 //disp(sprintf("The percent efficiency is %f W",eff  

74 ));  

75 disp(" ");  

76 // The answers from V_dash_2 calculation onward do  

77 // not match with the book on page 7.21 and 7.22  

78 //END

```

Scilab code Exa 7.4 10 kVA transformer

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER  

2 //Example 4  

3  

4 clc;  

5 disp("CHAPTER 7");  

6 disp("EXAMPLE 4");

```

```

7
8 // 10kVA Transformer with 50 turns on primary and 10
   turns on secondary
9 //connected to 440 V 50Hz supply
10 //VARIABLE INITIALIZATION
11 va=10*1000;                                // apparent power ,
   converting kVA to VA
12 N1=50;                                     //number of turns on
   primary side
13 N2=10;                                     //number of turns on
   secondary side
14 v1=440;                                    //primary voltage in
   Volts
15 f=50;                                      //in Hertz
16
17 //SOLUTION
18
19 //solution (a)
20 //K=N2/N1=V2/V1
21 v2=v1*(N2/N1);
22 disp(sprintf("(a) The secondary voltage on no load
   is %d V",v2));
23
24 //solution (b)
25 //Current on Full load
26 //primary side I1=VA/V1
27 //secondary side I2=VA/V2
28 I1=va/v1;
29 disp(sprintf("(b) The full load primary current is %
   .4f A",I1));
30 I2=va/v2;
31 disp(sprintf("The full load secondary current is %.4
   f A",I2));
32
33 //solution (c)
34 //As per EMF equation
35 //E2=sqrt(2).pi.f.phimax.N2
36 phi_m=v2/(sqrt(2)*%pi*f*N2);

```

```

37 disp(sprintf("(c) The maximum value of the flux is %f mWb", phi_m*1000));
38
39 //END

```

Scilab code Exa 7.5 Transformer with 350 primary and 1050 secondary turns

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 5
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 5");
7
8 //single phase transformer
9 //350 primary and 1050 secondary turns
10 //VARIABLE INITIALIZATION
11 N1=350;                                //number of turns on
                                             primary side
12 N2=1050;                                //number of turns on
                                             secondary side
13 v1=400;                                  //primary voltage in
                                             Volts
14 f=50;                                    //in Hertz
15 ar=50/10000;                            //cross-sectional area
                                             of core in m^2
16
17 //SOLUTION
18
19 //solution (i)
20 //emf1=sqrt(2).pi.f.Phimax.N1
21 //Phimax=Bm.Area, Bm=flux density
22 //Bm=e1/sqrt(2).pi.A.f.N1
23 Bm=v1/(sqrt(2)*%pi*ar*f*N1);
24 disp(sprintf("(i) The maximum flux density is %.4f"))

```

```

    Wb/m^2" , Bm)) ;
25
26 //solution ( ii )
27 //e2/e1=n2/n1=K
28 K=N2/N1;
29 e2=K*v1;
30 disp(sprintf("( ii ) The induced emf in the secondary
   winding is %d V" ,e2));
31
32 //END

```

Scilab code Exa 7.6 Primary current and power factor

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 6
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 6");
7
8 //2200/20V 50Hz single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=2200;                                //primary voltage
   in Volts
11 v2=220;                                   //secondary
   voltage in Volts
12 I=0.6;                                    //exciting
   current in Amperes
13 p_c=361;                                  //core loss in
   Watts
14 I2=60;                                    //load current in
   Amperes
15 pf=0.8;                                   //power factor
16
17 //SOLUTION

```

```

18
19 //solution (a)
20 //core loss components
21 I1=p_c/v1;                                //vertical
22 component of I0
23 I_phi=sqrt((I^2)-(I1^2));                //horizontal
24 component of I0
25 disp(sprintf("(a) The core loss component is %.3f A"
26 ,I1));
27 disp(sprintf("And the magnetising component is %.3f f
28 A" ,I_phi));
29
30 //solution (b)
31 //I1.N1=I2.N2
32 I1_dash=(v2/v1)*I2;
33 theta=acos(pf);
34 I1_x=I1_dash*sin(theta)+I_phi;           //horizontal
35 component of I0
36 I1_y=I1_dash*pf+I1;                     //vertical
37 component of I0
38 I1_res=sqrt((I1_x^2)+(I1_y^2));         //primary current
39 pf_p=I1_y/I1_res;                      //primary power
40 factor
41 disp(sprintf("(b) The primary current is %.3f A",
42 I1_res));
43 disp(sprintf("And the power factor is %.3f f A" ,pf_p))
44 ;
45
46 //END

```

Scilab code Exa 7.8 Efficiency of transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 8
3

```

```

4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 8");
7
8 //23 kVA 2300/230 V 60 Hz step down transformer
9
10 //VARIABLE INITIALIZATION
11 va=23000;                                //apparent power
12 v1=2300;                                   //primary voltage in
                                              Volts
13 v2=230;                                    //secondary voltage
                                              in Volts
14 r1=4;                                       //primary resistance
                                              in Ohms
15 r2=0.04;                                     //secondary
                                              resistance in Ohms
16 X1=12;                                      //leakage reactance
                                              primary in Ohms
17 X2=0.12;                                     //leake reactance in
                                              secondary in Ohms
18 pf=0.866;                                    //power factor(
                                              leading)
19
20 //SOLUTION
21 //assume voltage across load be 230 V
22 //V'1=I2 .( Re2+jXe2 )+V2
23 //Re2=R'1+R2
24 //R'1=R1 .( N2/N1 ) ^2
25 //Xe2=X'1+X2
26 //X'1=X1 .( N2/N1 ) ^2
27 //Ze2=Re2+j .Xe2
28 r1_dash=r1*((v2/v1)^2);
29 r_e2=r1_dash+r2;
30 X1_dash=X1*((v2/v1)^2);
31 X_e2=X1_dash+X2;
32 //
33 //disp( sprintf(" The value of Re2 %f and Xe2 %f" ,r_e2
                                              ,X_e2));

```

```

34 I2=0.75*(va/v2);           //since transformer
   operates at 75% of its rated load
35 //
36 function [x,y]=pol2rect(mag,angle);
37 x=mag*cos(angle*(%pi/180));      //to convert the
   angle from degrees to radians
38 y=mag*sin(angle*(%pi/180));
39 endfunction;
40 [x,y]=pol2rect(I2,-30);
41 I_dash_2=x+y*i;
42 //disp(sprintf("The value %f %f",real(I_dash_2),imag(
   (I_dash_2)));
43 //
44 Z_e2=r_e2+x_e2*i;           //in rect
   coordinates
45 //disp(sprintf("The value %f %f",real(Z_e2),imag(
   (Z_e2)));
46 //
47 V_dash_1=v2+I_dash_2*Z_e2;
48 //disp(sprintf("The value %f %f",real(V_dash_1),imag(
   (V_dash_1)));
49 //
50 function [mag,angle]=rect2pol(x,y);
51 mag=sqrt((x^2)+(y^2));        //z is impedance &
   the resultant of x and y
52 angle=atan(y/x)*(180/%pi);    //to convert the
   angle from radians to degrees
53 endfunction;
54 //
55 [magV1,angleV1]=rect2pol(real(V_dash_1),imag(
   V_dash_1));
56 //disp(sprintf("The value %f <%f",magV1,angleV1));
57 //
58 //Pin=V1.I2.cos theta1
59 //Pout=V2.I2.cos theta2
60 Pin=magV1*I2*cos((30+angleV1)*%pi/180);
61 Pout=v2*I2*cos(30*%pi/180);
62 eff=Pout*100/Pin;

```

```

63 //
64 disp(sprintf("The efficiency of the transformer is %.
65 .2f", eff));
66 //
67 //END

```

Scilab code Exa 7.9 Core loss current of distribution transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 9
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 9");
7
8 //11000/400 V distribution transformer
9 //VARIABLE INITIALIZATION
10 v1=11000;                                //primary voltage in
11          Volts
12 v2=400;                                    //secondary voltage
13          in Volts
14 Io=1;                                       //primary current in
15          Amp
16 pf=0.24;                                    //power factor
17          lagging
18
19 //SOLUTION
20 //core loss current
21 //Ic=Io.cos phi
22 //Ic=Io.pf
23 Ic=Io*pf;
24 disp("SOLUTION ( a )");
25 disp(sprintf("The value of core loss current is %.2f
26 Amp", Ic));

```

```

22 //
23 //magnetizing current
24 //Iphi=sqrt(Io^2-Ic^2)
25 Iphi=sqrt(Io^2-Ic^2);
26 disp("SOLUTION (b)");
27 disp(sprintf("The value of magnetizing current is %.3
f Amp",Iphi));
28 //
29 //Iron Loss
30 //Iron loss=primary voltage X core loss current
31 IronLoss=v1*Ic;
32 disp("SOLUTION (c)");
33 disp(sprintf("The iron loss is %.0 f W",IronLoss));
34 disp(" ");
35 //
36 //END

```

Scilab code Exa 7.10 Number of turns on HT and LT sides

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 10
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 10");
7
8 //6600/220 V single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=6600;                                //primary voltage in
                                              Volts
11 v2=220;                                   //secondary voltage
                                              in Volts
12 coreA=0.05;                               //core section m^2
13 fluxD=1.2;                                //flux density in wbm
                                              /m^2

```

```

14 f=50;                                //Hz
15
16 //SOLUTION
17 //E1=sqrt(2).pi.f.N1. m
18 //flux density = Phimax/core area
19 phiM=coreA*fluxD;
20 N1=v1/(4.44*f*phiM);      //4.44=sqrt(2).pi
21 N1=round(N1);
22 //
23 //N2=N1.E2/E1
24 N2=N1*(v2/v1);
25 N2=round(N2);
26 disp(sprintf("The no. of turns on HT side is %d",N1)
   );
27 disp(sprintf("The no. of turns on LT side is %d",N2)
   );
28 disp("");
29 //
30 //END

```

Scilab code Exa 7.11 To calculate primary and full load currents

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 11
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 11");
7
8 //2200/220 V 44 kVA transformer with 50 turns in the
   secondary
9 //VARIABLE INITIALIZATION
10 va=44000;                         //
11 v1=2200;                           //primary voltage in
   Volts

```

```

12 v2=220;                                //secondary voltage
    in Volts
13 N2=50;                                  //turns in secondary
    coil
14
15 //SOLUTION
16 // N1/N2=V1/V2
17 N1=N2*(v1/v2);
18 disp("SOLUTION (a)");
19 disp(sprintf("The no. of turns on HT side is %f",N1)
      );
20 //
21 //since losses are negligible , input=output , V1.I1=
    V2.I2
22 I1=va/v1;
23 I2=va/v2;
24 disp("SOLUTION (b)");
25 disp(sprintf("The primary full load current is %.0 f
      Amp",I1));
26 disp(sprintf("The secondary full load current is %.0
      f Amp",I2));
27 disp(" ");
28 //
29 //END

```

Scilab code Exa 7.12 Magnetising component of no load current

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 12
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 12");
7
8 //no load cuurent of transformer ia 10A at pf of

```

```

          0.25 lagging when connected to 400V, 50 Hz supply
9 //VARIABLE INITIALIZATION
10 v1=400;                                //primary voltage in
     Volts
11 f=50;                                    //Hz
12 Io=10;                                   //in Amp no load
     current
13 pf =0.25;                                //lagging
14 N1=500;                                   //given
15
16 //SOLUTION
17 //magnetizing component of no load current
18 // N1/N2=V1/V2
19 //Iphi=Io.sin phi0
20 //pf=cos phi0
21 phi0=acos(pf);
22 Iphi=Io*sin(phi0);
23 disp("SOLUTION (a)");
24 disp(sprintf("The magnetic component of no load
     current is %f Amp",Iphi));
25 //
26 //iron loss
27 //Pi=ironloss=power input on no load
28 //Pi=Wo=V1.Io.cos phi0
29 ironLoss=v1*Io*pf;
30 disp("SOLUTION (b)");
31 disp(sprintf("The iron loss on no load is %.0f W",
     ironLoss));
32 //
33 //maximum flux in the core
34 //E1=sqrt(2).pi.f.N1. m
35 //E1=V1
36 phiM=v1/(4.44*f*N1);
37 disp("SOLUTION (c)");
38 disp(sprintf("The value of flux in the core is %5.4f
     mWb",phiM*1000));
39 disp(" ");
40 //

```

41 //END

Scilab code Exa 7.13 Current taken by primary

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 // Example 13
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 13");
7 //230/115 V single phase transformer
8 //VARIABLE INITIALIZATION
9 v1=230;                                //primary voltage
   in Volts
10 v2=115;                                 //Hz
11 f=50;                                    //in Amp no load
12 I0=2;                                     current
13 pf0 =0.28;                               //lagging
14 I2=20;                                    //
15 pf2=0.8;                                 //lagging
16
17 //SOLUTION
18 //
19 //given power factors in primary and secondary
20 // I1.N1=I2.N2
21 phi0=acos(pf0);
22 phi2=acos(pf2);
23 //let Ix and Iy be the components of I0 and I'1
   along X and Y axes
24 //then
25 //Ix=I0.sin phi0 + I'2.sin phi2
26 //
27 //Ix=I0.cos phi0 + I'2.cos phi2
28 I_dash_2=I2*v2/v1;
```

```

29 Ix=Io*sin(phi0)+I_dash_2*sin(phi2);
30 Iy=Io*cos(phi0)+I_dash_2*cos(phi2);
31 I1=sqrt(Ix^2+Iy^2);
32 disp(sprintf("The current taken by primary is %.1f
    Amp", I1));
33 disp("");
34 //
35 //END

```

Scilab code Exa 7.14 To calculate total resistance and reactance referred to primary

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 14
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 14");
7
8 //1100/110 V 22 kVA single phase transformer
9 //VARIABLE INITIALIZATION
10 va=22000;                                // apparent power
11 v1=1100;                                   //primary voltage in
     Volts
12 v2=110;                                    // secondary voltage
     in Volts
13 R1=2;                                       //in Ohms
14 R2=0.02;                                     //in Ohms
15 X1=5;                                       //in Ohms
16 X2=0.045;                                    //in Ohms
17
18 //SOLUTION
19 //N1/N2=v1/v2;
20
21 R_dash_2=R2*((v1/v2)^2);
22 X_dash_2=X2*((v1/v2)^2);

```

```

23 disp("SOLUTION (a)");
24 disp(sprintf("The equivalent resistance of secondary
               referred to primary is %.1f ",R_dash_2));
25 disp(sprintf("The equivalent reactance of secondary
               referred to primary is %.1f ",X_dash_2));
26 //
27 R_e1=R_dash_2+R1;
28 X_e1=X_dash_2+X1;
29 disp("SOLUTION (b)");
30 disp(sprintf("The total resistance referred to
               primary is %.1f ",R_e1));
31 disp(sprintf("The total reactance referred to
               primary is %.1f ",X_e1));
32 //
33 R_dash_1=R1*((v2/v1)^2);
34 X_dash_1=X1*((v2/v1)^2);
35 disp("SOLUTION (c)");
36 disp(sprintf("The equivalent resistance of secondary
               referred to secondary is %.2f ",R_dash_1));
37 disp(sprintf("The equivalent reactance of secondary
               referred to secondary is %.2f ",X_dash_1));
38 //
39 R_e2=R_dash_1+R2;
40 X_e2=X_dash_1+X2;
41 disp("SOLUTION (d)");
42 disp(sprintf("The total resistance referred to
               secondary is %.3f ",R_e2));
43 disp(sprintf("The total reactance referred to
               secondary is %.3f ",X_e2));
44 //
45 I1=va/v1;
46 I2=va/v2;
47 copperLoss=R1*I1^2+R2*I2^2;
48 disp("SOLUTION (e)");
49 disp(sprintf("The total copper loss is %4.0f W",
               copperLoss));
50 disp(" ");
51 //

```

52 //END

Scilab code Exa 7.15 To calculate percent regulation at full load

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 15
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 15");
7 //20kVA single phase transformer
8 //VARIABLE INITIALIZATION
9 va=20000;                                // apparent power
10 v1=2000;                                   // primary voltage
11 v2=200;                                    // secondary voltage
12 R1=2.5;                                    // in Ohms
13 R2=0.04;                                   // in Ohms
14 X1=8;                                      // in Ohms
15 X2=0.07;                                   // in Ohms
16 pf2=0.8;
17
18 //SOLUTION
19 //N1b/N2=v1/v2;
20 I2=va/v2;
21 phi2=acos(pf2);
22 //
23 R_dash_1=R1*((v2/v1)^2);
24 X_dash_1=X1*((v2/v1)^2);
25 //
26 R_e2=R_dash_1+R2;
27 X_e2=X_dash_1+X2;
28 //disp(sprintf("The total resistance referred to
      secondary is %f    ",R_e2));
```

```

29 // disp(sprintf("The total reactance referred to
    secondary is %f    ",X_e2));
30 //
31 //R=ercosphi2+vx.sinphi2
32 //E2=V2+I2 .R
33 V2=v2-(I2*R_e2*pf2+I2*X_e2*sin(phi2));
34 %reg=(v2-V2)*100/v2;
35 disp(sprintf("The secondary terminal voltage is %.2f
    V",V2));
36 disp(sprintf("The percent regulation at full load is
    %.2f",%reg));
37 disp("");
38 //
39 //END

```

Scilab code Exa 7.16 Maximum value of percent regulation

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 16
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 16");
7
8 //Values from the previous example.
9 //VARIABLE INITIALIZATION
10 va=20000;                                // apparent power
11 v1=2000;                                   // primary voltage
12 v2=200;                                    // secondary voltage
13 R1=2.5;                                     // in Ohms
14 R2=0.04;                                    // in Ohms
15 X1=8;                                       // in Ohms
16 X2=0.07;                                    // in Ohms

```

```

17 pf2=0.8;
18
19 //SOLUTION
20 //N1/N2=v1/v2;
21 I2=va/v2;
22 phi2=acos(pf2);
23
24 //
25 R_dash_1=R1*((v2/v1)^2);
26 X_dash_1=X1*((v2/v1)^2);
27 //
28 R_e2=R_dash_1+R2;
29 X_e2=X_dash_1+X2;
30 //disp(sprintf("The total resistance referred to
secondary is %f ",R_e2));
31 //disp(sprintf("The total reactance referred to
secondary is %f ",X_e2));
32 //
33 //power factor angle at which regulation is zero is
given by tan.phi2=-Re2/Xe2
34 phi2=atan(-R_e2/X_e2);
35 disp(sprintf("The PF at which the regulation is zero
is %.3f",cos(phi2)));
36 //
37 //power factor angle at which regulation is maximum
is given by tan.phi2=Xe2/Re2
38 phi2=atan(X_e2/R_e2);
39 disp(sprintf("The PF at which the regulation is
maximum is %.3f",cos(phi2)));
40 //R=rcosphi2+vx.sinphi2
41 //E2=V2+I2.R
42
43 V2=v2-(I2*R_e2*cos(phi2)+I2*X_e2*sin(phi2));
44 %reg=(v2-V2)*100/v2;
45 disp(sprintf("The maximum value of percent
regulation is %.2f ",%reg));
46 disp("");
47 //

```

48 //END

Scilab code Exa 7.17 200 kVA transformer with 1000 W iron loss and 2000 W copper loss

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 // Example 17
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 17");
7
8 //200kVA single phase transformer
9 //VARIABLE INITIALIZATION
10 va=200000;                                //
11 ironLoss=1000;                             // Watts
12 cuLoss=2000;                              //Watts
13 pf=0.8;
14 //
15 //SOLUTION
16 //
17 Pout=va*pf;                               // Full load output
18 loss=ironLoss+cuLoss;
19 Pin=Pout+loss;                            //INPUT=OUTPUT+LOSS
20 eff=Pout*100/Pin;
21 disp("SOLUTION (a)");
22 disp(sprintf("The percent efficiency at full load is
% .2f",eff));
23 //
24 //at half load
25 Pout=va*pf/2;
26 loss=ironLoss+cuLoss*(1/2)^2;           // ironloss is
                                             independent of output
27 Pin=Pout+loss;
28 eff=Pout*100/Pin;
29 disp("SOLUTION (b)");
```

```

30 disp(sprintf("The percent efficiency at full load is
31     %.2f",eff));
32 // fraction x of copperloss=ironloss for maximum
33 // efficiency
34 x=sqrt(ironLoss/cuLoss);
35 Pout=x*va*pf;
36 loss=ironLoss+cuLoss*x^2;
37 Pin=Pout+loss;
38 eff=Pout*100/Pin;
39 disp("SOLUTION (c)");
40 disp(sprintf("The percent efficiency at %f load is %
41     %.2f",x,eff));
42 disp("");
43 //
44 //END

```

Scilab code Exa 7.18 To calculate all day efficiency

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 18
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 18");
7
8 // 400kVA distribution transformer variously loaded
8 // during day
9 //VARIABLE INITIALIZATION
10 va=400000;                                //
11 ironLoss=1500;                             // Watts
12 cuLoss=4000;                               //Watts
13 //during the day frommidnight to midnight is as

```

```

        below :
14 h1=6;                                // first 6 hours from
      midnight to 6 hrs
15 load1=0;
16 pf1=0;
17 h2=6;                                // next 6 hours from
      6 am to noon
18 load2=100000;                         //kVA converted to
      VA
19 pf2=0.8;
20 h3=5;                                // next from noon to
      5 pm
21 load3=400000;
22 pf3=0.8;
23 h4=3;                                // next from 5 pm to
      8 pm
24 load4=300000;
25 pf4=0.7;
26 h5=4;                                // next from 8 pm to
      midnight
27 load5=200000;
28 pf5=0.85;
29 //
30 //SOLUTION
31 //
32 //energy loss at any load=(VA output/VA rated)^2 .
      Full load cuLoss
33 loss1=h1*load1;
34 loss2=h2*(load2/va)^2*cuLoss;
35 loss3=h3*(load3/va)^2*cuLoss;
36 loss4=h4*(load4/va)^2*cuLoss;
37 loss5=h5*(load5/va)^2*cuLoss;
38 //loss in 24 hours
39 loss24=loss1+loss2+loss3+loss4+loss5;
40 //disp(sprintf("The all day loss is %f ",loss24));
41 Pout=h1*load1*pf1+h2*load2*pf2+h3*load3*pf3+h4*load4
      *pf4+h5*load5*pf5;
42 //disp(sprintf("The all day energy output is %f ",

```

```

        Pout));
43 Pin=Pout+ironLoss*24+loss24;
44 eff=Pout*100/Pin;
45 disp(sprintf("The all day percent efficiency is %.2f
",eff));
46 disp("");
47 //
48 //END

```

Scilab code Exa 7.19 Open circuit and short circuit test

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 19
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 19");
7
8 //Open circuit and short circuit test on 10 kVA
     transformer 500/250 V 50 Hz single phase
     transformer
9 //VARIABLE INITIALIZATION
10 va=10000;                                //apparent power
11 v1=500;                                    //primary
     voltage in Volts
12 v2=250;                                    //secondary
     voltage in Volts
13 f=50;
14 //open circuit parameters
15 Voc=500;
16 Io=2;
17 Wi=100;                                     // watts HT side
18 Woc=Wi;                                    //just another
     nomenclature
19 //short circuit test

```

```

20 Vsc=25;
21 Isc=20;
22 Wc=90; // watts HT side
23 //
24 pf=0.8;
25 //SOLUTION
26 //open circuit
27 phi0=acos(Woc/(v1*Io));
28 Ic=Io*cos(phi0);
29 Iphi=Io*sin(phi0);
30 Rc=v1/Ic;
31 X=v1/Iphi;
32 disp("SOLUTION (a)");
33 disp(sprintf("The value of Ic is %.2f Amp",Ic));
34 disp(sprintf("The value of Iphi is %.2f Amp",Iphi));
35 disp(sprintf("The value of Rc is %.0f Ohm",Rc));
36 disp(sprintf("The value of X is %.0f ",X));
37 //
38 //short circuit
39 phisc=acos(Wc/(Vsc*Isc));
40 pf1=cos(phisc);
41 R_e1=Vsc*pf1/Isc;
42 Z_e1=Vsc/Isc;
43 X_e1=sqrt(Z_e1^2-R_e1^2);
44 disp(sprintf("The value of Power factor is %.3f",pf1));
45 disp(sprintf("The value of Re1 is %.3f Ohm",R_e1));
46 disp(sprintf("The value of Ze1 is %.3f Ohm",Z_e1));
47 disp(sprintf("The value of Xe1 is %.3f ",X_e1));
48 //
49 //Regulation and efficiency
50 // Regulation
51 I1=va/v1;
52 phi=acos(pf);
53 //R=ercosphi2+vx.sinphi2
54 //E2=V2+I2.R
55 %reg=(Isc*R_e1*pf+Isc*X_e1*sin(phi))*100/v1;
56 disp("SOLUTION (c(i))");

```

```

57 disp(sprintf("The percent regulation at full load is
58     %.2f",%reg));
59 // 
60 // Efficiency
61 // full load output at pf=0.8
62 Pout=va*pf;
63 ironLoss=Wi;
64 cuLoss=Wc;
65 loss=ironLoss+cuLoss;
66 Pin=Pout+loss;
67 eff=Pout*100/Pin;
68 disp("SOLUTION (c(i))");
69 disp(sprintf("The percent efficiency at full load is
70     %.2f",eff));
71 disp("");
72 // 
73 //END

```

Scilab code Exa 7.20 4kVA 200 400 V transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 20
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 20");
7
8 //4 kVA 200/400 V 50 hz single phase transformer
9 //VARIABLE INITIALIZATION
10 va=4000;                                //apparent power
11 v1=200;                                   //primary
12 v2=400;                                   //secondary
13 f=50;                                     voltage in Volts

```

```

14 R_e1=0.15;
15 Pi=60;                                //core losses
16 pf1=0.9;                               //power factor
17 pf2=0.8;                               //power factor
18
19 //SOLUTION
20 //Copper loss on full load
21 R_e2=(v2/v1)^2*R_e1;
22 I1=va/v1;
23 I2=va/v2;
24 Pcu=I2^2*R_e2;                         //cu losses
25 disp("SOLUTION ( i )");
26 disp(sprintf("The value of Copper Losses at full
load is %.0f W",Pcu));
27 //
28 //efficiency
29 Pout=va*pf1;
30 Pin=Pout+Pi+Pcu;
31 eff=Pout*100/Pin;
32 disp("SOLUTION ( ii )");
33 disp(sprintf("The percent efficiency at full load %f
PF is %.2f",pf1,eff));
34 //
35 //
36 //efficiency at half load
37 Pout=va*pf2/2;
38 Pin=Pout+Pi+Pcu*(1/2)^2;
39 eff=Pout*100/Pin;
40 disp("SOLUTION ( ii )");
41 disp(sprintf("The percent efficiency at half load %f
PF is %.2f",pf2,eff));
42
43 disp(" ");
44 //
45 //END

```

Scilab code Exa 7.21 To determine the regulation while supplying full load

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 21
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 21");
7
8 //250/125 V 5kVA single phase transformer
9 //VARIABLE INITIALIZATION
10 va=5000;                                //apparent power
11 v1=250;                                   //primary
   voltage in Volts
12 v2=125;                                   //secondary
   voltage in Volts
13 R1=0.2;                                    //resistance of
   primary
14 X1=0.75;                                  //leakage
   reactance of primary
15 R2=0.05;                                  //resistance of
   secondary
16 X2=0.2;                                   //leakage
   reactance of secondary
17 pf=0.8;                                    //power factor (
   leading)
18
19 //SOLUTION
20 R_e2=(v2/v1)^2*R1+R2;
21 X_e2=(v2/v1)^2*X1+X2;
22 I1=va/v1;
23 I2=va/v2;
24 //
25 //at full load leading
```

```

26 phi=acos(pf);
27 %reg=(I2*R_e2*pf-I2*X_e2*sin(phi))*100/v2;
28 disp("SOLUTION ( i )");
29 disp(sprintf("The percent regulation at full load is
    %.2f",%reg));
30 //
31 //R=(E2-V2).100/E2
32 V2=v2-%reg*v2/100;
33 disp("SOLUTION ( ii )");
34 disp(sprintf("The secondary terminal voltage at full
    load is %.2f V",V2));
35 disp(" ");
36 //
37 //END

```

Scilab code Exa 7.22 Total equivalent resistance referred to primary and secondary

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 22
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 22");
7
8 //6600/400 V single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=6600;                                //primary
     voltage in Volts
11 v2=400;                                  //secondary
     voltage in Volts
12 R1=2.5;                                  //primary
     resistance
13 R2=0.01;                                 //secondary
     resistance
14

```

```

15 //SOLUTION
16 //while finding equivalent resistance referrd to
   primary
17 //transfer R2 resistance to R'2
18 R_dash_2=R2*(v1/v2)^2;
19 R_e1=R1+R_dash_2;
20 //
21 //to find total equivalent resistance referred to
   secondary
22 //first calculate R'1
23 R_dash_1=R1*(v2/v1)^2;
24 R_e2=R2+R_dash_1;
25 //
26 disp(sprintf("The total equivalent resistance
   referred to primary is %.6f ",R_e1));
27 disp(sprintf("The total equivalent resistance
   referred to secondary is %.6f ",R_e2));
28 disp("");
29 //
30 //END

```

Scilab code Exa 7.23 33 kVA 2200 220 V 50 Hz transformer

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 23
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 23");
7
8 //33kVA 2200/220 V 50Hz single phase transformer
9 //VARIABLE INITIALIZATION
10 va=33000;
11 v1=2200;                                //primary
   voltage in Volts

```

```

12 v2=220;                                //secondary
    voltage in Volts
13 f=50;                                    // frequency in
    Hz
14 R1=2.4;                                  //primary
    winding (High Voltage side) resistance
15 X1=6;                                    //primary
    winding (High Voltage side) leakage reactance
16 R2=0.03;                                 //secondary
    winding (Low Voltage side) resistance
17 X2=0.07;                                 //secondary
    winding (Low Voltage side) leakage reactance
18
19 //SOLUTION
20 //
21 //Primary resistance and leakage reactance referred
    to secondary
22 //R'1 & X'1
23 //Secondary resistance and leakage reactance
    referred to primary
24 //R'2 & X'2
25 //Equivalent resistance & leakage reactance referred
    to primary
26 //Re1 & Xe1
27 //Equivalent resistance & leakage reactance referred
    to secondary
28 //Re2 & Xe2
29 //
30 R_dash_2=R2*(v1/v2)^2;
31 R_e1=R1+R_dash_2;
32 X_dash_2=X2*(v1/v2)^2;
33 X_e1=X1+X_dash_2;
34 //
35 R_dash_1=R1*(v2/v1)^2;
36 R_e2=R2+R_dash_1;
37 X_dash_1=X1*(v2/v1)^2;
38 X_e2=X2+X_dash_1;
39

```

```

40 disp("SOLUTION (a)");
41 disp(sprintf("The primary resistance referred to
        secondary %.2f    ",R_dash_1));
42 disp(sprintf("The primary leakage reactance referred
        to secondary %.2f    ",X_dash_1));
43 //
44 disp("SOLUTION (b)");
45 disp(sprintf("The secondary resistance referred to
        secondary %.2f    ",R_dash_2));
46 disp(sprintf("The secondary leakage reactance
        referred to secondary %.2f    ",X_dash_2));
47 //
48 disp("SOLUTION (C(i))");
49 disp(sprintf("The equivalent resistance referred to
        primary %.2f    ",R_e1));
50 disp(sprintf("The equivalent leakage reactance
        referred to primary %.2f    ",X_e1));
51 //
52 disp("SOLUTION (C(ii))");
53 disp(sprintf("The equivalent resistance referred to
        secondaryy %.2f    ",R_e2));
54 disp(sprintf("The equivalent leakage reactance
        referred to secondary %.2f    ",X_e2));
55 //
56 //Ohmic load
57 I1=va/v1;                      // primary full load
      current
58 I2=va/v2;                      // secondary full load
      current
59 oLoss=I2^2*R_e2;                //ohmic loss
60 disp("SOLUTION (d)");
61 disp(sprintf("The ohmic loss at full load %.0f W",
        oLoss));
62 //
63 //Voltage to be applied on the HV side
64 //to obtain short circuit currnet of 160 A in L.V
      side winding
65 Z_e1=sqrt(R_e1^2+X_e1^2);          //

```

```

        equivalent leakage impedance
66 // voltage to be applied on HV side is equivalent
    leakage reactance x primary current
67 // relationship between current and voltage in
    transformer
68 //I1/I2=V2/V1
69 //Given V2=220 V, V1=2200 V, I2=160 Amp
70 //Therefore , I1=I2 .(V2/V1)
71 I1=160*(v2/v1) ;
72 V=I1*Z_e1;                                // 160*(v2/v1)*Z_e1 ;
73 //Power Input
74 P=(I1)^2*R_e1                            //P=I ^ 2.R
75 disp("SOLUTION ( e )");
76 disp(sprintf("The voltage to be applied on HV side
    is %.2f V",V));
77 disp(sprintf("The power input is %.1f W",P));
78 disp(" ");
79 //
80 //END

```

Scilab code Exa 7.24 To calculate secondary terminal voltage

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 24
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 24");
7
8 //10kVA 2500/250 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=10000;
11 v1=2500;                                     // primary
    voltage in Volts
12 v2=250;                                       // secondary

```

```

        voltage in Volts
13 R1=4.8;                                // primary HV
      side winding resistance
14 X1=11.2;                                // primary HV
      side winding leakage reactance
15 R2=0.048;                               // secondary LV
      side winding resistance
16 X2=0.112;                               // secondary LV
      side winding leakage reactaance
17
18 //SOLUTION
19 //
20 //Primary resistance and leakage reactance referred
      to secondary
21 //R'1 & X'1
22 //Secondary resistance and leakage reactance
      referred to primary
23 //R'2 & X'2
24 //Equivalent resistance & leakage reactance referred
      to primary
25 //Re1 & Xe1
26 //Equivalent resistance & leakage reactance referred
      to secondary
27 //Re2 & Xe2
28 //
29 R_dash_2=R2*(v1/v2)^2;
30 R_e1=R1+R_dash_2;
31 X_dash_2=X2*(v1/v2)^2;
32 X_e1=X1+X_dash_2;
33 //
34 R_dash_1=R1*(v2/v1)^2;
35 R_e2=R2+R_dash_1;
36 X_dash_1=X1*(v2/v1)^2;
37 X_e2=X2+X_dash_1;
38 //leakage impedance
39 //The transformer leakage impedance=z0=Re2+j . Xe2
40 //Therefore:
41 z0=R_e2+X_e2*%i;

```

```

42 //Further Given
43 //the LV winding side is connected to load impedance
44 //of 5+j.3.5 Ohm
45 //The power factor 0.8 lagging on LV side
46 //applied load is
47 Z1=5+3.5*j;
48 //total impedance in series
49 //The leakage impedance and load impedance are in
50 //series , therefore , total impedance is sum of the
51 //two
52 //Z=z0+Z1;
53 magZ=sqrt(real(Z)^2+imag(Z)^2);
54 magZ1=sqrt(real(Z1)^2+imag(Z1)^2);
55 //V2=I2.Z1
56 I2=v2/magZ;
57 V2=I2*magZ1
58 disp("SOLUTION (a)");
59 disp(sprintf("The secondary terminal voltage is %.0f
      V",V2));
60 disp("");
61 //
62 //END

```

Scilab code Exa 7.25 15 kVA 2200 110 V transformer

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 25
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 25");

```

```

7
8 //15kVA 2200/110 V transformer
9 //VARIABLE INITIALIZATION
10 va=25000;                                //power rating
11 v1=2200;                                  //primary
12           voltage in Volts
13 v2=110;                                    //secondary
14           voltage in Volts
15 f=50;
16 R1=1.75;
17 X1=2.6;
18 R2=0.0045;
19 X2=0.0075;
20
21 //SOLUTION
22 //
23 //Primary resistance and leakage reactance referred
24      to secondary
25 //R'1 & X'1
26 //Secondary resistance and leakage reactance
27      referred to primary
28 //R'2 & X'2
29 //Equivalent resistance & leakage reactance referred
30      to primary
31 //Re1 & Xe1
32 //Equivalent resistance & leakage reactance referred
33      to secondary
34 //Re2 & Xe2
35 //
36 R_dash_2=R2*(v1/v2)^2;
37 R_e1=R1+R_dash_2;
38 X_dash_2=X2*(v1/v2)^2;
39 X_e1=X1+X_dash_2;
40 //
41 R_dash_1=R1*(v2/v1)^2;
42 R_e2=R2+R_dash_1;
43 X_dash_1=X1*(v2/v1)^2;
44 X_e2=X2+X_dash_1;

```

```

39 // 
40 Z_e1=R_e1+X_e1*%i;
41 Z_e2=R_e2+X_e2*%i;
42 magZ_e1=sqrt(real(Z_e1)^2+imag(Z_e1)^2);
43 magZ_e2=sqrt(real(Z_e2)^2+imag(Z_e2)^2);
44 //
45 //
46 disp("SOLUTION (a)");
47 disp(sprintf("The equivalent resistance referred to
primary %.2f ",R_e1));
48 disp("SOLUTION (b)");
49 disp(sprintf("The equivalent resistance referred to
secondaryy %.5f ",R_e2));
50 disp("SOLUTION (c)");
51 disp(sprintf("The equivalent leakage reactance
referred to primary %.1f ",X_e1));
52 disp("SOLUTION (d)");
53 disp(sprintf("The equivalent leakage reactance
referred to secondary %.3f ",X_e2));
54 disp("SOLUTION (e)");
55 disp(sprintf("The equivalent impedance referred to
primary %.5f ",magZ_e1));
56 disp("SOLUTION (f)");
57 disp(sprintf("The equivalent impedance referred to
secondary %.5f ",magZ_e2));
58 //
59 //primary and secondary full load current and
//voltage relationship with power rating
60 I1=va/v1;           //primary current
61 I2=va/v2;           //secondary current
62 cuLoss=I2^2*R_e2;   //copper loss      or also as I1
^2.R1 + I2 ^ 2.R2
63 disp("SOLUTION (d)");
64 disp(sprintf("The copper loss at full load %f W",
cuLoss));
65 disp(" ");
66 //
67 //END

```

Scilab code Exa 7.26 Open circuit and short circuit test

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 26
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 26");
7
8 //open circuit & short circuit test
9 //10 kVA 500/250 V 50 Hz single phase
10 //VARIABLE INITIALIZATION
11 va=10000;                                //apparent power
12 v1=500;                                    //primary
13 voltage in Volts
14 v2=250;                                    //secondary
15 voltage in Volts
16 f=50;                                       // frequency
17 //open circuit parameters
18 Voc=500;
19 Io=2;
20 Wi=100;                                     // watts HT side
21 Woc=Wi;                                     //just to keep
22 symbology
23 //short circuit test
24 Vsc=25;
25 Isc=20;
26 Wc=90;                                       // watts HT side
27 //
28 pf=0.8;
29 //SOLUTION
30 //open circuit
31 phi0=acos(Woc/(v1*Io));
32 Ic=Io*cos(phi0);
```

```

30 Iphi=Io*sin(phi0);
31 Rc=v1/Ic;
32 X=v1/Iphi;
33 disp("SOLUTION (a)");
34 disp(sprintf("The value of Ic is %.2f Amp",Ic));
35 disp(sprintf("The value of I is %.2f Amp",Iphi));
36 disp(sprintf("The value of Rc is %.2f Ohm",Rc));
37 disp(sprintf("The value of X is %.2f ",X));
38 //
39 //short circuit
40 phisc=acos(Wc/(Vsc*Isc));
41 pf1=cos(phisc);
42 R_e1=Vsc*pf1/Isc;
43 Z_e1=Vsc/Isc;
44 X_e1=sqrt(Z_e1^2-R_e1^2);
45 disp(sprintf("The value of Power factor is %f",pf1))
;
46 disp(sprintf("The value of Re1 is %f Ohm",R_e1));
47 disp(sprintf("The value of Ze1 is %f Ohm",Z_e1));
48 disp(sprintf("The value of Xe1 is %f ",X_e1));
49 //
50 I1=va/v1;
51 phi=acos(pf);
52 //R=er.cos phi2+vx.sin phi2
53 //E2=V2+I2.R
54 %reg=(Isc*R_e1*pf+Isc*X_e1*sin(phi))*100/v1;
55 disp("SOLUTION (c(i))");
56 disp(sprintf("The percent regulation at full load is
%.2f",%reg));
57 //
58 //full load output at pf=0.8
59 Pout=va*pf; // Output Power
60 ironLoss=Wi;
61 cuLoss=Wc;
62 loss=ironLoss+cuLoss;
63 Pin=Pout+loss; // Input Power
64 eff=Pout*100/Pin; // efficiency
65 disp("SOLUTION (c(ii))");

```

```

66 disp(sprintf("The percent efficiency at full load is
67 %f",eff));
68 //
69 //END

```

Scilab code Exa 7.27 Open and short circuit test

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 27
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 27");
7
8 //200kVA 1100/400 V delta star distribution
   transformer
9 //three phase
10 //VARIABLE INITIALIZATION
11 va=200000;                                // apparent
   power
12 v1=11000;                                  // primary
   voltage in Volts
13 v2=400;                                    // secondary
   voltage in Volts
14 f=50;                                       // frequency
15 //open circuit test parameters
16 V3=400;
17 I3=9;
18 W3=1500;                                   //load in watts
   HT side
19 //short circuit test parameters
20 Vsc=350;
21 Isc=20;
22 Wc=2100;                                   //load in watts

```

```

        HT side
23 // 
24 pf=0.8;
25 //SOLUTION
26 Voc=V3/sqrt(3);                                // per phase
    applied voltage in open circuit
27 Io=9;                                         // per phase
    exciting current.= I3
28 Wi=W3/3;                                       // per phase
    core loss in watts HT side
29 Pc=Wi;                                         //core losses
30 //power factor Pc=V1.Io.cos phi0 //v1=Voc
31 //open circuit test performed on LV side
32 phi0=acos(Wi/(Voc*Io));
33 Ic=Io*cos(phi0);                               //core loss
    current
34 Iphi=Io*sin(phi0);                            //magnetising
    current
35 Rc=Voc/Ic;                                     //Core loss
    resistance
36 X=Voc/Iphi;                                    //
37 disp("SOLUTION ( a )");
38 disp(sprintf("The value of Ic is %.0f Amp",Ic));
39 disp(sprintf("The value of I   is %.2f Amp",Iphi));
40 disp(sprintf("The value of Rc is %.2f Ohm",Rc));
41 disp(sprintf("The value of X is %.2f ",X));
42 //
43 //core loss resistance referred to hv side
44 Rch=Rc*(v1/Voc)^2;
45 XphiH=X*(v1/Voc)^2;
46 disp(sprintf("The value of Rch is %.2f k  ",Rch
    /1000));
47 disp(sprintf("The value of X h is %.2f K  ",XphiH
    /1000));
48 //short circuit
49 //This test performed on HV side
50 //first find rated current
51 Isc=va/(3*v1);

```

```

52 Psc=Wc/3;                                //ohmic loss per
      phase
53 phisc=acos(Wc/(Vsc*Isc));
54 pf1=cos(phisc);
55 R_e1=Psc/Isc^2;
56 Z_e1=Vsc/Isc;
57 X_e1=sqrt(Z_e1^2-R_e1^2);
58 disp(sprintf("The value of ohmic loss per phase is %
.0f W",Psc));
59 disp(sprintf("The value of Re1 is %.2f Ohm",R_e1));
60 disp(sprintf("The value of Ze1 is %.2f Ohm",Z_e1));
61 disp(sprintf("The value of Xe1 is %.2f ",X_e1));
62 //
63 //efficiency at half load
64 pf=1;                                     //unity
      power factor
65 Pout=(va/3)*(1/2)*pf;
66 //core losses=Pc
67 //cuLosses ohmic loss =Psc
68 Pin=Pout+Pc+(1/2)^2*Psc;
69 eff=Pout*100/Pin;
70 disp(sprintf("The efficiency at half load is %.2f",
    eff));
71
72 disp("");
73 //
74 //END

```

Scilab code Exa 7.28 Open and short circuit test

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 28
3
4 clc;
5 disp("CHAPTER 7");

```

```

6 disp("EXAMPLE 28");
7
8 //10 kVA 2500/250 V single phase transformer
9 //open circuit and short circuit tests
10 //VARIABLE INITIALIZATION
11 va=10000;                                // apparent
12 v1=2500;                                  // primary
13 v2=250;                                   // secondary
14 f=50;
15 //open circuit parameters
16 Voc=250;
17 Io=0.8;
18 Wi=50;                                    // watts HT
19 //short circuit test
20 Vsc=60;
21 Isc=3;
22 Wc=45;                                    // watts HT side
23 //
24 //loads
25 pf=0.8;
26 //SOLUTION
27 //Open circuit test conducted on lv because 250 V
28      during this test is equal to rated voltage on lv
29      side.
30 I1=va/v1;                                // full rated
31      current on hv side
32 Psc0=Wc*(I1/Isc)^2;                      //ohmic loss/
33      cu loss at full load rated current
34 Pc=Wi;                                    // core losses
35 // 1/4 load
36 Psc=(1/4)^2*Psc0;
37 Pout=va*pf*(1/4);
38 Pin=Pout+Pc+Psc;
39 eff=Pout*100/Pin;

```

```

36 disp("SOLUTION (a)");
37 disp(sprintf("The efficiency at 1/4 load is %.2f",
   eff));
38 //
39 // 1/2 load
40 Psc=(1/2)^2*Psc0;
41 Pout=va*pf*(1/2);
42 Pin=Pout+Pc+Psc;
43 eff=Pout*100/Pin;
44 disp(sprintf("The efficiency at 1/2 load is %.2f",
   eff));
45 //
46 // full load
47 Psc=(1/1)^2*Psc0;
48 Pout=va*pf*(1/1);
49 Pin=Pout+Pc+Psc;
50 eff=Pout*100/Pin;
51 disp(sprintf("The efficiency at full load is %.2f",
   eff));
52 //
53 // 1 1/4 = 5/4 load
54 Psc=(5/4)^2*Psc0;
55 Pout=va*pf*(5/4);
56 Pin=Pout+Pc+Psc;
57 eff=Pout*100/Pin;
58 disp(sprintf("The efficiency at 1 1/4 or 5/4 load is
   %.2f",eff));
59 //
60 //maximum efficiency at x, but then ohmic loss=core
   loss
61 x=sqrt(Pc/Psc0);
62 Pout=va*x*pf;
63 Pin=Pout+Pc+Psc;                                //Ohmic
   losses = core losses at max efficiency
64 eff=Pout*100/Pin;
65 disp("SOLUTION (b)");
66 disp(sprintf("The maximum efficiency is %.2f",eff))
   ;

```

```

67 //
68 //short circuit test performed on lv side
69 phisc=acos(Wc/(Vsc*Isc));
70 pf1=cos(phisc);
71 R_e1=Vsc*pf1/Isc;
72 Z_e1=Vsc/Isc;
73 X_e1=sqrt(Z_e1^2-R_e1^2);
74 disp("SOLUTION (c)");
75 disp(sprintf("The value of Re1 is %.2f Ohm",R_e1));
76 disp(sprintf("The value of Ze1 is %.2f Ohm",Z_e1));
77 disp(sprintf("The value of Xe1 is %.2f ",X_e1));
78 //
79 //ee , ex;
80 er=I1*R_e1/v1;
81 ex=I1*X_e1/v1;
82 disp(sprintf("The value of Er is %.3f pu",er));
83 disp(sprintf("The value of Ex is %.3f",ex));
84 //
85 phi=acos(pf);
86 //R=ercosphi2+vx.sinphi2
87 //E2=V2+I2.R
88 %reg=(I1*R_e1*pf+I1*X_e1*sin(phi))*100/v1; //same as
     using er and ex
89 disp(sprintf("The percent regulation at full load
     lagging is %.2f",%reg));
90 %reg1=(I1*R_e1*pf-I1*X_e1*sin(phi))*100/v1; //same
     as using er and ex
91 disp(sprintf("The percent regulation at full load
     leading is %.2f",%reg1));
92 V21=(1-%reg/100)*v2;
93 V22=(1-%reg1/100)*v2;
94 disp(sprintf("The secondary terminal voltage at full
     load lagging is %.2f",V21));
95 disp(sprintf("The secondary terminal voltage at full
     load leading is %.2f",V22));
96 disp("");
97 //
98 //END

```

Scilab code Exa 7.29 200 kVA 4000 1000 V transformer

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 29
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 29");
7
8 //20kVA 4000/1000 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=200000;                                // apparent
11 v1=4000;                                    // primary
12 v2=1000;                                    // secondary
13 f=50;                                       // frequency
14 //loads
15 pf=1;                                       // power
16 factor is unity
16 eff=0.97;                                  // at full
16 load and at 60% of full load
17 nlpf=0.5;                                  //no load pf
18 lpf=0.8;                                    //lagging pf
19 reg=0.05;                                   //
19 %regulation at 0.8 pf
20 //
21 //SOLUTION
22 loss=(1-eff)*va/eff;                         // =Pc+Pcu
22 losses
23 //simultaneous equation to be solved
24 //eq 1: Pc+Pcu=loss;
```

```

25 // fraction of copper/ ohmic losses
26 f=(0.6)^2;                                // 60% of
     full load
27 //the 2nd equation is  $P_c + f * P_{cu} = \text{loss}$ 
28 //now the matrix
29 M=[1,1,1,f];
30 A=[loss,loss*0.6];
31 Mi=inv(M);
32 Ans=A*inv(M);
33 Pc=Ans(1,1);
34 Pcu=Ans(1,2);
35 //disp(sprintf("The Pc is %f",Pc));
36 //disp(sprintf("The Pcu is %f",Pcu));
37 //LV side
38 Re2=Pcu/va;
39 //from %reg find Xe2
40 phi=acos(lpf);
41 Xe2=(reg-Re2*cos(phi))/sin(phi);
42 // in oms units
43 Re2=Re2*v22/va;                  // in ohms
44 Xe2=Xe2*v22/va;                  // in ohms
45 disp(sprintf("The Re2 is %.3f      ",Re2));
46 disp(sprintf("The Xe2 is %.3f      ",Xe2));
47 //
48 Rc=v22/Pc;
49 Ie2=Pc/(v2*0.25);
50 Ic=Pc/v2;
51 Iphi=sqrt(Ie22-Ic2);
52 Xphi=v2/Iphi;
53 disp(sprintf("The Rc is %.2f      ",Rc));
54 disp(sprintf("The Ie2 is %.3f A",Ie2));
55 disp(sprintf("The Ic is %.3f A",Ic));
56 disp(sprintf("The Iphi is %.4f A",Iphi));
57 disp(sprintf("The Xphi is %.2f      ",Xphi));
58 disp(" ");
59 //
60 //END

```

Scilab code Exa 7.30 Secondary terminal voltage at full load

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 30
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 30");
7
8 //6600/440 V single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=6600;                                // primary
     voltage in Volts
11 v2=440;                                  // secondary
     voltage in Volts
12 e_r=0.02;                                 // equivalent
     resistance
13 e_x=0.05;                                // equivalent
     reactance
14 pf=0.8;                                   // power
     factor
15 //
16 //SOLUTION
17 //worked out differently a bit from the text book in
     terms of the steps
18 phi=acos(pf);                            // phase
     angle
19 reg=e_r*cos(phi)+e_x*sin(phi);           // voltage
     regulation
20 V2=v2*(1-reg);                          // secondary
     terminal voltage
21 disp(sprintf("The secondary terminal voltage is %.2f
     V",V2));
22 disp("");
```

```
23 //  
24 //END
```

Scilab code Exa 7.31 To calculate the value of maximum flux density in the core an

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER  
2 //Example 31  
3  
4 clc;  
5 disp("CHAPTER 7");  
6 disp("EXAMPLE 31");  
7  
8 //single phase transformer having 400 primary and  
// 1000 secondary turns  
9 //VARIABLE INITIALIZATION  
10 N1=400;  
11 N2=1000;  
12 coreA=60; // net core  
// area in cm^2  
13 v1=500; //primary  
// voltage in Volts  
14 f=50; //frequency  
15  
16 //  
17 //SOLUTION  
18 //v1=E1=4.44. m .N1.f Volts  
19 phiM=v1/(4.44*N1*f);  
20 // flux density Bm= m /area  
21 Bm=phiM/coreA; // lines per  
// cm  
22 // voltage per turn  
23 vpt=v1/N1;  
24 v2=N2*vpt;  
25 //  
26 disp(sprintf("The maximum flux density is %.3fx10^-5
```

```

Wb per cm^2" ,Bm*10^5)); //text book anser is 9383
lines per cm^2
27 disp(sprintf("The secondary voltage is %.0f V",v2));
28 disp("");
29 //
30 //END

```

Scilab code Exa 7.32 To calculate total copper loss

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 32
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 32");
7
8 //50 kVA 4400/220 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=50000;
11 v1=4400;                                // primary
12 v2=220;                                  // secondary
13 f=50;
14 R1=3.45;
15 X1=5.2;
16 R2=0.0009;
17 X2=0.015;
18
19 //SOLUTION
20 //
21 //Primary resistance and leakage reactance referred
22 //to secondary
23 //R'1 & X'1
24 //Secondary resistance and leakage reactance

```

```

        referred to primary
24 //R'2 & X'2
25 //Equivalent resistance & leakage reactance referred
   to primary
26 //Re1 & Xe1
27 //Equivalent resistance & leakage reactance referred
   to secondary
28 //Re2 & Xe2
29 //
30 R_dash_2=R2*(v1/v2)^2;
31 R_e1=R1+R_dash_2;
32 X_dash_2=X2*(v1/v2)^2;
33 X_e1=X1+X_dash_2;
34 //
35 R_dash_1=R1*(v2/v1)^2;
36 R_e2=R2+R_dash_1;
37 X_dash_1=X1*(v2/v1)^2;
38 X_e2=X2+X_dash_1;
39 //
40 Z_e1=R_e1+X_e1*%i;
41 Z_e2=R_e2+X_e2*%i;
42 magZ_e1=sqrt(real(Z_e1)^2+imag(Z_e1)^2);
43 magZ_e2=sqrt(real(Z_e2)^2+imag(Z_e2)^2);
44 //
45 disp("SOLUTION ( i )");
46 disp(sprintf("The equivalent resistance referred to
   primary %.4f      ",R_e1)); //text book answer is
   7.05 ohm
47 disp("SOLUTION ( ii )");
48 disp(sprintf("The equivalent resistance referred to
   secondary %.4f      ",R_e2));
49 disp("SOLUTION ( iii )");
50 disp(sprintf("The equivalent leakage reactance
   referred to primary %.4f      ",X_e1));
51 disp(sprintf("The equivalent leakage reactance
   referred to secondary %.4f      ",X_e2));
52 disp("SOLUTION ( iv )");
53 disp(sprintf("The equivalent impedance referred to

```

```

    primary %.4f    " ,magZ_e1)); // text book answer
    is 13.23 ohm
54 disp(sprintf("The equivalent impedance referred to
    secondary %.4f    " ,magZ_e2)); //text book answer
    is 0.0331 ohm
55 //
56 I1=va/v1;
57 I2=va/v2;
58 Pcu=I2^2*R_e2;
59 disp("SOLUTION (d)");
60 disp(sprintf("The copper loss at full load %.0f W",
    Pcu));
61 disp(" ");
62 //The answers in the book on page 7.77 are wrong for
    all but Xe1 and Xe2 values.
63 //END

```

Scilab code Exa 7.33 No load and short circuit results of transformer

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 33
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 33");
7
8 // 5kVA 400/200 V 50 Hz single phase transformer
9 //open circuit and short circuit tests
10 //VARIABLE INITIALIZATION
11 va=5000; // apparent power
12 v1=400; // primary voltage in Volts
13 v2=200; //secondary voltage in Volts
```

```

14 f=50;
15 //no load parameters
16 Voc=400;
17 Io=1;
18 Woc=50; // watts HT side
19 //short circuit test
20 Vsc=12;
21 Isc=10;
22 Wc=40; // watts HT side
23 //
24 pf=0.8;
25 //SOLUTION
26 //no load condition
27 phi0=acos(Woc/(v1*Io));
28 Ic=Io*cos(phi0);
29 Iphi=Io*sin(phi0);
30 Rc=v1/Ic;
31 X=v1/Iphi;
32 disp("SOLUTION ( i )");
33 disp(sprintf("The value of Ic is %f Amp",Ic));
34 disp(sprintf("The value of Iphi is %f Amp",Iphi));
35 //disp(sprintf("The value of Rc is %f Ohm",Rc));
36 //disp(sprintf("The value of X is %f ",X));
37 //
38 //short circuit
39 phisc=acos(Wc/(Vsc*Isc));
40 pf1=cos(phisc);
41 R_e1=Vsc*pf1/Isc;
42 Z_e1=Vsc/Isc;
43 X_e1=sqrt(Z_e1^2-R_e1^2);
44 disp(sprintf("The value of Re1 is %.2 f Ohm",R_e1));
45 disp(sprintf("The value of Ze1 is %.2 f Ohm",Z_e1));
46 disp(sprintf("The value of Xe1 is %.2 f ",X_e1));
47 //
48 I1=va/v1;
49 phi=acos(pf);
50 //R=ercosphi2+vx.sinphi2
51 //E2=V2+I2.R

```

```

52 %reg=(I1*R_e1*pf+I1*X_e1*sin(phi))*100/v1;
53 disp("SOLUTION (c(i))");
54 disp(sprintf("The percent regulation at full load is
55 // %.3f",%reg));
56 //full load output at pf=0.8
57 Pout=va*pf; //output power
58 ironLoss=Woc;
59 cuLoss=Wc;
60 loss=ironLoss+cuLoss;
61 Pin=Pout+loss; // input power
62 eff=Pout*100/Pin;
63 disp("SOLUTION (c(ii))");
64 disp(sprintf("The percent efficiency at full load is
65 // %.2f",eff)); // not calculated in the text book
66 disp("");
67 //END

```

Scilab code Exa 7.34 50 kVA transformer of 5 is to 1 ratio of turns

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 35
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 35");
7
8 //single phase 50 hz , 200kVA, 11kVA/230 V
9 //open circuit and short circuit tests
10 //VARIABLE INITIALIZATION
11 va=200000; // apparent
12 power
12 v1=11000; //primary
13 voltage in Volts

```

```

13 v2=230;                                //secondary
    voltage in Volts
14 Woc=1600;                               //watts also
    equals core losses
15 Wc=2600;                                //watts , also
    equals cu losses
16 f=50;
17 //no load parameters
18 //day cycle given
19 h1=8;                                    // hours
20 load1=160000;                            //load in
    watts
21 pf1=0.8;                                //power
    factor
22 h2=6;
23 load2=100000;
24 pf2=1;
25 h3=10;
26 load3=0;
27 pf3=0;
28 //SOLUTION
29 //24 hr energy output
30 Pout=load1*h1*pf1+load2*h2*pf2+load3*h3*pf3;
31 Pc24=Woc*24;                            // 24 hours
    Pc loss
32 //cu loss= hours.(kva output/kva rated)^2. Full load
    Cu loss
33 Pcu24=h1*(load1/va)^2*Wc+h2*(load2/va)^2*Wc+h3*(
    load3/va)^2*Wc;
34 Pin=Pout+Pc24+Pcu24;
35 eff=Pout*100/Pin;
36 //disp(sprintf("The value Pout is %f",Pout));
37 //disp(sprintf("The value Pc is %f",Pc24));
38 //disp(sprintf("The value Pcu is %f",Pcu24));
39 disp(sprintf("The percent efficiency at full load is
    %.2f",eff));
40 disp("");
41 //

```

42 //END

Scilab code Exa 7.35 No load and short circuit results of transformer

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 // Example 36
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 36");
7
8 // 100kVA 50 Hz 440/11000 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=100000;                                // apparent
11 v1=440;                                     // primary
12 voltage in Volts
12 v2=11000;                                  // secondary
12 voltage in Volts
13 f=50;                                       //
13 efficiency
14 //loads
15 pf=1;                                       // power
15 factor at half load current
16 eff1=0.985;                                 // at full
16 load at 0.8 pf
17 eff2=0.99;                                  // at half
17 full load at unity pf
18 pf1=0.8;                                    // power
18 factor at full load current
19 pf2=1;                                       //
20 //
21 //SOLUTION
22 loss1=(1-eff1)*va*pf1/eff1;                // =Pc
22 +Pcu losses
```

```

23 loss2=(1-eff2)*va*(1/2)*pf2/eff2;
                           // =Pc+Pcu losses
24 // simultaneous equation to be solved
25 //eq 1: Pc+Pcu=loss;
26 //fractipon of copper/ ohmic losses
27 f=(1/2)^2;                                // 60% of
                                             full load
28 //the 2nd equation is Pc+f*Pcu=loss
29 //now the matrix
30 M=[1,1;1,f];                               //Pc+Pcu=
                                             loss1; Pc+(1/2)^2*Pcu=loss2: 1,1,; 1,f
31 A=[loss1,loss2];
32 Mi=inv(M);
33 Ans=A*inv(M);
34 Pc=Ans(1,1);
35 Pcu=Ans(1,2);
36 disp(sprintf("The Pc is %.1f W",Pc));
37 disp(sprintf("The Pcu is %.1f W",Pcu));
38 //
39 //maximum efficiency at farction x times the full
      load; and then f.Pcu=Pc
40 x=sqrt(Pc/Pcu);
41 disp(sprintf("The maximum efficiency would occur at
      a load of %.0f kVA",x*va/1000));
42 I1=va/v1;
43 I1maxEff=I1*x;
44 disp(sprintf("The current at maximum efficeincy is %
      .0f A",I1maxEff));
45 disp("");
46 //
47 //END

```

Scilab code Exa 7.36 Value of load for maximum efficiency

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER

```

2 //Example 36
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 36");
7
8 //100kVA 50 Hz 440/1100 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=100000;                                // apparent
11 v1=440;                                     // primary
12 v2=11000;                                    // secondary
13 f=50;                                       // frequency
14 //loads
15 pf=1;                                        // power
16 eff1=0.985;                                 // at full
17 load at 0.8 pf
17 eff2=0.99;                                  // at half
18 full load at unity pf
18 pf1=0.8;                                    // power
19 factor
19 pf2=1;                                       // power
19 factor
20 //
21 //SOLUTION
22 loss1=(1-eff1)*va*pf1/eff1;                // =Pc
22 +Pcu losses
23 loss2=(1-eff2)*va*(1/2)*pf2/eff2;          // =Pc+Pcu losses
23 // simultaneous equation to be solved
25 //eq 1: Pc+Pcu=loss;
26 //fractipon of copper/ ohmic losses
27 f=(1/2)^2;                                   // 60% of
27 full load
28 //the 2nd equation is Pc+f*Pcu=loss

```

```

29 //now the matrix
30 M=[1,1;1,f]; //Pc+Pcu=
    loss1; Pc+(1/2)^2*Pcu=loss2: 1,1,; 1,f
31 A=[loss1,loss2];
32 Mi=inv(M);
33 Ans=A*inv(M);
34 Pc=Ans(1,1);
35 Pcu=Ans(1,2);
36 disp(sprintf("The Pc is %.1f W",Pc));
37 disp(sprintf("The Pcu is %.1f W",Pcu));
38 //
39 //maximum efficiency at farction x times the full
    load; and then f.Pcu=Pc
40 x=sqrt(Pc/Pcu);
41 disp(sprintf("The maximum efficiency would occur at
    a load of %.0f kVA",x*va/1000));
42 I1=va/v1;
43 I1maxEff=I1*x;
44 disp(sprintf("The current at maximum efficiency is %
    .0f A",I1maxEff));
45 disp("");
46 //
47 //END

```

Scilab code Exa 7.37 To calculate regulation at full load

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 37
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 37");
7
8 //500 kVA 3300/500 V 50 hz single phase transformer
9 //VARIABLE INITIALIZATION

```

```

10 va=500000; // apparent power
11 v1=3300; // primary voltage in Volts
12 v2=500; // secondary voltage in Volts
13 f=50; // loads
14 pf=1; // power factor unity
15 eff=0.97; // at 3/4 full load at unity pf
16 pf2=0.8; // power factor
17 // //SOLUTION
18 I1=va/v1;
19 loss=(1-eff)*va*(3/4)*pf/eff; // =Pc+Pcu
20 // since the eff value is maximum, Pcu=Pc; therefore ,
21 // 2*Pc=loss
22 Pc=loss/2;
23 // (3/4)^2*Pcu=Pc;
24 f=(3/4)^2; // 3/4 load
25 //Pcu=Pc/f
26 Pcu=Pc/f;
27 //disp(sprintf("The Pc is %f W",Pc));
28 //disp(sprintf("The Pcu is %f W",Pcu));
29 //
30 R_e1=Pcu/I1^2;
31 disp(sprintf("The value of Re1 is %.3f W",R_e1));
32 // 10% impedance
33 Z_e1=v1*0.1/I1;
34 X_e1=sqrt(Z_e1^2-R_e1^2);
35 phi=acos(0.8);
36 %reg=(I1*R_e1*cos(phi)+I1*X_e1*sin(phi))*100/v1;
37 disp(sprintf("The percent regulation at full load

```

```

        0.8 pf is %.2f W",%reg));
39 disp("");
40 //
41 //END

```

Scilab code Exa 7.38 Total no load loss

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 38
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 38");
7
8 //220/115 V 25 Hz single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=220;                                // primary
    voltage in Volts
11 v2=115;                                 //
    secondary voltage in Volts
12 f1=25;                                  //
    frequency rating of the transformer in Hz
13 f2=50;                                  //
    frequency of the connected load
14 //loads
15 V=440;                                   // i
    Volts
16 We1=100;                                 // in
    Watts at 220 V, eddy losses
17 Pcl=2*We1;                             //
    Total iron losses which equals We+Wh due to eddy
    and hysteresis
18 Wh1=Pcl-We1;
19 //
20 //SOLUTION

```

```

21 //since we know that We=kh.f.B^1.6 and Wh=Ke.Kf^2.f
22 // ^2.B^2
23 //since all being constant except frequency , we may
24 //take We2/We1=f2^2/f1^2
25 //and Wh2/Wh1=f2/f1
26 //flux density in both cases is same as in second
27 //case voltage and frequency both are doubled
28 //find values for We2 and Wh2, whence Pc2=We2+Wh2
29 We2=f2^2*We1/f1^2;
30 Wh2=f2*Wh1/f1;
31 Pc2=We2+Wh2;
32 disp(sprintf("The total no load losses at 400 V is %
33 .0 f W",Pc2));
34 disp("");
35 //
36 //END

```

Scilab code Exa 7.39 Percentage of hysteresis and copperloss

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 39
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 39");
7
8 //220/440 v 50 Hz transformer
9 //VARIABLE INITIALIZATION
10 v1=220;
    //primary voltage in Volts
11 v2=440;
    //secondary voltage in Volts
12 f1=50;
    //rated frequency in Hz
13
```

```

14 //loads
15 V=110;
16 f2=25;
    //frequency of the applied load
17 //say, else computation may not be possible using
    computer
18 Pout1=100;
                                //in
    watt, just assumed for computational purposes
    for the 220V supply
19 We1=0.01*Pout1;
                                //in
    Watts at 220 V, eddy losses which are 1% of the
    output at 220V
20 Wh1=0.01*Pout1;
                                //in
    Watts at 220 V, hysteresis losses which are 1% of
    the output at 220V
21 //Pc1=We1+Wh1;
                                //Total
    iron losses which equals We+Wh due to eddy and
    hysteresis
22 Pcu1=0.01*Pout1;
                                //copper
    losses
23 //
24 //SOLUTION
25 //since on connecting to half the power ie 110V, the
    output would get halved
26 Pout2=Pout1/2;
27 xPcu=Pcu1/Pout2;
28 disp(sprintf("The copper losses at 110 V would be %
    .0f percent of the output",xPcu*100));
29 //now coming to frequency dependant losses ie eddy
    and hysteresis
30 //since we know that We=kh.f.B^1.6 and Wh=Ke.Kf^2.f
    ^2.B^2
31 //since all being constant except frequency , we may

```

```

        take We2/We1=f2 ^2 / f1 ^2
32 //and Wh2/Wh1=f2 / f1
33 // find values for We2 and Wh2, whence Pc2=We2+Wh2
34 We2=f2^2*We1/f1^2;
35 Wh2=f2*Wh1/f1;
36 xWe=We2/Pout2;
37 xWh=Wh2/Pout2;
38 disp(sprintf("The eddy losses at 110 V would be %.2f
               percent of the output",xWe*100));
39 disp(sprintf("The hysteresis losses at 110 V would
               be %.2f percent of the output",xWh*100));
40 disp("");
41 //
42 //END

```

Scilab code Exa 7.40 To draw the phasor diagram

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 40
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 40");
7
8 //Given
9 //transformer on no load has a core loss 50W, draws
   a current of 2 A (RMS) and induced emf 220 V(RMS)
10 //VARIABLE INITIALIZATION
11 loss=50;                                //core loss in Watts
12 I0=2;                                    //no load current in
   Amperes
13 v0=220;                                  //induced emf in
   Volts
14
15 //SOLUTION

```

```

16 pf=loss/(v0*I0);
17 I_c=I0*pf;                                //core loss component
18 I_phi=I0*sin(acos(pf));                  //magnetizing
    component
19 disp(sprintf("The magnetizing component , I_c= %.4f A
    " , I_phi));
20 disp(sprintf("The core loss component , I_ = %.4f A,
    " , I_c));
21
22 //END

```

Scilab code Exa 7.41 Star connected auto transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 41
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 41");
7
8 //3-phase 550/440 V star connected transformer
    supplies a load of 400kW
9 //VARIABLE INITIALIZATION
10 v1=550;                                     //primary voltage in
    Volts
11 v2=440;                                     //secondary voltage
    in Volts
12 p=400*1000;                                 //load in Watts
13 pf=0.8;                                     //power factor(
    lagging)
14
15 //SOLUTION
16
17 //solution (a)
18 I2=p/(sqrt(3)*v2*pf);                      //current on

```

```

    secondary side
19 I1=I2*(v2/v1);           //since I1:I2=N2:N1
20 I=I2-I1;                 //in sections Oa, Ob
   and Oc
21 disp(sprintf("(a) The current flowing in sections Oa
   , Ob and Oc is %.0f A",I));
22 disp(sprintf("The current flowing in sections aA, bB
   and cC is %.0f A",I1));
23
24 //solution (b)
25 //power transferred by transformer action = Pin.(1-k
   )
26 p_o=p*(1-(v2/v1));       //k=v2/v1
27 disp(sprintf("(b) The power transferred by
   transformer action %.0f kW",p_o/1000));
28
29 //solution (c)
30 p_d=p-p_o;
31 disp(sprintf("(c) The power conducted directly %d kW
   ",p_d/1000));
32
33 //END

```

Chapter 8

Direct Current Machines

Scilab code Exa 8.1 Generated emf

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 1
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;           //terminal voltage in Volts
10 I_l=500;          //load current in Amperes
11 r_a=0.04;         //armature resistance in Ohms
12 r_f=50;           //shunt field resistance in Ohms
13
14 //SOLUTION
15 I_f=v_t/r_f;
16 I_a=I_l+I_f;
17 E_a=v_t+(I_a*r_a); //E_a=emf of generator
18 disp(sprintf("The generated emf is %f V",E_a));
19
20 //END
```

Scilab code Exa 8.2 Ratio of speed

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 2
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALZATION
9 v_t=230;           //terminal voltage in Volts
10 r_a=0.5;          //armature resistance in Ohms
11 r_f=115;          //shunt field resistance in Ohms
12 I_l=40;           //line current in Amperes
13
14 //SOLUTION
15
16 //for generator
17 I_f=v_t/r_f;
18 I_a=I_l+I_f;
19 E_a=v_t+(I_a*r_a); //here E_a=emf of generator
20
21 //for motor
22 I_f=v_t/r_f;
23 I_a=I_l-I_f;
24 E_b=v_t-(I_a*r_a); //here E_b=emf of motor
25
26 ratio=E_a/E_b;     //E_a:E_b=(k_a*flux*N_g):(k_a*
27   flux*N_m) =>E_a:E_b=N_g:N_m (as flux is constant)
28 disp(sprintf("The ratio of speed as a generator to
29   the speed as a motor i.e. N_g:N_m is %f",ratio));
30
31 //END
```

Scilab code Exa 8.3 Armature induced emf and developed torque and efficiency

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 3
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 p_o=10*1000;                                //output of generator in
                                                Watts
10 v_t=250;                                     //terminal voltage in
                                                Volts
11 N=1000;                                      //speed in rpm
12 r_a=0.15;                                     //armature resistance in
                                                Ohms
13 I_f=1.64;                                     //field current in
                                                Amperes
14 rot_loss=540;                                  //rotational loss in
                                                Watts
15
16 //SOLUTION
17
18 //solution (i)
19 I_l=p_o/v_t;
20 I_a=I_l+I_f;
21 E_a=v_t+(I_a*r_a);
22 disp(sprintf("(i) The armature induced emf is %f V", E_a));
23
24 //solution (ii)
25 w=(2*pi*N)/60;                               //in radian/sec
26 T_e=(E_a*I_a)/w;
```

```

27 disp(sprintf("( ii) The torque developed is %f N-m",  

    T_e));  

28  

29 //solution ( iii)  

30 arm_loss=(I_a^2)*r_a;           //armature loss  

31 fld_loss=v_t*I_f;             //field loss  

32 tot_loss=rot_loss+arm_loss+fld_loss;  

33 p_i=p_o+tot_loss;  

34 eff=(p_o/p_i)*100;  

35 disp(sprintf("( iii) The efficiency is %f %%",eff));  

36  

37 //END

```

Scilab code Exa 8.4 Armature resistance and load current at maximum efficiency

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 4
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 v_t=240;                                //in Volts
10 I_1=200;                                 //full load current in
11          Amperes
12 r_f=60;                                  //shunt field resisatnce
13          in Ohms
14 eff=90;                                   //percentage full load
15          efficiency
16 s_loss=800;                               //stray (iron + friction)
17          loss in Watts
18
19 //SOLUTION
```

```

17 //solution (a)
18 p_o=v_t*I_l; //output
19 eff=eff/100;
20 p_i=p_o/eff;
21 tot_loss=p_i-p_o; //since input=output+loss
22 I_f=v_t/r_f;
23 I_a=I_l+I_f;
24 cu_loss=(I_f^2)*r_f; //copper loss
25 c_loss=cu_loss+s_loss; //constant loss
26 arm_loss=tot_loss-c_loss; //armature loss ((I_a^2)*
    r_a)
27 r_a=arm_loss/(I_a^2);
28 disp(sprintf("(a) The armature resisatnce is %f ", r_a));
29
30 //solution (b)
31 //for maximum efficiency , armature loss = constant
    loss =>(I_a^2)*r_a=c_loss
32 I_a=sqrt(c_loss/r_a);
33 disp(sprintf("(b) The load current corresponding to
    maximum efficiency is %f A", I_a));
34
35 //END

```

Scilab code Exa 8.5 BHP of prime mover

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 5
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 v_t=200; //in Volts

```

```

10 I_l=50;                                //in Amperes
11 r_a=0.1;                               //armature resistance in
   Ohms
12 r_f=100;                                //field resistance in Ohms
13 s_loss=500;                             //core and iron loss in
   Watts
14
15 //SOLUTION
16
17 //solution (a)
18 I_f=v_t/r_f;                           //I_sh is same as I_f and
   r_sh is same as r_f
19 I_a=I_f+I_l;
20 E_a=v_t+(I_a*r_a);
21 disp(sprintf("(a) The induced emf is %f V",E_a));
22
23 //solution (b)
24 arm_loss=(I_a^2)*r_a;                  //armature copper loss
25 sh_loss=(I_f^2)*r_f;                  //shunt field copper loss
26 tot_loss=arm_loss+sh_loss+s_loss;
27 p_o=v_t*I_l;                         //output power
28 p_i=p_o+tot_loss;                    //input power
29 bhp=p_i/735.5;                      //1 metric horsepower=
   735.498W
30 disp(sprintf("(b) The Break Horse Power(B.H.P.) of
   the prime mover is %f H.P.(metric)",bhp));
31
32 //solution (c)
33 c_eff=(p_o/p_i)*100;
34 p_EE=E_a*I_a;                        //electrical power
35 m_eff=(p_EE/p_i)*100;
36 e_eff=(p_o/p_EE)*100;
37 disp(sprintf("(c) The commercial efficiency is %f %
   , the mechanical efficiency is %f %% and the
   electrical efficiency is %f %%",c_eff,m_eff,e_eff
   ));
38
39 //END

```

Scilab code Exa 8.6 20 HP 230 V 1150 rpm shunt motor

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 6
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 p_o=20*746;           //output power from H.P. to Watts
(1 H.P.=745.699 or 746 W)
10 v_t=230;              //in Volts
11 N=1150;               //speed in rpm
12 P=4;                  //number of poles
13 Z=882;                //number of armature conductors
14 r_a=0.188;             //armature resistance in Ohms
15 I_a=73;                //armature current in Amperes
16 I_f=1.6;               //field current in Amperes
17
18 //SOLUTION
19
20 //solution (i)
21 E_b=v_t-(I_a*r_a);
22 w=(2*pi*N)/60;        //in radian/sec
23 T_e=(E_b*I_a)/w;
24 disp(sprintf("( i) The electromagnetic torque is %f N
-m" ,T_e));
25
26 //solution (ii)
27 A=P;                  //since it is lap winding, so A=P
and A=number of parallel paths
28 phi=(E_b*60*A)/(P*N*Z);
29 disp(sprintf("( ii) The flux per pole is %f Wb" ,phi))
```

```

;
30
31 //solution ( iii )
32 p_rotor=E_b*I_a; //power developed on rotor
33 p_rot=p_rotor-p_o; //p_shaft=p_out
34 disp(sprintf("( iii) The rotational power is %f W" ,
35 p_rot));
35
36 //solution ( iv )
37 tot_loss=p_rot+((I_a^2)*r_a)+(v_t*I_f);
38 p_i=p_o+tot_loss;
39 eff=(p_o/p_i)*100;
40 disp(sprintf("( iv) The efficiency is %f %%" ,eff));
41
42 //solution ( v )
43 T=p_o/w;
44 disp(sprintf("( v) The shaft torque is %f N-m" ,T));
45
46 //The answers are slightly different due to the
47 //precision of floating point numbers
47
48 //END

```

Scilab code Exa 8.7 New operating speed

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 7
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 p_o=20*746; //output power from H.P
. to Watts (1 H.P.=745.699 or 746 W)

```

```

10 v_t=230; //in Volts
11 N1=1150; //speed in rpm
12 P=4; //number of poles
13 Z=882; //number of armature
    conductors
14 r_a=0.188; //armature resistance
    in Ohms
15 I_a1=73; //armature current in
    Amperes
16 I_f=1.6; //field current in
    Amperes
17 ratio=0.8; //phi2 : phi1 = 0.8 ( here
    phi=flux )
18
19 //SOLUTION
20
21 E_b1=v_t-(I_a1*r_a);
22 I_a2=I_a1/ratio; // ( phi2 * I_a2 ) = ( phi1 *
    I_a1 )
23 E_b2=v_t-(I_a2*r_a);
24 N2=(E_b2/E_b1)*(1/ratio)*N1; //N2:N1=(E_b2/E_b1)*(
    phi1 / phi2 )
25 N2=round(N2); //to round off the
    value of N2 ( before rounding off N2=1414.695516
    rpm )
26 disp(sprintf("The new operating speed is %d rpm",N2));
27
28 //The answer is slightly different due to the
    precision of floating point numbers
29
30 //END

```

Scilab code Exa 8.8 250 V DC shunt machine

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 8
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts
10 r_a=0.1;                                 //armature resistance
    in Ohms
11 r_f=125;                                //field resistance in
    Ohms
12 p_o=20*1000;                            //output power in Watts
13 N_g=1000;                               //speed as generator in
    rpm
14
15 //SOLUTION
16
17 // machine as a generator
18 I_l=p_o/v_t;                            //I_f is same as I_sh
19 I_f=v_t/r_f;
20 I_ag=I_l+I_f;
21 E_a=v_t+(I_ag*r_a);                  //induced emf = E_a =
    E_g
22
23 // machine as a motor
24 I_l=p_o/v_t;
25 I_f=v_t/r_f;
26 I_am=I_l-I_f;
27 E_b=v_t-(I_am*r_a);                  //back emf = E_b = E_m
28
29 //solution (a)
30 N_m=(N_g*E_b)/E_a;
31 N_m=round(N_m);                      //to round off the value
    of N_m
32 disp(sprintf("(a) The speed of the same machine as a
    motor is %d rpm",N_m));

```

```

33
34 // solution (b)
35
36 // (i)
37 p1=(E_a*I_ag)/1000;           // to express the answer
      in kW
38 disp(sprintf("(b) (i) The internal power developed
      as generator is %f kW",p1));
39
40 // (ii)
41 p2=(E_b*I_am)/1000;
42 disp(sprintf("(b) (ii) The internal power developed
      as motor is %f kW",p2));
43
44 //END

```

Scilab code Exa 8.9 Torque developed in the motor

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 9
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 v_t=230;                             //in Volts
11 I_l=52;                              //in Amperes
12 Z=600;                               //tottal number of
      conductors
13 r_f=115;                            //in Ohms
14 d=30/100;                           //airgap diameter from cm
      to m
15 l=20/100;                           //effective length of pole

```

```

16 B=4100/10000; // flux density from Gauss
      to Wb/m^2
17
18 //SOLUTION
19 I_f=v_t/r_f; // I_f is same as I_sh
20 I_a=I_l-I_f;
21 ar=(%pi*d*l)/P; // area of pole
22 phi=ar*B; // phi = flux
23 A=P;
24 T=(phi*Z*I_a)/(2*%pi*A);
25 disp(sprintf("The torque developed in the motor is
      %f N-m",T));
26
27 //The answer is different as 'A' has not been
      included in the denominator(in the book)
28
29 //END

```

Scilab code Exa 8.10 6 pole DC machine with 400 conductors

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 10
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 P=6; //number of poles
10 I=80; //current per conductor in
      Amperes
11 Z=400; //tottal number of
      conductors
12 phi=0.020; //flux per pole in Wb
13 N=1800; //in rpm

```

```

14
15 //SOLUTION
16
17 //soluion (a): for wave connected
18 disp(" (a) For Wave connected");
19
20 // (i)
21 A=2;                                //A=number of parallel
22                                     paths
23 I_a=I*A;
24 disp(sprintf("( i ) The total current is %f A",I_a));
25
26 // (ii)
27 E_a=(phi*Z*N*P)/(60*A);
28 disp(sprintf("( ii ) The emf is %f V",E_a));
29
30 // (iii)
31 p=E_a*I_a;
32 disp(sprintf("( iii ) The power developed in armature
33 is %f kW",p/1000));
34 w=(2*pi*N)/60;
35 T_e=p/w;
36 disp(sprintf("The electromagnetic torque is %f N-m",
37 T_e));
38
39 //soluion (b): for lap connected
40 disp(" (b) For Lap connected");
41
42 // (i)
43 A=P;
44 I_a=I*A;
45 disp(sprintf("( i ) The total current is %f A",I_a));
46
47 // (ii)
48 E_a=(phi*Z*N*P)/(60*A);
49 disp(sprintf("( ii ) The emf is %f V",E_a));

```

```

49 // (iii)
50 p=E_a*I_a;
51 disp(sprintf("(iii) The power developed in armature
      is %f kW",p/1000));
52 w=(2*pi*N)/60;
53 T_e=p/w;
54 disp(sprintf("The electromagnetic torque is %f N-m",
      T_e));
55
56 //END

```

Scilab code Exa 8.11 Total emf generated in the armature

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 11
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 11");
7
8 //VARIABLE INITIALIZATION
9 p_o=20*1000;           //output in W
10 v_t=250;               //in Volts
11 r_a=0.05;              //aramture resistance in
                           Ohms
12 r_se=0.025;            // series resistance in
                           Ohms
13 r_sh=100;               // shunt resistance in Ohms
14
15 //SOLUTION
16 I_t=p_o/v_t;
17 v_se=I_t*r_se;          //for series winding
18 v_sh=v_t+v_se;          //for shunt winding
19 I_sh=v_sh/r_sh;
20 I_a=I_sh+I_t;

```

```

21 E_a=v_t+(I_a*r_a)+v_se;
22 disp(sprintf("The total emf generated is %f V",E_a))
   ;
23
24 //END

```

Scilab code Exa 8.12 Terminal voltage of the machine

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 12
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 N=750;                               //in rpm
11 r_a=0.4;                             //in Ohms
12 r_f=200;                            //in Ohms
13 Z=720;
14 phi=2.895*(10^6)*(10^(-8));        //in Wb (1 line=10^(-8)
   Wb)
15 r_l=10;                             //load resistance in
   Ohms
16 A=2;                                //for wave winding
17
18 //SOLUTION
19 E_a=(phi*Z*N*P)/(60*A);
20 disp(sprintf("The induced emf is %f V",E_a));
21 // E_a=v+(I_a*r_a) but I_a=I_l+I_f and I_l=v/r_l ,
   I_f=v/r_f =>I_a=(v/r_l) + (v/r_f)
22 // =>E_a=v+(((v/r_l) + (v/r_f))*r_a)
23 // taking v common, the following equation is
   obtained

```

```

24 v=E_a/(1+(r_a/r_f)+(r_a/r_l));
25 disp(sprintf("The terminal voltage of the machine is
26 %f V",v));
27 //The answer is slightly different due to the
28 //precision of floating point numbers
29 //END

```

Scilab code Exa 8.13 Current in each conductor and emf generated

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 13
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 13");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 v_t=220;                             //in Volts
11 I_l=42;                               //load current in
12 r_a=0.1;                            //in Ohms
13 r_f=110;                            //in Ohms
14 drop=1;                              //contact drop per brush
15 //SOLUTION
16
17 //solution (i)
18 A=P;                                  //for lap winding
19 I_f=v_t/r_f;                         //I_f is same as I_sh
20 I_a=I_l+I_f;
21 I_c=I_a/A;                           //conductor current
22 disp(sprintf("The current in each conductor of the
23 armature is %d A",I_c));

```

```

23
24 // solution ( ii )
25 v_a=I_a*r_a;                                // armature voltage drop
26 v_b=2*drop;                                 // brush drop
27 emf=v_t+v_a+v_b;
28 disp(sprintf("The total emf generated is %f V",emf))
      ;
29
30 //END

```

Scilab code Exa 8.14 Armature resistance and load current at maximum efficiency

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 14
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 14");
7
8 //VARIABLE INITIALIZATION
9 v_t=220;                                     //in Volts
10 I_l=196;                                      //in Amperes
11 s_loss=720;                                    //stray loss in Watts
12 r_f=55;                                       //shunt field ressistance
      in Ohms
13 eff=88/100;                                   //efficiency
14
15 //SOLUTION
16 p_o=v_t*I_l;                                 // electrical input
17 p_i=p_o/eff;
18 tot_loss=p_i-p_o;
19 I_f=v_t/r_f;
20 I_a=I_l+I_f;
21 cu_loss=v_t*I_f;                            //shunt field copper
      loss

```

```

22 c_loss=cu_loss+s_loss;           //constant loss
23 arm_loss=tot_loss-c_loss;       //armature copper loss
24 r_a=arm_loss/(I_a^2);
25 disp(sprintf("The armature resistance is %f ",r_a))
   );
26
27 //for maximum efficiency , armature loss = constant
   loss =>(I_a^2)*r_a=c_loss
28 I_a=sqrt(c_loss/r_a);
29 disp(sprintf("The load current corresponding to
   maximum efficiency is %f A",I_a));
30
31 //END

```

Scilab code Exa 8.15 Full load speed

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 15
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 v_t=230;                      //in Volts
10 I_a1=3.33;                     //in Amperes
11 N1=1000;                       //in rpm
12 r_a=0.3;                       //armature resistance in
   Ohms
13 r_f=160;                       // field resistance in
   Ohms
14 I_l=40;                        //in Amperes
15 phi1=1;                         //in Wb (phi=1 is an
   assumption)
16 phi2=(1-(4/100));              //in Wb (phi2=0.96 of

```

```

    phi1)
17
18 //SOLUTION
19
20 //At no load
21 E_a1=v_t-(I_a1*r_a);
22 I_f=v_t/r_f;
23
24 //At full load
25 I_a2=I_l-I_f;
26 E_a2=v_t-(I_a2*r_a);
27 N2=(E_a2/E_a1)*(phi1/phi2)*N1;
28 N2=round(N2);           //to round off the value
29 disp(sprintf("The full load speed is %d rpm",N2));
30
31 //END

```

Scilab code Exa 8.16 250 V 4 pole shunt motor

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 16
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 16");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                      //in Volts
10 P=4;                          //number of poles
11 Z=500;                        //number of conductors
12 r_a=0.25;                     //in Ohms
13 r_f=125;                      //in Ohms
14 phi=0.02;                     //in Wb
15 I_l=14;                       //in Amperes
16 A=2;

```

```

17 rot_loss=300; // rotational loss in
    Watts
18
19 //SOLUTION
20
21 // solution ( i )
22 I_f=v_t/r_f;
23 I_a=I_l-I_f;
24 E_a=v_t-(I_a*r_a);
25 N=(E_a*A*60)/(phi*Z*P);
26 N=round(N); //to round off the value
    of N
27 disp(sprintf("( i ) The speed is %d rpm",N));
28 p_e=E_a*I_a;
29 w=(2*pi*N)/60;
30 T1=p_e/w;
31 disp(sprintf("The internal torque developed is %f N-
    m",T1));
32
33 // solution ( ii )
34 p_o=p_e-rot_loss;
35 disp(sprintf("( ii ) The shaft power is %f W",p_o));
36 T2=p_o/w;
37 disp(sprintf("The shaft torque is %f N-m",T2));
38 p_i=v_t*I_l;
39 eff=(p_o/p_i)*100;
40 disp(sprintf("The efficiency is %f %%",eff));
41
42 //END

```

Scilab code Exa 8.17 200 V DC shunt motor

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 17
3

```

```

4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 17");
7
8 //VARIABLE INITIALIZATION
9 v_t=200;                                //in Volts
10 I_l=22;                                  //in Amperes
11 N1=1000;                                 //in rpm
12 r_a=0.1;                                 //in Ohms
13 r_f=100;                                 //in Ohms
14 N2=800;                                  //in rpm
15
16 //SOLUTION
17
18 //solution (i)
19 I_f=v_t/r_f;
20 I_a1=I_l-I_f;
21 E_a1=v_t-(I_a1*r_a);
22 //on rearranging the equation E_a2:E_a1=N2:N1, where
   E_a2=v_t-I_a1*(r_a+r_s) and E_a1=v_t-(I_a1*r_a),
   we get,
23 r_s1=((v_t - ((N2*E_a1)/N1))/I_a1)-r_a;
24 disp(sprintf("(i) When the load torque is
   independent of speed, the additional resistance
   is %f ",r_s1));
25
26 //solution (ii)
27 I_a2=(N2/N1)*I_a1;
28 //on rearranging the equation E_a2:E_a1=N2:N1, where
   E_a2=v_t-I_a2*(r_a+r_s) and E_a1=v_t-(I_a1*r_a),
   we get,
29 r_s2=((v_t - ((N2*E_a1)/N1))/I_a2)-r_a;
30 disp(sprintf("(ii) When the load torque is
   proportional to speed, the additional resistance
   is %f ",r_s2));
31
32 //solution (iii)
33 I_a2=(N2^2/N1^2)*I_a1;

```

```

34 //on rearranging the equation E_a2:E_a1=N2:N1, where
    E_a2=v_t-I_a2*(r_a+r_s) and E_a1=v_t-(I_a1*r_a),
    we get ,
35 r_s3=((v_t - ((N2*E_a1)/N1))/I_a2)-r_a;
36 disp(sprintf("(iii)When the load torque varies as
    the square of speed , the additional resistance is
    %f      ",r_s3));
37
38 //solution (iv)
39 I_a2=(N2^3/N1^3)*I_a1;
40 //on rearranging the equation E_a2:E_a1=N2:N1, where
    E_a2=v_t-I_a2*(r_a+r_s) and E_a1=v_t-(I_a1*r_a),
    we get ,
41 r_s4=((v_t - ((N2*E_a1)/N1))/I_a2)-r_a;
42 disp(sprintf("(iv)When the load torque varies as the
    cube of speed , the additional resistance is %f
    ",r_s4));
43
44 //END

```

Scilab code Exa 8.18 Value of inserted resistance

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 18
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 18");
7
8 //VARIABLE INITIALIZATION
9 v_t=460;                                //in Volts
10 p_o=10*736;                             //in Watts (1 metric H.
11 P=735.5 W);                            //as given in the
                                             question

```

```

12 eff=84/100;
13 I_f=1.1;                                //in Amperes
14 r_a=0.2;                                //in Ohms
15
16 //SOLUTION
17 p_i=p_o/eff;
18 I_l=p_i/v_t;
19 I_a=I_l-I_f;
20 E1=v_t-(I_a*r_a);
21 E2=E1*ratio;                            //E2:E1=N2:N1=ratio
22 v=v_t-E2;                               //voltage drop across
   r_a and r_s (r_s is the series resistance to be
   inserted)
23 r_s=(v/I_a)-r_a;
24 disp(sprintf("The resistance required is %f ",r_s))
   ;
25
26 //The answer is different because ratio equals
   85/100 and not 75/100
27
28 //END

```

Scilab code Exa 8.19 New speed of motor on inserting a 250 ohm resistance

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 19
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 19");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                  //in Volts
10 r_a=0.5;                                 //in Ohms
11 r_f=250;                                 //in Ohms

```

```

12 N1=600;                                //in rpm
13 I=21;                                    //in Amperes
14 r_s=250;                                 //in Ohms
15
16 //SOLUTION
17 I_f1=v_t/r_f;
18 I_f2=v_t/(r_f+r_s);
19 I_a1=I-I_f1;
20 // T is directly proportional to ( *I_a )
21 // I_f is directly proportional to
22 // => I_f1*I_a1=I_f2*I_a2 , therefore ,
23 I_a2=(I_f1*I_a1)/I_f2;
24 E_b1=v_t-(I_a1*r_a);
25 E_b2=v_t-(I_a2*r_a);
26 // E_b is directly proportional to ( *N)
27 // ( *N) is directly proportional to ( I_f*N )
28 // =>E_b1:E_b2=(I_f1:I_f2)*(N1:N2)
29 N2=(I_f1/I_f2)*(E_b2/E_b1)*N1;
30 N2=round(N2);                           //to round off the value
31 disp(sprintf("The new speed of the motor is %d rpm", N2));
32
33 //END

```

Scilab code Exa 8.20 Reduction of main flux to raise the speed by 50 percent

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 20
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 20");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts

```

```

10 I_a1=20;                                //in Amperes
11 N1=1000;                                 //in rpm
12 r_a=0.5;                                 //in Ohms
13 drop=1;                                  //brush contact drop in
   Volts
14 ratio=1.5;                               //N2:N1=1.5
15 phi1=1;                                   //it is an assumption
16
17 //SOLUTION
18 E_1=v_t-(I_a1*r_a)-(2*drop);
19 //solving the quadratic equation directly ,
20 a=1;
21 b=-496;
22 c=14280;
23 D=b^2-(4*a*c);
24 x1=(-b+sqrt(D))/(2*a);
25 x2=(-b-sqrt(D))/(2*a);
26 if(x1<40)
27 I_a2=x1;
28 else if(x2<40)
29 I_a2=x2;
30 end;
31 phi2=(I_a1/I_a2)*phi1;
32 phi=(1-phi2)*100;
33 disp(sprintf("The flux to be reduced is %f %% of the
   main flux",phi));
34
35 //END

```

Scilab code Exa 8.21 10 kW 6 pole DC generator

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 21
3
4 clc;

```

```

5 disp("CHAPTER 8");
6 disp("EXAMPLE 21");
7
8 //VARIABLE INITIALIZATION
9 p_o=10*1000;                                //in Watts
10 P=6;                                         //number of poles
11 E_g=200;                                      //in Volts
12 N=1500;                                       //in rpm
13 A=P;                                         //since the armature
14     is lap connected
15 B=0.9;                                         //flux density in
16     Tesla
17 l=0.25;                                       //length of armature
18     in m
19 dia=0.2;                                       //diameter of armature
20     in m
21
22 //SOLUTION
23
24 //solution (a)
25 area=2*pi*(dia/2)*l;
26 phi=B*area;
27 disp(sprintf("(a) The flux per pole is %f Wb",phi));
28
29 //solution (b)
30 Z=(60*E_g)/(phi*N);
31 disp(sprintf("(b) The total number of active
32 conductors is %d",Z));
33
34 //solution (c)
35 I_a=50;
36 p=E_g*I_a;
37 w=(2*pi*N)/60;
38 T=p/w;
39 disp(sprintf("(c) The torque developed when armature
40 current is 50 A is %f N-m",T));
41
42 //END

```

Scilab code Exa 8.22 Shunt wound motor running at 600 rpm from a 230 V supply

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 22
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 22");
7
8 //VARIABLE INITIALIZATION
9 N1=600;                                //in rpm
10 v=230;                                  //in Volts
11 I_11=50;                                 //line current in
                                             Ampères
12 r_a=0.4;                                //armature resistance
                                             in Ohms
13 r_f=104.5;                               //field resistance in
                                             Ohms
14 drop=2;                                  //brush drop in Volts
15
16 //SOLUTION
17
18 //solution (i)
19 I_12=5;
20 I_a1=I_11-(v/r_f);
21 E_b1=v-(I_a1*r_a)-drop;
22 I_a2=I_12-(v/r_f);
23 E_b2=v-(I_a2*r_a)-drop;
24 N2=(E_b2/E_b1)*N1;
25 N2=round(N2);
26 disp(sprintf("(i) The speed at no load is %d rpm",N2));
27
28 //solution (ii)
```

```

29 I_12=50;
30 N2=500;
31 E_b2=(N2/N1)*E_b1;
32 dif=v-drop; // difference
33 I_a2=I_12-(v/r_f);
34 r_se=((dif-E_b2)/I_a2)-r_a;
35 disp(sprintf("( ii) The additional resistance is %f
   ",r_se));
36
37 //solution ( iii)
38 phi1=1; // it is an assumption
39 I_a3=30;
40 N2=750;
41 E_b3=v-(I_a3*r_a)-drop;
42 phi2=(E_b3/E_b1)*(N1/N2)*phi1;
43 red=((1-phi2)*100*phi1)/phi1;
44 disp(sprintf("( iii) The percentage reduction of flux
   per pole is %f %%",red));
45
46 //END

```

Scilab code Exa 8.23 Value of inserted resistance in field circuit for increasing

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 23
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 23");
7
8 //VARIABLE INITIALIZATION
9 v=230; // in Volts
10 r_a=0.4; // in Ohms
11 r_f1=115; // in Ohms
12 I_a=20; // in Amperes

```

```

13 N1=800; // in rpm
14 N2=1000; // in rpm
15
16 //SOLUTION
17 I_f1=v/r_f1;
18 E_b1=v-(I_a*r_a);
19 // rearranging the equation , we get ,
20 r_f2=((E_b1*N2)/((v*N1)-(N1*I_a*r_a)))*r_f1;
21 r_f2_dash=r_f2-r_f1;
22 disp(sprintf("The external resistance is %f ", r_f2_dash));
23
24 //The answer is slightly different due to the
precision of floating point numbers
25
26 //END

```

Scilab code Exa 8.24 New speed of motor on inserting a 250 ohm resistance in the f

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 24
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 24");
7
8 //This example is same as example 19
9
10 //VARIABLE INITIALIZATION
11 v=250; // in Volts
12 r_a=0.5; // in Ohms
13 r_f=250; // in Ohms
14 N1=600; // in rpm
15 I_l=21; // in Amperes
16 r=250; // in Ohms

```

```

17
18 //SOLUTION
19 I_f1=v/r_f ;
20 I_a1=I_1-I_f1 ;
21 I_a2=2*I_a1 ;
22 E_b1=v-(I_a1*r_a) ;
23 E_b2=v-(I_a2*r_a) ;
24 ratio=(r+r_f)/r_f ;
25 N2=(ratio*N1*E_b2)/E_b1 ;
26 N2=round(N2) ;
27 disp(sprintf("The new speed is %d rpm",N2)) ;
28
29 //END

```

Scilab code Exa 8.25 24 slot 2 pole DC machine

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 25
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 25");
7
8
9 //VARIABLE INITIALIZATION
10 slot=24;                                //number of slots
11 P=2;                                      //number of poles
12 N=18;                                     //number of turns per
     coil
13 B=1;                                       //in Webers
14 l=20/100;                                  //effective length in
     meters
15 rad=10/100;                                //radius in meters
16 w=183.2;                                   //angular velocity in
     rad/s

```

```

17
18 //SOLUTION
19 A=2;
20 Z=slot*P*N; // total number of
   conductors
21 ar1=(2*%pi*rad*l)/P;
22 ar2=ar1*0.8; //since the magnetic
   poles 80% of the armature periphery
23 phi=B*ar2; //effective flux per
   pole
24
25 //solution (a)
26 E_a=(P*Z*phi*w)/(2*%pi*A);
27 disp(sprintf("(a) The induced emf is %f V",E_a));
28
29 //solution (b)
30 coil=slot/P; //number of coils in
   each path
31 E_coil=E_a/coil;
32 disp(sprintf("(b) The induced emf per coil is %f V",
   E_coil));
33
34 //solution (c)
35 E_turn=E_coil/N;
36 disp(sprintf("(c) The induced emf per turn is %f V",
   E_turn));
37
38 //solution (d)
39 E_cond=E_turn/A;
40 disp(sprintf("(d) The induced emf per conductor is
   %f V",E_cond));
41
42 //The answers are slightly different due to the
   precision of floating point numbers
43
44 //END

```

Scilab code Exa 8.27 Counter emf of motor and power developed in armature

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 27
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 27");
7
8
9 //VARIABLE INITIALIZATION
10 v_t=200;                                //in volts
11 r_a=0.06;                                 //in Ohms
12 r_se=0.04;                                //in Ohms
13 p_i=20*1000;                             //in Watts
14
15 //SOLUTION
16
17 //solution (a)
18 I_a=p_i/v_t;
19 E_b=v_t-I_a*(r_a+r_se);
20 disp(sprintf("(a) The counter emf of the motor is %d
V",E_b));
21
22 //solution (b)
23 p_a=E_b*I_a;
24 p_a=p_a/1000;                            //from W to kW
25 disp(sprintf("(b) The power developed in the
armature is %d kW",p_a));
26
27 //END
```

Scilab code Exa 8.28 Voltage between far end of feeder and bus bar

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 28
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 28");
7
8 //VARIABLE INITIALIZATION
9 E_a=120;                                //in Volts
10 r_se=0.03;                               //in Ohms
11 r_a=0.02;                                //in Ohms
12 v1=240;                                  //in Volts
13 r=0.25;                                   //in Ohms
14 I=300;                                    //in Amperes
15
16 //SOLUTION
17 v=I*(r_se+r_a+r);
18 disp(sprintf("The voltage drop across the three
             resistances is %d V",v));
19 v_t=v1+E_a-v;
20 disp(sprintf("The voltage between far end and the
             bus bar is %d V",v_t));
21 disp(sprintf("The net increase of %d V may be beyond
             the desired limit",v_t-v1));
22 disp("Hence, a field diverter resistance may be
             necessary to regulate the far-end terminal
             voltage");
23
24 //END
```

Scilab code Exa 8.29 Speed of motor when connected in series with 5 ohm resistance

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
```

```

2 //Example 29
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 29");
7
8 //VARIABLE INITIALIZATION
9 r_a=1;                                //in Ohms
10 N1=800;                                 //in rpm
11 v_t=200;                                //in Volts
12 I_a=15;                                 //in Amperes
13 r_s=5;                                  //series resistance in
                                           Ohms
14
15 //SOLUTION
16 E_b1=v_t-(I_a*r_a);
17 E_b2=v_t-I_a*(r_a+r_s);
18 N2=(E_b2/E_b1)*N1;
19 N2=round(N2);                          //to round off the value
20 disp(sprintf("The speed attained after connecting
               the series resistance is %d rpm",N2));
21
22 //END

```

Scilab code Exa 8.30 Value of starting torque

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 30
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 30");
7
8 //VARIABLE INITIALIZATION
9 p=5*735.5;                               //in Watts (1 metric H.P

```

```

    .=735.5 W)
10 N=1000;                      //in rpm
11 I=30;                         //in Amperes
12 I_s=45;                        //starting current in
                                  Amperes
13
14 //SOLUTION
15 T=(p*60)/(2*pi*1000);
16 T_s=(T*(I_s^2))/(I^2);
17 disp(sprintf("The starting torque is %f N-m",T_s));
18
19 //The answer is slightly different due to precision
   of floating point numbers
20
21 //END

```

Scilab code Exa 8.31 Value of speed when flux is increased by 20 percent

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 31
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 31");
7
8 //VARIABLE INITIALIZATION
9 r_a=0.1;                      //combined resistance of
                                  armature & field resistance in Ohms
10 v_t=230;                       //in Volts
11 I_a1=100;                      //in Amperes
12 N1=1000;                       //in rpm
13 I_a2=200;                      //in Amperes
14 ratio=1.2;                     //ratio of 2 : 1 =1.2
15
16 //SOLUTION

```

```

17 E_b1=v_t-(I_a1*r_a);           // numerator of LHS
    according to the book
18 E_b2=v_t-(I_a2*r_a);           // denominator of LHS
    according to the book
19 N2=(E_b2/E_b1)*(1/ratio)*N1;
20 N2=round(N2);                  //to round off the value
21 disp(sprintf("The new speed of the armature is %d
    rpm",N2));
22
23 //END

```

Scilab code Exa 8.32 250 V series motor with 20 A current and 1000 rpm

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 32
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 32");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                         //in Volts
10 I=20;                            //in Amperes
11 N1=1000;                          //in rpm
12 P=4;                             //number of poles
13 r_p=0.05;                         //resistance of field
    coil on each pole in Ohms
14 r_a=0.2;                          //in Ohms
15
16 //SOLUTION
17
18 r_se=P*r_p;
19 r_m=r_a+r_se;                   // resistance of motor
20 E_b1=v_t-(I*r_m);
21 T1=I^2;

```

```

22
23 //solution (a)
24 //solving the quadratic equation directly ,
25 r=10;                                //in Ohms
26 a=1.02;
27 b=-25;
28 c=-400;
29 D=b^2-(4*a*c);
30 x1=(-b+sqrt(D))/(2*a);
31 x2=(-b-sqrt(D))/(2*a);
32 //to extract the positive root out of the two
33 if (x1>0 & x2<0)
34 I1=x1;
35 else (x1<0 & x2>0)
36 I1=x2;
37 end;
38 I_a=((10.2*I1)-v_t)/r;
39 E_b2=v_t-(I_a*r_a);
40 N2=((E_b2/E_b1)*I*N1)/I1;
41 N2=round(N2);                      //to round off the value
42 disp(sprintf("(a) The speed with 10      resistance in
parallel with the armature is %d rpm",N2));
43
44 //solution (b)
45 //solving the quadratic equation directly ,
46 a=5/7;
47 b=0;
48 c=-400;
49 D=b^2-(4*a*c);
50 y1=(-b+sqrt(D))/(2*a);
51 y2=(-b-sqrt(D))/(2*a);
52 //to extract the positive root out of the two
53 if (y1>0 & y2<0)
54 I2=y1;
55 else (y1<0 & y2>0)
56 I2=y2;
57 end;
58 E_b3=v_t-(I2*r_a);

```

```

59 N3=((E_b3/E_b1)*I*N1)/(I2*a);
60 N3=round(N3); //to round off the value
61 disp(sprintf("(b) The speed with 0.5 resistance
       in parallel with series field is %d rpm",N3));
62
63 //The answers are slightly different due to the
   precision of floating point numbers
64
65 //END

```

Scilab code Exa 8.33 Resistance to be added to obtain rated torque at starting and

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 33
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 33");
7
8 //VARIABLE INITIALIZATION
9 v_t=230; //in Volts
10 N1=1500; //in rpm
11 I_a1=20; //in Amperes
12 r_a=0.3; //armature resistance
           in Ohms
13 r_se=0.2; //series field
             resistance in Ohms
14
15 //SOLUTION
16
17 //solution (a)
18 E_b=0; //at starting
19 nr1=v_t-I_a1*(r_a+r_se); //value of numerator
20 r_ext=nr1/I_a1;
21 disp(sprintf("(a) At starting , the resistance that

```

```

        must be added is %f    ",r_ext));
22
23 //solution (b)
24 I_a2=I_a1;
25 N2=1000;
26 ratio=N2/N1;
27 nr2=v_t-I_a2*(r_a+r_se);
28 r_ext=((ratio*nr1)-nr2)/(-I_a2);
29 disp(sprintf("(b) At 1000 rpm, the resistance that
        must be added is %f    ",r_ext));
30
31 //END

```

Scilab code Exa 8.34 Total emf and armature current

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 34
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 34");
7
8 //VARIABLE INITIALIZATION
9 r_a=0.06;                                //armature resistance
     in Ohms
10 r_se=0.04;                                //series resistance in
      Ohms
11 r_sh=25;                                   //shunt resistance in
      Ohms
12 v_t=110;                                    //in Volts
13 I_l=100;                                    //in Amperes
14
15 //SOLUTION
16
17 //solution (a)

```

```

18 I_sh=v_t/r_sh;
19 I_a=I_sh+I_l;
20 E_g=v_t+I_a*(r_a+r_se);
21 disp(" (a) When the machine is connected as long
      shunt compound generator -");
22 disp(sprintf("The armature current is %f A and the
      total emf is %f V", I_a, E_g));
23
24 //solution (b)
25 I_sh=(v_t/r_sh)+(I_l*r_se/r_sh);
26 I_a=I_sh+I_l;
27 E_g=v_t+(I_a*r_a)+(I_l*r_se);
28 disp(" (b) When the machine is connected as short
      shunt compound generator -");
29 disp(sprintf("The armature current is %f A and the
      total emf is %f V", I_a, E_g));
30
31 //END

```

Scilab code Exa 8.35 Armature current and induced emf

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 35
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 35");
7
8 //VARIABLE INITIALIZATION
9 r_a=0.06;                                //armature resistance
   in Ohms
10 r_se=0.04;                                //series resistance in
   Ohms
11 r_sh=25;                                   //shunt resistance in
   Ohms

```

```

12 v_t=110;                                //in Volts
13 I_l=100;                                 //in Amperes
14
15 //SOLUTION
16
17 //solution (a)
18 I_sh=v_t/r_sh;
19 I_a=I_l-I_sh;
20 E_g=v_t-I_a*(r_a+r_se);
21 disp(" (a) When the machine is connected as long
      shunt compound generator -");
22 disp(sprintf("The armature current is %f A and the
      total emf is %f V", I_a, E_g));
23
24 //solution (b)
25 I_sh=(v_t/r_sh)-(I_l*r_se/r_sh);
26 I_a=I_l-I_sh;
27 E_g=v_t-(I_a*r_a)-(I_l*r_se);
28 disp(" (b) When the machine is connected as short
      shunt compound generator -");
29 disp(sprintf("The armature current is %f A and the
      total emf is %f V", I_a, E_g));
30
31 //END

```

Scilab code Exa 8.36 Constant losses and full load efficiency

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 36
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 36");
7
8 //VARIABLE INITIALIZATION

```

```

9 v_t=250; //in Volts
10 I_l=150; //in Amperes
11 loss1=1200; //core loss at full load
12 loss2=800; //mechanical loss in
13 r_b=0.08; //brush resistance in
14 r_sh=62.5; //shunt field resistance
15 r_se=0.03; //series field
16 r_ip=0.02; //interpole resistance
17
18 //SOLUTION
19
20 //solution (a)
21 p_o=v_t*I_l;
22 I_sh=v_t/r_sh;
23 I_a=I_l+I_sh;
24 r_tot=r_b+r_se+r_ip;
25 arm_loss=(I_a^2)*r_tot; //armature circuit
26 cu_loss=v_t*I_sh; //shunt field copper
27 c_loss=cu_loss+loss1+loss2; //constant loss
28 disp(sprintf("(a) The constant loss is %f W",c_loss));
29
30 //solution (b)
31 tot_loss=arm_loss+c_loss; //total loss
32 p_i=p_o+tot_loss;
33 eff=(p_o/p_i)*100;
34 disp(sprintf("(b) The full load efficiency is %f %%",eff));
35
36 //END

```

Scilab code Exa 8.37 Hysteresis and eddy current losses

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 37
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 37");
7
8 //VARIABLE INITIALIZATION
9 p_o=50*1000;           //in Watts
10 v_t=250;              //in Volts
11 loss1=5000;           //total core loss in
                        Watts
12 loss2=2000;           //total core loss in
                        Watts (when speed is reduced to half)
13 speed=125/100;
14
15 //SOLUTION
16
17 //solution (a)
18
19 //W_h=A*N, where W_h=hysteresis loss , A=constant and
   N=speed
20 //W_e=B*(N^2) , where W_e=eddy current loss , B=
   constant and N=speed
21 //W_h+(W_e^2)=loss1 =>W_h+W_e=5000
22 // (W_h/2)+(W_e/4)=loss2 =>(0.5*W_h)+(0.25*W_e)=2000
   (when speed reduces to half)
23 //So, we get two equations
24 //W_h+W_e = 5 0 0 0 ..... eq( i )
25 // (0.5*W_h)+(0.25*W_e) = 2 0 0 0 ..... eq( ii )
26 //solving the equations by matrix method
27 A=[1 1;0.5 0.25];
```

```

28 b=[5000;2000];
29 x=inv(A)*b;
30 W_h1=x(1,:); // to access the 1st row
      of 2X1 matrix
31 W_e1=x(2,:); // to access the 2nd row
      of 2X1 matrix
32 disp("Solution (a)");
33 disp(sprintf("The hysteresis loss at full speed is
    %d W",W_h1));
34 disp(sprintf("The eddy current loss at full speed is
    %d W",W_e1));
35
36 //solution (b)
37 W_h2=speed*W_h1;
38 W_e2=(speed^2)*W_e1;
39 disp("Solution (b)");
40 disp(sprintf("The hysteresis loss at 125% of the
    full speed is %d W",W_h2));
41 disp(sprintf("The eddy current loss at 125% of the
    full speed is %d W",W_e2));
42
43 //END

```

Scilab code Exa 8.38 Speed of motor when flux per pole is increased by 10 percent

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 38
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 38");
7
8 //VARIABLE INITIALIZATION
9 v_t=215; //in Volts
10 r_a=0.4; //in Ohms

```

```

11 p=5*1000;                                //in Watts
12 N_g=1000;                                 //speed as generator in
13 ratio=1.1;                                //according to the
14                                         solution , _b : _a =1.1
15 //SOLUTION
16
17 //As generator
18 I_ag=p/v_t;
19 E_a=v_t+(I_ag*r_a);
20
21 //As motor
22 I_am=p/v_t;
23 E_b=v_t-(I_am*r_a);
24 N_m=(1/ratio)*N_g*(E_b/E_a);
25 N_m=round(N_m);                           //to round off the
26                                         value
26 disp(sprintf("The speed of the machine as motor is
27                                         %d rpm",N_m));
27
28 //END

```

Chapter 10

Three Phase Induction Machines

Scilab code Exa 10.2 6 pole wound rotor induction motor

```
1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 2
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 P=6;                                //number of poles
10 f1=60;                               //stator frequency in
                                         Hertz
11 N_r1=1140;                           //in rpm
12
13 //SOLUTION
14 N_s=(120*f1)/P;                     //synchronous speed
15 s1=(N_s-N_r1)/N_s;                  //slip at full load
16
17 //solution (a)
18 N_r2=0;                             //rotor speed at
```

```

        standstill is zero
19 s2=(N_s-N_r2)/N_s;
20 disp(sprintf("(a) At standstill , the slip is %f %%",
    s2*100));
21 if(s2>1)
22 disp("Since the slip is greater than 100%, the motor
    operates as brake");
23 end;
24 if(s2<0)
25 disp("Since the slip is negative , the motor operates
    as generator");
26 end;
27 f2=s2*f1;
28 disp(sprintf("And the frequency of rotor current is
    %d Hz",f2));
29 if(f2<0)
30 disp("Since frequency is negative , phase sequence of
    voltage induced in rotor winding is reversed");
31 end;
32
33 //solution (b)
34 N_r3=500;
35 s3=(N_s-N_r3)/N_s;
36 disp(sprintf("(b) At %d rpm , the slip is %f %%",N_r3
    ,s3*100));
37 if(s3>1)
38 disp("Since the slip is greater than 100%, the motor
    operates as brake");
39 end;
40 if(s3<0)
41 disp("Since the slip is negative , the motor operates
    as generator");
42 end;
43 f3=s3*f1;
44 disp(sprintf("And the frequency is %d Hz",f3));
45 if(f3<0)
46 disp("Since frequency is negative , phase sequence of
    voltage induced in rotor winding is reversed");

```

```

47 end;
48
49 //solution (c)
50 N_r4=500;
51 s4=(N_s+N_r4)/N_s; //as motor runs in
    opposite direction
52 disp(sprintf("(c) At %d rpm, the slip is %f %%",N_r4
    ,s4*100));
53 if(s4>1)
54 disp("Since the slip is greater than 100%, the motor
    operates as brake");
55 end;
56 if(s4<0)
57 disp("Since the slip is negative, the motor operates
    as generator");
58 end;
59 f4=s4*f1;
60 disp(sprintf("And the frequency is %d Hz",f4));
61 if(f4<0)
62 disp("Since frequency is negative, phase sequence of
    voltage induced in rotor winding is reversed");
63 end;
64
65 //solution (d)
66 N_r5=2000;
67 s5=(N_s-N_r5)/N_s;
68 disp(sprintf("(d) At %d rpm, the slip is %f %%",N_r5
    ,s5*100));
69 if(s5>1)
70 disp("Since the slip is greater than 100%, the motor
    operates as brake");
71 end;
72 if(s5<0)
73 disp("Since the slip is negative, the motor operates
    as generator");
74 end;
75 f5=s5*f1;
76 disp(sprintf("And the frequency is %d Hz",f5));

```

```

77 if(f5<0)
78 disp("Since frequency is negative , phase sequence of
      voltage induced in rotor winding is reversed");
79 end;
80
81 //END

```

Scilab code Exa 10.3 3 phase induction motor running at 1140 rpm

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 3
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 N_r=1140;                                // full load speed
     in rpm
10 f=60;                                     // frequency in Hz
11
12 //SOLUTION
13
14 //solution (i)
15 P=(120*f)/N_r;
16 P=round(P);                               //since the number
     of poles cannot be a fraction
17 disp(sprintf("(i) The number of poles is %d",P));
18
19 //solution (ii)
20 N_s=(120*f)/P;
21 s=(N_s-N_r)/N_s;
22 disp(sprintf("(ii) The slip at full load is %d %%",s
     *100));
23

```

```

24 //solution (iii)
25 f_r=s*f;
26 disp(sprintf("(iii) The frequency of the rotor
    voltge is %d Hz",f_r));
27
28 //solution (iv)
29 N1=(120*f_r)/P;                                //speed of rotor
    field w.r.t stator
30 N1=round(N1);
31 disp(sprintf("(iv) The speed of rotor field w.r.t
    rotor is %d rpm",N1));
32
33 //solution (v)
34 N2=N_r+N1;                                     //speed of stator
    field w.r.t stator field
35 N3=N_s-N2;                                     //speed of rotor
    field w.r.t stator field
36 disp(sprintf("(v) The speed of rotor field w.r.t
    stator field is %d rpm",N3));
37 disp("Hence, the rotor field is stationary w.r.t
    stator field");
38
39 //solution (vi)
40 ratio=10/100;                                  //since it is
    specified that slip is 10%
41 N_r=N_s*(1-ratio);
42 N_r=round(N_r);
43 disp(sprintf("(vi) The speed of rotor at 10% slip
    is %d rpm",N_r));
44 s1=(N_s-N_r)/N_s;
45 fr=s1*f;
46 disp(sprintf(" The rotor frequency at this speed is
    %f Hz",fr));
47
48 //solution (vii)
49 v=230;
50 ratio1=1/0.5;                                  //stator to rotor
    turns ratio

```

```

51 E_rotor=v*(1/ratio1);
52 E_rotor_dash=ratio*E_rotor;
53 disp(sprintf("(vii) The rotor induced emf is %f V" ,
54 E_rotor_dash));
55 //END

```

Scilab code Exa 10.4 3 phase squirrel cage motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 4
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 r2=0.2;                                // in Ohms
10 X2=2;                                    // in Ohms
11
12 //SOLUTION
13 s_m=r2/X2;
14
15 //solution (a)
16 s=1;
17 ratio1=2/((s/s_m)+(s_m/s));           // ratio of T_starting
18 and T_max
19 ratio2=2*ratio1;                      // ratio of T_starting
20 and T_full-load (T_max=2*T_full-load)
21 disp(sprintf("(a) If the motor is started by direct-
22 on-line starter , the ratio of starting torque to
23 full load torque is %f",ratio2));
24
25 //solution (b)
26 ratio3=(1/3)*ratio2;                  // In star-delta

```

```

        starter , T_starting=(1/3)*T_starting_of_DOL
23 disp(sprintf("(b) If the motor is started by star-
    delta starter , the ratio of starting torque to
    full load torque is %f",ratio3));
24
25 //solution (c)
26 ratio4=0.7*2*ratio2;           //due to 70% tapping
27 disp(sprintf("(c) If the motor is started by auto-
    transformer , the ratio of starting torque to full
    load torque is %f",ratio4));
28
29 //END

```

Scilab code Exa 10.5 Speed of motor

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 5
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 P1=12;                                //number of poles
    of alternator
10 N_s1=500;                             //synchronous speed
    of 12-pole alternator in rpm
11 P2=8;                                  //number of poles
    of motor
12 s=0.03;                               //slip of the motor
    in p.u.
13
14 //SOLUTION
15 f=(N_s1*P1)/120;                      //synchronous speed
16 N_s2=(120*f)/P2;

```

```

        of 8-pole alternator in rpm
17 N_r=N_s2*(1-s);
18 N_r=round(N_r);                                //to round off the
      value
19 disp(sprintf("The speed of the motor is %d rpm",N_r))
   );
20
21 //END

```

Scilab code Exa 10.6 Speed of 4 pole induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 6
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                         //number of poles
10 f_r=2;                                       //rotor frequency in
      Hertz
11 f_s=50;                                      //stator frequency in
      Hertz
12 E=400;                                       //line voltage in Volts
13 ratio=1/0.5;                                 //stator to rotor turn
      ratio
14
15 //SOLUTION
16 s=f_r/f_s;
17 N_s=(120*f_s)/P;                            //synchronous speed
18 N_r=N_s*(1-s);                            //rotor speed
19 N_r=round(N_r);
20 disp(sprintf("The speed of the motor is %d rpm",N_r))
   );

```

```

21 E_s=E/sqrt(3); //phase voltage=(line
                  voltage)/sqrt(3) for star connection
22 E_r=E_s*(1/ratio);
23 E_r_dash=s*E_r;
24 disp(sprintf("The rotor induced emf above 2 Hz is %f
                  V per phase",E_r_dash)); //Answer given in the
                  book is wrong
25
26 //END

```

Scilab code Exa 10.7 4 pole 3 phase induction motor

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 7
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 P=4; //number of poles
10 f=50; //frequency in Hz
11 r2=0.1; //rotor resistance in
            Ohms
12 X2=2; //standstill
            reactance in Ohms
13 E1=100; //induced emf between
            slip ring in Volts
14 N_r=1460; //full load speed in
            rpm
15
16 //SOLUTION
17
18 //solution (i)
19 N_s=(120*f)/P;

```

```

20 s_f1=(N_s-N_r)/N_s;
21 disp(sprintf("( i) The slip at full load is %f %%",
22 s_m=r2/X2;
23 disp(sprintf("The slip at which maximum torque
24 occurs is %f %%",s_m*100));
24
25 //solution (ii)
26 E2=E1/sqrt(3); //phase voltage=(line
27 disp(sprintf("( ii) The emf induced in rotor is %f V
28 per phase",E2));
29
30 X2_dash=s_f1*X2;
31 disp(sprintf("( iii) The rotor reactance per phase is
32 %f ",X2_dash));
33
34 z=sqrt((r2^2)+(X2_dash)^2);
35 I2=(s_f1*E2)/z;
36 disp(sprintf("( iv) The rotor current is %f A",I2));
37
38 //solution (v)
39 pow_fact_r=r2/z;
40 disp(sprintf("( v) The rotor power factor is %f (
41 lagging)",pow_fact_r));
42 //END

```

Scilab code Exa 10.8 3 phase induction motor with synchronous speed 1200 rpm

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 8
3

```

```

4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 N_s=1200;                                // synchronous speed in
                                             rpm
10 p_in=80;                                  // input power in kW
11 loss=5;                                   // copper and iron
                                             losses in kW
12 f_loss=2;                                 // friction and windage
                                             loss in kW
13 N=1152;                                   // rotor speed in rpm
14
15 //SOLUTION
16
17 //solution (a)
18 p_rotor=p_in-loss;
19 disp(sprintf("(a) The active power transmitted to
rotor is %d kW",p_rotor));
20
21 //solution (b)
22 s=(N_s-N)/N_s;
23 cu_loss=s*p_rotor;
24 disp(sprintf("(b) The rotor copper loss is %d kW",
cu_loss));
25
26 //solution (c)
27 p_m=(1-s)*p_rotor;                      // since P2:Pcu:Pm=1:s
                                             :(1-s)
28 disp(sprintf("(c) The mechanical power developed is
%d kW",p_m));
29
30 //solution (d)
31 p_shaft=p_m-f_loss;                     // output power
32 disp(sprintf("(d) The mechanical power developed to
load is %d kW",p_shaft));
33

```

```

34 //solution (e)
35 eff=p_shaft/p_in;
36 disp(sprintf("(e) The efficiency of the motor is %f
    %%",eff*100));
37
38 //END

```

Scilab code Exa 10.9 150 kW 6 pole star connected induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 9
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 p=150*1000;                                //in Watts
10 v=3000;                                     //in Volts
11 f=50;                                       //in Hertz
12 P=6;                                         //number of poles
13 ratio=3.6;                                   //ratio of stator
14                                                 turn to rotor turn
14 r2=0.1;                                      //rotor resistance
15                                                 in Ohms
15 L=3.61/1000;                                 //leakage
15                                                 inductance per phase in Henry
16
17 //SOLUTION
18
19 //solution (a)
20 X2=2*pi*f*L;
21 E1=v/sqrt(3);
22 E2=E1*(1/ratio);
23 z1=sqrt((r2^2)+(X2^2));

```

```

24 I2=E2/z1;                                // rotor current
25 I_s=I2/ratio;                            // stator current
26 N_s=(120*f)/P;
27 w=(2*pi*N_s)/60;
28 T_s1=(3*E2^2*r2)/(w*z1^2);
29 disp(sprintf("(a) The starting current is %f A and
    torque is %f N-m", I_s, T_s1));
30
31 //solution (b)
32 I_s1=30;
33 I_r=ratio*I_s1;
34 r=sqrt(((E2/I_r)^2)-(X2^2));
35 r_ext=r-r2;
36 z2=sqrt((r_ext^2)+(X2^2));
37 T_s2=(3*E2^2*r)/(w*z2^2);
38 disp(sprintf("(b) The external resistance is %f
    and torque is %f N-m", r_ext, T_s2));
39
40 //There answers are different due to precision of
    floating point numbers
41
42 //END

```

Scilab code Exa 10.10 6 pole 60 Hz induction motor

```

1 //CHAPTER 10— THREE-PHASE INDUCTION MACHINES
2 //Example 10
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 P=6;                                     //number of poles
10 f=60;                                    //in Hertz

```

```

11 p=48;                                // stator input in
   Watts
12 N_r=1140;                            // in rpm
13 cu_loss=1.4;                          // stator copper loss
   in Watts
14 cr_loss=1.6;                          // stator core loss
   in Watts
15 me_loss=1;                            // rotor mechanical
   loss in Watts
16
17 //SOLUTION
18 N_s=(120*f)/P;
19 s=(N_s-N_r)/N_s;
20 p_g=p-(cu_loss+cr_loss);            // rotor input
21 p_m=p_g*(1-s);                      // output mechanical
   power
22 p_sh=p_m-me_loss;                  // shaft power
23 eff=p_sh/p;
24 disp(sprintf("The motor efficiency is %f %%", eff
   *100));
25
26 //END

```

Scilab code Exa 10.11 4 pole induction motor

```

1 //CHAPTER 10— THREE-PHASE INDUCTION MACHINES
2 //Example 11
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 11");
7
8 //VARIABLE INITIALIZATION
9 P1=4;                                // number of poles
10 s=5/100;                             // slip

```

```

11 f=60;                                //frequency of
   synchronous generator in Hertz
12
13 //SOLUTION
14
15 //solution (a)
16 N_s=(120*f)/P1;                      //synchronous speed of
   generator in rpm with four poles
17 N_r=N_s*(1-s);                       //rotor or motor speed
   in rpm
18 N_r=round(N_r);                      //to round off the
   value
19 disp(sprintf("(a) The speed of the motor is %d rpm", N_r));
20
21 //solution (b)
22 P2=6;
23 N_s=(120*f)/P2;                      //synchronous speed of
   generator in rpm with six poles
24 disp(sprintf("(b) The speed of the generator is %d
   rpm", N_s));
25
26 //END

```

Scilab code Exa 10.12 3 phase 440 V distribution

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 12
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION
9 v=440;                                //line voltage in

```

```

    Volts
10 I=1200;                                // line current in
    Amperes
11 eff=0.85;                                // full load
    efficiency
12 pow_fact=0.8;                            // full load power
    factor
13
14 //SOLUTION
15
16 //solution (a)
17 I_f11=I/5;                               // starting current
    at rated voltage is 5 times the rated full-load
    current
18 p1=sqrt(3)*v*I_f11*pow_fact*eff;
19 disp(sprintf("(a) The maximum permissible kW rating
    when the motor when it starts at full voltage is
    %f kW",p1/1000));
20
21 //solution (b)
22 x=0.8;                                    // voltage is
    stepped down to 80%
23 I_f12=I/((x^2)*5);
24 p2=sqrt(3)*v*I_f12*pow_fact*eff;
25 disp(sprintf("(b) The maximum permissible kW rating
    when the motor is used with an auto-transformer
    is %f kW",p2/1000));
26
27 //solution (c)
28 I_f13=I/((0.578^2)*5);                  // since a star-
    delta is equivalent to an auto-transformer
    starter with 57.8% tapping
29 p3=sqrt(3)*v*I_f13*pow_fact*eff;
30 disp(sprintf("(c) The maximum permissible kW rating
    when the motor is used with star-delta starter is
    %f kW",p3/1000));
31
32 //The answers are slightly different due to

```

```
precision of floating point numbers
33
34 //END
```

Scilab code Exa 10.13 3 phase 50 Hz induction motor

```
1 //CHAPTER 10— THREE-PHASE INDUCTION MACHINES
2 //Example 13
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 13");
7
8 //VARIABLE INITIALIZATION
9 f=50;                                //frequency in Hertz
10 N_r=1440;                            //full-load rotor
    speed in rpm
11
12 //SOLUTION
13
14 //solution (a)
15 function N=speed(pole);           //function 'speed()',
    calculates the synchronous speed in rpm
16 N=(120*f)/pole;
17 endfunction;
18
19 pole=2;
20 N=speed(pole);
21 if(N>N_r & N<2000)
22 P=pole;
23 N_s1=N;
24 disp(sprintf("(a) The number of poles is %d",P));
25 end;
26 pole=4;
27 N=speed(pole);
```

```

28 if(N>N_r & N<2000)
29 P=pole;
30 N_s1=N;
31 disp(sprintf("(a) The number of poles is %d",P));
32 end;
33 pole=6;
34 N=speed(pole);
35 if(N>N_r & N<2000)
36 P=pole;
37 N_s1=N;
38 disp(sprintf("(a) The number of poles is %d",P));
39 end;
40
41 //solution (b)
42 s=(N_s1-N_r)/N_s1;
43 f_r=s*f;
44 disp(sprintf("(b) The slip is %f %% and rotor
frequency is %d Hz",s*100,f_r));
45
46 //solution (c)
47 w1=(2*pi*N_s1)/60;
48 disp(sprintf("(c(i)) The speed of stator field w.r.t
.stator structure is %f rad/s",w1)); //Answer
given in the book is wrong
49 N_s2=N_s1-N_r;
50 w2=(2*pi*N_s2)/60;
51 disp(sprintf("(c(ii)) The speed of stator field w.r.
t. rotor structure is %f rad/s",w2));
52
53 //solution (d)
54 factor=(2*pi)/60; //converting rpm to
radian/second
55 N_r1=(120*f_r)/P;
56 disp(sprintf("(d(i)) The speed of rotor field w.r.t
rotor structure is %f rad/s",N_r1*factor));
57 N_r2=N_r+N_r1;
58 disp(sprintf("(d(ii)) The speed of rotor field w.r.t
.stator structure is %f rad/s",N_r2*factor));

```

```

59 N_r3=N_s1-N_r2;
60 disp(sprintf("(d(iii)) The speed of rotor field w.r.
t. stator structure is %d rad/s",N_r3));
61
62 //END

```

Scilab code Exa 10.14 10 kW 400 V delta connected induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 14
3
4 clc;
5 clear
6 disp("CHAPTER 10");
7 disp("EXAMPLE 14");
8
9 //VARIABLE INITIALIZATION
10 p=10*1000; //in Watts
11 I_nl=8; //no load line
12 current in Amperes
13 p_ni=660; //input power at no
load in Watts
14 I_f1=18; //full load current
in Amperes
15 p_fi=11.20*1000; //input power at
full load in Watts
16 r=1.2; //stator resistance
per phase in Ohms
17 loss=420; //friction and
winding loss in Watts
18
19 //SOLUTION
20 //solution (a)
21 I1=I_nl/sqrt(3); //phase current=(

```

```

    line current)/sqrt(3) for delta connection
22 i_sq_r1=(I1^2)*r*3;                                //stator ((I^2)*R)
    loss at no load; since resistance is given in per
    phase, 3 needs to be multiplied for 3-phase
23 s_loss=(p_ni-loss)-(i_sq_r1);
24 disp(sprintf("(a) The stator core loss is %f W" ,
    s_loss));
25
26 //solution (b)
27 I2=I_f1/sqrt(3);
28 i_sq_r2=(I2^2)*r*3;
29 p_g=p_fi-s_loss-i_sq_r2;                          //air-gap power at
    full load
30 r_loss=p_g-p;
31 disp(sprintf("(b) The total rotor loss at full load
    is %f W" ,r_loss));
32
33 //solution (c)
34 o_loss=r_loss-loss;
35 disp(sprintf("(c) The total rotor ohmic loss at full
    load is %f W" ,o_loss));
36
37 //solution (d)
38 s_f1=o_loss/p_g;                                  //full load slip
39 N_s=1500;
40 N_r=N_s*(1-s_f1);
41 disp(sprintf("(d) The full load speed is %f rpm" ,N_r
    ));
42
43 //solution (e)
44 w=(2*pi*N_s)/60;
45 T_e=p_g/w;
46 disp(sprintf("(e) The internal torque is %f N-m" ,T_e
    ));
47 T_sh=p/(w*(1-s_f1));
48 disp(sprintf("      The shaft torque is %f N-m" ,T_sh))
    ;
49 eff=p/p_fi;

```

```

50 disp(sprintf("      The motor efficiency is %f %%",eff
   *100));
51
52 //The answers may be slightly different due to
   precision of floating point numbers
53
54 //END

```

Scilab code Exa 10.15 4 pole 3 phase SRIM

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 15
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 f_s=50;                             //in Hertz
11 f_l=20;                            //in Hertz
12
13 //SOLUTION
14
15 // solution (a)
16 N1=(120*f_s)/P;                     //speed of rotor
   field w.r.t. stator structure
17 N2=(120*f_l)/P;                     //speed of rotor
   field w.r.t. rotor structure
18 N_r1=N1-N2;
19 N_r2=N1+N2;
20 disp("(a) The prime mover should drive the
   rotor at two speeds-");
21 disp(sprintf("At %d rpm in the direction of stator
   field",N_r1));

```

```

22 disp(sprintf("At %d rpm against the direction of
    stator field",N_r2));
23
24 //solution (b)
25 s1=(N1-N_r1)/N1;
26 s2=(N1-N_r2)/N1;
27 ratio=s1/s2;                                // all other
    parameters in the expressions of the two voltages
    are equal
28 disp(sprintf("(b) The ratio of the two voltages at
    the two speeds is %d",ratio));
29
30 //solution (c)
31 disp("(c) The poles sequence of -3    rotor voltage
    do not remain the same");
32
33 //END

```

Scilab code Exa 10.16 3 phase induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 16
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 16");
7
8 //VARIABLE INITIALIZATION
9 ratio1=1.5;                                // ratio of starting
    torque (T_est) and full load torque (T_efl)
10 ratio2=2.5;                                // ratio of maximum
    torque (T_em) and T_efl
11
12 //SOLUTION
13

```

```

14 // solution (a) (taking the ratio of T_est and T_em)
15 s=1; //at starting slip is
      equal to 1
16
17 //directly solving the quadratic equation (a,b and c
      are the coefficients of the quadratic equation)
18 a=1;
19 b=-3.333;
20 c=1;
21 D=(b)^2-(4*a*c); //discriminant
22 sm1=(-b+sqrt(D))/(2*a);
23 sm2=(-b-sqrt(D))/(2*a);
24 if(sm1<=0 & sm2<=0) then
25 disp("The value of the slip at maximum torque (
      maximum slip) is not valid");
26 else if(sm1>0 & sm1<1)
27 disp(sprintf("The slip at maximum torque (maximum
      slip) is %f",sm1)); //slip is a unitless
      quantity
28 else if(sm2>0 & sm2<1)
29 disp(sprintf("The slip at maximum torque (maximum
      slip) is %f",sm2));
30 end;
31
32 //solution (b) (taking the ratio of T_efl and T_em)
33 //directly solving the quadratic equation
34 a=1;
35 b=-1.665;
36 c=0.111;
37 D=(b)^2-(4*a*c);
38 ans1=(-b+sqrt(D))/(2*a);
39 ans2=(-b-sqrt(D))/(2*a);
40 if(ans1>0 & ans1<1)
41 disp(sprintf("The full load slip is %f",ans1));
42 sfl=ans1;
43 else if(ans2>0 & ans2<1)
44 disp(sprintf("The full load slip is %f",ans2));
45 sfl=ans2;

```

```
46 end;
47
48 //solution (c)
49 I=sqrt(ratio1/sf1);
50 disp(sprintf("The rotor current at the starting in
      terms of full load current is %f A",I));
51
52 //END
```

Chapter 11

Single Phase Induction Motor

Scilab code Exa 11.1 Shaft torque

```
1 //CHAPTER 11- SINGLE PHASE INDUCTION MOTOR
2 //Examle 1
3
4 clc;
5 disp("CHAPTER 11");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 P=6;                                //number of poles
10 f=50;                               //frequency in Hz
11 p_fd=160;                            //gross power absorbed by
   forward field in Watts
12 p_bd=20;                            //gross power absorbed by
   backward field in Watts
13 N_r=950;                            //rotor speed in rpm
14 loss=75;                             //no load frictional loss
   in Watts
15
16 //SOLUTION
17 P_g=p_fd-p_bd;                      //air-gap power in Watts
18 N_s=(120*f)/P;                      //synchronous speed in rpm
```

```

19 S=(N_s-N_r)/N_s;           // slip
20 P_m=P_g*(1-S);           // mechanical power
   developed in Watts
21 P_o=P_m-loss;            // output or shaft power in
   Watts
22 w=(2*pi*N_r)/60;
23 T=P_o/w;                 // shaft torque in Newton-
   meters
24 disp(sprintf("The shaft torque is %f N-m",T));
25
26 //END

```

Scilab code Exa 11.2 Slip and resistance in forward and backward direction

```

1 //CHAPTER 11- SINGLE PHASE INDUCTION MOTOR
2 //Example 2
3
4 clc;
5 disp("CHAPTER 11");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 P=4;                      //number of poles
10 f=60;                     //frequency in Hz
11 N_r=1710;                  //rotor speed in rpm
12 r2=12.5;                  //rotor resistance at standstill
   in Ohms
13
14 //SOLUTION
15
16 N_s=(120*f)/P;           //synchronous speed in rpm
17
18 //solution (a)
19 disp("Solution (a)");
20 S_f=(N_s-N_r)/N_s;

```

```
21 disp(sprintf("The per unit slip in the direction of  
rotation is %f pu",S_f));  
22 r_f=0.5*(r2/S_f);  
23 disp(sprintf("The effective forward rotor resistance  
is %f ",r_f));  
24  
25 //solution (b)  
26 disp("Solution (b)");  
27 S_b=(N_s+N_r)/N_s;  
28 disp(sprintf("The per unit slip in the opposite  
direction is %f pu",S_b));  
29 r_b=0.5*(r2/S_b);  
30 disp(sprintf("The effective backward rotor  
resistance is %f ",r_b));  
31  
32 //END
```
