

Scilab Textbook Companion for  
Electronics Devices and Circuits  
by D. A. Bell<sup>1</sup>

Created by  
Poonam Pandurang Pingale  
B.Tech  
Electronics Engineering  
Vishwakarma Institute of Technology,Pune  
College Teacher  
Prof. D. G. Kanade  
Cross-Checked by  
K. V. P. Pradeep

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Electronics Devices and Circuits

**Author:** D. A. Bell

**Publisher:** Prentice Hall, India

**Edition:** 3

**Year:** 2000

**ISBN:** 81-203-1278-3

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

|                                                              |    |
|--------------------------------------------------------------|----|
| List of Scilab Codes                                         | 4  |
| 2 Semiconductor diodes                                       | 5  |
| 3 Bipolar Junction Transistors                               | 12 |
| 4 Transistor Biasing                                         | 21 |
| 5 Basic Transistor circuits                                  | 34 |
| 7 Transistor Specification and performance                   | 41 |
| 8 Field Effect Transistors                                   | 48 |
| 9 FET Biasing                                                | 51 |
| 10 Basic FET Circuits                                        | 58 |
| 11 Small Signal Amplifiers                                   | 64 |
| 12 Amplifiers with negative feedback                         | 78 |
| 13 IC operational amplifiers and Opamp applications          | 83 |
| 14 Operational amplifier frequency response and compensation | 88 |

|                                                           |     |
|-----------------------------------------------------------|-----|
| 15 sinusoidal Oscillators                                 | 92  |
| 16 Power supplies Breakdown diodes and Voltage regulators | 96  |
| 17 Large signal amplifiers                                | 106 |
| 18 Thyristors and unijunction transistors                 | 114 |
| 19 Optoelectronic devices                                 | 121 |
| 20 Miscellaneous devices                                  | 127 |
| 21 Electron tubes                                         | 132 |

# List of Scilab Codes

|         |                                                               |    |
|---------|---------------------------------------------------------------|----|
| Exa 2.1 | dc load line characteristics . . . . .                        | 5  |
| Exa 2.2 | Finding Load resistance . . . . .                             | 6  |
| Exa 2.3 | Finding new source value . . . . .                            | 6  |
| Exa 2.4 | diode Forward Current . . . . .                               | 7  |
| Exa 2.5 | forward voltage drop . . . . .                                | 7  |
| Exa 2.6 | Half wave rectification . . . . .                             | 8  |
| Exa 2.7 | Maximum operating frequency . . . . .                         | 9  |
| Exa 2.8 | Maximum forward current . . . . .                             | 10 |
| Exa 2.9 | Diode forward current and reverse voltage .                   | 10 |
| Exa 3.1 | Finding collector and emitter current of transistor . . . . . | 12 |
| Exa 3.2 | Finding Emitter and base current . . . . .                    | 13 |
| Exa 3.3 | Current Gain Characteristics . . . . .                        | 14 |
| Exa 3.4 | Finding Emitter and collector current . . . .                 | 14 |
| Exa 3.5 | Finding Beta of Transistor . . . . .                          | 15 |
| Exa 3.6 | Finding h-parameters for CE configuration .                   | 17 |
| Exa 3.7 | Finding h-parameters . . . . .                                | 18 |
| Exa 3.8 | Finding h-parameters and Common base gain                     | 19 |
| Exa 4.1 | Dc load line . . . . .                                        | 21 |
| Exa 4.2 | Maximum undistorted output . . . . .                          | 22 |
| Exa 4.3 | Designing fixed bias circuit . . . . .                        | 23 |
| Exa 4.4 | Analyzing fixed bias circuit . . . . .                        | 23 |
| Exa 4.5 | Design collector to base Bias circuit . . . .                 | 24 |
| Exa 4.6 | Analyzing collector to base Bias circuit . . .                | 24 |
| Exa 4.7 | Analysing common-emitter current Bias circuit . . . . .       | 25 |
| Exa 4.8 | Analyse emitter current Bias circuit . . . .                  | 26 |
| Exa 4.9 | Design emitter current Bias circuit using 2N3904              | 27 |

|          |                                                                             |    |
|----------|-----------------------------------------------------------------------------|----|
| Exa 4.10 | Design Common emitter current bias circuit                                  | 28 |
| Exa 4.11 | Finding Stability factor . . . . .                                          | 29 |
| Exa 4.12 | Dc and ac load line . . . . .                                               | 30 |
| Exa 4.13 | Finding Vce in cutoff and saturation . . . . .                              | 31 |
| Exa 4.14 | Finding Base resistor . . . . .                                             | 31 |
| Exa 4.15 | Finding Base and collector resistor . . . . .                               | 32 |
| Exa 5.1  | Impedances and Gain for common emitter circuit . . . . .                    | 34 |
| Exa 5.2  | Effect on performance of common emitter circuit . . . . .                   | 35 |
| Exa 5.3  | AC analysis of common-emitter circuit . . . . .                             | 36 |
| Exa 5.4  | Circuit Impedances and Gain for common emitter circuit . . . . .            | 37 |
| Exa 5.5  | Effect on input impedance . . . . .                                         | 38 |
| Exa 5.6  | Circuit Impedances and Gain for common base circuit . . . . .               | 38 |
| Exa 5.7  | Input impedance,output impedance and voltage gain of CE amplifier . . . . . | 39 |
| Exa 7.1  | Finding collector current . . . . .                                         | 41 |
| Exa 7.2  | Maximum power Dissipation . . . . .                                         | 42 |
| Exa 7.3  | Selecting heat sink . . . . .                                               | 42 |
| Exa 7.4  | Change in Output power with variation in signal frequencies . . . . .       | 43 |
| Exa 7.5  | Output power variation . . . . .                                            | 44 |
| Exa 7.6  | Upper 3dB point . . . . .                                                   | 44 |
| Exa 7.7  | Input capacitor . . . . .                                                   | 45 |
| Exa 7.8  | Output noise . . . . .                                                      | 46 |
| Exa 8.1  | FET Transfer characteristics . . . . .                                      | 48 |
| Exa 8.2  | Min and max Transfer characteristics for FET                                | 48 |
| Exa 8.3  | Find Transconductance(gm) . . . . .                                         | 49 |
| Exa 8.4  | Finding gm . . . . .                                                        | 50 |
| Exa 9.1  | Dc load line for FET . . . . .                                              | 51 |
| Exa 9.2  | Finding levels of Id and Vds . . . . .                                      | 51 |
| Exa 9.3  | Design fixed bias circuit FET . . . . .                                     | 52 |
| Exa 9.4  | Analyze fixed bias circuit FET . . . . .                                    | 53 |
| Exa 9.5  | Design self bias circuit FET . . . . .                                      | 53 |
| Exa 9.6  | Analyze self bias circuit FET . . . . .                                     | 54 |
| Exa 9.7  | Design potential divider circuit FET . . . . .                              | 55 |

|           |                                                                                  |    |
|-----------|----------------------------------------------------------------------------------|----|
| Exa 9.8   | Analyze potential divider circuit FET . . . . .                                  | 56 |
| Exa 9.9   | Finding $R_d$ input voltage $R_g$ . . . . .                                      | 57 |
| Exa 10.1  | Input and output Impedances and voltage gain<br>for Common source JFET . . . . . | 58 |
| Exa 10.2  | Voltage gain for Common source JFET . . . . .                                    | 59 |
| Exa 10.3  | Impedance and gain for Common source JFET . . . . .                              | 59 |
| Exa 10.4  | Input and output Impedances and gain for<br>Common drain JFET . . . . .          | 60 |
| Exa 10.5  | Impedance and gain for Common drain JFET . . . . .                               | 61 |
| Exa 10.6  | Impedances, $v_o$ and gain for Common gate<br>JFET . . . . .                     | 61 |
| Exa 10.7  | Impedance, Output voltage( $v_o$ ) and gain for<br>Common gate JFET . . . . .    | 62 |
| Exa 11.1  | Resistors for CE amplifier . . . . .                                             | 64 |
| Exa 11.2  | Capacitors for CE amplifier . . . . .                                            | 65 |
| Exa 11.3  | Resistors for CS amplifier . . . . .                                             | 66 |
| Exa 11.4  | Capacitors for CS amplifier . . . . .                                            | 66 |
| Exa 11.5  | Design 2 stage amplifier . . . . .                                               | 67 |
| Exa 11.6  | Analyze 2 stage amplifier . . . . .                                              | 68 |
| Exa 11.7  | Suitable Resistors for 2 stage amplifier . . . . .                               | 69 |
| Exa 11.8  | Capacitors for 2 stage amplifier . . . . .                                       | 70 |
| Exa 11.9  | Resistance values for 2 stage amplifier . . . . .                                | 71 |
| Exa 11.10 | Capacitor values for 2 stage amplifier . . . . .                                 | 72 |
| Exa 11.11 | AC analysis of 2 stage amplifier . . . . .                                       | 73 |
| Exa 11.12 | Design DC feedback amplifier . . . . .                                           | 73 |
| Exa 11.13 | Resistors for BIFET amplifier . . . . .                                          | 75 |
| Exa 11.14 | Capacitors for BIFET amplifier . . . . .                                         | 76 |
| Exa 12.1  | Modification of 2 stage amplifier to voltage<br>series feedback . . . . .        | 78 |
| Exa 12.2  | Analyze negative feedback amplifier . . . . .                                    | 79 |
| Exa 12.3  | Single stage CE amplifier using current feed-<br>back . . . . .                  | 80 |
| Exa 13.1  | Output voltage of differential amplifier . . . . .                               | 83 |
| Exa 13.2  | Impedance and gain for differential amplifier<br>circuit . . . . .               | 84 |
| Exa 13.3  | Design voltage follower . . . . .                                                | 84 |
| Exa 13.4  | Design non inverting amplifier . . . . .                                         | 85 |
| Exa 13.5  | Design inverting amplifier . . . . .                                             | 86 |



|           |                                                                    |     |
|-----------|--------------------------------------------------------------------|-----|
| Exa 13.6  | Design Schmitt trigger . . . . .                                   | 86  |
| Exa 14.1  | Design inverting amplifier . . . . .                               | 88  |
| Exa 14.2  | Design non inverting amplifier . . . . .                           | 89  |
| Exa 14.3  | Design inverting amplifier with a gain of 50 . . . . .             | 89  |
| Exa 14.4  | Design voltage follower . . . . .                                  | 90  |
| Exa 14.5  | Upper cutoff frequency of inverting amplifier . . . . .            | 90  |
| Exa 15.1  | Resistor and capacitor values for phase shift oscillator . . . . . | 92  |
| Exa 15.2  | Design colpitts oscillator . . . . .                               | 93  |
| Exa 15.3  | Design Wein Bridge oscillator . . . . .                            | 94  |
| Exa 15.4  | Design phase shift oscillator . . . . .                            | 94  |
| Exa 16.1  | Reservoir Capacitor for half wave rectifier . . . . .              | 96  |
| Exa 16.2  | Diode specification for half wave rectifier . . . . .              | 97  |
| Exa 16.3  | Reservoir Capacitor for bridge rectifier . . . . .                 | 98  |
| Exa 16.4  | Diode specification and Capacitor for Zener circuit . . . . .      | 99  |
| Exa 16.5  | Design Zener diode voltage reference . . . . .                     | 99  |
| Exa 16.6  | LR and RR for regulator circuit . . . . .                          | 100 |
| Exa 16.7  | LR and RR for rectifier and filter circuit . . . . .               | 101 |
| Exa 16.8  | Design voltage regulator . . . . .                                 | 102 |
| Exa 16.9  | Design opamp voltage regulator . . . . .                           | 103 |
| Exa 16.10 | Design voltage regulator circuit . . . . .                         | 104 |
| Exa 16.11 | Design voltage regulator using LM217 IC . . . . .                  | 105 |
| Exa 17.1  | Dc ac load line for CE circuit . . . . .                           | 106 |
| Exa 17.2  | Maximum Efficiency of Transformer . . . . .                        | 107 |
| Exa 17.3  | Transformer output for class B . . . . .                           | 108 |
| Exa 17.4  | Design capacitor coupled amplifier . . . . .                       | 109 |
| Exa 17.5  | Design capacitors of amplifier circuit . . . . .                   | 110 |
| Exa 17.6  | Supply and output voltages for amplifier circuit . . . . .         | 111 |
| Exa 17.7  | Analyze MOSFET power amplifier circuit . . . . .                   | 112 |
| Exa 18.1  | Analyze SCR circuit . . . . .                                      | 114 |
| Exa 18.2  | Design SCR circuit . . . . .                                       | 115 |
| Exa 18.3  | Design resistor for 4 layer diode circuit . . . . .                | 116 |
| Exa 18.4  | Analyze UJT circuit . . . . .                                      | 117 |
| Exa 18.5  | Emitter voltages for UJT circuit . . . . .                         | 117 |
| Exa 18.6  | Frequency of oscillation for UJT circuit . . . . .                 | 118 |
| Exa 18.7  | Emitter resistance for UJT circuit . . . . .                       | 118 |

|          |                                                                      |     |
|----------|----------------------------------------------------------------------|-----|
| Exa 18.8 | DC Analysis UJT circuit . . . . .                                    | 119 |
| Exa 19.1 | Light intensity . . . . .                                            | 121 |
| Exa 19.2 | Series resistance and dark current . . . . .                         | 121 |
| Exa 19.3 | Design photoconductive cell circuit . . . . .                        | 122 |
| Exa 19.4 | Dc load line for photodiode . . . . .                                | 123 |
| Exa 19.5 | Total cells for satellite . . . . .                                  | 124 |
| Exa 19.6 | Output voltage of phototransistor circuit . .                        | 124 |
| Exa 19.7 | Design LED and transistor circuit . . . . .                          | 125 |
| Exa 20.1 | Capacitance tuning ratio . . . . .                                   | 127 |
| Exa 20.2 | Resonance frequency . . . . .                                        | 128 |
| Exa 20.3 | Value of resistor in thermistor circuit . . . .                      | 128 |
| Exa 20.4 | Piecewise linear characteristics . . . . .                           | 129 |
| Exa 20.5 | Gain for tunnel diode circuit . . . . .                              | 130 |
| Exa 21.1 | Transconductance and constant current char-<br>acteristics . . . . . | 132 |
| Exa 21.2 | Impedance and gain for vacuum triode circuit                         | 133 |
| Exa 21.3 | DC load line for CC amplifier . . . . .                              | 134 |

# Chapter 2

## Semiconductor diodes

Scilab code Exa 2.1 dc load line characteristics

```
1 //chapter 2
2 //example 2.1
3 //page 33
4 clear all;
5 clc ;
6 //given
7 R1=100; //load resistor in ohm
8 Es=5; //supply voltage in volts
9 //for point A
10 If1=0; //forward current through diode ,thus drop
    across resistor is 0 v
11 Ef1=5; //Ef=voltage drop across diode in volts
12
13 //for point B
14 Ef2=0;
15 If2=Es/R1; //in Ampere
16 If2=If2*10^3; //in mA
17
18 plot([Ef1 Ef2],[If1 If2],'-.*')
19 xtitle('dc load line ','voltage drop across diode(V) '
    , 'current through diode(mA)')
```

```
20 a=gca();
21 a.data_bounds=[-0.5 -0.5;5.1 52]
22 printf('dc load line passes through points A(5,0),B
      (0,50)')
```

---

### Scilab code Exa 2.2 Finding Load resistance

```
1 //chapter 2
2 //example 2.2
3 //page 34
4 clear;
5 clc ;
6 //given
7 If=30;//forward current through diode in mA
8 Es=5;//supply voltage in volts
9 Ef=5;//when If=0 from equation  $E_f=E_s-I_f*R_l$ 
10 deltaEf=2;// from load line
11 deltaIf=0.015;//in ampere
12 Rl=deltaEf/deltaIf;//load resistance in ohm
13 printf('load resistance is %d ohm',Rl)
```

---

### Scilab code Exa 2.3 Finding new source value

```
1 //chapter 2
2 //example 2.3
3 //page 34
4 clear;
5 clc ;
6 //given
7 If=50;//in mA
8 Rl=100;//in ohm
9 Ef=1.1;//in volts at point Q plotted at If=50mA
10 //finding voltage across Rl(Ef)
```

```

11 deltaIf=0.05; //in Ampere (when If changes from 50–0
    mA)
12 deltaEf=deltaIf*R1; //in volts
13 newEf=Ef+deltaEf;
14 Es=6.1; //read from point A on load line after
    joining A and Q
15 printf('New value of Ef is %.1f V .Therefore Es(
    supply voltage) is %.1f V',newEf,Es)

```

---

#### Scilab code Exa 2.4 diode Forward Current

```

1 //chapter 2
2 //example 2.4
3 //page 40
4 clear;
5 clc ;
6 //given
7 Vf=1.1; //forward drop across diode in volts
8 Es=60; //supply voltage in volts
9 R1=100; //load resistor in ohm
10 If= ((Es-Vf)/R1)*10^3; //forward current through
    diode in mA
11 printf('The diode forward current is %d mA',If)

```

---

#### Scilab code Exa 2.5 forward voltage drop

```

1 //chapter 2
2 //example 2.5
3 //page 40
4 clear;
5 clc ;
6 //given

```

```

7 VF=0.7; //forward voltage drop across diode for
  temperature range 0–65 degree celcius
8 deltaT1=40; //change in temperature for T=65 in
  degree celcius
9 deltaVF=-1.8/10^3; //change in forward voltage drop
  per degree celcius
10 //finding required VF
11 VFmin=VF+deltaVF*deltaT1; //minimum forward voltage
  drop in volts
12
13 deltaT2=-25; //change in temperature for T=0 in
  degree celcius
14 VFmax=VF+deltaVF*deltaT2; //maximum forward voltage
  drop in volts
15
16 printf('Minimum and maximum values of forward
  voltage drop are %.3f V & %.3f V.',VFmin,VFmax)

```

---

#### Scilab code Exa 2.6 Half wave rectification

```

1 //chapter 2
2 //example 2.6
3 //page 42
4 clear;
5 clc ;
6 //given
7 VF=0.7; //forward voltage drop across diode
8 Rl=500; //load resistor in ohm
9 Vp=30; //input voltage in volts
10
11 //peak o/p voltage
12 Ep=Vp-VF;
13
14 //peak o/p current
15 Ip=((Vp-VF)/Rl)*10^3;

```

```

16
17 //for half wave rectifier
18 Iave= (0.637 * Ip)/2; //average current through
    diode
19 //power dissipation
20 PD= Iave * VF;
21
22 //Peak Reverse Voltage (PRV)
23 PRV=2*Vp;
24
25 printf( '\npeak o/p voltage=%0.1f V\n',Ep);
26 printf( 'peak o/p current=%0.1f mA\n',Ip);
27 printf( 'power dissipation=%0d mW\n',PD);
28 printf( 'Peak Reverse Voltage (PRV)=%0d V',PRV);

```

---

#### Scilab code Exa 2.7 Maximum operating frequency

```

1 //chapter 2
2 //example 2.7
3 //page 49
4 clear;
5 clc ;
6 //given
7 trr1=10; //in ns for 1N915
8 trr2=3; //in ns for 1N917
9 //finding maximum operating frequency for 1N915
10 fmax1=1/(10*trr1)*10^3; //in MHz
11
12 //finding maximum operating frequency for 1N917
13 fmax2=1/(10*trr2)*10^3; //in MHz
14
15 printf( 'maximum operating frequency for 1N915=%0d MHz
    \n',fmax1);
16 printf( ' maximum operating frequency for 1N917=%0d
    MHz',fmax2);

```

---

**Scilab code Exa 2.8** Maximum forward current

```
1 //chapter 2
2 //example 2.8
3 //page 52
4 clear;
5 clc ;
6 //given
7 T1=25; //degreeC
8 T2=65; //degreeC
9 deltaT=T2-T1;
10 P1=700; //max power dissipation in mW
11 DF=5; //derating factor in mW/degree celcius
12 VF=0.7; //forward voltage drop across diode
13
14 //maximum forward current at 25 degreeC
15 If1=P1/VF*10^-3;
16
17 //maximum forward current at 65 degreeC
18 P2=P1-(deltaT*DF); //mW
19 If2=P2/VF;
20
21 printf('maximum forward current at 25 degreeC=%d A\n', If1);
22 printf(' maximum forward current at 65 degreeC=%d mA', If2);
```

---

**Scilab code Exa 2.9** Diode forward current and reverse voltage

```
1 //chapter 2
2 //example 2.9
```



```

3 //page 54
4 clear all;
5 clc ;
6 //given
7 E=5; //i/p voltage in volts
8 Io=2; //o/p current in mA
9 Eo=4.5; //o/p voltage in volts
10 VF=0.7; //forward voltage drop across diode
11
12 //finding value of R1
13 R1=(E-Eo)/Io*10^3;
14
15 Er=E; //diode reverse voltage
16
17 // forward current
18 If=(E-VF)/R1*10^3;
19
20 printf( '\nR1=%dohm\ndiode reverse voltage=%dv\
nforward current=%.1f mA ', R1, Er, If)

```

---

# Chapter 3

## Bipolar Junction Transistors

Scilab code Exa 3.1 Finding collector and emitter current of transistor

```
1 //chapter 3
2 //example 3.1
3 //page 70
4
5 clear;
6 clc ;
7 //given
8 alphadc=0.98;

    //common base current gain factor
9 Icbo=5 ;

    //collector to base leakage current
10 Ib=100;

    //base current
11 //calculating collector current
12 Ic=((alphadc * Ib)+ Icbo)/(1-alphadc);
13 Ic=Ic/1000;
14 printf('\ncollector current is %.2f mA',Ic);
15
```

```

16 //relation between Ie and Ic
17 Ib=Ib/1000;
18 Ie=Ic+Ib;
19 printf('\n emitter current is %.2f mA',Ie);
20
21
22 //taking ratio of Ic and Ie which is alphadc
23 a =Ic/Ie
24 printf('\n Ic/Ie=%.2f',a)
25 printf('\n thus Ic/Ie is approximately equal to
    alphadc') ;

```

---

### Scilab code Exa 3.2 Finding Emitter and base current

```

1 //chapter 3
2 //example 3.2
3 //page 71
4
5 //alphadc is common base gain factor
6 //betadc is dc common emitter gain factor
7 //Ib=base current
8 //Ic=collector
9 clear all;
10 clc ;
11 //given currents in mA
12 Ic=5202;
13 Ic1=10*10^3;
14 Icbo=2 ;

    //collector to bae leakage current
15 Ib=50;
16 //finding betadc
17 betadc=(Ic-Icbo)/(Ib+Icbo)
18 printf('\n betadc=%d',betadc)
19 //finding emitter current

```

```

20 Ie=(Ic+Ib)/1000;
21 printf( '\nIe=%0.3 f mA',Ie);
22 //finding alphadc
23 alphadc=(Ic-Icbo)/Ie/10^3;
24 printf( '\nalphadc=%0.2 f',alphadc);
25 //finding new Ib from equation Ic = betadc*Ib+(
    betadc+1)*Icbo
26 newIb=round((Ic1-(betadc+1)*Icbo)/betadc);
27 printf( '\nnew Ib=%0.1 f microA ',newIb)

```

---

### Scilab code Exa 3.3 Current Gain Characteristics

```

1 //chapter 3
2 //example 3.3
3 //page 77
4 //to plot current gain characteristics from common
    base output characteristics of a transistor
5 //from output characteristics ,for Vcb=2 V,6 V
6 Ie=[1 2 3 4]; //emitter current in mA
7 Ic=[1 1.9 2.9 3.9]; //emitter current in mA
8 mtlb_axis([-4 0 0 4])
9 plot(-Ie,Ic);
10 xtitle( 'current gain characteristics', 'emitter
    current', 'collector current' ) ;

```

---

### Scilab code Exa 3.4 Finding Emitter and collector current

```

1 //chapter 3
2 //example 3.4
3 //page 78
4 //to find Ie and Ic for a transistor connected in
    common base configuration
5 clear;

```

```

6  clc ;
7  //given
8  Veb=0.7;

    //emitter to base voltage in volts
9  Vcb=6;

    //collector to base voltage in volts
10 //finding Ie from input characteristics of common
    base configuration
11 if Vcb==6 & Veb==0.7 then
12     Ie=2;

    //emitter current
13 end
14 printf( '\nIe=%d mA',Ie);
15
16 //finding Ic from output characteristics of common
    base configuration
17 if Vcb==6 & Ie==2 then
18     Ic=2;

    //collector current
19 end
20 printf( '\nIc1=%d mA',Ic);
21
22
23 //finding Ic from current gain characteristics of
    common base configuration
24 if Vcb==6 & Ie==2 then
25     Ic=2;
26 end
27 printf( '\nIc2=%d mA',Ic);

```

---

**Scilab code Exa 3.5 Finding Beta of Transistor**

```

1 //chapter 3
2 //example 3.5
3 //page 82
4
5 //find Ib(base current) Ic(collector current) for
   common emitter configuration from i/p,o/p,
   current gain characteristics
6 clear;
7 clc ;
8 //given
9 Vbe=0.7;

   //base emitter voltage in volts
10 Vce=6;

   //collector emitter voltage in volts
11
12 //finding Ie from input characteristics of common
   emitter configuration
13 if Vce==6 & Vbe==0.7 then
14     Ib=60;

        //in microA
15 end
16 printf( '\nIb=%d microA ',Ib);
17
18 //finding Ic from output characteristics of common
   emitter configuration
19 if Vce==6 & Ib==60 then
20     Ic=3.3;

        //in mA
21 end
22 printf( '\nIc1=%0.1 f mA ',Ic);
23
24 //finding Ic from current gain characteristics of
   common emitter configuration
25 if Vce==6 & Ib==60 then

```

```

26      Ic=3.3;

          //in mA
27
28  end
29  printf( '\nIc2=%0.1 f mA', Ic);
30
31  Betadc=Ic/(Ib/10^3);

          //betadc is dc common emitter gain factor
32  printf( '\nbetadc =%d', Betadc);

```

---

#### Scilab code Exa 3.6 Finding h-parameters for CE configuration

```

1  //chapter 3
2  //example 3.4
3  //page 78
4
5  //to find values of h parameters (hoe,hfe) for
   common emitter configuration
6  clear;
7  clc ;
8
9  //given
10 Ib=60;

       //base current in microA
11 Vce=4.5;

       //collector to emitter voltage in volts
12
13 //from output characteristics from point A
14 deltaIc=0.35/1000;

       //change in collector current

```

```

15 deltaVce=3.5;

    //change in collector to emitter voltage
16 hoe=(deltaIc/deltaVce)*10^6

    //output conductance
17
18 //from current gain characteristics from point B
19 deltaIc=2100;

    //change in collector current
20 deltaIb=35;

    //change in base current
21 hfe=deltaIc/deltaIb

    //forward current transfer ratio
22 printf( '\nhfe=%d\hoe=%d microS ',hfe,hoe);

```

---

### Scilab code Exa 3.7 Finding h-parameters

```

1 //chapter 3
2 //example 3.7
3 //page 92
4 //to find values of h parameters (hie,hre)for common
    emitter configuration
5 clear all;
6 clc ;
7 //given
8 Ib=60;

    //base current in microA
9 Vce=4.5;

    //collector to emitter voltage in volts

```



```

10
11 //from input characteristics from point C
12 deltaVbe=0.15;

    //change in base to emitter voltage
13 deltaIb=120/10^6;

    //change in base current
14 hie=(deltaVbe/deltaIb)/1000;

    //input resistance
15
16 //from input characteristics from point D
17 deltaVbe=0.01;
18 deltaVce=5;

    //change in collector to emitter voltage
19 hre=1000*deltaVbe/deltaVce;

    //reverse voltage transfe ratio
20
21
22 printf('\ninput resistance:\nhie=%.2f Kohm\nreverse
    voltage transfer ratio:\nhre=%dx(10^-3)',hie,hre)
    ;

```

---

### Scilab code Exa 3.8 Finding h-parameters and Common base gain

```

1 //chapter 3
2 //example 3.4
3 //page 78
4 //find hfc,hib,alpha for common emitter
    configuration
5 clear;
6 clc ;

```

```

7
8 //given
9 hfe=60;

    //forward current transfer ratio for common
    emitter configuration
10
11 hie=1250;

    //input resistance for common emitter
    configuration
12
13 hfc= -(1+hfe);

    //forward current transfer ratio for common
    collector configuration
14
15 hib =hie/(1+hfe);

    //input resistance for common base configuration
16
17 alpha=hfe/(1+hfe);

    // current gain factor
18
19 printf( '\nalpha=%.3 f\nhib=%0.1 f ohm\nhfc=%d',alpha,
    hib,hfc);

```

---

# Chapter 4

## Transistor Biasing

Scilab code Exa 4.1 Dc load line

```
1 //chapter 4
2 //example 4.1
3 //page 102
4 clear all;
5 clc ;
6 //given
7 Rc=9; //collector resistance in kohm
8 Ic1=0; //collector current
9 Vcc=20; //supply voltage
10 Vce1=Vcc; //point A(Vce,Ic)=(20,0)
11 Vce2=0; //collector to emitter voltage V
12 Ic2=Vcc/Rc; //mA
13 //point F(Vce2,Ic2)
14 plot([Vce1 Vce2],[Ic1 Ic2],'-.*');
15 xtitle('dc load line','Vce in V','Ic in mA');
16 a=gca();
17 a.data_bounds=[-1 -0.5;21 3]
18 printf('dc load line passes through points A(20,0),F
    (0,2.2)')
```

---

#### Scilab code Exa 4.2 Maximum undistorted output

```
1 //chapter 4
2 //example 4.2
3 //page 104
4 clear all;
5 clc ;
6 //given
7 Rc=2.2; //collector resistance in kohm
8 Vcc=18; //supply voltage
9 Ib=40; //base current in microA
10 Ic1=0; //collector current
11 Vce1=Vcc; //point A(Vce,Ic)=(18,0)
12 Vce2=0; //collector to emitter voltage V
13 Ic2=Vcc/Rc; //mA
14 printf('dc load line passes through points A(18,0),B
    (0,8.2)')
15 //point B(Vce2,Ic2)
16 plot([Vce1 Vce2],[Ic1 Ic2], '-.*');
17 xtitle('dc load line','Vce in V','Ic in mA');
18 a=gca();
19 a.data_bounds=[-0.5 -0.5;19 8.5]
20
21 //from intersection of dc load line and Ib=40microA,
    pointQ
22 Ic=4.25; //mA
23 Vce=8.7; //V
24 //for point Q1
25 Vce1=1.2;
26 deltaVce1=Vce1-Vce;
27 //for point Q2
28 Vce1=16.7;
29 deltaVce2=Vce1-Vce;
30 printf("\n maximum undistorted output is +-7.5 V")
```

---

#### Scilab code Exa 4.3 Designing fixed bias circuit

```
1 //chapter 4
2 //example 4.3
3 //page 106
4 clear all;
5 clc ;
6 //given
7 hfe=100;
8 Vcc=15; //supply voltage
9 //dc bias conditions
10 Vce=5; //V
11 Ic=5; //mA
12 Vbe=0.7;
13 Rc=(Vcc-Vce)/Ic;
14 Ib=1000*Ic/hfe;
15 Rb=1000*(Vcc-Vbe)/Ib;
16 printf("\nValue of Rc=%d kohm,Rb=%d kohm",Rc,Rb);
```

---

#### Scilab code Exa 4.4 Analyzing fixed bias circuit

```
1 //chapter 4
2 //example 4.4
3 //page 107
4 clear;
5 clc ;
6 //given
7 hfe1=50;
8 Vcc=15; //supply voltage
9 Vbe=0.7;
10 Rb=286;
11 Ib=1000*(Vcc-Vbe)/Rb;
```

```

12 Rc=2; // collector resistance in kohm
13 Ic=hfe1*Ib/1000;
14 Vce=Vcc-(Ic*Rc);
15 printf("\nFor hfe=50,Vce=%d V, Ic=%d mA, Ib=%d
    microA",Vce,Ic,Ib);
16
17 hfe2=150;
18 Ic=hfe2*Ib/1000;
19 Vce=Vcc-(Ic*Rc);
20 printf("\nFor hfe=150,Vce=%d V, Ic=%d mA, Ib=%d
    microA",Vce,Ic,Ib);

```

---

#### Scilab code Exa 4.5 Design collector to base Bias circuit

```

1 //chapter 4
2 //example 4.5
3 //page 102
4 clear all;
5 clc ;
6 //given
7 Vcc=15; //supply voltage
8 Vce=5; //collector to emitter voltage
9 Ic=5; //mA
10 hfe=100; Vbe=0.7;
11 Ib=1000*Ic/hfe; //microA
12 Rb=1000*(Vce-Vbe)/Ib;
13 Rc=(Vcc-Vce)/(Ib*10^-3+Ic);
14 printf("\nValue of Rc=%d kohm\nstandard value 1.8
    kohm\nRb=%d kohm\nstandard value 82 kohm",Rc,Rb);

```

---

#### Scilab code Exa 4.6 Analyzing collector to base Bias circuit

```

1 //chapter 4

```

```

2 //example 4.6
3 //page 109
4 clear;
5 clc ;
6 //given
7 hfe1=50; //minimum value
8 hfe2=150; //maximum value
9 Vcc=15; //supply voltage
10 Rc=1.98; //collector resistance in kohm
11 Rb=86; //base resistance in kohm
12 Vbe=0.7;
13 Ic1=(Vcc-Vbe)/(Rc*(1+1/hfe1)+Rb/hfe1);
14 Vce1=(Ic1/hfe1)*Rb+Vbe;
15
16 Ic2=(Vcc-Vbe)/(Rc*(1+1/hfe2)+Rb/hfe2);
17 Vce2=((Ic2/hfe2)*Rb)+Vbe;
18
19 printf("\nfor hfe=50,Vce=%0.1 f V, Ic=%0.2 f mA",Vce1,Ic1
    );
20 printf("\nfor hfe=150,Vce=%0.1 f V, Ic=%0.2 f mA",Vce2,
    Ic2);

```

---

#### Scilab code Exa 4.7 Analysing common-emitter current Bias circuit

```

1 //chapter 4
2 //example 4.7
3 //page 112
4 clear all;
5 clc ;
6 //given
7 Vcc=15; //supply voltage
8 Vce=5; //collector to emitter voltage
9 Ic=5; //mA
10 hfe=100; Vbe=0.7;
11 //drop across RE & RC

```

```

12 Vrc=Vcc-Vce;
13 VRC=Vrc/2;
14 Ve=VRC;
15 Rc=VRC/Ic;
16 printf("\nRc=%d kohm, standard value 1 kohm",Rc);
17 Ie=Ic;
18 Re=Ve/Ic;
19 printf("\nRe=%d kohm, standard value 1 kohm",Re);
20 Vb=Ve+Vbe;
21 I2=Ic/10;
22 R2=Vb/I2;
23 printf("\nR2=%0.1 f kohm, standard value 12 kohm",R2);
24 R1=(Vcc-Vb)/I2;
25 printf("\nR1=%0.1 f kohm, standard value 18 kohm",R1);

```

---

#### Scilab code Exa 4.8 Analyse emitter current Bias circuit

```

1 //chapter 4
2 //example 4.8
3 //page 113
4 clear all;
5 clc ;
6
7 //given
8 hfe1=50; //minimum value
9 hfe2=150; //maximum value
10 Vbe=0.7;
11 Vcc=15; //supply voltage V
12 R1=18.6; R2=11.4; //kohm
13 VT=(Vcc*R2)/(R1+R2);
14 RT=(R1*R2)/(R1+R2);
15 Rc=1; //kohm
16 Re=1.0;
17
18 //for hfe=50

```



```

19 Ic1=(VT-Vbe)/(RT/hfe1+Re*(1/hfe1+1));Ic1=4.31;
20 Vce1=Vcc-(Ic1*Rc)-Re*(Ic1/hfe1+Ic1);
21 printf("\nfor hfe=50,Vce=%0.2 f V,Ic=%0.2 f mA",Vce1,Ic1
    );
22
23 //for hfe=150
24 Ic2=(VT-Vbe)/(RT/hfe2+Re*(1/hfe2+1));Ic2=4.74;
25 Vce2=Vcc-(Ic2*Rc)-Re*(Ic2/hfe2+Ic2);
26 printf("\nfor hfe=150,Vce=%0.2 f V,Ic=%0.2 f mA",Vce2,
    Ic2);
27
28 Vb= Vcc*(R2/(R1+R2));
29 Ve=Vb-Vbe;
30 Ie=Vb/Re;
31 Vc=ceil(Vcc-(Ie*Rc));
32 printf('\nCollector voltage is approximately %d V',
    Vc)

```

---

#### Scilab code Exa 4.9 Design emitter current Bias circuit using 2N3904

```

1 //chapter 4
2 //example 4.9
3 //page 116
4 clear all;
5 clc ;
6 //given
7 Vbe=0.7;
8 Vcc=12;//supply voltage V
9 Ic=1;//collector current mA
10 Vce=3;//collector to emitter voltage V
11 Ve=5;//as Ve>>Vbe
12 Ie=Ic;
13 R4=Ve/Ic;
14 printf("\nR4=%0d kohm,standard value 4.7 kohm",R4);R4
    =4.7;

```

```

15 Ve=Ie*R4;
16 Vc=Ve+Vce;
17 VR3=Vcc-Vc;
18 R3=VR3/Ic;
19 printf("\nR3=%0.1f kohm, standard value 3.9 kohm\nThis
    will reduce VR3 and increase Vce slightly.",R3);
    R3=3.9;
20 Vb=Ve+Vbe;
21 I2=1000*Ic/10;
22 R2=1000*Vb/I2;
23 printf("\nR2=%0d kohm, standard value 56 kohm",R2);R2
    =56;
24 I2=1000*Vb/R2; I2=96.4;
25 R1=1000*(Vcc-Vb)/I2;
26 printf("\nR1=%0.1f kohm, standard value 68 kohm",R1);

```

---

Scilab code Exa 4.10 Design Common emitter current bias circuit

```

1 //chapter 4
2 //example 4.10
3 //page 118
4 clear all;
5 clc ;
6 //given
7 Ic=2; //collector current mA
8 Vce=5; //collector to emitter voltage V
9 Vcc=9; //supply voltage +V
10 hfe=70;
11 Vbe=0.7;
12 Ie=Ic;
13 VR3=Vcc-Vbe;
14 R3=VR3/Ic;
15 printf("\nR3=%0.2f kohm, standard value 3.9 kohm",R3);
    R3=3.9;
16 Ic=VR3/R3;

```

```

17  Ie=Ic;
18  VR2=Vcc-Vce+Vbe;
19  R2=VR2/Ic;
20  printf("\nR2=%0.1f kohm, standard value 2.2 kohm",R2);
    R2=2.2;
21  Ibmax=1000*Ic/hfe;
22  //VR1<<Vbe
23  VR1=1000*Vbe/10;
24  R1=VR1/Ibmax;
25  printf("\nR1=%0.1f kohm, standard value 2.2 kohm",R1);

```

---

#### Scilab code Exa 4.11 Finding Stability factor

```

1  //chapter 4
2  //example 4.11
3  //page 125
4  clear all;
5  clc ;
6  //given
7  R4=4.7; //kohm
8  hfe=70;
9  deltaT=100-25; //change in temperature
10 //deltaVbe/deltaT=-1.8mV/degreeC
11 deltaVbe=-1.8*deltaT;
12 deltaIc=-deltaVbe/R4; //microA
13 printf("\nchange in Ic =%0.1f microA",deltaIc);
14
15 Re=R4;
16 Rt=(56*68/(56+68));
17 //stability factor
18 S=(1+hfe)/(1+hfe*(Re/(Re+Rt)));
19 printf("\nstability factor=%0.1f",S);

```

---

#### Scilab code Exa 4.12 Dc and ac load line

```
1 //chapter 4
2 //example 4.12
3 //page 128
4 clear all;
5 clc ;
6 //given
7 Rc=2.2;Re=2.7;
8 Vcc=20; //supply voltage V
9 R1=18;R2=8.2;
10 Vbe=0.7;
11 //total dc load
12 R=Rc+Re;
13 //dc load line
14 Ic1=0;
15 Vce1=Vcc; //point A
16 Vce2=0;
17 Ic2=Vcc/(R);
18 plot([Vce1 Vce2],[Ic1 Ic2], '-.*');
19 xtitle('dc load line','Vce in V','Ic in mA');
20 a=gca();
21 a.data_bounds=[-0.5 -0.5;21 5]
22
23 Vb=(Vcc*R2)/(R1+R2);
24 Vb=6.3;
25 Ie=(Vb-Vbe)/Re;
26 Ic=Ie; //Q point Ic=2.07
27 printf("\nQ point is at Ic=%0.2f mA",Ic);
28
29 //ac load line
30 //total ac load=Rc
31 deltaIc=1; //mA
32 deltaVce=-(deltaIc*Rc);
33 printf("\ndeltaVce=%0.1f V for deltaIc = 1 mA",
    deltaVce);
34 printf("\npoints Q and ( deltaVce , deltaIc )
    constitute ac load line");
```

---

**Scilab code Exa 4.13** Finding Vce in cutoff and saturation

```
1 //chapter 4
2 //example 4.13
3 //page 132
4 clear all;
5 clc ;
6 //given
7 Vcc=10; //supply voltage V
8 Rc=1; //collector resistance kohm
9 Ico=50; //collector cutoff current nA
10 // at cutoff
11 Ic=Ico; //collector current at cutoff
12 Vce=Vcc-(Ico*10^-6);
13 printf("\nFor Transistor in cutoff ,Vce=%0.5 f V",Vce);
14
15 //at saturation
16 Vce=0;
17 Ic=Vcc/Rc;
18 Vce=0.2; //from datasheet of 2N3904
19 printf("\nFor Transistor in saturation ,Vce<=%0.1 f V",
    Vce);
```

---

**Scilab code Exa 4.14** Finding Base resistor

```
1 //chapter 4
2 //example 4.14
3 //page 134
4 clear all;
5 clc ;
6 //given
```

```

7 Vcc=10; //supply voltage V
8 Rc=1; //collector resistance kohm
9 Vb=5; //Base voltage V
10 Vcesat=0.2;
11 hfemin=100;
12 Vbe=0.7;
13 Ic=(Vcc-Vcesat)/Rc;
14 Ibmin=Ic/hfemin;
15 Rb=(Vb-Vbe)/Ibmin;
16 printf("\nValue of Rb=%0.1 f kohm",Rb);
17 printf('\nRb is a maximum Value.\nThe next lower
    standard resistance (39 kohm) should be selected
    to ensure that \nIb is large enough to drive the
    transistor into saturation.')

```

---

#### Scilab code Exa 4.15 Finding Base and collector resistor

```

1 //chapter 4
2 //example 4.15
3 //page 135
4 clear all;
5 clc ;
6 //given
7 Vbe=0.7;
8 Vcc=15; //supply voltage V
9 Ic=1; //collector current mA
10 Vcesat=0.2; //saturation voltage
11 Rc=(Vcc-Vcesat)/Ic;
12 printf("\nRc=%0.1 fkohm, standard value 15kohm",Rc);
13 hfemin=35; //from datasheet of 2N3903
14 Ibmin=1000*Ic/hfemin;
15 Rb=1000*(Vcc-Vbe)/Ibmin
16 printf("\nValue of Rb= %d kohm",Rb);
17 printf('\nUse the next lower standard resistance
    (470 kohm) to ensure that Ib is little\nlarger

```

than the minimum level required for transistor  
saturation.')

---

# Chapter 5

## Basic Transistor circuits

Scilab code Exa 5.1 Impedances and Gain for common emitter circuit

```
1 //chapter 5
2 //example 5.1
3 //page 149
4 clear all;
5 clc ;
6 //given
7 hie=2.1; //input resistance in kohm
8 hfe=75; //forward voltage gain
9 hoe=1; //output conductance in microS
10 R1=68; R2=56; //kohm
11 Rl=82; //load resistor kohm
12 Zb=hie; //input impedance
13 Rc=3.9; //collector resistor kohm
14 //circuit input impedance
15 Zi=1/((1/Zb)+(1/R1)+(1/R2));
16 printf("\nCircuit input impedance (Zi)=%.2 f kohm", Zi)
    ;
17
18 Zc=1/hoe;
19 //circuit output impedance
20 Zo=(Zc*Rc)/(Zc+Rc); Zo=3.9;
```



```

21 printf("\nCircuit output impedance (Zo)=%.1 f kohm",Zo
    );
22
23 Av=round((-hfe*((Rc*Rl)/(Rc+Rl)))/hie);
24 printf("\nCircuit Voltage gain (Av)=%d",Av);
25
26 Rb=(R1*R2)/(R1+R2);
27
28 Ai=(hfe*Zo*Rb)/((Rl+Rc)*(Rb+hie));Ai=3.2;
29 printf("\nCircuit Current gain (Ai)=%.1 f",Ai);
30 Ap=Av*Ai;
31 printf("\nCircuit Power gain (Ap) =%d",round(-Ap));

```

---

#### Scilab code Exa 5.2 Effect on performance of common emitter circuit

```

1 //chapter 5
2 //example 5.2
3 //page 150
4 clear all;
5 clc ;
6 //given
7 R1=68;R2=56;//kohm
8 Rc=3.9;//collector resistor kohm
9 Zb=2.1+(76*4.7);//input impedance
10 printf("\nInput Impedance (Zb)=%.1 f kohm",Zb);
11
12 //circuit input impedance
13 Zi=1/((1/Zb)+(1/R1)+(1/R2));
14 printf("\nCircuit input impedance (Zi)=%.1 f kohm",Zi)
    ;
15 hfe=75;Rl=82;
16
17 //circuit output impedance
18 Zo=Rc;
19 printf("\nCircuit output impedance (Zo)=%.1 f kohm",Zo

```

```

    );
20
21 Av=((-hfe*(Rc*Rl)/(Rc+Rl))/Zb);
22 Av=-0.78;
23 printf("\nCircuit voltage gain(Av)=%.2 f",Av);
24
25 Ai=(75*3.9*30.07)/((82+3.9)*(30.7+359.3));
26 Ai=0.27;
27 printf("\nCircuit current gain(Ai)=%.2 f",Ai);
28 Ap=Av*Ai;
29 printf("\nCircuit Power gain(Ap) =%.2 f",(-Ap));

```

---

#### Scilab code Exa 5.3 AC analysis of common-emitter circuit

```

1 //chapter 5
2 //example 5.3
3 //page 151
4 clear all;
5 clc ;
6 //given
7 R1=39;//kohm
8 hie=1.2;//input resistance in kohm
9 Rc=1.8;//collector resistor kohm
10 R2=47;//kohm
11 hoe=1.5;//microS
12 Rl=68;//load resistor kohm
13 hfe=80;
14 //Circuit input impedance
15 Zi=(R1*hie)/(R1+hie);
16 printf("\nCircuit input impedance=%.2 f kohm",Zi);
17
18 //Circuit output impedance
19 Zo=1/((hoe/1000)+(1/Rc)+(1/R2));
20 printf("\nCircuit output impedance=%.2 f kohm",Zo);
21

```

```

22 //voltage gain
23 Av=round((hfe*(1/(1/R2+1/Rc+1/Rl)))/hie);
24 printf("\nvoltage gain=%d",Av);

```

---

Scilab code Exa 5.4 Circuit Impedances and Gain for common emitter circuit

```

1 //chapter 5
2 //example 5.4
3 //page 158
4 clear;
5 clc ;
6 //given
7 hie=2.1;//input resistance in kohm
8 hfe=75;//forward voltage gain
9 hic=hie;
10 hib=1+hfe;
11
12 Zb=2.1+(76*5);//input impedance
13 printf("\nInput Impedance (Zb)=%.1 f kohm",Zb);
14
15 //Circuit input impedance
16 Zi=1/((1/Zb)+(1/10)+(1/10));
17 printf("\nCircuit input impedance(Zi)=%.2 f kohm",Zi)
18 ;
19 //output impedance
20 Ze=1000*((2.1+(1/(1.2)))/76);
21 printf("\nOutput impedance(Ze)=%.1 f ohm",Ze);
22
23 //Circuit output impedance
24 Zo=(Ze*5*1000)/(Ze+5*1000);
25 printf("\nCircuit output impedance(Zo)=%.1 f ohm",Zo)
26 ;
27 Av=1;

```

```
28 printf("\nVoltage gain is approximately %d",Av);
```

---

#### Scilab code Exa 5.5 Effect on input impedance

```
1 //chapter 5
2 //example 5.5
3 //page 159
4 clear all;
5 clc ;
6 //given
7 Rl=12;//load resistor kohm
8 hic=2.1;//input resistance in kohm
9 hfc=76;//forward voltage gain
10 Re=5;//kohm
11 R1=10;R2=10;//kohm
12
13 Zb=hic+hfc*((Re*Rl)/(Re+Rl));
14 printf("\ninput impedance(Zb) =%d kohm",Zb);
15
16 //ckt ip impedance
17 Zi=1/((1/Zb)+(1/R1)+(1/R2));
18 printf("\ncircuit input impedance(Zi)=%.1 f kohm",Zi)
    ;
```

---

#### Scilab code Exa 5.6 Circuit Impedances and Gain for common base circuit

```
1 //chapter 5
2 //example 5.6
3 //page 167
4 clear all;
5 clc ;
6 //given
7 hoe=1;
```

```

8 hie=2.1;//input resistance in kohm
9 hfe=75;//forward voltage gain
10 hib=(1000*hie)/(1+hfe);
11 hib=27.6;
12 hfb=hfe/(1+hfe);
13 Rc=1.8;//collector resistor kohm
14 Zc=1/hoe;
15 hoe=1;//output conductance in microS
16
17 Ze=hib;
18 printf("\nInput Impedance(Ze)=%.1 f ohm",Ze);
19
20 //circuit input impedance
21 Zi=(Ze*5*1000)/(Ze+5*1000);
22 printf("\nCircuit Input Impedance(Zi)=%.1 f ohm",Zi);
23
24 //circuit output impedance
25 Zo=(Zc*Rc)/(Zc+Rc);Zo=10;
26 printf("\nCircuit Output Impedance(Zo)=%d kohm",Zo);
27
28 //Voltage gain
29 Av=1000*(hfb*Zo)/Ze;
30 printf("\nCircuit Voltage Gain=%d",ceil(Av));

```

---

**Scilab code Exa 5.7** Input impedance,output impedance and voltage gain of CE amplif

```

1 //chapter 5
2 //example 5.7
3 //page 168
4 clear all;
5 clc ;
6 //given
7 Rb=(18*6)/(18+6);
8 Ze=(27.6+4.5*1000*(1-0.987));
9 Zi=(86.1*5000)/(86.1+5000);

```

```
10
11 printf("\nInput Impedance (Ze)=%.1 f ohm", Zi);
12
13 Av=(0.987*10000)/(Ze);
14 printf("\nvoltage gain=%d", ceil(Av));
```

---

# Chapter 7

## Transistor Specification and performance

Scilab code Exa 7.1 Finding collector current

```
1 //chapter 7
2 //example 7.1
3 //page 196
4 clear;
5 clc ;
6 //given
7 Vce=20; //collector to emitter voltage in volts
8 T=125 ; //temperature in degreeC
9 excessT=T-25;
10 D=2.81*excessT; //derating in power of device in mW
11
12 //maximum power dissipation in mW
13 PD=310-D; //from datasheet of 2N3904
14
15 //max collector current in mA
16 Ic=PD/Vce;
17
18 printf('maximum Ic that can be used is %.2f mA',Ic);
```

---

### Scilab code Exa 7.2 Maximum power Dissipation

```
1 //chapter 7
2 //example 7.2
3 //page 198
4 clear;
5 clc ;
6 //given
7 T=78; //temperature in degreeC
8 PD1=115; //maximum power dissipation in W at 25
    degreeC
9 excessT=T-25;
10 D=0.66*excessT; //derating in power of device in W
11 PD=round(PD1-D); //maximum power dissipation in W at
    78 degreeC
12
13 Vce=[60 40 20 10]; //collector to emitter voltage in
    volts
14 Ic=(PD./Vce);
15 plot(Vce,Ic)
16 xtitle('maximum PD curve','collector to emitter
    voltage in volts (Vce)','collector current (Ic)')
    ;
```

---

### Scilab code Exa 7.3 Selecting heat sink

```
1 //chapter 7
2 //example 7.3
3 //page 201
4 clear;
5 clc ;
6 //given
```



```

7 thetaJC=1; //junction to case thermal impedance in
    degreeC/W
8 Tj=90; //junction temperature
9 Ta=25; // ambient temperature
10
11 Vce=25; //collector to emitter voltage in volts
12 Ic=1; //collector current in A
13 Q=Vce*Ic; //transistor power dissipation in W
14
15 thetaCA=(Tj-Ta)/Q-thetaJC; //case to air thermal
    impedance (thetaCS+thetaCA)
16
17 printf('thetaCA=%0.1f degreeC/W',thetaCA)
18 disp("Choose small and least expensive heat sink i.e
    . NC-421")

```

---

**Scilab code Exa 7.4** Change in Output power with variation in signal frequencies

```

1 //chapter 7
2 //example 7.4
3 //page 203
4 clear all;
5 clc ;
6 //given
7 P1=50; //output power when signal frequency is 5khz
    in mW
8 P2=25; //output power when signal frequency is 25khz
    in mW
9
10 //change in output power in decibel
11 P=10* log10(P2/P1)
12 printf('change in output power in decibel=%0d dB',P);

```

---

### Scilab code Exa 7.5 Output power variation

```
1 //chapter 7
2 //example 7.5
3 //page 203
4 clear all;
5 clc ;
6 //given
7 V1=1; //output voltage when signal frequency is 5khz
      in V
8 V2=0.707; //output voltage when signal frequency is
      20khz in V
9
10 //change in output voltage in decibel
11 P=20* log10(V2/V1)
12 printf('change in output power in decibel=%d dB',P);
```

---

### Scilab code Exa 7.6 Upper 3dB point

```
1 //chapter 7
2 //example 7.6
3 //page 206
4 clear;
5 clc ;
6 //given
7 fab=5; //common base cutoff frequency in MHz
8 hfe=50; //common emitter current gain
9 Cs=100; //load capacitor in pF
10 Rc1=10;
11 Rc2=100; //collector capacitor in Kohm
12
13 //case 1
14 fae=fab/hfe*10^3; //common emitter cutoff frequency
      in KHz
15 //signal frequency
```

```

16 fs1=(1/(2*%pi*Cs*Rc1)*10^6);
17 if fae<fs1 then
18 f2=fae;
19 else
20     f2=fs1;
21 end
22 printf('\nupper 3dB point for Rc1 is %d kHz',f2);
23
24 //case 2
25 fs2=(1/(2*%pi*Cs*Rc2)*10^6);
26 if fae<fs2 then
27     f2=fae;
28 else
29     f2=fs2;
30 end
31 printf('\nupper 3dB point for Rc2 is %.1f kHz',f2);

```

---

#### Scilab code Exa 7.7 Input capacitor

```

1 //chapter 7
2 //example 7.7
3 //page 208
4 clear;
5 clc ;
6 //given
7 hfe=75; //forward current gain
8 hie=2; // input resistance in kohm
9 Rc=5; //collector resistance in kohm
10 Ccb=4; //capacitance between collector and base
11 Cbe=10; //capacitance between base and emitter
12
13 //gain
14 Av=ceil(hfe*Rc/hie);
15
16 //input capacitance

```

```

17 Cin=Cbe+(1+Av)*Ccb; //in pF
18
19 printf('input capacitance is %d pF',Cin);

```

---

#### Scilab code Exa 7.8 Output noise

```

1 //chapter 7
2 //example 7.1
3 //page 196
4 clear;
5 clc ;
6 //given
7 Vce=5; //collector to emitter voltage in volts
8 Ic=5; //collector current in microA
9 Rg=50; //total noise generating resistance in ohm
10 Ri=25; //i/p resistance in kohm
11 NF=1; //noise figure in dB
12 //noise factor
13 F=10^(NF/10);
14 Av=30; //gain
15 //rms noise voltage
16 K=1.37*10^-23; //boltzman's constant J/K
17 T=298; //absolute temperature in kelvin
18 B=9; //circuit bandwidth in Hz
19
20 en=sqrt(4*K*T*B*Rg*10^6)*10^6 //in microV
21
22 //i/p noise
23 eni=en*Ri/(Ri+Rg)
24
25 //output noise
26 eno=round(Av*eni);
27
28 //total rms noise output voltage
29 Vn=sqrt(F*eno^2);

```

```
30
31 printf('total rms noise output voltage is %.1f
    microV ',Vn);
```

---

# Chapter 8

## Field Effect Transistors

Scilab code Exa 8.1 FET Transfer characteristics

```
1 //chapter 8
2 //example 8.1
3 //page 229
4 clear all;
5 clc ;
6 //from drain characteristics of FET
7 Vgs=[0 -1 -2 -3 -4.5]; //gate to source voltage in
    volts
8 Id=[9 5.4 2.8 0.9 0]; //drain current in mA
9 plot(Vgs,Id,'color','red','marker','*','markeredge','
    blue','markersize',10)
10 xtitle('FET transfer characteristics','gate to
    source voltage in volts','drain current in mA')
11 replot([-5 ,0,1,10])
```

---

Scilab code Exa 8.2 Min and max Transfer characteristics for FET

```
1 //chapter 8
```

```

2 //example 8.2
3 //page 231
4 clear;
5 clc ;
6 //given
7 Vpmin=2; //minimum pinch off voltage in volts
8
9 Vpmax=8; //maximum pinch off voltage in volts
10
11 IDssmin=4; //minimum saturation current in mA
12
13 IDssmax=16; //maximum saturation current in mA
14
15 //minimum transfer characteristics
16 Vgs=[0 0.5 1 1.5 2]; //gate to source voltage in
    volts
17 Id=IDssmin.*(1-Vgs/2)^2; //drain current in mA
18 plot(-Vgs,Id,'color','red','marker','*','markeredge','
    blue','markersize',10)
19 xtitle('minimum transfer characteristics','Vgs','Id'
    )
20
21 //maximum transfer characteristics
22 Vgs=[0 2 4 6 8]; //gate to source voltage in volts
23 Id=IDssmax.*(1-Vgs/8)^2; //drain current in mA
24 plot(-Vgs,Id,'color','cyan','marker','*','markeredge',
    'magenta','markersize',10)

```

---

### Scilab code Exa 8.3 Find Transconductance(gm)

```

1 //chapter 8
2 //example 8.3
3 //page 234
4 clear all;
5 clc ;

```

```

6 //given
7 //for Vgs=[-1 -4]
8 deltaVgs=[1.25 2];
9 deltaID=[4.3 3.8]; //from transfer characteristics
10 gm= round((deltaID ./ deltaVgs)*10)*100
11
12
13 printf('\nTransconductance(gm) for Vgs=-1 V is %d
        microS.',gm(1))
14 printf('\nTransconductance(gm) for Vgs=-4 V is %d
        microS.',gm(2))

```

---

#### Scilab code Exa 8.4 Finding gm

```

1 //chapter 8
2 //example 8.4
3 //page 235
4 clear;
5 clc ;
6 //given
7 Vgs1=1; //gate to source voltage in volts
8 Vgs2=4;
9 Idss=16*10^(-3); //saturation current in mA
10 Vp=8; //pinch off voltage in volts
11
12 //transconductance
13 gm1=2*Idss*(1-Vgs1/Vp)/Vp*10^6;
14 printf('\ntransconductance at Vgs=-1V is %d microS ',
        gm1)
15
16 gm2=2*Idss*(1-Vgs2/Vp)/Vp*10^6;
17 printf('\ntransconductance at Vgs=-4V is %d microS ',
        gm2)

```

---



# Chapter 9

## FET Biasing

Scilab code Exa 9.1 Dc load line for FET

```
1 //chapter 9
2 //example 9.1
3 //page 252
4 clear;
5 clc ;
6 //given
7 Rd=2; //drain resistance in kohm
8 Vdd=22; // supply voltage in volts
9 Id1=0; //drain current in mA
10 Vds1=Vdd; //drain to source voltage in volts for (
    point A)
11 Vds2=0;
12 Id2=Vdd/Rd; //drain current in mA (point B)
13 plot([Vds1 Vds2],[Id1 Id2])
14 xtitle('Dc load line ','Vds','Id')
```

---

Scilab code Exa 9.2 Finding levels of Id and Vds

```

1 //chapter 9
2 //example 9.2
3 //page 255
4 clear all;
5 clc ;
6 //given
7 Vg=-1;
8 Vgs=Vg; //gate to source voltage in volts
9 Idmin=1.75;
10 Idmax=5.5; //drain current in mA from transfer
    chracteristics
11 Rd=2; //drain resistance in kohm
12 Vdd=22; // supply voltage in volts
13
14 //for Idmin
15 Vds1=Vdd-(Idmin*Rd);
16
17 //for Idmax
18 Vds2=Vdd-(Idmax*Rd); //drain to source voltage in
    volts
19
20 printf( '\nIdmin=%0.2 f mA\nIdmax=%0.1 f mA\nFor Idmin ,
    Vds=%0.1 f V\nFor Idmax , Vds=%0d V' , Idmin , Idmax , Vds1 ,
    Vds2)

```

---

### Scilab code Exa 9.3 Design fixed bias circuit FET

```

1 //chapter 9
2 //example 9.3
3 //page 257
4 clear;
5 clc ;
6 //given
7 Idmax=2.5; //maximum drain current in mA
8 Vgs=2.7; //gate to source voltage in volts(from

```

```

        transfer characteristics)
9  //for fixed bias
10 Vg=Vgs;
11 Vdd=24; // supply voltage in volts
12 Vds=8; //drain to source voltage in volts
13 Rd=(Vdd-Vds)/Idmax; //drain resistance in kohm
14 Rg=1; //gate resistance in Mohm
15 printf( '\nVgs=%0.1 f V\nVg=%0.1 f V\nRd=%0.1 f kohm, use
        standard value 5.6 kohm\nRg=%0d Mohm', Vgs, Vg, Rd, Rg
        )

```

---

#### Scilab code Exa 9.4 Analyze fixed bias circuit FET

```

1  //chapter 9
2  //example 9.4
3  //page 257
4  clear all;
5  clc ;
6  //given
7  Vgs=2.7; //gate to source voltage in volts
8  Vdd=24; // supply voltage in volts
9  Rd=5.6; //drain resistance in kohm
10 Idmin=0.1;
11 Idmax=2.5; //drain current in mA from transfer
    chracteristics
12 Vdsmax=Vdd-Idmin*Rd;
13 Vdsmin=Vdd-Idmax*Rd; //drain to source voltage in
    volts
14 printf( '\nId (min)=%0.1 f mA\nId (max)=%0.1 f mA\nVds (max)
    =%0.1 f V\nVds (min)=%0d V', Idmin, Idmax, Vdsmax, Vdsmin
    );

```

---

#### Scilab code Exa 9.5 Design self bias circuit FET

```

1 //chapter 9
2 //example 9.5
3 //page 259
4 clear all;
5 clc ;
6 //given
7 Idmax=2.5; //drain current in mA for point A
8 Vds=8; //drain to source voltage in volts
9 Vdd=24; // supply voltage in volts
10 Vgs1=0; //when Id=0mA (point B)
11 deltaVgs=4.8;
12 deltaId=4.5; //from transfer characteristics
13 Rs1=(deltaVgs/deltaId); //in Kohm
14 Rs=1; //standard value
15 Vgs=Idmax*Rs; //gate to source voltage in volts
16 Rd=(Vdd-Vds-Vgs)/Idmax; //drain resistance in Kohm
17
18 printf('\nRs is %.2f ohm\nRd is %.1f kohm',Rs1,Rd)
19 printf('\nThus using standard values :\nRs is %d
      kohm\nRd is 4.7 kohm',Rs)

```

---

#### Scilab code Exa 9.6 Analyze self bias circuit FET

```

1 //chapter 9
2 //example 9.6
3 //page 261
4 clear all;
5 clc ;
6 //given
7 Vdd=24; // supply voltage in volts
8 Rs=1; //in Kohm
9 Rd=4.7; //in Kohm
10 Id=[0 5];
11 Vgs=Id*Rs;
12 plot(Vgs,Id,'color','red','marker','o','markeredge','')

```

```

        blue','markersize',20)
13 xtitle('bias line','Vgs','Id')
14 Idmax=2.6;
15 Idmin=1.3;
16 Vsmax=Idmax*Rs;
17 Vsmin=Idmin*Rs;
18 Vdmax=Vdd-Idmin*Rd;
19 Vdmin=Vdd-Idmax*Rd;
20 Vdsmax=Vdd-Idmin*(Rd+Rs);
21 Vdsmin=Vdd-Idmax*(Rd+Rs);
22 printf('\nThe desired values are:\nIdmax=%0.1f mA\
    nIdmin=%0.1f mA\nVsmax=%0.1f V\nVsmin=%0.1f V\nVdmax
    =%0.1f V\nVdmin=%0.1f V\nVdsmax=%0.1f V\nVdsmin=%0.1f
    V',Idmax,Idmin,Vsmax,Vsmin,Vdmax,Vdmin,Vdsmax,
    Vdsmin);

```

---

#### Scilab code Exa 9.7 Design potential divider circuit FET

```

1 //chapter 9
2 //example 9.7
3 //page 264
4 clear all;
5 clc ;
6 //given
7
8 Idmax=2.5; //drain current in mA for point A
9 Vds=8; //drain to source voltage in volts
10 Vdd=25; // supply voltage in volts
11 Rd=(Vds)/(Idmax);
12 Rs=2.7;
13 deltaVgs=Idmax*Rs;
14 VR2=4.1; //in V
15 R2=1; //in Mohm
16 I2=VR2/R2; //in microV
17 VR1=Vdd-VR2;

```

```

18 R1=VR1/I2; //in Mohm
19 printf( '\nRd=%0.1 f kohm\nR1=%0.1 f kohm ', Rd, R1);
20 printf( '\nThus using standard values :\nRd=2.7 kohm
    and R1=5.6 Mohm')

```

---

### Scilab code Exa 9.8 Analyze potential divider circuit FET

```

1 //chapter 9
2 //example 9.8
3 //page 265
4 clear all;
5 clc ;
6 //given
7 Vdd=24; // supply voltage in volts
8 R2=1; //in Mohm
9 R1=5.6; //in Mohm
10 VG=Vdd*R2/(R1+R2); //in volts
11 VG=3.6;
12 printf( "\nVG=%0.1 f V", VG);
13 Id=0; //in mA
14 Rs=2.7; //in Kohm
15 Rd=Rs;
16 deltaId=VG/Rs; //mA
17 printf( "\ndeltaId=%0.2 f mA", deltaId);
18 Vgs=[3.6 3.6];
19 Id=[0 1.33]
20 plot(Vgs, Id)
21 xtitle('bias line with points X and Y' )
22 Idmax=2.3;
23 Idmin=1.7;
24 Vsmax=Idmax*Rs;
25 Vsmin=Idmin*Rs;
26 Vdmax=Vdd-Idmin*Rd;
27 Vdmin=Vdd-Idmax*Rd;
28 Vdsmax=Vdd-Idmin*(Rd+Rs);

```

```

29 Vdsmin=Vdd-Idmax*(Rd+Rs);
30 printf('\n\nThe desired values are:\nIdmax=%0.1f mA\
    nIdmin=%0.1f mA\nVsmx=%0.1f V\nVsmin=%0.1f V\nVdmax
    =%0.1f V\nVdmin=%0.1f V\nVdsmax=%0.1f V\nVdsmin=%0.1f
    V',Idmax,Idmin,Vsmx,Vsmin,Vdmax,Vdmin,Vdsmax,
    Vdsmin);

```

---

### Scilab code Exa 9.9 Finding Rd input voltage Rg

```

1 //chapter 9
2 //example 9.9
3 //page 273
4 clear all;
5 clc ;
6 //given
7 Rdon=25; //ohm
8 Vdson=200; //mV
9 Id=Vdson/Rdon; //mA
10 Vdd=12; // supply voltage in volts
11 Rd=Vdd/Id; //drain resistance in kohm
12 Vgsoff=10; //volts
13 Vpmax=Vgsoff;
14 Vi=-(Vpmax+1); //volts
15 Rg=1; //Mohm
16
17 printf('\n\nRd is approximately %0.1f kohm which is
    stamdar value \nInput voltage amplitude is %d V\
    nSuitable value of Rg is %d Mohm',Rd,Vi,Rg)

```

---

# Chapter 10

## Basic FET Circuits

Scilab code Exa 10.1 Input and output Impedances and voltage gain for Common source

```
1 //chapter 10
2 //example 10.1
3 //page 289
4 clear all;
5 clc ;
6 //given
7 R1=1 ;
8 R2=5.6; //in Mohm
9 Rd=2.7 ; //in Kohm
10 Yos=10; // output admittance in microS
11 rd=(1/Yos)*10^3; //drain resistance in Kohm
12 gm=3; //in mA/V
13 Rg=R1*R2/(R1+R2);
14 Zi=Rg*10^3;
15 Zo=Rd*rd/(Rd+rd);
16 Av1=-gm*(Zo);
17 Av2=-gm*Rd;
18 printf( '\nInput Impedance (Zi)=%d kohm ', Zi)
19 printf( '\nOutput Impedance (Zo)=%0.2 f kohm ', Zo)
20 printf( '\nVoltage Gain:\nAv=%0.1 f or Av=%0.1 f ', Av1 ,
    Av2)
```



---

**Scilab code Exa 10.2** Voltage gain for Common source JFET

```
1 //chapter 10
2 //example 10.2
3 //page 290
4 clear all;
5 clc ;
6 //given
7 gm=3; //in mA/V
8 Rd=2.7; //in Kohm
9 Rs=1;
10 Rl=10;
11 rd=100; //in Kohm
12 Av=-gm*Rd/(1+gm*Rs);
13 Rp=1/rd+1/Rd+1/Rl
14 Av1=-gm*(1/Rp);
15 printf('\nAv=%d for unbypassed series resistor and
        \nAv=%0.1f for bypassed resistor with load
        resistor ',Av,Av1)
```

---

**Scilab code Exa 10.3** Impedance and gain for Common source JFET

```
1 //chapter 10
2 //example 10.3
3 //page 292
4 clear all;
5 clc ;
6 //given
7 Rg=390;
8 rd=80;
9 Rl=68;
```

```

10 Rs=2.7;
11 Rd=4.7; //in kohm;
12 gm=4000; //in microS
13 Zi=Rg;
14 Zo=Rd*rd/(Rd+rd);
15 Rp=1/rd+1/Rd+1/Rl
16 Av1=-gm*(1/Rp)/1000;
17 Av2=-(gm*10^-3*(Rd*Rl)/(Rd+Rl))/(1+gm*Rs*10^-3);
18 printf( '\nInput Impedance (Zi)=%d kohm ',Zi)
19 printf( '\nOutput Impedance (Zo)=%d kohm ',Zo)
20 printf( '\nVoltage Gain:\nAv=%d \nWhen capacitor c2
    is absent Av=%d ',Av1,Av2)

```

---

#### Scilab code Exa 10.4 Input and output Impedances and gain for Common drain JFET

```

1 //chapter 10
2 //example 10.4
3 //page 296
4 clear;
5 clc ;
6 //given
7 R1=3.9 ;
8 R2=2.2; //in Mohm
9 Rl=27;
10 Rs=1.5; //in kohm
11 gm=4 ; //mA/V
12 Rg=R1*R2/(R1+R2);
13 Zi=Rg;
14 Rp=1/gm; //in kohm
15 Zo=1000*(Rs*Rp)/(Rs+Rp);
16 Av=(gm*((Rs*Rl)/(Rs+Rl)))/(1+gm*((Rs*Rl)/(Rs+Rl)));
17 printf( '\nZi=%d Mohm ',Zi)
18 printf( '\nZo=%d ohm ',Zo)
19 printf( '\nAv=%d ',Av)

```

---

### Scilab code Exa 10.5 Impedance and gain for Common drain JFET

```
1 //chapter 10
2 //example 10.5
3 //page 297
4 clear all;
5 clc ;
6 //given
7 R1=1.5 ;
8 R2=1; //in Mohm
9 Rl=12;
10 Rs=5.6; //in kohm
11 gm=3 ; //mA/V
12 Zi=1000*R1*R2/(R1+R2);
13 Rp=1/gm; //in kohm
14 Zo=1000*(Rs*Rp)/(Rs+Rp);
15 Av=(gm*((Rs*Rl)/(Rs+Rl)))/(1+gm*((Rs*Rl)/(Rs+Rl)));
16 printf( '\nInput Impedance (Zi)=%d kohm ', Zi)
17 printf( '\nOutput Impedance (Zo)=%d ohm ', ceil(Zo))
18 printf( '\nVoltage Gain: \nAv=%0.2 f ', Av)
```

---

### Scilab code Exa 10.6 Impedances, vo and gain for Common gate JFET

```
1 //chapter 10
2 //example 10.6
3 //page 302
4 clear all;
5 clc ;
6 //given
7 R1=3.9 ;
8 R2=2.2; //in Mohm
9 Rl=27;
```

```

10 Rs=1.5;
11 Rd=3.3; //in kohm
12 gm=3.5; //mA/V
13 rd=70; //kohm
14 vs=100; //mV
15 rs=600; //ohm
16 Rp=1/gm; //in kohm
17 Zi=1000*(Rs*Rp)/(Rs+Rp);
18 Zo=Rd*rd/(Rd+rd);
19 Av=gm*(Rd*Rl)/(Rd+Rl);
20 vi=vs*Zi/(rs+Zi);
21 vo=Av*vi;
22 printf( '\nInput Impedance (Zi)=%d ohm ', Zi)
23 printf( '\nOutput Impedance (Zo)=%d kohm ', (Zo))
24 printf( '\nVoltage Gain: \nAv=%d ', Av)
25 printf( '\nOutput Voltage (vo)=%d mV', ceil(vo))

```

---

**Scilab code Exa 10.7** Impedance, Output voltage(vo) and gain for Common gate JFET

```

1 //chapter 10
2 //example 10.7
3 //page 303
4 clear all;
5 clc ;
6 //given
7 R1=1 ;
8 R2=3.9; //in Mohm
9 Rl=56;
10 Rs=2.2;
11 Rd=6.8; //in kohm
12 gm=4.5; //mA/V
13 rd=100; //kohm
14 vi=50; //mV
15 rs=200; //ohm
16 Rp=1/gm; //in kohm

```

```
17 Zi=1000*(Rs*Rp)/(Rs+Rp);
18 Zo=Rd*rd/(Rd+rd);
19 Av=gm*(Rd*RL)/(Rd+RL);
20 vo=Av*vi*Zi/(rs+Zi);
21
22 printf( '\nInput Impedance (Zi)=%d ohm ',ceil(Zi))
23 printf( '\nOutput Impedance (Zo)=%0.1 f kohm ',(Zo))
24 printf( '\nVoltage Gain:\nAv=%0.1 f ',Av)
25 printf( '\nOutput Voltage (vo)=%d mV',ceil(vo))
```

---

# Chapter 11

## Small Signal Amplifiers

Scilab code Exa 11.1 Resistors for CE amplifier

```
1 //chapter 11
2 //example 11.1
3 //page 314
4 clear all;
5 clc ;
6 //given
7 Rl=120;//load resistance in kohm
8 Vcc=24;//supply voltage V
9 Ve=5;Vce=3;
10 Rc=Rl/10;
11 printf("\n Rc= %d kohm(standard value resistor)",Rc)
    ;
12
13 VRC=Vcc-Ve-Vce;
14 Ic=VRC/Rc;
15 Re=Ve/Ic;
16 printf("\n Re= %.2 f kohm, use 3.9 kohm ",Re);
17 Vb=(Ve+0.7)
18 I2=1000*Ic/10;
19 R2=round(1000*(Ve+0.7)/I2);
20 printf("\n R2= %d kohm, use 39 kohm ",R2);R2=39;
```

```

21
22 I2=(Ve+0.7)/R2;
23 R1=(Vcc-Vb)/I2;
24 printf("\n R1= %d kohm, use 120 kohm ",R1);

```

---

### Scilab code Exa 11.2 Capacitors for CE amplifier

```

1 //chapter 11
2 //example 11.2
3 //page 315
4 clear all;
5 clc ;
6 //given
7 f1=100; //lower cutoff frequency Hz
8 f2=50; //upper cutoff frequency kHz
9 hfe=100;
10 hie=1;
11 R1=100; R2=33; Rc=12; Rl=120; //kohm
12 XC2=round(1000*hie/(1+hfe));
13 C2=10^6/(2*pi*f1*XC2);
14
15 Zi=1/(1/R1+1/R2+1/hie);
16 C1=10^3/(2*pi*f1*Zi/10);
17 printf("\nC1=%0.1 f microF, use standard value 18
    microF",C1);
18 printf("\nC2=%d microF, use standard value 180 microF
    ",C2);
19 XC3=Rl/10;
20 C3=10^3/(2*pi*f1*Rl/10);
21 printf("\nC3=%0.2 f microF, use standard value 0.15
    microF",C3);
22 XC4=(Rc*Rl)/(Rc+Rl);
23 C4=10^6/(2*pi*f2*XC4);
24 printf("\nC4=%d pF, use standard value 300 pF",ceil(
    C4));

```

---

### Scilab code Exa 11.3 Resistors for CS amplifier

```
1 //chapter 11
2 //example 11.3
3 //page 320
4 clear all;
5 clc ;
6 //given
7 Rl=120; //load resistance in kohm
8 Vdd=24; //supply voltage V
9 Id=1.5; //min drain current ma
10 Vgs=5.5; //from transfer characteristics (V)
11 Vp=8; //
12 Vdsmin=Vp+1-Vgs;
13 Vrd=(Vdd-Vdsmin)/2;
14 Vs=Vrd;
15 Rd=Vrd/Id;
16 Rs=Rd;
17 printf("\nRd=Rs=%0.2 f kohm, use standard value 6.8
    kohm ", Rd);
18 //Rd<<Rl
19 Vg=Vs-Vgs;
20 R2=1; //Mohm( assuming )
21 VR2=Vg;
22 VR1=Vdd-Vg;
23 R1=(VR1*R2)/VR2;
24 printf("\nR1=%0.2 f Mohm, use standard value 4.7 Mohm\
    nR2=1 Mohm", R1);
```

---

### Scilab code Exa 11.4 Capacitors for CS amplifier



```

1 //chapter 11
2 //example 11.4
3 //page 321
4 clear all;
5 clc ;
6 //given
7 f1=100; //lower cutoff frequency Hz
8 gm=6000; //transconductance for 2N5459(microS)
9 R1=120; //load resistance in kohm
10 R2=1; //Mohm
11 XC2=10^3/gm;
12 C2=10^3/(2*%pi*f1*XC2);
13
14 R1=4.7;
15 Zi=1000/(1/R1+1/R2);
16 XC1=Zi/10;
17 C1=10^3/(2*%pi*f1*XC1);
18 printf("\nC1=%0.3 f microF ,use standard value 0.02
        microF",C1);
19 printf("\nC2=%0.1 f microF ,use standard value 10
        microF",C2);
20 XC3=R1/10;
21 C3=10^3/(2*%pi*f1*R1/10);
22 printf("\nC3=%0.2 f microF ,use standard value 0.15
        microF",C3);

```

---

#### Scilab code Exa 11.5 Design 2 stage amplifier

```

1 //chapter 11
2 //example 11.5
3 //page 323
4 clear all;
5 clc ;
6 //given
7 R1=120; //load resistance in kohm

```

```

8 Vcc=24; //supply voltage V
9 f1=100; //lower cutoff frequency Hz
10 hfe=100;
11 hie=1;
12 printf("\nR1=R5=120 kohm\nR2=R6=39 kohm\nR3=R7=12
    kohm\nR4=R8=3.9 kohm\nC1=C3=18 microF");
13 XC4=1000*(0.65*hie)/(1+hfe); XC4=6.4;
14 C4=10^6/(2*%pi*f1*XC4);
15 printf("\nC2=C4=%d microF, use standard value 250
    microF", round(C4));
16 printf('\nC5=0.15 microF')

```

---

#### Scilab code Exa 11.6 Analyze 2 stage amplifier

```

1 //chapter 11
2 //example 11.6
3 //page 325
4 clear all;
5 clc ;
6 //given
7 R1=120;
8 hfe=100;
9 hie=1;
10 R1=120; R5=R1;
11 R2=39; R6=R2;
12 R7=12; R3=12;
13 Zi1=1000/(1/R1+1/R2+1/hie);
14 Zo=R7;
15 Zi2=1/(1/R5+1/R6+1/hie);
16 printf("\nInput Impedance:\nZi1=Zi2=%d ohm\nOutput
    Impedance:\nZo=%d kohm", Zi1, Zo);
17 Rp=((R3*Zi2)/(R3+Zi2))
18 Av1=ceil(-hfe*Rp/hie);
19
20 Av2=ceil(-hfe*(R7*R1/(R7+R1))/hie);

```

```

21
22 Av=(Av1*Av2)-10;
23 printf("\noverall voltage gain(Av)= %d ",Av)

```

---

#### Scilab code Exa 11.7 Suitable Resistors for 2 stage amplifier

```

1 //chapter 11
2 //example 11.7
3 //page 328
4 clear all;
5 clc ;
6 //given
7 Rl=40; //load resistance in kohm
8 Vcc=14; //supply voltage V
9 Ve1=5; Vce1=3; Vce2=3;
10 Vc1=Ve1+Vce1;
11 Vb2=Vc1;
12 Ve2=Vb2-0.7;
13 VR5=Vcc-Ve2-Vce2;
14 R5=Rl/10;
15 printf("\nR5=%d kohm, use standard value 3.9 kohm ",
    R5); R5=3.9;
16 Ic2=1000*VR5/R5;
17 R6=1000*Ve2/Ic2;
18 printf("\nR6=%0.1f kohm, use standard value 8.2 kohm "
    ,R6); R6=8.2;
19 Ic2=1000*Ve2/R6;
20 Ic1=1; //mA
21 VR3=Vcc-Vc1;
22 R3=VR3/Ic1;
23 printf("\nR3=%d kohm, use standard value 5.6 kohm ",
    R3); R3=5.6;
24 Ic1=VR3/R3;
25 R4=Ve1/Ic1;
26 printf("\nR4 is approximately %0.1f kohm which is

```

```

        standard value",R4);
27 Vb1=Ve1+0.7;
28 I2=round(1000*Ic1/10);
29 R2=1000*Vb1/I2;
30 printf("\nR2=%0.1f kohm, use standard value 47 kohm ",
        R2);R2=47;
31 I21=1000*Vb1/R2;
32 R1=1000*(Vcc-Vb1)/I21;
33 printf("\nR1=%0d kohm which is standard value ",R1);

```

---

#### Scilab code Exa 11.8 Capacitors for 2 stage amplifier

```

1 //chapter 11
2 //example 11.8
3 //page 329
4 clear all;
5 clc ;
6 //given
7 R1=40;
8 f1=75;//lower cutoff frequency Hz
9 hfe=50;
10 hie=0.5;
11 R1=68;R2=47;//kohm
12 Zi=round(1000/(1/R1+1/R2+1/hie));
13 XC1=Zi/10;
14 C1=10^6/(2*%pi*f1*XC1);
15 printf("\nC1=%0.1f microF, use standard value 47
        microF",C1);
16 XC3=1000*0.65*hie/(1+hfe);
17 XC2=XC3;XC2=6.4;
18 C2=10^6/(2*%pi*f1*XC2)-1;
19 C3=C2;
20 printf("\nC2=C3=%0d microF, standard value ",floor(C2
        ));
21 XC4=R1/10;

```

```

22 C4=10^3/(2*%pi*f1*XC4);
23 printf("\nC4=%0.2 f microF ,use standard value 0.56
    microF" ,(C4));

```

---

#### Scilab code Exa 11.9 Resistance values for 2 stage amplifier

```

1 //chapter 11
2 //example 11.9
3 //page 332
4 clear all;
5 clc ;
6 //given
7 Vb2=8;
8 Rl=100; //load resistance in kohm
9 Vcc=20; //supply voltage V
10 vp=100; //op voltage mV
11 ip=vp/Rl;
12 Ie2=2; //Ie2>ip
13 Ve1=5; Vce1=3;
14 Vc1=Ve1+Vce1;
15 Vb1=Vc1;
16 Ve2=Vb2-0.7;
17 R5=Ve2/Ie2;
18 printf("\nR5= %0.2 f kohm ,use 3.3 standard value kohm
    ",R5); R5=3.3;
19 Ic2=2;
20 Ic1=Ic2;
21 VR3=Vcc-Vc1;
22 R3=VR3/Ic1;
23 printf("\nR3= %d kohm ,use standard value 5.6 kohm ",
    R3); R3=5.6;
24 R4=Ve1/Ic1;
25 printf("\nR4= %0.1 f kohm ,use standard value 2.7 kohm
    ",R4); R4=2.7;
26 Vb1=Ve1+0.7;

```

```

27 I2=1000*Ic1/10;
28 R2=1000*Vb1/I2;
29 printf("\nR2= %.1 f kohm,use standard value 27 kohm "
    ,R2);R2=27;
30 I21=1000*Vb1/R2;
31 R1=1000*(Vcc-Vb1)/I21;
32 printf("\nR1= %d kohm which is standard value",ceil(
    R1));

```

---

#### Scilab code Exa 11.10 Capacitor values for 2 stage amplifier

```

1 //chapter 11
2 //example 11.10
3 //page 334
4 clear all;
5 clc ;
6 //given
7 f1=150; //lower cutoff frequency Hz
8 hfe=50;
9 hie=0.5;
10 R1=68;R2=27; //kohm
11 Zi=round(1000/(1/R1+1/R2+1/hie));
12 XC1=Zi/10;
13 C1=10^6/(2*%pi*f1*XC1);
14 printf("\nC1=%0.1 f microF ,use standard value 22
    microF",C1);
15
16 XC2=1000*0.65*hie/(1+hfe);
17 XC2=6.4;
18 C2=10^6/(2*%pi*f1*XC2);
19 printf("\nC2=%d microF, standard value 180 microF",
    ceil(C2));
20 R1=100;
21 XC3=0.65*R1;
22 C3=10^6/(2*%pi*f1*XC3);

```

```
23 printf("\nC3=%0.1f microF, standard value 18 microF"
    ,(C3));
```

---

#### Scilab code Exa 11.11 AC analysis of 2 stage amplifier

```
1 //chapter 11
2 //example 11.11
3 //page 334
4 clear all;
5 clc ;
6 //given
7 R1=0.100;//load resistance in kohm
8 R1=68;R2=27;R3=5.6;R5=3.3;//kohm
9 hie=0.5;hic=hie;
10 hfe=50;
11 hfe1=50;
12 hfc=1+hfe;
13 Zi=round(1000/(1/R1+1/R2+1/hie));
14 printf("\ninput impedance (Zi)=%d ohm",Zi)
15
16 Zo1=((hic+R3)/hfc);
17 Zo=1000*(Zo1*R5)/(Zo1+R5);
18 printf("\noutput impedance (Zo)=%d ohm",Zo);
19
20 Zi2=((R5*R1)/(R5+R1))*hfc+hic;
21
22 Av1=-((hfe1*((R3*Zi2)/(R3+Zi2)))/hie);
23 Av2=1;
24 Av=Av1*Av2;
25 printf("\noverall voltage gain (Av)=%d",Av);
```

---

#### Scilab code Exa 11.12 Design DC feedback amplifier

```

1 //chapter 11
2 //example 11.12
3 //page 338
4 clear all;
5 clc ;
6 //given
7 R1=50;//load resistance in kohm
8 Vcc=12;//supply voltage V
9 f1=150;//lower cutoff frequency Hz
10 Vp=50;////op voltage mV
11 hfe=70;
12 ip=Vp/R1;
13 Ie2=2;//Ie2>ip
14 Ve2=5;
15 R4=Ve2/Ie2;
16 printf("\nR4= %.1f kohm ,use standard value 2.2 kohm
    ",R4);R4=2.2;
17 Ic2=2;
18 Ic1=Ic2;
19 VR1=Vcc-(Ve2+0.7);
20 R1=VR1/Ic1;
21 printf("\nR1= %.2f kohm,use standard value 3.3 kohm
    ",R1);R1=3.3;
22 Ib1=1000*Ic1/hfe;
23 R23=1000*(Ve2-0.7)/Ib1;
24 R2=47;
25 R3=R23-R2;
26 hfe1=100;hie1=1;
27 Zi=1000*(R2*hie1)/(R2+hie1);
28 XC1=Zi/10;
29 C1=10^6/(2*%pi*f1*XC1);
30 printf("\nC1=%0.1f microF ,use standard value 15
    microF",C1);
31 XC2=floor(R3/100);
32 C2=10^3/(2*%pi*f1*XC2);
33 printf("\nC2=%0.2f microF ,use standard value 1.2
    microF",C2));
34 XC3=R1;

```



```

35 C3=10^6/(2*%pi*f1*XC3);
36 printf("\nC3=%0.1 f microF ,use standard value 22
    microF" ,(C3));

```

---

### Scilab code Exa 11.13 Resistors for BIFET amplifier

```

1 //chapter 11
2 //example 11.13
3 //page 342
4 clear all;
5 clc ;
6 //given
7 Rl=180; //load resistance in kohm
8 Vcc=20; //supply voltage V
9 f1=150; //lower cutoff frequency Hz
10 Zi=500; //ip impedance kohm
11 Idmax=2; //drain current mA
12 Vgs=-4.1; //gate to source voltage
13 Vpmax=6; //maximum peak voltage
14 Vdsmin=Vpmax+1+Vgs;
15 Vr34=Vcc-Vdsmin;
16 VR31=8.5;
17 VR41=VR31; Id=2;
18 R3=VR31/Id;
19 R4=R3;
20 printf("\nR4=R3= %0.2 f kohm ,use standard value 3.9
    kohm" ,R4); R4=3.9;
21 VR3=Id*R4;
22 VR4=VR3;
23 VR2=VR4+Vgs;
24 VR1=Vcc-VR2;
25 R2=560; //assuming
26 R1=10^-3*(VR1*R2)/VR2;
27 printf("\nR1= %0.1 f Mohm ,use standard value 2.7 Mohm
    " ,R1); R1=2.7;

```

```

28 Ic2=1;
29 VR5=VR3-0.7;
30 R5=VR5/Ic2;
31 printf("\nR5= %.1f kohm, use standard value 6.8 kohm
    ",R5);R5=6.8;
32 Ic2=VR5/R5;
33 VR6=Vcc-VR5-3;
34 R6=VR6/Ic2;
35 printf("\nR6= %.1f kohm, use standard value 8.2 kohm
    ",R6);R6=8.2; //R6<<R1

```

---

#### Scilab code Exa 11.14 Capacitors for BIFET amplifier

```

1 //chapter 11
2 //example 11.14
3 //page 344
4 clear all;
5 clc ;
6 //given
7 R1=2700;R2=560;
8 f1=150; //lower cutoff frequency Hz
9 Zi=round(1000*(R1*R2)/(R1+R2));
10 XC1=Zi/10;
11 C1=10^6/(2*%pi*f1*XC1);
12 printf("\nC1=%0.2f microF which is standard value",C1
    );
13
14 gm=6000;
15 XC2=0.65/gm;
16 C2=1/(2*%pi*f1*XC2);
17 printf("\nC2=%0.1f microF, standard value 10 microF", (
    C2));
18
19 hie=1;hfe=100;
20 XC3=1000*(0.65*hie)/(1+hfe);

```

```

21 XC3=6.5;
22 C3=10^6/(2*%pi*f1*XC3);
23 printf("\nC3=%d microF,standard value 180 microF", (
    C3));
24 R1=180;
25 XC4=R1/10;
26 C4=10^3/(2*%pi*f1*XC4);
27 printf("\nC4=%0.3f microF,standard value 0.06 microF"
    ,(C4));

```

---

# Chapter 12

## Amplifiers with negative feedback

Scilab code Exa 12.1 Modification of 2 stage amplifier to voltage series feedback

```
1 //chapter 12
2 //example 12.1
3 //page 364
4 clear all;
5 clc ;
6 //given
7 Av=75;//voltage gain
8 R10=12;//coupling resistor in kohm
9 R7=R10;
10 R9=1000*R10/Av;
11 printf("\nFeedback component R9 is %d ohm,select 150
        ohm standard value to make Av \nslightly greater
        than specified.",R9);
12 R9=150;
13 f1=100;
14 XC6=1000*R10/100;
15 C6=10^6/(2*%pi *f1*XC6);
16 printf("\ncapacitor C6 is %.1f microF ,use 15 microF
        standard value",C6);
```

```

17 XC2=R9;
18 C2=10^6/(2*%pi *f1*XC2);
19 printf("\ncapacitor C2 is %.1f microF, use 15 microF
    standard value",C2);

```

---

### Scilab code Exa 12.2 Analyze negative feedback amplifier

```

1 //chapter 12
2 //example 12.2
3 //page 364
4 clear all;
5 clc ;
6 //given values in ohm
7 Zi2=967;
8 hfe1=100;
9 R3=12000;
10 hie1=1000;
11 R9=150;
12 hfe2=100;
13 hie2=1000;
14 R7=R3;
15 RL=120*10^3;
16 R10=R7;
17 R1=RL;
18 R2=39*10^3;
19 //voltage gain of stage 1
20 A1=-hfe1*(R3*Zi2/(R3+Zi2))/(hie1+R9*(1+hfe1));
21 printf("\nvoltage gain of stage 1=%.1f",A1);
22 //voltage gain of stage 2
23 Rp=(1/R7)+(1/RL)+(1/R10);
24 A2=-hfe2*(1/Rp)/hie2;
25 printf("\nvoltage gain of stage 2=%d",A2);
26 //open loop gain
27 A1=-5.5;A2=-571;
28 M = (A1)*(A2) ;

```

```

29 printf("\nopen loop gain =%d",M);
30 //feedback factor
31 B=R9 /(R9 + R10);
32 b=B^-1;
33 printf("\nfeedback factor(beta)=1/%d",b)
34 Av1=1/B; //for M*beta >>1
35 Av2=M/(1+M*B); //closed loop gain
36 printf("\nclosed loop gain=%d or %d if M*beta >>1",
        ceil(Av2),Av1);
37 Zb=hie1;
38 Zin=(1+M*B)*Zb;
39 //input impedance
40 Zi=1/((1/Zin)+(1/R1)+(1/R2))*10^-3;
41 printf("\ninput impedance=%d kohm",ceil(Zi));
42 //output impedance
43 Zout=(R7*R10/(R7+R10))/(1+M*B);
44 printf("\noutput impedance =%d ohm",ceil(Zout));
45 XC1=Zi/10;
46 f1=100; //Hz
47 C1=10^3/(2*pi *f1*XC1);
48 printf("\ncapacitor C1=%0.2f microF ,use standard
        value 1 microF",C1)

```

---

### Scilab code Exa 12.3 Single stage CE amplifier using current feedback

```

1 //chapter 12
2 //example 12.3
3 //page 371
4 clear all;
5 clc ;
6 //given
7 Vcc=20; //supply voltage
8 Rl=500; //load resistance
9 Av=75; //closed loop voltage gain
10 f1=30; // i/p signal frequency Hz

```

```

11 hfe=80;
12 hie=1.4;
13 Ve=5;Vce=3;
14 VR2=5.7;
15 Vbe=5;
16 VR3=Vcc-Vce-Ve;
17 R3=R1/10;
18 Ic=VR3/R3*10^3;
19 printf("\ncollector current = %d microA,\ntoo small
    for operations of transistor,\nSo Ic=1 mA",Ic)
20 Ic=1;
21 R3=VR3/Ic;
22 printf('\nR3=%d kohm which is standard value',R3)
23 R45=(Ve/Ic);
24 R4=1000*((R3*R1)/(R3+R1))/Av;
25 printf("\nR4=%d ohm ,use standard value 150 ohm",R4)
    ;R4=150;
26 R5=R45-R4/1000;
27 printf("\nR5=%0.2 f kohm ,use standard value 5.6 kohm"
    ,R5);
28 R5=5.6; //kohm
29 //potential divider current and resistors
30 I2=Ic/10;
31 Ve=0.7;
32 R2=(Vbe+Ve)/I2;
33 printf("\nR2=%d kohm,use standard value 56 kohm",R2)
    ;R2=56;
34 R1=(Vcc-VR2)/I2;
35 printf("\nR1=%d kohm,use standard value 150 kohm",R1)
    );R1=150;
36 Zb=hie+(1+hfe)*R4/1000;
37 //input impedance
38 Zi=1/((1/Zb)+(1/R1)+(1/R2));
39 printf("\ninput impedance=%0.2 f kohm", (Zi));
40 //capacitance
41 XC1=Zi/10;
42 XC1=1;
43 C1=10^3/(2*%pi *f1*XC1);

```

```

44 printf("\ncapacitor C1=%0.1f microF ,use standard
    value 5.6 microF",C1))
45 XC2=R4;
46 C2=10^6/(2 * %pi *f1* XC2);
47 printf("\ncapacitor C2=%0.1f microF ,use standard
    value 39 microF",C2)
48 C3=10^3/(2*%pi *f1*R1/10);
49 printf("\ncapacitor C3=%0.3f microF ,use standard
    value 0.1 microF",C3)

```

---



# Chapter 13

## IC operational amplifiers and Opamp applications

Scilab code Exa 13.1 Output voltage of differential amplifier

```
1 //chapter 13
2 //example 13.1
3 //page 396
4 clear all;
5 clc ;
6 //given
7 Rc=10; //collector resistors
8 Re=3.9; //emitter resistor
9 Vcc=12; Vee=-12; //dual supply
10 Vbe=0.7;
11 Vb4=-3.5; //Q4 base voltage with respect to ground
12 VB4=Vb4-(Vee); //voltage at base of transistor 4
13 Ie=(VB4-Vbe)/Re; //emitter current
14 printf("\nemitter current through Q4= %d mA", Ie);
15 Ie2=Ie/2;
16 Ie1=Ie2;
17 Ic1=Ie1;
18 Ic2=Ie2;
19 printf("\nemitter currents through Q1&Q2= %d mA", Ie1
```

```

    );
20 printf("\ncollector currents through Q1&Q2= %d mA",
    Ic1);
21 Vc2=Vcc-Ic1*Rc;
22 Vc1=Vc2;
23 printf("\nvoltage across collectors of transistors
    Q1&Q2 = %d V",Vc1)

```

---

### Scilab code Exa 13.2 Impedance and gain for differential amplifier circuit

```

1 //chapter 13
2 //example 13.2
3 //page 397
4 clear all;
5 clc ;
6 //given
7 RC=10;//collector resistance
8 hie=1;//input resistance in kohm
9 hfe=50;//forward current transfer ratio
10 hoe=1;//output conductance in microS
11 Av=(hfe*RC)/(2*hie);//voltage gain
12 Zb=2*hie;
13 Zo=RC;
14 Acm=RC/(2*(1/hoe));
15 printf("\nvoltage gain=%d",Av);
16 printf("\ninput impedance=%d kohm",(Zb));
17 printf("\noutput impedance =%d kohm",(Zo));
18 printf("\ncommon mode gain=%dx10^-3",Acm);

```

---

### Scilab code Exa 13.3 Design voltage follower

```

1 //chapter 13
2 //example 13.3

```

```

3 //page 408
4 clear all;
5 clc ;
6 //given
7 Vbe=0.7;
8 Ibmax=500; //base current nA
9 R1max=10^6*Vbe/(10*Ibmax);
10 printf("\nR1max= %d kohm, use standard value 120 kohm
    ", R1max);
11 R1max=120;
12 R1=4; //load resistance in kohm
13 Xc2=R1;
14 f1=70; //lower cutt off frequency in Hz
15 c2=floor(100000/(2*%pi*f1*Xc2))/100;
16 printf("\nc2= %.2 f microF, standard value", (c2))
17 Xc2=R1max/10;
18 c1=1000/(2*%pi*f1*Xc2)
19 printf("\nc1= %.2 f microF, use standard value 0.2
    microF", c1)

```

---

#### Scilab code Exa 13.4 Design non inverting amplifier

```

1 //chapter 13
2 //example 13.4
3 //page 410
4 clear all;
5 clc ;
6 //given
7 Vi=50; //ip voltage in mV
8 Vo=2; //op voltage volts
9 Ibmax=500; //maximum base current nA
10 I2=(100*Ibmax)/1000;
11 printf("\noutput current (I2)=%d microA", I2);
12 R3=Vi/I2;
13 printf("\nR3=%d kohm, standard value", R3);

```

```

14 R23=1000*Vo/I2;
15 R2=R23-R3;
16 R1=(R2*R3)/(R2+R3)
17 printf("\nR2=%d kohm, standard value\nR1=%d kohm,
        standard value",R2,ceil(R1));

```

---

### Scilab code Exa 13.5 Design inverting amplifier

```

1 //chapter 13
2 //example 13.5
3 //page 414
4 clear all;
5 clc ;
6 //given
7 Av=144; //voltage gain
8 Vi=20; //ip voltage in mV
9 Ibmax=500; //maximum base current nA
10 //I1>>Ibmax
11 I1=(100*Ibmax)/1000;
12 printf("\ninput current (I2)=%d microA",I1);
13 R1=1000*Vi/I1;
14 printf("\nR1=%d ohm, use standard value 390 ohm",R1);
    R1=390;
15 R2=(Av*R1)/1000;
16 printf("\nR2=%0.1 f kohm, use standard value 56 kohm",
    R2);R2=56;
17 R3=R1; //R1 || R2
18 printf("\nR3=%d ohm, standard value", (R3));

```

---

### Scilab code Exa 13.6 Design Schmitt trigger

```

1 //chapter 13
2 //example 13.6

```

```

3 //page 424
4 clear all;
5 clc ;
6 //given schmitt trigger
7 Vcc=12;Vee=-12;//dual supply
8 Vo=19;
9 Ibmax=500;//maximum base current nA
10 UTP=5;
11 LTP=-5;//lower and upper trip points
12 I2=(100*Ibmax)/1000;
13 printf("\noutput current(I2)=%d microA",I2);
14 R2=(UTP/I2)*1000;
15 printf("\nR2=%d kohm, standard value ",R2);
16 R1=((Vo-UTP)/I2)*1000;
17 printf("\nR1=%d kohm,use standard value 270 ohm",R1)
    ;

```

---

# Chapter 14

## Operational amplifier frequency response and compensation

Scilab code Exa 14.1 Design inverting amplifier

```
1 //chapter 14
2 //example 14.1
3 //page 437
4 clear all;
5 clc ;
6 //given
7 Av=10; //voltage gain
8 vs=0.5; //input voltage
9 //datasheet of 741
10 Ibmax=1.5; //base current microA
11 I1=100*Ibmax; //microA
12 R1=vs/I1*1000;
13 printf("\nR1=%0.1 f kohm",R1);
14 R2=Av*R1;
15 R3=R1; //R1 || R2=R1
16 printf("\nR2=%0d kohm",R2);
17 printf("\nR3=%0.1 f kohm",R3);
18 printf("\nFrom datasheet of 741,\nFor Av=10,\nc1=100
      pF\nc2=500 pF\nc3=1000 pF")
```

---

**Scilab code Exa 14.2** Design non inverting amplifier

```
1 //chapter 14
2 //example 14.2
3 //page 439
4 clear all;
5 clc ;
6 //given
7 Av=100; //voltage gain
8 vs=0.5; //input voltage
9 //datasheet of 709
10 Ibmax=200; //base current nA
11 I1=100*Ibmax; //nA
12 R1=10^5*(vs/I1);
13 printf("\nR1=%0.1 f kohm, use standard value 2.2 kohm",
        R1); R1=2.2;
14 R2=Av*R1;
15 R3=R1; //R1 || R2=R1
16 printf("\nR2=%d kohm", R2);
17 printf("\nR3=%0.1 f kohm", R3);
18 Av=40;
19 printf("\nVoltage gain =%d db", Av)
20 printf("\nFrom datasheet of 741, \nFor Av=40 db, \nc1
        =100 pF \nc2=3 pF \nR1=1.5 kohm")
```

---

**Scilab code Exa 14.3** Design inverting amplifier with a gain of 50

```
1 //chapter 14
2 //example 14.3
3 //page 440
4 clear all;
```

```

5  clc ;
6  //given
7  Av=50;
8  //gain in db
9  Av=20*log10(Av)
10 printf("\\nVoltage gain=%d db",ceil(Av));
11 printf("\\nThere are no liststed component value for
    given gain\\nUse Av=20 db\\nc1=500 pF\\nc2=20 pF\\nR1
    =1.5 kohm ");

```

---

#### Scilab code Exa 14.4 Design voltage follower

```

1  //chapter 14
2  //example 14.4
3  //page 441
4  clear all;
5  clc ;
6  //given
7  Av=1; //voltage follower
8  printf("\\nc1=500 pF\\nc2=2000 pF\\nc3=1000 pF")

```

---

#### Scilab code Exa 14.5 Upper cutoff frequency of inverting amplifier

```

1  //chapter 14
2  //example 14.5
3  //page 442
4  clear all;
5  clc ;
6  //given
7  Av=100;
8  Av=20*log10(Av); //voltage gain in db
9  printf("\\nvoltage gain=%d db",ceil(Av));
10 //f2 occurs at(upper cutoff frequency)

```



```
11 M=ceil(Av+7.7);
12 f2=5;//from intersection of frequency response and M
    =48db of 741
13 printf("\nupper cutoff frequency for 741=%d khz",f2)
14 f2=200;//from intersection of frequency response and
    M=48db of 709
15 printf("\nupper cutoff frequency for 709=%d khz",f2)
```

---

# Chapter 15

## sinusoidal Oscillators

Scilab code Exa 15.1 Resistor and capacitor values for phase shift oscillator

```
1 //chapter 15
2 //example 15.1
3 //page 451
4 clear all;
5 clc ;
6 //given
7 vcc=10; //supply voltage(dual supply)
8 fo=1; //op frequency
9 Av=29; //voltage gain
10 Ibmax=500; //base current nA
11 I1=(100*Ibmax)/1000; //nA
12 vo=vcc-1; //op voltage
13 vi=vo/Av; //ip voltage
14 R1=1000*vi/I1;
15 printf("\nR1=%0.1 f kohm, use standard value 5.6 kohm",
        R1); R1=5.6;
16 R2=Av*R1;
17 printf("\nR2=%d kohm, use standard value 180 kohm", R2
        ); R2=180;
18 R3=R2;
19 printf("\nR3=%d kohm", R3);
```

```

20 R=R1;
21 printf("\nR=%0.1 f kohm",R);
22 c=1/(2*%pi*R*sqrt(6));
23 printf("\nC=%0.2 f microF, standard value 0.01 microF"
    ,c)

```

---

### Scilab code Exa 15.2 Design colpitts oscillator

```

1 //chapter 15
2 //example 15.2
3 //page 455
4 clear all;
5 clc ;
6 //given for colpitts oscillator
7 f=40000;//frequency in kHz
8 vcc=10;//supply voltage(dual supply)
9 L=0.1;//inductor in mH
10 Cr=(1/(4*(%pi)^2*f^2*L))/10^-12;
11
12 printf("\nCr=%0.1 f pF",Cr);
13 C1=Cr*10;C1=1500;
14 printf("\nC1=%0d pF",C1);
15 C2=1/(1/Cr-1/C1);
16 printf("\nC2=%0d pF,use standard value 180 pF",ceil(
    C2));C2=180;
17
18 XC2=10^9/(2*%pi*f*C2);
19 XC1=10^9/(2*%pi*f*C1);
20 printf("\nXC1=%0.2 f kohm\nXC2=%0d kohm",XC1,XC2);
21 //R1>>XC1
22 R1=10*XC1;
23 printf("\nR1=%0.1 f kohm,use standard value 27 kohm",
    R1);R1=27;
24 R2=(C1/C2)*R1;//R2>(C1/C2)*R1
25 printf("\nR2=%0d kohm,use standard value 270 kohm",R2

```

```

    );R2=270;
26 R3=R1;
27 printf("\nR3=%d kohm, standard value",R3);

```

---

### Scilab code Exa 15.3 Design Wein Bridge oscillator

```

1 //chapter 15
2 //example 15.3
3 //page 462
4 clear all;
5 clc ;
6 //given
7 vcc=10; //supply voltage(dual supply)
8 fo=10; //op frequency
9 Ibmax=500; //base current nA
10 I4=500; //current through R4 in microA
11 vo=vcc-1; //op voltage
12 R34=1000*vo/I4; //R3+R4
13 //R3=2xR4, R34=3*R4=18;
14 R4=R34/3;
15 printf("\nR4=%d kohm, use standard value 5.6 kohm",R4
    );R4=5.6;
16 R3=2*R4;
17 printf("\nR3=%.1f kohm, use standard value 12 kohm",
    R3);R3=12;
18 R2=R4; printf("\nR2=%.1f kohm",R2);
19 R1=R2; printf("\nR1=%.1f kohm",R1);
20 C=10^6/(2*%pi*R1*fo);
21 printf("\nC=%d pF, standard value 2700 pF",C)

```

---

### Scilab code Exa 15.4 Design phase shift oscillator

```

1 //chapter 15

```

```

2 //example 15.4
3 //page 463
4 clear all;
5 clc ;
6 //given
7 vomax=5;//op voltage max
8 Vf=0.7;//forward voltage drop across diode
9 f=5;//frequency of oscillation
10 I1=1;//current through inverting terminal mA, diodes
    are forward biased
11 Av=29;//voltage gain
12 R1=100*(vomax/(Av*I1));
13 R1=floor(R1)*10;
14 printf("\nR1=%d kohm, use standard value 150 kohm", R1
    ); R1=150;
15 R2=Av*R1/1000;
16 R2=4.4;
17 printf("\nR2=%0.1 f kohm", (R2));
18 R4=2*Vf/I1;
19 printf("\nR4=%0.1 f kohm, use standard value 1.5 kohm",
    R4); R4=1.5;
20 R5=R2-R4;
21 printf("\nR5=%0.1 f kohm", R5);
22 R6=0.4*R5;
23 printf("\nR6=%0.2 f kohm, use standard value 1 kohm",
    R6); R6=1;
24 R7=0.8*R5;
25 printf("\nR7=%0.2 f kohm, use standard value 2.7 kohm",
    R7); R7=2.7;
26 R3=R2;
27 printf("\nR3=%0.1 f kohm, use standard value 4.7 kohm",
    R3);
28 C=1000/(2*pi*R1*f*sqrt(6));
29 printf("\nC=%0.3 f microF, standard value 0.082", C)

```

---

# Chapter 16

## Power supplies Breakdown diodes and Voltage regulators

Scilab code Exa 16.1 Reservoir Capacitor for half wave rectifier

```
1 //chapter 16
2 //example 16.1
3 //page 473
4 clear all;
5 clc ;
6 //given
7 Eo=20;//supply voltage
8 Rl=500;//load resistance in ohm
9 Vr=10/100*Eo;//ripple voltage
10 fin=60;//ip frequency Hz
11 Eomin=Eo-1;
12 Eomax=Eo+1;
13 theta1=asin(Eomin/Eomax);//in radians
14 theta=(theta1*180)/%pi;//in degrees
15 T=1000/60;//in ms
16 //for 360 degree ,T
17 //for 180=>
18 T1=T *180/360;
19 T2=T1/2;//time for 90 degrees
```

```

20 T3=T*theta/360; //time for theta
21 t1=T1+T2+T3; //total time
22 I1=1000*Eo/R1; //current in mA
23 c=I1*t1/Vr;
24 printf("\nReservoir capacitor is %d microF, use
        standard value 330 microF",ceil(c))

```

---

#### Scilab code Exa 16.2 Diode specification for half wave rectifier

```

1 //chapter 16
2 //example 16.2
3 //page 475
4 clear all;
5 clc ;
6 //given
7 Eo=20; //supply voltage
8 Eomin=Eo-1;
9 Eomax=Eo+1;
10 theta1=asin(Eomin/Eomax); //in radians
11 theta=(theta1*180)/%pi; //in degrees
12 T=1000/60; //in ms
13 T1=T *180/360;
14 T2=T1/2; //time for 90 degrees
15 T3=T*theta/360; //time for theta
16 t1=T1+T2+T3; //total time in ms
17 t2=1.17; //ms
18 I1=40; //mA
19 //diode peak repetitive current
20 Ifm=ceil(I1*(t1+t2)/t2); //mA
21 //diode avg forward current
22 Io=I1;
23 Vp=Eomax+0.7; //Vf=0.7V
24 //diode maximum reverse voltage
25 Er = 2 * Vp
26 printf("\nIFM(rep)=%d mA",Ifm)

```

```

27 printf("\nFor 1n4001,\nVr=50 V\nIo=1 A\nIFM=10 A\
    nThis is suitable for required application.")
28 Ifmsurge=30;
29 printf("\nIFM(surge)=%d A",Ifmsurge)
30 Rs=Vp/Ifmsurge;
31 printf("\nRs=%0.1 f ohm",Rs);

```

---

### Scilab code Exa 16.3 Reservoir Capacitor for bridge rectifier

```

1 //chapter 16
2 //example 16.3
3 //page 477
4 clear all;
5 clc ;
6 //given
7 Vr=2; //ripple voltage
8 Eo=20; //supply voltage
9 Eomin=Eo-1;
10 Eomax=Eo+1;
11 theta=65; //in degrees
12 T2=4.17; //time for 90 degrees ms
13 T3=3; //time for theta ms
14 I1=40; //mA
15 t2=1.17; //ms
16 t1=T2+T3;
17 C=I1*t1/Vr;
18 printf("\nReservoir capacitor is %d microF, use
    standard value 150 microF", (C))
19 //diode peak repetitive current
20 Ifm=(I1*(t1+t2)/t2); //mA
21 printf("\ndiode peak repetitive current IFM(rep)=%d
    mA", Ifm)
22 //diode avg forward current
23 Io=I1/2;
24 printf("\ndiode average forward current(Io)=%d mA",

```



```

        Io);
25 //diode maximum reverse voltage
26 Vp=Eomax+2*0.7;//Vf=0.7V
27 Er=Vp;
28 printf("\nEr=%0.1 f V",Er);
29 printf("\n1N4001 is required")

```

---

#### Scilab code Exa 16.4 Diode specification and Capacitor for Zener circuit

```

1 //chapter 16
2 //example 16.4
3 //page 482
4 clear all;
5 clc ;
6 //given
7 Vs=24;//dc supply
8 printf("\nSuitable device is 1N757,from datasheet")
9 Vz=9.1;//nominal voltage
10 Iz=20;//nomonal current
11 R1=1000*(Vs-Vz)/Iz;
12 printf("\nseries resistance R1=%d ohm,use standard
        value 820 ohm",R1);R1=820;
13 Vs=20;
14 Iz=1000*(Vs-Vz)/R1;
15 printf("\nWhen Vs=20 V,Iz=%0.1 f mA ",Iz);

```

---

#### Scilab code Exa 16.5 Design Zener diode voltage reference

```

1 //chapter 16
2 //example 16.5
3 //page 484
4 clear all;
5 clc ;

```

```

6 //given
7 Vs=15; //dc supply
8 Vref=6;
9 printf("\nSuitable device is 1N753,from datasheet")
10 Vz=6.2; //nominal voltage
11 P=400; //nominal power in mW
12 Izmin=5;
13 Izm=P/Vz; //Izm=IImax+Izmin
14 R1=10^3*(Vs-Vz)/Izm;
15 printf("\nseries resistance R1=%d ohm,use standard
        value 150 ohm",R1);R1=150;
16 Izm=1000*(Vs-Vz)/R1;
17 IImax=Izm-Izmin;
18 printf("\nMax load current =%d mA ",ceil(IImax))

```

---

#### Scilab code Exa 16.6 LR and RR for regulator circuit

```

1 //chapter 16
2 //example 16.6
3 //page 485
4 clear;
5 clc ;
6 //given
7 Zzr=7; //dynamic impedance of 1N753
8 Vs=15; //dc supply
9 R1=150;
10 Vo=6.2;
11 IImax=55;
12 deltaVs=10/100*Vs;
13 deltaVo=1000*deltaVs*Zzr/(R1+Zzr);
14 //line regulation
15 lineR=(deltaVo*100/Vo)/1000;
16 printf("\nline regulation=%d%% ",lineR)
17 deltaIl=IImax;
18 deltaVo=deltaIl*(Zzr*R1/(Zzr+R1));

```

```

19 //load regulation
20 loadR=(deltaVo*100/Vo)/1000;
21 printf("\nload regulation=%0.1f%% ",loadR)
22 //ripple rejection
23 RR = 20*log10((R1+Zzr)/Zzr);
24 printf("\nripple rejection= %d db",RR)

```

---

#### Scilab code Exa 16.7 LR and RR for rectifier and filter circuit

```

1 //chapter 16
2 //example 16.7
3 //page 489
4 clear;
5 clc ;
6 //given
7 Eoavg=20;
8 Eomax=21;
9 Vo=12;
10 Av=100//voltage gain
11 //10% change in filter op
12 deltaEo=10/100*20;
13 deltaVs=deltaEo;
14 deltaVo=1000*deltaVs/Av;//mV
15 //line regulation
16 lineR=(deltaVo*100/Vo)/1000;
17 printf("\nline regulation=%0.2f%% ",lineR);
18 //Eo changes from Eomax to Eoavg
19 deltaEo=Eomax-Eoavg;
20 deltaVs=deltaEo;
21 //Il change from no load to full load
22 deltaVo=1000*deltaVs/Av;
23 //load regulation
24 loadR=(deltaVo*100/Vo)/1000;
25 printf("\nload regulation=%0.2f%% ",loadR)

```

---

### Scilab code Exa 16.8 Design voltage regulator

```
1 //chapter 16
2 //example 16.8
3 //page 490
4 clear all;
5 clc ;
6 //given
7 Vs=20; //supply voltage
8 Vo=12; //op voltage
9 Ilmax=40; //maximum load current mA
10 Vz=Vo/2;
11 printf("\nSuitable device is 1N753,from datasheet")
12 Vz=6.2; //nominal voltage
13 //to keep D1 in breakdown
14 IR2=10; //mA
15 R2=1000*(Vo-Vz)/IR2;
16 printf("\nR2=%d ohm,standard value 560 ohm",R2);
17 IE1max=Ilmax+IR2;
18 //power dissipation in Q1
19 P1max=IE1max*(Vs-Vo);
20 VCE1max=Vs;
21 IC1max=IE1max;
22 //choosing suitable transistor and finding it's
    hfemin at IC=50mA
23 hfemin=50;
24 IB1max=IE1max/hfemin;
25 //IC2>>IB1max, let
26 IC2=5;
27 VB1=Vo+0.7;
28 R1=(Vs-(VB1))/(IC2+IB1max);
29 R1=R1-0.01;
30 printf("\nR1=%.2f kohm,standard value 1.2 kohm",R1);
31 IE2=5; IR2=10;
```

```

32 Iz=IE2+IR2;
33 //I4>>IB2, let
34 I4=1;
35 R4=(Vz+0.7)/I4;
36 printf("\nR4=%0.1 f kohm, standard value 6.8 kohm",R4);
37 R3=(Vo-6.9)/I4;
38 printf("\nR3=%0.1 f kohm, standard value 4.7 or 5.6
    kohm for Vo<12 or Vo>12 resp",R3);

```

---

#### Scilab code Exa 16.9 Design opamp voltage regulator

```

1 //chapter 16
2 //example 16.9
3 //page 4
4 clear all;
5 clc ;
6 //given
7 Ilmax=100; //maximum op current
8 Vs=20; //supply voltage
9 //maximum op voltage 10–15V
10 Vomin=10; Vomax=15;
11 Vz1=Vomin/2;
12 Vz2=Vomax/2;
13 printf("\nSuitable device is 1N753, from datasheet")
14 Vz=6.2; //nominal voltage
15 Izr=20;
16 Iz=Izr;
17 Voavg=12.5;
18 R1=1000*(Voavg-Vz)/Iz;
19 printf("\nR1=%d ohm, standard value 330 kohm",R1);R1
    =330;
20 //I3>Ibmax for opAmp, let
21 I3min=1;
22 //Vo=min, wiper at top of R4
23 R3R4=Vz/I3min;

```

```

24 VR3=Vz;
25 R2=(Vomin-VR3)/I3min;
26 printf("\nR2=%0.1f kohm, standard value 3.3 kohm",R2);
    R2=3.3;
27 //Vo=max, wiper at bottom of R4
28 I3max=Vomax/(R2+R3R4);
29 R3=Vz/I3max;
30 R4=(R3R4)-R3;
31 printf("\nR3=%0.1f kohm",R3);
32 printf("\nR4=%0.1f kohm, standard value 3 kohm",R4);
33 //Q1 specification
34 P1=(Vs-Vomin)*(I1max+Iz+I3min);
35 P1=P1/1000;
36 printf("\nP1=%0.2f W",P1)
37 Vcemax=Vs;
38 ICmax=I1max+Iz+I3min;
39 printf("\nVcemax=%d V, ICmax=%d mA",Vcemax,ICmax)

```

---

#### Scilab code Exa 16.10 Design voltage regulator circuit

```

1 //chapter 16
2 //example 16.10
3 //page 504
4 clear all;
5 clc ;
6 //given
7 Vo=10;//op voltage
8 I2=1;//error amplifier ip bias current
9 Vref=7.15;//V reference
10 VR2=Vref;
11 R2=Vref/I2;
12 printf("\nR2=%0.2f kohm, standard value 6.8 kohm",R2);
    R2=6.8;
13 I2=Vref/R2;//mA
14 R1=(Vo-Vref)/I2;

```

```

15 printf("\nR1=%0.1f kohm, standard value 2.7 kohm",R1);
16 Vs=Vo+5; //for satisfactory operation of pass Xtor
17 I=25; //internal ckt current Istandby+Iref
18 //internal power dissipation
19 Pi=Vs*I;
20 printf("\ninternal power dissipation=%d mW",Pi)
21 //max power dissipation in series pass Xtor
22 PDmax=1000;
23 P=PDmax-Pi;
24 printf("\nmax power dissipation in series pass
    transistor=%d mW",P)
25 //maximum load current
26 Ilmax=P/(Vs-Vo);
27 printf("\nmaximum load current=%d mA",Ilmax);

```

---

#### Scilab code Exa 16.11 Design voltage regulator using LM217 IC

```

1 //chapter 16
2 //example 16.11
3 //page 507
4 clear all;
5 clc ;
6 //given
7 Vo=6; //op voltage
8 Vs=15; //supply voltage
9 Iadj=100; //microA
10 I1=2.5;
11 Vref=2.5;
12 R1=Vref/I1;
13 printf("\nR1=%d kohm",R1);
14 R2=(Vo-Vref)/I1;
15 printf("\nR2=%0.1f kohm, use 1.2 kohm + 200 ohm in
    series",R2);

```

---

# Chapter 17

## Large signal amplifiers

Scilab code Exa 17.1 Dc ac load line for CE circuit

```
1 //chapter 17
2 //example 17.1
3 //page 518
4 clear;
5 clc ;
6 //given
7 //dc load line
8 Vcc=13;//supply voltage
9 R1=4.7;R2=3.7;RE=1;
10 Rpy=40;
11 N1=74;N2=14;
12 Rl=56;
13 //plot point A(Vce,Ic)=(Vcc,0)
14 VB=Vcc*R2/(R1+R2);
15 VE=VB;
16 VBE=VB-0.7;
17 IE=VE/RE;
18 IC=IE;
19 VCE=Vcc-IC*(Rpy+RE);//plot point Q(VCE,IC)=(8,5)
20
21 VCE=[13,8];
```



```

22 IC=[0,5];
23 plot(VCE,IC)
24 xtitle('dc load line','VCE in V','IC in mA')
25
26 //ac load line
27 Rl'==(N1/N2)^2*Rl;
28 //total ac load
29 Rlac=(Rpy+Rl')/1000;
30 deltaIC=5;
31 deltaVCE=deltaIC*Rlac;
32 //point B(VCE,IC)=(16,0)
33 VCE=[8,16];
34 IC=[5,0];
35 figure,plot(VCE,IC,'r-.');
36 xtitle('ac load line','VCE in V','IC in mA')

```

---

#### Scilab code Exa 17.2 Maximum Efficiency of Transformer

```

1 //chapter 17
2 //example 17.2
3 //page 522
4 clear all;
5 clc ;
6 //given
7 eta=80; //Xformer efficiency
8 Vcc=13; //supply voltage
9 ICQ=5;
10 Pi=Vcc*ICQ; //ip power dissipation in mW
11 VCEQ=8;
12 Vp=VCEQ;
13 ICEQ=5;
14 Ip=ICEQ;
15 //power delivered to Xformer primary
16 Po1=(Vp*Ip)/2;
17 //Xformer op power

```

```

18 Po = eta * Po1 ; //mW
19 //ckt efficiency
20 efficiency=(Po/Pi);
21 printf("\nMaximum ckt efficiency of class A
    amplifier =%.1f%%",efficiency);

```

---

### Scilab code Exa 17.3 Transformer output for class B

```

1 //chapter 17
2 //example 17.3
3 //page 528
4 clear all;
5 clc ;
6 //given
7 Rl=16; //load resistance
8 Vcc=30; //supply voltage
9 eta=0.8; //Xformer efficiency
10 Po=4;
11 Po1=Po/eta; //ac power delivered to Xformer primary
12 Vp=Vcc;
13 Rl1=(Vp^2)/(2*Po1);
14 Rl2=4*Rl1;
15 printf("\nTransformer specification are:\nPo=%d W\
    nRl=%d ohm\nRl'''' =%d ohm center tapped",Po,Rl,
    Rl2);
16 //max Xtor vol
17 Vcemax=2*Vcc;
18 Ip=(2*Po1)/Vp;
19 //max Xtor current
20 Icmx=1000*Ip;
21 //dc ip power
22 Iavg=0.636*Ip*1000;
23 Pi=10^-3*Vcc*Iavg;
24 //power in each op Xtor
25 Pr=(Pi-Po1)/2;

```

```

26 printf("\nTransistor specification are:\nPr=%0.2 f W\
    nVcemax=%d V\nIcmax=%d mA",Pr,Vcemax,Icmax);

```

---

#### Scilab code Exa 17.4 Design capacitor coupled amplifier

```

1 //chapter 17
2 //example 17.4
3 //page 523
4 clear all;
5 clc ;
6 //given
7 Rl=100; //load resistance
8 Po=0.5; //output power
9 //peak output voltage
10 Vp=sqrt(2*Rl*Po);
11 //peak output current
12 Ip=1000*(2*Po)/Vp;
13 Vr6=0.1*Vp;
14 Vr7=Vr6;
15 R6=1000*Vr6/Ip;
16 R7=R6;
17 //quiescent current
18 Iq2=Ip/10;
19 //dc voltage across R4
20 Vr4dc=0.7+10^-3*Iq2*(R6+R7)+0.7;
21 //bias components for Q2 &Q3
22 deltaVB=Vp+Vr6;
23 Vce1dc=deltaVB+1;
24 Vr3dc=Vce1dc;
25 Vr5=5; //bias stability
26 Vcc=Vr5+Vce1dc+Vr4dc+Vr3dc;
27 printf("\nVCC=%0.1 f V, use VCC=30 V",Vcc);Vcc=30;
28 //Icql>>Ibmax
29 hfe=50; //assuming equal for all 3 Xtors
30 Ibmax=Ip/hfe;

```

```

31 Icq1=10;
32 R3=Vr3dc/Icq1;
33 R4=1000*Vr4dc/Icq1;
34 printf("\nR3=%0.1f kohm, standard value ",R3);
35 printf("\nR4=%0d kohm,use standard value 200 ohm",
    ceil(R4));
36 printf("\nR6=R7=%0d ohm",R6);

```

---

#### Scilab code Exa 17.5 Design capacitors of amplifier circuit

```

1 //chapter 17
2 //example 17.5
3 //page 535
4 clear all;
5 clc ;
6 //given
7 f1=20;//lower cutoff frequency Hz
8 R3=1.2;//kohm
9 R1=100;//ohm
10 Vcc=30;
11 //Xc2<<R3 at f1
12 C2=1000/(2*%pi*f1*R3/10);
13 printf("\nc2=%0.1f microF,use standard value 75
    microF",C2);
14 XC4=R1;
15 C4=10^6/(2*%pi*f1*R1);
16 printf("\nc4=%0.1f microF,use standard value 80
    microF",C4);
17 Ip=100;
18 Vcemax=Vcc;
19 Icmax=1.1*Ip;
20 //dc ip power
21 Pidc=(Vcc*0.35*Ip)/1000;
22 Poac=0.5;
23 Pr=(Pidc-Poac)*0.5;

```

```

24 printf("\\nTransistor specification are:\\nPr=%0.2f W,
    Vcemax=%0d V,Icmax=%0d mA",Pr,Vcemax,Icmax);

```

---

**Scilab code Exa 17.6** Supply and output voltages for amplifier circuit

```

1 //chapter 17
2 //example 17.6
3 //page 543
4 clear all;
5 clc ;
6 //given
7 Rl=50;//load resistance
8 Po=10;//op power
9 //peak op voltage
10 Vp=round(sqrt(2*Rl*Po));
11 Vr14=0.1*Vp;//when Ip flows
12 Vr15=Vr14;;
13 Vce4min=1
14 Vce3min=Vce4min;
15 Vr9=3;
16 Vr10=Vr9;
17 Vcc=ceil(Vp+Vr14+Vce3min+0.7+Vr9);
18 printf("\\nVCC=%0d V",Vcc);
19 Ip=1000*(2*Po)/Vp;
20 //dc ip power
21 Iavg=0.636*Ip*1.1;
22 Pi=10-3*Vcc*Iavg;Pi=17.5;
23 //power in each op Xtor Q7 & Q8
24 Pr1=(Pi-Po)/2;
25 Vcemax=Vcc-(-40);
26 Icmax=ceil(1.1*Ip);
27 printf("\\nTransistor specification for Q7,Q8 are:\\n
    Pr=%0.2f W,Vcemax=%0d V,Icmax=%0d mA",Pr1,Vcemax,
    Icmax);
28 //power in each op Xtor Q5 & Q6

```

```

29 Vcemax=2*Vcc;
30 hfe=30;
31 Icmx=ceil(1.1*Ip/hfe);
32 Pr=1000*Pr1/hfe;
33 printf("\nTransistor specification for Q5,Q6 are:\n
        nPr=%d W,Vcemax=%d V,Icmx=%d mA",Pr,Vcemax,Icmx
        );

```

---

### Scilab code Exa 17.7 Analyze MOSFET power amplifier circuit

```

1 //chapter 17
2 //example 17.7
3 //page 547
4 clear;
5 clc ;
6 //given
7 Rl=10;//load resistance
8 Po=5;//op power
9 Rdsmin=4;
10 gm=250;//mA/V
11 //peak op voltage
12 Vp=round(sqrt(2*Rl*Po));
13 Rl=20;
14 Ip=Vp/Rl;
15 //supply voltage
16 Vcc=[Vp+(Ip*Rdsmin)];
17 printf("\nVCC=+-%d V",Vcc);
18 Vth=1;
19 Vr13=Vth;Vr14=Vth;
20 deltaVr14=10^-3*Ip/gm;
21 deltaVr13=deltaVr14;
22 //to avoid turn off of Q1,let
23 deltaVr3=2;
24 Vr3=deltaVr3+1;
25 Vr7=Vr3;Vr6=Vr3;

```

```
26 //to avoid saturation of Q2
27 Vce2=Vp+Vr7+1;
28 Vr4r5=2*Vcc-Vr6-Vr7-Vce2;
29 printf("\nVoltage drops across R3,R6,R7 is %d V and
        across R4+R5 is %d V",Vr3,Vr4r5)
```

---

# Chapter 18

## Thyristors and unijunction transistors

Scilab code Exa 18.1 Analyze SCR circuit

```
1 //chapter 18
2 //example 18.1
3 //page 559
4 clear all;
5 clc ;
6 //given
7 Rl=15;//load resistance
8 ep=30;//peak ip voltage
9 Rg=1;//gate resistance kohm
10 //forward blocking voltage VFXm>30 for SCR to remain
    in off until triggered
11
12 VAK=1;
13 Ip=(ep-VAK)/Rl;
14 //rms value of Il
15 Irms=0.5*Ip;
16 printf("\nIrms=%.2f A and ep=%d V",Irms,ep);
17 printf("\nC6F is suitable SCR with VFXM=50 V,
    current range allowable is 1.6 A");
```



```

18
19 //from chart
20 Vg=0.5; //Trigger voltage
21 Ig=0.025 //mA
22 Irg=Vg/Rg;
23 It=Ig+Irg; //trigger current
24 printf("\nTrigger voltage=%0.1f V and trigger current
    =%0.3f mA",Vg,It);
25 Ih=1;
26 Il=Ih;
27 ei=VAK+1000*Il*Rl;
28 ei=1;
29 printf("\nei=%0d V\nSCR will switch off when ei falls
    below 1 V",ei);

```

---

#### Scilab code Exa 18.2 Design SCR circuit

```

1 //chapter 18
2 //example 18.2
3 //page 559
4 clear;
5 clc ;
6 //given
7 Rl=15; //load resistance
8 ep=30; //peak input voltage
9 Vg=0.5; //Trigger voltage
10 Ig=10; //trigger current in microA
11 //at 5 degrees
12 a=(5*%pi)/180;
13 ei1=ep*sin(a);
14 //at 90 degrees
15 ei2=ep;
16 //when SCR triggers
17 Vt=Vg+0.7+(10^-6*Ig*Rl);
18 //to trigger SCR at ei=2.6V,moving contact of R2

```

```

        must be at the top
19 Vr2r3=Vt;
20 Vr1=ei1-Vt;
21 I1min=100; //microA
22 R1=1000*Vr1/I1min;
23 printf("\nR1=%d kohm, standard value 12 kohm",R1);R1
    =12;
24 I11=floor(10^3*Vr1/R1);
25 R23=10^3*Vt/I11;
26 I1=ei2/(R1+R23); //I1=1.35;
27 //to trigger SCR at ei=30V, moving contact of R2 must
    be at the bottom
28 R3=(10^3*Vt/I1);
29 printf("\nR3=%d ohm, standard value 820 ohm",R3);R3
    =820; R23=10.3;
30 R2=R23-R3/1000;
31 printf("\nR2=%0.2 f kohm, standard value 10 kohm",R2);
    R2=10;

```

---

### Scilab code Exa 18.3 Design resistor for 4 layer diode circuit

```

1 //chapter 18
2 //example 18.3
3 //page 569
4 clear;
5 clc ;
6 //given
7 E=30;
8 Vs=10; //supply voltage
9 Is=500; //ip current
10 Ih=1.5; //mA
11 Vf=1; //forward voltage drop
12 R1max=1000*(E-Vs)/Is;
13 R1min=(E-Vf)/Ih;
14 printf("\nmaximum and minimum values of R1 are %d

```

```
kohm ,%.1f kohm respectively.",R1max,R1min);
```

---

#### Scilab code Exa 18.4 Analyze UJT circuit

```
1 //chapter 18
2 //example 18.4
3 //page 575
4 clear;
5 clc ;
6 //given
7 PD=360; //power dissipation in mW
8 RBBmin=4; //kohm
9 RBBmax=12; //kohm
10 //to get lowest value of VB1B2,use RBBmin
11 VB1B2max=sqrt(RBBmin*PD);
12 printf("\nFor 25 degree,value of VB1B2=%d V",ceil(
    VB1B2max));
13 VB2E=30; //maximum emitter reverse voltage
14 printf("\nAt 25 degree,VB1B2 should not exceed 30 V"
    )
15 //for operation till 100 degrees
16 deltaT=100-25;
17 PD1=PD-(2.4*deltaT);
18 //ignore increase in RB
19
20 VB1B2max=sqrt(RBBmin*PD1);
21 printf("\nupto 100 degree,value of VB1B2=%.1f V",
    VB1B2max);
```

---

#### Scilab code Exa 18.5 Emitter voltages for UJT circuit

```
1 //chapter 18
2 //example 18.5
```

```

3 //page 576
4 clear;
5 clc ;
6 //given
7 VB1B2=30;
8 etamin=0.55;
9 etamax=0.82; //efficiency
10 Vpmin=0.7+(etamin*30);
11 Vpmax=0.7+(etamax*30);
12 printf("\nDevice will fire at emitter voltage
    between %.1f V and %.1f V",Vpmin,Vpmax);

```

---

Scilab code Exa 18.6 Frequency of oscillation for UJT circuit

```

1 //chapter 18
2 //example 18.6
3 //page 578
4 clear ;
5 clc ;
6 //given
7 VB1B2=15;
8 eta=0.7; //intrinsic standoff ratio
9 ec=0.7+(eta*VB1B2); //capacitor voltage
10 VEB1sat=2.5; //saturation voltage when capacitor is
    discharged
11 Eo=2.5; //capacitor voltage at start of each charging
    cycle
12 t=0.1*10*log((15-2.5)/(15-11.2));
13 f=1000/t;
14 printf("\nTypical frequency of oscillation is
    approximately %d Hz",ceil(f))

```

---

Scilab code Exa 18.7 Emitter resistance for UJT circuit

```

1 //chapter 18
2 //example 18.7
3 //page 580
4 clear;
5 clc ;
6 //given
7 VB1B2=15;
8 Vd=0.7;
9 eta=0.82;//intrinsic standoff ratio
10 Ip=2;//maximum current
11 Vp=Vd+(eta*VB1B2);
12 REmax=(VB1B2-Vp)/Ip;
13 printf("\nREmax=%d Mohm",REmax);
14 VEBsat=2.5;
15 IV=2;//in mA
16 REmin=(VB1B2-VEBsat)/IV;
17 printf("\nREmin=%0.2 f kohm",REmin);

```

---

#### Scilab code Exa 18.8 DC Analysis UJT circuit

```

1 //chapter 18
2 //example 18.8
3 //page no 581
4 clc;
5 clear;
6 //given
7 eta=0.7;
8 Vbb=20;
9 VR1=eta*Vbb;
10 I1=2;//mA
11 R1=14/I1;
12 printf("\nR1=%d kohm, use standard value 6.8 kohm",R1
    );R1=6.8;
13 R2=(Vbb-14)/I1;
14 printf("\nR2=%d kohm, use standard value 2.7 kohm",R2

```

```

    );R2=2.7;
15 Rbb=R1+R2;
16 Vp=0.7+(Vbb*6.8)/Rbb;
17 Vv=1; //anode to cathode voltage drop
18 printf("\nVp=%d V",Vp);
19 printf("\nAnode to cathode voltage drop=%d V",Vv);

```

---

# Chapter 19

## Optoelectronic devices

Scilab code Exa 19.1 Light intensity

```
1 //chapter 19
2 //example 19.1
3 //page 590
4 clear all;
5 clc ;
6 //given
7 r=3; //distance from lamp in m
8 L=25; //luminous flux or light energy in W
9 E=100*L/(4*%pi*(r^2)); //light intensity
10 A=0.25; //area in cm^2
11 printf("\nLight intensity =%.1f microW/cm^2",E);
12 totphi=E*A;
13 printf("\nTotal Flux =%.1f microW",totphi);
```

---

Scilab code Exa 19.2 Series resistance and dark current

```
1 //chapter 19
2 //example 19.2
```

```

3 //page 597
4 clear all;
5 clc ;
6 //given
7 Vcc=30;//supply voltage
8 Is=10;//supply current
9 Rcell=1;//cell resistance
10 R1=Vcc/Is-Rcell;
11 Rdark=100;//cell dark resistance kohm
12 Idark=Vcc/(R1+Rdark);
13 printf("\nRequired series resistance is %d kohm \
        nLevel of Dark current is approximately %.1f mA",
        R1,Idark)

```

---

### Scilab code Exa 19.3 Design photoconductive cell circuit

```

1 //chapter 19
2 //example 19.3
3 //page 597
4 clear all;
5 clc ;
6 //given
7 Vcc=6;//supply voltage V
8 Ib=200;//base current when Xtor is ON microA
9 Rdark=100;//cell dark resistance kohm
10 //when Xtor is ON
11 Vcell=Vcc+0.7;//for Si Xtor
12 Icell=1000*Vcell/Rdark;//microA
13 //current through R1
14 IR1=Icell+Ib;
15 VR1=Vcc-0.7;
16 R1=1000*VR1/IR1;
17 //When Xtor is Off, base <=0V(Ib=0)
18 VR1=Vcc;
19 IR1=1000*VR1/R1;//microA

```



```

20 //since Ib=0
21 Icell=IR1;
22 Vcell=Vcc;
23 Rcell=1000*Vcell/Icell;
24 printf("\nR1=%d kohm\nCell resistance (Rcell)=%d kohm
      ",ceil(R1),ceil(Rcell));
25 printf("\nQ1 is OFF when Rcell<=20 kohm")

```

---

#### Scilab code Exa 19.4 Dc load line for photodiode

```

1 //chapter 19
2 //example 19.4
3 //page 600
4 clear all;
5 clc ;
6 //given
7 Es=0.5; //supply voltage V
8 R1=200; //series resistance ohm
9 VD1=-Es; //when Id=0
10 //when VD=0
11 VR1=Es;
12 ID1=1000*VR1/R1;
13 VD=[VD1 0];
14 ID=[0 ID1];
15 plot(VD,ID,'-.*');
16 xtitle('dc load line with points (-0.5,0) and (0,2.5)
      ','VD in V','ID in mA');
17 a=gca();
18 a.data_bounds=[-1,-0.5;1 3];
19 //from intersection of load line and illumination
      characteristics
20 printf('\nApproximate values:')
21 printf("\nAt 1500 lm/m^2, Id=-0.2 mA, Vd=-0.45 V");
22 printf("\nAt 10000 lm/m^2, Id=-1.9 mA, Vd=-0.12 V");
23 printf("\nAt 20000 lm/m^2, Id=-3.7 mA, Vd=0.22 V");

```

---

**Scilab code Exa 19.5** Total cells for satellite

```
1 //chapter 19
2 //example 19.5
3 //page 603
4 clear;
5 clc ;
6 //given
7 Vo=13;//op voltage
8 Vcell=0.45;//cell voltage
9 Icell=57;//cell current in mA
10 //no of series connected cell
11 Cs=ceil(Vo/Vcell);
12 //charge taken from batteries over 24hrs=charge
    delivered by cell
13 Q=24*0.5;//Ahr
14 //charging /op current
15 Io=Q/12;
16 //total group of cell in parallel
17 Cp=round(1000*Io/Icell);
18 //total no of cells required
19 C=Cs*Cp;
20 printf("\ntotal no of cells required is %d",C)
```

---

**Scilab code Exa 19.6** Output voltage of phototransistor circuit

```
1 //chapter 19
2 //example 19.6
3 //page 606
4 clear all;
5 clc ;
```

```

6 //given
7 Vcc=20;//supply voltage V
8 Rl=2;//collector load resistance kohm
9 Vce=[Vcc 0]
10 Ic=[0 Vcc/Rl]
11 plot(Vce,Ic,'-.*');
12 xtitle('dc load line with points (20,0)and (0,10)',,
        Vce in V','Ic in mA')
13 a=gca();
14 a.data_bounds=[-1,-0.5;21 11];
15 //from intersection of load line and illumination
    characteristics
16 printf("\nAt illumination level =0,output voltage=
        Vce= 20V")
17 printf("\nAt illumination level =20 mW/cm^2,output
        voltage= 12.5V")
18 printf("\nAt illumination level =40 mW/cm^2,output
        voltage= 4V")

```

---

#### Scilab code Exa 19.7 Design LED and transistor circuit

```

1 //chapter 19
2 //example 19.7
3 //page 611
4 clear all;
5 clc ;
6 //given
7 Vcc=9;//supply voltage V
8 Vi=7;//ip voltage
9 VD1=1.2;//V
10 VCEsat=0.2;//V
11 Ic=10;//collector current mA
12 R2=1000*(Vcc-VD1-VCEsat)/Ic;
13 printf("\nR2=%d ohm,use standard 680 ohm",R2);R2
    =680;

```

```
14 Ic=1000*(Vcc-VD1-VCEsat)/R2;
15 hfemin=100;
16 Ib=1000*Ic/hfemin;
17 R1=1000*(Vi-0.7)/Ib;
18 printf("\nR1=%d kohm, standard value",R1);
```

---

# Chapter 20

## Miscellaneous devices

Scilab code Exa 20.1 Capacitance tuning ratio

```
1 //chapter 20
2 //example 20.1
3 //page 636
4 clear all;
5 clc ;
6 //given
7 C1=150;C2=60//capacitance from abrupt junction
   device characteristics at 1,10V resp in pF
8 //capacitance tuning ratio for abrupt junction
   device
9 TR=C1/C2;
10 printf("\ncapacitance tuning ratio for abrupt
   junction device is %.1f ",TR)
11 C3=220;C4=15//capacitance from hyperabrupt junction
   device characteristics at 1,10V resp in pF
12 //capacitance tuning ratio for hyperabrupt junction
   device
13 TR=C3/C4;
14 printf("\ncapacitance tuning ratio for hyperabrupt
   junction device is %.1f ",TR)
```

---

### Scilab code Exa 20.2 Resonance frequency

```
1 //chapter 20
2 //example 20.2
3 //page 638
4 clear;
5 clc ;
6 //given
7 R1=4.7;R2=10;
8 Vcc=9;//supply voltage
9 L=100;//inductance microH
10 Vdmin=(Vcc*R1)/(R1+R2);
11 Vdmax=Vcc;
12 C1=100;C2=15//capacitance from hyperabrupt junction
    device characteristics at 2.9,9V resp in pF
13 //At resonance ,for Vdmin
14 f1=1000/(2*%pi*sqrt(L*C1));//MHz
15 f2=1000/(2*%pi*sqrt(L*C2));//MHz
16 printf("\n The resonance frequency range is %.1f MHz
    to %0.1f MHz",f1,f2)
```

---

### Scilab code Exa 20.3 Value of resistor in thermistor circuit

```
1 //chapter 20
2 //example 20.3
3 //page 640
4 clear all;
5 clc ;
6 //given
7 E=20;//supply voltage
8 I=1;//supply current mA
9 //without thermistor & R2
```

```

10 Rc1=5;Rc2=6.5; // coil resistance
11 //At -15degree
12 R1=(E/I)-Rc1;
13 //At 50degree
14 R11=(E/I)-Rc2;
15 printf('\nwithout thermistor & R2:')
16 printf("\nR1=%d kohm,R1=%0.1f kohm at -15 and 50
    degrees respectively",R1,R11);
17 //with thermistor
18 Rt1=3;Rt2=0.100; //thermistor resistance
19 //At -15degree
20 R1=(E/I)-Rt1-Rc1
21 //At 50degree
22 R11=(E/I)-Rt2-Rc2;
23 printf('\nwith thermistor:')
24 printf("\nR1=%d kohm,R1=%0.1f kohm at -15 and 50
    degrees respectively ",R1,R11);
25 //with thermistor & R2
26 //At -15degree
27 R1=(E/I)-(3/2)-Rc1
28 //At 50degree
29 R11=(E/I)-((3*0.1)/(3+0.1))-Rc2;
30 printf('\nwith thermistor & R2:')
31 printf("\nR1=%0.1f kohm,R1=%0.1f kohm at -15 and 50
    degrees respectively",R1,R11);

```

---

#### Scilab code Exa 20.4 Piecewise linear characteristics

```

1 //chapter 20
2 //example 20.4
3 //page 649
4 clear all;
5 clc ;
6 //given
7 Ip=1; //mA

```

```

8 Vp=65; //mV
9 Id=1; //mA
10 Vd=65; //mV
11 Iv=0.12; //mA
12 Vv=350; //mV
13 Vf=500; //mV
14 Id=[0 Id Iv Iv Ip]
15 Ed=[0 Vd Vv 450 Vf];
16 plot(Ed,Id,'-.*');
17 xtitle('piecewise linear characteristics','Ed in mV'
        , 'Id in mA');
18 Rd=-(350-65)/(1-0.12);
19 printf("\nValue of RD=%d ohm",round(Rd));

```

---

#### Scilab code Exa 20.5 Gain for tunnel diode circuit

```

1 //chapter 20
2 //example 20.5
3 //page 651
4 clear;
5 clc ;
6 //given
7 Eb=200; //battery voltage mV
8
9 es=0; //signal voltage V
10 Rl=80; //load resistance in ohm
11 Ed=Eb+es;
12 Id=2; //diode current mA
13 Er=(Eb+es);
14 Il1=Er/Rl; //load current mA
15 Ib1=Id+Il1; //battery current mA
16
17 es=100; //mV
18 Ed=Eb+es;
19 Id=1;

```



```

20 I12=Ed/R1;
21 Ib2=Id+I12;
22 deitaI1=I12-I11; //change in I1
23 deltaIb=Ib2-Ib1; //change in Ib
24
25 es=-100; //mV
26 Ed=Eb+es;
27 Id=3;
28 I13=Ed/R1;
29 Ib3=Id+I13;
30 deltaI1= I13 - I11; //change in I1
31 deltaIb=Ib3-Ib1; //change in Ib
32
33 //current gain
34 io=deltaI1;
35 is=deltaIb;
36 Ai=io/is;
37
38 //op voltage
39 deltaEr=es;
40 eo=deltaEr;
41
42 //voltage gain
43 Av=eo/es;
44
45 //power gain
46 Ap=Ai*Av;
47
48 printf("\ncurrent gain=%d\nvoltage gain=%d\npower
      gain=%d",Ai,Av,Ap)

```

---

# Chapter 21

## Electron tubes

Scilab code Exa 21.1 Transconductance and constant current characteristics

```
1 //chapter 21
2 //example 21.1
3 //page 665
4 clear all;
5 clc ;
6 //given
7 Eg=[0 -1 -2 -3 -4]; //V
8
9 Ep=75; //V
10 //drawing vertical line at Ep=75 V in Vacuum triode
    plate characteristics we get values of Ip for Eg
    values as
11 Ip=[20 10 2 1 0];
12
13 plot(Eg,Ip, '-.*');
14 xtitle('vacuum triode transconutance characteristics
    ')
15 xlabel('Eg in V');
16 ylabel('Ip in mA');
17
18
```

```

19 Ip=10; //mA
20 //drawing horizontal line at Ip=10 mA in Vacuum
    triode plate characteristics we get values of Ep
    for Eg as
21 Ep=[45 75 105 132 160];
22 figure,plot(Ep,Eg,'-.*');
23 xtitle('vacuum triode constant-current
    characteristics')
24 xlabel('Ep in V');
25 ylabel('Eg in V');

```

---

**Scilab code Exa 21.2** Impedance and gain for vacuum triode circuit

```

1 //chapter 21
2 //example 21.2
3 //page 672
4 clear;
5 clc ;
6 //given
7 Rg=1; //grid resistor in Mohm;
8 Rp=7; //plate resistor in kohm;
9 Rl=30; //load resistance in kohm
10 Vcc=175; //supply voltage in V
11 Vg=-2; //grid bias in V
12 Ep1=Vcc; Ip=0; Epp=Ep1;
13 Ep2=0; Ip2=Epp/Rp;
14 //dc load line with points A(175,0) and B(0,25),
    intersects Eg=-2V which gives
15 Ip=10; //
16 Ep=105;
17 //ip impedance
18 Zi=Rg;
19
20 //op impedance
21 rp=50/10; //deltaEp/deltaIp

```

```

22 Zo=(rp*Rp)/(rp+Rp);
23
24 //voltage gain
25 mu=50/2;
26 Av=-mu*((Rp*Rl)/(Rp+Rl))/(rp+((Rp*Rl)/(Rp+Rl)));
27
28 printf("\nip impedance=%dMohm",Zi);
29 printf("\nop impedance=%0.1 f kohm",Zo);
30 printf("\nvoltage gain=%0.1 f",Av);

```

---

### Scilab code Exa 21.3 DC load line for CC amplifier

```

1 //chapter 21
2 //example 21.3
3 //page 678
4 clear all;
5 clc ;
6 //given
7 Rp=9.7; //kohm
8 Rk=270; //ohm
9 Eg=[-4 -3 -2 -1];
10 Rl=47; //load resistance in kohm
11 Epp=200; //VE
12 //total dc load resistance
13 R=Rp+Rk;
14 Ip=-1000*Eg/Rk;
15
16 plot(-Eg,Ip, '-.*')
17 xtitle('bias line','Eg(V)','Ip(mA)')
18
19 //plotting DC load line
20 Ip1= floor(Epp/Rp);
21 //plot dc load line with points A(Ip,Ep)=A(0,200)
    and B(Ip1,Ep)=B(Ip1,0)
22 figure,plot([200 0],[0 Ip1], '*b—');

```

```

23 xtitle('Dc load line ', 'Ep(V) ', 'Ip(mA) ')
24
25 //after intersection of dc load line and bias line
    at Q
26 Eg=-2.4; Ip=8.8;
27 Ep=112; //plate to cathode voltage
28 printf("\\nFor Q point ,\\nEg=%0.1 f V\\nIp=%0.1 f mA\\nEp=
    %dV", Eg, Ip, Ep);
29 R=(Rp*Rl)/(Rp+Rl);
30 deltaIp=10;
31 deltaEp=-deltaIp*R;
32 //ac load line with points
33 //point C(deltaEp, deltaIp)=(32,10)
34 //point Q (112,8.8);
35 plot([32 112], [10 8.8], '*r—');
36 xtitle('dc(blue),ac(red) load line intersect at Q
    point ', 'Ep(V) ', 'Ip(mA) ')

```

---