

Scilab Textbook Companion for Electrical Network

by R. Singh¹

Created by
Mohammed Ishak
B.E, EXTC(pursuing)
Electronics Engineering
AIKTC, New Panvel, Navi Mumbai
College Teacher
Chaya Ravindra
Cross-Checked by
K. V. P. Pradeep

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Electrical Network

Author: R. Singh

Publisher: Tata McGraw-Hill, New Delhi

Edition: 1

Year: 2008

ISBN: 978-0-07-026096-2

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 basic circuit concept	5
2 Network Theorem 1	12
3 Network Theorem 2	35
4 AC Circuits	73
5 Steady State AC Analysis	94
6 Three phase Circuits	98
7 Graph Theory	111
8 Transient Analysis	120
10 Network Functions	122
11 Two Port Networks	124
12 Network Synthesis	136

List of Scilab Codes

Exa 1.1	example1	5
Exa 1.2	example2	5
Exa 1.3	example3	6
Exa 1.4	example4	7
Exa 1.5	example5	8
Exa 1.6	example6	8
Exa 1.7	example7	9
Exa 1.8	example8	9
Exa 1.12	example12	10
Exa 1.13	example13	10
Exa 1.14	example14	11
Exa 1.15	example15	11
Exa 2.1	example1	12
Exa 2.2	example2	12
Exa 2.3	example3	13
Exa 2.5	example5	14
Exa 2.8	example8	14
Exa 2.9	example9	15
Exa 2.10	example10	16
Exa 2.11	example11	16
Exa 2.12	example12	17
Exa 2.13	example13	18
Exa 2.14	example14	18
Exa 2.15	example15	19
Exa 2.17	example17	20
Exa 2.18	example18	20
Exa 2.19	example19	21
Exa 2.20	example20	22

Exa 2.21	example21	22
Exa 2.22	example22	23
Exa 2.24	example24	24
Exa 2.25	example25	25
Exa 2.26	example26	25
Exa 2.27	example27	26
Exa 2.28	example28	26
Exa 2.29	example29	27
Exa 2.30	example30	28
Exa 2.31	example31	28
Exa 2.32	example32	29
Exa 2.33	example33	30
Exa 2.34	example34	31
Exa 2.35	example35	31
Exa 2.37	example37	32
Exa 2.38	example38	32
Exa 2.39	example39	33
Exa 2.40	example40	34
Exa 3.1	example1	35
Exa 3.2	example2	35
Exa 3.3	example3	36
Exa 3.4	example4	37
Exa 3.5	example5	37
Exa 3.6	example6	38
Exa 3.7	example7	39
Exa 3.8	example8	39
Exa 3.9	example9	40
Exa 3.10	example10	41
Exa 3.11	example11	42
Exa 3.12	example12	42
Exa 3.13	example13	43
Exa 3.14	example14	44
Exa 3.15	example15	45
Exa 3.16	example16	46
Exa 3.17	example17	47
Exa 3.18	example18	48
Exa 3.19	example19	49
Exa 3.20	example20	50

Exa 3.21	example21	51
Exa 3.22	example22	51
Exa 3.23	example23	52
Exa 3.24	example24	53
Exa 3.25	example25	54
Exa 3.26	example26	55
Exa 3.27	example27	56
Exa 3.28	example28	57
Exa 3.29	example29	58
Exa 3.30	example30	59
Exa 3.31	example31	60
Exa 3.33	example33	61
Exa 3.41	example41	62
Exa 3.42	example42	63
Exa 3.43	example43	64
Exa 3.44	example44	65
Exa 3.45	example45	66
Exa 3.46	example46	67
Exa 3.47	example47	68
Exa 3.48	example48	68
Exa 3.49	example49	69
Exa 3.50	example50	70
Exa 3.51	example51	72
Exa 4.1	example1	73
Exa 4.2	example2	73
Exa 4.3	example3	74
Exa 4.4	example4	75
Exa 4.5	example5	75
Exa 4.14	example14	76
Exa 4.15	example15	76
Exa 4.33	example33	77
Exa 4.42	example42	77
Exa 4.47	example47	78
Exa 4.48	example48	79
Exa 4.49	example49	80
Exa 4.51	example51	81
Exa 4.52	example52	82
Exa 4.53	example53	83

Exa 4.54	example54	83
Exa 4.57	Series RLC circuit	84
Exa 4.58	Series RLC circuit	84
Exa 4.59	Series RLC circuit	85
Exa 4.60	Series RLC Circuit	85
Exa 4.79	Series Resonance	86
Exa 4.80	Series Resonance	87
Exa 4.81	Series Resonance	88
Exa 4.82	Series Resonance	89
Exa 4.83	Series Resonance	89
Exa 4.84	Series Resonance	90
Exa 4.85	Series Resonance	91
Exa 4.87	Series Resonance	91
Exa 4.88	Parallel Resonance	92
Exa 4.89	Parallel Resonance	92
Exa 5.1	example1	94
Exa 5.2	example2	95
Exa 5.11	example11	96
Exa 6.8	Interconnection of Three phases	98
Exa 6.9	Interconnection of Three phases	98
Exa 6.10	Interconnection of Three phases	99
Exa 6.11	Interconnection of Three phases	100
Exa 6.12	Interconnection of Three phases	101
Exa 6.13	Interconnection of Three phases	102
Exa 6.14	Interconnection of Three phases	103
Exa 6.17	Interconnection of Three phases	103
Exa 6.18	Interconnection of Three phases	104
Exa 6.19	Interconnection of Three phases	105
Exa 6.20	Interconnection of Three phases	106
Exa 6.27	Measurement of three phase power	107
Exa 6.28	Measurement of three phase power	108
Exa 6.29	Measurement of three phase power	108
Exa 6.30	Measurement of three phase power	109
Exa 6.31	Measurement of three phase power	109
Exa 7.7	Graph of a Network	111
Exa 7.8	Graph of a Network	112
Exa 7.11	Graph of a Network	112
Exa 7.14	Network Equilibrium Equation	113

Exa 7.15	Network Equilibrium Equation	114
Exa 7.19	Network Equilibrium Equation	115
Exa 7.20	Network Equilibrium Equation	116
Exa 7.21	Network Equilibrium Equation	117
Exa 8.13	example13	120
Exa 8.14	example14	121
Exa 10.35	Determination of Residue	122
Exa 10.36	Determination of Residue	122
Exa 11.16	Two Port Parameters	124
Exa 11.19	Interrelationships between parameters . . .	124
Exa 11.20	Interrelationships between parameters . . .	125
Exa 11.22	Interrelationships between parameters . . .	127
Exa 11.23	Interrelationships between parameters . . .	127
Exa 11.24	Interrelationships between parameters . . .	128
Exa 11.25	Interrelationships between parameters . . .	129
Exa 11.26	Interrelationships between parameters . . .	130
Exa 11.27	Interrelationships between parameters . . .	131
Exa 11.28	Interrelationships between parameters . . .	132
Exa 11.29	Interrelationships between parameters . . .	132
Exa 11.30	Interrelationships between parameters . . .	133
Exa 11.31	Interrelationships between parameters . . .	134
Exa 12.2	Hurwitz Polynomials	136
Exa 12.3	Hurwitz Polynomial	137
Exa 12.4	Hurwitz Polynomials	137
Exa 12.5	Hurwitz Polynomials	138
Exa 12.6	Hurwitz Polynomials	139
Exa 12.7	Hurwitz Polynomials	139
Exa 12.8	Hurwitz Polynomials	140
Exa 12.9	Hurwitz Polynomials	141
Exa 12.10	Hurwitz Polynomials	141

Chapter 1

basic circuit concept

Scilab code Exa 1.1 example1

```
1 //Basic Circuit Concepts
2 //page no-1.9
3 //example1.1
4 disp("Current through 15Ohm resistor is given by:");
5 disp("I1=30/15");
6 I1=30/15
7 printf("current through 15Ohm resistor = %.2f Ampere
", I1)
8 disp("Current through 5Ohm resistor is given by:")
9 disp("I2=5+2");
10 I2=5+2
11 printf("current through 5ohm resistor = %.2f Ampere"
, I2)
12 disp("R=100-30-5*I2/I1");
13 R=(100-30-5*I2)/I1
14 printf("R = %.2f Ohm", R);
```

Scilab code Exa 1.2 example2

```

1 //Basic Circuit Concepts
2 //page no-1.10
3 //example1.2
4 disp("from the given fig:")
5 disp("I2-I3=13");
6 disp("-20*I1+8*I2=0");
7 disp("-12*I1-16*I3=0");
8 //solving these equations in the matrix form
9 A=[0 1 -1;-20 8 0;-12 0 -16]
10 B=[13 0 0];
11 disp("A=")
12 disp(A)
13 disp("B=")
14 disp(B)
15 X=inv(A)*B
16 disp("X=")
17 disp(X)
18 disp("I1 = 4Ampere")
19 disp("I2 = 10Ampere")
20 disp("I3 = -3Ampere")

```

Scilab code Exa 1.3 example3

```

1 //Basic Circuit Concepts
2 //pg no-1.11
3 //example 1.3
4 disp("Iaf=x")
5 disp("Ifc=x-30")
6 disp("Ied=x+40")
7 disp("Idc=x-80")
8 disp("Icb=x-20")
9 disp("Iba=x-80")
10 disp("Applying KVL to the closed path AFEDCBA://")
     Applying KVL to the path AFEDCBA
11 disp("x=4.1/0.1")

```

```

12 x=4.1/0.1;
13 Iaf=x;
14 printf("\nIaf = %.2f Ampere", Iaf);
15 Ife=x-30
16 printf("\nIf e = %.2f Ampere", Ife);
17 Ied=x+40;
18 printf("\nIed = %.2f Ampere", Ied);
19 Idc=x-80;
20 printf("\nIdc = %.2f Ampere", Idc);
21 Icb=x-20;
22 printf("\nIcb = %.2f Ampere", Icb);
23 Iba=x-80;
24 printf("\nIba = %.2f Ampere", Iba);

```

Scilab code Exa 1.4 example4

```

1 //Basic Circuit Concepts
2 //pg no- 1.12
3 //example 1.4
4 disp("Applying KVL to the closed path OBAO");//  

      Applying KVL to the closed path OBAO
5 disp("3*x-3*y=2");
6 disp("Applying KVL to the closed path ABCA");//  

      Applying KVL to the closed path ABCA
7 disp("9*x+12*y=4");
8 a=[3 -3;9 12];
9 b=[2 4];
10 disp("a=");
11 disp(a)
12 disp("b=");
13 disp(b)
14 X=inv(a)*b;
15 disp(X)
16 disp("x=0.5714286 Ampere");
17 disp("y=-0.095238 Ampere");

```

```

18 disp("Ioa=0.57A")
19 disp("Iob=1-0.57")
20 Iob=1-0.57;
21 printf("\nIob = %2f A", Iob);
22 disp("Iab = 0.095");
23 Iac=0.57-0.095;
24 printf("\nIac = %2f A", Iac);
25 disp("Iab=1-0.57 + 0.095")
26 Iab=1-0.57 + 0.095;
27 printf("\nIob = %2f A", Iab)

```

Scilab code Exa 1.5 example5

```

1 //Basic Circuit Concepts
2 //pg no-1.12
3 //example 1.5
4 I1=2/5;
5 printf("I1=2/5= %2f Ampere", I1)
6 I2=4/8;
7 printf("\nI2=4/8= %2f Ampere", I2)
8 printf("\nPotential difference between points x and
y = Vxy = Vx-Vy")
9 printf("\nWriting KVL equations for the path x to y"
) //Writing KVL equation from x to y
10 printf("\nVs+3*I1+4-3*I2-Vy=0")
11 printf("\nVs+3*(0.4) + 4- 3*(0.5) -Vy = 0")
12 printf("\nVs+3*I1+4-3*I2-Vy = 0")
13 printf("\nVx-Vy = -3.7")
14 printf("\nVxy = -3.7V")

```

Scilab code Exa 1.6 example6

```
1 //Basic Circuit Concepts
```

```

2 //pg no-1.13
3 //example 1.6
4 I1=20/15;
5 printf("I1=2/5= %2f Ampere" , I1)
6 I2=15/10;
7 printf("\nI2=4/8= %2f Ampere" , I2)
8 disp("Voltage between points A and B = VAB = VA-VB")
;
9 disp("Writing KVL equations for the path A to B:");
//Writing KVL equations for the path A to B
10 disp("VA - 5*I1 - 5 - 15 + 6*I2 - VB = 0");
11 disp("VA - VB = 5*1.33 + 5 + 15 + 6*1.5");
12 VAB=(5*1.33)+5+15-(6*1.5);
13 printf("VAB = %.2 f Volt" , VAB)

```

Scilab code Exa 1.7 example7

```

1 //Basic Circuit Concepts
2 //page no-1.13
3 //example1.7
4 I1=5/2;
5 printf("I1=2/5= %2f Ampere" , I1)
6 I2=2;
7 printf("\nI2=4/8= %2f Ampere" , I2)
8 disp("Potential difference VAB = VA - VB");
9 disp("Writing KVL equations for path A to B") // 
    Writing KVL equations for path A to B
10 disp("VA - 2*I1 + 8 - 5*I2 - VB = 0");
11 disp("VA - VB = (2*2.5) - 8 5 + (5*2)");
12 VAB=(2*2.5)-8+(5*2)
13 printf("VAB = %.2 f Volt" , VAB);

```

Scilab code Exa 1.8 example8

```
1 //Basic Circuit Concepts
2 //page no-1.14
3 //example1.8
4 I1=10/8;
5 printf("I1=2/5= %2f Ampere" , I1)
6 I2=5;
7 printf("\nI2=4/8= %2f Ampere" , I2)
8 disp(" Applying KVL to the path from A to B") //
    Applying KVL to the path from A to B
9 disp("VA - 3*I1 - 8 + 3*I2 - VB = 0");
10 disp("VA - VB = 3*1.25 + 8 - 3*5")
11 VAB= (3*1.25)+8-(3*5);
12 printf("VAB = %.2 f Volt" , VAB);
```

Scilab code Exa 1.12 example12

```
1 //Basic Circuit Concepts
2 //page no-1.17
3 //example1.12
4 disp(" Applying KVL to the circuit :");
5 disp("50 - 5*I - 1.2*I - 16 = 0")
6 I=(50-16)/6.2;
7 printf("I= %.2 f Amp" , I);
8 P=50*I;
9 printf("\nPower delivered 50 V source = 50 * 5.48= %
    .2 f W" , P);
```

Scilab code Exa 1.13 example13

```
1 //Basic Circuit Concepts
2 //page no-1.18
3 //example1.13
4 disp("By Current Division formula ;");
```

```
5 I4=4*(2/(2+4));
6 printf("I4 = 4 * (2/(2+4)) = %.2f Amp", I4);
```

Scilab code Exa 1.14 example14

```
1 //Basic Circuit Concepts
2 //page no-1.19
3 //example1.14
4 disp("Applying KVL to the mesh");
5 disp("15 - 50*I - 50*I - 5*I");
6 I=15/105;
7 printf("I=15/105 = %.2f Amp", I);
8 V=15-(50*0.143);
9 printf("\nVoltage at node 2 = 15 - 50*I = %.2f Volt"
, V);
```

Scilab code Exa 1.15 example15

```
1 //Basic Circuit Concepts
2 //pg no.-1.20
3 //example 1.15
4 r1=3;
5 r2=2.33;
6 r3=6;
7 v1=18;
8 v2=5.985;
9 mprintf("\nApplying KCL at the node , \n(Va-18)/3+(Va
-5.985)/2.33+Va/6 = 0");
10 Va=((v1*r2*r3)+(v2*r1*r3))/((r2*r3)+(r1*r3)+(r1*r2))
;
11 printf("\nSolving the equation ,we get , \nVa = %.2f V
", Va);
```

Chapter 2

Network Theorem 1

Scilab code Exa 2.1 example1

```
1 //Network Theorem-1
2 //pg no.-2.4
3 //example2.1
4 printf("\nConverting the two delta networks formed
       by resistors 4.5 Ohm, 3Ohm, and 7.5Ohm into
       equivalent star networks");
5 a=4.5;
6 b=3;
7 c=7.5;
8 R1= (a*c)/(a+b+c);
9 R2= (c*b)/(c+b+a);
10 R3= (a*b)/(a+b+c);
11 mprintf("\nR1=R6 = %.2 f Ohm \nR2=R5 = %.1 f Ohm \nR3=
           R4 = %.1 f Ohm",R1,R2,R3);
```

Scilab code Exa 2.2 example2

```
1 //Network Theorem-1
```

```

2 //pg no.-2.2
3 //example2.5
4 //converting delta network to star network
5 a=10;
6 b=10;
7 c=10;
8 R=(a*b)/(a+b+c);
9 printf("\nConverting the delta formed by three
      resistors of 10 Ohm into an equivalent star
      network");
10 mprintf("\nR1=R2=R3= %.3f Ohm",R);

```

Scilab code Exa 2.3 example3

```

1 //Network Theorem-1
2 //pg no.-2.7
3 //example2.3
4 a=4;
5 b=3;
6 c=6;
7 //star to delta conversion
8 R1=c+a+((a*c)/b);
9 R2=c+b+((c*b)/a);
10 R3=a+b+((a*b)/c);
11 x=1.35;
12 y=0.9;
13 RAB=(c*(x+y))/(c+x+y);
14 printf("\nR1 = %.f Ohm",R1);
15 printf("\nR2 = %.1f Ohm",R2);
16 printf("\nR3 = %.f Ohm",R3);
17 printf("\nThe network can be simplified as , \nRAB =
      %.2f Ohm",RAB);

```

Scilab code Exa 2.5 example5

```
1 //Network Theorem-1
2 //pg no.-2.9
3 //example2.5
4 //converting delta network to star network
5 a=25;
6 b=20;
7 c=35;
8 R1=(b*c)/(a+b+c);
9 R2=(a*b)/(a+b+c);
10 R3=(a*c)/(a+b+c);
11 printf("\nConverting the delta formed by resistors
20 Ohm ,25 Ohm, 35 Ohm into an equivalent star
network");
12 printf("\nR1= %.2 f Ohm" ,R1);
13 printf("\nR2= %.2 f Ohm" ,R2);
14 printf("\nR3= %.2 f Ohm" ,R3);
```

Scilab code Exa 2.8 example8

```
1 //Network Theorem-1
2 //pg no.-2.15
3 //example2.8
4 a=5;
5 b=4;
6 c=3;
7 //Star to delta conversion
8 R1=a+b+((a*b)/c);
9 R2=c+b+((c*b)/a);
10 R3=a+c+((a*c)/b);
11 a1=6;
12 b1=4;
13 c1=8;
14 //Satr to delta conversion
```

```

15 R4=a1+b1+((a1*b1)/c1);
16 R5=c1+b1+((c1*b1)/a1);
17 R6=a1+c1+((a1*c1)/b1);
18 x=6.17;
19 y=9.78;
20 RAB=(x*y)/(x+y);
21 printf("\nConverting star network formed by 3 Ohm,4
          Ohm ,5 Ohm into equivalent delta network ");
22 mprintf("\nR1= %.2f Ohm \nR2= %.1f Ohm \nR3 = %.2f
          Ohm",R1,R2,R3);
23 printf("\nSimilarly , converting star network formed
          by 6 Ohm,4 Ohm ,8 Ohm into equivalent delta
          network");
24 mprintf("\nR4= %.f Ohm \nR5= %.2f Ohm \nR6 = %.f Ohm
          ",R4,R5,R6);
25 printf("\n Simplifying the parallel networks , we get
          \nRAB = %.2f Ohms",RAB);

```

Scilab code Exa 2.9 example9

```

1 //Network Theorem 1
2 //page no-2.18
3 //example2.9
4 disp(" Applying KVL to mesh 1");
5 disp(" 10*I1-3*I2-6*I3=0");.... //equation 1
6 disp(" Applying KVL to mesh 2");
7 disp(" -3*I1+10*I2=-5");.... //equation 2
8 disp(" Applying KVL to mesh 3");
9 disp(" -6*I1+10*I3=25");.... //equation 3
10 disp(" Solving the three equations");
11 A=[10 -3 -6;-3 10 0;-6 0 10] //solving the equations
      in matrix form
12 B=[10 -5 25];
13 X=inv(A)*B;
14 disp(X);

```

```
15 disp("I1=4.27 A");
16 disp("I2=0.78 A");
17 disp("I3=5.06 A");
18 disp("I5ohm=4.27 A");
```

Scilab code Exa 2.10 example10

```
1 //Network Theorem 1
2 //page no-2.19
3 //example 2.10
4 disp("Applying KVL to mesh 1");
5 disp("7*I1-I2=10");....//equation 1
6 disp("Applying KVL to mesh 2");
7 disp("-I1+6*I2-3*I3=0");....//equation 2
8 disp("Applying KVL to mesh 3");
9 disp("-3*I2+13*I3=-20");....//equation 3
10 disp("Solving the three equations");
11 A=[7 -1 0;-1 6 -3;0 -3 13];//solving the equations
    in matrix form
12 B=[10 0 -20]',
13 X=inv(A)*B;
14 disp(X);
15 disp("I1=1.34 A");
16 disp("I1=-0.62 A");
17 disp("I3=-1.68 A");
18 disp("I2ohm=1.34 A");
```

Scilab code Exa 2.11 example11

```
1 //Network Theorem 1
2 //page no-2.20
3 //example 2.11
4 disp("Applying KVL to mesh 1");
```

```

5 disp("3*I1-I2-2*I3=8");.... //equation 1
6 disp(" Applying KVL to mesh 2");
7 disp("-I1+8*I2-3*I3=10");.... //equation 2
8 disp(" Applying KVL to mesh 3");
9 disp("-2*I1-3*I2+10*I3=12");.... //equation 3
10 disp(" Solving the three equations");
11 A=[3 -1 -2;-1 8 -3;-2 -3 10]; //solving the equations
    in matrix form
12 B=[8 10 12] '
13 X=inv(A)*B;
14 disp(X);
15 disp(" I1=6.01 A");
16 disp(" I1=3.27 A");
17 disp(" I3=3.38 A");
18 disp(" I5ohm=3.38 A");

```

Scilab code Exa 2.12 example12

```

1 //Network Theorem 1
2 //page no-2.21
3 //example 2.12
4 disp(" Applying KVL to mesh 1");
5 disp("8*I1-I2-4*I3=4");.... //equation 1
6 disp(" Applying KVL to mesh 2");
7 disp("-I1+8*I2-5*I3=0");.... //equation 2
8 disp(" Applying KVL to mesh 3");
9 disp("-4*I1-5*I2+15*I3=0");.... //equation 3
10 disp(" Solving the three equations");
11 A=[8 -1 -4;-1 8 -5;-4 -5 15]; //solving the equations
    in matrix form
12 B=[4 0 0] '
13 X=inv(A)*B;
14 disp(X);
15 disp(" I1=0.66");
16 disp(" I1=0.24 A");

```

```
17 disp("I3=0.26 A");
18 disp(" current supplied by the battery = 0.66 A");
```

Scilab code Exa 2.13 example13

```
1 //Network Theorem 1
2 //page no-2.22
3 //example 2.13
4 disp("Applying KVL to mesh 1");
5 disp("V+13*I1-2*I2-5*I3=20");...//mesh equation 1
6 disp("Applying KVL to mesh 2");
7 disp("2*I1-6*I2+I3=0");//mesh equation 2
8 disp("Applying KVL to mesh 3");
9 disp("V+5*I1+I2-10*I3=0");//mesh equation 3
10 disp(" putting I1=0 in equation 1, 2 and 3 we get");
11 disp("V-2*I2-5*I3=20");....//equation 1
12 disp("-6*I2+I3=0");....//equation 2
13 disp("V+I2-10*I3=0");....//equation 3
14 disp("Solving the three equations");
15 A=[1 -2 -5;0 -6 1;1 1 -10];//solving the equations
   in matrix form
16 B=[20 0 0]';
17 X=inv(A)*B;
18 disp(X);
19 disp("V=43.7 V")
```

Scilab code Exa 2.14 example14

```
1 //Network Theorem 1
2 //page no-2.13
3 //example2.14
4 disp("Mesh 1 contains a current source of 6A.Hence,
   we cannot write KVL equation for Mesh 1.direction
```

```

        of current source and mesh current I1 are same ,"
);
5 disp("I1=6A");....//equation 1
6 disp("Applying KVL to mesh 2");
7 disp("18*I2-6*I3=108");....//equation 2
8 disp("Applying KVL to mesh 3");
9 disp("6*I2-11*I3=9");....//equation 3
10 disp("Solving the three equations");
11 A=[18 -6;6 -11];...//solving the equations in matrix
    form
12 B=[108 9];
13 X=inv(A)*B;
14 disp(X);
15 disp("I3 = 3A");
16 disp("I2ohm = 3A");

```

Scilab code Exa 2.15 example15

```

1 //Network Theorem 1
2 //page no-2.23
3 //example2.15
4 disp("from the fig ,");
5 disp("IA=I1");....//equation 1
6 disp("IB=I2");....//equation 2
7 disp("Applying Kvl to mesh 1:");
8 disp("5-5*I1-10*IB-10*(I1-I2)-5*IA=0");
9 disp("5-5*I1-10*I2-10*I1+10*I2-5*I1=0");
10 disp("-20*I1=-5");
11 I1=5/20;
12 printf("I1= %.2 f A", I1);....//equation 3
13 disp("Applying Kvl to mesh 2:");
14 disp("15*I1-15*I2=10");....//equation 4
15 disp("Put I1=0.25 A in equation 4");
16 disp("-6.25=15*I2");
17 I2=-6.25/15;

```

```
18 printf("I2= %.2f A", I2);
```

Scilab code Exa 2.17 example17

```
1 //Network Theorem 1
2 //page no-2.25
3 //example2.17
4 disp("from the fig,");
5 disp("V1=-5*I1");....//equation 1
6 disp("V2=2*I2");....//equation 2
7 disp("Applying Kvl to mesh 1:");
8 disp("20*I1+3*I2=-5");....//equation 3
9 disp("Applying Kvl to mesh 2:");
10 disp("11*I1-3*I2=10");...//equation 4
11 disp("Solving equations 3 and 4");...//solving
    equations in matrix form
12 A=[20 3;11 -3];
13 B=[-5 10]';
14 X=inv(A)*B;
15 disp(X);
16 disp("I1=0.161 A");
17 disp("I2=-2.742 A");
```

Scilab code Exa 2.18 example18

```
1 //Network Theorem-1
2 //pg no.-2.25
3 //example2.18
4 disp("from the fig,");
5 disp("Iy=I1");....//equation 1
6 disp("Ix=I1-I2");....//equation 2
7 disp("Applying Kvl to mesh 1:");
8 disp("-10*I1+3*I2=5");....//equation 3
```

```

9 disp(" Applying Kvl to mesh 2:");
10 disp("-I1-3*I2=10");... //equation 4
11 disp(" Solving equations 3 and 4");... //solving
    equations in matrix form
12 A=[-10 3;-1 -3];
13 B=[5 10]';
14 X=inv(A)*B;
15 disp(X);
16 disp(" I1=-1.364 A");
17 disp(" I2=-2878 A");
18 x=-1.364;
19 y=-2.878;
20 Ix=x-y;
21 mprintf("\nIy = %.3f A \nIx = %.3f A",x,Ix);

```

Scilab code Exa 2.19 example19

```

1 //Network Theorem 1
2 //page no-2.26
3 //example2.19
4 disp(" Applying KVL to mesh 1:");
5 disp(" 11*I1-10*I2=2");... //equation 1
6 disp(" Writing current equation to supermesh:")
7 disp(" I3-I2=4");... //equation 2
8 disp(" Applying KVL to outer path of supermesh:");
9 disp(" 2*I1-3*I2-3*I3=0");... //equation 3
10 disp(" solving these equations we get :");... //
    solving equations in matrix form
11 A=[11 -10 0;0 -1 1;2 -3 -3];
12 B=[2 4 0]';
13 X=inv(A)*B;
14 disp(X);
15 I1=-2.35
16 I2=-2.78
17 I3=1.22

```

```
18 I4=I1-I2;
19 printf("\n current through the 10 ohm resistor = I1-
    I2 = %.2f A", I4);
```

Scilab code Exa 2.20 example20

```
1 //Network Theorem 1
2 //page no-2.26
3 //example2.20
4 disp(" writing equation for supermesh ,");
5 disp(" I1-I3=7");....//equation 1
6 disp(" Applying Kvl to the outer path of the
    supermesh :");
7 disp("-I1+4*I2-4*I3 = -7");....//equation 2
8 disp(" Applying Kvl to mesh 2: ");
9 disp(" I1-6*I2+3*I3 = 0");...//equation 3
10 disp(" Solving equations 1 ,2 and 3");...//solving
    equations in matrix form
11 A=[1 0 -1;-1 4 -4;1 -6 3];
12 B=[7 -7 0]';
13 X=inv(A)*B;
14 disp(X);
15 disp(" I1=9 A");
16 disp(" I2=-2.5 A");
17 disp(" I3=-2 A");
18 x=2.5;
19 y=2;
20 z=x-y;
21 mprintf("\nCurrent through the 3-Ohm resistor = I2-
    I3 =%.1f A",z);
```

Scilab code Exa 2.21 example21

```

1 //Network Theorem 1
2 //page no-2.27
3 //example2.21
4 disp(" Applying KVL to mesh 1:");
5 disp(" 15*I1 -10*I2 -5*I3=50");....//equation 1
6 disp(" Writing current equation to supermesh:");
7 disp(" I2-I3=2 A");....//equation 2
8 disp(" Applying KVL to outer path of supermesh:");
9 disp(" -15*I1+12*I2+6*I3=0");....//equation 3
10 disp(" solving these equations we get :");...//  

     solving equations in matrix form
11 A=[15 -10 -5;0 1 -1;-15 12 6];
12 B=[50 2 0]';
13 X=inv(A)*B;
14 disp(X);
15 I1=20
16 I2=17.33
17 I3=15.33
18 I4=I1-I3;
19 printf("\ncurrent through the 5 ohm resistor = I1-I3  

      = %.2f A", I4);

```

Scilab code Exa 2.22 example22

```

1 //Network Theorem 1
2 //page no-2.28
3 //example2.22
4 disp(" from the fig ,");
5 disp(" I4=40");....//equation 1
6 disp("\nmeshes 2 and 3 form a supermesh. current  

     equation for supermesh ,")
7 disp("-I1+2*I2-I3 = 0");....//equation 2
8 disp(" Applying Kvl to supermesh:");
9 disp(" -1/5(I2-I1)-1/20*I2-1/15*I3-1/2(I3-I4)=0")  

      ;....//equation 3

```

```

10 disp(" applying KVL to mesh 1");
11 disp("-1/10*I1-1/5(I1-I2)-1/6(I1-I4)=6");... // 
    equation 4
12 disp(" Solving equations 1 ,2 ,3 and 4");... // solving
    equations in matrix form
13 A=[0 0 0 1;-1 2 -1 0;0.2 -0.25 -17/30 0.5;-7/15 0.2
    0 1/6];
14 B=[40 0 0 6]';
15 X=inv(A)*B;
16 disp(X);
17 disp(" I1=10 A");
18 disp(" I2=-20 A");
19 disp(" I3=30 A");
20 disp(" I4=40 A");

```

Scilab code Exa 2.24 example24

```

1 //Network Theorem 1
2 //page no-2.29
3 //example2.24
4 disp(" Applying KCL to node 1:");
5 disp(" 2*V1-V2 = 2");... //equation 1
6 disp(" Applying KCL to node 2:");
7 disp(" 3*V2-V1 = 4");... //equation 2
8 disp(" Solving equations 1 and 2");... //solving
    equations in matrix form
9 A=[2 -1;-1 3];
10 B=[2 4]';
11 X=inv(A)*B;
12 disp(X);
13 disp("V1= 2 V");
14 disp("V2=-2 V");

```

Scilab code Exa 2.25 example25

```
1 //Network Theorem 1
2 //page no-2.30
3 //example2.25
4 disp("Applying KCL to node 1:");
5 disp("8*VA-2*VB = 50");....//equation 1
6 disp("Applying KCL to node 2:");
7 disp("-3*VA+9*VB = 85");...//equation 2
8 disp("Solving equations 1 and 2");...//solving
    equations in matrix form
9 A=[8 -2;-3 9];
10 B=[50 85]';
11 X=inv(A)*B;
12 disp(X);
13 disp("VA= 9.39 V");
14 disp("VB= 12.58 V");
```

Scilab code Exa 2.26 example26

```
1 //Network Theorem 1
2 //page no-2.30
3 //example2.26
4 disp("Applying KCL to node 1:");
5 disp("5*V1-2*V2 = -24");....//equation 1
6 disp("Applying KCL to node 2:");
7 disp("10*V1-31*V2+6*V3 = 300");...//equation 2
8 disp("Applying KCL to node 3:");
9 disp("-4*V2 +9*V3 = 160");...//equation 3
10 disp("Solving equations 1,2 and 3");...//solving
    equations in matrix form
11 A=[5 -2 0;10 -31 6;0 -4 9];
12 B=[-24 300 160]';
13 X=inv(A)*B;
14 disp(X);
```

```

15 disp("V1= -8.77 V");
16 disp("V2= -9.92 V");
17 disp("V3= 13.37 V");
18 x=13.37;
19 y=-9.92;
20 z=(x-y)/5;
21 printf("\n current through the 5 ohm resistor = V3-V2
      /5 = %.2f A",z);

```

Scilab code Exa 2.27 example27

```

1 //Network Theorem 1
2 //page no-2.31
3 //example2.27
4 disp(" Applying KCL to node 1:");
5 disp(" 50*V1-20*V2 = 2400");...//equation 1
6 disp(" Applying KCL to node 2:");
7 disp(" -10*V1+19*V2 = 240");...//equation 2
8 disp(" Solving equations 1 and 2");...//solving
    equations in matrix form
9 A=[50 -20;-10 19];
10 B=[2400 240]';
11 X=inv(A)*B;
12 disp(X);
13 disp("V1= 67.2 V");
14 disp("V2=-48 V");

```

Scilab code Exa 2.28 example28

```

1 //Network Theorem 1
2 //page no-2.32
3 //example2.28
4 disp(" Applying KCL to node 1");

```

```

5 disp("4*VA-2*VB = 5");....//equation 1
6 disp(" Applying KCL to node 2:");
7 disp("-2*VA+3*VB = 4");...//equation 2
8 disp("Solving equations 1 and 2");...//solving
    equations in matrix form
9 A=[4 -2;-2 3];
10 B=[5 4]';
11 X=inv(A)*B;
12 disp(X);
13 disp("VA= 2.88 V");
14 disp("VB= 3.25 V");

```

Scilab code Exa 2.29 example29

```

1 //Network Theorem 1
2 //page no-2.33
3 //example2.29
4 disp(" Applying KCL to node 1:");
5 disp("4*V1-2*V2-V3 = -24");....//equation 1
6 disp(" Applying KCL to node 2:");
7 disp("-50*V1+71*V2-20*V3 = 0");...//equation 2
8 disp(" Applying KCL to node 3:");
9 disp("-5V1-4*V2 +10*V3 = 180");...//equation 3
10 disp("Solving equations 1,2 and 3");...//solving
    equations in matrix form
11 A=[4 -2 -1;-50 71 -20;-5 -4 10];
12 B=[-24 0 180]';
13 X=inv(A)*B;
14 disp(X);
15 disp("V1= 6.35 V");
16 disp("V2= 11.76 V");
17 disp("V3= 25.88 V");
18 x=25.88;
19 y=11.76;
20 z=(x-y);

```

```
21 printf("\ncurrent through the 5 ohm resistor = V3-V2  
/5 = %.2f A",z);
```

Scilab code Exa 2.30 example30

```
1 //Network Theorem 1  
2 //page no-2.34  
3 //example2.30  
4 disp("Applying KCL to node 1:");  
5 disp("8*V1-V2 = 50");....//equation 1  
6 disp("Applying KCL to node 2:");  
7 disp("-2*V1+11*V2 = -500");....//equation 2  
8 disp("Solving equations 1 and 2");....//solving  
equations in matrix form  
9 A=[8 -1;-2 17];  
10 B=[50 -500]';  
11 X=inv(A)*B;  
12 disp(X);  
13 disp("V1= 2.61 V");  
14 disp("V2=-29.1 V");  
15 x=2.61;  
16 y=-29.1;  
17 I1=-x/2;  
18 I2=(x-y)/10;//current through 10 Ohm resistor  
19 I3=(y+50)/2;//50 volts is the supply to the circuit  
20 mprintf("\nI1= %.2f A \nI2= %.2f A \nI3= %.2f A",I1,  
I2,I3);
```

Scilab code Exa 2.31 example31

```
1 //Network Theorem 1  
2 //page no-2.34  
3 //example2.30
```

```

4 disp(" Applying KCL to node a:");
5 disp(" 0.5*Va-0.2*Vb = 34.2");... //equation 1
6 disp(" Applying KCL to node b:");
7 disp(" 0.1*Va-0.4*Vb = -32.4");... //equation 2
8 disp(" Solving equations 1 and 2");... //solving
    equations in matrix form
9 A=[0.5 -0.2;0.1 -0.4];
10 B=[34.2 -32.4]';
11 X=inv(A)*B;
12 disp(X);
13 disp("Va= 112 V");
14 disp("Vb= 109 V");
15 x=112;
16 y=109;
17 I1=(120-x)/0.2;
18 I2=(x-y)/0.3;
19 I3=(110-y)/0.1;
20 mprintf("\nI1= %.f \nI2= %.f \nI3= %.f",I1,I2,
    I3);

```

Scilab code Exa 2.32 example32

```

1 //Network Theorem 1
2 //page no-2.35
3 //example2.35
4 disp(" Applying KCL to node 1:");
5 disp("V1 = 50");... //equation 1
6 disp(" Applying KCL to node 2:");
7 disp("-2*V1+17*V2 = 50");... //equation 2
8 disp(" Solving equations 1 and 2");... //solving
    equations in matrix form
9 A=[1 0;-2 17];
10 B=[50 50]';
11 X=inv(A)*B;
12 disp(X);

```

```

13 disp("V1= 50 V");
14 disp("V2= 8.82 V");
15 x=8.82;
16 y=(x/10);
17 printf("\ncurrent in the 10-Ohm resistor =V2/10 =%.2
f A",y);

```

Scilab code Exa 2.33 example33

```

1 //Network Theorem 1
2 //page no-2.36
3 //example2.33
4 disp(" Applying KCL to node a:");
5 disp(" 6*Va-5*Vb = -20");....//equation 1
6 disp(" Applying KCL to node b:");
7 disp(" -10*Va+17*Vb-5*Vc = 0");...//equation 2
8 disp("At node c");
9 disp("Vc = 20");
10 disp("Solving equations 1,2 and 3");...//solving
    equations in matrix form
11 A=[6 -5 0;-10 17 -5;0 0 1];
12 B=[-20 0 20]';
13 X=inv(A)*B;
14 disp(X);
15 disp("Va= 3.08 V");
16 disp("Vb= 7.69 V");
17 x=3.08;
18 y=7.69;
19 z=20;
20 Va = x-y;
21 Vb = y-z;
22 mprintf("\nV1 = Va-Vb =%.2 f V \nV2 = Vb-Vc =%.2 f V",
Va ,Vb);

```

Scilab code Exa 2.34 example34

```
1 //Network Theorem 1
2 //page no-2.37
3 //example2.334
4 disp("At node A:");
5 disp("VA = 60");....//equation 1
6 disp("Applying KCL to node B:");
7 disp("-VA+3*VB-VC = 12");....//equation 2
8 disp("Applying KCL to node C:");
9 disp("-2*VA-5*VB+10*VC");....//equation 3
10 disp("Solving equations 1,2 and 3");...//solving
    equations in matrix
11 A=[1 0 0;-1 3 -1;-2 -5 10];
12 B=[60 12 24],
13 X=inv(A)*B;
14 disp(X);
15 disp("VC= 31.68 V");
16 disp("Voltage across the 100 Ohm resistor = 31.68 V"
);
```

Scilab code Exa 2.35 example35

```
1 //Network Theorem 1
2 //page no-2.38
3 //example2.35
4 disp("Applying KCL to node 1:");
5 disp("2.5*V1-0.5*V2 = 5");....//equation 1
6 disp("Applying KCL to node 2:");
7 disp("V1-V2 = 0");....//equation 2
8 disp("Solving equations 1 and 2");...//solving
    equations in matrix form
```

```
9 A=[2.5 -0.5;1 -1];
10 B=[5 0]';
11 X=inv(A)*B;
12 disp(X);
13 disp("V1= 2.5 V");
14 disp("V2=-2.5 V");
```

Scilab code Exa 2.37 example37

```
1 //Network Theorem 1
2 //page no-2.39
3 //example2.37
4 disp(" Applying KCL to node 1:");
5 disp("2*V1+17*V2 = 0");....//equation 1
6 disp(" Applying KCL to node 2:");
7 disp("V1+6V2 = 0");....//equation 2
8 disp(" Solving equations 1 and 2");...//solving
    equations in matrix form
9 A=[2 17;1 6];
10 B=[0 0]';
11 X=inv(A)*B;
12 disp(X);
13 disp("V1= 0 V");
14 disp("V2= 0 V");
```

Scilab code Exa 2.38 example38

```
1 //Network Theorem 1
2 //page no-2.40
3 //example2.38
4 disp(" Applying KCL to node a:");
5 disp("2*Va-0.5*Vb-0.5*Vc = 5");....//equation 1
6 disp(" Applying KCL to node b");
```

```

7 disp(" -3/2*Va+5/6*Vb+2/3*Vc = -1");... //equation 2
8 disp(" Applying KCL to node c:");
9 disp(" 1/2*Va+1/3*Vb-31/30*Vc = -1");... //equation 3
10 disp(" Solving equations 1,2 and 3");... //solving
    equations in matrix form
11 A=[2 -0.5 -0.5;-3/2 5/6 2/3;0.5 1/3 -31/30];
12 B=[5 -1 0]';
13 X=inv(A)*B;
14 disp(X);
15 disp("Va= 4.303 V");
16 disp("Vb= 3.87 V");
17 disp("Vc= 3.33 V");

```

Scilab code Exa 2.39 example39

```

1 //Network Theorem 1
2 //page no-2.41
3 //example2.39
4 disp("from the figure");
5 disp("V4= 40 V"); //equation 1
6 disp("nodes 2 and 3 form suoernode:");
7 disp("V1-2*V2+V3 = 0");... //equation 2
8 disp("Applying KCL to node 1:");
9 disp("7/15*V1-1/5*V2 = 2/3");... //equation 3
10 disp("Applying KCL to supernode :");
11 disp("-23/30*V1 +83/60*V3 = 20");... //equation 4
12 disp("Solving equations 1,2,3 and 4");... //solving
    equations in matrix form
13 A=[0 0 0 1;1 -2 1 0;7/15 -1/5 0 0;-23/30 83/60 0 0];
14 B=[40 0 2/3 20]';
15 X=inv(A)*B;
16 disp(X);
17 disp("V1= 10 V");
18 disp("V2= 20 V");
19 disp("V3= 30 V");

```

Scilab code Exa 2.40 example40

```
1 //Network Theorem 1
2 //page no-2.42
3 //example2.40
4 disp("selecting central node as reference node");
5 disp("V1= -12 V"); //equation 1
6 disp("Applying KCL at node 1:");
7 disp("-2*V1+2.5*V2-0.5V3 = 14");.... //equation 2
8 disp("nodes 3 and 4 form a supernode");
9 disp("0.2*V1+V3-1.2*V4 = 0");... //equation 3
10 disp("Applying KCL to supernode :");
11 disp("0.1*V1-V2+0.5*V3+1.4*V4 = 0");... //equation 4
12 disp("Solving equations 1,2,3 and 4");... //solving
    equations in matrix form
13 A=[1 0 0 0;-2 2.5 -0.5 0;0.2 0 1 -1.2;0.1 -1 0.5
    1.4];
14 B=[-12 14 0 0] ;
15 X=inv(A)*B;
16 disp(X);
17 disp("V1= -12 V");
18 disp("V2= -4 V");
19 disp("V3= 0");
20 disp("V4= -2 V");
```

Chapter 3

Network Theorem 2

Scilab code Exa 3.1 example1

```
1 //Network Theorem 2
2 //pg no 3.2
3 //example 3.1
4 disp("When 10-V source is acting alone:");
5 disp("By current-division formula :");
6 I1=10*(0.87/(10+0.87));
7 printf("I1=10*(0.87/(10+0.87))= %.2f A (down)" , I1);
8 disp("When 4 A source is acting alone:");
9 disp("By current-division formula :");
10 I2=2.86*(0.875/(10+0.875));
11 printf("I2=2.86*(0.875/(10+0.875))= %.2f A (down)" ,
12 I2);
12 disp("By superposition theorem:");
13 I=I1+I2;
14 printf("\nI=I1+I2=0.8+0.23= %.2f A (down)" , I);
```

Scilab code Exa 3.2 example2

```

1 //Network Theorem 2
2 //pg no 3.4
3 //example 3.2
4 disp("When 4-A source is acting alone:");
5 disp("By current-division formula :");
6 I1=3.33*(3.53/(6+3.53));
7 printf("I1=3.33*(3.53/(6+3.53)) = %.2f A (down)", I1
);
8 disp("When 10-V source is acting alone:");
9 disp("By current-division formula :");
10 I2=0.833*(3.53/(6+3.53));
11 printf("I2=0.833*(3.53/(6+3.53))= %.2f A (up)", I2);
12 disp("When 3-A source is acting alone:");
13 disp("By current-division formula :");
14 I3=3*(3.53/(6+3.53));
15 printf("I3=3*(3.53/(6+3.53))= %.2f A (down)", I3);
16 disp("By superposition theorem:");
17 I=I1-I2+I3;
18 printf("\nI=I1-I2+I3=1.23-0.31+1.11= %.2f A (down)", I);

```

Scilab code Exa 3.3 example3

```

1 //Network Theorem 2
2 //pg no 3.5
3 //example 3.3
4 disp("When 4-A source is acting alone:");
5 disp("By current-division formula :");
6 I1=4/(2+1);
7 printf("I1=4/(2+1) = %.2f A (down)", I1);
8 disp("When 3-A source is acting alone:");
9 disp("By current-division formula :");
10 I2=3*(2/(2+1));
11 printf("I2=3*(2/(2+1)) = %.2f A (down)", I2);
12 disp("When 1-A source is acting alone:");

```

```

13 disp("By current-division formula :");
14 I3=1*(2/(2+1));
15 printf("I3=1*(2/(2+1)) = %.2f A (down)" , I3);
16 disp("By superposition theorem:");
17 I=I1+I2+I3;
18 printf("\nI=I1+I2+I3=1.33+2+0.66= %.2f A (down)" , I)
;
```

Scilab code Exa 3.4 example4

```

1 //Network Theorem 2
2 //pg no 3.
3 //example 3.4
4 disp("When 6-V source is acting alone:");
5 VAB1=6;
6 printf("VAB1 = %.2f V" , VAB1);
7 disp("When 10-V source is acting alone:");
8 disp("Since the resistor of 5 ohm is shorted ,the
      voltage across it is zero")
9 VAB2=10;
10 printf("VAB2= %.2f V" , VAB2);
11 disp("When 5-A source is acting alone:");
12 disp("Due to short circuit in both the parts");
13 VAB3=0;
14 printf("VAB3 = %.2f V" , VAB3);
15 disp("By superposition theorem:");
16 VAB=VAB1+VAB2+VAB3;
17 printf("\nVAB=VAB=VAB1+VAB2+VAB3= %.2f V" , VAB);
```

Scilab code Exa 3.5 example5

```

1 //Network Theorem 2
2 //pg no 3.7
```

```

3 //example 3.5
4 disp("When 5-A source is acting alone:");
5 disp("By current-division formula :");
6 I1=5*(2/(2+4));
7 printf("I1=5*(2/(2+4)) = %.2f A (down)", I1);
8 disp("When 2-A source is acting alone:");
9 disp("By current-division formula :");
10 I2=2*(2/(2+4));
11 printf("I2=2*(2/(2+4)) = %.2f A (down)", I2);
12 disp("When 6-V source is acting alone:");
13 disp("Applying KVL to the mesh");
14 disp("-2*I3-6-4*I3=0");
15 disp("I3=-1");
16 I3=-1;
17 printf("I3=-1 A= %.2f A (down)", I3);
18 disp("By superposition theorem:");
19 I=I1+I2+I3;
20 printf("\nI=I1+I2+I3=1.67+0.67-1= %.2f A (down)", I)
;
```

Scilab code Exa 3.6 example6

```

1 //Network Theorem 2
2 //pg no 3.8
3 //example 3.6
4 a=15/38;
5 b=10/38;
6 x=a+b;
7 mprintf("\nApplying KCL at node 1, \nI1 = %.3f",a);
    //When the 15 V source is acting alone
8 mprintf("\nApplying KCL at node 1, \nI1 = %.3f",b);
    //When the 10 V source is acting alone
9 mprintf("\nBy superposition theorem, \nI = I1+I2 = %
.3 f A",x);
```

Scilab code Exa 3.7 example7

```
1 //Network Theorem 2
2 //pg no 3.8
3 //example 3.7
4 a=3;
5 b=2;
6 x=a+b;
7 mprintf("\napplying KCL at node 1, \nIx1 = %.f A",a)
    ;//when the 30 V source is acting alone
8 mprintf("\napplying KCL at the mesh, \nIx2 = %.f A",
    b); //when the 20 V source is acting alone
9 mprintf("\nBy superposition theorem, Ix = Ix1+Ix2 =
    %.f A",x);
```

Scilab code Exa 3.8 example8

```
1 //Network Theorem 2
2 //pg no 3.10
3 //example 3.8
4 //when 5 V source is acting alone
5 disp("Vx+10I1=5"); //equation 1
6 disp("Applying KVL to mesh,");
7 disp("4Vx+12I1=5"); //equation 2
8 A=[1 10;4 12]; //solving equation in matrix form
9 B=[5 5];
10 X=inv(A)*B;
11 disp(X);
12 disp("I1 = 0.535 A");
13 //when the 2 A source is acting alone
14 disp("Vx+10I2=0"); //equation 1
15 disp("Applying KCL at Node x,");
```

```

16 disp("Vx=-10/7"); //equation 2
17 A=[1 10;1 0]; //solving equation in matrix form
18 B=[0 -10/7]';
19 X=inv(A)*B;
20 disp(X);
21 disp("I2 = 0.1428 A");
22 a=0.535;
23 b=0.1428;
24 x=a+b;
25 printf("\nBy superposition theorem , \nI = I1+I2 = %
.3f A ",x);

```

Scilab code Exa 3.9 example9

```

1 //Network Theorem 2
2 //pg no 3.10
3 //example 3.9
4 //when 100 V source is acting alone
5 disp("Vx-5I1=0"); //equation 1
6 disp("Applying KVL to mesh ,");
7 disp("10Vx-15I1=-100"); //equation 2
8 A=[1 -5;10 -15]; //solving equation in matrix form
9 B=[0 -100]';
10 X=inv(A)*B;
11 disp(X); //negative because of opposite direction
12 disp("I1 = 2.857 A");
13 //when the 10 A source is acting alone
14 disp("9Vx+10I2=0"); //equation 1
15 disp("Applying KCL at Node 1,");
16 disp("Vx=-100/7"); //equation 2
17 A=[9 10;1 0]; //solving equation in matrix form
18 B=[0 -100/7]';
19 X=inv(A)*B;
20 disp(X);
21 disp("I2 = 12.857 A");

```

```
22 a=2.857;
23 b=12.857;
24 x=a+b;
25 printf("\nBy superposition theorem , \nI = I1+I2 = %
.3f A ",x);
```

Scilab code Exa 3.10 example10

```
1 //Network Theorem 2
2 //pg no 3.11
3 //example 3.10
4 //when 17 V source is acting alone
5 disp("Vx+2I1=0"); //equation 1
6 disp(" Applying KVL to mesh ,");
7 disp("-5Vx-5I1=17"); //equation 2
8 A=[1 2;-5 -5]; //solving equation in matrix form
9 B=[0 17]';
10 X=inv(A)*B;
11 disp(X);
12 disp(" I1 = 3.4 A");
13 //when the 1 A source is acting alone
14 disp("4Vx+3I2=0"); //equation 1
15 disp(" Applying KCL at Node x ,");
16 disp("Vx=-6/5"); //equation 2
17 A=[4 3;1 0]; //solving equation in matrix form
18 B=[0 -6/5]';
19 X=inv(A)*B;
20 disp(X);
21 disp(" I2 = 1.6 A");
22 a=3.4;
23 b=1.6;
24 x=a+b;
25 printf("\nBy superposition theorem , \nI = I1+I2 = %
.3f A ",x);
```

Scilab code Exa 3.11 example11

```
1 //Network Theorem 2
2 //pg no 3.12
3 //example 3.11
4 //when 5 A source is acting alone
5 disp(" -V1+4I=0"); //equation 1
6 disp(" Applying KCL to node 1,");
7 disp(" 1.25V1-4I=5"); //equation 2
8 A=[-1 4;1.25 -4]; //solving equation in matrix form
9 B=[0 5];
10 X=inv(A)*B;
11 disp(X);
12 disp(" V1 = 20 V");
13 //when the 20 V source is acting alone
14 disp(" from the figure,");
15 disp(" V2-3I=0"); //equation 1
16 disp(" Applying KVL to the mesh,");
17 disp(" I=-20"); //equation 2
18 A=[1 -3;0 1]; //solving equation in matrix form
19 B=[0 -20];
20 X=inv(A)*B;
21 disp(X);
22 disp(" V2 = -60 V");
23 a=20;
24 b=-60;
25 x=a+b;
26 mprintf("\nBy superposition theorem, \n V = V1+V2 =
    %.f V ",x);
```

Scilab code Exa 3.12 example12

```

1 //Network Theorem 2
2 //pg no 3.13
3 //example 3.12
4 //when 18 V source is acting alone
5 disp("Vx+I1=0"); //equation 1
6 disp("Applying KVL to mesh ,");
7 disp("3Vx-6I1=-18"); //equation 2
8 A=[1 1;3 -6]; //solving equation in matrix form
9 B=[0 -18];
10 X=inv(A)*B;
11 disp(X);
12 disp("I1 = 2 A");
13 //when the 3 A source is acting alone
14 disp("from the figure ,");
15 disp("Vx=2 V"); //equation 1
16 disp("Applying KCL at node 1,");
17 disp("3Vx-6I2=0"); //equation 2
18 A=[1 0;3 -6]; //solving equation in matrix form
19 B=[2 0];
20 X=inv(A)*B;
21 disp(X);
22 disp("I2 =1 V");
23 a=2;
24 b=1;
25 x=a+b;
26 mprintf("\nBy superposition theorem , \n I = I1+I2 =
%.f A ",x);

```

Scilab code Exa 3.13 example13

```

1 //Network Theorem 2
2 //pg no 3.14
3 //example 3.13
4 //when 120 V source is acting alone
5 disp("Applying KVL to mesh ,");

```

```

6 disp("Iy1=5.45 A");
7 //when the 12 A source is acting alone
8 disp("from the figure ,");
9 disp("V1+4Iy2=0"); //equation 1
10 disp("Applying KCL at node 1,");
11 disp("-V1/8 +9/4Iy2=-12"); //equation 2
12 A=[1 4;-1/8 9/4]; //solving equation in matrix form
13 B=[0 -12];
14 X=inv(A)*B;
15 disp(X);
16 disp("Iy2 =-4.36 A");
17 //when 40 V source is acting alone
18 disp("Applying KVL to mesh ,");
19 disp("Iy3=-1.82 A");
20 a=5.45;
21 b=-4.36;
22 c=-1.82;
23 x=a+b+c;
24 mprintf("\nBy superposition theorem , \n I = Iy1+Iy2+
           Iy3 = %.2f A ",x);

```

Scilab code Exa 3.14 example14

```

1 //Network Theorem 2
2 //pg no 3.15
3 //example 3.14
4 //when 18 V source is acting alone
5 disp("Vx1-31=0"); //equation 1
6 disp("Applying KVL to mesh ,");
7 disp("-3Vx1-9I=-18"); //equation 2
8 A=[1 -3;-3 -9]; //solving equation in matrix form
9 B=[0 -18];
10 X=inv(A)*B;
11 disp(X);
12 disp("Vx1 = 3 V");

```

```

13 //when the 5 A source is acting alone
14 disp("from the figure ,");
15 disp("V1+Vx2=0"); //equation 1
16 disp("Applying KCL at node 1 ,");
17 disp("1/2V1-1/2Vx2=5"); //equation 2
18 A=[1 1/2 -1/2]; //solving equation in matrix form
19 B=[0 5];
20 X=inv(A)*B;
21 disp(X);
22 disp("Vx2= -5 V");
23 //when the 36 V source is acting alone
24 disp("from the figure ,");
25 disp("Vx3+3I=0"); //equation 1
26 disp("Applying KVL to the mesh ,");
27 disp("3Vx3-9I=-36"); //equation 2
28 A=[1 3;3 -9]; //solving equation in matrix form
29 B=[0 -36];
30 X=inv(A)*B;
31 disp(X);
32 disp("Vx3= -6 V");
33 a=3;
34 b=-5;
35 c=-6;
36 x=a+b+c;
37 mprintf("\nBy superposition theorem , \n Vx = Vx1+Vx2
+Vx3 = %.f V ",x);

```

Scilab code Exa 3.15 example15

```

1 //Network Theorem 2
2 //pg no 3.16
3 //example 3.15
4 a=10;
5 b=2;
6 c=(5*a)-(20*b);

```

```

7 x=20;
8 y=30;
9 z=5;
10 r=z+((x*y)/(x+y));
11 i=c/(r+c);
12 // Calculation of Vth(Thevenin's voltage)
13 disp("removing the 10 ohm resistor from the circuit"
);
14 printf("\nFor mesh 1, \nI1 = %.f A",a);
15 printf("\nApplying KVL to mesh 2,, \nI2 = %.f A",b);
16 printf("\nWriting Vth equation, \n Vth = %.f V",c);
17 // Calculation of Rth(Thevenin's Resistance)
18 disp("replacing the current source of 10 A with an
open circuit and voltage source of 100 V with a
short circuit,");
19 printf("\nRth = %.f Ohm",r);
20 // Calculation of IL(load current)
21 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.16 example16

```

1 //Network Theorem 2
2 //pg no 3.17
3 //example 3.16
4 a=30;
5 b=20;
6 c=50;
7 d=5;
8 e=24;
9 v=220;
10 x=(v/(a+c));
11 y=(v/(b+d));
12 z=(20*y)-(30*x);
13 r=((a*c)/(a+c))+((b*d)/(b+d));
14 i=z/(r+e);

```

```

15 // Calculation the Vth (Thevenin's voltage)
16 disp("removing the 24 Ohm resistor from the network"
      );
17 printf("\nI1 = %.2f A",x);
18 printf("\nI2 = %.1f A",y);
19 printf("\nWriting Vth equation , \n Vth = %.1f V",z);
20 // Calculation of Rth (Thevenin's resistance)
21 disp("replacing the 220 V source with short circuit"
      );
22 printf("\nRth = %.2f Ohm",r);
23 // Calculation of IL (load current)
24 printf("\nIL = %.f A",i);

```

Scilab code Exa 3.17 example17

```

1 //Network Theorem 2
2 //pg no 3.18
3 //example 3.17
4 disp("removing the 3 Ohm resistor from the network")
      ;
5 disp("Applying KVL to mesh 1");
6 disp("11*I1-9*I2=50");....//equation 1
7 disp("Applying KVL to mesh 2");
8 disp("-9*I1+18*I2=0");....//equation 2
9 A=[11 -9;-9 18];//solving the equations in matrix
      form
10 B=[50 0];
11 X=inv(A)*B;
12 disp(X);
13 disp("I1=7.69 A");
14 disp("I2=3.85 A");
15 //Calculation of Vth (Thevenin's voltage)
16 a=7.69;
17 b=3.85;
18 v=-((5*b)+(8*(b-a))); //the B terminal is positive w.

```

```

    r.t A
19 printf("\nWriting Vth equation , \n Vth = %.1f V",v);
20 //Calculation of Rth (Thevenin's resistance)
21 x=4;
22 y=2;
23 z=5;
24 //delta into star network
25 r1=((x*y)/(x+y+z));
26 r2=((x*z)/(x+y+z));
27 r3=((z*y)/(x+y+z));
28 mprintf("\nR1 = %.2f Ohm \nR2 = %.2f Ohm \nR3 = %.2f
    Ohm",r1,r2,r3);
29 m=1.73;
30 n=8.91;
31 r=(r2+(m*n)/(m+n));
32 printf("\nRth = %.2f Ohm",r);
33 //Claculation of IL (Load Current)
34 i=v/(r+3);
35 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.18 example18

```

1 //Network Theorem 2
2 //pg no 3.21
3 //example 3.18
4 disp("removing the 20 Ohm resistor from the network"
    );
5 disp("Applying KVL to mesh 1");
6 disp("30*I1-15*I2=-75");....//equation 1
7 disp("Applying KVL to mesh 2");
8 disp("-15*I1+20*I2=20");....//equation 2
9 A=[30 -15;-15 20];//solving the equations in matrix
    form
10 B=[-75 20];
11 X=inv(A)*B;

```

```

12 disp(X);
13 disp("I1=-3.2 A");
14 disp("I2=-1.4 A");
15 //Calculation of Vth (Thevenin's voltage)
16 a=-3.2;
17 b=-1.4;
18 v=45;
19 v1=45-10*(a-b);
20 printf("\nWriting Vth equation , \n Vth = %.f V",v1);
21 //Calculation of Rth (Thevenin's resistance)
22 x=10;
23 y=5;
24 z=5;
25 //delta into star network
26 r1=((x*y)/(x+y+z));
27 r2=((x*z)/(x+y+z));
28 r3=((z*y)/(x+y+z));
29 mprintf("\nR1 = %.1 f Ohm \nR2 = %.1 f Ohm \nR3 = %.1 f
          Ohm",r1,r2,r3);
30 m=16.25;
31 r=((m*r1)/(m+r1))+r1;
32 printf("\nRth = %.2 f Ohm",r);
33 //Claculation of IL (Load Current)
34 i=v1/(r+20);
35 printf("\nIL = %.2 f A",i);

```

Scilab code Exa 3.19 example19

```

1 //Network Theorem 2
2 //pg no 3.22
3 //example 3.19
4 disp("removing the 3 Ohm resistor from the network")
      ;
5 disp("Applying KVL to mesh 1");
6 disp("I1=6");....//equation 1

```

```

7 disp(" Applying KVL to mesh 2");
8 disp("-12*I1+18*I2=42");....//equation 2
9 A=[1 0;-12 18]; //solving the equations in matrix
form
10 B=[6 42];
11 X=inv(A)*B;
12 disp(X);
13 disp(" I2= 6.33 A");
14 //Calculation of Vth (Thevenin's voltage)
15 a=6.33;
16 v=6*a;
17 printf("\nWriting Vth equation , \n Vth = %.f V",v);
18 //Calculation of Rth (Thevenin's resistance)
19 disp("replacing the voltage source with short
circuit and current source by open circuit");
20 x=6;
21 y=12;
22 r=(x*y)/(x+y);
23 printf("\nRth = %.f Ohm",r);
24 //Calculation of IL (load current)
25 i=v/(r+3);
26 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.20 example20

```

1 //Network Theorem 2
2 //pg no 3.23
3 //example 3.20
4 disp("removing the 30 Ohm resistor from the network"
);
5 disp(" Applying KVL to supermesh ");
6 disp("-I1+I2=13");....//equation 1
7 disp(" 15*I1+100*I2=150");....//equation 2
8 //Calculation of Vth (Thevenin's voltage)
9 a=3;

```

```

10 v=(40*a)-50;
11 printf("\nWriting Vth equation , \n Vth = %.f V",v);
12 //Calculation of Rth (Thevenin's resistance)
13 disp("replacing the voltage source with short
      circuit and current source by open circuit");
14 r=(75*40)/(75+40);
15 printf("\nRth = %.2f Ohm",r);
16 //Calculation of IL (load current)
17 i=v/(r+30);
18 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.21 example21

```

1 //Network Theorem 2
2 //pg no 3.25
3 //example 3.21
4 //Calculation of Vth
5 v=100;
6 r=20;
7 x=v/r;
8 disp("Removing the 20 Ohm resistor from the network"
      );
9 printf("\nVth = %.f V ",v);
10 //calculation of Rth
11 disp("replacing the voltage source with short
      circuit and current source by open circuit");
12 disp("Rth = 0");
13 //calculation of IL
14 printf("\nIL = %.f A",x);

```

Scilab code Exa 3.22 example22

```
1 //Network Theorem 2
```

```

2 //pg no 3.25
3 //example 3.22
4 disp("removing the 10 Ohm resistor from the network"
      );
5 disp("Applying KVL to mesh 1");
6 disp("4*I1-I2=-25");....//equation 1
7 disp("Applying KVL to mesh 2");
8 disp("-I1+4*I2=10");....//equation 2
9 A=[4 -1;-1 4];//solving the equations in matrix form
10 B=[-25 10]';
11 X=inv(A)*B;
12 disp(X);
13 disp("I1=-6 A");
14 disp("I2=1 A");
15 //Calculation of Vth (Thevenin's voltage)
16 a=-6;
17 b=1;
18 v=-((2*a)+(2*b));//the terminal B is positive w.r.t
      A
19 printf("\nWriting Vth equation , \n Vth = %.f V",v);
20 //Calculation of Rth (Thevenin's resistance)
21 x=2;
22 y=2;
23 z=1;
24 //star into delta network
25 r1=x+y+((x*y)/z);
26 r2=x+z+((x*z)/y);
27 r3=z+y+((z*y)/x);
28 fprintf("\nR1 = %.f Ohm \nR2 = %.f Ohm \nR3 = %.f
      Ohm",r1,r2,r3);
29 //Claculation of IL (Load Current)
30 r=1.33;
31 i=v/(r+v);
32 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.23 example23

```
1 //Network Theorem 2
2 //pg no 3.28
3 //example 3.23
4 disp("removing the 1 Ohm resistor from the network")
      ;
5 disp("writing current equation for meshes 1 & 2 ");
6 disp("I1= -3 A");....//equation 1
7 disp("I2=1 A");....//equation 2
8 //Calculation of Vth (Thevenin's voltage)
9 a=-3;
10 b=1;
11 r=2;
12 v=4-2*(a-b);
13 printf("\nWriting Vth equation , \n Vth = %.f V",v);
14 //Calculation of Rth (Thevenin's resistance)
15 disp("replacing the voltage source with short
      circuit and current source by open circuit");
16 disp("Rth = 2 Ohm");
17 //Calculation of IL (load current)
18 i=v/(r+1);
19 printf("\nIL = %.f A",i);
```

Scilab code Exa 3.24 example24

```
1 //Network Theorem 1
2 //page no-3.29
3 //example3.24
4 //calculation of Isc (short-circuit current)
5 disp("Applying KVL to mesh 1:");
6 disp("I1=2");....//equation 1
7 disp("Writing current equation to supermesh://
      meshes 2 & 3 will form a supermesh
8 disp("I3-I2=4");....//equation 2
```

```

9 disp(" Applying KVL to supermesh:");
10 disp("-5I2-15I3=0");....//equation 3
11 disp(" solving these equations we get :");...//
    solving equations in matrix form
12 A=[1 0 0;0 -1 1;0 -5 -15];
13 B=[2 4 0]';
14 X=inv(A)*B;
15 disp(X);
16 disp(" I1 = 2 A");
17 disp(" I2 = -3 A");
18 disp(" I3 = 1 A");
19 a=2;
20 b=-3;
21 x=a-b;
22 printf("\nIsc = %.f A",x);
23 //calculation of Rn (norton's resistance)
24 disp(" replacing the voltage source with short
    circuit and current source by open circuit");
25 c=1;
26 m=15;
27 y=(c*(m+x))/(c+m+x);
28 printf("\nRn = %.2 f Ohm",y);
29 //calculation of IL (load current)
30 z=10;
31 i=x*(y/(z+y));
32 printf("\nIL = %.2 f A",i);

```

Scilab code Exa 3.25 example25

```

1 //Network Theorem 1
2 //page no-3.30
3 //example3.25
4 //calculation of Isc (short-circuit current)
5 disp(" Applying KVL to mesh 1:");
6 disp(" 7*I1-2*I2=20");....//equation 1

```

```

7 disp(" Applying KVL to mesh 2,");
8 disp("-2*I1+10*I2=-12");....//equation 2
9 disp(" solving these equations we get :");...//
    solving equations in matrix form
10 A=[7 -2;-2 10];
11 B=[20 -12];
12 X=inv(A)*B;
13 disp(X);
14 disp(" I2 = -0.67 A");
15 a=-0.67;
16 printf("\nIsc = I2 = %.2f A",a);
17 //calculation of Rn (norton's resistance)
18 disp(" replacing the voltage source with short
    circuit ");
19 b=5;
20 c=2;
21 d=8;
22 y=((b*c)/(b+c))+d;
23 printf("\nRn = %.2f Ohm",y);
24 //calculation of IL (load current)
25 z=10;
26 i=-a*(y/(10+y));
27 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.26 example26

```

1 //Network Theorem 1
2 //page no-3.31
3 //example3.26
4 //calculation of Isc (short-circuit current)
5 disp(" Applying KVL to mesh 1:");
6 disp(" 7*I1-I2=10");....//equation 1
7 disp(" Applying KVL to mesh 2:");
8 disp("-I1+6*I2-3*I3=0");....//equation 2
9 disp(" Applying KVL to mesh 3:");

```

```

10 disp("3*I2 -3*I3=20");....//equation 3
11 disp(" solving these equations we get :");...//
    solving equations in matrix form
12 A=[7 -1 0;-1 6 -3;0 3 -3];
13 B=[10 0 20]';
14 X=inv(A)*B;
15 disp(X);
16 disp("I1 = -13.17 A");
17 a=13.17;
18 printf("\nIsc = %.2f A",a);
19 //calculation of Rn (norton's resistance)
20 disp("replacing the voltage source with short
    circuit ");
21 c=1;
22 b=6;
23 x=(c*b)/(c+b);
24 y=x+2;
25 z=(y*3)/(y+3);
26 printf("\nRn = %.2f Ohm",z);
27 //calculation of IL (load current)
28 n=10;
29 i=a*(z/(z+n));
30 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.27 example27

```

1 //Network Theorem 1
2 //page no-3.32
3 //example3.27
4 //calculation of Isc (short-circuit current)
5 disp(" Applying KVL to mesh 1:");
6 disp(" 20*I1 -20*I2=10");....//equation 1
7 disp(" Applying KVL to mesh 2:");
8 disp(" -20*I1 +60*I2 -20*I3=40");....//equation 2
9 disp(" Applying KVL to mesh 3:");

```

```

10 disp(" -20*I2+50*I3=-100");.... //equation 3
11 disp(" solving these equations we get :");... //
    solving equations in matrix form
12 A=[20 -20 0;-20 60 -20;0 -20 50];
13 B=[10 40 -100]';
14 X=inv(A)*B;
15 disp(X);
16 disp(" I1 = 0.81A");
17 a=0.81;
18 printf("\nIsc = %.2f A",a);
19 //calculation of Rn (norton's resistance)
20 disp(" replacing the voltage source with short
    circuit ");
21 c=20;
22 b=30;
23 x=(c*b)/(c+b);
24 y=x+c;
25 z=(y*c)/(y+c);
26 printf("\nRn = %.1f Ohm",z);
27 //calculation of IL (load current)
28 n=10;
29 i=a*(z/(z+n));
30 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.28 example28

```

1 //Network Theorem 1
2 //page no-3.33
3 //example3.28
4 //calculation of Isc (short-circuit current)
5 disp(" Applying KVL to mesh 1:");
6 disp(" 90*I1-60*I2=120");.... //equation 1
7 disp(" Applying KVL to mesh 2:");
8 disp(" -60*I1+100*I2-30*I3=40");.... //equation 2
9 disp(" Applying KVL to mesh 3:");

```

```

10 disp("30*I2 -30*I3=-10");....//equation 3
11 disp(" solving these equations we get :");...//
    solving equations in matrix form
12 A=[90 -60 0;-60 100 -30;0 30 -30];
13 B=[120 40 -10]';
14 X=inv(A)*B;
15 disp(X);
16 disp(" I3 = 4.67A");
17 a=4.67;
18 printf("\nIsc = %.2f A",a);
19 //calculation of Rn (norton's resistance)
20 disp(" replacing the voltage source with short
    circuit ");
21 c=30;
22 b=60;
23 x=(c*b)/(c+b);
24 y=x+10;
25 z=(y*c)/(y+c);
26 printf("\nRn = %.f Ohm",z);

```

Scilab code Exa 3.29 example29

```

1 //Network Theorem 1
2 //page no-3.34
3 //example3.29
4 //calculation of Isc (short-circuit current)
5 disp("Writing current equation for supermesh :");
6 disp("I2-I1=2");....//equation 1
7 disp(" Applying KVL to supermesh ,");
8 disp("12*I1= 55");....//equation 2
9 disp(" solving these equations we get :");...//
    solving equations in matrix form
10 A=[-1 1;12 0];
11 B=[2 55]';
12 X=inv(A)*B;

```

```

13 disp(X);
14 disp("I1 = 4.58 A");
15 disp("I2 = 6.58 A");
16 a=6.58;
17 printf("\nIsc = I2 = %.2f A",a);
18 //calculation of Rn (norton's resistance)
19 disp("replacing the voltage source with short
      circuit and current source with open circuit ");
20 b=12;
21 c=4;
22 y=((b*c)/(b+c));
23 printf("\nRn = %.f Ohm",y);
24 //calculation of IL (load current)
25 z=8;
26 i=a*(y/(z+y));
27 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.30 example30

```

1 //Network Theorem 1
2 //page no-3.35
3 //example3.30
4 //calculation of Isc (short-circuit current)
5 disp("Applying KVL to mesh 1:");
6 disp("5*I1-2*I2=-2");....//equation 1
7 disp("Applying KVL to mesh 2:");
8 disp("4*I2-2*I3=-1");....//equation 2
9 disp("Applying KVL to mesh 3:");
10 disp("-2*I1-2*I2+4*I3=0");....//equation 3
11 disp("solving these equations we get :");...//
      solving equations in matrix form
12 A=[5 -2 0;0 4 -2 ;-2 -2 4];
13 B=[-2 -1 0];
14 X=inv(A)*B;
15 disp(X);

```

```

16 disp("I1 = -0.64A");
17 disp("I2 = -0.55A");
18 disp("I3 = -0.59A");
19 a=-0.64;
20 b=-0.55;
21 c=-0.59;
22 printf("\nIsc = I3 = %.2f A",a);
23 //calculation of Rn (norton's resistance)
24 disp("replacing the voltage source with short
circuit");
25 z=2.2;
26 printf("\nRn = %.1f Ohm",z);
27 //calculation of IL (load current)
28 n=1;
29 i=-c*(z/(z+n));
30 printf("\nIL = %.2f A",i);

```

Scilab code Exa 3.31 example31

```

1 //Network Theorem 1
2 //page no-3.39
3 //example3.31
4 //calculation of Vth (Thevenin's voltage)
5 a=0.25;
6 v=(10*a)+(8*a);
7 disp("Writing Vth equation ,");
8 printf("\nVth = %.f V",v);
9 //calculation of Isc (short-circuit current)
10 disp("Applying KVL to mesh 1:");
11 disp("4*I1-2*I2 = 1");....//equation 1
12 disp("Applying KVL to mesh 2:");
13 disp("-18*I1-11*I2=0");....//equation 2
14 A=[4 -2;18 -11];
15 B=[1 0]';
16 X=inv(A)*B;

```

```

17 disp(X);
18 disp("I2 = 2.25 A");
19 a=2.25;
20 printf("\nIsc = I2 = %.2f A",a);
21 //Calculation of Rth
22 x=v/a;
23 printf("\nRth = %.f Ohm",x);

```

Scilab code Exa 3.33 example33

```

1 //Network Theorem 1
2 //page no-3.39
3 //example3.33
4 //calculation of Vth (Thevenin's voltage)
5 a=0.25;
6 v=(10*a)+(8*a);
7 disp("Writing Vth equation ,");
8 printf("\nVth = %.f V",v);
9 //calculation of Isc (short-circuit current)
10 disp("Applying KVL to mesh 1:");
11 disp("4*I1-2*I2 = 1");....//equation 1
12 disp("Applying KVL to mesh 2:");
13 disp("-18*I1-11*I2=0");....//equation 2
14 A=[4 -2;18 -11];
15 B=[1 0];
16 X=inv(A)*B;
17 disp(X);
18 disp("I2 = 2.25 A");
19 a=2.25;
20 printf("\nIsc = I2 = %.2f A",a);
21 //Calculation of Rth
22 x=v/a;
23 printf("\nRth = %.f Ohm",x);

```

Scilab code Exa 3.41 example41

```
1 //Network Theorem 1
2 //page no-3.47
3 //example3.41
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
       network:");
6 disp("I2-I1=4");....//equation 1
7 disp("Applying KVL at the outerpath:");
8 disp("-6*I1-5*I2=2");....//equation 2
9 A=[-1 1;-6 -5];
10 B=[4 2]';
11 X=inv(A)*B;
12 disp(X);
13 disp("I1 = -2 A");
14 disp("I2 = 2 A");
15 disp("Writing Vth equation ,");
16 a=-2;
17 v=8-a;
18 printf("\nVth = %.f V",v);
19 //calculation of Rth
20 disp("replacing the voltage source with short
       circuit and current source by an open circuit ");
21 x=(v*1)/(v+1);
22 printf("\nRth = %.2 f Ohm",x);
23 //calculation of RL
24 disp("For maximum power transfer");
25 printf("\nRth = RL =%.2 f Ohm",x);
26 //calculation of Pmax
27 m=(v^2)/(4*x);
28 printf("\nPmax = %.2 f W",m);
```

Scilab code Exa 3.42 example42

```
1 //Network Theorem 1
2 //page no-3.48
3 //example3.42
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
       network:");
6 disp("I1=50");....//equation 1
7 disp("Applying KVL to mesh 2:");
8 disp("5*I1-10*I2=0");....//equation 2
9 A=[1 0;5 -10];
10 B=[50 0]';
11 X=inv(A)*B;
12 disp(X);
13 disp("I2 = 25 A");
14 disp("Writing Vth equation ,");
15 a=25;
16 v=3*a;
17 printf("\nVth = %.f V",v);
18 //calculation of Rth
19 disp("replacing the current source of 50 A by an
       open circuit ");
20 x=7;
21 y=3;
22 m=(x*y)/(x+y);
23 printf("\nRth = %.1f Ohm",m);
24 //calculation of RL
25 disp("For maximum power transfer");
26 printf("\nRth = RL =%.1f Ohm",m);
27 //calculation of Pmax
28 n=(v^2)/(4*m);
29 printf("\nPmax = %.2f W",n);
```

Scilab code Exa 3.43 example43

```
1 //Network Theorem 1
2 //page no-3.49
3 //example3.43
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
     network:");
6 disp("Writing the current equation for the supermesh
     ");
7 disp("I2-I1=6");....//equation 1
8 disp("Applying KVL to the supermesh :");
9 disp("5*I1+2*I2=10");....//equation 2
10 A=[-1 1;5 1];
11 B=[6 10]';
12 X=inv(A)*B;
13 disp(X);
14 disp("I1 = -0.29 A");
15 disp("I2 = 5.71 A");
16 disp("Writing Vth equation ,");
17 a=5.71;
18 v=2*a;
19 printf("\nVth = %.f V",v);
20 //calculation of Rth
21 disp("replacing the current source of 50 A by an
     open circuit ");
22 x=5;
23 y=2;
24 m=((x*y)/(x+y))+3+4;
25 printf("\nRth = %.2 f Ohm",m);
26 //calculation of RL
27 disp("For maximum power transfer");
28 printf("\nRth = RL =%.2 f Ohm",m);
29 //calculation of Pmax
```

```
30 n=(v^2)/(4*m);
31 printf("\nPmax = %.2 f W",n);
```

Scilab code Exa 3.44 example44

```
1 //Network Theorem 1
2 //page no-3.50
3 //example3.44
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
       network:");
6 disp("Applying KVL to mesh 1");
7 disp("15*I1-5*I2=120");....//equation 1
8 disp("Applying KVL to the mesh 2:");
9 disp("I2=-6");....//equation 2
10 A=[15 -5;0 1];
11 B=[120 -6];
12 X=inv(A)*B;
13 disp(X);
14 disp("I1 = 6 A");
15 disp("Writing Vth equation ,");
16 a=6;
17 v=120-(10*a);
18 printf("\nVth = %.f V",v);
19 //calculation of Rth
20 disp("replacing the current source of 50 A by an
       open circuit ");
21 x=10;
22 y=5;
23 m=((x*y)/(x+y));
24 printf("\nRth = %.2 f Ohm",m);
25 //calculation of RL
26 disp("For maximum power transfer");
27 printf("\nRth = RL =%.2 f Ohm",m);
28 //calculation of Pmax
```

```
29 n=(v^2)/(4*m);
30 printf("\nPmax = %.2 f W",n);
```

Scilab code Exa 3.45 example45

```
1 //Network Theorem 1
2 //page no-3.51
3 //example3.45
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
       network:");
6 disp("I1=3 A");....//equation 1
7 disp("Applying KVL to the mesh 2:");
8 disp("-25*I1+41*I2=0");....//equation 2
9 A=[1 0;-25 41];
10 B=[3 0]';
11 X=inv(A)*B;
12 disp(X);
13 disp("I2 = 1.83 A");
14 disp("Writing Vth equation ,");
15 a=1.83;
16 v=-20+(10*a)+(6*a);
17 printf("\nVth = %.2 f V",v);
18 //calculation of Rth
19 disp("replacing the current source of 50 A by an
       open circuit ");
20 x=25;
21 y=16;
22 m=((x*y)/(x+y));
23 printf("\nRth = %.2 f Ohm",m);
24 //calculation of RL
25 disp("For maximum power transfer");
26 printf("\nRth = RL =%.2 f Ohm",m);
27 //calculation of Pmax
28 n=(v^2)/(4*m);
```

```
29 printf("\nPmax = %.2f W",n);
```

Scilab code Exa 3.46 example46

```
1 //Network Theorem 1
2 //page no-3.52
3 //example3.46
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
       network:");
6 disp("I2-I1=2");....//equation 1
7 disp("I2=-3 A");....//equation 2
8 A=[-1 1;0 1];
9 B=[2 -3]';
10 X=inv(A)*B;
11 disp(X);
12 disp("I1 = -5 A");
13 disp("Writing Vth equation ,");
14 a=-5;
15 b=-3;
16 v=8-(2*a)-b-6;
17 printf("\nVth = %.f V",v);
18 //calculation of Rth
19 disp("replacing the voltage source with short
       circuit and current source by an open circuit ");
20 m=5;
21 printf("\nRth = %.f Ohm",m);
22 //calculation of RL
23 disp("For maximum power transfer");
24 printf("\nRth = RL =%.f Ohm",m);
25 //calculation of Pmax
26 n=(v^2)/(4*m);
27 printf("\nPmax = %.2f W",n);
```

Scilab code Exa 3.47 example47

```
1 //Network Theorem 1
2 //page no-3.52
3 //example3.46
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
     network:");
6 disp("By star-delta transformation");
7 a=5;
8 b=20;
9 c=9;
10 v=100;
11 i=v/(a+a+b+c+c);
12 disp("Writing Vth equation ,");
13 vth=v-(14*i);
14 printf("\nVth = %.2f V",vth);
15 //calculation of Rth
16 disp("replacing the voltage source with short
     circuit ");
17 m=23.92;
18 printf("\nRth = %.2f Ohm",m);
19 //calculation of RL
20 disp("For maximum power transfer");
21 printf("\nRth = RL =%.2f Ohm",m);
22 //calculation of Pmax
23 n=(vth^2)/(4*m);
24 printf("\nPmax = %.2f W",n);
```

Scilab code Exa 3.48 example48

```
1 //Network Theorem 1
```

```

2 //page no-3.55
3 //example3.48
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
network:");
6 disp("Applying KVL to the mesh 1:");
7 disp("35*I1-30*I2=60");....//equation 1
8 disp("Applying KVL to the mesh 2:");
9 disp("I2=2");....//equation 2
10 A=[35 -30;0 1];
11 B=[60 2];
12 X=inv(A)*B;
13 disp(X);
14 disp("I1 = 3.43 A");
15 disp("Writing Vth equation ,");
16 a=3.43;
17 b=2;
18 v=20*(a-b)+20;
19 printf("\nVth = %.2f V",v);
20 //calculation of Rth
21 disp("replacing the voltage source with short
circuit and current source by an open circuit ");
22 x=15;
23 y=20;
24 m=((x*y)/(x+y));
25 printf("\nRth = %.2f Ohm",m);
26 //calculation of RL
27 disp("For maximum power transfer");
28 printf("\nRth = RL =%.2f Ohm",m);
29 //calculation of Pmax
30 n=(v^2)/(4*m);
31 printf("\nPmax = %.1f W",n);

```

Scilab code Exa 3.49 example49

```

1 //Network Theorem 1
2 //page no-3.56
3 //example3.49
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
       network:");
6 x=100;
7 a=10;
8 b=20;
9 c=30;
10 d=40;
11 i1=x/(a+c);
12 i2=x/(b+d);
13 printf("\nI1 = %.1f A",i1);
14 printf("\nI2 = %.2f A",i2);
15 disp("Writing Vth equation ,");
16 x=2.5;
17 y=1.66;
18 v=(20*y)-(10*x);
19 printf("\nVth = %.1f V",v);
20 //calculation of Rth
21 disp("replacing the voltage source of 100V with
       short circuit ");
22 m=((a*c)/(a+c))+((b*d)/(b+d));
23 printf("\nRth = %.2f Ohm",m);
24 //calculation of RL
25 disp("For maximum power transfer");
26 printf("\nRth = RL =%.2f Ohm",m);
27 //calculation of Pmax
28 n=(v^2)/(4*m);
29 printf("\nPmax = %.2f W",n);

```

Scilab code Exa 3.50 example50

```
1 //Network Theorem 1
```

```

2 //page no-3.57
3 //example3.50
4 //calculation of Vth
5 disp("Removing the variable resistor RL from the
       network:");
6 disp("Applying KVL to the mesh 1:");
7 disp("9*I1-3*I2=72");....//equation 1
8 disp("Applying KVL to the mesh 2:");
9 disp("-3*I1+9*I2=0");....//equation 2
10 A=[9 -3;-3 9];
11 B=[72 0];
12 X=inv(A)*B;
13 disp(X);
14 disp("I1 = 9 A");
15 disp("I2 = 3 A");
16 disp("Writing Vth equation ,");
17 a=9;
18 b=3;
19 v=(6*a)+(2*b);
20 printf("\nVth = %.f V",v);
21 //calculation of Rth
22 disp("replacing the voltage source with short
       circuit and current source by an open circuit ");
23 x=6;
24 y=2;
25 z=4;
26 m=((x*b)/(x+b))+2;
27 l=((m*z)/(m+z));
28 printf("\nRth = %.f Ohm",l);
29 //calculation of RL
30 disp("For maximum power transfer");
31 printf("\nRth = RL =%.f Ohm",l);
32 //calculation of Pmax
33 n=(v^2)/(4*l);
34 printf("\nPmax = %.f W",n);

```

Scilab code Exa 3.51 example51

```
1 //Network Theorem 1
2 //page no-3.58
3 //example3.51
4 //Calculation of Vth
5 disp("from the figure");
6 disp("Vth=4*I");
7 disp("Applying KVL to the mesh");
8 disp("0.5*Vth-8*I=-12");
9 A=[1 -4;0.5 -8];
10 B=[0 -12]';
11 X=inv(A)*B;
12 disp(X);
13 disp("Vth=8 V");
14 //Calculation of Isc
15 v=8;
16 i=12/4;
17 printf("\nIsc = %.f A",i);
18 //Calculation of Rth
19 r=v/i;
20 printf("\nRth = Vth/Isc = %.3f Ohm",r);
21 //calculation of RL
22 disp("For maximum power transfer");
23 printf("\nRth = RL =%.3f Ohm",r);
24 //calculation of Pmax
25 x=v/(2*r);
26 printf("\nIL = %.1f A",x);
27 n=(x^2)*r;
28 printf("\nPmax = %.f W",n);
```

Chapter 4

AC Circuits

Scilab code Exa 4.1 example1

```
1 //AC Circuits :example 4.1:( pg4.4)
2 i=15;
3 t=3.375*10^-3;
4 f=40;
5 pi=3.14;
6 Im=(i/sin(2*pi*f*t));
7 disp("i=15 Amp");
8 disp("t =3.375 ms");
9 disp("f=40 Hz");
10 disp("i=Im*sin (2*pi*f*t)");
11 printf("Im=%fAmp",Im);
```

Scilab code Exa 4.2 example2

```
1 //AC Circuits :example 4.2:( pg4.4)
2 f=50;
3 Im=100;
4 i1=86.6;
```

```

5 t=(1/600);
6 pi=3.14;
7 disp("f=50 c/s");
8 disp("Im=100 A");
9 // part(a)
10 disp("i=Im*sin(2*pi*f*t)");
11 i=Im*sin(2*pi*f*t);
12 printf("i=%f A",i);
13 // part(b)
14 disp("i=Im*sin(2*pi*f*t1)");
15 t1=(asind(i1/Im)/(2*pi*f));
16 printf("t1=%f second",t1);

```

Scilab code Exa 4.3 example3

```

1 //AC Circuits:example 4.3:( pg4.5)
2 f=50;
3 I=20;
4 t1=0.0025;
5 t2=0.0125;
6 I1=14.14;
7 pi=3.14;
8 disp("f=50 c/s");
9 disp("I=20 A");
10 mprintf("Im=I*sqrt(2)");
11 Im=(sqrt(2)*I);
12 printf("\nIm=%f A",Im);
13 mprintf("\nEquation of current , \ni=Im*sin(2*pi*f*t)");
14 disp("=28.28 sin(2*pi*f*t)=28.28 sin(100*pi*t)");
15 disp("(a)At t=0.0025 seconds");
16 i=(Im*sin(2*pi*f*t1));
17 printf("i=%f A",i); //when t=0.0025 seconds
18 disp("(b)At t=0.0125 seconds");
19 i=(Im*sin(2*pi*f*t2));

```

```

20 printf("i=%f A",i); //when t=0.0125 seconds
21 disp("(c) i=28.28 sin(100*pi*t)");
22 t=(asind(I1/Im)/(2*pi*f));
23 printf("t=%f second",t); // when I=14.14A

```

Scilab code Exa 4.4 example4

```

1 //AC Circuits : example 4.4 : pg(4.5)
2 pi=3.14;
3 Vm=200;
4 disp("v=200 sin 314t");
5 disp("v=Vmsin(2*pi*f*t)");
6 disp("(2*pi*f)=314");
7 f=(314/(2*pi));
8 printf("f=%f Hz",f);
9 Vavg=((2*Vm)/pi);
10 Vrms=(Vm/sqrt(2));
11 mprintf('nFor a sinusoidal waveform, \nVavg=(2*Vm/
    pi) \nVrms=(Vm/sqrt(2))');
12 kf=(Vrms/Vavg);
13 kc=(Vm/Vrms);
14 mprintf('\nform factor=%f',kf);
15 mprintf('\ncrest factor=%f',kc);

```

Scilab code Exa 4.5 example5

```

1 //AC Circuits : example 4.5 :( pg 4.6)
2 kf=1.2;
3 kp=1.5;
4 Vavg=10;
5 disp("kf=1.2");
6 disp("kp=1.5");
7 disp("Vavg=10");

```

```

8 disp("form factor kf=(Vrms/Vavg)") ;
9 Vrms=(kf*Vavg) ;
10 printf("\nVrms=% . f V" ,Vrms) ;
11 disp("peak factor kp=(Vm/Vrms)") ;
12 Vm=(kp*Vrms) ;
13 printf("\nVm=% . f V" ,Vm) ;

```

Scilab code Exa 4.14 example14

```

1 //AC Circuits: example 4.14 :( pg 4.11)
2 v1=0;
3 v2=40;
4 v3=60;
5 v4=80;
6 v5=100;
7 t=8;
8 Vavg=((v1+v2+v3+v4+v5+v4+v3+v2)/t);
9 Vrms=sqrt((v1^2+v2^2+v3^2+v4^2+v5^2+v4^2+v3^2+v2^2)/
    t);
10 disp("Vavg=((0+40+60+80+100+80+60+40)/8)");
11 printf("\nVavg=% . 1 f V" ,Vavg);
12 disp("Vrms=sqrt((0+(40)^2+(60)^2+(80)^2+(100)^2+(80)
    ^2+(60)^2+(40)^2)/8)");
13 printf("\nVrms=% . 2 f V" ,Vrms);

```

Scilab code Exa 4.15 example15

```

1 //AC Circuits : example 4.15 :pg(4.11 & 4.12)
2 v1=0;
3 v2=10;
4 v3=20;
5 t=3;
6 Vavg=((v1+v2+v3)/t);

```

```

7 Vrms=(sqrt((v1^2+v2^2+v3^2)/t));
8 disp("Vavg=((0+10+20)/3)");
9 printf("Vavg=%f V",Vavg);
10 disp("Vrms=(((0)^2+(10)^2+(20)^2)/3)");
11 printf("Vrms=%f V",Vrms);

```

Scilab code Exa 4.33 example33

```

1 //AC Circuits : example 4.33 :pg(4.27)
2 Vm=177;
3 Im=14.14;
4 phi=30;
5 V=(Vm/sqrt(2));
6 I=(Im/sqrt(2));
7 pf=cosd(30);
8 P=(V*I*pf);
9 disp("v(t)=177sin(314t+10)"); // value of 10 is in
    degrees
10 disp("i(t)=14.14sin(314t-20)"); // value of 20 is in
    degrees
11 mprintf("\nCurrent i(t) lags behind voltage v(t) by
    30 degrees");
12 disp("phi=30 degrees");
13 printf("Power factor          pf=cos(30)=%f (lagging)
    ",pf);
14 printf("\nPower consumed      P=V*I*cos(phi)=%f W",P);

```

Scilab code Exa 4.42 example42

```

1 //AC Circuits : example 4.42 :pg(4.32 & 4.33)
2 PR=1000;
3 VR=200;

```

```

4 Pcoil=250;
5 Vcoil=300;
6 R=((VR^2)/PR);
7 I=(VR/R);
8 r=((Pcoil/(I^2)));
9 Zcoil=(Vcoil/I);
10 XL=sqrt((Zcoil^2)-(r^2));
11 RT=(R+r);
12 ZT=sqrt((RT^2)+(XL^2));
13 V=(ZT*I);
14 printf("\nPR=1000 W \nVR=200 V \nPcoil=250 W \nVcoil
      =300 V \nPR=(VR^2/R)");
15 printf("\nR=%f Ohms",R);
16 printf("\nVR=R*I \nI=%f A",I);
17 disp("Pcoil=(I^2)*r");
18 printf("\nResistance of coil      r=%f Ohm");
19 printf("\nImpedance of coil      Zcoil=(Vcoil/I)=%.
      f Ohms",Zcoil);
20 printf("\nReactance of coil      XL=sqrt((Zcoil^2)
      -(r^2))=%f Ohms",XL);
21 printf("\nCombined resistance      RT=R+r=%f Ohms",
      RT);
22 printf("\nCombined impedance      ZT=sqrt(((R+r)^2)
      +(XL^2))=%f Ohms",ZT);
23 printf("\nSupply voltage      V=ZT*I=%f V",V);

```

Scilab code Exa 4.47 example47

```

1 //AC Circuits : example 4.47 : pg(4.47)
2 f1=60;
3 V=200;
4 P=600;
5 I=5;
6 f=50;
7 Z=V/I;

```

```

8 r=(P/(I^2));
9 XL=sqrt((Z^2)-(r^2));
10 L=(XL/(2*pi*f));
11 XL1=(2*pi*f1*L);
12 Z1=sqrt((r^2)+(XL1^2));
13 I=(V/Z1);
14 printf("\nI=5 A \nV=200 V \nP=600 W \nFor f=50 Hz,");
15 ;
15 printf("\nZ=V/I =%.f Ohms",Z);
16 printf("\nP=((I^2)*r) \nr=%.f Ohms",r);
17 printf("\nXL=sqrt ((Z^2)-(r^2)) \nXL=%.f Ohms",XL);
18 printf("\nXL=(2*pi*f*L)\nL=%.4f H",L);
19 printf("\nFor f=60 Hz \nXL=%.1f Ohm",XL1);
20 printf("\n\nr=24 Ohms \nZ=sqrt ((r^2)+(XL^2))=% .2f Ohms
",Z1);
21 printf("\nI=V/Z=%.3f A",I);

```

Scilab code Exa 4.48 example48

```

1 //AC Circuits : example 4.48 :( pg 4.37)
2 f=50;
3 pi=3.14;
4 Vdc=12;
5 Idc=2.5;
6 Vac=230;
7 Iac=2;
8 Pac=50;
9 R=(Vdc/Idc);
10 Z=(Vac/Iac);
11 Pi=(Pac-((Iac^2)*R));
12 RT=(Pac/(Iac^2));
13 XL=sqrt((Z^2)-(RT^2));
14 L=(XL/(2*pi*f));
15 pf=(RT/Z);
16 i=(Pi/(Iac^2));

```

```

17 printf("\nFor dc      V=12 V,      I=2.5 A \nFor ac
           V=230 V,      I=2 A,      P=50 W");
18 printf("\nIn an iron-cored coil , there are two types
           of losses \n(i) Losses in core known as core or
           iron loss \n(ii) Losses in winding known as copper
           loss");
19 printf("\nP=(I^2)*R+Pi \nP/(I^2)=R+((Pi)/(I^2)) \nRT
           =R+(Pi/(I^2)) \nwhere R is the resistance of the
           coil and (Pi/I^2) is the resistance which is
           equivalent to the effect of iron loss");
20 printf("\nFor dc supply ,   f=0 \nXL=0");
21 printf("\nR=%f Ohm",R);
22 printf("\nFor ac supply \nZ=%f Ohms",Z);
23 printf("\nIron loss      Pi=P-I^2*R=%f W",Pi);
24 printf("\nRT=(P/I^2)=%f Ohm",RT);
25 printf("\nXL=sqrt ((Z^2)-(RT^2))=%f Ohm",XL);
26 printf("\nXL=2*pi*L \nInductance      L=%f H",L);
27 printf("\nPower factor      =RT/Z=%f (lagging)",pf
           );
28 printf("\nThe series resistance equivalent to the
           effect of iron loss= Pi/(I^2)=%f Ohms",i);

```

Scilab code Exa 4.49 example49

```

1 //AC Circuits : example 4.49 :( pg 4.37 & 4.38)
2 f=50;
3 I1=4;
4 pf1=0.5;
5 V1=200;
6 I2=5;
7 pf2=0.8;
8 V2=40;
9 Z1=(V2/I2);
10 R=(Z1*pf2);
11 XL1=sqrt((Z1^2)-(R^2));

```

```

12 L1=(XL1/(2*pi*f));
13 Z2=(V1/I1);
14 RT=(Z2*pf1);
15 XL2=sqrt((Z2^2)-(RT^2));
16 L2=(XL2/(2*pi*f));
17 Pi=(V1*I1*pf1-(I1^2)*R);
18 printf("\nWith iron core I=4 A pf=0.5, V
        =200 V \nWithout iron core I=5 A pf=0.8,
        V=40 V \nWhen the iron-core is removed ,");
19 printf("\nZ=V/I=%.f Ohms",Z1);
20 printf("\nPF=R/Z \nR=%.1f Ohms",R);
21 printf("\nXL=sqrt ((Z^2)-(RT^2))=%.1f Ohms",XL1);
22 printf("\nXL=(2*pi*f*L) \nInductance L=%.4f H",L1
        );
23 printf("\nWith iron core , \nZ=%.f Ohms",Z2);
24 printf("\nPF=RT/Z \nRT=%.f Ohm",RT);
25 printf("\nXL=sqrt ((Z^2)-(RT^2))=%.2f Ohm",XL2);
26 printf("\nXL=(2*pi*f*L) \nInductance L=%.4f H
        ",L2);
27 printf("\nIron loss Pi=P=(I^2)*R \n=VIcos(phi)-
        I^2*R \n=%.1f W",Pi);

```

Scilab code Exa 4.51 example51

```

1 //AC Circuits : example 4.51 :( pg 4.40 & 4.41)
2 P=2000;
3 pf=0.5;
4 V=230;
5 S=(P/pf);
6 phi=acosd(pf);
7 I=(P/(V*pf));
8 Q=(V*I*sind(phi));
9 disp("P=2000 W");
10 disp("pf=0.5 (leading)");
11 disp("V=230 V");

```

```

12 disp("P=V*I*cos(phi)");
13 printf("\nI=%f A", I);
14 printf("\nS=V*I=P/cos(phi)=%f VA", S);
15 printf("\nphi=%f degrees", phi);
16 printf("\nQ=V*I*sin(phi)=%f VAR", Q);

```

Scilab code Exa 4.52 example52

```

1 //AC Circuits : example 4.52 :( pg 4.41)
2 V=240;
3 VR=100;
4 P=300;
5 f=50;
6 R=((VR^2)/P);
7 I=sqrt(P/R);
8 Z=V/I;
9 XC=sqrt((Z^2)-(R^2));
10 C=(1/(2*pi*f*XC));
11 VC=sqrt((V^2)-(VR^2));
12 VCmax=(VC*sqrt(2));
13 Qmax=(C*VCmax);
14 Emax=((1/2)*C*(VCmax^2));
15 printf("\nV=240 V \nVR=100 V \nP=300 W \nf=50 Hz");
16 printf("\nP=(VR^2)/R \nR=((VR^2)/P)=%f Ohm", R);
17 printf("\nP=(I^2)*R \nI=sqrt((P/R)) \nI=%f A", I);
18 printf("\nZ=V/I=%f Ohm", Z);
19 printf("\nXC=sqrt((Z^2)-(R^2))=%f Ohm", XC);
20 printf("\nXC=1/2*pi*f*C \nC=%f F", C);
21 printf("\nVoltage across capacitor VC=sqrt((V^2)-(VR^2))=%f V", VC);
22 printf("\nMaximum value of max charge \nVC=%f V \nQmax=C*VCmax=%f C", VCmax, Qmax);
23 printf("\nMax stored energy Emax=((1/2)*C*(VCmax^2)) \n=%f J", Emax);

```

Scilab code Exa 4.53 example53

```
1 //AC Circuits : example 4.53 :( pg 4.42)
2 C=35*10^-6;
3 f=50;
4 XC=(1/(2*pi*f*C));
5 R=sqrt(3*(XC^2));
6 R^2=(3*(XC^2));
7 printf("\nC=35*10^-6 F \nf=50 Hz \nVC=1/2.V \nXC
     =1/(2*pi*f*C)=%.3f Ohm",XC);
8 printf("\nVC=1/2.V \nXC. I=1/2.Z. I \nXC=1/2.Z \nZ=2.
     XC \nZ=sqrt((R^2)+(XC^2)) \n(2XC)^2=(R^2)+(XC^2)
     \n3XC^2=R^2");
9 mprintf("\nR^2=3*XC^2=%.2f Ohm \nR=%.1f Ohm",R^2,R);
```

Scilab code Exa 4.54 example54

```
1 //AC Circuits : example 4.54 :( pg 4.42)
2 V=125;
3 I=2.2;
4 P=96.8;
5 f=50;
6 Z=V/I;
7 R=(P/(I^2));
8 Xc=sqrt((Z^2)-(R^2));
9 C=(1/(2*pi*f*Xc));
10 printf("\nV=125 V \nP=96.8 W \nI=2.2 A \nf=50 Hz");
11 printf("\nZ=V/I=%.2f A",Z);
12 printf("\nP=(I^2)*R \nR=%.f Ohm",R);
13 printf("\nXc=sqrt((Z^2)-(R^2))=%.2f Ohm",Xc);
14 printf("\nXc=1/(2*pi*f*C) \n C=%.2e F",C);
```

Scilab code Exa 4.57 Series RLC circuit

```
1 //AC Circuits : example 4.57 :( pg 4.46)
2 j=%i;
3 f=50;
4 L=0.22;
5 R1=3;
6 Z=3.8+j*6.4;
7 XL=2*pi*f*L;
8 R2=3.8;
9 R=R2-R1;
10 X=6.4;
11 XC=XL-X;
12 C=(1/(2*pi*f*XC));
13 printf("\nZ=(3.8+j*6.4) Ohm");
14 printf("\nXL=2*pi*f*L=%f Ohm",XL);
15 printf("\nZ=(3+j69.12+R-jXC) \n=(3+R)+j(69.12-XC)");
16 printf("\n3+R=3.8 \nR=%f Ohm",R);
17 printf("\nXC=%f Ohm",XC);
18 printf("\nXC=1/2.pi.f.C \nC=%e F",C);
```

Scilab code Exa 4.58 Series RLC circuit

```
1 //AC Circuits : example 4.58 :( pg 4.46)
2 R=20;
3 phi=45;
4 Z=R/cosd(phi);
5 XC=sqrt((Z^2)-(R^2));
6 XL=(2*XC);
7 w=1000;
8 L=(XL/w);
9 C=(1/(w*XC));
```

```

10 printf("\nvL=300 sin (1000t) \nR=20 Ohm \nphi=45 \nVL(
    max)=2Vcc(max) \nsqrt(2)*VL=2*sqrt(2)*VC \nI*XL
    =2*I*XC \nXL=2*XC \ncos(phi)=R/Z");
11 printf("\nZ=%f Ohm",Z);
12 printf("\nZ=sqrt((R^2)+(XL-XC)^2) \nXC=%f Ohm",XC);
    //for series R-L-C ckt
13 printf("\nXL=2*XC=%f Ohm",XL);
14 printf("\nXL=w*L \nL=%f H",L);
15 printf("\nXC=1/w*C \nC=%f F",C);

```

Scilab code Exa 4.59 Series RLC circuit

```

1 //AC Circuits : example 4.59 :( pg 4.47)
2 pf=0.5;
3 C=79.59*10^-6;
4 f=50;
5 XC=(1/(2*pi*f*C));
6 R=pf*XC;
7 Zcoil=XC;
8 XL=sqrt((Zcoil^2)-(R^2));
9 L=(XL/(2*pi*f));
10 printf("\n pf=0.5 \nC=79.57uF \nf=50 Hz \nVcoil=VC ")
    ;
11 printf("\n XC=1/2*pi*f*C=%f Ohm",XC);
12 printf("\n Vcoil=VC \nZcoil=XC=%f Ohm",XC);
13 printf("\n pf of coil=cos(phi)=R/Zcoil \nResistance
    of coil R=%f Ohm",R);
14 printf("\nXL=sqrt((Zcoil^2)-(R^2))=%f Ohm",XL);
15 printf("\nXL=2*pi*f*L \nInductance of coil=%f H",L)
    );

```

Scilab code Exa 4.60 Series RLC Circuit

```

1 //AC Circuits : example 4.60 :( pg 4.48)
2 f=50;
3 V=250;
4 R=5;
5 L=9.55;
6 Vcoil=300;
7 XL=2*pi*f*L;
8 Zcoil=(sqrt((R^2)+(XL^2)));
9 I=Vcoil/Zcoil;
10 Z=V/I;
11 XC1=Zcoil-Z;
12 XC2=Zcoil+Z;
13 C1=(1/(2*pi*f*XC1));
14 C2=(1/(2*pi*f*XC2));
15 printf("\nV=250 V \nR=5 Ohm \nL=9.55 H \nVcoil=300 V
      ");
16 printf("\nXL=2*pi*f*L =%.f Ohm",XL);
17 printf("\nZcoil=sqrt(R^2)+(XL^2) =%.f Ohm",Zcoil);
18 printf("\nI=Vcoil/Zcoil =%.1f A",I);
19 printf("\nZ=V/I =%.f Ohm",Z); //total impedance
20 printf("\nZ=sqrt((R^2)+(XL-XC)^2) \nXC=%.f Ohm",XC1)
      ; //when XL>XC
21 printf("\nC=1/2*pi*f*XC =%.e F",C1);
22 printf("\nZ=sqrt((R^2)+(XC-XL)^2) \nXC=%.f Ohm",XC2)
      ; //when XC>XL
23 printf("\nC=%.e F",C2);

```

Scilab code Exa 4.79 Series Resonance

```

1 //AC Circuits : example 4.79 :( pg 4.64)
2 R=10;
3 L=0.01;
4 C=100*10^-6;
5 f0=(1/(2*pi*sqrt(L*C)));
6 BW=(R/(2*pi*L));

```

```

7 f1=f0-(BW/2);
8 f2=f0+(BW/2);
9 printf("\nR=10 Ohm \nL=0.01H \nC=100uF");
10 printf("\nf0=1/2*pi*sqrt(L*C)=%f Hz",f0); //resonant frequency
11 printf("\nBW=R/2*pi*L =%f Hz",BW); //bandwidth
12 printf("\nf1=f0-BW/2 \nn=%f Hz",f1); //lower frequency
13 printf("\nf2=f0+BW/2 =%f Hz",f2); //higher frequency

```

Scilab code Exa 4.80 Series Resonance

```

1 //AC Circuits : example 4.80 :( pg 4.65)
2 R=10;
3 L=0.2;
4 C=40*10^-6;
5 V=100;
6 f0=(1/(2*pi*sqrt(L*C)));
7 I0=(V/R);
8 P0=((I0^2)*R);
9 pf=1;
10 Vr=(R*I0);
11 Vl=((2*pi*f0*L)*I0);
12 Vc=((1/(2*pi*f0*C))*I0);
13 Q=((1/R)*sqrt(L/C));
14 f1=(f0-(R/(4*pi*L)));
15 f2=(f0+(R/(4*pi*L)));
16 printf("\nR=10 Ohm \nL=0.2 H \nC=40uF \nV=100 V");
17 printf("\n(i) f0= 1/2*pi*sqrt(LC) =%f Hz",f0); //resonant frequency
18 printf("\n(ii) I0= V/R =%f A",I0); //current
19 printf("\n(iii) P0=(I0^2)*R =%f W",P0); //power
20 printf("\n(iv) pf=1"); //power factor
21 printf("\n(v) Rv = R. I =%f V",Vr); //voltage across

```

```

    resistor
22 printf("\n Lv = XL. I =%.1f V" ,V1); // voltage across
     inductor
23 printf("\n Cv = XC. I =%.1f V" ,Vc); // voltage across
     capacitor
24 printf("\n(vi) Q =1/R*sqrt(L/C)=%.2f" ,Q); // Quality
     factor
25 printf("\n(vii)f1 = f0-R/4. pi .L = %.2f Hz" ,f1); //
     half power points
26 printf("\nf2=f0+R/4. pi .L = %.1f Hz" ,f2);
27 // x initialisation
28 x=[-1:0.1:2*pi];
29 //simple plot
30 plot(sin(x))

```

Scilab code Exa 4.81 Series Resonance

```

1 //AC Circuits : example 4.81 :( pg 4.66)
2 V=200;
3 Vc=5000;
4 I0=20;
5 C=4*10^-6;
6 R=V/I0;
7 Xco=Vc/I0;
8 f0=(1/(2*pi*Xco*C));
9 L=(Xco/(2*pi*f0));
10 printf("\nV=200 V \nI0= 20 A \nVc=5000 V \nC=4uF");
11 printf("\nR=V/I0 =%. f Ohm" ,R); // resistance
12 printf("\nXco=Vco/Io =%. f Ohm" ,Xco);
13 printf("\nXco=1/2*pi*f0*C \nf0=1/2*pi*Xco*C =%.2f Hz
     " ,f0);
14 printf("\nat resonance Xco=Xlo \nXlo=% . f Ohm" ,Xco);
15 printf("\nXlo=2*pi*f0*L \nL=% .2f H" ,L);

```

Scilab code Exa 4.82 Series Resonance

```
1 //AC Circuits : example 4.82 :( pg 4.66)
2 V=230;
3 f0=50;
4 I0=2;
5 Vco=500;
6 R=V/I0;
7 Xco=Vco/I0;
8 C=(1/(2*pi*f0*Xco));
9 L=(Xco/(2*pi*f0));
10 printf("\nV = 230 V \nf0 = 50 Hz \nI0 = 2A \nVco =
      500 V");
11 printf("\nR=V/I0 =%.f Ohm",R);
12 printf("\nXco=Vco/I0 =%.f Ohm",Xco);
13 printf("\nXco=1/2.pi.f0.C \nC= %.e F",C); //
      capacitance
14 printf("\nXco=Xlo \nXlo=%.f Ohm",Xco); //at resonance
15 printf("\nXlo=2.pi.f0.L \nL=%.3f H",L); //inductance
```

Scilab code Exa 4.83 Series Resonance

```
1 //AC Circuits : example 4.82 :( pg 4.66)
2 R=2;
3 L=0.01;
4 V=200;
5 f0=50;
6 C=(1/(4*(pi)^2*L*(f0^2)));
7 I0=V/R;
8 Vco=I0*(1/(2*pi*f0*C));
9 printf("\nR= 2 Ohm \nL= 0.01 H \nV=200 V \nf0=50 Hz
      \nf0=1/(2.pi.sqrt(LC));
```

```

10 printf("\nC = %.e F",C); // capacitance
11 printf("\nI0= V/R =%.f A",I0); // current
12 printf("\nVco=I0 . Xco \n=%f V",Vco); // voltage
   across capacitor

```

Scilab code Exa 4.84 Series Resonance

```

1 //AC Circuits : example 4.84 :( pg 4.67)
2 BW=400;
3 Vco=500;
4 R=100;
5Vm=10;
6 V=(Vm/sqrt(2));
7 I0=V/R;
8 L=R/BW;
9 Q0=Vco/V;
10 C=(L/(Q0*R)^2);
11 f0=(1/(2*pi*sqrt(L*C)));
12 f1=(f0-(R/(4*pi*L))); //lower cut-off frequency
13 f2=(f0+(R/(4*pi*L))); //upper cut-off frequency
14 printf("\nv(t)=10sinwt \nVco=5000V \nBW=400rad/s \nR
   =100 Ohm");
15 printf("\nV=%f V",V);
16 printf("\nI0=V/R=%f A",I0);
17 printf("\nBW=R/L \nL=%f H",L);
18 printf("\nQ0=Vco/V =%.2f",Q0);
19 printf("\nQ0=1/R*sqrt(L/C) \nC=%e F",C);
20 printf("\nf0=1/2.pi.sqrt(LC)=%.2f Hz",f0);
21 printf("\nf1=f0-R/4.pi.L =%.2f Hz",f1); //lower cut-
   off frequency
22 printf("\nf2=f0+R/4.pi.L =%.2f Hz",f2); //upper cut-
   off frequency

```

Scilab code Exa 4.85 Series Resonance

```
1 //AC Circuits : example 4.85 :( pg 4.68)
2 R=500;
3 f1=100;
4 f2=10*10^3;
5 BW=f2-f1;
6 f0=((f1+f2)/2);
7 L=(R/(2*pi*BW));
8 XL0=(2*pi*f0*L);
9 C=(1/(2*pi*f0*XL0));
10 Q0=((1/R)*(sqrt(L/C)));
11 printf("\nR= 500 Ohm \nf1 = 100 Hz \nf2=10kHz \nBW=
    f2-f1 =%. f Hz",BW);
12 printf("\nf1=f0-BW/2 ----- (i) \nf2=f0+BW/2 -----
    ii) \nf1+f2 =2f0 \nf0=(f1+f2)/2 =%. f Hz",f0);
13 printf("\nBW=R/2. pi . f0 . L \nL=%.6 f H",L);
14 printf("\nXL0=2. pi . f0 . L =%.2 f Ohm",XL0);
15 printf("\nXL0=XC0 =%.2 f Ohm",XL0); //at resonance
16 printf("\nXC0 =1/2. pi . f0 . C \nC=%. e F",C);
17 printf("\nQ0=(1/R*sqrt (L/C)) =%.4 f",Q0);
```

Scilab code Exa 4.87 Series Resonance

```
1 //AC Circuits : example 4.87 :( pg 4.69 & 4.70)
2 f0=10^6;
3 C1=500*10^-12;
4 C2=600*10^-12;
5 C=500*10^-12;
6 x=((2*pi*f0)^2);
7 L=(1/(x*C));
8 XL=(2*pi*f0*L);
9 y=2*pi*f0*C2;
10 XC=(1/y);
11 R=sqrt(((XL-XC)^2)/3);
```

```

12 x=sqrt(L/C);
13 Q0=((1/R)*x);
14 printf("\n f0= 1MHz \n C1=500pF \n C2=600pF \n C=500pF")
    ; //At resonance
15 printf("\n f0=1/2.pi.sqrt(LC)\n L=%f H",L);
16 printf("\n XL=2.pi.f0.L=%f Ohm",XL);
17 printf("\n XC=1/2.pi.f0.C \n XC=%f Ohm",XC);
18 printf("\n I=1/2.I0 \n V/Z=1/2.V/R \n Z=2R");
19 printf("\n sqrt((R^2)-(XL-XC)^2)=2R \n R=%f Ohm",R);
    //Resistance of Inductor
20 printf("\n Q0=1/R.sqrt(L/C) \n=%f",Q0);

```

Scilab code Exa 4.88 Parallel Resonance

```

1 //AC Circuits : example 4.88 :( pg 4.72)
2 R=20;
3 C=100*10^-6;
4 L=0.2;
5 DR=(L/(C*R));
6 x=(1/(L*C));
7 y=((R/L)^2);
8 f0=((1/(2*pi))*sqrt(x-y));
9 DR=(L/(C*R));
10 printf("\n R=20 Ohm \n L=0.2 H \n C=100uF");
11 printf("\n f0=1/2.pi.sqrt(1/LC-R^2/L^2) \n=%f Hz",
    f0);
12 printf("\n dynamic resistance =L/CR \n=%f Ohm",DR)
    ;

```

Scilab code Exa 4.89 Parallel Resonance

```

1 //AC Circuits : example 4.89 :( pg 4.72 & 4.73)
2 R=20;

```

```

3 L=200*10^-6;
4 f=10^6;
5 V=230;
6 Rs=8000;
7 XL=2*%pi*f*L;
8 x=((2*%pi*f)^2);
9 y=((R/L)^2);
10 C=(1/((x+y)*L));
11 Q=((2*%pi*f*L)/R);
12 Z=(L/(C*R));
13 ZT=(Rs+Z);
14 IT=(V/ZT);
15 printf("\nR=20 Ohm \nL=200uH \nf=10^6 \nV=230 V \nRs
     =8000 Ohm \nXL=2. pi . f . L =%.1f Ohm",XL);
16 printf("\nf0=1/2. pi . sqrt (1/LC-R^2/L^2) \nC=%e F",C)
     ;
17 printf("\nQ0=2. pi . f . L/R =%.2f",Q); // quality factor
18 printf("\nZ=L/CR \nf =%.f Ohm",Z); // dynamic impedance
19 printf("\nZt=%.f Ohm",ZT); // total equivalent Z at
     resonance
20 printf("\nIt=%e A",IT); // total ckt current

```

Chapter 5

Steady State AC Analysis

Scilab code Exa 5.1 example1

```
1 //Steady-State AC Analysis
2 //page no - 5.1
3 //example 5.1
4 // A = p2z(R,Theta) - Convert from polar to complex
   form.
5 //      R is a matrix containing the magnitudes
6 //      Theta is a matrix containing the phase angles
   (in degrees).
7 function [A] = p2z(R,Theta)
8 if argn(2) <> 2 then
9     error("incorrect number of arguments.");
10 end
11 if ~and(size(R) == size(Theta)) then
12     error("arguments must be of the same dimension.")
13 ;
14 A = R.*exp(%i*pi*Theta/180.);
15 endfunction
16
17 A=p2z(100,45); //converting from polar to rectangular
18 disp(A);
```

```

19 disp(" Applying KVL to Mesh 1 we get :");
20 disp("(3+j14)I1-j10I2=70.710678+j70.710678");//  

    Equation 1
21 disp(" Applying KVL to Mesh 2 we get :");
22 disp("I1=0");//equation 2
23 disp(" putting equation 2 in equation 1:");//putting  

    equation 2 in equation 1
24 disp("I2=(70.710678+j70.710678)/-j10");
25 I2=A/10*i;
26 disp(I2);
27 function [r,th]=rect2pol(x,y)
28 //rectangle to polar coordinate conversion
29 //based on "Scilab from a Matlab User's Point of  

    View", Eike Rietsch ,
30 2002
31 r=sqrt(x^2+y^2);
32 th = atan(y,x)*180/%pi;
33 endfunction
34 [r,th]=rect2pol(- 7.0710678,7.0710678)//converting  

    back to polar form
35 disp(r);
36 disp(th);
37 disp("I2= mag - 10 ang - 135 A");

```

Scilab code Exa 5.2 example2

```

1 //Steady-State AC Analysis
2 //page no - 5.1
3 //example 5.1
4 // A = p2z(R,Theta) - Convert from polar to complex  

    form .
5 // R is a matrix containing the magnitudes
6 // Theta is a matrix containing the phase angles  

    (in degrees).
7 function [A] = p2z(R,Theta)

```

```

8 if argn(2) <> 2 then
9     error("incorrect number of arguments.");
10 end
11 if ~and(size(R) == size(Theta)) then
12     error("arguments must be of the same dimension.")
13 ;
14 A = R.*exp(%i*pi*Theta/180.);
15 endfunction
16 A=p2z(10,30);
17 disp(A); //converting to rectangular form
18 M=[8-2*i, -3, 0; -3, 8+5*i, -5; 0, -5 7-2*i];
19 N=[A, 0, 0]';
20 O=inv(M);
21 X=O*N;
22 disp(X);
23 function [r,th]=rect2pol(x,y)
24 //rectangle to polar coordinate conversion
25 //based on "Scilab from a Matlab User's Point of
View", Eike Rietsch ,
26 2002
27 r=sqrt(x^2+y^2);
28 th = atan(y,x)*180/%pi;
29 endfunction
30 [r,th]=rect2pol(1.3340761,- 0.5209699) //converting
back to polar form

```

Scilab code Exa 5.11 example11

```

1 //Steady-State AC Analysis
2 //page no - 5.10
3 //example 5.11
4 disp("when mag-50 ang-0 source is acting alone :");
5 function [A] = p2z(R,Theta)
6 if argn(2) <> 2 then

```

```

7     error("incorrect number of arguments.");
8 end
9 if ~and(size(R) == size(Theta)) then
10    error("arguments must be of the same dimension.")
11 ;
11 end
12 A = R.*exp(%i*pi*Theta/180.);
13 endfunction
14 A=p2z(50,0); //converting polar to rec
15 disp(A);
16 disp("when mag=4 ang=0 source is acting alone :");
17 Vab2=0;
18 disp("By Super-position theorem :")
19 disp("Vab=Vab1+Vab2");
20 Vab=A+Vab2;
21 printf("Vab = %.f", Vab);
22 function [r,th]=rect2pol(x,y)
23 //rectangle to polar coordinate conversion
24 //based on "Scilab from a Matlab User's Point of
View", Eike Rietsch ,
25 2002
26 r=sqrt(x^2+y^2);
27 th = atan(y,x)*180/%pi;
28 endfunction
29 [r,th]=rect2pol(50,0)      //converting back to polar
form
30 disp(r);
31 disp(th);
32 disp("Vab= mag=50 ang=0 V")

```

Chapter 6

Three phase Circuits

Scilab code Exa 6.8 Interconnection of Three phases

```
1 // Three-Phase Circuits :example 6.8 :( pg 6.14)
2 VL=440;
3 P=50*10^3;
4 IL=90;
5 Iph=IL/sqrt(3);
6 pf=(P/(sqrt(3)*VL*IL));
7 S=sqrt(3)*VL*IL;
8 printf("\nVL=440 V \nP=50kW \nIL=90 A");
9 printf("\nVL=Vph=%f V",VL); //For delta-connected
    load
10 printf("\nIph=IL/sqrt(3)=%f A",Iph);
11 printf("\nP=sqrt(3)*VL*IL*cos(phi)");
12 printf("\ncos(phi)=%f (lagging)",pf);
13 printf("\nS=sqrt(3)*VL*IL =%f VA",S);
```

Scilab code Exa 6.9 Interconnection of Three phases

```
1 // Three-Phase Circuits :example 6.9 :( pg 6.15)
```

```

2 IL=15;
3 P=11*10^3;
4 S=15*10^3;
5 VL=S/(sqrt(3)*IL);
6 Vph=VL/sqrt(3);
7 x=P/S;
8 phi=acosd(P/S);
9 Q=sqrt(3)*VL*IL*sind(phi);
10 Iph=IL;
11 Zph=Vph/Iph;
12 R=Zph*cosd(phi);
13 XL=Zph*sind(phi);
14 Vph1=VL;
15 Iph1=(Vph1/Zph);
16 IL1=sqrt(3)*Iph1;
17 P1=sqrt(3)*VL*IL1*cosd(phi);
18 Q1=sqrt(3)*VL*IL1*sind(phi);
19 printf("\nIL=15 A \nP=11kW \nS=15kVA ");
20 //For a star-connected load
21 printf("\nS=sqrt(3)*VL*IL \nVL=%f V",Vph);
22 printf("\ncos(phi)=P/S =%f",x);
23 printf("\nphi=%f degrees",phi);
24 printf("\nQ=sqrt(3).VL.IL.sin(phi) = %f VAR",Q);
25 printf("\nIph=IL = %.f A",IL);
26 printf("\nZph=Vph/Iph = %.2f Ohm",Zph);
27 printf("\nR= Zph*cos(phi) =%.2f Ohm",R);
28 printf("\nXL=Zph*sin(phi)= %.2f Ohm",XL);
29 //If these coils are connected in Delta
30 printf("\nCph =VL =%.2f V",VL);
31 printf("\nZph= %.2f Ohm",Zph);
32 printf("\nIph=Vph/Zph =%.2f A ",Iph1);
33 printf("\nIL=sqrt(3)*Iph =%.f A",IL1);
34 printf("\nP=sqrt(3)*VL*IL*cos(phi) =%.2f W",P1);
35 printf("\nQ=sqrt(3)*VL*IL*sin(phi) =%.2f VAR",Q1);

```

Scilab code Exa 6.10 Interconnection of Three phases

```
1 // Three-Phase Circuits :example 6.10 :( pg 6.16)
2 P=1500*10^3;
3 pf=0.85;
4 VL=2.2*10^3;
5 phi=acosd(pf);
6 IL=P/(sqrt(3)*VL*pf);
7 Iph=IL/sqrt(3);
8 AC=Iph*pf;
9 RC=Iph*sind(phi);
10 IAC=IL*pf;
11 IRC=IL*sind(phi);
12 printf("\nP=1500kW \n pf=0.85 (lagging) \n VL=2.2kV");
13 //For Delta-connected load
14 printf("\nP=sqrt(3)*VL*IL*cos(phi) \n IL=%f A",IL);
15 printf("\nIph=IL/sqrt(3)= %f A",Iph);
16 //AC=Active Component
17 printf("\nAC=Iph*cos(phi) =%f A",AC); //in each
    phase of load
18 //RC=Reactive Component
19 printf("\nRC=Iph*sin(phi) =%f A",RC); //in each
    phase of load
20 //For star-connected source
21 printf("\nIAC =%f A",IAC); // current of AC in
    each phase of source
22 printf("\nIRC =%f A",IRC); // current of RC in
    each phase of source
```

Scilab code Exa 6.11 Interconnection of Three phases

```
1 // Three-Phase Circuits :example 6.11 :( pg 6.16)
2 VL=208;
3 P=1800;
4 IL=10;
```

```

5 Vph=VL/sqrt(3);
6 Zph=(Vph/IL);
7 pf=P/(sqrt(3)*VL*IL);
8 phi=acosd(pf);
9 Rph=Zph*pf;
10 Xph=Zph*sind(phi);
11 printf("\nVL=208 V \nP=1800 W \nIL= 10 A");
12 //For a Wye-connected load ,
13 printf("\nVph = VL/sqrt(3) =%.2f V",Vph);
14 printf("\nIph = IL =%.f A",IL);
15 printf("\nZph=Vph/Iph =%.2f Ohm",Zph);
16 printf("\nP=sqrt(3)*VL*IL*cos(phi)");
17 printf("\ncos(phi)=%.1f degrees",pf);
18 printf("\nphi=%.f degrees",phi);
19 printf("\nRph=Zph*cos(phi) =%.2f Ohm",Rph);
20 printf("\nXph=Zph*sin(phi) =%.2f Ohm",Xph);

```

Scilab code Exa 6.12 Interconnection of Three phases

```

1 // Three-Phase Circuits :example 6.12 :( pg 6.17)
2 P=100*10^3;
3 IL=80;
4 VL=1100;
5 f=50;
6 Vph=(VL/sqrt(3));
7 Iph=IL;
8 Zph=(Vph/Iph);
9 pf=(P/(sqrt(3)*VL*IL));
10 phi=acosd(pf);
11 Rph=Zph*pf;
12 Xph=Zph*sind(phi);
13 C=(1/(2*pi*f*Xph));
14 printf("\nP=100kW \nIL=80 A \nVL=1100 V \nf=50 Hz");
15 //For a star-connected load
16 printf("\nVph =V/sqrt(3) =%.2f",Vph);

```

```

17 printf("\nIph=IL =%. f A", Iph);
18 printf("\nZph=(Vph/Iph)= %.2 f Ohm", Zph);
19 printf("\nP=sqrt(3)*VL*IL*cos(phi)");
20 printf("\ncos(phi)=%.3 f (leading)", pf);
21 printf("\nphi=%. f degrees", phi);
22 printf("\nRph=Zph*cos(phi) =%.2 f Ohm", Rph);
23 printf("\nXph =Zph*sin(phi) =%. f Ohm", Xph);
24 // as current is leading ,reactance will be
    capacitive in nature
25 printf("\nXC=(1/2*pi*C)");
26 printf("\nC=%e F", C);

```

Scilab code Exa 6.13 Interconnection of Three phases

```

1 // Three-Phase Circuits :example 6.13 :( pg 6.17 &
   6.18)
2 VL=400;
3 IL=34.65;
4 P=14.4*10^3;
5 Iph=(IL/sqrt(3));
6 Zph=(VL/Iph);
7 pf=(P/(sqrt(3)*VL*IL));
8 phi=acosd(pf);
9 Rph=(Zph*pf);
10 Xph=(Zph*sind(phi));
11 printf("\nVL=400 V \nIL=34.65 A \nP=14.4kW");
12 //For a Delta-connected load
13 printf("\nVL=Vph=%. f V", VL);
14 printf("\nIph=IL/sqrt(3)=%. f A", Iph);
15 printf("\nZph=Vph/Iph =%. f Ohm", Zph);
16 printf("\ncos(phi)=P/sqrt(3).VL.IL =%.1 f", pf);
17 printf("\nphi=%.2 f degrees", phi);
18 printf("\nRph=Zph.cos(phi) =%. f Ohm", Rph);
19 printf("\nXph=Zph.sin(phi)=%. f Ohm", Xph);

```

Scilab code Exa 6.14 Interconnection of Three phases

```
1 // Three-Phase Circuits :example 6.14 :( pg 6.18)
2 P=10.44*10^3;
3 VL=200;
4 pf=0.5;
5 x=acosd(pf);
6 IL=(P/(sqrt(3)*VL*pf));
7 Iph=(IL/sqrt(3));
8 Zph=(VL/Iph);
9 Rph=(Zph*pf);
10 Xph=(Zph*sind(x));
11 Q=(sqrt(3)*VL*IL*sind(x));
12 printf("\nP=10.44kW \nVL=200 V \nnpf=0.5(leading)");
13 // For a delta-connected load,
14 printf("\nVL=Vph=%f V",VL);
15 printf("\nP=qrt(3)*VL*IL*cos(phi) \nIL=%f A",IL);
16 printf("\nIph=IL/sqrt(3)=%f A",Iph);
17 printf("\nZph=Vph/Iph=%f Ohm",Zph);
18 printf("\nRph =Zph.cos(phi)=%f Ohm",Rph);
19 printf("\nXph=Zph.sin(phi)=%f Ohm",Xph);
20 printf("\nQ=sqrt(3)*VL*IL*sin(phi) = %f VAR",Q);
```

Scilab code Exa 6.17 Interconnection of Three phases

```
1 // Three-Phase Circuits :example 6.17 :( pg 6.20)
2 Po=200*10^3;
3 f=50;
4 VL=440;
5 N=0.91;
6 pf=0.86;
7 phi=acosd(pf);
```

```

8 Pi=(Po/N);
9 IL=(Pi/(sqrt(3)*VL*pf));
10 Iph=(IL/sqrt(3));
11 AC=(Iph*pf);
12 RC=(Iph*sind(phi));
13 printf("\nPo=200 kW \nf=50Hz \nVL= 440 V \nN=0.91 \
    npf=0.86");
14 //For a delta connected load (induction motor)
15 printf("\nVph =VL =%.f V",VL);
16 printf("\nN=(Po/Pi)"); //efficiency
17 printf("\nPi=%.f W",Pi); //Input power
18 printf("\nPi=sqrt(3)*VL*IL*cos(phi) \nIL=%.1f A",IL)
    ;
19 printf("\nAC = (Iph*cos(phi))=%.1f A",AC); //Active
    component of phase current
20 printf("\nRC=(Iph*sin(phi)) =%.1f A",RC); //Reactive
    component of phase current

```

Scilab code Exa 6.18 Interconnection of Three phases

```

1 // Three-Phase Circuits :example 6.18 :( pg 6.20)
2 VL=400;
3 Po=112*10^3;
4 pf=0.86;
5 phi=acosd(pf);
6 N=0.88; //Efficiency
7 Pi=(Po/N);
8 IL=(Pi/(sqrt(3)*VL*pf));
9 Iph=(IL/sqrt(3));
10 AC=(Iph*pf);
11 RC=(Iph*sind(phi));
12 Aac=(IL*pf);
13 Arc=(IL*sind(phi));
14 printf("\nVL=400 V \nPo=112kW \npf=0.86 \nN=0.88");
15 //For a mesh-connected load (induction motor)

```

```

16 printf("\nVph=VL=%f V", VL);
17 printf("\nN=Po/Pi \nPi=%f W", Pi); //Input power
18 printf("\nPi=sqrt(3)*VL*IL*cos(phi) \nIL=%f A", IL)
    ;
19 printf("\nIph=IL/sqrt(3) =%f A", Iph);
20 //current in star-connected load=line current drawn
    by motor
21 printf("\nIA=%f A", IL); //current in alternate
    phase
22 printf("\nAC=Iph*cos(phi) =%f A", AC); //active
    component in each phase of motor
23 printf("\nRC=Iph*sin(phi) =%f A", RC); //Reactive
    component in each phase of motor
24 printf("\nAac=%f A", Aac); //active component in
    each alternate phase
25 printf("\nArc=%f A", Arc); //reactive component in
    each alternate phase

```

Scilab code Exa 6.19 Interconnection of Three phases

```

1 // Three-Phase Circuits :example 6.19 :( pg 6.21 &
    6.22)
2 VL=400;
3 IL=5;
4 Vph=(VL/sqrt(3));
5 Zph=(Vph/IL);
6 Iph=(IL/sqrt(3));
7 Vph1=(Iph*Zph);
8 printf("\nVl=400 V \nIL=5 A");
9 //For a star-connected load
10 printf("\nVph=VL/sqrt(3) =%f V", Vph);
11 printf("\nIph=IL=%f A", IL);
12 printf("\nZph=Rph=Vph/Iph =%f Ohm", Zph);
13 //For a delta connected load
14 printf("\nIL=5 A \nRph=%f Ohm", Zph);

```

```

15 printf("\nIph=IL/sqrt(3)=%f A", Iph);
16 printf("\nVph=Iph*Rph \n=%f V", Vph1);
17 //Voltage needed is 1/3 of the star value

```

Scilab code Exa 6.20 Interconnection of Three phases

```

1 // Three-Phase Circuits :example 6.20 :( pg 6.22 &
6.23)
2 VL=400;
3 Zph=100;
4 Vph=(VL/sqrt(3));
5 Iph=(Vph/Zph);
6 pf=1;
7 P=(sqrt(3)*VL*Iph*pf);
8 Iph1=(VL/Zph);
9 IL1=(sqrt(3)*Iph1);
10 P1=(sqrt(3)*VL*IL1*pf);
11 I1=(VL/200);
12 Pa=(VL*I1);
13 I2=(VL/100);
14 Pb=(VL*I1*I2);
15 printf("\nVL=400 V \nZph = 100 Ohm");
16 //For a star connected load
17 printf("\nVph=VL/sqrt(3) =%f V", Vph);
18 printf("\nIph = VL/Zph =%f A", Iph);
19 printf("\nIL=Iph =%f A", IL1);
20 printf("\ncos(phi)=1 \nP=sqrt(3).VL.IL.cos(phi) =%f W", P);
21 //For a delta connected load
22 printf("\nVph=VL=%f V", VL);
23 printf("\nIph=Vph/Zph =%f A", Iph1);
24 printf("\nIL=sqrt(3)*Iph =%f A", IL1);
25 printf("\nP=sqrt(3)*VL*IL*cos(phi) =%f W", P1);
26 //When resistors are open circuited
27 // (i) Star connection

```

```

28 printf("\nI= %.f A", I1); //Current in lines
29 printf("\nP=% .f W", Pa); //Power taken from mains
30 // (ii) Delta connection
31 printf("\nI= %.f A", I2); //Current in each phase
32 printf("\nP=% .f W", Pb); //Power taken from mains

```

Scilab code Exa 6.27 Measurement of three phase power

```

1 // Three-Phase Circuits :example 6.27 :( pg 6.30 &
   6.31)
2 W1=2000;
3 W2=500;
4 W3=-500;
5 x=sqrt(3)*((W1-W2)/(W1+W2));
6 phi=atand(x);
7 pf=cosd(phi);
8 y=sqrt(3)*((W1-W3)/(W1+W3));
9 phi1=atand(y);
10 pf1=cosd(phi1);
11 printf("\nW1 = 2000W \nW2 = 500 W");
12 // (i) When both readings are same
13 printf("\nWhen W1 &W2 are same \nW1 = 2000W \nW2 =
      500 W");
14 printf("\ntan(phi)= sqrt(3) .(W1-W2/W1+W2) =%.3f ",x)
      ;
15 printf("\nphi=%.3f degrees",phi);
16 printf("\npf=cos(phi)=%.3f ",pf); //Power factor
17 // (ii) When the latter reading is obtained after
      reversing the connection to the current coil of 1
      instrument
18 printf("\nWhen W2 is reversed \nW1= 2000 W \nW2=
      -500 W");
19 printf("\ntan(phi)= sqrt(3) .(W1-W2/W1+W2) =%.3f ",y)
      ;
20 printf("\nphi=%.2f degrees",phi1);

```

```
21 printf("\n pf=cos(phi)=%f",pf); //Power factor
```

Scilab code Exa 6.28 Measurement of three phase power

```
1 // Three-Phase Circuits :example 6.28 :( pg 6.31)
2 W1=5*10^3;
3 W2=-(0.5*10^3);
4 P=(W1+W2);
5 x=sqrt(3)*((W1-W2)/(W1+W2));
6 phi=atand(x);
7 pf=cosd(phi);
8 printf("\nW1=5kW \W2=0.5kW");
9 // When the latter readings are obtained after the
   reversal of the current coil terminals of the
   wattmeter
10 printf("\nWhen W2 is reversed \nW1=5kW \nW2=-0.5kW")
11 ;
11 printf("\nP=W1+W2 = %f W",P); //Power
12 printf("\ntan(phi)=sqrt(3)*(W1-W2/W1+W2)=%f",x);
13 printf("\nphi= %f degrees ",phi);
14 printf("\n pf=cos(phi)=%f",pf); //Power factor
```

Scilab code Exa 6.29 Measurement of three phase power

```
1 // Three-Phase Circuits :example 6.29 :( pg 6.31)
2 S=10*10^3;
3 pf=0.342;
4 x=(S/sqrt(3));
5 phi=acosd(pf);
6 W1=x*cosd(30+phi);
7 W2=x*cosd(30-phi);
8 printf("\nS=10kVA \n pf=0.342 \n S=sqrt(3)*VL*IL");
9 printf("\n VL*IL=%f VA",x);
```

```

10 printf("\ncos(phi)=%f",pf);
11 printf("\nphi=%f degrees",phi);
12 // (i) when power factor is leading
13 printf("\nPF leading \nW1=VL*IL*cos(30+phi)= %f W",W1);
14 printf("\n \nW2=VL*IL*cos(30-phi)= %f W",W2);
15 // (i) when power factor is lagging
16 printf("\nPF lagging \nW1=VL*IL*cos(30-phi)= %f W",W2);
17 printf("\n \nW2=VL*IL*cos(30+phi)= %f W",W1);

```

Scilab code Exa 6.30 Measurement of three phase power

```

1 // Three-Phase Circuits :example 6.30 :( pg 6.31 &
2 // 6.32)
3 VL=2000;
4 N=0.9; //efficiency
5 W1=300*10^3;
6 W2=100*10^3;
7 P=W1+W2;
8 x=sqrt(3)*((W1-W2)/(W1+W2));
9 phi=atand(x);
10 pf=cosd(phi);
11 IL=(P/(sqrt(3)*VL*pf));
12 printf("\nVL=2000 V \nN=0.9 \nW1=300kW \nW2=100kW");
13 printf("\nP=W1+W2 =%f W",P); //Input Power
14 printf("\ntan(phi)=(sqrt(3)*(W1-W2/W1+W2)) =%f",x);
15 printf("\nphi=%f degrees ",phi);
16 printf("\ncos(phi)=%f",pf); //Power factor
17 printf("\nP=sqrt(3)*VL*IL*cos(phi) \nIL=%f A",IL);

```

Scilab code Exa 6.31 Measurement of three phase power

```

1 // Three-Phase Circuits :example 6.31 :( pg 6.32)
2 VL=220;
3 Po=11.2*10^3;
4 N=0.88; // efficiency
5 IL=38;
6 Pi=(Po/N);
7 x=(Pi/(sqrt(3)*VL*IL));
8 phi=acosd(x);
9 W1=(VL*IL*cosd(30-phi));
10 W2=(VL*IL*cosd(30+phi));
11 printf("\nVL=220 V \nPo=11.2kW \nN=0.88 \nIL=38A \n
        =(Po/Pi)= %.2f W",Pi);
12 printf("\nPi=sqrt (3)*VL*IL*cos (phi) \ncos (phi)=%.2f
        lagging",x);
13 printf("\nphi=%.2f degrees",phi);
14 printf("\nW1 =VL*IL*cos(30-phi) =%.2f W",W1);
15 printf("\nW2 =VL*IL*cos(30+phi) =%.2f W",W2);

```

Chapter 7

Graph Theory

Scilab code Exa 7.7 Graph of a Network

```
1 // Graph Theory : example 7.7 : (pg 7.18 & 7.19)
2 //Complete incidence matrix Aa
3 printf("\nAa=");
4 disp(Aa=[1 0 0 -1 1 0 0 0;-1 1 0 0 0 1 0 0;0 -1 1 0
          0 0 1 0;0 0 -1 1 0 0 0 1;0 0 0 0 -1 -1 -1 -1]);
5 //eliminating last row from Aa
6 printf("\nA=");
7 disp(A=[1 0 0 -1 1 0 0 0;-1 1 0 0 0 1 0 0;0 -1 1 0 0
          0 1 0;0 0 -1 1 0 0 0 1]);
8 //Tieset matrix B
9 printf("\ntwigs={1,3,5,7} \nlinks={2,4,6,8} \ntieset
          2={2,7,5,1} \ntieset 4={4,5,7,3} \ntieset
          6={6,5,1} \ntieset 8={8,7,3}");
10 // forward direction = 1, reverse direction = -1
11 printf("\nB=");
12 disp(B=[1 1 0 0 -1 0 1 1;0 0 1 1 1 0 -1 0;1 0 0 0 -1
          1 0 0;0 0 1 0 0 0 -1 1]);
13 // f-cutset matrix Q
14 printf("\nf-cutset 1={1,6,2} \nf-cutset 3={3,4,8} \
          nf-cutset 5={5,4,6,2} \nf-cutset 7={7,2,8,4}");
15 printf("\nQ=");
```

```
16 disp(Q=[1 -1 0 0 0 -1 0 0 0;0 0 1 -1 0 0 0 -1;0 1 0 -1  
1 1 0 0;0 -1 0 1 0 0 1 1]);
```

Scilab code Exa 7.8 Graph of a Network

```
1 // Graph Theory : example 7.8 :( pg 7.19 & 7.20)  
2 //Complete Incidence Matrix Aa  
3 printf("\nAa=");  
4 disp(Aa=[1 0 -1 1;-1 1 0 0;0 -1 1 -1]);  
5 // Reduced Incidence matrix A (by eliminating last  
row from Aa)  
6 A=[1 0 -1 1;-1 1 0 0];  
7 printf("\nA=");  
8 disp(A=[1 0 -1 1;-1 1 0 0]);  
9 printf("\nNumber of possible trees=|A*A^T|"); //A^T=A  
'= transpose of A  
10 x=(A*A');  
11 disp(x);  
12 printf("\n|A*A^T|="); //determinant of A  
13 disp(det(x));
```

Scilab code Exa 7.11 Graph of a Network

```
1 // Graph Theory : example 7.11 :( pg 7.21 & 7.22)  
2 printf("\nAa=");  
3 disp(Aa=[0 -1 1 0 0 0;0 0 -1 -1 -1;-1 0 0 0 1;1 1 0 1  
0]); //Complete incidence matrix  
4 A=[0 -1 1 0 0 ;0 0 -1 -1 -1;-1 0 0 0 1]; //Reduced  
incidence matrix  
5 printf("\nNumber of possible trees = |A*A^T|"); //A^T  
=A'=transpose of A  
6 x=(A*A');  
7 disp(x);
```

```

8  det(x);
9  printf("\n|A*A^T|=%f",det(x)); //No. of possible
   trees
10 //Tieset Matrix B
11 printf("\ntwigs={3,4,5} \nlinks={1,2} \ntieset
   1={1,4,5} \ntieset 2={2,3,4}"); 
12 printf("\nB=");
13 disp(B=[1 0 0 -1 1;0 1 1 -1 0]);
14 //f-cutset Matrix Q
15 printf("\nf-cutset 3={3,2} \nf-cutset 4={4,2,1} \nf-
   cutset 5={5,1}"); 
16 printf("\nQ=");
17 disp(Q=[0 -1 1 0 0;1 1 0 1 0;-1 0 0 0 1]);

```

Scilab code Exa 7.14 Network Equilibrium Equation

```

1 //Graph Theory : example 7.14 :( pg 7.37 & 7.38)
2 //Tieset Matrix B
3 printf("\ntieset1={1,4,5} \ntieset2={2,4,6} \ntieset
   ={3,5,6} \nB=");
4 B=[1 0 0 1 1 0;0 1 0 -1 0 -1;0 0 1 0 -1 1];
5 disp(B);
6 printf("\nThe KVL equation in matrix form \nB.Zb.(B^
   T).I1 = B.Vs-B.Zb.Is");
7 printf("\nB.Zb.(B^T).I1 = B.Vs \nZb="); //Is=0
8 Zb=diag([1,1,1,2,2,2]);
9 disp(Zb);
10 printf("\n(B^T)=");
11 disp(B');
12 Vs=[2;0;0;0;0;0];
13 printf("\nVs=");
14 disp(Vs);
15 printf("\nB.Zb=");
16 x=(B*Zb);
17 disp(x);

```

```

18 printf("\nB.Zb.(B^T)=");
19 y=(x*B');
20 disp(y);
21 printf("\nB.Vs=");
22 z=(B*Vs);
23 disp(z);
24 printf("\nLoad currents:");
25 M=[5 -2 -2;-2 5 -2;-2 -2 5];
26 H=inv(M);
27 N=[2;0;0];
28 X=H*N;
29 disp(X);
30 printf("\nI1=0.857 A \nI2=0.571 A \nI3=0.571 A");
31 printf("\nBranch currents:");
32 P=(B')*X;
33 disp(P); // Currents in amperes

```

Scilab code Exa 7.15 Network Equilibrium Equation

```

1 //Graph Theory : example 7.15 :( pg 7.38 & 7.39)
2 //Tieset Matrix B
3 printf("\ntieset1={1,4,6} \ntieset2={2,5,6} \ntieset
   ={3,5,4} \nB=");
4 B=[1 0 0 1 0 1;0 1 0 0 1 -1;0 0 1 -1 -1 0];
5 disp(B);
6 printf("\nThe KVL equation in matrix form \nB.Zb.(B^
   T).I1 = B.Vs-B.Zb.Is");
7 printf("\nB.Zb.(B^T).I1 = B.Vs \nZb="); // Is=0
8 Zb=diag([6,4,3,4,6,2]);
9 disp(Zb);
10 printf("\n(B^T)=");
11 disp(B');
12 Vs=[12;-6;-8;0;0;0];
13 printf("\nVs=");
14 disp(Vs);

```

```

15 printf("\nB.Zb=");
16 x=(B*Zb);
17 disp(x);
18 printf("\nB.Zb.(B^T)=");
19 y=(x*B');
20 disp(y);
21 printf("\nB.Vs=");
22 z=(B*Vs);
23 disp(z);
24 printf("\nLoad currents:");
25 M=[12 -2 -4;-2 12 -6;-4 -6 12];
26 H=inv(M);
27 N=[12;-6;-8];
28 X=H*N;
29 disp(X);
30 printf("\nI1=0.55 A \nI2=-0.866 A \nI3=-0.916 A")
;
```

Scilab code Exa 7.19 Network Equilibrium Equation

```

1 //Graph Theory : example 7.15 :( pg 7.34 & 7.35)
2 Q=[1 -1 0 0;0 -1 1 1];
3 printf("\nQ=");
4 disp(Q);
5 printf("\nThe KCL equation in matrix form is given
    by");
6 printf("\nQ.Yb.(Q^T).Vl=Q.Is-Q.Yb.Vs");
7 printf("\nQ.Yb.(Q^T).Vl=Q.Is"); //Vs=0
8 Yb=diag([5,5,5,10]);
9 Is=[-10;0;0;0];
10 printf("\nYb=");
11 disp(Yb);
12 printf("\n(Q^T)=");
13 disp(Q');
14 printf("\nIs=");
```

```

15 disp(Is); // current entering into nodes is taken as
             negative
16 x=(Q*Yb);
17 printf("\nQ. Yb=");
18 disp(x);
19 y=(x*Q');
20 printf("\nQ. Yb . (Q^T)=");
21 disp(y);
22 z=(Q*Is);
23 printf("\nQ. Is=");
24 disp(z);
25 printf("\nLoad voltages:");
26 M=[10 5;5 20];
27 P=inv(M);
28 N=[-10;0];
29 X=(P*N);
30 disp(X);
31 printf("\nv11=-1.14 V \nv12=0.28 V");

```

Scilab code Exa 7.20 Network Equilibrium Equation

```

1 //Graph Theory : example 7.20 :( pg 7.35 & 7.36)
2 printf("\nf-cutset1={1,4,5,6} \nf-cutset2={2,4,5} \
           nf-cutset3={3,4,6}");
3 Q=[1 0 0 -1 -1 1;0 1 0 -1 -1 0;0 0 1 -1 0 1];
4 printf("\nQ=");
5 disp(Q);
6 printf("\nThe KCL equation in matrix form is given
           by");
7 printf("\nQ. Yb . (Q^T) . Vl=Q. Is - Q. Yb . Vs");
8 printf("\nQ. Yb . (Q^T) . Vl=Q. Is"); // Is=0
9 Yb=diag([0.2,0.2,0.2,0.1,0.5,0.1]);
10 Vs=[910;0;0;0;0;0];
11 Is=[0;0;0;0;0;0];
12 printf("\nYb=");

```

```

13 disp(Yb);
14 printf("\nVs=");
15 disp(Vs);
16 printf("\nIs=");
17 disp(Is);
18 x=(Q*Yb);
19 printf("\nQ.Yb=");
20 disp(x);
21 y=(x*Q');
22 printf("\nQ.Yb.(Q^T)=");
23 disp(y);
24 z=(x*Vs);
25 printf("\nQ.Yb.Vs=");
26 disp(z);
27 printf("\nQ.Is=");
28 u=(Q*Is);
29 disp(Q*Is);
30 v=(u-z);
31 printf("\nQ.Is-Q.Yb.Vs=");
32 disp(v);
33 printf("\nLoad voltages:");
34 M=[0.9 0.6 0.2;0.6 0.8 0.1;0.2 0.1 0.3];
35 P=inv(M);
36 N=[-182;0;0];
37 X=(P*N);
38 disp(X);
39 printf("\nv11=-460 V \nv12=320 V \nv13=200 V");

```

Scilab code Exa 7.21 Network Equilibrium Equation

```

1 //Graph Theory : example 7.22 :( pg 7.38 & 7.39)
2 printf("\ntwigs={1,2} \nf-cutset1={1,4} \nf-cutset2
   ={2,3}");
3 Q=[1 0 0 -1;0 1 -1 0];
4 printf("\nQ=");

```

```

5  disp(Q);
6  printf("\nThe KCL equation in matrix form is given
      by");
7  printf("\nQ.*Yb.(Q^T).*Vl=Q.*Is-Q.*Yb.*Vs");
8  Yb=diag([0.25,0.5,0.25,0.5]);
9  Vs=[1;1;0;0];
10 Is=[0;0;0.5;-0.5];
11 printf("\nYb=");
12 disp(Yb);
13 printf("\n(Q^T)=");
14 disp(Q');
15 printf("\nVs=");
16 disp(Vs);
17 printf("\nIs=");
18 disp(Is);
19 x=(Q*Yb);
20 printf("\nQ.*Yb=");
21 disp(x);
22 y=(x*Q');
23 printf("\nQ.*Yb.(Q^T)=");
24 disp(y);
25 printf("\nQ.*Is=");
26 u=(Q*Is);
27 disp(Q*Is);
28 z=(x*Vs);
29 printf("\nQ.*Yb.*Vs=");
30 disp(z);
31 v=(u-z);
32 printf("\nQ.*Is-Q.*Yb.*Vs=");
33 disp(v);
34 printf("\nLoad voltages:");
35 M=[0.75 0;0 0.75];
36 P=inv(M);
37 N=[0.25;-1];
38 X=(P*N);
39 disp(X);
40 printf("\nv11=0.33 V \n v12=-1.33 V");
41 v12=-1.33;

```

```
42 v=1+v12;  
43 printf("\nV=%,.2f",v);
```

Chapter 8

Transient Analysis

Scilab code Exa 8.13 example13

```
1 // Transient analysis
2 //pg no - 8.17
3 //example no - 8.13
4 a=((10*30)/(10+30));
5 d=5/a;
6 b=0;
7 c=5*(20/30);
8 printf("iL(0-) = %.2f A", d);
9 printf("\nvb(0-) = %.f", b);
10 printf("\nva(0-) = %.2f V", c);
11 disp("Applying Kcl equations at t=0+");
12 disp(((va(0+)-5)/10)+(va(0+)/10)+(va(0+)-vb(0+))/20
      = 0); //equation 1
13 disp(((vb(0+)-va(0+))/20)+((vb(0+)-5)/10)+(2/3) = 0
      ); //equation 2
14 //solving 1 and 2
15 M=[0.25, -0.05; -0.05, 0.15];
16 N=[0.5, -0.167]';
17 O=inv(M);
18 X=O*N;
19 disp(X);
```

```
20 disp("va(0+)= 1.9 A");  
21 disp("vb(0+)= -0.477 A");
```

Scilab code Exa 8.14 example14

```
1 //Transient analysis  
2 //pg no - 8.17  
3 //example no - 8.13  
4 disp("va(0+) = 5V");  
5 disp("vb(0+) = 5V");  
6 disp("vb(0+) = 5V");  
7 disp("Writing KCL Equation at t=0+");  
8 disp("0.25*va(0+) = 0.75");  
9 x=(0.75)/(0.25);  
10 printf("va(0+) = %.f V", x);
```

Chapter 10

Network Functions

Scilab code Exa 10.35 Determination of Residue

```
1 // Network Functions : example 10.35 : (pg 10.35)
2 m=(2/(sqrt(2)*sqrt(10)));
3 a=90;
4 x=(a-atand(3)-atand(1));
5 printf("\nF(s) =(4s/s^2+2s+2) = 4s/(s+1-j)*(s+1-j)");
6 printf("\n At s=j2");
7 //pmag = phasor magnitudes
8 printf("\n|F(j2)|=Product of pmag from all zeros to
j2/Product of pmag from all poles to j2");
9 printf("\n = %.3f",m);
10 printf("\n f(w) = atand(2/0)-atand(3)-atand(1)= %.2f
degrees",x);
```

Scilab code Exa 10.36 Determination of Residue

```
1 // Network Functions : example 10.36 : (pg 10.35 &
10.36)
```

```
2 m=((5*sqrt(17))/(sqrt(20)*4));
3 a=90;
4 w=(atand(4)+atand(4/3)-(a)-atand(4/2));
5 printf("\nF(s) = (s+1)(s+3)/s(s+2))";
6 printf("\nAt s=j4");
7 //vmag = vector magnitudes
8 printf("\nProduct of vmag from all zeros to j4/
          Product of vmag from all poles to j4");
9 printf("\nm =%.2f",m);
10 printf("\nphi(w)= atand(4)+atand(4/3)-atand(4/0)-
           atand(4/2)");
11 printf("\n = %.2f degrees",w);
```

Chapter 11

Two Port Networks

Scilab code Exa 11.16 Two Port Parameters

```
1 //Two-Port Networks : example 11.16 :( pg11.39 )
2 V1s=25;
3 I1s=1;
4 I2s=2;
5 V1o=10;
6 V2o=50;
7 I2o=2;
8 h11=(V1s/I1s);
9 h21=(I2s/I1s);
10 h12=(V1o/V2o);
11 h22=(I2o/V2o);
12 printf("\nh11 = V1/I1 = %.f Ohm",h11); //when V2=0
13 printf("\nh21= I2/I1 = %.f",h21); //when V2=0
14 printf("\nh12 = V1/V2 = %.1f",h12); //when I1=0
15 printf("\nh22 = I2/V2 = %.2f mho",h22); //when I1=0
16 printf("\nth h-parameters are");
17 disp([h11 h12;h21 h22]);
```

Scilab code Exa 11.19 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.19 :( pg11.49 &
11.50)
2 Z11=20;
3 Z22=30;
4 Z12=10;
5 Z21=10;
6 dZ=((Z11*Z22)-(Z12*Z21));
7 Y11=(Z22/dZ);
8 Y12=(-Z12/dZ);
9 Y21=(-Z21/dZ);
10 Y22=(Z11/dZ);
11 A=(Z11/Z21);
12 B=(dZ/Z21);
13 C=(1/Z21);
14 D=(Z22/Z21);
15 printf("\nY-parameters");
16 printf("\nY11 = Z22/dZ = %.2f mho",Y11);
17 printf("\nY12 = -Z12/dZ = %.2f mho",Y12);
18 printf("\nY21 = -Z21/dZ = %.2f mho",Y21);
19 printf("\nY22 = Z11/dZ = %.2f mho",Y22);
20 printf("\n Y-parameters are:");
21 disp([Y11 Y12;Y21 Y22]); //Y-parameters in matrix
form
22 printf("\nABCD parameters");
23 printf("\nA = Z11/Z21 = %.f",A);
24 printf("\nB = dZ/Z21 = %.f",B);
25 printf("\nC = 1/Z21 = %.1f",C);
26 printf("\nD = Z22/Z21 = %.f",D);
27 printf("\n ABCD parameters are:");
28 disp([A B;C D]); //ABCD parameters in matrix form

```

Scilab code Exa 11.20 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.20 :( pg11.50 &
11.51)

```

```

2 a=0.5;
3 b=-0.2;
4 d=1
5 printf("\nI1 =0.5V1-0.2V2 \nI2=-0.2V1+V2");
6 printf("\n Y11 =I1/V1 =%.1f mho",a); //when V2 is 0
    in the 1st eqn
7 printf("\n Y21 =I2/V1 =%.1f mho",b); //when V2 is 0
    in the 1st eqn
8 printf("\n Y12 =I1/V2 =%.1f mho",b); //when V1 is 0
    in the 2nd eqn
9 printf("\n Y22 =I2/V2 =%.1f mho",d); //when V1 is 0 in
    the 2nd eqn
10 printf("\nY-parameters are");
11 disp([a b;b d]);
12 dY=((a*d)-(b*b));
13 Z11=(d/dY);
14 Z12=(-b/dY);
15 Z21=(-b/dY);
16 Z22=(a/dY);
17 A=(-d/b);
18 C=(-dY/b);
19 D=(-a/b);
20 printf("\n dY=Y11.Y22-Y12.Y21 =%.2f",dY);
21 printf("\n Z11 = Y22/dY = %.3f Ohm",Z11);
22 printf("\n Z12 = -Y12/dY = %.3f Ohm",Z12);
23 printf("\n Z21 = -Y21/-dY = %.3f Ohm",Z21);
24 printf("\n Z22 = Y11/dY = %.3f Ohm",Z22);
25 printf("\n Z-parameters :");
26 disp([Z11 Z12;Z21 Z22]);
27 printf("\n A = -Y22/Y21 =%.1f",A);
28 printf("\n B = -1/Y21 =%.1f",A);
29 printf("\n C = -dY/Y21 =%.1f",C);
30 printf("\n D = -Y11/Y21 =%.1f",D);
31 printf("\n ABCD parameters :");
32 disp([A A;C D]);

```

Scilab code Exa 11.22 Interrelationships between parameters

```
1 //Two-Port Networks : example 11.22 :( pg11.52 &
2   11.53)
3 printf("\nApplying KVL to Mesh 1 \nV1 = I1 - I3 -- -
4   -(i))";
5 printf("\nApplying KVL to Mesh 2 \nV2 = -4I2 + 2I3 -
6   -- -(ii))";
7 printf("\nApplying KVL to Mesh 3 \nI3 = (1/5)I1 +
8   (4/5)I2 -- -(iii))";
9 //substituting (iii) in (i) & (ii),we get
10 printf("\nV1 = (4/5)I1 - (4/5)I2 \nV2 = (2/5)I1 -
11   (12/5)I2");
12 printf("\nZ-parameters :");
13 a=4/5;b=-4/5;c=2/5;d=-12/5;
14 disp([a b;c d]);
15 dZ=(a*d)-(b*c);
16 Y11=(d/dZ);
17 Y12=(-b/dZ);
18 Y21=(-c/dZ);
19 Y22=(a/dZ);
20 printf("\nY-parameters are:");
21 printf("\ndZ = Z11.Z22 - Z12.Z21 = %.1f",dZ);
22 printf("\nY11 = Z22/dZ = %.1f mho",Y11);
23 printf("\nY12 = -Z12/dY = %.1f mho",Y12);
24 printf("\nY21 = -Z21/-dY = %.1f mho",Y21);
25 printf("\nY22 = Z11/dY = %.1f mho",Y22);
26 disp([Y11 Y12;Y21 Y22]);
```

Scilab code Exa 11.23 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.23 :( pg11.53 &
11.54)
2 printf("\nApplying KVL to Mesh 1 \nV1 = 4I1 - 2I3 -
--(i));
3 printf("\nApplying KVL to Mesh 2 \nV2 = 4I2 + 2I3 -
--(ii));
4 printf("\nApplying KVL to Mesh 3 \n-2I3 = I1 + I2 -
--(iii));
5 //substituting (iii) in (i) & (ii),we get
6 printf("\nV1 = 5I1 + I2 \nV2 = -I1 + 3I2");
7 printf("\nZ-parameters :");
8 a=5;b=1;c=-1;d=3;
9 disp([a b;c d]);
10 dZ=(a*d)-(b*c);
11 h11=(dZ/d);
12 h12=(b/d);
13 h21=(-c/d);
14 h22=(1/d);
15 printf("\ndZ = Z11.Z22 - Z12.Z21 = %.1f",dZ);
16 printf("\nh11 = dZ/Z22 = %.1f ",h11);
17 printf("\nh12 = Z12/Z22 = %.1f ",h12);
18 printf("\nh21 = -Z21/Z22 = %.1f ",h21);
19 printf("\nh22 = 1/Z22 = %.1f ",h22);
20 printf("\nh-parameters are :");
21 disp([h11 h12;h21 h22]);

```

Scilab code Exa 11.24 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.24 :( pg11.54 &
11.55)
2 printf("\nApplying KCL to Node 3 \nV3 = V2/3 -- -
--(i));
3 printf("\nI1 = 2V1 - (2/3)V2 -- -(ii)");
4 printf("\nI2 = 3V2 - (V2/3) = (8/3)V2 -- -(iii)")
;
```

```

5 //Comparing ( iii ) & ( ii ) ,we get
6 printf("\nY-parameters :");
7 a=2;b=(-2/3);c=0;d=(8/3);
8 disp([a b;c d]);
9 dY=((a*d)-(b*c));
10 Z11=(d/dY);
11 Z12=(-b/dY);
12 Z21=(c/dY);
13 Z22=(a/dY);
14 printf("\ndY=Y11.Y22-Y12.Y21 =%.1f",dY);
15 printf("\nZ11 = Y22/dY = %.1f Ohm",Z11);
16 printf("\nZ12 = -Y12/dY = %.1f Ohm",Z12);
17 printf("\nZ21 = -Y21/-dY = %.1f Ohm",Z21);
18 printf("\nZ22 = Y11/dY = %.1f Ohm",Z22);
19 printf("\nZ-parameters :");
20 disp([Z11 Z12;Z21 Z22]);

```

Scilab code Exa 11.25 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.25 :( pg11.55 &
11.56)
2 printf("\nApplying KCL to Node 1 \nI1 = (-3/2)V1 -
V2- -(i)");
3 printf("\nApplying KCL to Node 2 \nI2 = 2V1 + 2V2 -
-(ii)");
4 //observing ( i ) & ( ii )
5 printf("\nY-parameters :");
6 a=(-3/2);b=(-1);c=2;d=2;
7 disp([a b;c d]);
8 dY=((a*d)-(b*c));
9 Z11=(d/dY);
10 Z12=(-b/dY);
11 Z21=(-c/dY);
12 Z22=(a/dY);
13 printf("\ndY=Y11.Y22-Y12.Y21 =%.f",dY);

```

```

14 printf("\nZ11 = Y22/dY = %.f Ohm",Z11);
15 printf("\nZ12 = -Y12/dY = %.f Ohm",Z12);
16 printf("\nZ21 = -Y21/-dY = %.f Ohm",Z21);
17 printf("\nZ22 = Y11/dY = %.1f Ohm",Z22);
18 printf("\nZ-parameters :");
19 disp([Z11 Z12;Z21 Z22]);

```

Scilab code Exa 11.26 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.22 :( pg11.52 &
11.53)
2 printf("\nApplying KVL to Mesh 1 \nV1 = 2I1 + I2 -- -
-(i )";
3 printf("\nApplying KVL to Mesh 2 \nV2 = 10I1 + 11I2
-- -(ii )";
4 //observing (i) & (ii )
5 printf("\nV1 = (4/5)I1 - (4/5)I2 \nV2 = (2/5)I1 -
(12/5)I2");
6 printf("\nZ-parameters :");
7 a=2;b=1;c=10;d=11;
8 disp([a b;c d]);
9 dZ=(a*d)-(b*c);
10 Y11=(d/dZ);
11 Y12=(-b/dZ);
12 Y21=(-c/dZ);
13 Y22=(a/dZ);
14 printf("\nY-parameters are:");
15 printf("\ndZ = Z11.Z22 - Z12.Z21 = %.1f",dZ);
16 printf("\nY11 = Z22/dZ = %.1f mho",Y11);
17 printf("\nY12 = -Z12/dY = %.1f mho",Y12);
18 printf("\nY21 = -Z21/-dY = %.1f mho",Y21);
19 printf("\nY22 = Z11/dY = %.1f mho",Y22);
20 disp([Y11 Y12;Y21 Y22]);
21 h11=(dZ/d);
22 h12=(b/d);

```

```

23 h21=(-c/d);
24 h22=(1/d);
25 printf("\ndZ = Z11.Z22 - Z12.Z21 = %.1f",dZ);
26 printf("\nh11 = dZ/Z22 = %.1f Ohm ",h11);
27 printf("\nh12 = Z12/Z22 = %.1f ",h12);
28 printf("\nh21 = -Z21/Z22 = %.1f ",h21);
29 printf("\nh22 = 1/Z22 = %.1f mho",h22);
30 printf("\nh-parameters are:");
31 disp([h11 h12;h21 h22]);

```

Scilab code Exa 11.27 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.27 :( pg11.58)
2 printf("\nApplying KCL to Node 1 \nI1 = 4V1 - 3V2--(i)");
3 printf("\nApplying KCL to Node 2 \nI2 = -3V1 + 1.5V2--(ii)");
4 //observing (i) & (ii)
5 printf("\nY-parameters:");
6 a=4;b=(-3);c=(-3);d=1.5;
7 disp([a b;c d]);
8 dY=((a*d)-(b*c));
9 Z11=(d/dY);
10 Z12=(-b/dY);
11 Z21=(-c/dY);
12 Z22=(a/dY);
13 printf("\ndY=Y11.Y22-Y12.Y21 =%.f",dY);
14 printf("\nZ11 = Y22/dY = %.f Ohm",Z11);
15 printf("\nZ12 = -Y12/dY = %.f Ohm",Z12);
16 printf("\nZ21 = -Y21/-dY = %.f Ohm",Z21);
17 printf("\nZ22 = Y11/dY = %.1f Ohm",Z22);
18 printf("\nZ-parameters :");
19 disp([Z11 Z12;Z21 Z22]);

```

Scilab code Exa 11.28 Interrelationships between parameters

```
1 //Two-Port Networks : example 11.28 :( pg11.58 &
2   11.59)
3 printf("\nApplying KCL to Node 1 \nI1 = 1.5V1 - 0.5
4 V2--(i));
5 printf("\nApplying KCL to Node 2 \nI2 = 4V1 - 0.5V2
6 ---(ii));
7 //observing (i) & (ii)
8 printf("\nY-parameters :");
9 a=1.5;b=(-0.5);c=(4);d=(-0.5);
10 disp([a b;c d]);
11 dY=((a*d)-(b*c));
12 Z11=(d/dY);
13 Z12=(-b/dY);
14 Z21=(-c/dY);
15 Z22=(a/dY);
16 printf("\ndY=Y11.Y22-Y12.Y21 =%. f",dY);
17 printf("\nZ11 = Y22/dY = %. f Ohm",Z11);
18 printf("\nZ12 = -Y12/dY = %. f Ohm",Z12);
19 printf("\nZ21 = -Y21/-dY = %. f Ohm",Z21);
20 printf("\nZ22 = Y11/dY = %.1 f Ohm",Z22);
21 printf("\nZ-parameters :");
22 disp([Z11 Z12;Z21 Z22]);
```

Scilab code Exa 11.29 Interrelationships between parameters

```
1 //Two-Port Networks : example 11.29 :( pg11.59 &
2   11.60)
3 printf("\nApplying KCL to Node 1 \nI1 = 3V1 - 2V2--(i));
```

```

3 printf("\nApplying KCL to Node 2 \nI2 = 3V2 - V3 --  

       -(ii));  

4 printf("\nApplying KCL to Node 3 \nV3 = (1/3)V2 --  

       -(ii));  

5 //substituting (iii) in (i) & (ii),we get  

6 printf("\nI1 = 3V1 - (2/3)V2 \nI2 = 0V1 + (8/3)V2");  

7 printf("\nY-parameters :");  

8 a=3;b=(-2/3);c=(0);d=(8/3);  

9 disp([a b;c d]);  

10 dY=((a*d)-(b*c));  

11 Z11=(d/dY);  

12 Z12=(-b/dY);  

13 Z21=(c/dY);  

14 Z22=(a/dY);  

15 printf("\ndY=Y11.Y22-Y12.Y21 =%.f",dY);  

16 printf("\nZ11 = Y22/dY = %.1f Ohm",Z11);  

17 printf("\nZ12 = -Y12/dY = %.1f Ohm",Z12);  

18 printf("\nZ21 = -Y21/-dY = %.f Ohm",Z21);  

19 printf("\nZ22 = Y11/dY = %.1f Ohm",Z22);  

20 printf("\nZ-parameters :");  

21 disp([Z11 Z12;Z21 Z22]);

```

Scilab code Exa 11.30 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.30 :( pg11.60 &  

   11.561)  

2 printf("\nApplying KVL to Mesh 1 \nV1 = 4I1 + (0.05)  

       I2 -- -(i));  

3 printf("\nApplying KVL to Mesh 2 \nV2 = 2I1 - 10I2 --  

       -(ii));  

4 //substituting (i) in (ii),  

5 printf("\nV2 = -40I1 + (1.5)I2");  

6 printf("\nZ-parameters :");  

7 a=4;b=0.05;c=-40;d=1.5;  

8 disp([a b;c d]);

```

```

9 dZ=(a*d)-(b*c);
10 Y11=(d/dZ);
11 Y12=(b/dZ);
12 Y21=(-c/dZ);
13 Y22=(a/dZ);
14 printf("\nY-parameters are:");
15 printf("\ndZ = Z11.Z22 - Z12.Z21 = %.1f",dZ);
16 printf("\nY11 = Z22/dZ = %.1f mho",Y11);
17 printf("\nY12 = -Z12/dY = %.1f mho",Y12);
18 printf("\nY21 = -Z21/-dY = %.1f mho",Y21);
19 printf("\nY22 = Z11/dY = %.1f mho",Y22);
20 disp([Y11 Y12;Y21 Y22]);

```

Scilab code Exa 11.31 Interrelationships between parameters

```

1 //Two-Port Networks : example 11.31 :( pg11.61 &
11.62)
2 printf("\nApplying KVL to Mesh 1 \nV1 = 3I1 + 5I2 -
--(i)");
3 printf("\nApplying KVL to Mesh 2 \nV2 = 2I1 + 4I2 -
2I3 ---(ii)");
4 printf("\nApplying KVL to Mesh 3 \nI3 = 2V3 ---(i
iii));
5 //substituting (iii) in (i) & (ii),we get
6 printf("\n2V3 = 4I1 + 4I2 \nV2 = -6I1 + 4I2");
7 printf("\nZ-parameters:");
8 a=3;b=5;c=-6;d=-4;
9 disp([a b;c d]);
10 dZ=(a*d)-(b*c);
11 Y11=(d/dZ);
12 Y12=(-b/dZ);
13 Y21=(-c/dZ);
14 Y22=(a/dZ);
15 printf("\nY-parameters are:");
16 printf("\ndZ = Z11.Z22 - Z12.Z21 = %.1f",dZ);

```

```
17 printf("\nY11 = Z22/dZ = %.1f mho",Y11);
18 printf("\nY12 = -Z12/dY = %.1f mho",Y12);
19 printf("\nY21 = -Z21/-dY = %.1f mho",Y21);
20 printf("\nY22 = Z11/dY = %.1f mho",Y22);
21 disp([Y11 Y12;Y21 Y22]);
```

Chapter 12

Network Synthesis

Scilab code Exa 12.2 Hurwitz Polynomials

```
1 // Network Synthesis : example 12.2 : (pg 12.2)
2 s=poly(0,'s');
3 p1=((s^4)+(5*(s)^2)+4);
4 p2=((s^3)+(3*s));
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
9 printf("\nEven part of P(s) = (s^4)+(5s^3)+4");
10 printf("\nOdd part of P(s) = (s^3)+(3s)");
11 printf("\nQ(s)= m(s)/n(s)");
12 // values of quotients in continued fraction
   expansion
13 disp(q);
14 disp(q1);
15 disp(q2);
16 disp(q3);
17 printf("\nSince all the quotient terms are positive ,
P(s) is hurwitz");
```

Scilab code Exa 12.3 Hurwitz Polynomial

```
1 // Network Synthesis : example 12.3 : (pg 12.2 &
2 s=poly(0, 's');
3 p1=((s^3)+(5*(s)));
4 p2=((4*s^2)+(2));
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 printf("\nEven part of P(s) = ((4*s^2)+(2))");
9 printf("\nOdd part of P(s) = ((s^3)+(5*(s)))");
10 printf("\nQ(s)= n(s)/m(s)");
11 // values of quotients in continued fraction
12 // expansion
12 disp(q);
13 disp(q1);
14 disp(q2);
15 printf("\nSince all the quotient terms are positive ,
P(s) is hurwitz");
```

Scilab code Exa 12.4 Hurwitz Polynomials

```
1 // Network Synthesis : example 12.4 : (pg 12.3)
2 s=poly(0, 's');
3 p1=((s^4)+(3*(s)^2)+12);
4 p2=((s^3)+(2*s));
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
```

```

9 printf("\nEven part of P(s) = ((s^4)+(3*(s)^2)+12)");
;
10 printf("\nOdd part of P(s) = ((s^3)+(2*s))");
11 printf("\nQ(s)= m(s)/n(s)");
12 // values of quotients in continued fraction
    expansion
13 disp(q);
14 disp(q1);
15 disp(q2);
16 disp(q3);
17 printf("\nSince two quotient terms are negative , P(s)
    is not hurwitz");

```

Scilab code Exa 12.5 Hurwitz Polynomials

```

1 // Network Synthesis : example 12.5 : (pg 12.3 &
   12.4)
2 s=poly(0,'s');
3 p1=((s^4)+(2*(s)^2)+2);
4 p2=((s^3)+(3*s));
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
9 printf("\nEven part of P(s) = ((s^4)+(2*(s)^2)+2)");
10 printf("\nOdd part of P(s) = (s^3)+(3s)");
11 printf("\nQ(s)= m(s)/n(s)");
12 // values of quotients in continued fraction
    expansion
13 disp(q);
14 disp(q1);
15 disp(q2);
16 disp(q3);
17 printf("\nSince two terms are negative , P(s) is not
    hurwitz");

```

Scilab code Exa 12.6 Hurwitz Polynomials

```
1 // Network Synthesis : example 12.6 : (pg 12.4)
2 s=poly(0, 's');
3 p1=((2*(s^4))+(6*(s)^2)+1);
4 p2=((5*(s^3))+(3*s));
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
9 printf("\nEven part of P(s) = ((2*s^4)+(6*(s)^2)+1)");
10 printf("\nOdd part of P(s) = ((5*s^3)+(3*s))");
11 printf("\nQ(s)= m(s)/n(s)");
12 // values of quotients in continued fraction
   expansion
13 disp(q);
14 disp(q1);
15 disp(q2);
16 disp(q3);
17 printf("\nSince all the quotient terms are positive ,
P(s) is hurwitz");
```

Scilab code Exa 12.7 Hurwitz Polynomials

```
1 // Network Synthesis : example 12.7 : (pg 12.4 &
   12.5)
2 s=poly(0, 's');
3 p1=((s^4)+(6*(s)^2)+8);
4 p2=(7*(s^3)+(21*s));
5 [r,q]=pdiv(p1,p2);
```

```

6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
9 printf("\nEven part of P(s) = ((s^4)+(6*(s)^2)+8)");
10 printf("\nOdd part of P(s) = (7*(s^3)+(21*s))");
11 printf("\nQ(s)= m(s)/n(s)");
12 // values of quotients in continued fraction
   expansion
13 disp(q);
14 disp(q1);
15 disp(q2);
16 disp(q3);
17 printf("\nSince all the quotient terms are positive ,
P(s) is hurwitz");

```

Scilab code Exa 12.8 Hurwitz Polynomials

```

1 // Network Synthesis : example 12.8 : (pg 12.5)
2 s=poly(0,'s');
3 p1=((s^4)+(5*(s)^2)+10);
4 p2=(5*(s^3)+(4*s));
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
9 printf("\nEven part of P(s) = ((s^4)+(5*(s)^2)+10)")
;
10 printf("\nOdd part of P(s) = (5*(s^3)+(4*s))");
11 printf("\nQ(s)= m(s)/n(s)");
12 // values of quotients in continued fraction
   expansion
13 disp(q);
14 disp(q1);
15 disp(q2);
16 disp(q3);

```

```
17 printf("\nSince two terms are negative , P(s) is not
        hurwitz");
```

Scilab code Exa 12.9 Hurwitz Polynomials

```
1 // Network Synthesis : example 12.9 : (pg 12.6)
2 s=poly(0, 's');
3 p1=((s^5)+(3*(s^3))+(2*s));
4 p2=((5*(s^4))+9*(s^2)+2);
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
9 [r4,q4]=pdiv(r2,r3);
10 printf("\n P(s) = ((s^5)+(3*(s^3))+(2*s))");
11 printf("\n d/ds.P(s)= ((5*(s^4))+9*(s^2)+2)");
12 printf("\nQ(s)=P(s)/d/ds.P(s)");
13 // values of quotients in continued fraction
     expansion
14 disp(q);
15 disp(q1);
16 disp(q2);
17 disp(q3);
18 disp(q4);
19 printf("\nSince all the quotient terms are positive ,
        P(s) is hurwitz");
```

Scilab code Exa 12.10 Hurwitz Polynomials

```
1 // Network Synthesis : example 12.10 : (pg 12.6 &
     12.7)
2 s=poly(0, 's');
3 p1=((s^5)+((s^3))+(s));
```

```

4 p2=((5*(s^4))+3*(s^2)+1);
5 [r,q]=pdiv(p1,p2);
6 [r1,q1]=pdiv(p2,r);
7 [r2,q2]=pdiv(r,r1);
8 [r3,q3]=pdiv(r1,r2);
9 [r4,q4]=pdiv(r2,r3);
10 printf("\\n P(s) = ((s^5)+((s^3))+(s))");
11 printf("\\n d/ds.P(s)= ((5*(s^4))+3*(s^2)+1)");
12 printf("\\nQ(s)=P(s)/d/ds.P(s)");
13 // values of quotients in continued fraction
   expansion
14 disp(q);
15 disp(q1);
16 disp(q2);
17 disp(q3);
18 disp(q4);
19 printf("\\nSince two quotient terms are negative , P(s)
   ) is not hurwitz");

```
