

# Scilab Textbook Companion for Electric Circuits

by M. Navhi And J. A. Edminister<sup>1</sup>

Created by  
Dhaivat Udayan Mandavia  
B.E. (pursuing)  
Electronics Engineering  
B. V. B. C. E. T., Hubli  
College Teacher  
Prof. Sujata Kotabagi, B. V. B. C. E. T., Hubli  
Cross-Checked by  
sonanya tatikola, IITB

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Electric Circuits

**Author:** M. Navhi And J. A. Edminster

**Publisher:** Tata McGraw - Hill Publishing Co. Ltd., New Delhi

**Edition:** 4

**Year:** 2007

**ISBN:** 0070601739

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 Introduction</b>	<b>6</b>
<b>2 Circuit Concepts</b>	<b>9</b>
<b>3 Circuit Laws</b>	<b>17</b>
<b>5 Analysis Methods</b>	<b>22</b>
<b>6 Amplifiers and Operational Amplifiers</b>	<b>27</b>
<b>7 Waveforms and Signals</b>	<b>33</b>
<b>8 First order Circuits</b>	<b>45</b>
<b>9 Higher order circuits and Complex frequency</b>	<b>57</b>
<b>10 Sinusoidal Steady state Circuit Analysis</b>	<b>66</b>
<b>11 AC Power</b>	<b>70</b>
<b>12 Polyphase Circuits</b>	<b>84</b>
<b>13 Frequency Response Filters and Resonance</b>	<b>90</b>

<b>14 Two Port Networks</b>	<b>93</b>
<b>15 Mutual Inductance and Transformers</b>	<b>100</b>
<b>17 The Laplace Transform Method</b>	<b>105</b>

# List of Scilab Codes

Exa 1.1	Force Work and Power . . . . .	6
Exa 1.2	Electric Charge and Current . . . . .	7
Exa 1.3	Electric Potential . . . . .	7
Exa 1.4	Energy and Electrical Power . . . . .	8
Exa 2.1	Resistance . . . . .	9
Exa 2.2	Inductance . . . . .	10
Exa 2.3	Capacitance . . . . .	12
Exa 2.4	Nonlinear Resistors . . . . .	14
Exa 2.5	Nonlinear Resistors . . . . .	15
Exa 3.3	Circuit elements in series . . . . .	17
Exa 3.4	Circuit elements in series . . . . .	17
Exa 3.5	Circuit elements in parallel . . . . .	18
Exa 3.6	Circuit elements in parallel . . . . .	19
Exa 3.7	Voltage division . . . . .	19
Exa 3.8	Current division . . . . .	20
Exa 5.8	Thevenin and Norton theorem . . . . .	22
Exa 6.8	Operational amplifiers . . . . .	27
Exa 6.10	Summing circuit . . . . .	28
Exa 7.1	Sinusoidal Functions . . . . .	33
Exa 7.2	Sinusoidal Functions . . . . .	35
Exa 7.3	Time Shift and Phase Shift . . . . .	36
Exa 7.5	Combinations of Periodic Functions . . . . .	37
Exa 7.13	The Average and Effective RMS values . . . . .	38
Exa 7.17	The Unit Impulse Function . . . . .	38
Exa 7.22	The Exponential Function . . . . .	40
Exa 7.23	The Exponential Function . . . . .	40
Exa 7.25	Random Signals . . . . .	42
Exa 7.26	Random Signals . . . . .	43

Exa 8.1	Capacitor Discharge in a Resistor . . . . .	45
Exa 8.10	Transitions at Switching Time . . . . .	54
Exa 9.6	Generalized Impedance RLC in s domain . .	58
Exa 9.7	Generalized Impedance RLC in s domain . .	60
Exa 9.8	Network function and Pole zero plots . . . .	64
Exa 9.9	The Forced Response . . . . .	65
Exa 9.11	The Natural Response . . . . .	65
Exa 10.4	Phasors . . . . .	66
Exa 10.5	Impedance and Admittance . . . . .	67
Exa 10.7	Superposition of AC sources . . . . .	68
Exa 11.1	Power in time domain . . . . .	70
Exa 11.2	Power in time domain . . . . .	71
Exa 11.4	Average or Real Power . . . . .	73
Exa 11.5	Reactive Power . . . . .	74
Exa 11.10	Complex power Apparent power and Power triangle . . . . .	74
Exa 11.11	Complex power Apparent power and Power triangle . . . . .	76
Exa 11.12	Parallel connected Networks . . . . .	77
Exa 11.13	Power factor improvement . . . . .	78
Exa 11.14	Power factor improvement . . . . .	78
Exa 11.16	Maximum power transfer . . . . .	79
Exa 11.17	Superposition of average powers . . . . .	81
Exa 12.2	Balanced Delta connected load . . . . .	84
Exa 12.5	Unbalanced Delta connected load . . . . .	86
Exa 12.6	Unbalanced Wye connected load . . . . .	87
Exa 13.2	High pass and Low pass networks . . . . .	90
Exa 13.7	Bandpass filters and Resonance . . . . .	91
Exa 13.8	Bandpass filters and Resonance . . . . .	92
Exa 14.1	Z parameters . . . . .	93
Exa 14.2	Reciprocal and non reciprocal networks . . .	94
Exa 14.4	Y parameters . . . . .	95
Exa 14.6	Conversion between Z and Y parameters . .	96
Exa 14.7	H parameters . . . . .	96
Exa 14.8	g parameters . . . . .	97
Exa 14.10	Choice of parameter type . . . . .	98
Exa 15.4	Energy in a pair of coupled coils . . . . .	100
Exa 15.7	Ampere Turn Dot rule . . . . .	101

Exa 15.8	Reflected Impedance . . . . .	102
Exa 15.9	Reflected Impedance . . . . .	103
Exa 17.2	Convergence of the integral . . . . .	105
Exa 17.4	Partial Fractions Expansions . . . . .	105

# List of Figures

2.1	Resistance . . . . .	11
2.2	Inductance . . . . .	13
2.3	Capacitance . . . . .	15
5.1	The branch current method . . . . .	23
5.2	The branch current method . . . . .	24
5.3	Network reduction . . . . .	25
5.4	Network reduction . . . . .	25
5.5	Superposition . . . . .	26
5.6	Superposition . . . . .	26
6.1	Analysis of circuits containing ideal op amps . . . . .	28
6.2	Analysis of circuits containing ideal op amps . . . . .	29
6.3	Noninverting circuit . . . . .	30
6.4	Noninverting circuit . . . . .	30
6.5	Circuits containing several Op amps . . . . .	31
6.6	Circuits containing several Op amps . . . . .	32
7.1	Sinusoidal Functions . . . . .	35
7.2	Sinusoidal Functions . . . . .	36
7.3	Time Shift and Phase Shift . . . . .	37
7.4	The Exponential Function . . . . .	41
7.5	The Exponential Function . . . . .	42
7.6	The Exponential Function . . . . .	43

8.1	Capacitor Discharge in a Resistor . . . . .	46
8.2	Capacitor Discharge in a Resistor . . . . .	47
8.3	Establishing a DC Voltage across a Capacitor . . . . .	48
8.4	Establishing a DC Voltage across a Capacitor . . . . .	48
8.5	The Source free RL Circuit . . . . .	49
8.6	The Source free RL Circuit . . . . .	49
8.7	Complex first order RL and RC Circuits . . . . .	50
8.8	Complex first order RL and RC Circuits . . . . .	50
8.9	Complex first order RL and RC Circuits . . . . .	51
8.10	Complex first order RL and RC Circuits . . . . .	52
8.11	DC Steady state in Inductors and Capacitors . . . . .	52
8.12	DC Steady state in Inductors and Capacitors . . . . .	53
8.13	DC Steady state in Inductors and Capacitors . . . . .	53
8.14	DC Steady state in Inductors and Capacitors . . . . .	54
8.15	Transitions at Switching Time . . . . .	55
8.16	Transitions at Switching Time . . . . .	55
9.1	Series RLC Circuit . . . . .	58
9.2	Series RLC Circuit . . . . .	59
9.3	Series RLC Circuit . . . . .	60
9.4	Series RLC Circuit . . . . .	61
9.5	Parallel RLC circuit . . . . .	62
9.6	Parallel RLC circuit . . . . .	63
11.1	Power in time domain . . . . .	71
11.2	Power in time domain . . . . .	72
11.3	Power in time domain . . . . .	73

# Chapter 1

## Introduction

### Scilab code Exa 1.1 Force Work and Power

```
1 clc
2 disp(" Example 1.1")
3 printf(" \n")
4 printf(" Given")
5 disp(" Acceleration is 2.0m/s^2")
6 disp(" Mass is 10kg")
7 m=10; a=2;
8 disp(" a")
9 disp(" F=m*a")
10 F=m*a
11 printf(" Force is %dN\n",F)
12 disp(" b")
13 printf(" time=4s\n")
14 t=4;
15 x=(a*t*t)/2
16 KE=(F*x)
17 P=KE/t
18 printf(" Position is %dm\n",x)
19 printf(" Kinetic energy =%3.1fJ\n",KE)
20 printf(" Power =%3.1fW\n",P)
```

---

### Scilab code Exa 1.2 Electric Charge and Current

```
1 clc
2 disp("Example 1.2")
3 printf("\\n")
4 printf("Given")
5 disp("Current flow is 5A")
6 disp("Time is 1 minute")
7 i=5;
8 //As electroms/min is asked so we need to convert A(
    C/s) to C/min
9 i1=5*60;
10 //Let e be electronic charge
11 e=1.602*10^-19
12 n=(i1/e)
13 printf("Number of electrons =%3.2f electrons/min\\n",
    n)
```

---

### Scilab code Exa 1.3 Electric Potential

```
1 clc
2 disp("Example 1.3")
3 printf("\\n")
4 printf("Given")
5 disp("Energy is 9.25 uJ")
6 disp("Charge to be transferred is 0.5uC")
7 E=9.25*10^-6;q=0.5*10^-6;
8 //1 volt is 1 joule per coulomb
9 V=E/q;
10 printf("Potential difference between two points a
    and b is %3.1fV\\n",V)
```

---

### Scilab code Exa 1.4 Energy and Electrical Power

```
1 clc
2 disp("Example 1.4")
3 printf("\\n")
4 printf("Given")
5 disp(" Potential difference is 50V")
6 disp("Charge per minute is 120C/min")
7 V=50;x=120;
8 //As Electrical energy is to be calculated charge
   per minute is to be converted in charge per
   second
9 //Charge per second is nothing but the current
10 i=x/60;
11 P=i*V;
12 //Since is 1W=1J/s
13 printf("Rate of energy conversion is %dJ/s\\n",P)
```

---

# Chapter 2

## Circuit Concepts

### Scilab code Exa 2.1 Resistance

```
1
2 disp("Example 2.1")
3 printf("\n")
4 printf("Given")
5 disp("Resistance used is 4 ohm")
6 disp("Current flow is i=2.5*sin(w*t)")
7 disp("Angular frequency (w)=500 rad/s")
8
9 R=4;
10 iamp=2.5;w=500;
11 t=0:0.001:0.012566
12 i=2.5*sin(w*t)
13
14
15 Vamp=iamp*R;
16 printf("v=%d*sin (%d*t) (V)\n",Vamp ,w)
17
18 pamp=iamp*iamp*R;
19 printf("p=%d( sin (%d*t) ) ^ 2(W)\n",pamp ,w)
20 p=pamp*sin(w*t)^2;
21
```

```

22 //On integrating p with respect to t
23 W=25*(t/2-sin(2*w*t)/(4*w))
24
25 function p=f(t),p=pamp*sin(w*t)^2, endfunction
26 w1=intg(0,2*pi/w,f);
27
28
29 subplot(221)
30 plot(t,i)
31 xtitle ('i vs wt', 'wt', 'i');
32
33 subplot(222)
34 plot(t,p)
35 xtitle ('p vs wt', 'wt', 'p');
36
37
38
39 subplot(223)
40 plot(t,W)
41 xtitle ('w vs wt', 'wt', 'w');

```

---

### Scilab code Exa 2.2 Inductance

```

1 clc
2 disp("Example 2.2")
3 printf("\n")
4 printf("Given")
5 disp("Inductance used is 30mH")
6 disp("Current flow is i=10*sin(50*t)")
7 L=30*10^-3; iamp=10;
8 t=0:0.01:0.06283;
9 i=10*sin(50*t)
10 //v=L*d/dt(i)

```

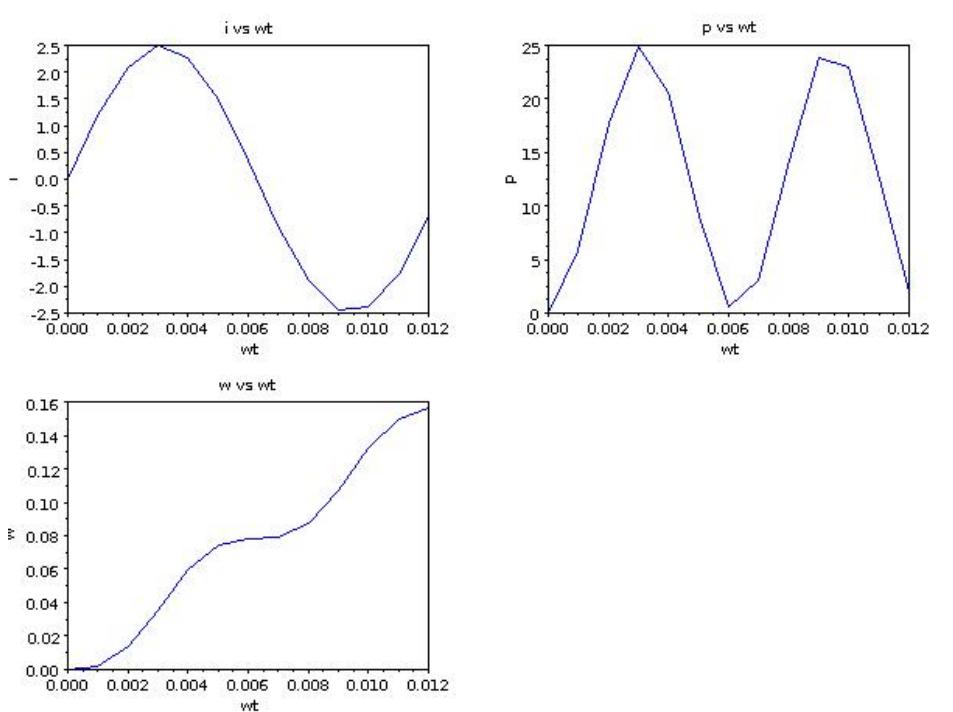


Figure 2.1: Resistance

```

11 //d/dt( sin 50t)=50*cos t
12 vamp=L*iamp*50;
13 v=vamp*cos(50*t)
14
15 //sinA*cosB=(sin (A+B)+sin (A-B))/2
16
17 pamp=vamp*iamp/2;
18 p=pamp*sin(100*t)
19 //On integrating 'p' w.r.t t
20
21 wL=0.75*(1-cos(100*t));
22
23
24 subplot(221)
25 plot(t,i)
26 xtitle ('i vs wt', 'wt', 'i');
27
28 subplot(222)
29 plot(t,v)
30 xtitle ('v vs wt', 'wt', 'v');
31
32 subplot(223)
33 plot(t,p)
34 xtitle ('p vs wt', 'wt', 'p');
35
36 subplot(224)
37 plot(t,wL)
38 xtitle ('wL vs wt', 'wt', 'wL');

```

---

### Scilab code Exa 2.3 Capacitance

```

1 clc
2 disp("Example 2.3")

```

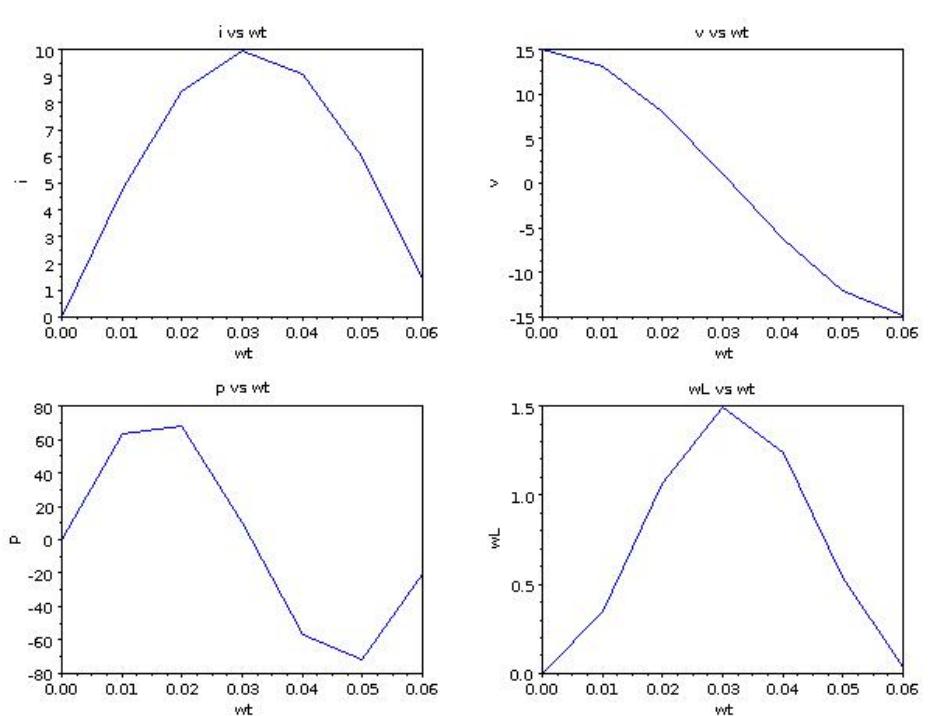


Figure 2.2: Inductance

```

3 printf("\n")
4 printf("Given")
5 disp("Capacitance used is 20uF")
6 disp("Voltage is v=50*sin(200*t)")
7 C=20*10^-6;
8 // Given that v=50*sin(200*t);
9 vamp=50;
10 t=0:0.001:0.015;
11 //q=C*v
12 qamp=vamp*C
13 q=qamp*sin(200*t)
14 //i=C*d/dt(v)
15 //d/dt(sin 200t)=200*cos t
16 iamp=C*vamp*200;
17 i=iamp*cos(200*t)
18
19 //sinA*cosB=(sin(A+B)+sin(A-B))/2
20
21 pamp=vamp*iamp/2;
22 p=pamp*sin(400*t)
23
24 //On integrating 'p' w.r.t t
25
26 wC=12.5*(1-cos(400*t));
27
28 figure
29 a= gca ();
30 plot(t,wC)
31 xtitle ('wC vs wt', 'wt', 'wC (mJ)');
32 a.thickness = 2;

```

---

### Scilab code Exa 2.4 Nonlinear Resistors

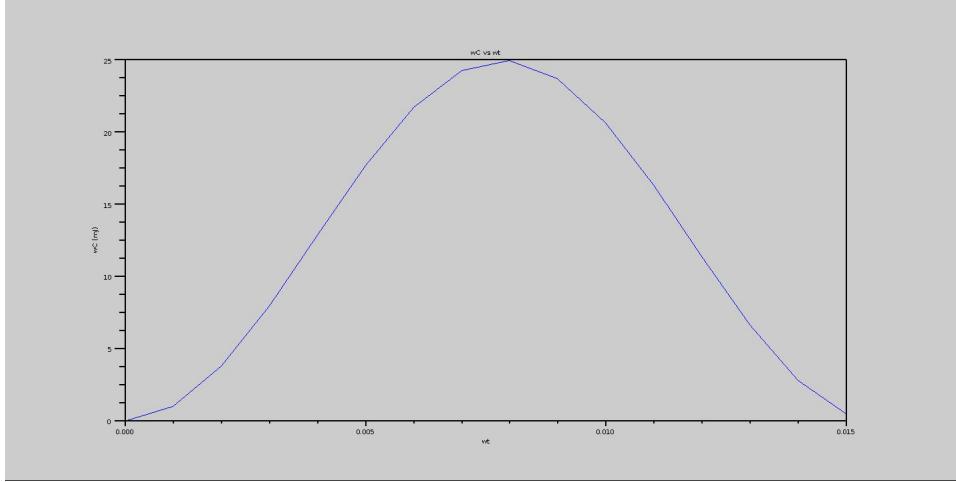


Figure 2.3: Capacitance

```

1 clc
2 disp(" Example 2.4 ")
3 printf(" \n")
4 printf(" Given")
5 disp(" Current through diode is 30mA")
6 //From the table the nearest value is at v=0.74V
7 V=0.74;I=28.7*10^-3;
8 R=V/I;
9 delV=0.75-0.73
10 delI=42.7*10^-3-19.2*10^-3
11 r=delV/delI
12 p=(V*I)*10^3
13 printf(" \n \n Static resistance is %3.2f ohm\n",R)
14 printf(" Dynamic resistance is %3.2f ohm\n",r)
15 printf(" Power consumption is %3.2fmW\n",p)

```

---

### Scilab code Exa 2.5 Nonlinear Resistors

```

1 clc
2 disp(" Example 2.5 ")

```

```

3 printf("\n")
4 printf("Given")
5 disp("a")
6 disp(" Current through diode is 10mA")
7 //From the table the value is at v=2.5V
8 V=2.5; I=10*10^-3;
9 R=V/I;
10 delV=3-2
11 delI=11*10^-3-9*10^-3
12 r=delV/delI
13 p=(V*I)*10^3
14 printf("\n \n Static resistance is %3.2f ohm\n",R)
15 printf("Dynamic resistance is %3.2f ohm\n",r)
16 printf("Power consumption is %3.2fmW\n",p)
17
18 disp("b")
19 disp(" Current through diode is 15mA")
20 //From the table the value is at v=5V
21 V=5; I=15*10^-3;
22 R=V/I;
23 delV=5.5-4.5
24 delI=16*10^-3-14*10^-3
25 r=delV/delI
26 p=(V*I)*10^3
27 printf("\n \n Static resistance is %3.2f ohm\n",R)
28 printf("Dynamic resistance is %3.2f ohm\n",r)
29 printf("Power consumption is %3.2fmW\n",p)

```

---

# Chapter 3

## Circuit Laws

Scilab code Exa 3.3 Circuit elements in series

```
1 clc
2 disp("Example 3.3")
3 printf("\n")
4 printf("Given")
5 disp("Equivalent resistance of three resistors is
    750 ohm")
6 disp("values of two resistors are 40 ohm and 410 ohm
    ")
7 Req=750;R1=40;R2=410;
8
9 //For series resistance
10 disp("Req=R1+R2+R3")
11 //On solving for R3
12 R3=Req-R1-R2
13 printf("Value of third ohmic resistor is %dohm\n",R3
)
```

---

Scilab code Exa 3.4 Circuit elements in series

```

1 clc
2 disp(" Example 3.4")
3 printf(" \n")
4 printf(" Given")
5 disp(" values of two capacitors are 2uF and 10uF")
6 C1=2*10^-6;C2=10*10^-6;
7 //For two capacitors in series
8 disp(" Ceq=(C1*C2)/(C1+C2)")
9 //On solving for Ceq
10 Ceq=((C1*C2)/(C1+C2))*10^6
11 printf(" Value of equivalent capacitance is %3.2fuF\n"
    ",Ceq)
12
13 disp(" If C2=10pF")
14 C2=10*10^-12;
15
16 Ceq=((C1*C2)/(C1+C2))*10^12
17 printf(" Value of equivalent capacitance is %3.2fpF\n"
    ",Ceq)

```

---

### Scilab code Exa 3.5 Circuit elements in parallel

```

1 clc
2 disp(" Example 3.5")
3 printf(" \n")
4 printf(" Given")
5 disp(" a")
6 disp(" values of two resistors are 60 ohm and 60 ohm"
    )
7 R1=60;R2=60;
8 disp(" If resistors are parallel")
9 Req=(R1*R2)/(R1+R2)
10 printf(" Value of equivalent resistance is %dohm\n",
    Req)
11

```

```
12 disp("b")  
13 disp(" values of three equal resistors are 60 ohm")  
14 R1=60;R2=60;R3=60;  
15 disp(" If resistors are parallel")  
16 x=1/R1+1/R2+1/R3  
17 Req=1/x;  
18 printf("Value of equivalent resistance is %dohm\n",  
Req)
```

---

### Scilab code Exa 3.6 Circuit elements in parallel

```
1 clc  
2 disp("Example 3.6")  
3 printf("\n")  
4 printf("Given")  
5  
6 disp(" values of two inductors are 3mH and 6 mH")  
7 L1=3*10^-3;L2=6*10^-3;  
8 disp(" If inductors are parallel")  
9 Leq=((L1*L2)/(L1+L2))*10^3  
10 printf("Value of equivalent inductance is %3.1fmH\n"  
,Leq)
```

---

### Scilab code Exa 3.7 Voltage division

```
1 clc  
2 disp("Example 3.7")  
3 printf("\n")  
4 printf("Given")  
5 disp(" Total resistance of three resistors is 50 ohm")  
6 R=50;
```

```

7 disp("Output voltage is 10 percent of the input
      voltage")
8 //Let v be input voltage and v1 be output voltage
9 //Let v1/v=V
10 V=0.1;
11 //As V=R1/(Total resistance)
12 //Solving for R1
13 R1=V*R;
14 //As R=R1+R2
15 //Solving for R2
16 R2=R-R1;
17 printf("R1=%dohm\n R2=%dohm\n",R1,R2)

```

---

### Scilab code Exa 3.8 Current division

```

1 clc
2 disp("Example 3.8")
3 printf("\n")
4 printf("Given")
5 disp("Total current is 30mA")
6 disp("Branch currents are 20mA and 10mA")
7 disp("Equivalent resistance is equal to or greater
      than 10 ohm")
8
9 //From Fig 3.6
10 //Current flowing through R1 be i1 and let it be
      equal to 10mA
11 //Current flowing through R2 be i2 and let it be
      equal to 20mA
12 i1=10*10^-3; i2=20*10^-3;
13 i=30*10^-3;
14
15 //Let R1/(R1+R2)=X1          (1)
16 //Let R2/(R1+R2)=X2          (2)
17 X1=i1/i;

```

```
18 X2=i2/i;
19 //Let R1*R2(R1+R2)=Y          (3)
20 //Given that
21 printf("\n Given")
22 disp("R1*R2(R1+R2)>=10")
23 //Solving (1),(2) and (3) we get
24 printf("R1>=%dohm\nR2>=%dohm\n",15,30)
```

---

# Chapter 5

## Analysis Methods

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 5.8 Thevenin and Norton theorem**

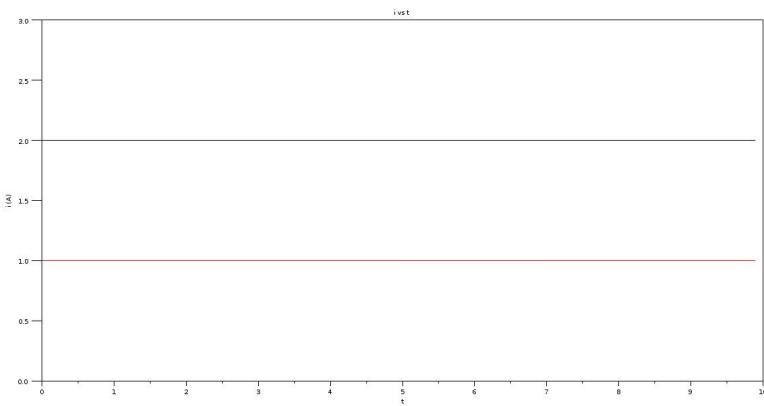


Figure 5.1: The branch current method

```

1 clc
2 //From figure 5.13(a)
3 //Applying KVL equation to the loop
4 I=(20+10)/(3+6)
5 //As current will not flow in upper 3 ohm resistor
   so Thevenin voltage is equal to either of the two
   parallel branches
6 V1=20-I*3
7 printf("Thevenin voltage = %dV\n",V1)
8
9 // Left 3 ohm and 6 ohm resistor are in parallel and
   their equivalent is in series with 3 ohm
10 R1=3+(3*6)/(3+6)
11 printf("Thevenin resistance =%dohm\n",R1)
12
13 //Now to find Norton's equivalent
14 I1=V1/R1
15 printf("\n Norton current =%dA\n",I1)
16 disp("The value of resistance in Norton equivalent
   will not change but will come in parallel with
   current source")

```

---

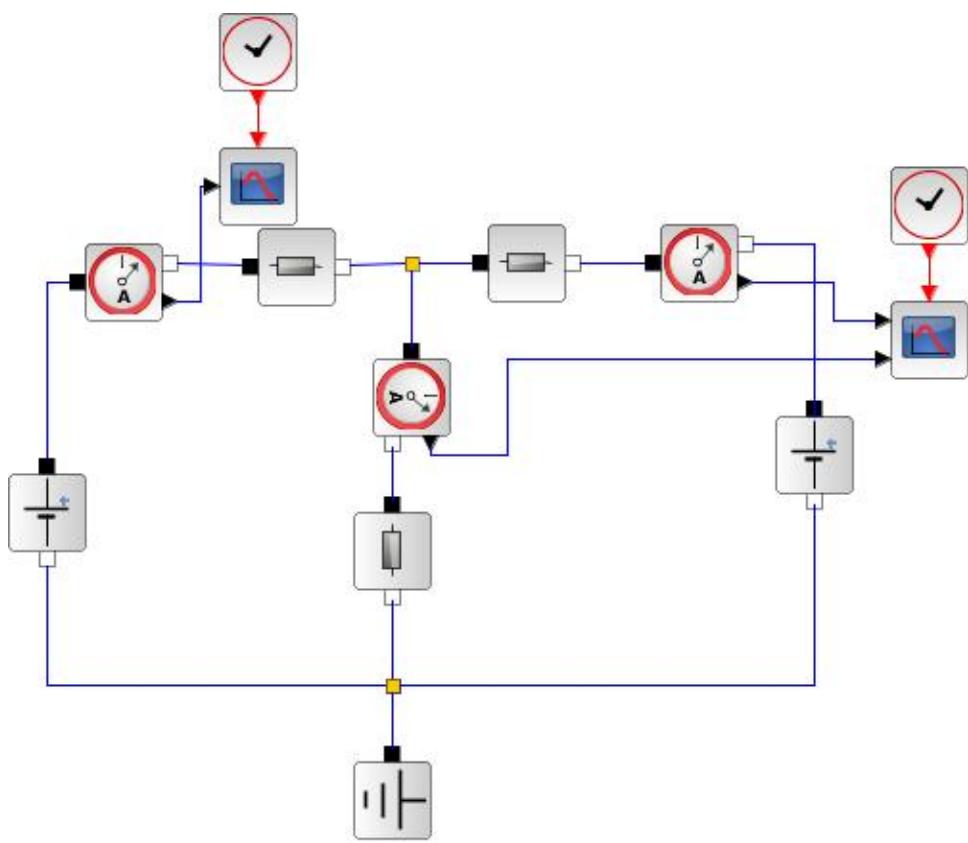


Figure 5.2: The branch current method

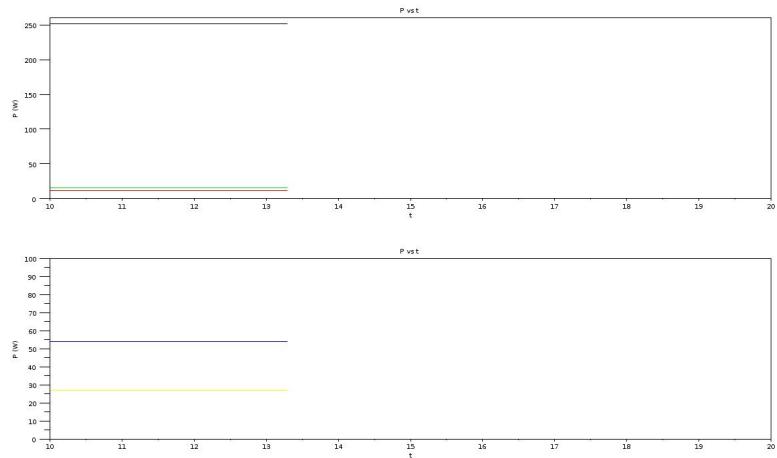


Figure 5.3: Network reduction

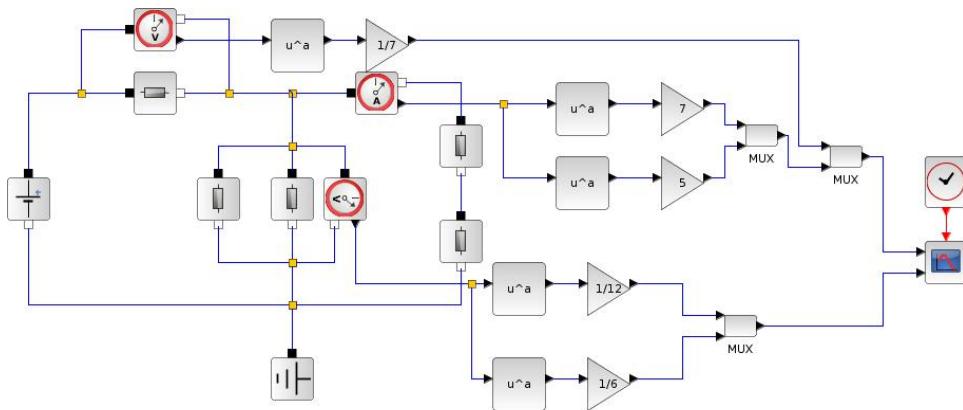


Figure 5.4: Network reduction

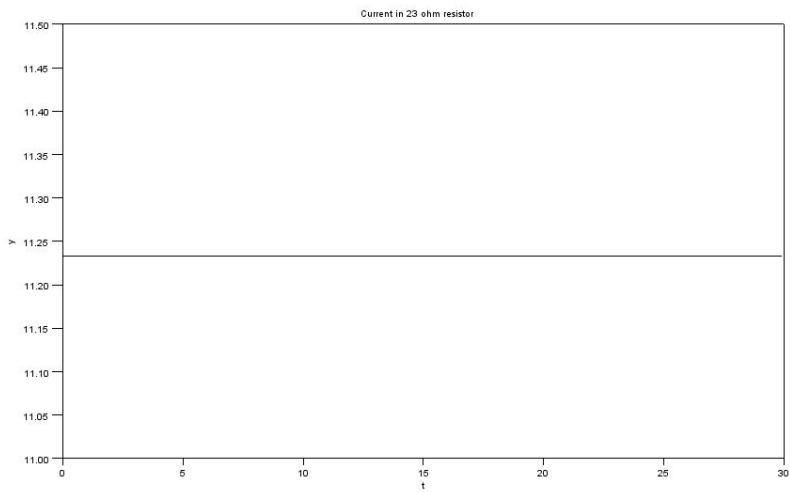


Figure 5.5: Superposition

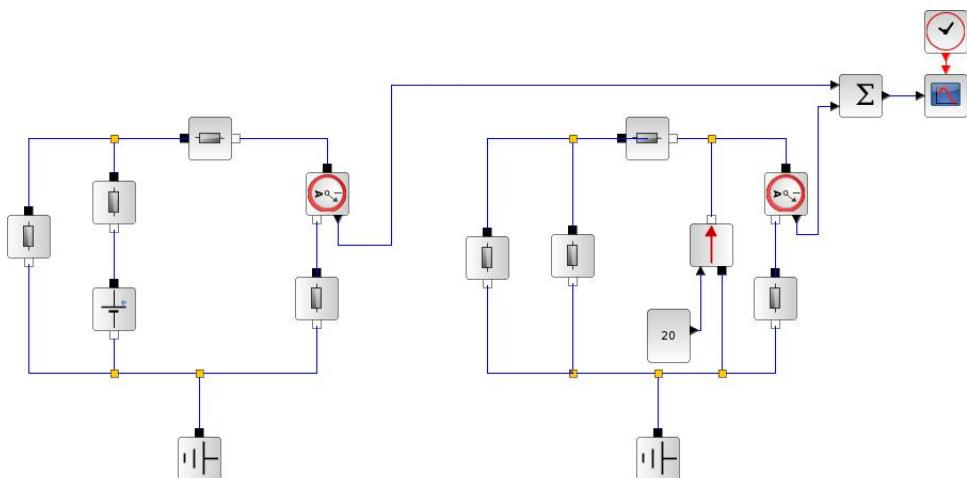


Figure 5.6: Superposition

# Chapter 6

## Amplifiers and Operational Amplifiers

Scilab code Exa 6.8 Operational amplifiers

```
1 clc
2 disp(" Example 6.8 ")
3 printf("Given")
4 disp("R1= 10kohm R2=50kohm Ri=500kohm R0=0")
5 disp("Open loop gain (A)=10^5")
6 A=10^5;R1=10*10^3;R2=50*10^3;Ri=500*10^3;
7 //From figure 6.11
8 //Applying KCL equation at node B
9 disp("( v1+vd)/10+ (v2+vd)/50+ vd/500=0 (1)")
10 //Since R0=0
11 disp("v2=A*vd")
12 //Solving for vd
13 disp("vd=10^-5*v2 (2)")
14 //Substituting (2) in (1) we get
15 printf("v2/v1=%d\n", -5)
```

---

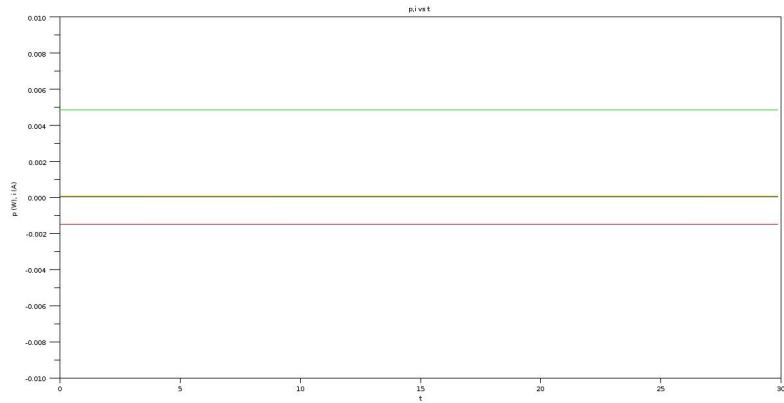


Figure 6.1: Analysis of circuits containing ideal op amps

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 6.10 Summing circuit

```

1 clc
2 printf("Given")
3 disp("R1=1 ohm; R2=1/2 ohm; R3=1/4 ohm; R4=1/8 ohm")
4 disp("Rf=1 ohm")
5 //From figure 6.14
6 //THe output of summing circuit can be written as
7 disp("v0=-((Rf/R1)*v1+(Rf/R2)*v2+(Rf/R3)*v3+.....")
8 //From above equation
9 disp("v0=-(8v4+4v3+2v2+v1)-----(1)")
10 disp("a")
```

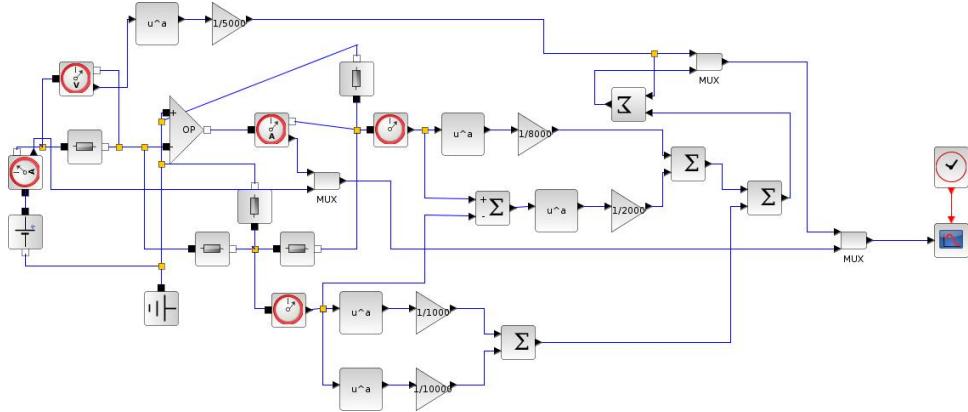


Figure 6.2: Analysis of circuits containing ideal op amps

```

11 v1=1; v2=0; v3=0; v4=1;
12 //Substituting in equation (1)
13 v0=-(8*v4+4*v3+2*v2+v1)
14 printf("v0=%dV\n",v0);
15
16 disp("b")
17 v1=0; v2=1; v3=1; v4=1;
18 //Substituting in equation (1)
19 v0=-(8*v4+4*v3+2*v2+v1)
20 printf("v0=%dV\n",v0);

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

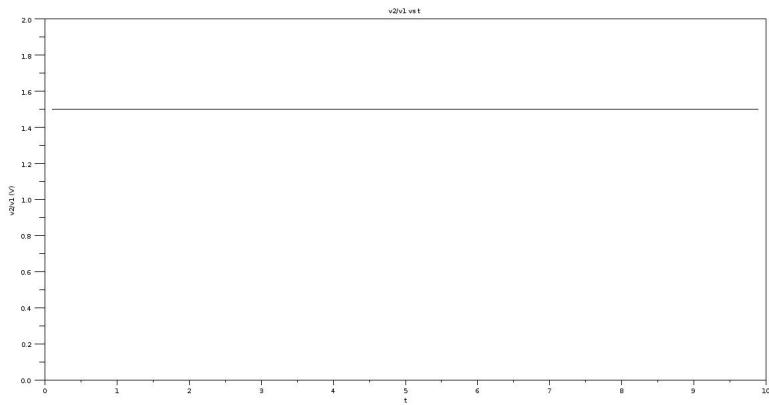


Figure 6.3: Noninverting circuit

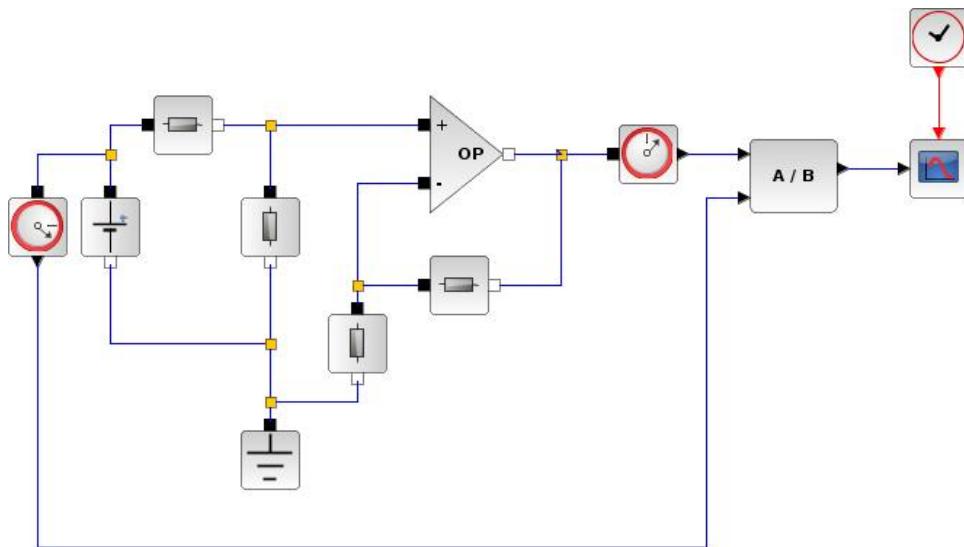


Figure 6.4: Noninverting circuit

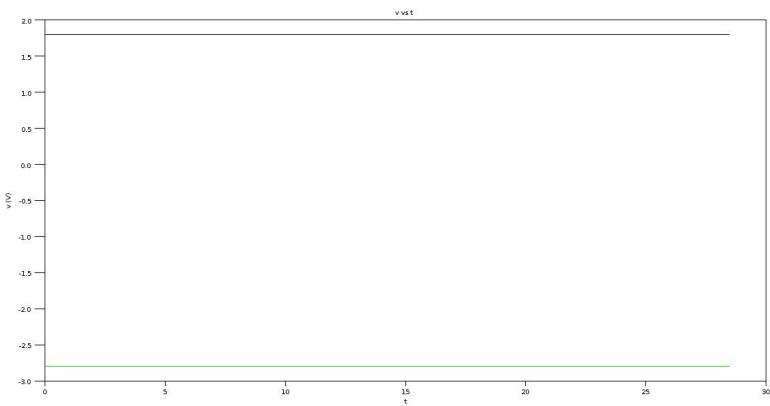


Figure 6.5: Circuits containing several Op amps

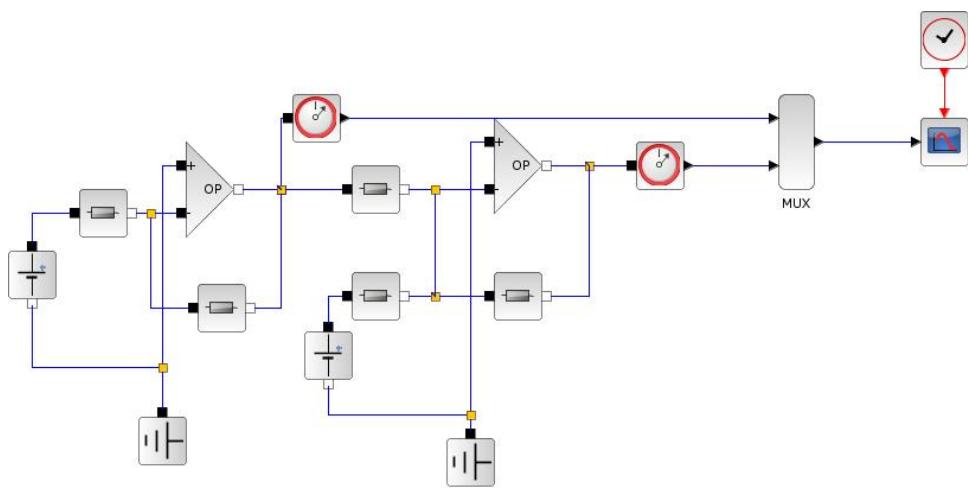


Figure 6.6: Circuits containing several Op amps

# Chapter 7

## Waveforms and Signals

### Scilab code Exa 7.1 Sinusoidal Functions

```
1 clc
2 disp("Example 7.1")
3 printf("\\n")
4
5 t1=-5:0.5:8
6 v1=cos (t1)
7 figure
8 a= gca ();
9 plot(t1,v1)
10 xtitle ('v1 vs t1 ','t1 ','v1 ');
11 a. thickness = 2;
12 //From the graph
13 printf("Time period1= %3.3 fs \\n Frequency 1=%0.3 fHz \\n
" ,6.2832 ,0.159)
14
15 t2=-4:0.5:10
16 v2=sin (t2)
17 figure
18 a= gca ();
19 plot(t2,v2)
20 xtitle ('v2 vs t2 ','t2 ','v2 ');
```

```

21 a. thickness = 2;
22 //From the graph
23 printf("Time period 2= %3.3 fs\n Frequency 2=%0.3 fHz\
n" ,6.2832,0.159)
24
25 t3=-1:0.05:1.5
26 v3=2*cos (2*pi*t3)
27 figure
28 a= gca ();
29 plot(t3,v3)
30 xtitle ('v3 vs t3 ', 't3 ', 'v3 ');
31 a. thickness = 2;
32 //From the graph
33 printf("Time period 3= %ds\n Frequency 3=%dHz\n"
,1,1)
34
35 t4=-5:0.5:12
36 v4=2*cos (%pi*t4/4-%pi/4)
37 figure
38 a= gca ();
39 plot(t4,v4)
40 xtitle ('v4 vs t4 ', 't4 ', 'v4 ');
41 a. thickness = 2;
42 //From the graph
43 printf("Time period 4= %ds\n Frequency 4=%0.3 fHz\n"
,8,0.125)
44
45 t5=-1:0.005:1
46 v5=5*cos (10*t5+%pi/3)
47 figure
48 a= gca ();
49 plot(t5,v5)
50 xtitle ('v5 vs t5 ', 't5 ', 'v5 ');
51 a. thickness = 2;
52 //From the graph
53 printf("Time period 5= %0.3 fs\n Frequency 5=%3.2 fHz\
n" , .62832,1.59)

```

---

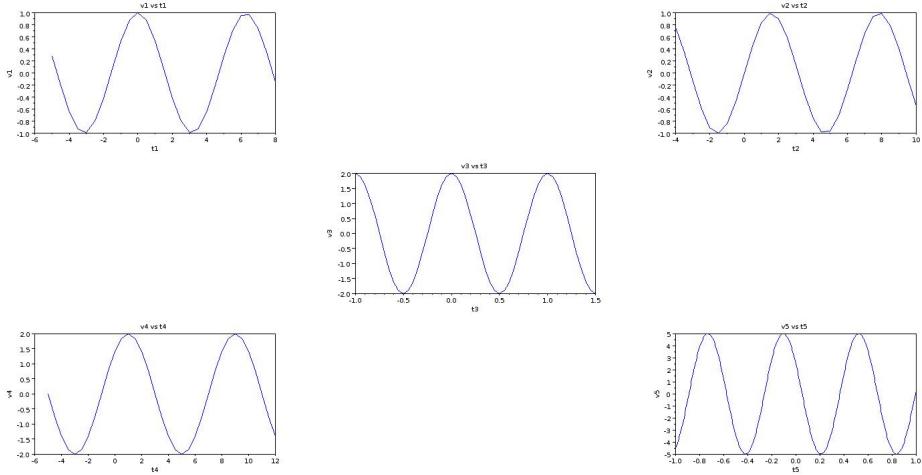


Figure 7.1: Sinusoidal Functions

### Scilab code Exa 7.2 Sinusoidal Functions

```

1 clc
2 disp( " Example 7.2 " )
3 printf( "\n" )
4
5 // Let wt=q
6 q=-8:0.5:8
7 v=5*cos (q)
8 figure
9 a= gca ();
10 plot(q,v)
11 xtitle ('v vs wt', 'wt', 'v');
12 a. thickness = 2;

```

---

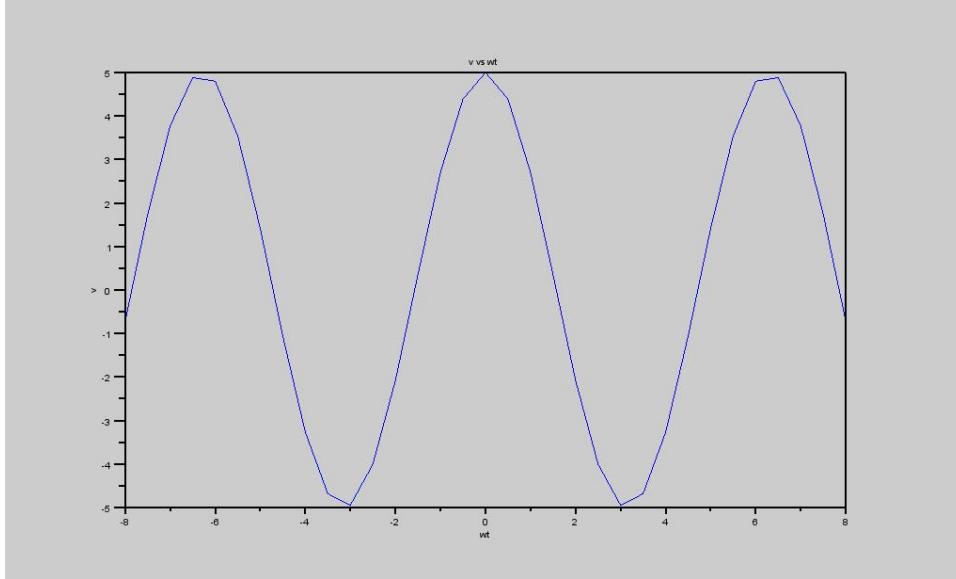


Figure 7.2: Sinusoidal Functions

### Scilab code Exa 7.3 Time Shift and Phase Shift

```

1 clc
2 disp("Example 7.3")
3 printf("\\n")
4
5 t1=-10:0.05:10
6 v=5*cos (%pi*t1/6+%pi/6)
7 figure
8 a= gca ();
9 plot(t1,v)
10 xtitle ('v vs %pi*t/6 , '%pi*t/6 , 'v ')
11 a. thickness = 2;

```

---

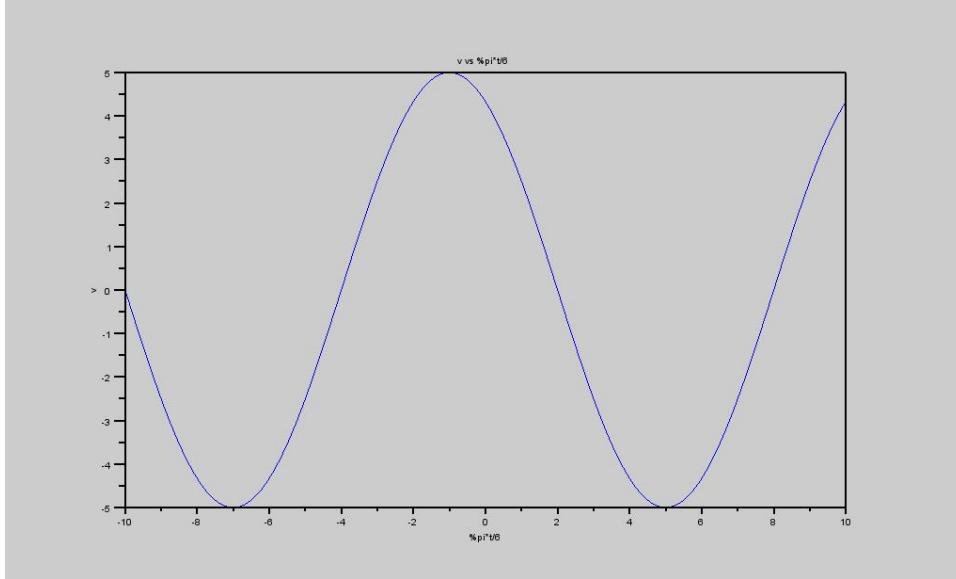


Figure 7.3: Time Shift and Phase Shift

### Scilab code Exa 7.5 Combinations of Periodic Functions

```

1 clc
2 disp("Example 7.5")
3 printf("\\n")
4
5 printf("Given")
6 disp("v(t)=cos5t+3sin(3t+45)")
7 //Finding the periods of individual terms
8 disp("Period of cos5t=2*pi/5")
9 disp("Period of 3*sin(3t+45)=2*pi/3")
10 //If T=2*pi
11 T=2*pi;
12 disp("Now T=5*T1=3*T2")
13 //Now the relation for T is the smallest common
   integral multiple of T1 and T2

```

```
14 printf("Period = %3.2 fs\n",T)
```

---

### Scilab code Exa 7.13 The Average and Effective RMS values

```
1 clc
2 disp("Example 7.13")
3 printf("\n")
4
5 printf("Given")
6 disp("Capacitance is 1uF")
7 C=1*10^-6;
8 disp("a")
9 //Let k=1 which results in t=5ms
10 t=5*10^-3;
11 vac=(integrate('0.004','t',0,0.003)-integrate('0.002',
    't',0.003,0.005))/C;
12 printf("vac=%dV\n",vac);
13
14 //In general
15 disp("At t=5k voltage follows as v=8k ms")
16
17 disp("b")
18 //As vdc=1/C*integrate(Idc*dt)
19 //On solving for Idc
20 vdc=vac
21 Idc=(1/((integrate('1/vac','t',0,0.005))/C))*10^3
22 printf("Idc=%3.2 fmA\n",Idc);
23 disp("Idc is equal to <i(t)> in the period of 5ms")
```

---

### Scilab code Exa 7.17 The Unit Impulse Function

```
1 clc
2 disp("Example 7.17")
```

```

3 printf("\n")
4
5 printf("Given")
6 disp("Capacitance is 100nF")
7 disp("The voltage across capacitor increases
     linearly from 0 to 10V")
8 C=100*10^-9;
9 //From figure 7.10(a)
10 disp("a"))
11 //At t=T voltage across capacitor =10V
12 vc=10;
13 Q=C*vc;
14 printf("Charge across capacitor is %fC\n",Q)
15 disp("b"))
16 //The waveform shown in fig 7.10(a) can be written
     as
17 disp("0                  t<0")
18 disp("I0=10^-6/T      0<t<T")
19 disp("0                  t>T")
20
21
22 //For T=1s;
23 T=1;
24 I0=10^-6/T;
25 printf("I0 (1 s)=%fA\n",I0);
26
27 //For T=1ms;
28 T=1*10^-3;
29 I0=10^-6/T;
30 printf("I0 (1 ms)=%.3 fA\n",I0);
31
32 //For T=1us;
33 T=1*10^-6;
34 I0=10^-6/T;
35 printf("I0 (1 us)=%dA",I0);

```

---

### Scilab code Exa 7.22 The Exponential Function

```
1 clc
2 disp("Example 7.22")
3 printf("\\n")
4
5 //The general equation of exponential decay function
   is given by
6 disp("v(t)=A*e(-t/T)+B")
7 //We need to solve A and B
8 //At t=0 we get v(0)=A+B      (1)
9 //at t=inf we get B=1        (2)
10 //Solving (1) and (2)
11 A=4;B=1;
12 T=3;
13 t=0:0.05:10
14 v=4*exp(-t/T)+1;
15 figure
16 a= gca ();
17 plot(t,v)
18 xtitle ('v vs t', 't', 'v');
19 a. thickness = 2;
```

---

### Scilab code Exa 7.23 The Exponential Function

```
1 clc
2 disp("Example 7.23")
3 printf("\\n")
4
5 //Sketch voltage 'v'
```

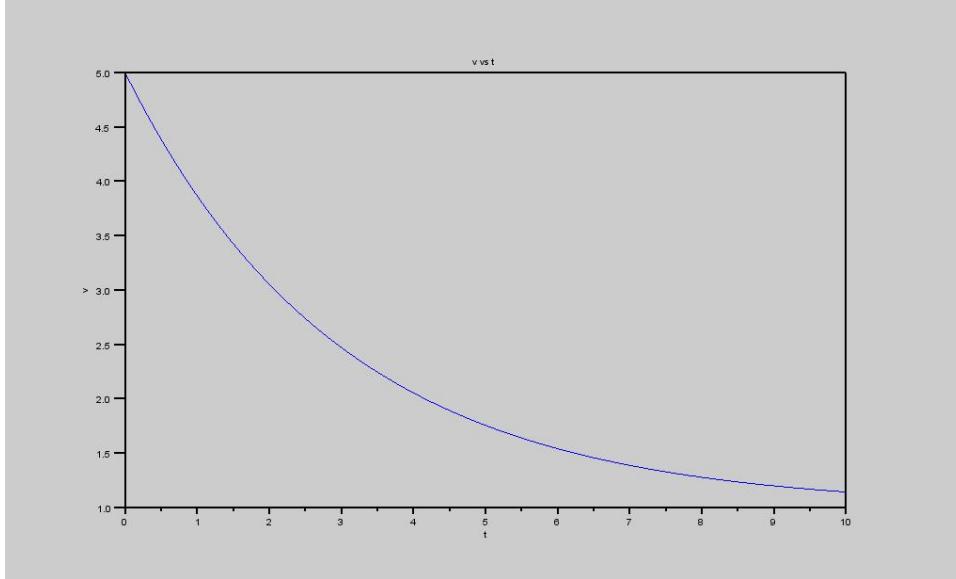


Figure 7.4: The Exponential Function

```

6 t=-.001:0.00005:0
7 t1=0:0.00005:.001
8 T=1*10^-3;
9 V0=10;
10 v=V0*exp(t/T)
11 v1=V0*exp(-t1/T)
12 figure
13 a= gca ();
14 plot(t,v)
15 plot(t1,v1)
16 xtitle ('v vs t', 't (ms)', 'v ')
17 a. thickness = 2;
18
19 //Sketch current 'i'
20 t=-.001:0.00005:0
21 t1=0:0.00005:.001
22 T=1*10^-3;
23 I0=10*10^-3;
24 i=I0*exp(t/T)

```

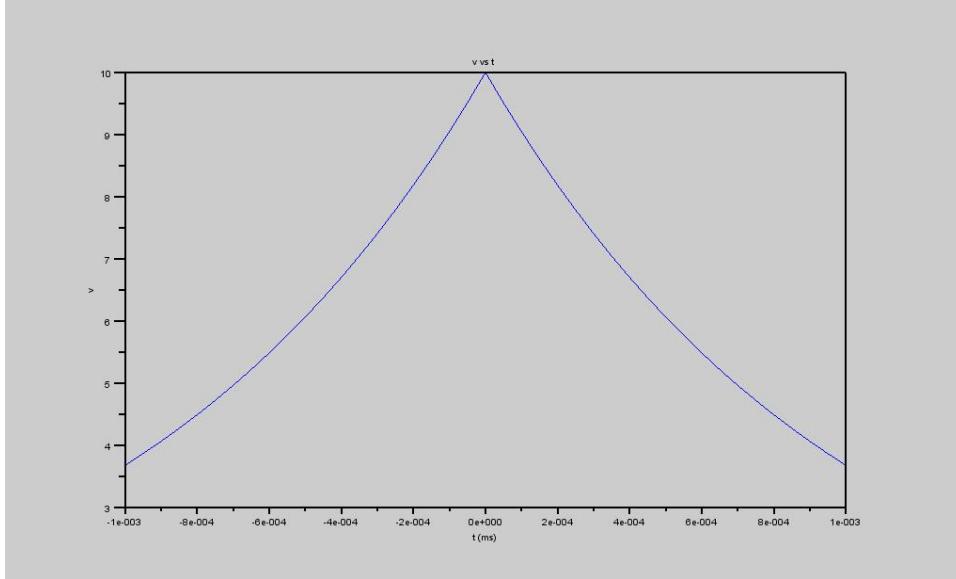


Figure 7.5: The Exponential Function

```

25 i1=-I0*exp(-t1/T)
26 figure
27 a= gca ();
28 plot(t,i)
29 plot(t1,i1)
30 xtitle ('i vs wt', 't (ms)', 'i (mA)');
31 a. thickness = 2;

```

---

### Scilab code Exa 7.25 Random Signals

```

1 clc
2 disp("Example 7.25")
3 printf("\n")

```

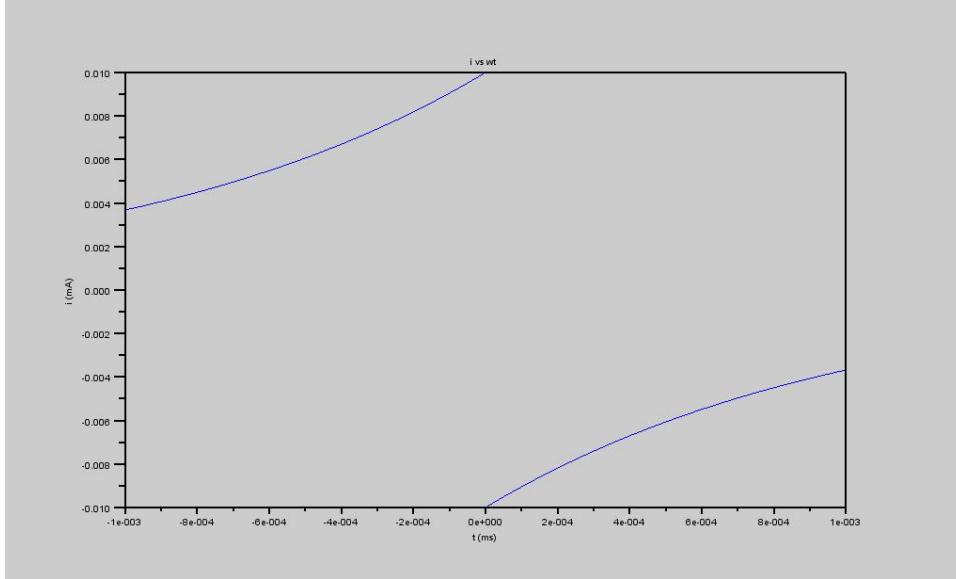


Figure 7.6: The Exponential Function

```

4
5 Xavg=(2+4+11+5+7+6+9+10+3+6+8+4+1+3+5+12)/16;
6 // Let X=X^2 eff
7 X
     =(2^2+4^2+11^2+5^2+7^2+6^2+9^2+10^2+3^2+6^2+8^2+4^2+1^2+3^2+5^2+12^2)/16
8 Xeff=sqrt(X);
9 printf("Xavg=%d\n Xeff=%3.2f\n",Xavg,Xeff)

```

---

### Scilab code Exa 7.26 Random Signals

```

1 clc
2 disp("Example 7.26")
3 printf("\n")
4
5 printf("Given")
6 disp("Period =10s")

```

```

7 disp("Interval is 1ms")
8 disp("Voltage of binary signal is either 0.5 or -0.5
      ")
9 T=10;
10 //During 10s period there are 10000 intervals of 1ms
    each
11 //For calculating average equal number of intervals
    are considered at 0.5V and -0.5V
12 vavg=(0.5*5000-0.5*5000)/10000
13 //The effective value of v(t) is
14 //Let V=V^2 eff
15 V=(0.5^2*5000+(-0.5)^2*5000)/10000
16 Veff=sqrt(V)
17 printf("vavg=%d\nVeff=%3.2f\n",vavg,Veff)

```

---

# Chapter 8

## First order Circuits

Scilab code Exa 8.1 Capacitor Discharge in a Resistor

```
1 clc
2 disp("Example 8.1")
3 printf("\n")
4
5 printf("Given")
6 disp("Capacitance is 1uF")
7 disp("Resistance is 1Mohm")
8 disp("Voltage across capacitor is 10V")
9 R=1*10^6;C=1*10^-6;V=10
10 //Let T be time constant
11 T=R*C
12 //v(t)=V*exp(-t/T)
13 disp("v(t)=10*exp(-t) (1)")
14 //Substituting value of t=5 in (1)
15 v5=10*exp(-5)
16 printf("Time constant is %ds\n",T)
17 printf("v(5)=%0.3fV\n",v5)
```

---

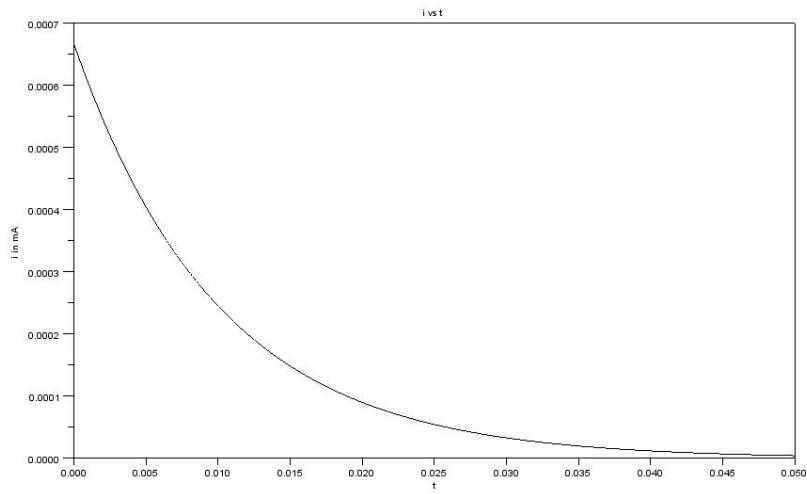


Figure 8.1: Capacitor Discharge in a Resistor

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

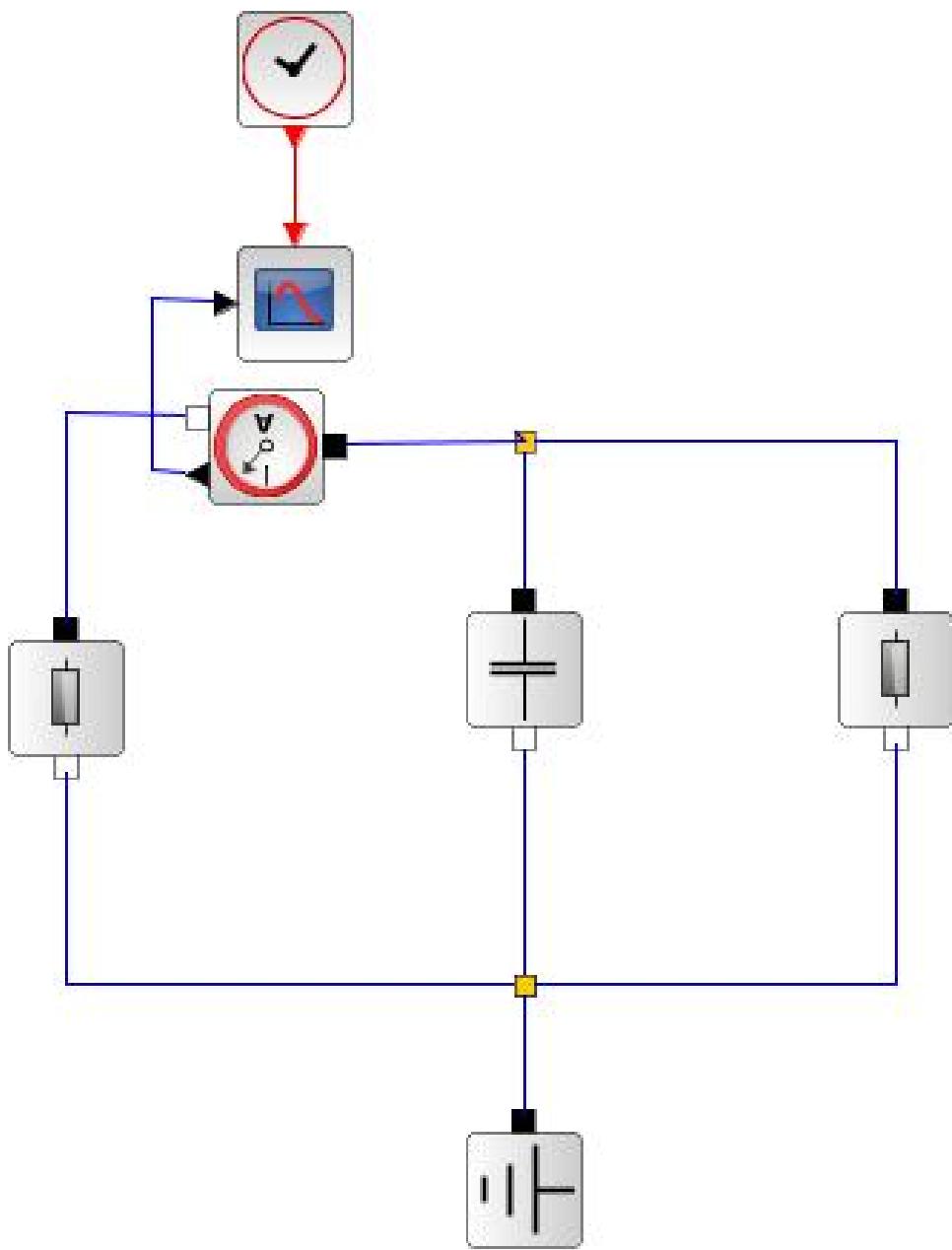


Figure 8.2: Capacitor Discharge in a Resistor

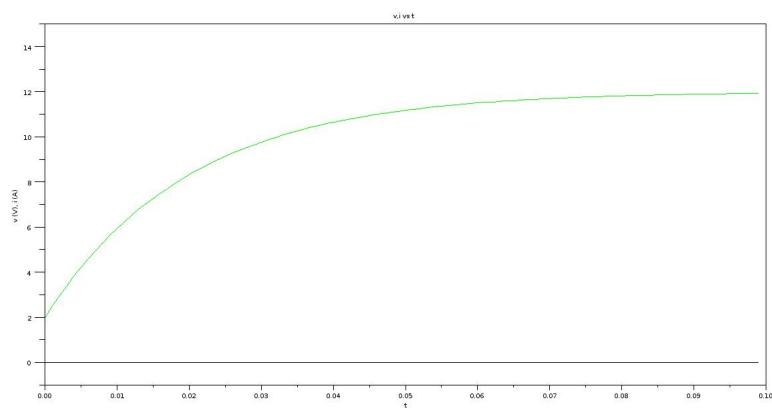


Figure 8.3: Establishing a DC Voltage across a Capacitor

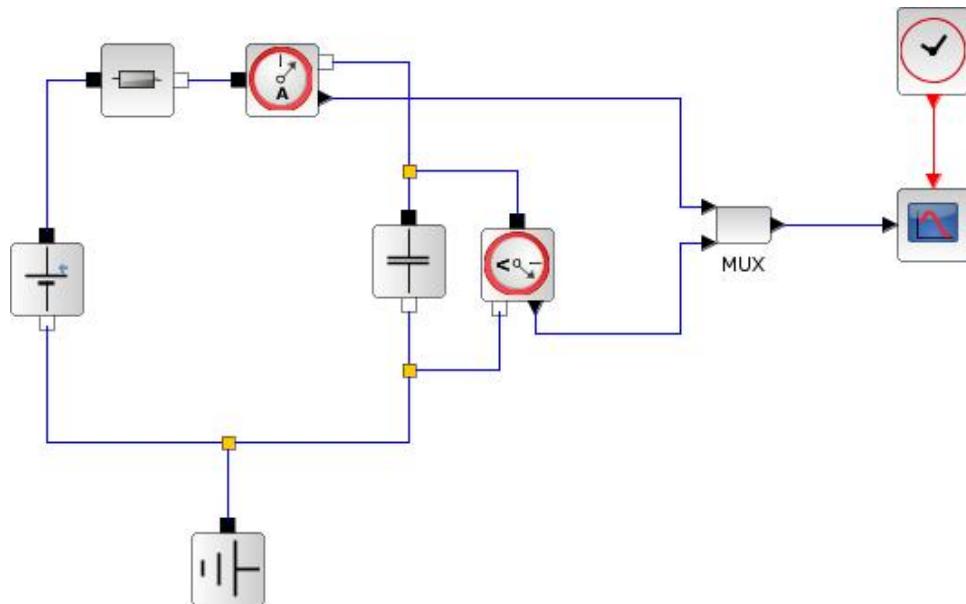


Figure 8.4: Establishing a DC Voltage across a Capacitor

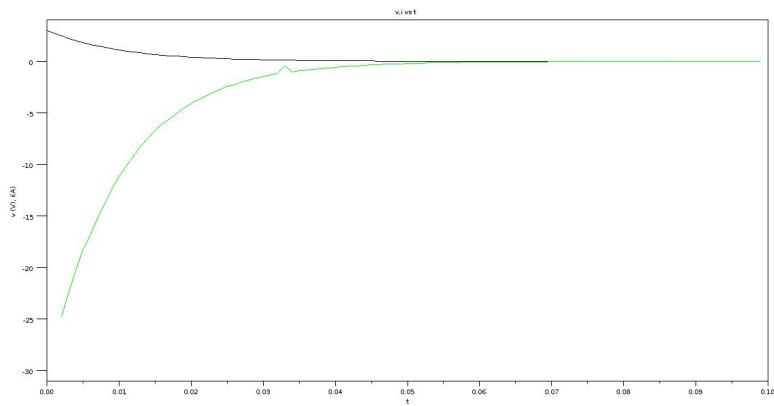


Figure 8.5: The Source free RL Circuit

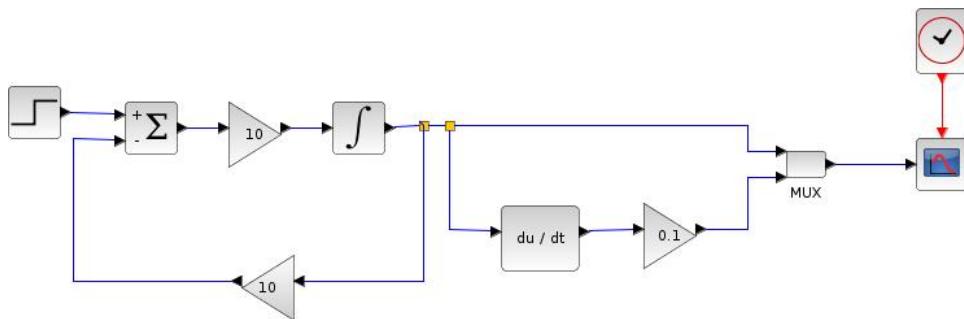


Figure 8.6: The Source free RL Circuit

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

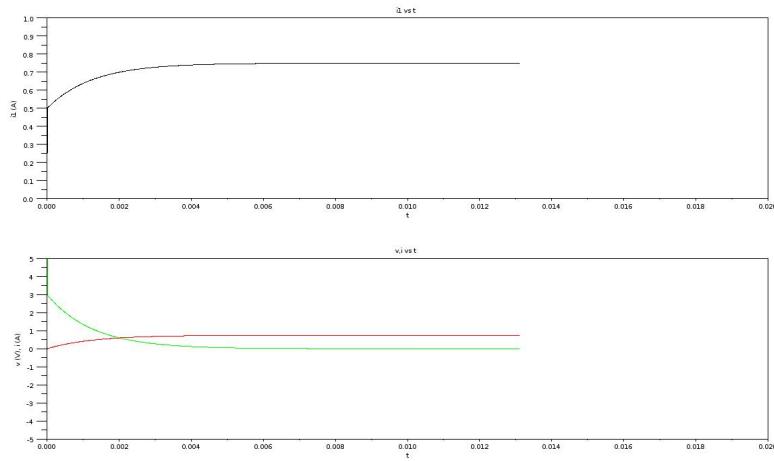


Figure 8.7: Complex first order RL and RC Circuits

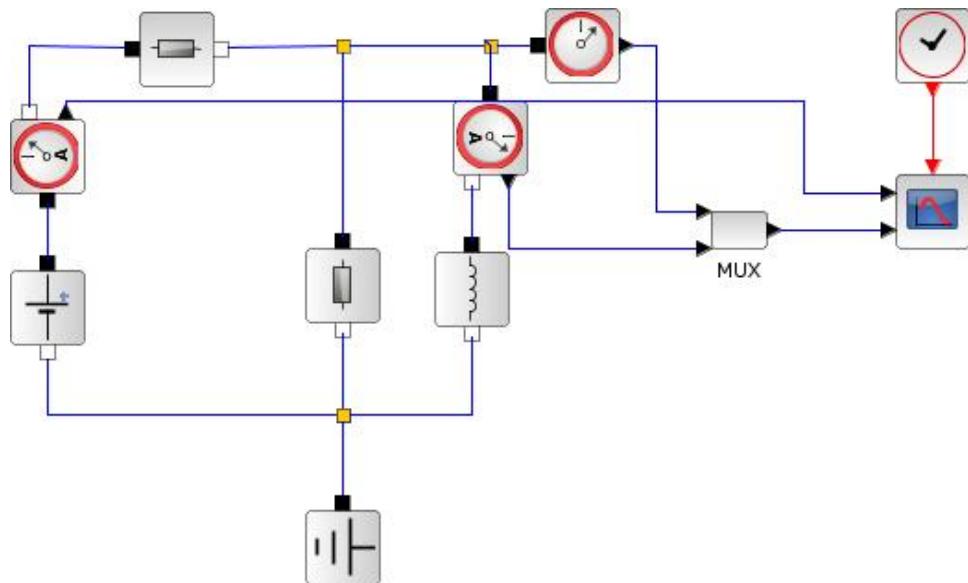


Figure 8.8: Complex first order RL and RC Circuits

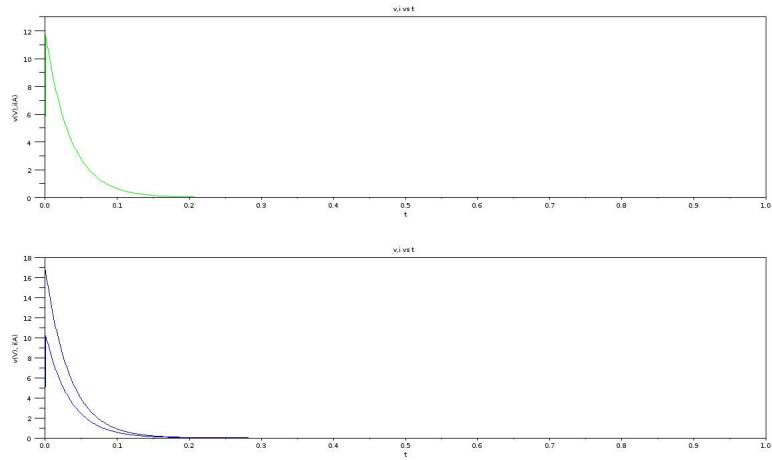


Figure 8.9: Complex first order RL and RC Circuits

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

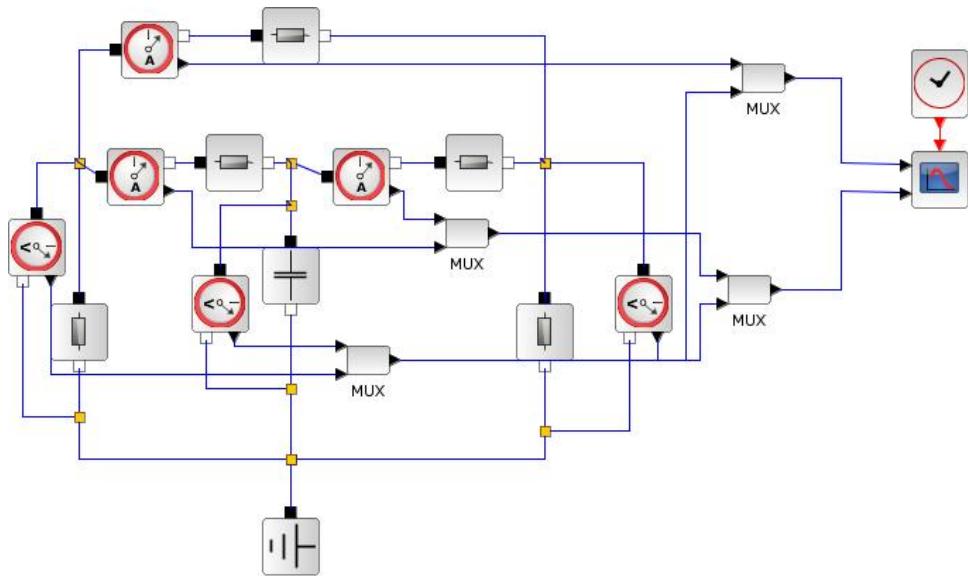


Figure 8.10: Complex first order RL and RC Circuits

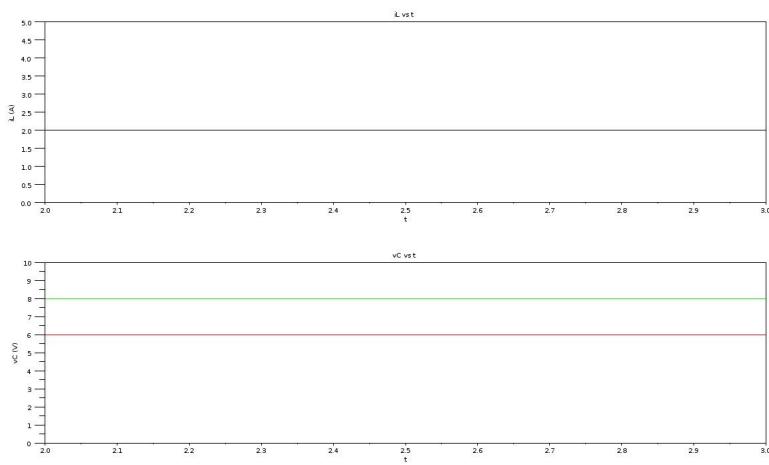


Figure 8.11: DC Steady state in Inductors and Capacitors

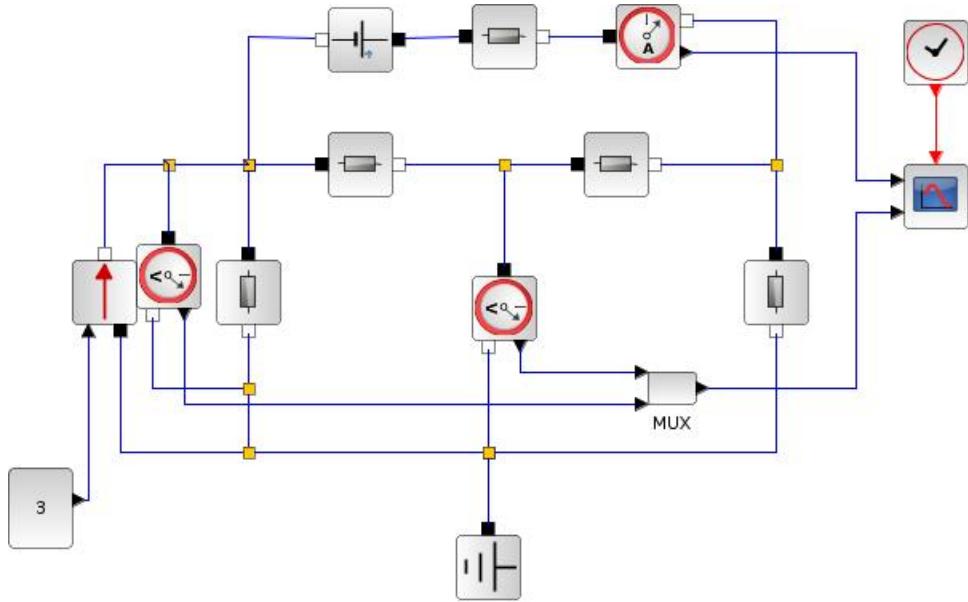


Figure 8.12: DC Steady state in Inductors and Capacitors

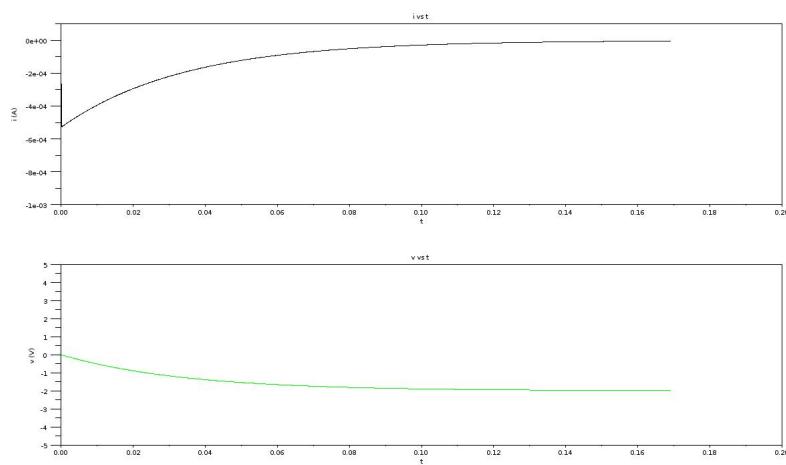


Figure 8.13: DC Steady state in Inductors and Capacitors

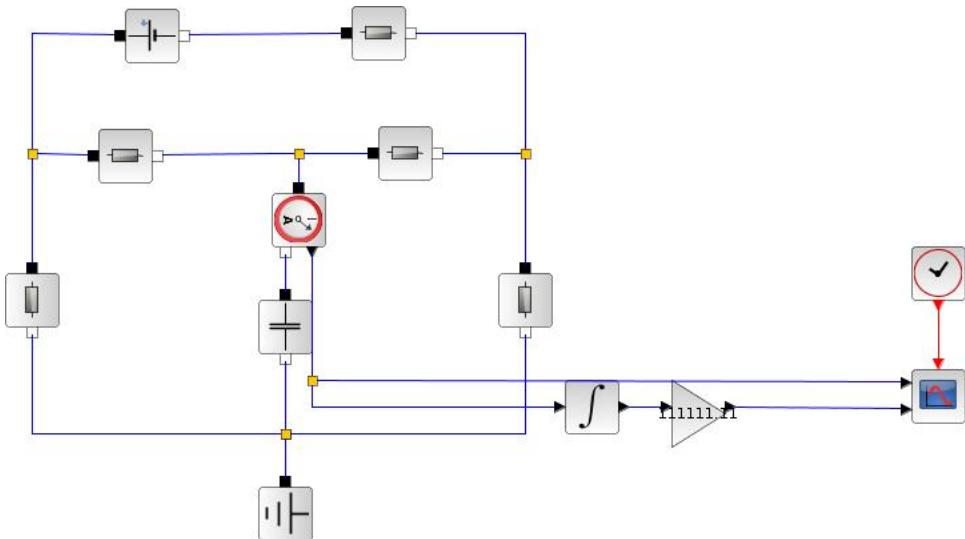


Figure 8.14: DC Steady state in Inductors and Capacitors

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 8.10 Transitions at Switching Time

```

1 clc
2 disp("Example 8.10")
3 printf("\n")
4
5 printf("Given")
6 disp("vs= 5V      t<0")
7 disp("vs=5*sin(w*t)  t>0")

```

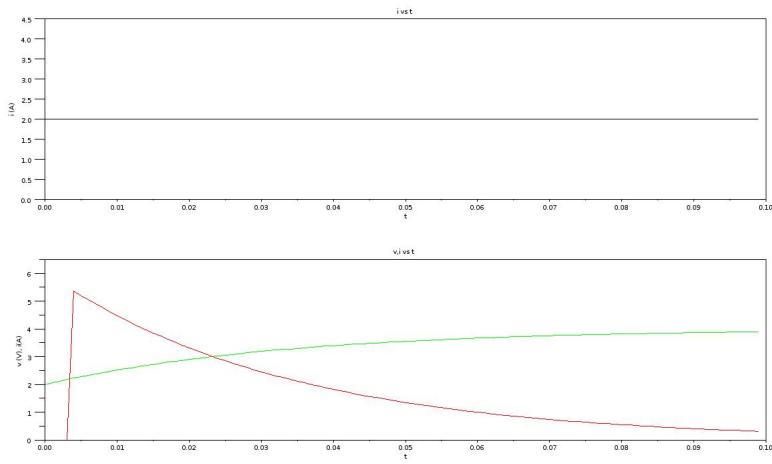


Figure 8.15: Transitions at Switching Time

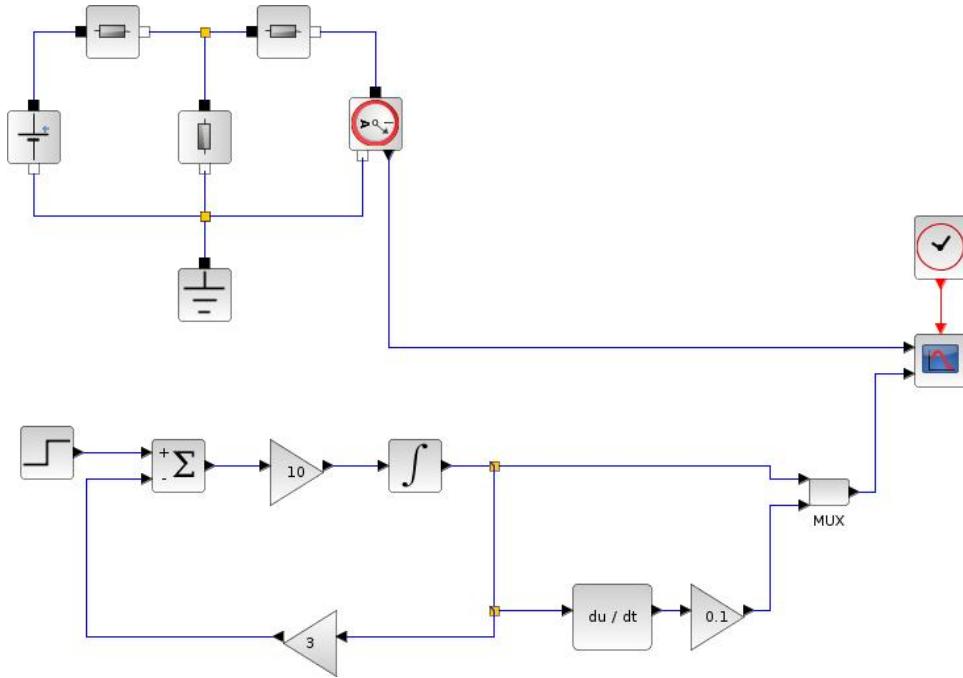


Figure 8.16: Transitions at Switching Time

```

8 vs=5;
9 R=5;L=10*10^-3;
10 //At t<0
11 //Inductor behaves as a short circuit
12 //Let i(0-)=i
13 i=vs/R;
14 printf("i(0-)=%dA\n",i)
15 //During the transition from t=0- to t=0+
16 //Let i(0+)=i1
17 i1=i
18 printf("i(0+)=%dA\n",i1)
19 //Applying KVL equation to the loop
20 disp("vs=i*R+v")
21 //Let v(0+)=v1 ; vs(0+)=vs1
22 //From given vs(0+)=0
23 vs1=0;
24 v1=vs1-i*R
25 printf("\nv(0+)=%dV\n",v1)

```

---

# **Chapter 9**

## **Higher order circuits and Complex frequency**

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

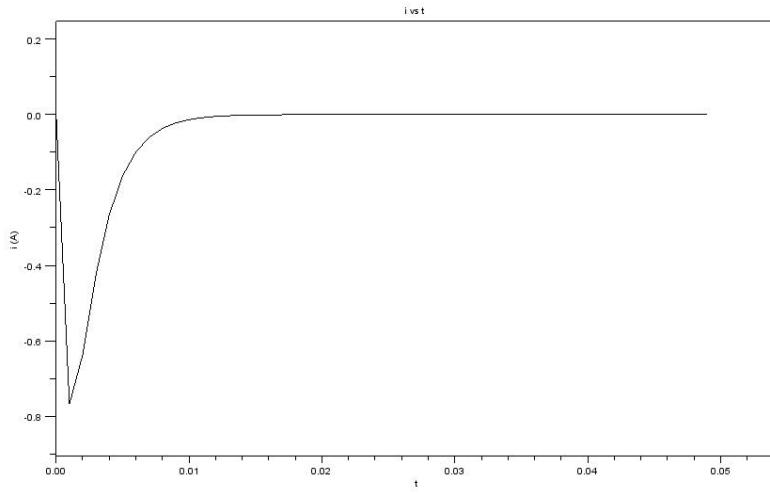


Figure 9.1: Series RLC Circuit

### Scilab code Exa 9.6 Generalized Impedance RLC in s domain

```

1 clc
2 disp("Example 9.6")
3 printf("\n")
4
5 printf("Given")
6 disp("Resistance is 10ohm and inductance is 2H")
7 disp("Applied voltage is 10*exp(-2*t)*cos(10*t+30)")
8 s=%s;
9 //For a RL circuit
10 //Applying KVL equation
11 //v=i*R+L*d/dt(i) (1)
12 //As v=10(30 deg) (2)
13 //Equating (1) and (2)
14 // Let i=I*exp(s*t) (3)
15 // 10(30 deg)*exp(s*t)=10*I*exp(s*t)+2*s*I*exp(s*t)
16 // Solving for I

```

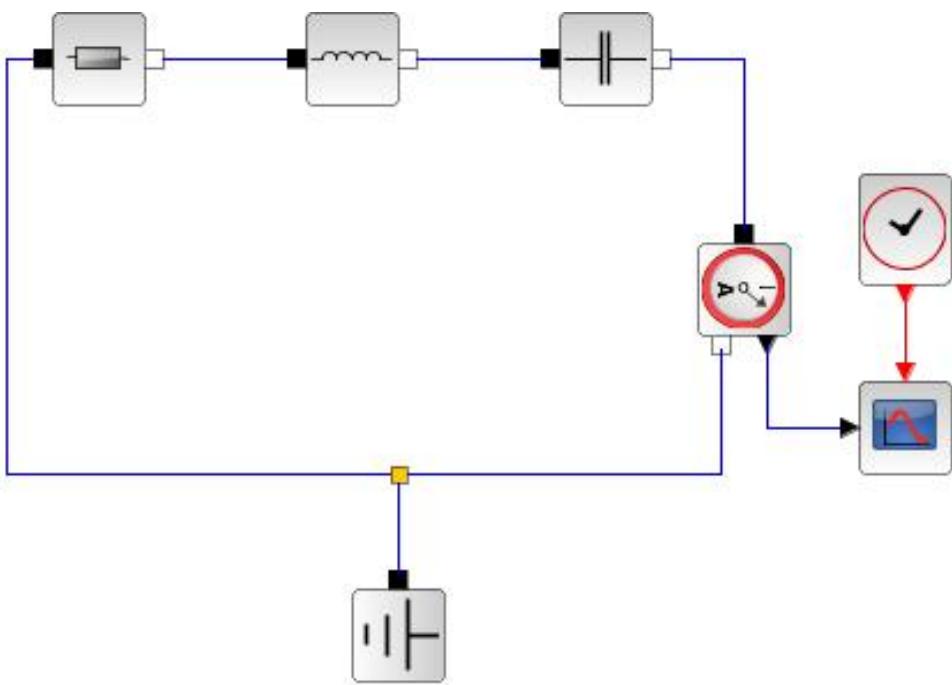


Figure 9.2: Series RLC Circuit

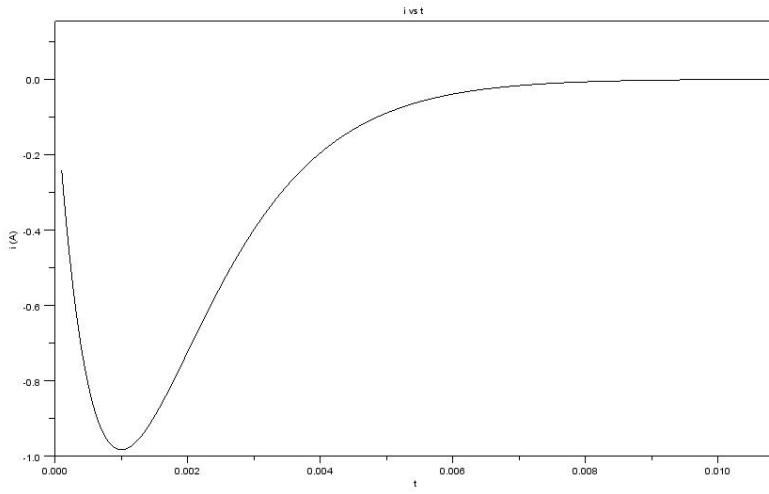


Figure 9.3: Series RLC Circuit

```

17 disp("I=10(30 deg)/10+2*s")
18 s=-2+%i*10
19 a=10+2*s
20 x=10*cos((30*pi)/180);
21 y=10*sin((30*pi)/180);
22 z=complex(x,y)
23 I=z/a
24 b=real(I);
25 c=imag(I);
26 magn=sqrt(b^2+c^2)
27 ph=(atan(c/b)*180)/pi
28 //From (3)
29 printf("\ni=%0.2f*exp(-2*t)*cos(10t%3.1f deg) (A)\n",
       magn,ph);

```

---

**Scilab code Exa 9.7 Generalized Impedance RLC in s domain**

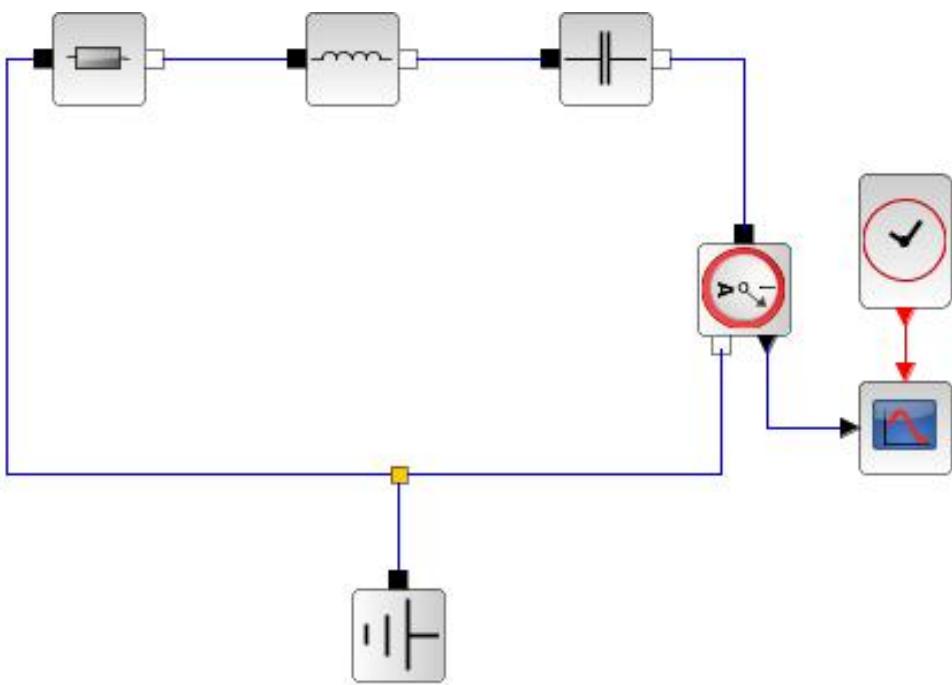


Figure 9.4: Series RLC Circuit

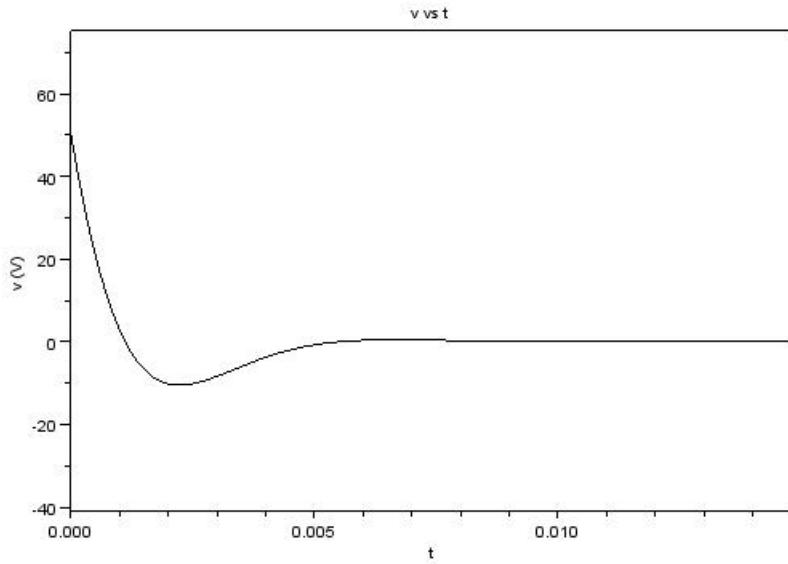


Figure 9.5: Parallel RLC circuit

```

1 clc
2 disp("Example 9.7")
3 printf("\\n")
4
5 printf("Given")
6 disp("Resistance is 10ohm and Capacitance is 0.2F")
7 disp("Applied voltage is 10*exp(-2*t)*cos(10*t+30")")
8 s=%s;
9 //For a RC circuit
10 //Applying KVL equation
11 //v=i*R+(1/C)*integrate(i*dt) (1)
12 //As v=10(30 deg) (2)
13 //Equating (1) and (2)
14 // Let i=I*exp(s*t) (3)
15 // 10(30 deg)*exp(s*t)=10*I*exp(s*t)+(5/s)*I*exp(s*t)
// )")
16 //Solving for I
17 disp("I=10(30 deg)/10+(5/s)")
```

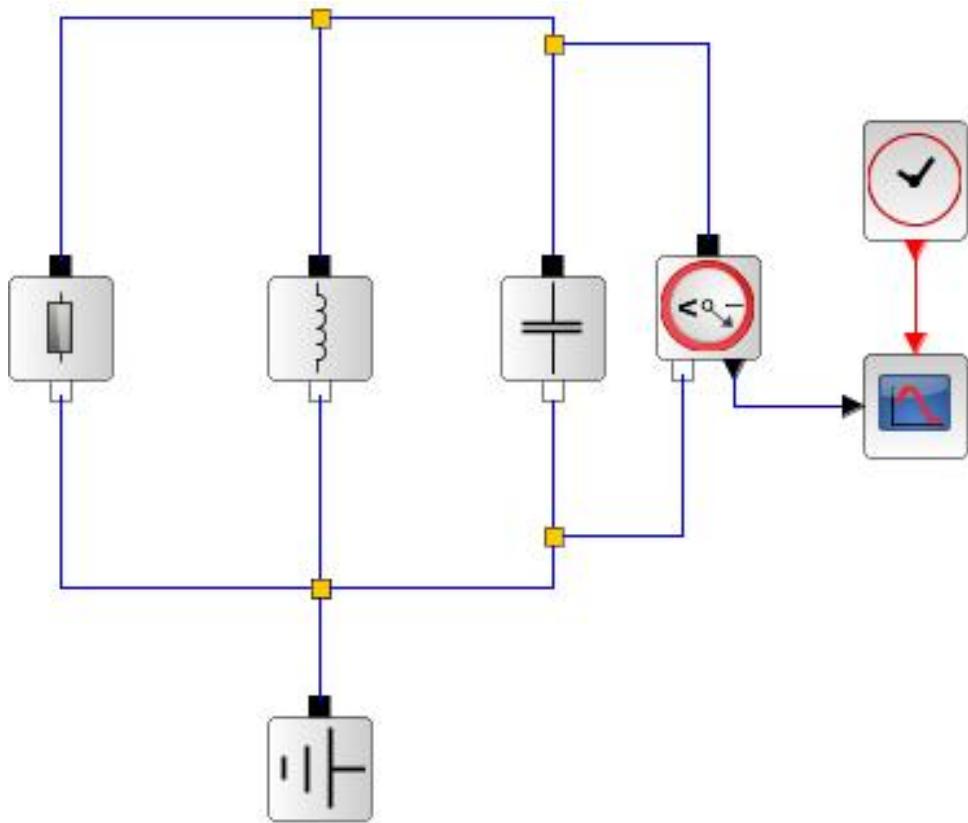


Figure 9.6: Parallel RLC circuit

```

18 s=-2+%i*10
19 a=10+(5/s)
20 x=10*cos((30*pi)/180);
21 y=10*sin((30*pi)/180);
22 z=complex(x,y)
23 I=z/a
24 b=real(I);
25 c=imag(I);
26 magn=sqrt(b^2+c^2)
27 ph=(atan(c/b)*180)/pi
28 //From (3)
29 printf("\ni=%0.2f*exp(-2*t)*cos(10t+%3.1f deg) (A)\n"
" ,magn ,ph);

```

---

### Scilab code Exa 9.8 Network function and Pole zero plots

```

1 clc
2 disp("Example 9.8")
3 printf("\n")
4
5 s=%s ;
6
7 //From figure 9.13
8 disp("Z(s)=(2.5+((5*s/3)*(20/s))/(5*s/3+20/s))")
9 //On solving
10 z1=poly([12 8 1], 's', 'coeff')
11 z2=poly([12 0 1], 's', 'coeff')
12 Z=2.5*(z1/z2)
13 disp(Z,"Z(s)")
14 //H(s)=I(s)/Z(s)
15 //Let I(s)=1 the H(s)=1/Z(s)
16 H=(1/2.5)*(z2/z1)
17 disp(H,"H(s)")

```

---

### Scilab code Exa 9.9 The Forced Response

```
1 clc
2 disp(”Example 9.9”)
3 printf(”\n”)
4
5 s=%s ;
6 H=syslin ( ’c’ ,(0.4*(s2+12))/((s+2)*(s+6)) ) ;
7 evans (H,1)
8 // If s=1Np/s
9 H1=0.4*(1+12)/((1+2)*(1+6))
10 printf(”H(1)=%0.3 f\n”,H1)
```

---

### Scilab code Exa 9.11 The Natural Response

```
1 clc
2 disp(”Example 9.11”)
3 printf(”\n”)
4
5 //From figure 9.16
6 //H(s)=V(s)/I(s)=Z(s)
7 //Let V(s)=1 the H(s)=Z(s)
8 s=%s
9 z1=(1/2.5)+(3/(5*s))+(s/20)
10 Z=1/z1
11 Dem=Z(’den’)
12 //The roots are
13 q=roots(Dem)
14 disp(q,”Poles are”)
```

---

# Chapter 10

## Sinusoidal Steady state Circuit Analysis

### Scilab code Exa 10.4 Phasors

```
1 clc
2 disp(" Problem 10.4 ")
3 printf("\n")
4
5 //For V1
6 Ro1=25
7 Theta1=143.13
8 //For V1
9 Ro2=11.2
10 Theta2=26.57
11 //We need to find V1/V2
12 //Let V=V1/V2
13 Vmag=(Ro1/Ro2)
14 Vph=Theta1-Theta2
15 x=Vmag*cos((Vph*%pi)/180);
16 y=Vmag*sin((Vph*%pi)/180);
17 z=complex(x,y)
18 //Let V1+V2=V12
19 x1=Ro1*cos((Theta1*%pi)/180);
```

```

20 y1=Ro1*sin((Theta1*pi)/180);
21 z1=complex(x1,y1)
22 x2=Ro2*cos((Theta2*pi)/180);
23 y2=Ro2*sin((Theta2*pi)/180);
24 z2=complex(x2,y2)
25 V12=z1+z2
26 [R,Theta]=polar(V12)
27 printf("V1/V2=%0.2f+i%3.2f \nV1+V2=%3.2f (%3.2f deg)
",x,y,R,(Theta*180)/pi)

```

---

### Scilab code Exa 10.5 Impedance and Admittance

```

1 clc
2 disp("Problem 10.5")
3 printf("\n")
4
5 printf("Given")
6 disp("Voltage is 100(45 deg)")
7 disp("Current is 5(15 deg)")
8 //For V
9 Ro1=100
10 Theta1=45
11 //For I
12 Ro2=5
13 Theta2=15
14 //We need to find V/I=Z
15
16 Zmag=(Ro1/Ro2)
17 Zph=Theta1-Theta2
18 x=Zmag*cos((Zph*pi)/180);
19 y=Zmag*sin((Zph*pi)/180);
20 z=complex(x,y)
21 //Let Y=1/Z
22 Ymag=(Ro2/Ro1)
23 Yph=Theta2-Theta1

```

```

24 x1=Ymag*cos((Yph*%pi)/180);
25 y1=Ymag*sin((Yph*%pi)/180);
26 z1=complex(x1,y1)
27
28 printf("R=%3.2f ohm XL=%3.2f H \nG=%0.3f S BL=%0.3f S",x
, y, x1, abs(y1));

```

---

### Scilab code Exa 10.7 Superposition of AC sources

```

1 clc
2 disp(" Problem 10.7")
3 printf("\n")
4
5 printf(" Voltage v1=5*cos(w1*t)")
6 printf(" Voltage v2=10*cos(w2*t+60)")
7 //The circuit is modeled as
8 disp(" Resistance is 10ohm and inductance is 5mH")
9 R=10;L=5*10^-3;
10 disp("a")
11 w1=2000;w2=2000;
12 //Let Z be the impedance of the coil
13 Z1=R+%i*L*w1
14 Z2=R+%i*L*w2
15 //Let V be phasor voltage between the terminals
16 Vmag=10;
17 Vph=60;
18 x=Vmag*cos((Vph*%pi)/180);
19 y=Vmag*sin((Vph*%pi)/180);
20 z=complex(x,y)
21 v=5-z;
22 //Let I be the current
23 I=v/Z1
24 [R,Theta]=polar(I)
25 printf(" i=%0.2f *cos(%dt%d deg)",R,w1,(Theta*180)/%pi
);

```

```

26
27 disp("b")
28 R=10;L=5*10^-3;
29 w1=2000;w2=4000;
30 //Let Z be the impedance of the coil
31 Z1=R+%i*L*w1
32 Z2=R+%i*L*w2
33 V1=5;
34 //By applying superposition i=i1-i2
35 I1=V1/Z1
36 [R,Theta]=polar(I1)
37 printf("i1=%0.2f*cos(%dt%deg)\n",R,w1,(Theta*180)/
    %pi);
38 V2mag=10;V2ph=60;
39 I2=z/Z2
40 [R1,Theta1]=polar(I2)
41 printf("i2=%0.2f*cos(%dt%3.2f deg)\n",R1,w2,(Theta1
    *180)/%pi);
42 // i=i1-i2
43 printf("i=%0.2f*cos(%dt%deg)-%0.2f*cos(%dt%3.2f
    deg)\n",R,w1,(Theta*180)/%pi,R1,w2,(Theta1*180)/
    %pi)

```

---

# Chapter 11

## AC Power

Scilab code Exa 11.1 Power in time domain

```
1 clc
2 disp("Problem 11.1")
3 printf("\\n")
4
5 printf("Given")
6 disp("Resistance =1000ohm")
7 t=0:0.5:1;
8 i=ones(length(t),1) ;i1=-1;
9 figure
10 a=gca()
11 plot(t,i,t+1,i1,t+2,i,t+3,i1)
12 xtitle("i vs t",'t in ms','i in mA')
13 i=1*10^-3;R=1000;
14 //p=i^2*R
15 p=i^2*R*ones(length(t),1) ;
16 figure
17 a=gca()
18 plot(t,p)
19 xtitle("p vs t",'t in ms','p in mW')
```

---

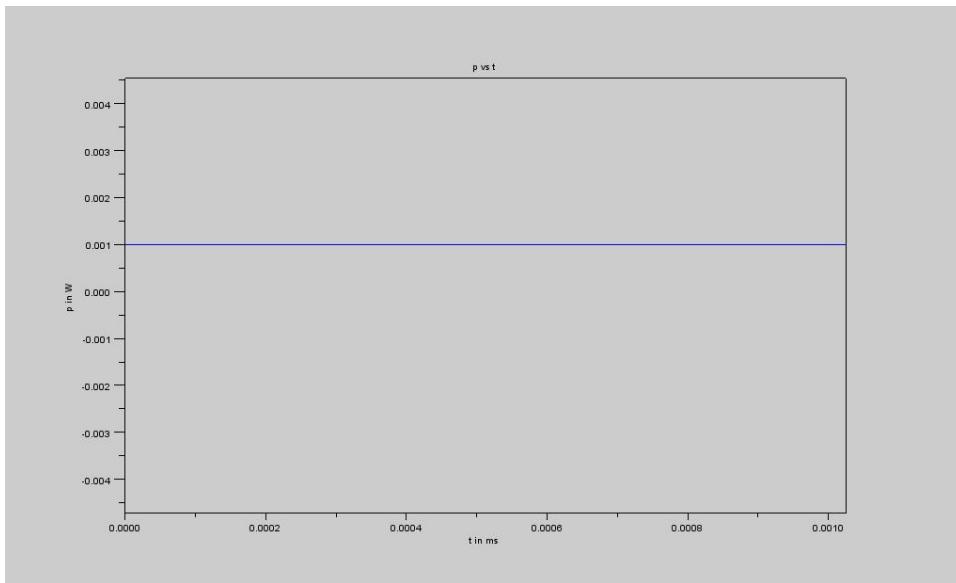


Figure 11.1: Power in time domain

### Scilab code Exa 11.2 Power in time domain

```
1 clc
2 disp("Problem 11.2")
3 printf("\n")
4
5 t=0:0.5:1;
6 i=ones(length(t),1);i1=-1;
7 figure
8 a=gca()
9 plot(t,i,t+1,i1)
10 xtitle("i vs t",'t in ms','i in mA')
```

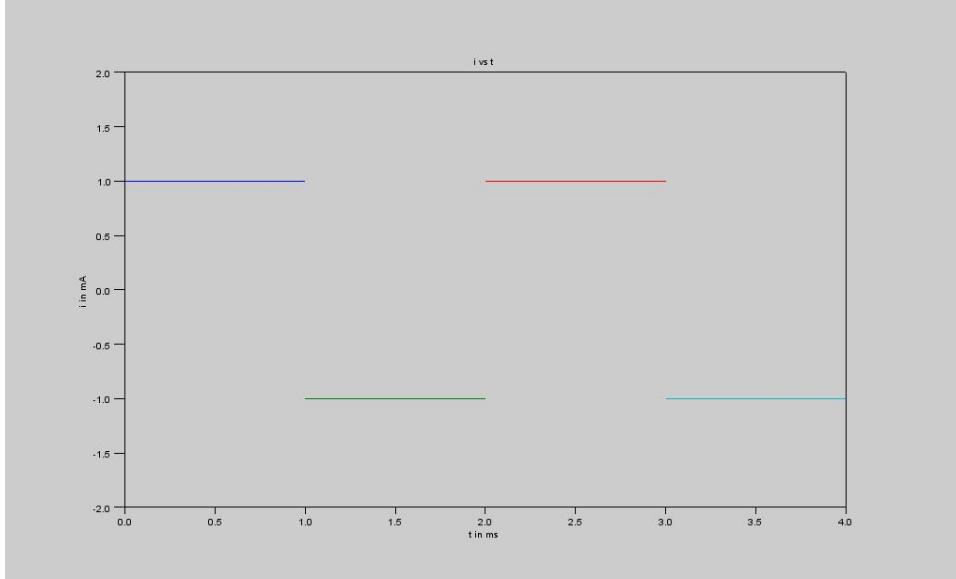


Figure 11.2: Power in time domain

```

11 //Voltage across capacitor vC=(1/C)*integrate(i*dt)
12 //On integration
13 t=0:0.0005:0.001
14 v=2000*t
15 v1=2-v;
16 figure
17 a=gca()
18 plot(t,v,t+0.001,v1,t+0.002,v,t+0.003,v1)
19 xlabel("v vs t",'t in ms','v in V')
20
21 //Power is p=v*i
22 t=0:.0005:.001
23 p=2000*t
24 p1=p-2;
25 figure
26 a=gca()
27 plot(t,p,t+0.001,p1,t+0.002,p,t+0.003,p1)
28 xlabel("p vs t",'t in ms','p in W')
29

```

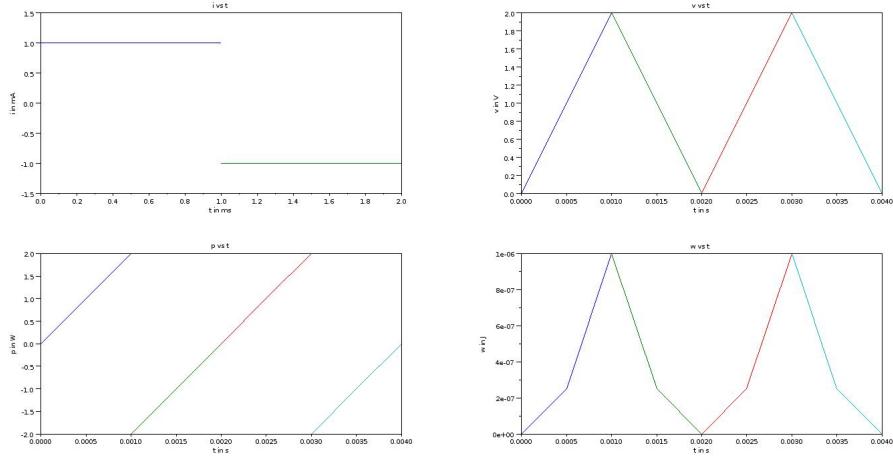


Figure 11.3: Power in time domain

```

30 //Work is (C*v^2)/2
31 t=0:.0005:.001
32 w=t.^2
33 w1=t.^2+1*10^-6-(2*10^-3*t);
34 figure
35 a=gca()
36 plot(t,w,t+0.001,w1,t+0.002,w,t+0.003,w1)
37 xtitle("w vs t",'t in ms','w in J')

```

---

#### Scilab code Exa 11.4 Average or Real Power

```

1 clc
2 disp("Problem 11.4")
3 printf("\n")
4
5 printf("Given")
6 disp("Veff=110V Z=10+i8 ohm")
7 Veff=110;

```

```

8 Z=10+%i*8;
9 R = 10;
10 Zmag=sqrt(10^2+8^2)
11 Zph=(atan(8/10)*180)/%pi
12 P=(Veff^2*R)/(Zmag^2)
13 pf=cos((Zph*%pi)/180)
14
15 disp(pf,"Power factor is")

```

---

### Scilab code Exa 11.5 Reactive Power

```

1 clc
2 disp("Problem 11.5")
3 printf("\n")
4
5 printf("Given")
6 disp(" Veff=110V Ieff=20(-50 deg)")
7 Imagn=20; Iph =-50;
8 Veff=110;
9
10 P=Veff*Imagn*cos((abs(Iph)*%pi)/180)
11 Q=Veff*Imagn*sin((abs(Iph)*%pi)/180)
12 printf(" Average power is %3.1fW\n",P)
13 printf(" Reactive power is %3.1fvar\n",Q)

```

---

### Scilab code Exa 11.10 Complex power Apparent power and Power triangle

```

1 clc
2 disp("Problem 11.10")
3 printf("\n")
4
5 printf("Given")
6 disp(" Veff=10V v=10*sqrt(2)*cos(w*t);")

```

```

7 Veff=10;vmag=10*1.414
8
9 disp("a")
10 Z1=1+%i
11 [R,Theta]=polar(Z1)
12 printf("i1=%d*cos(w*t-%d)\n", (vmag/R),Theta)
13 I1eff=(vmag/R)/1.414
14 //p1(t)=100*sqrt(2)*cos(wt)*cos(wt-45)
15 //On solving
16 disp("p1(t)=50+50*sqrt(2)*cos(2*w*t-45) W")
17 P1=Veff*I1eff*cos(Theta)
18 Q1=Veff*I1eff*sin(Theta)
19 S1=P1+%i*Q1
20 S1mag=sqrt(P1^2+Q1^2)
21 pf1=P1/S1mag
22 printf("P1=%dW\nQ1=%dvar\npf1=%0.4f(lag)\n",P1,Q1,
    pf1)
23
24
25 disp("b")
26 Z2=1-%i
27 [R,Theta]=polar(Z2)
28 printf("i2=%d*cos(w*t%d)\n", (vmag/R),Theta)
29 I2eff=(vmag/R)/1.414
30 //p2(t)=100*sqrt(2)*cos(wt)*cos(wt+45)
31 //On solving
32 disp("p2(t)=50+50*sqrt(2)*cos(2*w*t+45) W")
33 P2=Veff*I2eff*cos(Theta)
34 Q2=Veff*I2eff*sin(Theta)
35 S2=P2+%i*Q2
36 S2mag=sqrt(P2^2+Q2^2)
37 pf2=P2/S2mag
38 printf("P2=%dW\nQ2=%dvar\npf2=%0.4f(lag)\n",P2,Q2,
    pf2)
39
40 disp("c")
41 Zmag=(Z1*Z2)/(Z1+Z2)
42 printf("i=%d*cos(w*t)\n", (vmag/Zmag))

```

```

43 Ieff=(vmag/Zmag)/1.414
44 //p(t)=100*sqrt(2)*sqrt(2)*cos(wt)*cos(wt)
45 //On solving
46 disp("p2(t)=200*cos(w*t)^2 W")
47 P=Veff*Ieff
48 Q=0
49 S=P%i*Q
50 Smag=sqrt(P^2+Q^2)
51 pf=P/Smag
52 printf("P=%dW\nQ=%dvar\npf=%0.4f\n",P,Q,PF)

```

---

### Scilab code Exa 11.11 Complex power Apparent power and Power triangle

```

1 clc
2 disp("Problem 11.11")
3 printf("\n")
4
5 printf("Given")
6 disp("v=42.5*cos(1000*t+30 deg)V Z=3+i4 ohm")
7 Vmag=42.5;
8 Z=3+%i*4;
9 R=sqrt(3^2+4^2)
10 Theta=atan(4/3)*(180/%pi)
11 Veffm=Vmag/sqrt(2)
12 Veffph=30
13 Ieffm=Veffm/R
14 Ieffph=30-Theta
15
16 Smag=Veffm*Ieffm
17 Sph=Veffph-Ieffph
18 x=Smag*cos((Sph*%pi)/180)
19 y=Smag*sin((Sph*%pi)/180)
20 z=complex(x,y)
21 pf=cos((Theta*%pi)/180);
22

```

```

23 printf("Real Power is %fW\n",x)
24 printf("Reactive Power is %fvar(inductive)\n",y)
25 printf("Complex Power is %fVA\n",Smag)
26 printf("Power factor is %3.1f(lag)\n",pf)

```

---

### Scilab code Exa 11.12 Parallel connected Networks

```

1 clc
2 disp("Problem 11.12")
3 printf("\n")
4
5 printf("Given")
6 disp("pf1=1 ; pf2=0.5 ; pf3=0.5")
7 disp("P1=10kW; P2=20kW; P3=15kW")
8 disp("Power supply is 6kV")
9 P1=10000; P2=20000; P3=15000;
10 Veff=6000;
11 pf1=1 //implifies that theta1=0
12 t1=0
13 Q1=P1*t1
14
15 pf2=0.5 //implifies that theta1=60
16 t2=1.73;
17 Q2=P2*t2
18
19 pf3=1 //implifies that theta1=53.13
20 t3=1.33;
21 Q3=P3*t3
22
23 PT=P1+P2+P3
24 QT=Q1+Q2+Q3
25 ST=sqrt(PT^2+QT^2)
26 pfT=PT/ST
27 Ieff=ST/Veff
28 Ieffph=acos(pfT)*(180/%pi)

```

```
29 printf("PT=%dW\nQT=%dvar\nST=%dVA\npf=%0.2f(lag) \
nIeff=%3.1f(%3.2f deg)\n",PT,QT,ST,pfT,Ieff,
Ieffph)
```

---

### Scilab code Exa 11.13 Power factor improvement

```
1 clc
2 disp("Problem 11.13")
3 printf("\n")
4
5 printf("Given")
6 disp("Power factor is 0.95(lag)")
7 vmag=240; Zmag=3.5; Zph=25;
8 I1mag=vmag/Zmag; iph=0-Zph;
9 //Smag=Veff*Ieff
10 Smag=(vmag/sqrt(2))*(I1mag/sqrt(2))
11 Sph=0+abs(iph)
12 x=Smag*cos((Sph*pi)/180)
13 y=Smag*sin((Sph*pi)/180)
14 z=complex(x,y)
15 pf=0.95
16 theta=acos(0.95)*(180/pi)
17 //From fig 11.11
18 //Solving for Qc
19 Qc=y-(tan((theta*pi)/180)*x)
20 printf("\n Qc=%dvar(Capacitive )\n",Qc)
```

---

### Scilab code Exa 11.14 Power factor improvement

```
1 clc
2 disp("Problem 11.14")
3 printf("\n")
4
```

```

5 printf("Given")
6 disp("Power =1000kW ; pf=0.5(lag)")
7 disp("Voltage source is 5kV")
8 disp("Improved power factor is 0.8")
9
10 // Before improvement
11 P=1000*10^3;
12 pf=0.5; V=5*10^3;
13 S=(P/pf)*10^-3
14 I=S/V
15
16 // After improvement
17 P=1000*10^3;
18 pf=0.8; V=5*10^3;
19 S=(P/pf)*10^-3
20 I1=S/V
21
22 disp("Current is reduced by ")
23 red=((I-I1)/I)*100
24 printf("Percentage reduction in current is %3.1
    fpercent\n",red)

```

---

### Scilab code Exa 11.16 Maximum power transfer

```

1 clc
2 disp("Problem 11.16")
3 printf("\n")
4
5 printf("Given")
6 disp("Vg=100V(rms)")
7 disp("Zg=1+i Z1=2")
8 Vg=100;
9
10 disp("a")
11 Zg=1+%i;

```

```

12 Z1=2
13 Z=Z1+Zg
14 Zmag=sqrt(real(Z)^2+imag(Z)^2)
15 I=Vg/Zmag
16 PZ1=real(Z1)*(I^2)
17 Pg=real(Zg)*(I^2)
18 PT=PZ1+Pg
19 printf("PZ=%dW\n Pg=%dW\n PT=%dW\n", PZ1, Pg, PT);
20
21 disp("b")
22 // If Z2=a+i*b
23 //Zg*=1-i
24 //Given that
25 //(Z1*Z2)/(Z1+Z2)=1-i
26 //As Z1=2 and solving for Z2
27 disp(-%i,"Z2=")
28
29 disp("c")
30 // If Z2 is taken the value as calculated in b) then
31 Z=1-i
32 Zg=1+%i;
33 Z1=2;
34 Z=1-%i;
35 Zt=Z+Zg
36 Zmag=sqrt(real(Zt)^2+imag(Zt)^2)
37 I=Vg/Zmag
38 PZ=real(Z)*(I^2)
39 Pg=real(Zg)*(I^2)
40 //To calculate PZ1 and PZ2 we need to first
41 // calculate IZ1 nad IZ2
42 VZ=I*(1-%i)
43 IZ1=VZ/Z1
44 IZ1mag=sqrt(real(IZ1)^2+imag(IZ1)^2)
45 PZ1=real(Z1)*(IZ1mag^2)
46 PZ2=PZ-PZ1
47 PT=PZ1+PZ2+Pg
48 printf("PZ=%dW\n Pg=%dW\n PT=%dW\n", PZ, Pg, PT);

```

---

### Scilab code Exa 11.17 Superposition of average powers

```
1 clc
2 disp("Problem 11.17")
3 printf("\\n")
4
5 printf("Given")
6 disp("v1=5*cos(w1*t) v2=10*cos(w2*t+60)")
7 //The circuit is modeled as
8 disp("Resistance is 10ohm and inductance is 5mH")
9 R=10;L=5*10^-3;
10 //Let V be phasor voltage between the terminals
11 Vmag=10;
12 Vph=60;
13 x=Vmag*cos((Vph*%pi)/180);
14 y=Vmag*sin((Vph*%pi)/180);
15 z=complex(x,y)
16
17 disp("a")
18 w1=2000;w2=4000;
19 //Let Z be the impedance of the coil
20 Z1=R+%i*L*w1
21 Z2=R+%i*L*w2
22 V1=5;
23 //By applying superposition i=i1-i2
24 I1=V1/Z1
25 [R1,Theta]=polar(I1)
26 printf("i1=%0.2f*cos(%dt%d deg)\\n",R1,w1,(Theta*180)
    /%pi);
27 P1=(R*R1^2)/2
28
29 V2mag=10;V2ph=60;
30 I2=z/Z2
31 [R2,Theta1]=polar(I2)
```

```

32 printf(" i2=%0.2f*cos (%dt%3.2f deg)\n" ,R2 ,w2 ,(Theta1
    *180)/%pi);
33 P2=(R*R2^2)/2
34
35 // i=i1-i2
36 printf(" i=%0.2f*cos (%dt%d deg)-%0.2f*cos (%dt%3.2f
    deg)\n" ,R1 ,w1 ,(Theta*180)/%pi ,R2 ,w2 ,(Theta1*180)/
    %pi)
37
38 printf("P1=%0.3fW\nP2=%3.1fW\nTotal power (P)=%3.3fW\
    n" ,P1 ,P2 ,(P1+P2))
39
40 disp("b")
41 //From problem 10.7
42 imagin=0.61
43 P=(R*imagin^2)/2
44 printf("Power dissipated in the coil=%3.3fW\n" ,P)
45
46 disp("c")
47 w1=2000;w2=1414;
48 //Let Z be the impedance of the coil
49 Z1=R+%i*L*w1
50 Z2=R+%i*L*w2
51 V1=5;
52 //By applying superposition i=i1-i2
53 I1=V1/Z1
54 [R1 ,Theta]=polar(I1)
55 printf(" i1=%0.2f*cos (%dt%d deg)\n" ,R1 ,w1 ,(Theta*180)
    /%pi);
56 P1=(R*R1^2)/2
57
58 V2mag=10;V2ph=60;
59 x1=V2mag*cos((V2ph*pi)/180);
60 y1=V2mag*sin((V2ph*pi)/180);
61 z1=complex(x1,y1)
62 I3=z1/Z2
63 [R3 ,Theta3]=polar(I3)
64 printf(" i2=%0.2f*cos (%dt+%3.2f deg)\n" ,R3 ,w2 ,(Theta3
    *180)/%pi);

```

```
    *180)/%pi);
65 P3=(R*R3^2)/2
66
67 // i=i1-i2
68 printf(" i=%0.2f*cos(%dt%d deg)-%0.2f*cos(%dt+%3.2f
deg)\n",R1,w1,(Theta*180)/%pi,R3,w2,(Theta3*180)/
%pi)
69
70 printf("P1=%0.3fW\nP2=%3.1fW\nTotal power(P)=%3.3fW\
n",P1,P3,(P1+P3))
```

---

# Chapter 12

## Polyphase Circuits

Scilab code Exa 12.2 Balanced Delta connected load

```
1 clc
2 disp("Example 12.2")
3 printf("\n")
4
5 printf("Given")
6 disp("The system ABC is DELTA connected")
7 disp("Effective line voltage is 120V")
8 disp("The three impedances are 5(45 deg)")
9 Zmag=5; Zph=45;
10 //Let maximum line voltage is Vmax
11 Vmax=120*sqrt(2)
12 //From fig 12.7(a)
13 //VAB=Vmax(120 deg)
14 //VBC=Vmax(0 deg)
15 //VCA=Vmax(240 deg)
16
17 //From figure 12.8
18 IABmag=Vmax/Zmag
19 IABph=120-Zph
20 printf("IAB=%3.2 f (%d deg)\n", IABmag, IABph);
21
```

```

22 IBCmag=Vmax/Zmag
23 IBCph=0-Zph
24 printf("IBC=%3.2f (%d deg)\n", IBCmag, IBCph);
25
26 ICAmag=Vmax/Zmag
27 ICAph=240-Zph
28 printf("ICA=%3.2f (%d deg)\n", ICAmag, ICAph);
29
30 // Applying KCL equation
31 //IA=IAB+IAC
32 //IB=IBC+IBA
33 //IC=ICA+ICB
34
35 x=IABmag*cos((IABph*pi)/180);
36 y=IABmag*sin((IABph*pi)/180);
37 z=complex(x,y)
38
39 x1=ICAmag*cos((ICApH*pi)/180);
40 y1=ICAmag*sin((ICApH*pi)/180);
41 z1=complex(x1,y1)
42
43 x2=IBCmag*cos((IBCph*pi)/180);
44 y2=IBCmag*sin((IBCph*pi)/180);
45 z2=complex(x2,y2)
46
47 IA=z-z1;
48 [RA,ThetaA]=polar(IA)
49
50 IB=z2-z;
51 [RB,ThetaB]=polar(IB)
52
53 IC=z1-z2
54 [RC,ThetaC]=polar(IC)
55
56 disp("Therefore")
57
58 printf("\nIA=%3.2f (%d deg)A\n", RA, ThetaA*(180/pi));
59 printf("\nIB=%3.2f (%d deg)A\n", RB, ThetaB*(180/pi));

```

```
60 printf("\nIC=%3.2f (%d deg)A\n",RC,ThetaC*(180/pi));
```

---

### Scilab code Exa 12.5 Unbalanced Delta connected load

```
1 clc
2 disp("Example 12.5")
3 printf("\n")
4
5 printf("Given")
6 disp("The system ABC is DELTA connected")
7 disp("Maximum line voltage is 339.4V")
8 disp("The three impedances are 10(0 deg),10(30 deg)
      ,15(-30 deg)")
9
10 ZABmag=10; ZABph=0;
11 ZBCmag=10; ZBCph=30;
12 ZCAmag=15; ZCAph=-30;
13 //Let maximum line voltage is Vmax
14 Vmax=339.4
15 //From fig 12.7(a)
16 //VAB=Vmax(120 deg)
17 //VBC=Vmax(0 deg)
18 //VCA=Vmax(240 deg)
19
20 //From figure 12.15
21 IABmag=Vmax/ZABmag
22 IABph=120-ZABph
23 printf("IAB=%3.2f (%d deg)\n",IABmag,IABph);
24
25 IBCmag=Vmax/ZBCmag
26 IBCph=0-ZBCph
27 printf("IBC=%3.2f (%d deg)\n",IBCmag,IBCph);
28
29 ICAmag=Vmax/ZCAmag
30 ICAph=240-ZCAph
```

```

31 printf("ICA=%3.2f (%d deg)\n", ICAmag, ICAph);
32
33 // Applying KCL equation
34 //IA=IAB+IAC
35 //IB=IBC+IBA
36 //IC=ICA+ICB
37
38 x=IABmag*cos((IABph*pi)/180);
39 y=IABmag*sin((IABph*pi)/180);
40 z=complex(x,y)
41
42 x1=ICAmag*cos((ICApH*pi)/180);
43 y1=ICAmag*sin((ICApH*pi)/180);
44 z1=complex(x1,y1)
45
46 x2=IBCmag*cos((IBCph*pi)/180);
47 y2=IBCmag*sin((IBCph*pi)/180);
48 z2=complex(x2,y2)
49
50 IA=z-z1;
51 [RA,ThetaA]=polar(IA)
52
53 IB=z2-z;
54 [RB,ThetaB]=polar(IB)
55
56 IC=z1-z2
57 [RC,ThetaC]=polar(IC)
58
59 disp("Therefore")
60
61 printf("\nIA=%3.2f (%d deg)\n", RA, ThetaA*(180/pi));
62 printf("\nIB=%3.2f (%d deg)\n", RB, ThetaB*(180/pi));
63 printf("\nIC=%3.2f (%d deg)\n", RC, ThetaC*(180/pi));

```

---

**Scilab code Exa 12.6 Unbalanced Wye connected load**

```

1 clc
2 disp("Example 12.6")
3 printf("\n")
4
5 printf("Given")
6 disp("The system CBA is WYE connected")
7 disp("Maximum line voltage is 150V")
8 disp("The three impedances are 6(0 deg),6(30 deg)
      ,5(45 deg)")
9 ZAmag=6;ZAph=0;
10 ZBmag=6;ZBph=30;
11 ZCmag=5;ZCph=45;
12 //Let maximum line voltage is Vmax
13 Vmax=150
14 //Let the line to neutral voltage magnitude be Vn
15 Vn=Vmax/sqrt(3)
16 //From fig 12.7(b)
17 //VAN=Vn(-90 deg)
18 //VBN=Vn(30 deg)
19 //VCN=Vn(150 deg)
20
21 //From figure 12.16
22 IAmag=Vn/ZAmag
23 IApH=-90-ZAph
24 printf("\nIA=%3.2f (%d deg)A\n",IAmag,IAph);
25
26 IBmag=Vn/ZBmag
27 IBph=30-ZBph
28 printf("\nIB=%3.2f (%d deg)A\n",IBmag,IBph);
29
30 ICmag=Vn/ZCmag
31 ICph=150-ZCph
32 printf("\nIC=%3.2f (%d deg)A\n",ICmag,ICph);
33
34 //Now to calculate IN
35 //IN=-(IA+IB+IC)
36 x=IAmag*cos((IAph*pi)/180);
37 y=IAmag*sin((IAph*pi)/180);

```

```
38 z=complex(x,y)
39
40 x1=ICmag*cos((ICph*%pi)/180);
41 y1=ICmag*sin((ICph*%pi)/180);
42 z1=complex(x1,y1)
43
44 x2=IBmag*cos((IBph*%pi)/180);
45 y2=IBmag*sin((IBph*%pi)/180);
46 z2=complex(x2,y2)
47
48 IN=-(z+z1+z2)
49
50 [R,Theta]=polar(IN)
51
52 printf("\nIN=%3.2f(%d deg)\n",R,Theta*(180/%pi));
```

---

# Chapter 13

## Frequency Response Filters and Resonance

Scilab code Exa 13.2 High pass and Low pass networks

```
1 clc
2 disp(" Problem 13.2")
3 printf("\n")
4
5 printf(" Given")
6 disp("|Hv|=1/sqrt(2) (1)") 
7 disp(" Resistance R1=5kohm")
8 R1=5000;
9 disp(" Hv(w)=1/(1+i*(w/wx)) (2)")
10 //wx=1/(R1*C2)
11 //On solving we get
12 disp(" wx=2*10^-4/C2 (3)")
13
14 disp(" a")
15 C2=10*10^-9;
16 //Taking modulus of (2)
17 disp(" |Hv(w)|=sqrt(1+(w/wx)^2)")
18 //Equating (1) and (2)
19 wx=2*10^-4/C2;
```

```

20 fx=(wx/(2*pi))*10^-3
21 printf(" Frequency (a) is %3.2 fkHz\n",fx)
22
23 disp("b")
24 C2b=1*10^-9;
25 //As frequency is inversely proportional to C2 (from
26 // (3))
26 fx1=(C2/C2b)*fx
27 printf(" Frequency (b) is %3.2 fkHz\n",fx1)

```

---

### Scilab code Exa 13.7 Bandpass filters and Resonance

```

1 clc
2 disp(" Problem 13.7")
3 printf("\n")
4
5 s=%s;
6 printf(" Given")
7 H=(10*s)/(s^2+300*s+10^6)
8 disp(H,"H(s)=")
9 //From the above transfer function
10 //Comparing the denominator with s^2+a*s+b with w=
11 //sqrt(b)
11 a=300;b=10^6;
12 //Therefore center frequency is
13 w0=sqrt(10^6)
14 //The lower and upper frequencies are
15 wl=sqrt(a^2/4+b)-a/2
16 wh=sqrt(a^2/4+b)+a/2
17 B=wh-wl           // It can be inferred that B=a
18 Q=sqrt(b)/a
19 printf("\nCenter frequency= %drad/s\n",w0);
20 printf("Low power frequency = %3.2 frad/s\nHigh power
21 frequency = %3.2 frad/s\n",wl,wh);
21 printf("Bandwidth= %drad/s\nQuality factor =%3.2 f\n"

```

,B ,Q)

---

### Scilab code Exa 13.8 Bandpass filters and Resonance

```
1 clc
2 disp(" Problem 13.8 ")
3 printf(" \n")
4
5 s=%s;
6 printf(" Given")
7 H=(10*s)/(s^2+30*s+10^6)
8 disp(H,"H(s) =")
9 //From the above transfer function
10 //Comparing the denominator with s^2+a*s+b with w=
    sqrt(b)
11 a=30; b=10^6;
12 //Therefore center frequency is
13 w0=sqrt(10^6)
14 //The lower and upper frequencies are
15 wl=sqrt(a^2/4+b)-a/2
16 wh=sqrt(a^2/4+b)+a/2
17 B=wh-wl
18 Q=sqrt(b)/a
19 printf(" \nCenter frequency= %drad/s \n",w0);
20 printf(" Low power frequency = %3.2 frad/s \nHigh power
    frequency = %3.2 frad/s \n",wl,wh);
21 printf(" Bandwidth= %drad/s \nQuality factor =%3.2 f \n"
    ,B,Q)
```

---

# Chapter 14

## Two Port Networks

Scilab code Exa 14.1 Z parameters

```
1 clc
2 disp("Example 14.1")
3 printf("\\n")
4
5 s=%s;
6 //Applying KVL equation to the two loops we get
7 //V1=2*I1+s*(I1+I2)
8 //V2=3*I2+s*(I1+I2)
9
10 //On solving we get
11 disp("(s+2)*I1+s*I2=V1 (1)");
12 disp("s*I1+(s+3)*I2=V2 (2)");
13
14 //The equations which contain Z parameters are
15 //V1=Z11*I1+Z12*I2
16 //V2=Z21*I1+Z22*I2
17
18 //On comparing (1) and (2) with above equations
19 Z11=s+2;
20 Z12=s;
21 Z21=s;
```

```
22 Z22=s+3;
23
24 disp(Z11,"Z11=")
25 disp(Z12,"Z12=")
26 disp(Z21,"Z21=")
27 disp(Z22,"Z22=")
```

---

### Scilab code Exa 14.2 Reciprocal and non reciprocal networks

```
1 clc
2 disp("Example 14.2")
3 printf("\n")
4
5 s=%s;
6 //Applying KVL equation to the two loops we get
7 //V1=2*I1+s*(I1+I2)-I2
8 //V2=3*I2+s*(I1+I2)
9
10 //On solving we get
11 disp("(s+2)*I1+(s-1)*I2=V1      (1)");
12 disp("s*I1+(s+3)*I2=V2      (2)");
13
14 //The equations which contain Z parameters are
15 //V1=Z11*I1+Z12*I2
16 //V2=Z21*I1+Z22*I2
17
18 //On comparing (1) and (2) with above equations
19 Z11=s+2;
20 Z12=s-1;
21 Z21=s;
22 Z22=s+3;
23
24 disp(Z11,"Z11=")
25 disp(Z12,"Z12=")
26 disp(Z21,"Z21=")
```

```
27 disp(Z22,"Z22=")
```

---

### Scilab code Exa 14.4 Y parameters

```
1 clc
2 disp("Example 14.4")
3 printf("\n")
4
5 s=%s;
6 Ya=3/(5*s+6);
7 Yb=2/(5*s+6);
8 Yc=s/(5*s+6);
9
10 //Writing KCL equations
11 disp("I1=(Ya+Yc)*V1-Yc*V2" (1))
12 disp("I2=-Yc*V1+(Yb+Yc)*V2" (2))
13
14 //The equations which contain Y parameters are
15 //I1=Y11*V1+Y12*V2
16 //I2=Y21*V1+Y22*V2
17
18 //On comparing (1) and (2) with above equations
19 disp("Y11=Ya+Yc")
20 disp("Y12=-Yc=Y21")
21 disp("Y22=Yb+Yc")
22
23 //Substituting Ya , Yb and Yc
24 Y11=Ya+Yc
25 Y12=-Yc
26 Y21=-Yc
27 Y22=Yb+Yc
28
29 disp(Y11,"Y11=")
30 disp(Y12,"Y12=")
31 disp(Y21,"Y21=")
```

32 **disp**(Y22,"Y22=")

---

### Scilab code Exa 14.6 Conversion between Z and Y parameters

```
1 clc
2 disp("Example 14.6")
3 printf("\\n")
4
5 s=%s;
6 //From example 14.4
7
8 Y11=(3 + s)/(5*s+6)
9 Y12=- s/(6 + 5*s)
10 Y21=- s/(6 + 5*s)
11 Y22=(2+s)/(6+5*s)
12
13 DYY=Y11*Y22-Y12*Y21
14
15 Z11=Y22/DYY;
16 Z12=-Y12/DYY;
17 Z21=-Y21/DYY;
18 Z22=Y11/DYY;
19
20 disp(Z11,"Z11=")
21 disp(Z12,"Z12=")
22 disp(Z21,"Z21=")
23 disp(Z22,"Z22=")
```

---

### Scilab code Exa 14.7 H parameters

```
1 clc
2 disp("Example 14.7")
3 printf("\\n")
```

```

4
5 //From figure 14.9
6 disp("V1=50*I1          (1)");
7 disp("I2=300*I1          (2)");
8
9 //The equations which contain h parameters are
10 //V1=h11*I1+h12*V2
11 //I2=h21*I1+h22*V2
12
13 //On comparing (1) and (2) with above equations
14
15 printf("\nh11=%d\n",50);
16 printf("h12=%d\n",0);
17 printf("h21=%d\n",300);
18 printf("h22=%d\n",0);

```

---

### Scilab code Exa 14.8 g parameters

```

1 clc
2 disp("Example 14.8")
3 printf("\n")
4
5 //From figure 14.10
6 //By inspection
7 //V1=10^9*I1
8 //V2=10(I2-10^-3*V1)
9
10
11 //On solving we get
12 disp("I1=10^-9*V1          (1)");
13 disp("V2=10*I2-10^-2*V1      (2)");
14
15
16 //The equations which contain g parameters are
17 //I1=g11*V1+g12*I2

```

```

18 //V2=g21*V1+g22*I2
19
20 //On comparing (1) and (2) with above equations
21
22 printf("\n g11=%2.1e\n", 10^-9);
23 printf(" g12=%d\n", 0);
24 printf(" g21=%2.1e\n", -10^-2);
25 printf(" g22=%d\n", 10);

```

---

### Scilab code Exa 14.10 Choice of parameter type

```

1 clc
2 disp("Example 14.10")
3 printf("\n")
4
5 s=%s;
6 //Applying KVL equation to the two loops we get
7 //V1=3*I1+3*(I1+I2)
8 //V2=7*I1+3*(I1+I2)+2*I2
9
10 //On solving we get
11 disp("6*I1+3*I2=V1          (1)");
12 disp("10*I1+5*I2=V2          (2)");
13
14 //The equations which contain Z parameters are
15 //V1=Z11*I1+Z12*I2
16 //V2=Z21*I1+Z22*I2
17
18 //On comparing (1) and (2) with above equations
19 Z11=6;
20 Z12=3;
21 Z21=10;
22 Z22=5;
23
24 disp(Z11,"Z11=")

```

```
25 disp(Z12,"Z12=")
26 disp(Z21,"Z21=")
27 disp(Z22,"Z22=")
28
29 disp("As DZZ results in zero(0) therefore Y
      parameters are not defined")
```

---

# Chapter 15

## Mutual Inductance and Transformers

Scilab code Exa 15.4 Energy in a pair of coupled coils

```
1 clc
2 disp(" Example 15.4")
3 printf("\n")
4
5 printf(" Given")
6 disp("L1=0.1H L2=0.2H")
7 disp(" i1=4A i2=10A")
8 L1=0.1;L2=0.2
9 i1=4;i2=10;
10 //The energy stored in coupled coils is
11 disp("W=(L1*i1^2)/2+(L2*i2^2)/2+M*i1*i2")
12
13 disp(" a")
14 M=0.1;
15 W=(L1*i1^2)/2+(L2*i2^2)/2+M*i1*i2;
16 printf(" Total Energy in the coils=%3.2fJ\n",W);
17
18 disp(" b")
19 M=sqrt(2)/10;
```

```

20 W=(L1*i1^2)/2+(L2*i2^2)/2+M*i1*i2;
21 printf("Total Energy in the coils=%3.2fJ\n",W);
22
23 disp("c")
24 M=-0.1;
25 W=(L1*i1^2)/2+(L2*i2^2)/2+M*i1*i2;
26 printf("Total Energy in the coils=%3.2fJ\n",W);
27
28 disp("a")
29 M=-sqrt(2)/10;
30 W=(L1*i1^2)/2+(L2*i2^2)/2+M*i1*i2;
31 printf("Total Energy in the coils=%3.2fJ\n",W);

```

---

### Scilab code Exa 15.7 Ampere Turn Dot rule

```

1 clc
2 disp("Example 15.7")
3 printf("\n")
4
5 printf("Given")
6 disp("N1=20 N2=N3=10")
7 disp("I2=10(-53.13 deg) I3=10(-45 deg)")
8 N1=20; N2=10; N3=10;
9 I2mag=10; I2ph=-53.13;
10 I3mag=10; I3ph=-45;
11 //From figure 15.14
12 disp("N1*I1-N2*I2-N3*I3=0")
13 //Solving for I1
14 Xmag=N2*I2mag
15 Xph=I2ph
16 x=Xmag*cos((Xph*pi)/180);
17 y=Xmag*sin((Xph*pi)/180);
18 z=complex(x,y)
19
20 Ymag=N3*I3mag

```

```

21 Yph=I3ph
22 x1=Ymag*cos((Yph*pi)/180);
23 y1=Ymag*sin((Yph*pi)/180);
24 z1=complex(x1,y1)
25
26 I1=(z+z1)/N1
27 [R,Theta]=polar(I1);
28 printf("I1=%3.2f(%3.2f deg) A\n",R,(Theta*180)/pi);

```

---

### Scilab code Exa 15.8 Reflected Impedance

```

1 clc
2 disp("Example 15.8")
3 printf("\n")
4
5 printf("Given")
6 disp("L1=0.2H L2=0.1H")
7 disp("M=0.1H R=10ohm")
8 disp("v1=142.3*sin(100*t)")
9 L1=0.2;L2=0.1
10 M=0.1;R=10;
11 v1mag=142.3;
12 w=100;
13 //Let Input impedance be Z1 and can be calculated as
14 //From the equations in 15.10
15 disp("Z1=%i*w*L1+((M*w)^2)/(Z2+%i*w*L2)")
16 Z1=%i*w*L1+((M*w)^2)/(R+%i*w*L2)
17 [R,Theta]=polar(Z1)
18 //If I1 is the input current
19 I1mag=v1mag/R
20 I1ph=-(Theta*180)/pi
21 //In time domain form
22 printf("i1=%3.1f*sin(%d*t%3.1f deg) (A)",I1mag,w,
I1ph);

```

---

### Scilab code Exa 15.9 Reflected Impedance

```
1 clc
2 disp("Example 15.9")
3 printf("\\n")
4
5 s=%s;
6 printf("Given")
7 disp("L1=0.2H L2=0.1H")
8 disp("M=0.1H R=10ohm")
9 disp("v1=u(t) a unit step function")
10 L1=0.2;L2=0.1
11 M=0.1;R=10;
12 v1=1;
13 w=100;
14 //Let Input impedance be Z1 and can be calculated as
15 //From the equations in 15.10
16 disp("Z1(s)=L1*s-((M*s)^2)/(R+L2*s)")
17 Z1=L1*s-((M*s)^2)/(R+L2*s)
18 //Proper rearranging of co-efficients
19 Num=Z1('num')/0.01
20 Den=Z1('den')*100
21
22 disp(Num/Den,"Z1(s)")
23 Y1=1/Z1
24 disp(Den/Num,"Y1(s)")
25
26 //As the input is unit step function the value is 1V
    for t>0
27 //In exponential form the value is represented as
    exp(s*t) with s=0 as the pole of Y1(s)
28
29 //Therefore forced response
30 k=1/L1;
```

```
31 printf("Forced response i1 , f=(%d*t ) (A)\n" ,k);
```

---

# Chapter 17

## The Laplace Transform Method

check Appendix [AP 2](#) for dependency:

ch17\_2.sce

Scilab code Exa 17.2 Convergence of the integral

```
1 syms t s ;
2 x=laplace ('3*%e^(2*t)', t , s ) ;
3 disp (x , " X(s) = " )
```

---

check Appendix [AP 1](#) for dependency:

ch17\_4.sce

Scilab code Exa 17.4 Partial Fractions Expansions

```
1 clc
2 syms t
3 s=%s;
4 // Factorizing the denominator
5 I=(s-10)/((s^2)*(s-%i)*(s+%i));
```

```

6 disp(I,"I(s)="" )
7 //The principal part at s=0 is
8 //B1/s+B2/s^2
9 //Taking the limit s->0 to (s-10)/((s-%i)*(s+%i))
10
11 B2=-10
12
13 //Taking the limit s->0 to (s*(s-10))/(s^2)*(s^2+1)
14 // +(10/s)
15 B1=1
16
17 //The principal part at s=%i is
18 //A/(s-%i)
19 //Taking the limit s->%i to (s-10)/((s^2)*(s+%i))
20
21 A=(-0.5-%i*5)
22
23 //As the other co-efficient is conjugate of the
24 //above we can write the partial fraction expansion
25 //of I(s)
26 I=(1/s)-(10/s^2)-(0.5+%i*5)/(s-%i)-(0.5-%i*5)/(s+%i)
27 ;
28 //Taking inverse of each term
29 I1=ilaplace('1/s',s,t)
30 I2=ilaplace('10/s^2',s,t)
31 I3=ilaplace('((0.5+%i*5)/(s-%i))',s,t)
32 I4=ilaplace('((0.5-%i*5)/(s+%i))',s,t)
33 I=I1-I2-I3-I4
34 disp(I,"i(t)="" )

```

---

# Appendix

## Scilab code AP 1 Partial Fractions Expansions

```
1 clc
2 syms t
3 s=%s;
4 // Factorizing the denominator
5 I=(s-10)/((s^2)*(s-%i)*(s+%i));
6 disp(I,"I(s)='")
7 //The principal part at s=0 is
8 //B1/s+B2/s^2
9 //Taking the limit s->0 to (s-10)/((s-%i)*(s+%i))
10
11 B2=-10
12
13 //Taking the limit s->0 to (s*(s-10))/(s^2)*(s^2+1)
14 // +(10/s)
15 B1=1
16
17 //The principal part at s=%i is
18 //A/(s-%i)
19 //Taking the limit s->%i to (s-10)/((s^2)*(s+%i))
20
21 A=(-0.5-%i*5)
22
23 //As the other co-efficient is conjugate of the
// above we can write the partial fraction expansion
// of I(s)
```

```
24 I=(1/s)-(10/s^2)-(0.5+%i*5)/(s-%i)-(0.5-%i*5)/(s+%i)
    ;
25 //Taking inverse of each term
26 I1=ilaplace('1/s',s,t)
27 I2=ilaplace('10/s^2',s,t)
28 I3=ilaplace('(0.5+%i*5)/(s-%i)',s,t)
29 I4=ilaplace('(0.5-%i*5)/(s+%i)',s,t)
30 I=I1-I2-I3-I4
31 disp(I,"i(t)=""
```

---

### Scilab code AP 2 Convergence of the integral

```
1 syms t s ;
2 x=laplace ('3*%e^(2*t)' , t , s ) ;
3 disp (x , " X(s)="" )
```

---