

Scilab Textbook Companion for
Power Electronics
by B. R. Gupta And V. Singhal¹

Created by
Avishek Goyal
Electrical
Electrical Engineering
Thapar University patiala
College Teacher
Dr. Sunil Kumar Singla
Cross-Checked by
Prof. Chaya S

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Power Electronics

Author: B. R. Gupta And V. Singhal

Publisher: S. K. Kataria & Sons, New Delhi

Edition: 3

Year: 2002

ISBN: 8185749531

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Power electronics devices	5
2 Controlled Rectifiers	22
3 Inverters	43
4 Choppers	51
5 AC Regulators	60
6 Cycloconverters	68
7 Applications of Thyristors	70
8 Integrated circuits and operational amplifiers	84
9 Number systems	94

List of Scilab Codes

Exa 1.1	Calculate the equivalent capacitance of depletion layer	5
Exa 1.2	Calculate the voltage required to Turn ON the thyristor	5
Exa 1.3	Find gate voltage gate current and resistance to be connected in series	6
Exa 1.4	Calculate the minimum width of the gate pulse	6
Exa 1.5	Calculate the minimum width of the gate pulse	7
Exa 1.6	Find if thyristor will turn ON and the value of resistance	7
Exa 1.7	Find if thyristor will turn OFF and maximum value of resistance	8
Exa 1.8	Can a negative gate current turn off a thyristor	8
Exa 1.9	Find RMS current and form factor	8
Exa 1.10	Find the power supplied to load and average current	9
Exa 1.11	Calculate the average power loss	10
Exa 1.12	Find the resistance to be connected in series and average power loss	10
Exa 1.13	Find the value of power dissipation when the current flows for different periods of cycle	11
Exa 1.14	Find different current ratings	11
Exa 1.15	Find source resistance gate current and voltage	12
Exa 1.16	Find the thermal resistance and temperature	12
Exa 1.17	Find the maximum loss	13
Exa 1.18	Find the maximum loss	13
Exa 1.19	Design a UJT relaxation oscillator	13

Exa 1.20	Find the values of different components of circuit	14
Exa 1.21	Find the time of conduction of thyristor	15
Exa 1.22	Find the values of L and C	15
Exa 1.23	Find the value of C	16
Exa 1.24	Calculate the value of C and L	16
Exa 1.25	Find the commutation time and the current rating of the thyristor	16
Exa 1.26	Find the value of R and C	17
Exa 1.27	Find the value of R C and snubber power loss and power rating of resistance	17
Exa 1.28	Find the maximum permissible values	18
Exa 1.29	Find number of thyristor in series and parallel	19
Exa 1.30	Find the value of R and C for static and dynamic equalizing circuits	19
Exa 1.31	Find the value of resistance to be connected in series	19
Exa 1.32	Find the steady and transient state rating and derating of thyristor	20
Exa 1.33	Find number of thyristor in series and parallel	20
Exa 1.34	Find Stored charge and peak reverse current	21
Exa 2.3	Calculate the different parameters of half wave diode rectifier	22
Exa 2.4	Calculate the different parameters of full wave centre tapped diode rectifier	23
Exa 2.5	Find the RMS and average voltage and current	24
Exa 2.6	Find the average current	24
Exa 2.7	Find the average current	24
Exa 2.8	Calculate the various parameters of a single phase half wave rectifier	25
Exa 2.9	Find the RMS and average voltage and current of a single phase full wave rectifier	26
Exa 2.10	Calculate the different parameters of full wave converter with centre tapped transformer	26
Exa 2.11	Calculate the voltage rating of full wave central tap and bridge rectifiers	27
Exa 2.12	Find the output voltage firing angle and load current	27

Exa 2.13	Find the average power output of full wave mid point and bridge converter	28
Exa 2.14	Find dc output voltage and power	28
Exa 2.15	Find dc output voltage and power	29
Exa 2.16	Calculate the firing angle and power factor . .	29
Exa 2.17	Find the average value of load current	30
Exa 2.18	Calculate the different parameters of full wave converter with bridge transformer	30
Exa 2.19	Find the value of dc voltage rms voltage and form factor of a single phase semi converter	31
Exa 2.20	Calculate the different parameters of single phase semi converter bridge	31
Exa 2.21	Calculate the different parameters of single phase full converter	31
Exa 2.22	Calculate the different parameters of single phase full controlled bridge converter	32
Exa 2.23	Calculate the different parameters of single phase full controlled bridge converter	33
Exa 2.24	Calculate peak circulating current and peak current of converter	34
Exa 2.25	Calculate inductance of current limiting reactor and peak current of converter	35
Exa 2.26	Calculate inductance of current limiting reactor and resistance	35
Exa 2.27	Find the parameters of three phase bridge rectifier circuit	36
Exa 2.28	Find the parameters of three phase full converter	36
Exa 2.29	Find the firing angle of a 3 phase fully controlled bridge converter	37
Exa 2.30	Find the parameters of six pulse thyristor converter	37
Exa 2.31	Find the parameters of three phase semi converter bridge circuit	38
Exa 2.32	Find the parameters of three phase fully controlled bridge converter	39
Exa 2.33	Calculate the overlap angles	40

Exa 2.34	Find the value of circulating currents for 3 phase dual converter	41
Exa 2.35	Find the value of inductance	42
Exa 3.1	Find the maximum output frequency	43
Exa 3.2	Find the frequency of output	43
Exa 3.3	Find the available circuit turn off time and maximum possible frequency	44
Exa 3.4	Design a parallel inverter	44
Exa 3.5	Calculate the various parameters of single phase half bridge inverter	45
Exa 3.6	Calculate the various parameters of single phase full bridge inverter	46
Exa 3.7	Calculate the various parameters of full bridge inverter	46
Exa 3.8	Calculate the value of C for proper load commutation	47
Exa 3.9	Calculate peak value of load current	47
Exa 3.10	Find the different parameters of 3 phase bridge inverter for 120degree conduction mode . . .	48
Exa 3.11	Find the different parameters of 3 phase bridge inverter for 180degree conduction mode . . .	48
Exa 3.12	Find the RMS value of load current and thyristor current of 3 phase bridge inverter for 180degree conduction mode	49
Exa 3.13	Find the parameters of single phase full bridge inverter	49
Exa 3.14	Calculate the RMS value of the output voltage	50
Exa 3.15	Calculate the RMS value of the output voltage	50
Exa 4.1	Calculate the period of conduction and blocking	51
Exa 4.2	Calculate the period of conduction and blocking	51
Exa 4.3	Calculate the duty cycle for the rated torque and half of rated torque	52
Exa 4.4	Find the different parameters of a dc chopper	52
Exa 4.5	Find the chopper frequency	53
Exa 4.6	Find the different parameters of a chopper feeding a RL load	53

Exa 4.7	Calculate the load inductance	54
Exa 4.8	Calculate the current	55
Exa 4.9	Find the speed of motor	55
Exa 4.10	Calculate average load voltage	56
Exa 4.11	Find maximum minimum and average load current and load voltage	56
Exa 4.12	Find maximum minimum and average output voltage	57
Exa 4.13	Calculate the series inductance in the circuit	57
Exa 4.14	Calculate the motor speed and current swing	58
Exa 4.15	Calculate the value of capacitance and inductance	58
Exa 4.16	Calculate the period of conduction of a step up chopper	59
Exa 4.17	Calculate the period of conduction of a step up chopper	59
Exa 5.1	Calculate the different parameters of AC voltage regulator using integral cycle control . .	60
Exa 5.2	Calculate the different parameters of single phase half wave AC regulator	61
Exa 5.3	Calculate the different parameters of single phase full wave AC regulator	62
Exa 5.4	Calculate the different parameters of single phase full wave AC regulator	62
Exa 5.5	Find RMS output voltage and average power	63
Exa 5.6	Find the firing angle	64
Exa 5.7	Find the conduction angle and RMS output voltage	64
Exa 5.8	Calculate the different parameters of single phase full wave AC regulator	65
Exa 5.10	Find the current and voltage rating	65
Exa 5.11	Calculate the different parameters of 3 phase star connected resistance load with firing angle 30 degree	66
Exa 5.12	Calculate the different parameters of 3 phase star connected resistance load with firing angle 60 degree	66

Exa 6.1	Find the input voltage SCR rating and Input Power Factor	68
Exa 6.2	Find RMS value of output voltage for firing angle 30 and 45 degree	68
Exa 6.3	Find RMS value of output voltage for firing angle 0 and 30 degree	69
Exa 7.1	Find the value of Voltage which will turn On the crowbar	70
Exa 7.2	Find the value of input voltage	70
Exa 7.3	Find the value of R and C	71
Exa 7.4	Find Duty cycle and Ratio for different output powers	71
Exa 7.5	Find RMS value of output voltage	72
Exa 7.6	Find the power supplied to heater for different firing angles	72
Exa 7.7	Find the firing angles when different powers are supplied to heater	73
Exa 7.8	Find the current rating and peak inverse voltage	74
Exa 7.9	Find firing angle and power factor of converter in the armature circuit	74
Exa 7.10	Find the torque developed and motor speed	75
Exa 7.11	Find armature current and Firing angle of the semi converter	75
Exa 7.12	Find the firing angle of converter in the armature circuit and power fed back to the source	76
Exa 7.13	Find the firing angle of converter in the armature circuit	76
Exa 7.14	Find the input power speed and torque of separately excited dc motor	77
Exa 7.15	Find the average voltage power dissipated and motor speed of the chopper	78
Exa 7.16	Find the speed for different values of torque	78
Exa 7.17	Find the speed at no load and firing angle	80
Exa 7.18	Find the motor speed	80
Exa 7.19	Find the load torque stator applied voltage and rotor current	81

Exa 7.20	Find the load torque stator applied voltage and rotor current	81
Exa 7.21	Find the starting torques at different frequencies	82
Exa 8.1	Find dc currents and voltages	84
Exa 8.2	Calculate the different parameters of differential amplifier	84
Exa 8.3	Find the closed loop gain output and error voltage	85
Exa 8.4	Find the closed loop gain output and error voltage	86
Exa 8.5	Find the input and output impedances	86
Exa 8.6	Find closed loop gain and desensitivity	87
Exa 8.7	Find the closed loop gain and upper cut off frequency	87
Exa 8.8	Find the slew rate	88
Exa 8.9	Find the slew rate distortion of the op amp	88
Exa 8.10	Find the slew rate distortion of the op amp and amplitude of the input signal	89
Exa 8.11	Find the different parameters of inverting amplifier	89
Exa 8.12	Find the different parameters of non inverting amplifier	90
Exa 8.13	Find the different parameters of ac amplifier	90
Exa 8.14	Find the output voltage	91
Exa 8.17	Find the output voltage	92
Exa 8.18	Find CMRR in dB	92
Exa 8.21	Find the different parameters of high pass filter	92
Exa 8.22	Find the different parameters of low pass filter	93
Exa 9.1	Convert decimal number into equivalent binary number	94
Exa 9.2	Convert decimal number into equivalent binary number	94
Exa 9.3	Convert binary number into equivalent decimal number	95
Exa 9.4	Convert decimal number into equivalent binary number	95

Exa 9.5	Calculate the subtraction of two binary numbers	95
Exa 9.6	Calculate the subtraction of two binary numbers	96
Exa 9.7	Express the decimals in 16 bit signed binary system	96
Exa 9.8	Calculate the twos complement representation	97
Exa 9.9	Find the largest positive and negative number for 8 bits	97
Exa 9.10	Calculate addition and subtraction of the numbers	98
Exa 9.11	Calculate addition and subtraction of the numbers	98
Exa 9.12	Convert decimal number into equivalent binary number	99
Exa 9.13	Convert decimal number into equivalent binary number	100
Exa 9.14	Convert decimal number into equivalent binary number	101
Exa 9.15	Find the addition of binary numbers	102
Exa 9.16	Convert binary number into equivalent decimal number	102
Exa 9.17	Convert hexadecimal number into equivalent decimal number	103
Exa 9.18	Convert decimal number into equivalent hexadecimal number	103
Exa 9.19	Convert decimal number into equivalent hexadecimal number	104
Exa 9.20	Convert hexadecimal number into equivalent decimal number	104

Chapter 1

Power electronics devices

Scilab code Exa 1.1 Calculate the equivalent capacitance of depletion layer

```
1 // 1.1
2 clc;
3 Ic=8*10^-3;
4 // let dv/dt =A
5 A=190*10^6;
6 C=Ic/A*10^12;
7 printf("Equivalent capacitance of depletion layer =
%.1f uF", C)
```

Scilab code Exa 1.2 Calculate the voltage required to Turn ON the thyristor

```
1 // 1.2
2 clc;
3 disp('When thyristor is not conducting there is no
      current through it')
4 disp('so Vo=20V')
5 VG=0.75;
6 IG=7*10^-3;
```

```

7 RG=2000;
8 Vs=VG+IG*RG;
9 printf("Voltage required to Turn On The thyristor =
    %.2f V", Vs)
10 R= 200;
11 VR=5*10^-3*R;
12 printf("/nVoltage drop across R = %.0f V", VR)
13 disp('Hence Vcc should be reduced to less than 1V')
14 Vconduct=0.7;
15 Vreq=VR+Vconduct;
16 printf("Voltage required = %.1f V", Vreq)
17 disp('Hence Vcc should be reduced to less than 1.7V'
)

```

Scilab code Exa 1.3 Find gate voltage gate current and resistance to be connected

```

1 // 1.3
2 clc;
3 P_loss_avg=0.6;
4 P_loss_conduction=0.6*2*pi/pi;
5 Ig=0.314;
6 printf("Ig=% .3f A", Ig)
7 Vg=1+9*Ig;
8 printf("\nVg=% .3f V", Vg)
9 Rg=(24-9*Ig)/Ig;
10 printf("\nResistance to be connected in series=% .2f
    ohm", Rg)

```

Scilab code Exa 1.4 Calculate the minimum width of the gate pulse

```

1 // 1.4
2 clc;
3 V=100;

```

```
4 L=10;
5 i=80*10^-3;
6 t=i*L/V*10^3;
7 printf("t= %.0f ms", t)
8 disp('So the width of the pulse should be more than
     8 ms')
```

Scilab code Exa 1.5 Calculate the minimum width of the gate pulse

```
1 //1.5
2 clc;
3 V=100;
4 R=10;
5 i=50*10^-3;
6 t=-0.5*log(1-((i*R/V)))*10^3
7 printf("t= %.1f ms", t)
8 disp('So the minimum width of the gate pulse is 2.5
     ms')
```

Scilab code Exa 1.6 Find if thyristor will turn ON and the value of resistance

```
1 //1.6
2 clc;
3 V=90;
4 R=25;
5 t=40*10^-6;
6 L=0.5;
7 i=(V/R)*(1-exp(-R*t/L))
8 iL=40*10^-3;
9 printf("The circuit current is= %.4f A", i)
10 disp('Since the circuit current is less than
        latching current of 40mA so thyristor will not
        turn ON')
```

```
11 R=V/(iL-i);
12 printf("R= %.0 f Ohm", R)
13 disp('R should be less than 2743 ohm')
```

Scilab code Exa 1.7 Find if thyristor will turn OFF and maximum value of resistance

```
1 //1.7
2 clc;
3 V=100;
4 R=20;
5 t=50*10^-6;
6 L=0.5;
7 i=(V/R)*(1-exp(-R*t/L))
8 iH=50*10^-3;
9 printf("The circuit current is= %.5 f A", i)
10 disp('Since the circuit current is less than holding
        current of 50mA so thyristor will turn OFF')
11 R=V/(iH-i);
12 printf("Maximum value of R= %.3 f Ohm", R)
```

Scilab code Exa 1.8 Can a negative gate current turn off a thyristor

```
1 //1.8
2 clc;
3 disp('A negative gate current cannot turn off a
        thyristor. This is due to the reason that cathode
        region is much bigger in area than gate region')
```

Scilab code Exa 1.9 Find RMS current and form factor

```

1 // 1.9
2 clc;
3 I=120;
4 gama=180;
5 th=360;
6 I_rms=I*(gama/th)^0.5;
7 printf("The RMS value of current= %.2f A",I_rms)
8 I_avg=I*(gama/th);
9 Form_factor=I_rms/I_avg;
10 printf("\nForm factor= %.3f A",Form_factor)

```

Scilab code Exa 1.10 Find the power supplied to load and average current

```

1 // 1.10
2 clc;
3 disp('If the thyristor is fired at 60 degree')
4 Irms=(0.8405*((%pi-%pi*60/180)-sin(2*pi)/2+sin(2*
    %pi*60/180)/2))^0.5;
5 R=100;
6 P=Irms^2*R;
7 printf("Power supplied to load=%0.0f W",P)
8 disp('If the thyristor is fired at 45 degree')
9 Irms=(0.8405*((%pi-%pi*45/180)-sin(2*pi)/2+sin(2*
    %pi*45/180)/2))^0.5;
10 R=100;
11 P=Irms^2*R;
12 printf("Power supplied to load=%0.1f W",P)
13 disp('If the thyristor is fired at 60 degree')
14 Iavg=3.25/(2*pi)*(-cos(pi)+cos(pi*60/180))
15 printf("Average Current=%0.3f A",Iavg)
16 disp('If the thyristor is fired at 45 degree')
17 Iavg=3.25/(2*pi)*(-cos(pi)+cos(pi*45/180))
18 printf("Average Current=%0.3f A",Iavg)

```

Scilab code Exa 1.11 Calculate the average power loss

```
1 //1.11
2 clc;
3 //when conduction period is 2*pi
4 amplitude=200;
5 pd=1.8;
6 power_loss_average= amplitude*pd*2*%pi/(2*%pi);
7 printf("power loss average when conduction period is
2*pi= %.0f W",power_loss_average)
8
9 //when conduction period is pi
10 amplitude=400;
11 pd=1.9;
12 power_loss_average= amplitude*pd*%pi/(2*%pi);
13 printf("\n power loss average when conduction period
is pi= %.0f W",power_loss_average)
```

Scilab code Exa 1.12 Find the resistance to be connected in series and average pow

```
1 //1.12
2 clc;
3 P_loss_peak=6;
4 Ig=0.763;
5 Vg=1+9*Ig;
6 Rg=(11-9*Ig)/Ig;
7 printf("\nResistance to be connected in series=%f ohm",
Rg)
8 duty=0.3;
9 P_loss_average=P_loss_peak*duty;
10 printf("\nAverage power loss =%.1f W",
P_loss_average)
```

Scilab code Exa 1.13 Find the value of power dissipation when the current flows for

```
1 //1.13
2 clc;
3 disp('when current is constant 20A')
4 It=20;
5 Vt=0.9+0.02*It;
6 P_dissipation=Vt*It;
7 printf("Power dissipation=%f W",P_dissipation)
8 disp('when current is constant 20A for one half
      cycle in each full cycle')
9 P_dissipation=Vt*It/2;
10 printf("Power dissipation=%f W",P_dissipation)
11 disp('when current is constant 20A for one third
      cycle in each full cycle')
12 P_dissipation=Vt*It/3;
13 printf("Power dissipation=%f W",P_dissipation)
```

Scilab code Exa 1.14 Find different current ratings

```
1 //1.14
2 clc;
3 Isub=2000;
4 T=10*10^-3;
5 t=5*10^-3;
6 I=(Isub^2*t/T)^0.5;
7 printf("one cycle surge current rating=%f A", I)
8 //a=I^2*t
9 a=I^2*T;
10 printf("\nI^2*t=%f A^2 Sec", a)
```

Scilab code Exa 1.15 Find source resistance gate current and voltage

```
1 //1.15
2 clc;
3 P=0.3;
4 Vs=12;
5 disp('Since load line has a slope of -100V/A, the
       source resistance for the gate is 100 ohm')
6 Rs=100;
7 // since Vs=Vg+Ig*Rs
8 // on solving Ig=35.5 mA
9 Ig=35.5*10^-3;
10 printf("\nGate current=%f A",Ig)
11 Vg=P/Ig;
12 printf("\nGate voltage=%f V",Vg)
```

Scilab code Exa 1.16 Find the thermal resistance and temperature

```
1 //1.16
2 clc;
3 l=0.2;
4 w=0.01;
5 d=0.01;
6 the_cond=220;
7 the_res=l/(the_cond*w*d);
8 printf("Thermal resistance = %.3f degree C/W",
       the_res)
9 T1=30;
10 P=3;
11 T2=P*the_res+T1;
12 printf("\nTemperature of the surface = %.2f degree C
       ", T2)
```

Scilab code Exa 1.17 Find the maximum loss

```
1 //1.17
2 clc;
3 l=2*10^-3;
4 A=12*10^-4;
5 the_cond=220;
6 the_res=l/(the_cond*A);
7 T=4; //T=T2-T1
8 P=T/the_res;
9 printf("Maximum loss which can be handled by module=
%.2f W", P)
```

Scilab code Exa 1.18 Find the maximum loss

```
1 //1.18
2 clc;
3 T2=125;
4 T1=50;
5 T=T2-T1;
6 P=30;
7 Total_the_res=T/P;
8 the_res=Total_the_res-1-0.3;
9 printf("Thermal resistance of heat sink= %.1f degree
C/W", the_res)
```

Scilab code Exa 1.19 Design a UJT relaxation oscillator

```
1 //1.19
```

```

2 clc;
3 T=1/50;
4 V=32;
5 Vp=0.63*V+0.5;
6 C=0.4*10^-6;
7 Ip=10*10^-6;
8 Rmax=(V-Vp)/Ip;
9 printf("Rmax=%f ohm", Rmax)
10 Vv=3.5;
11 Iv=10*10^-3;
12 Rmin=(V-Vv)/Iv;
13 printf("\nRmin=%f ohm", Rmin)
14 R=T/(C*log(1/(1-0.63)));
15 printf("\nR=%f ohm", R)
16 disp('since the value of R is between Rmin and Rmax
so the value is suitable')
17 R4=50*10^-6/C;
18 printf("\nR4=%f ohm", R4)
19 R3=10^4/(0.63*V);
20 printf("\nR3=%f ohm", R3)

```

Scilab code Exa 1.20 Find the values of different components of circuit

```

1 // 1.20
2 clc;
3 T=.5*10^-3;
4 V=10;
5 Vp=0.6*V+0.5;
6 Ip=5*10^-3;
7 Rmax=(V-Vp)/Ip;
8 printf("Rmax=%f ohm", Rmax)
9 C=1*10^-6;
10 R=T/(C*log(1/(1-0.6)));
11 printf("\nR=%f ohm", R)
12 disp('since the value of R is less than Rmax so the

```

```
    value is suitable ')
```

Scilab code Exa 1.21 Find the time of conduction of thyristor

```
1 // 1.21
2 clc;
3 R=0.8;
4 L=10*10^-6;
5 C=50*10^-6;
6 t0=10^6*pi/((1/(L*C))-(R^2/(4*L^2)))^0.5;
7 printf("Time of conduction of thyristor= %.2f us" ,
t0)
```

Scilab code Exa 1.22 Find the values of L and C

```
1 // 1.22
2 clc;
3 Ip=16;
4 V=90;
5 // C/L=(Ip/V)^2;           ( i )
6 // Assume that circuit is reverse biased for one-
   fourth period of resonant circuit. thus
7 // %pi/2*(L*C)^0.5=40*10^-6;          ( ii )
8 // on solving (i) and (ii)
9 C=4.527*10^-6;
10 L=C/(Ip/V)^2*10^6;
11 C=4.527*10^-6*10^6;
12 printf("C=% .3 f uF" ,C)
13 printf("\nL=% .2 f uH" ,L)
```

Scilab code Exa 1.23 Find the value of C

```
1 // 1.23
2 clc;
3 t_off=50*10^-6;
4 R1=10;
5 a=log(2);
6 C=t_off/(a*R1)*10^6;
7 printf("The value of C= %.2f uF",C)
```

Scilab code Exa 1.24 Calculate the value of C and L

```
1 // 1.24
2 clc;
3 Vc=100;
4 IL=40;
5 t_off=40*10^-6*1.5;
6 C=IL*t_off/Vc;
7 printf("The value of capacitor= %.6f F",C)
8 //L>(VC^2*C/IL^2);
9 //IC_peak=Vc*(C/L)^0.5;
10 //IC_peak should be less than maximum load current
    so if L=2*10^-4
11 L=2*10^-4;
12 IC_peak=Vc*(C/L)^0.5;
13 printf("\nPeak capacitor current= %.2f A",IC_peak)
14 disp('Since the peak capacitor current less than
        maximum load current 40 A so L=2*10^-4 and C=24
        uF')
```

Scilab code Exa 1.25 Find the commutation time and the current rating of the thyri

```
1 // 1.25
```

```

2 clc;
3 L=0.1*10^-3;
4 Vc=100;
5 C=10*10^-6;
6 IL=10;
7 t_off=Vc*C/IL*10^6;
8 printf("Commutation time= %.0f us",t_off)
9 disp('The commutation time of the thyristor is more
       than the turn off time of the main thyristor i.e
       . 25us and is thus sufficient to commutate the
       main thyristor')
10 IC_peak= Vc*(C/L)^0.5;
11 printf("Peak capacitor current= %.2f A",IC_peak)
12 disp('The maximum current rating of the thyristor
       should be more than 31.62A')

```

Scilab code Exa 1.26 Find the value of R and C

```

1 //1.26
2 clc;
3Vm=230*2^0.5;
4 L=0.2*10^-3;
5 //a=dv/dt
6 a=25*10^6;
7 sig=0.65;
8 C=(1/(2*L))*(0.564*Vm/a)^2*10^9;
9 R=2*sig*(L/(C*10^-9))^0.5;
10 printf("The value of capacitor= %.2f nF",C)
11 printf("\nThe value of Resistor= %.1f Ohm",R)

```

Scilab code Exa 1.27 Find the value of R C and snubber power loss and power rating

```

1 //1.27

```

```

2 clc;
3 f=2000;
4 V=300;
5 RL=10;
6 // a=dv/dt
7 a=100*10^6;
8 R=300/100;
9 C=(0.632*V*RL)/(a*(R+RL)^2)*10^6;
10 printf("The value of capacitor= %.3f uF",C)
11 Power_Loss_snubber=0.5*C*10^-6*V^2*f;
12 printf("\nSnubber Power Loss= %.2f W",
    Power_Loss_snubber)
13 disp('All the energy stored in the capacitance C is
dissipated in resistance R. Hence power Rating of
R is 10.1W')

```

Scilab code Exa 1.28 Find the maximum permissible values

```

1 //1.28
2 clc;
3 C=6*10^-6;
4 R=4;
5 V=300;
6 L=6*10^-6;
7 b_max=V/L*10^-6; // b=di/dt
8 printf("The maximum permissible value of di/dt = %.0
    f MA/s",b_max)
9 Isc=V/R;
10 //a=dv/dt
11 a=((R*b_max*10^6)+(Isc/C))*10^-6;
12 printf("\nThe maximum permissible value of dv/dt = %
    .1f MV/s",a)

```

Scilab code Exa 1.29 Find number of thyristor in series and parallel

```
1 // 1.29
2 clc;
3 Im=750;
4 De=0.25;
5 It=175;
6 np=(Im/It)/(1-De);
7 printf("np = %.2f ",np)
8 disp('so the no. of thyristors in parallel are 6')
9 Vs=3000;
10 De=0.25;
11 Vd=800;
12 ns=(Vs/Vd)/(1-De);
13 printf("ns = %.2f ",ns)
14 disp('so the no. of thyristors in series are 5')
```

Scilab code Exa 1.30 Find the value of R and C for static and dynamic equalizing

```
1 // 1.30
2 clc;
3 ns=5;
4 Vd=800;
5 Vs=3000;
6 Ib=8*10^-3;
7 dQ=30*10^-6;
8 R=(ns*Vd-Vs)/((ns-1)*Ib)
9 C=((ns-1)*dQ)/(ns*Vd-Vs)*10^6;
10 printf("The value of resistance = %.2f ohm ",R)
11 printf("\nThe value of capacitance = %.2f uF ",C)
```

Scilab code Exa 1.31 Find the value of resistance to be connected in series

```
1 // 1.31
2 clc;
3 R=(1.5-1.2)/100;
4 printf(" The value of resistance to be connected in
series= %.3f ohm",R)
```

Scilab code Exa 1.32 Find the steady and transient state rating and derating of the

```
1 // 1.32
2 clc;
3 ns=12;
4 Vd=800;
5 V=16000;
6 Ib=10*10^-3;
7 dQ=150*10^-6;
8 C=0.5*10^-6;
9 R=56*10^3;
10 Vd=(V+(ns-1)*R*Ib)/ns;
11 printf("maximum steady state voltage rating of each
thyristor = %.2f V",Vd)
12 De=1-(V/(ns*Vd));
13 printf("\nSteady state voltage derating = %.3f ",De)
14 Vd=(V+(ns-1)*(dQ/C))/ns;
15 printf("\nmaximum transient state voltage rating of
each thyristor = %.2f V",Vd)
16 De=1-(V/(ns*Vd));
17 printf("\ntransient state voltage derating = %.3f ",
De)
```

Scilab code Exa 1.33 Find number of thyristor in series and parallel

```
1 // 1.33
2 clc;
```

```
3 Im=1000;
4 De=0.14;
5 It=75;
6 np=(Im/It)/(1-De);
7 printf("np = %.2f ",np)
8 disp('so the no. of thyristors in parallel are 16')
9 Vs=7500;
10 De=0.14;
11 Vd=500;
12 ns=(Vs/Vd)/(1-De);
13 printf("ns = %.2f ",ns)
14 disp('so the no. of thyristors in series are 18')
```

Scilab code Exa 1.34 Find Stored charge and peak reverse current

```
1 //1.34
2 clc;
3 trr=2.5*10^-6;
4 //b=di/dt
5 b=35*10^6;
6 Qrr=0.5*trr^2*b*10^6;
7 printf(" Stored charge= %.3f uC",Qrr)
8 Irr=(2*Qrr*10^-6*b)^0.5;
9 printf(" Peak reverse current= %.1f A",Irr)
```

Chapter 2

Controlled Rectifiers

Scilab code Exa 2.3 Calculate the different parameters of half wave diode rectifier

```
1 // 2.3
2 clc;
3 Vp_sec=230*2^0.5/4;
4 alph=asind(12/Vp_sec);
5 alph1=180-alph;
6 //the diode will conduct from 8.89 degree to 171.51
degree
7 Angle_conduction=alph1-alph;
8 printf("Conduction Angle = %.2 f degree" ,
Angle_conduction)
9 Idc=4;
10 R=1/(2*Idc*%pi)*(2*Vp_sec*cosd(alph)+(2*12*alph*%pi
/180)-12*%pi);
11 printf("\nResistance = %.2 f ohm" , R)
12 Irms=((1/(2*%pi*R^2))*(((Vp_sec^2/2+12^2)*(%pi-2*
alph*%pi/180))+(Vp_sec^2/2*sind(2*alph))-(4*
Vp_sec*12*cosd(alph)))^0.5;
13 P_rating=Irms^2*R;
14 printf("\nPower rating of resistor = %.2 f W" ,
P_rating)
15 Pdc=12*Idc;
```

```

16 t_charging=150/Pdc;
17 printf("\nCharging time = %.3f h", t_charging)
18 Rectifier_efficiency= Pdc/(Pdc+Irms^2*R);
19 printf("\nRectifier efficiency = %.2f %",
        Rectifier_efficiency)
20 PIV=Vp_sec+12;
21 printf("\nPIV = %.3f V", PIV)

```

Scilab code Exa 2.4 Calculate the different parameters of full wave centre tapped

```

1 // 2.4
2 clc;
3 Vm=100;
4 R=5;
5 Idc=2*Vm/(%pi*R);
6 printf("\nIdc = %.3f A", Idc)
7 Vdc=Idc*R;
8 printf("\nVdc = %.3f V", Vdc)
9 Irms=0.707*Vm/R;
10 printf("\nIrms = %.3f A", Irms)
11 Vrms=Irms*R;
12 printf("\nVrms = %.3f V", Vrms)
13 Pdc=Idc^2*R;
14 printf("\nPdc = %.3f W", Pdc)
15 Pac=Irms^2*R;
16 printf("\nPac = %.3f W", Pac)
17 FF=Vrms/Vdc;
18 printf("\nFF = %.3f ", FF)
19 RF=(FF^2-1)^0.5;
20 printf("\nRF = %.3f ", RF)
21 TUF=0.5732;
22 printf("\nTUF = %.3f ", TUF)
23 PIV=2*Vm;
24 printf("\nPIV = %.0f V", PIV)
25 CF=0.707;

```

```
26 printf("\nCF = %.3f ", CF)
```

Scilab code Exa 2.5 Find the RMS and average voltage and current

```
1 // 2.5
2 clc;
3 Vm=400;
4 alpha=30;
5 R=50;
6 Vdc=(Vm/(2*pi))*(1+cosd(alpha));
7 printf("Average Load voltage = %.1f V", Vdc)
8 Load_current_average=Vdc/R;
9 printf("\nAverage Load current = %.3f A",
       Load_current_average)
10 V=400*((%pi-(%pi/6))/(4*pi)+(sind(60)/(8*pi)))
    ^0.5;
11 printf("\nRMS voltage = %.1f V", V)
12 RMS_current=V/R;
13 printf("\nRMS current = %.3f A", RMS_current)
```

Scilab code Exa 2.6 Find the average current

```
1 // 2.6
2 clc;
3 current_average=(1/(2*pi))*(-10*cos(5*pi/6)+10*cos
    (%pi/6)-(5*5*pi/6)+(5*pi/6));
4 printf("\nAverage current = %.3f A",
       current_average)
```

Scilab code Exa 2.7 Find the average current

```

1 // 2.7
2 clc;
3 // the thyristor will conduct when instantaneous
   value of source emf is more than the back emf i.e
   . 2^0.5*100 sin wt=55.5
4 wt1=asind(55.5/(2^0.5*110));
5 wt2=180-wt1;
6 current_average=(1/(2*%pi))*(-15.554*(cosd(wt2)-cosd
   (wt1))-5.55*(2.7768-0.3684));
7 printf("\nAverage current = %.2f A",
   current_average)

```

Scilab code Exa 2.8 Calculate the various parameters of a single phase half wave rectifier

```

1 // 2.8
2 clc;
3 Vm=230*2^0.5;
4 Vdc=(Vm/(2*%pi))*(1+cosd(90));
5 Idc=Vdc/15;
6 Vrms=Vm*(((%pi-(%pi/2))/(4*%pi))+(%sin(2*%pi)/(8*%pi))
   ))^0.5;
7 Irms=Vrms/15;
8 Pdc=Vdc*Idc;
9 Pac=Vrms*Irms;
10 Rec_effi=Pdc/Pac;
11 Form_factor=Vrms/Vdc;
12 printf("\n Form Factor = %.1f ", Form_factor)
13 ripple_factor=(Form_factor^2-1)^0.5;
14 printf("\n Ripple Factor = %.1f ", ripple_factor)
15 VA_rating=230*7.66;
16 printf("\n VA rating = %.1f VA", VA_rating)
17 TUF=Pdc/VA_rating;
18 printf("\n TUF = %.3f ", Form_factor)
19 PIV=Vm;
20 printf("\n PIV = %.1f V", PIV)

```

Scilab code Exa 2.9 Find the RMS and average voltage and current of a single phase

```
1 // 2.9
2 clc;
3 Vm=150*2^0.5;
4 Vdc=(Vm/(%pi))*(1+cosd(45));
5 R=30;
6 Load_current_average=Vdc/R;
7 printf("\nAverage Load current = %.2f A",
       Load_current_average)
8 Vrms=Vm*(((%pi-(%pi/4))/(2*%pi)+(sind(90)/(4*%pi)))
            ^0.5;
9 printf("\nRMS voltage = %.1f V", Vrms)
10 RMS_current=Vrms/R;
11 printf("\nRMS current = %.3f A", RMS_current)
```

Scilab code Exa 2.10 Calculate the different parameters of full wave converter with

```
1 // 2.10
2 clc;
3 Vdc=100;
4 Vm=(Vdc+1.7)*%pi/(2*cosd(30));
5 Vrms_sec=Vm/2^0.5;
6 Vrms_pri=230;
7 Turn_ratio=Vrms_pri/Vrms_sec;
8 printf("\nTurn Ratio = %.2f ", Turn_ratio)
9 Ip=15;
10 Irms_sec=(Ip^2/2)^0.5;
11 Trans_rating=2*Vrms_sec*Irms_sec;
12 printf("\nTransformer rating = %.2f VA",
        Trans_rating)
```

```

13 PIV=2*Vm;
14 printf("\nPIV = %.2f V", PIV)
15 printf("\nRMS value of thyristor current = %.2f A",
    Irms_sec)

```

Scilab code Exa 2.11 Calculate the voltage rating of full wave central tap and bridge rectifier

```

1 // 2.11
2 clc;
3 Idc=50;
4 Vdc=10*1000/Idc;
5 Vm=200*pi/2;
6 PIV_central_tap=2*Vm;
7 V_rating_central_tap =2*PIV_central_tap;
8 printf("The rated voltage of full wave central tap
        transformer rectifier = %.2f V",
        V_rating_central_tap )
9 PIV_bridge=Vm;
10 V_rating_bridge=2*PIV_bridge;
11 printf("\nThe rated voltage of full wave bridge
        rectifier = %.2f V", V_rating_bridge )

```

Scilab code Exa 2.12 Find the output voltage firing angle and load current

```

1 // 2.12
2 clc;
3 Vm=230*2^0.5;
4 Vrms=(800/1000*230^2)^0.5;
5 printf("Output Voltage = %.2f V", Vrms )
6 //Vrms=Vm*((pi-alpha)/(2*pi)+sin(2*alpha)/(4*pi))
    ^0.5 on solving
7 alph=61;
8 printf("\nFiring angle = %.0f degree", alph )

```

```
9 I=800/Vrms;
10 printf("\nLoad current = %.2f A", I)
```

Scilab code Exa 2.13 Find the average power output of full wave mid point and bridge converter

```
1 //2.13
2 clc;
3 disp('For Mid point converter')
4 Vm=800/(2*2.5);
5 alph=0;
6 Vo=Vm/(%pi)*(1+cosd(alph));
7 Idc=30/2.5;
8 Pdc=Idc*Vo;
9 printf("Average output power = %.2f W", Pdc )
10 disp('For bridge converter')
11 Vm=800/(2.5);
12 alph=0;
13 Vo=Vm/(%pi)*(1+cosd(alph));
14 Idc=30/2.5;
15 Pdc=Idc*Vo;
16 printf("Average output power = %.2f W", Pdc )
```

Scilab code Exa 2.14 Find dc output voltage and power

```
1 //2.14
2 clc;
3 Vm=230*2^0.5;
4 alph=30;
5 Vo=Vm/(2*%pi)*(3+cosd(alph));
6 Idc=Vo/10;
7 printf("dc output voltage = %.1f V", Vo )
8 Pdc=Idc*Vo;
9 printf("\ndc power = %.2f W", Pdc )
```

Scilab code Exa 2.15 Find dc output voltage and power

```
1 // 2.15
2 clc;
3 Vm=230*2^0.5;
4 Vo=2*Vm/%pi;
5 Idc=Vo/10;
6 printf("dc output voltage = %.2f V" , Vo )
7 Pdc=Idc*Vo;
8 printf("\n dc power = %.2f W" , Pdc )
```

Scilab code Exa 2.16 Calculate the firing angle and power factor

```
1 //
2 clc;
3 disp('If E=100 V')
4 Vm=230*2^0.5;
5 E=100;
6 R=0.5;
7 Io=15;
8 alph=acosd((E+15*0.5)*%pi/(2*Vm));
9 printf("Firing Angle = %.2f degree" , alph)
10 pf=(100*15+15^2*0.5)/(230*15);
11 printf("\nPower factor = %.3f lagging" , pf)
12 disp('If E=-100 V')
13 E=-100;
14 alph=acosd((E+15*0.5)*%pi/(2*Vm));
15 printf("\nFiring Angle when E is -100 = %.2f W" ,
alph)
16 pf=(100*15-15^2*0.5)/(230*15);
17 printf("\nPower factor = %.3f lagging" , pf)
```

Scilab code Exa 2.17 Find the average value of load current

```
1 //2.17
2 clc;
3 Vm=230*2^0.5;
4 alph=40;
5 Io=((2*Vm/%pi*cosd(alph))-50)/5;
6 printf("Average value of load current = %.2f A", Io)
```

Scilab code Exa 2.18 Calculate the different parameters of full wave converter with

```
1 //2.18
2 clc;
3 Vdc=100;
4 Vm=(Vdc+2*1.7)*%pi/(2*cosd(30));
5 Vrms_sec=Vm/2^0.5;
6 Vrms_pri=230;
7 Turn_ratio=Vrms_pri/Vrms_sec;
8 printf("\nTurn Ratio = %.2f ", Turn_ratio)
9 Irms_sec=15/2^0.5;
10 Ip=15;
11 Trans_rating=Vrms_sec*Ip;
12 printf("\nTransformer rating = %.2f VA",
       Trans_rating)
13 PIV=Vm;
14 printf("\nPIV = %.2f V", PIV)
15 printf("\nRMS value of thyristor current = %.2f A",
       Irms_sec)
```

Scilab code Exa 2.19 Find the value of dc voltage rms voltage and form factor of a

```
1 // 2.19
2 clc;
3 Vm=230*2^0.5;
4 Vdc=Vm/%pi*(1+cosd(90));
5 printf("dc value of voltage = %.2f V", Vdc)
6 Vrms=230*((1/%pi)*(%pi-(%pi/2)+sin(%pi)/2))^0.5;
7 printf("\n RMS value of voltage= %.2f V", Vrms)
8 form_factor=Vrms/Vdc;
9 printf("\nForm factor = %.2f ", form_factor)
```

Scilab code Exa 2.20 Calculate the different parameters of single phase semi conver

```
1 // 2.20
2 clc;
3 Vm=230*2^0.5;
4 Vdc=Vm/%pi*(1+cosd(90));
5 printf("dc value of voltage = %.2f V", Vdc)
6 Vrms=230*((1/%pi)*(%pi-(%pi/2)+sin(%pi)/2))^0.5;
7 printf("\n RMS value of voltage= %.2f V", Vrms)
8 Is=(1-(%pi/2)/%pi)^0.5;
9 Is1=2/%pi*2^0.5*cos(%pi/4);
10 HF=((Is/Is1)^2-1)^0.5;
11 printf("\n Harmonic factor= %.3f ", HF)
12 Displacement_factor=cos(-%pi/4);
13 printf("\n Displacement factor= %.4f ", 
Displacement_factor)
14 Power_factor=Is1/Is*cos(-%pi/4);
15 printf("\n Power factor= %.4f lagging", Power_factor
)
```

Scilab code Exa 2.21 Calculate the different parameters of single phase full conver

```

1 // 2.21
2 clc;
3 Vm=230*2^0.5;
4 Vdc=2*Vm/%pi*cosd(60);
5 printf("dc value of voltage = %.2f V" , Vdc)
6 Vrms=230;
7 printf("\n RMS value of voltage= %.2f V" , Vrms)
8 Is1=2*2^0.5/%pi;
9 Is=1;
10 HF=((Is/Is1)^2-1)^0.5;
11 printf("\n Harmonic factor= %.3f " , HF)
12 Displacement_factor=cos(-%pi/3);
13 printf("\n Displacement factor= %.1f " ,
Displacement_factor)
14 Power_factor=Is1/Is*cos(-%pi/3);
15 printf("\n Power factor= %.2f lagging" , Power_factor
)

```

Scilab code Exa 2.22 Calculate the different parameters of single phase full contr

```

1 // 2.22
2 clc;
3 Vm=230*2^0.5;
4 Vdc=2*Vm/%pi*cosd(30);
5 R=Vdc/4;
6 printf("dc value of voltage = %.1f V" , Vdc)
7 IL=4;
8 I=2*2^0.5/%pi*IL;
9 P_input_active=230*I*cosd(30);
10 printf("\n Active input power= %.2f W" ,
P_input_active)
11 P_input_reactive=230*I*sind(30);
12 printf("\n reactive input power= %.2f Vars" ,
P_input_reactive)
13 P_input_appearent=230*I;

```

```

14 printf("\n Active input power= %.2f VA" ,
P_input_appearent)
15
16 disp('When freewheeling diode is present')
17 Vm=230*2^0.5;
18 Vdc=Vm/%pi*(1+cosd(30));
19 printf("dc value of voltage = %.1f V" , Vdc)
20 IL=Vdc/R;
21 I=2*2^0.5/%pi*IL*cosd(15);
22 P_input_active=230*I*cosd(15);
23 printf("\n Active input power= %.2f W" ,
P_input_active)
24 P_input_reactive=230*I*sind(15);
25 printf("\n reactive input power= %.2f Vars" ,
P_input_reactive)
26 P_input_appearent=230*I;
27 printf("\n Active input power= %.2f VA" ,
P_input_appearent)
28 disp('When Th3 get open circuit')
29 Vdc=230/(2^0.5*%pi)*(1+cosd(30));
30 printf("dc value of voltage = %.3f V" , Vdc)
31 Idc=Vdc/R;
32 printf("\n Average dc output current = %.2f A" , Idc)

```

Scilab code Exa 2.23 Calculate the different parameters of single phase full contr

```

1 //2.23
2 clc;
3 Vm=230*2^0.5;
4 Vdc=2*Vm/%pi*cosd(30);
5 printf("dc value of voltage = %.1f V" , Vdc)
6 Irms=10;
7 I=10;
8 printf("\n RMS value of current= %.0f A" , Irms)
9 Is1=2*2^0.5/%pi*I;

```

```

10 printf("\n Fundamental component of input current= %.
.0 f A", Is1)
11 Is=10;
12 HF=((Is/Is1)^2-1)^0.5;
13 printf("\n Harmonic factor= %.3f ", HF)
14 Displacement_factor=cosd(-30);
15 printf("\n Displacement factor= %.3f ",
Displacement_factor)
16 Power_factor=Is1/Is*cos(-%pi/6);
17 printf("\n Power factor= %.3f lagging", Power_factor
)
18 Out_rms=230;
19 Form_factor=Out_rms/Vdc;
20 Ripple_factor=(Form_factor^2-1)^0.5;
21 printf("\n Ripple factor= %.3f ", Ripple_factor)

```

Scilab code Exa 2.24 Calculate peak circulating current and peak current of converter

```

1 //2.24
2 clc;
3 Vm=230*2^0.5;
4 alph1=60;
5 alph2=120;
6 w=100*%pi;
7 L=50*10^-3;
8 wt=2*%pi;
9 R=15;
10 Ip_circulating=2*Vm/(w*L)*(cos(wt)-cosd(alph1));
11 printf("\n Peak circulating current= %.1f A",
Ip_circulating)
12 Ip_load=Vm/R;
13 Ip_converter1=Ip_circulating+Ip_load;
14 printf("\n Peak current of converter 1= %.2f A",
Ip_converter1)

```

Scilab code Exa 2.25 Calculate inductance of current limiting reactor and peak cur

```
1 // 2.25
2 clc;
3 Vm=230*2^0.5;
4 alph1=30;
5 alph2=150;
6 w=100*%pi;
7 wt=2*%pi;
8 R=10;
9 Ip_circulating=10.2;
10 L=2*Vm/(w*Ip_circulating)*(cos(wt)-cosd(alph1));
11 printf("\n Inductance of current limiting Reactor= %.
        .4 f H",L)
12 Ip_load=Vm/R;
13 Ip_converter1=Ip_circulating+Ip_load;
14 printf("\n Peak current of converter 1= %.2 f A",
        Ip_converter1)
```

Scilab code Exa 2.26 Calculate inductance of current limiting reactor and resistance of load

```
1 // 2.26
2 clc;
3 Vm=230*2^0.5;
4 alph1=45;
5 alph2=135;
6 w=100*%pi;
7 wt=2*%pi;
8 R=10;
9 Ip_circulating=11.5;
10 L=2*Vm/(w*Ip_circulating)*(cos(wt)-cosd(alph1));
```

```

11 printf("\n Inductance of current limiting Reactor= %
.4 f H" ,L)
12 Ip_converter1=39.7;
13 Ip_load= Ip_converter1-Ip_circulating ;
14 R=Vm/Ip_load;
15 printf("\n Load resistance= %.3f ohm" , R)

```

Scilab code Exa 2.27 Find the parameters of three phase bridge rectifier circuit

```

1 //2.27
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 Vdc=360;
5 alph=acosd(Vdc*%pi/(3*3^0.5*Vm));
6 printf("Firing Angle = %.1f degree" , alph)
7 VL=400;
8 IL=200;
9 S=3^0.5*VL*IL;
10 printf("\nApparent Power = %.0f VA" ,S)
11 P=S*cosd(alph);
12 printf("\nActive Power = %.1f W" ,P)
13 Q=(S^2-P^2)^0.5;
14 printf("\nReactive Power = %.1f VA" ,Q)
15 disp('When AC line voltage is 440V')
16 V=440;
17 alph=acosd(Vdc*%pi/(3*2^0.5*V));
18 printf("Firing Angle = %.1f degree" , alph)
19 disp('When AC line voltage is 360V')
20 V=360;
21 alph=acosd(Vdc*%pi/(3*2^0.5*V));
22 printf("Firing Angle = %.1f degree" , alph)

```

Scilab code Exa 2.28 Find the parameters of three phase full converter

```

1 //2,28
2 clc;
3 Vm=2^0.5*400/3^0.5;
4 Vdc=3*3^0.5*Vm/%pi*cos(%pi/3);
5 Idc=150;
6 Pdc=Vdc*Idc;
7 printf("Output Power = %.1f W", Pdc)
8 Iavg_thy=Idc/3;
9 printf("\nAverage thyristor current = %.0f A",
     Iavg_thy)
10 Irms_thy=Idc*(2/6)^0.5;
11 printf("\nRMS value of thyristor current = %.1f A",
     Irms_thy)
12 Ip_thy=Idc;
13 printf("\nPeak current through thyristor = %.0f A",
     Ip_thy)
14 PIV=2^0.5*400;
15 printf("\nPeak inverse voltage = %.1f V", PIV)

```

Scilab code Exa 2.29 Find the firing angle of a 3 phase fully controlled bridge converter

```

1 //2.29
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 Vrms=(400*100)^0.5;
5 alph=acosd(((Vrms/(Vm*3^0.5))^2-0.5)/(3*3^0.5/(4*pi
    )))/2;
6 printf("Firing angle = %.2f degree", alph)

```

Scilab code Exa 2.30 Find the parameters of six pulse thyristor converter

```

1 //2.30
2 clc;

```

```

3 Vm=415*2^0.5/3^0.5;
4 Vdc=460;
5 Idc=200;
6 alph=acosd(Vdc*pi/(3*3^0.5*Vm));
7 printf(" Firing Angle = %.2f degree", alph)
8 Pdc=Vdc*Idc;
9 printf("\n dc Power = %.2f W", Pdc)
10 Iac=Idc*(120/180)^0.5;
11 printf("\n AC line current = %.2f A", Iac)
12 Ip=Idc;
13 Irms_thy=Ip*(120/360)^0.5;
14 printf("\n RMS thyristor current = %.1f A", Irms_thy
)

```

Scilab code Exa 2.31 Find the parameters of three phase semi converter bridge circ

```

1 // 2.31
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 alph=0;
5 Vdc_max=3*3^0.5*Vm/(2*pi)*(1+cosd(alph));
6 Vdc=0.5*Vdc_max;
7 alph=acosd((Vdc/(3*3^0.5*Vm/(2*pi)))-1)
8 printf(" Firing Angle = %.2f degree", alph)
9 R=10;
10 Idc=Vdc/R;
11 disp('For discontinuous load')
12 Vrms=(3^0.5*Vm)*((3/(4*pi))*(pi-(pi/2)+0.5*sin(
    %pi)))^0.5;
13 printf("\n RMS value of voltage = %.2f V", Vrms)
14 Irms=Vrms/R;
15 printf("\n RMS value of current = %.2f A", Irms)
16 I_avg=Idc/3;
17 printf("\n Average value of thyristor current = %.2f
    A", I_avg)

```

```

18 I_rms=Irms/3^0.5;
19 printf("\nRMS value of thyristor current = %.2f A" ,
    I_rms)
20 efficiency=Vdc*Idc/(Vrms*Irms);
21 printf("\nRectification efficiency = %.3f A" ,
    efficiency)
22 Irms_line_current=Irms*(120/180)^0.5;
23 VA_input=3*400/3^0.5*Irms_line_current;
24 TUF=Vdc*Idc/VA_input;
25 printf("\nTransformer utilization factor = %.2f " ,
    TUF)
26 output_power_active=Irms^2*R;
27 input_power_active=output_power_active;
28 pf_input=input_power_active/VA_input;
29 printf("\ninput power factor = %.2f lagging" ,
    pf_input)

```

Scilab code Exa 2.32 Find the parameters of three phase fully controlled bridge co

```

1 //2.31
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 alph=0;
5 Vdc_max=3*3^0.5*Vm/(%pi)*cosd(alph);
6 Vdc=0.5*Vdc_max;
7 alph=acosd(0.5);
8 printf("Firing Angle = %.2f degree" , alph)
9 R=10;
10 Idc=Vdc/R;
11 disp('For discontinuous load')
12 Vrms=(3^0.5*Vm)*(3*3^0.5/(4*%pi)*cosd(2*alph)+0.5)
    ^0.5;
13 printf("\nRMS value of voltage = %.2f V" , Vrms)
14 Irms=Vrms/R;
15 printf("\nRMS value of current = %.2f A" , Irms)

```

```

16 I_avg=Idc/3;
17 printf("\nAverage value of thyristor current = %.2f
      A", I_avg)
18 Irms=Irms/3^0.5;
19 printf("\nRMS value of thyristor current = %.2f A",
      Irms)
20 efficiency=Vdc*Idc/(Vrms*Irms);
21 printf("\nRectification efficiency = %.3f A",
      efficiency)
22 Irms_line_current=Irms*(120/180)^0.5;
23 VA_input=3*400/3^0.5*Irms_line_current;
24 TUF=Vdc*Idc/VA_input;
25 printf("\nTransformer utilization factor = %.2f ",
      TUF)
26 output_power_active=Irms^2*R;
27 input_power_active=output_power_active;
28 pf_input=input_power_active/VA_input;
29 printf("\ninput power factor = %.2f lagging",
      pf_input)

```

Scilab code Exa 2.33 Calculate the overlap angles

```

1 //2.33
2 clc;
3 Vm=326.56;
4 f=50;
5 Ls=0.2*10^-3;
6 Io=200;
7 w=2*pi*f;
8 a=3*w*Ls*Io/pi;
9 b=3*3^0.5*Vm/pi;
10 disp('For firing angle 20 degree')
11 alph=20;
12 Angle_overlap=acosd((b*cosd(alph)-a)/b)-alph;
13 printf("Overlap angle= %.1f degree", Angle_overlap)

```

```

14 disp('For firing angle 30 degree')
15 alph=30;
16 Angle_overlap= acosd((b*cosd(alph)-a)/b)-alph;
17 printf("Overlap angle= %.2f degree", Angle_overlap)
18 disp('For firing angle 60 degree')
19 alph=60;
20 Angle_overlap= acosd((b*cosd(alph)-a)/b)-alph;
21 printf("Overlap angle= %.4f degree", Angle_overlap)

```

Scilab code Exa 2.34 Find the value of circulating currents for 3 phase dual conv

```

1 //2.34
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 f=50;
5 w=2*pi*f;
6 L=60*10^-3;
7 alph=0;
8 disp('Circulating current at wt=0')
9 wt=0;
10 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
11 printf("Circulating current at wt 0 is= %.3f A", ir)
12 disp('Circulating current at wt=30')
13 wt=30;
14 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
15 printf("Circulating current at wt 30 is= %.3f A", ir
    )
16 disp('Circulating current at wt=90')
17 wt=90;
18 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
19 printf("Circulating current at wt 90 is= %.3f A", ir
    )
20 disp('Maximum Circulating current will occur at wt
    =120')
21 wt=120;

```

```
22 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
23 printf("Maximum Circulating current is= %.3f A", ir)
```

Scilab code Exa 2.35 Find the value of inductance

```
1 // 2.35
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 f=50;
5 w=2*pi*f;
6 ir=42;
7 L=3*Vm/(w*ir)*(sind(120-30)-sind(0))
8 printf("Inductance= %.3f H", L)
```

Chapter 3

Inverters

Scilab code Exa 3.1 Find the maximum output frequency

```
1 // 3.1
2 clc;
3 R=80;
4 L=8*10^-3;
5 C=1.2*10^-6;
6 a=R^2;
7 b=4*L/C;
8 printf("R^2 = %.0f ", a)
9 printf("4*L/C = %.0f ", b)
10 disp('since R^2<4L/C it will work as series inverter')
11 fmax=(1/(L*C)-(R^2/(4*L^2)))^0.5;
12 printf("Maximum frequency = %.2f rad/sec", fmax)
```

Scilab code Exa 3.2 Find the frequency of output

```
1 // 3.2
2 clc;
```

```

3 f=1416.16;
4 T=1/f;
5 Toff=14*10^-6;
6 fo=1/(T+2*Toff);
7 printf("output frequency = %.1f Hz", fo)

```

Scilab code Exa 3.3 Find the available circuit turn off time and maximum possible

```

1 // 3.3
2 clc;
3 R=4;
4 L=50*10^-6;
5 C=6*10^-6;
6 a=R^2;
7 b=4*L/C;
8 wr=(1/(L*C)-(R^2/(4*L^2)))^0.5;
9 fr=wr/(2*pi);
10 Tr=1/fr;
11 fo=6000;
12 wo=2*pi*fo;
13 toff=%pi*(1/wo-1/wr);
14 printf("Avialable circuit turn off time = %.8f sec", toff)
15 fmax=1/(2*(pi/wr+6*10^-6));
16 printf("\nMaximum frequency = %.1f Hz", fmax)

```

Scilab code Exa 3.4 Design a parallel inverter

```

1 // 3.4
2 clc;
3 tq=50*10^-6;
4 Vin=40;
5 Vo=230;

```

```

6 IL=2;
7 IL_ref=2*Vo/Vin;
8 // C/L=(IL-ref/Vin)^2; ( i )
9 // Assume that circuit is reverse biased for one-
   fourth period of resonant circuit. thus
10 // %pi/3*(L*C)^0.5=50*10^-6; ( ii )
11 // on solving ( i ) and ( ii )
12 C=13.73*10^-6;
13 L=C/(IL_ref/Vin)^2*10^6;
14 C=13.73*10^-6*10^6;
15 printf("C=%f uF",C)
16 printf("\nL=%f uH",L)

```

Scilab code Exa 3.5 Calculate the various parameters of single phase half bridge i

```

1 //3.5
2 clc;
3 V=30;
4 Vrms1=2*V/(2^0.5*%pi);
5 printf("RMS value of fundamental component of input
         voltage = %.1f V", Vrms1)
6 VL=V/2;
7 R=3;
8 Pout=VL^2/R;
9 printf("\nOutput Power = %.0f W", Pout)
10 Ip_thy=VL/R;
11 printf("\nPeak current in each thyristor = %.0f A",
        Ip_thy)
12 Iavg=Ip_thy/2;
13 printf("\naverage current in each thyristor = %.1f A
        ", Iavg)
14 PIV=2*VL;
15 printf("\nPeak reverse blocking voltahe = %.0f V",
        PIV)

```

Scilab code Exa 3.6 Calculate the various parameters of single phase full bridge inverter

```
1 // 3.6
2 clc;
3 V=30;
4 Vrms1=4*V/(2^0.5*pi);
5 printf("RMS value of fundamental component of input
         voltage = %.1f V", Vrms1)
6 VL=V;
7 R=3;
8 Pout=VL^2/R;
9 printf("\nOutput Power = %.0f W", Pout)
10 Ip_thy=VL/R;
11 printf("\nPeak current in each thyristor = %.0f A",
        Ip_thy)
12 Iavg=Ip_thy/2;
13 printf("\naverage current in each thyristor = %.1f A
        ", Iavg)
14 PIV=VL;
15 printf("\nPeak reverse blocking voltahe = %.0f V",
        PIV)
```

Scilab code Exa 3.7 Calculate the various parameters of full bridge inverter

```
1 // 3.7
2 clc;
3 R=10;
4 V=200;
5 IL_rms_funda=9.28/2^0.5;
6 printf("RMS value of fundamental component of load
         current=% .2f A", IL_rms_funda)
7 IL_peak=(9.28^2+6.55^2+1.89^2+0.895^2+0.525^2);
```

```

8 printf("\nPeak value of load current=%f A" ,
    IL_peak)
9 Irms_harmonic=(11.56^2-9.28^2)^0.5/2^0.5;
10 printf("\nRMS harmonic current=%f A" ,Irms_harmonic
    )
11 TMH=(11.56^2-9.28^2)^0.5/9.28;
12 printf("\nTotal harmonic distortion=%f" ,TMH)
13 IL_rms=11.56/2^0.5;
14 Po=IL_rms^2*R;
15 printf("\nTotal output power=%f W" ,Po)
16 Po_funda=IL_rms_funda^2*R;
17 printf("\nFundamental Component of power=%f W" ,
    Po_funda)
18 Iavg=Po/V;
19 printf("\nAverage input current=%f A" ,Iavg)
20 Ip_thy=11.56;
21 printf("\nPeak thyristor current=%f A" , Ip_thy)

```

Scilab code Exa 3.8 Calculate the value of C for proper load commutation

```

1 // 3.8
2 clc;
3 toff=12*1.5*10^-6;
4 f=4000;
5 wt=2*pi*f*töff;
6 Xl=10;
7 R=2;
8 Xc=R*tan(wt)+Xl;
9 C=1/(2*pi*f*Xc)*10^6;
10 printf("Value of C for proper load commutation = %.2
    f uF" , C)

```

Scilab code Exa 3.9 Calculate peak value of load current

```
1 // 3.9
2 clc;
3 I1=6.84;
4 I3=0.881;
5 I5=0.32;
6 I7=0.165;
7 Ip=(I1^2+I3^2+I5^2+I7^2)^0.5;
8 printf("Peak value of load current=%f A", Ip)
```

Scilab code Exa 3.10 Find the different parameters of 3 phase bridge inverter for

```
1 // 3.10
2 clc;
3 Ip_load=400/(2*10);
4 Irms_load=(Ip_load^2*2/3)^0.5;
5 printf("RMS value of the load current = %f A" ,
       Irms_load)
6 Po=Irms_load^2*10*3;
7 printf("\nOutput power = %f W", Po)
8 Iavg_thy=Ip_load/3;
9 printf("\nAverage thyristor current = %f A" ,
       Iavg_thy)
10 Irms_thy=(Ip_load^2/3)^0.5;
11 printf("\nRMS value thyristor current = %f A" ,
       Irms_thy)
```

Scilab code Exa 3.11 Find the different parameters of 3 phase bridge inverter for

```
1 // 3.11
2 clc;
3 R=10;
4 RL=R+R/2;
5 i1=400/15;
```

```

6 i2=i1;
7 i3=i1;
8 Irms_load=(1/(2*pi)*(i1^2*2*pi/3+(i1/2)^2*4*pi/3)
    )^0.5;
9 printf("RMS value of the load current = %.3f A",
    Irms_load)
10 Po=i1^2*R*3;
11 printf("\nOutput power = %.2f W", Po)
12 Iavg_thy=1/(2*pi)*(i1*pi/3+(i1/2*2*pi/3));
13 printf("\nAverage thyristor current = %.2f A",
    Iavg_thy)
14 Irms_thy= (1/(2*pi)*(i1^2*pi/3+(i1/2)^2*2*pi/3))
    ^0.5;
15 printf("\nRMS value thyristor current = %.2f A",
    Irms_thy)

```

Scilab code Exa 3.12 Find the RMS value of load current and thyristor current of 3

```

1 //3.12
2 clc;
3 R=10;
4 RL=R+R/2;
5 i1=450/15;
6 Irms_load=(1/(2*pi)*(i1^2*2*pi/3+(i1/2)^2*4*pi/3)
    )^0.5;
7 printf("RMS value of the load current = %.2f A",
    Irms_load)
8 Irms_thy= (1/(2*pi)*(i1^2*pi/3+(i1/2)^2*2*pi/3))
    ^0.5;
9 printf("\nRMS value thyristor current = %.0f A",
    Irms_thy)

```

Scilab code Exa 3.13 Find the parameters of single phase full bridge inverter

```
1 // 3.13
2 clc;
3 Vdc=200;
4 VL=Vdc*(5*30/180)^0.5;
5 printf("RMS value of the output voltage = %.2f V" ,
       VL)
6 Vdc=220;
7 delta=(VL/Vdc)^2*180/5;
8 printf("\nPulse width = %.2f degree" , delta)
9 V=VL/((5*33/180)^0.5);
10 printf("\nMaximum possible input voltage = %.2f V" ,
        V)
```

Scilab code Exa 3.14 Calculate the RMS value of the output voltage

```
1 // 3.14
2 clc;
3 Vdc=200;
4 delta=120;
5 VL=Vdc*(delta/180)^0.5;
6 printf("RMS value of the output voltage = %.1f V" ,
       VL)
```

Scilab code Exa 3.15 Calculate the RMS value of the output voltage

```
1 // 3.15
2 clc;
3 Vdc=150;
4 VL=Vdc*(20/180+60/180+20/180)^0.5;
5 printf("RMS value of the output voltage = %.2f V" ,
       VL)
```

Chapter 4

Choppers

Scilab code Exa 4.1 Calculate the period of conduction and blocking

```
1 // 4.1
2 clc;
3 f=1000;
4 T=1/f;
5 Vav=150;
6 V=230;
7 Ton=(Vav/V)*T;
8 printf("Period of conduction = %.6f sec", Ton)
9 Toff=T-Ton;
10 printf("\nPeriod of blocking = %.6f sec", Toff)
```

Scilab code Exa 4.2 Calculate the period of conduction and blocking

```
1 // 4.2
2 clc;
3 f=500;
4 T=1/f;
5 Vav=15*(0.06+0.03)+100;
```

```

6 V=200;
7 Ton=(Vav/V)*T;
8 printf("Period of conduction = %.7f sec", Ton)
9 Toff=T-Ton;
10 printf("\nPeriod of blocking = %.7f sec", Toff)

```

Scilab code Exa 4.3 Calculate the duty cycle for the rated torque and half of rate

```

1 // 4.3
2 clc;
3 Vs=240;
4 emf_800=Vs-20*0.5;
5 emf_600=230*600/800;
6 Vav=emf_600+20*0.5;
7 Duty_cycle=Vav/Vs;
8 printf("Duty cycle when motor develop the rated
        torque = %.4f ", Duty_cycle)
9 //when motor develop half of the rated torque
10 Vav=emf_600+10*0.5;
11 Duty_cycle=Vav/Vs;
12 printf("\nDuty cycle when motor develop half of the
        rated torque = %.4f ", Duty_cycle)

```

Scilab code Exa 4.4 Find the different parameters of a dc chopper

```

1 // 4.4
2 clc;
3 Duty_cycle=0.4;
4 Vs=200;
5 Vd=2;
6 Vav=Duty_cycle*(Vs-Vd);
7 printf("Average output voltage = %.1f V", Vav)
8 VL=Duty_cycle^0.5*(Vs-Vd);

```

```

9 printf("\nRMS output voltage = %.3f V" , VL)
10 R=8;
11 Po=VL^2/R;
12 Pi=Duty_cycle*Vs*(Vs-Vd)/R;
13 Chopper_efficiency=Po/Pi*100;
14 printf("\nChopper efficiency = %.0f percent" ,
    Chopper_efficiency)
15 Rin=R/Duty_cycle;
16 printf("\nInput resistance = %.0f Ohm" , Rin)
17 V1=126.05/2^0.5;
18 printf("\nRMS value of fundamental component = %.3f
    V" , V1)

```

Scilab code Exa 4.5 Find the chopper frequency

```

1 // 4.5
2 clc;
3 Duty_cycle=0.25;
4 V=400;
5 Vav=Duty_cycle*V;
6 Vn=V-Vav;
7 L=0.05;
8 di=10;
9 Ton=L*di/Vn;
10 T=Ton/Duty_cycle;
11 f=1/T;
12 printf("\nChopper frequency = %.0f Hz" , f)

```

Scilab code Exa 4.6 Find the different parameters of a chopper feeding a RL load

```

1 // 4.6
2 clc;
3 V=200;

```

```

4 R=4;
5 L=6*10^-3;
6 f=1000;
7 T=1/f;
8 Duty_cycle=0.5;
9 E=0;
10 Imax=V/R*((1-exp(-Duty_cycle*T*R/L))/(1-exp(-T*R/L))-
    )-E/R;
11 printf("\nImax = %.2f A", Imax)
12 Imin=V/R*((exp(Duty_cycle*T*R/L)-1)/(exp(T*R/L)-1))-E/R;
13 printf("\nImin = %.2f A", Imin)
14 Maximum_ripple=V/(R*f*L);
15 printf("\nMaximum ripple = %.2f A", Maximum_ripple)
16 IL_avg=(Imax+Imin)/2;
17 printf("\nAverage Load current = %.0f A", IL_avg)
18 iL=(Imin^2+(Imax-Imin)^2/3+Imin*(Imax-Imin))^0.5;
19 printf("\nRMS value of Load current = %.2f A", iL)
20 Iavg=0.5*IL_avg;
21 printf("\nAverage value of input current = %.2f A",
    Iavg)
22 Irms=Duty_cycle^0.5*iL;
23 printf("\nRMS value of input current = %.3f A", Irms
    )

```

Scilab code Exa 4.7 Calculate the load inductance

```

1 // 4.7
2 clc;
3 V=300;
4 E=0;
5 R=5;
6 f=250;
7 Id=0.2*30;
8 L=V/(4*f*Id);

```

```
9 printf("Load inductance = %.3f H" , L)
```

Scilab code Exa 4.8 Calculate the current

```
1 // 4.8
2 clc;
3 V=200;
4 E=100;
5 R=0.5;
6 t=2*10^-3;
7 L=16*10^-3;
8 Imin=10;
9 i=(V-E)/R*(1-exp(-R*t/L))+Imin*exp(-R*t/L);
10 printf("Current at the instant of turn off thyristor
         = %.2f A" , i)
11 t=5*10^-3;
12 i_5=i*exp(-R*t/L);
13 printf("\nCurrent after 5ms of turn off thyristor =
         %.2f A" , i_5)
```

Scilab code Exa 4.9 Find the speed of motor

```
1 // 4.9
2 clc;
3 emf=220;
4 duty_cycle=0.6;
5 Vi=220*duty_cycle;
6 Ra=1;
7 I=20;
8 emf_back=Vi-I*Ra;
9 N_no_load=1000;
10 N=emf_back*N_no_load/emf;
11 printf("\nSpeed of motor = %.1f rpm" , N)
```

Scilab code Exa 4.10 Calculate average load voltage

```
1 // 4.10
2 clc;
3 Ton=25*10^-3;
4 Toff=10*10^-3;
5 V=230;
6 VL=V*Ton/(Ton+Toff);
7 printf("\nAverage value of Load voltage = %.3f V",
       VL)
```

Scilab code Exa 4.11 Find maximum minimum and average load current and load voltage

```
1 // 4.11
2 clc;
3 V=100;
4 R=0.5;
5 L=1*10^-3;
6 T=3*10^-3;
7 Duty_cycle=0.3333;
8 E=0;
9 Imax=V/R*((1-exp(-Duty_cycle*T*R/L))/(1-exp(-T*R/L))-
            )-E/R;
10 printf("\nImax = %.2f A", Imax)
11 Imin=V/R*((exp(Duty_cycle*T*R/L)-1)/(exp(T*R/L)-1))-
            E/R;
12 printf("\nImin = %.1f A", Imin)
13 IL_avg=(Imax+Imin)/2;
14 printf("\nAverage Load current = %.1f A", IL_avg)
15 Vavg=Duty_cycle*V;
16 printf("\nAverage Load Voltage = %.2f V", Vavg)
```

Scilab code Exa 4.12 Find maximum minimum and average output voltage

```
1 // 4.12
2 clc;
3 V=100;
4 R=0.2;
5 L=0.8*10^-3;
6 T=2.4*10^-3;
7 Duty_cycle=1/2.4;
8 E=0;
9 Imax=V/R*((1-exp(-Duty_cycle*T*R/L))/(1-exp(-T*R/L))-
) -E/R;
10 printf("\nImax = %.2f A", Imax)
11 Imin=V/R*((exp(Duty_cycle*T*R/L)-1)/(exp(T*R/L)-1))-
E/R;
12 printf("\nImin = %.2f A", Imin)
13 Vavg=Duty_cycle*V;
14 printf("\nAverage output Voltage = %.2f V", Vavg)
```

Scilab code Exa 4.13 Calculate the series inductance in the circuit

```
1 // 4.13
2 clc;
3 V=500;
4 f=400;
5 I=10;
6 L=V/(4*f*I);
7 printf("Series inductance = %.5f H", L)
```

Scilab code Exa 4.14 Calculate the motor speed and current swing

```
1 //4.14
2 clc;
3 Motor_output=300*735.5/1000;
4 efficiency=0.9;
5 Motor_input=Motor_output/efficiency;
6 Vdc=800;
7 Rated_current=Motor_input*1000/800;
8 R=0.1;
9 L=100*10^-3;
10 T=1/400;
11 emf=Vdc-Rated_current*0.1;
12 Duty_cycle=0.2;
13 emf_n=Duty_cycle*Vdc-Rated_current*0.1;
14 N=900/(emf/emf_n);
15 printf("\nSpeed of motor = %.2f rpm", N)
16 dia=(Vdc-Duty_cycle*Vdc)/L*Duty_cycle*T;
17 printf("\nCurrent swing = %.1f A", dia)
```

Scilab code Exa 4.15 Calculate the value of capacitance and inductance

```
1 //4.15
2 clc;
3 Vc=200;
4 Im=60;
5 toff=15*10^-6;
6 C1=töff*Im/Vc;
7 C=5*10^-6*10^6;
8 printf("\nCapacitance = %.0f uF", C)
9 Ipc=Im*1.5-Im;
10 L=C/(Ipc/Vc)^2*10^6;
11 printf("\nInductance = %.1f uH", L)
```

Scilab code Exa 4.16 Calculate the period of conduction of a step up chopper

```
1 //4.16
2 clc;
3 Vav=250;
4 V=200;
5 Toff=0.6*10^-3;
6 Ton=(Vav/V)*Toff-Toff;
7 printf("Period of conduction = %.5f sec", Ton)
```

Scilab code Exa 4.17 Calculate the period of conduction of a step up chopper

```
1 //4.16
2 clc;
3 Vav=250;
4 V=150;
5 Toff=1*10^-3;
6 Ton=(Vav/V)*Toff-Toff;
7 printf("Period of conduction = %.6f sec", Ton)
```

Chapter 5

AC Regulators

Scilab code Exa 5.1 Calculate the different parameters of AC voltage regulator usi

```
1 // 5.1
2 clc;
3 Vin=150;R=8;
4 duty_cycle=36/(36+64);
5 VL=Vin*duty_cycle^0.5;
6 printf("RMS output voltage=%f V", VL)
7 Po=VL^2/R;
8 printf("\nPower output =%f W", Po)
9 // since losses are neglected
10 Pi=Po;
11 printf("\nPower Input =%f W", Pi)
12 Irms_load=VL/R;
13 Irms_input=11.25;
14 VA_input=Irms_input*Vin;
15 pf_input=Po/VA_input;
16 printf("\nInput Power factor =%f lagging",
   pf_input)
17 Ip_thy=2^0.5*Vin/R;
18 Iavg_thy=duty_cycle*Ip_thy/%pi;
19 printf("\nAverage thyristor Current =%f A",
   Iavg_thy)
```

```
20 Irms_thy=Ip_thy*duty_cycle^0.5/2;
21 printf("\nRMS thyristor Current =%.3f A", Irms_thy)
```

Scilab code Exa 5.2 Calculate the different parameters of single phase half wave A

```
1 // 5.2
2 clc;
3 Vm=2^0.5*150;
4 alph=60;
5 R=8;
6 Vin=150;
7 Vavg_out=Vm*(cosd(alph)-1)/(2*pi);
8 printf("Average output voltage =%.2f V", Vavg_out)
9 disp('The average output voltage is negative only a
       part of positive half cycle appears at the output
       whereas the whole negative half cycle appears at
       the output')
10 VL=Vm*(1/(4*pi)*(2*pi-60*pi/180+sind(120)/2))
     ^0.5;
11 printf("\nRMS output voltage =%.2f V", VL)
12 Po=VL^2/R;
13 printf("\nPower output =%.1f W", Po)
14 Iin=VL/R;
15 VA_input=Iin*Vin;
16 pf_input=Po/VA_input;
17 printf("\nInput Power factor =%.2f lagging",
       pf_input)
18 Iavg_out=Vavg_out/R;
19 Iavg_input=Iavg_out;
20 printf("\nAverage input current =%.2f A",
       Iavg_input)
21 disp('The average input current is negative because
       input current during positive half cycle is less
       than during negative half cycle ')
```

Scilab code Exa 5.3 Calculate the different parameters of single phase full wave A

```
1 // 5.3
2 clc;
3 Vin=150;
4 Vm=2^0.5*Vin;
5 alph=60;
6 R=8;
7 Vavg_out=Vm*(cosd(alph)+1)/(%pi);
8 printf("Average output voltage over half cycle =%.2f
V" , Vavg_out)
9 VL=Vm*(1/(2*%pi)*(%pi-60*%pi/180+sind(120)/2))^0.5;
10 printf("\nRMS output voltage =%.2f V" , VL)
11 Po=VL^2/R;
12 printf("\nPower output =%.1f W" , Po)
13 Iin=VL/R;
14 VA_input=Iin*Vin;
15 pf_input=Po/VA_input;
16 printf("\nInput Power factor =%.1f lagging" ,
pf_input)
17
18 Iavg_thy=Vm*(1+cosd(alph))/(2*%pi*R);
19 printf("\nAverage thyristor Current =%.2f A" ,
Iavg_thy)
20 Irms_thy=Vm/(2*R)*(1/(%pi)*(%pi-%pi/3+sind(120)/2))
^0.5;
21 printf("\nRMS thyristor Current =%.3f A" , Irms_thy)
```

Scilab code Exa 5.4 Calculate the different parameters of single phase full wave A

```
1 // 5.4
2 clc;
```

```

3 Vin=120;
4 Vm=2^0.5*Vin;
5 alph=90;
6 R=10;
7
8 VL=Vm*(1/(2*pi)*(%pi-90*pi/180+sind(180)/2))^0.5;
9 printf("\nRMS output voltage =%.2f V", VL)
10 Po=VL^2/R;
11 IL=VL/R;
12 VA_input=IL*Vin;
13 pf_input=Po/VA_input;
14 printf("\nInput Power factor =%.3f lagging",
      pf_input)
15
16 Iavg_thy=Vm*(1+cosd(alph))/(2*pi*R);
17 printf("\nAverage thyristor Current =%.2f A",
      Iavg_thy)
18 Irms_thy=IL/2^0.5;
19 printf("\nRMS thyristor Current =%.3f A", Irms_thy)
20 Irms_load=VL/R;
21 printf("\nRMS Load Current =%.3f A", Irms_load)

```

Scilab code Exa 5.5 Find RMS output voltage and average power

```

1 // 5.5
2 clc;
3 Vin=110;
4 Vm=2^0.5*Vin;
5 alph=60;
6 R=400;
7 VL=Vm*(1/(2*pi)*(%pi-60*pi/180+sind(120)/2))^0.5;
8 printf("\nRMS output voltage =%.2f V", VL)
9 Po=VL^2/R;
10 printf("\nPower output =%.2f W", Po)

```

Scilab code Exa 5.6 Find the firing angle

```
1 // 5.6
2 clc;
3 disp('When the power delivered is 80% we have')
4 //0.8=1/(%pi)*(%pi-alpha+sin(2*alpha)/2)
5 //on solving
6 alpha=60.5;
7 printf("Firing angle=%f degree",alpha)
8 disp('When the power delivered is 30% we have')
9 //0.3=1/(%pi)*(%pi-alpha+sin(2*alpha)/2)
10 //on solving
11 alpha=108.6;
12 printf("Firing angle=%f degree",alpha)
```

Scilab code Exa 5.7 Find the conduction angle and RMS output voltage

```
1 // 5.7
2 clc;
3 f=50;
4 Vin=150;
5 w=2*%pi*f;
6 L=22*10^-3; R=4;
7 th=atand(w*L/R);
8 Beta=180+th;
9 printf("Conduction angle of thyristor=%f degree",
        Beta)
10 Vm=2^0.5*Vin;
11 VL=Vm*(1/(2*pi)*(pi+sind(120)/2-sind(2*240)/2))
    ^0.5;
12 printf("\nRMS output Voltage=%f V", VL)
```

Scilab code Exa 5.8 Calculate the different parameters of single phase full wave A

```
1 // 5.8
2 clc;
3 f=50;
4 Vin=230;
5 w=2*pi*f;
6 L=20*10^-3; R=5;
7 th=atand(R/(w*L));
8 printf("Firing angle=%f degree",th)
9 disp('Therefore, Range of firing angle is 38.51
degree to 180 degree')
10 Beta=180;
11 printf("Conduction angle of thyristor=%f degree",
Beta)
12 IL=Vin/((R^2+w^2*L^2))^.5;
13 printf("\nRMS load current =%f A", IL)
14 Po=IL^2*R;
15 printf("\nPower Output =%f W", Po)
16 pf_input=Po/(Vin*IL);
17 printf("\nInput Power factor =%f lagging",
pf_input)
```

Scilab code Exa 5.10 Find the current and voltage rating

```
1 // 5.10
2 clc;
3 V=415;
4 P=20*10^3;
5 disp('For Triacs')
6 I_line=P/(3^.5*V);
7 Irms=I_line*1.5;
```

```

8 printf("RMS current rating of each triac=%f A",
    Irms)
9 Vrms=1.5*V;
10 printf("\nRMS Voltage rating of each triac=%f V",
    Vrms)
11 disp('For reverse connected thyristors')
12 Irms_thy=1.5*I_line/2^0.5;
13 printf("RMS current rating of each thyristor=%f A"
    , Irms_thy)
14 Vrms_thy=1.5*V;
15 printf("\nRMS voltage rating of each thyristor=%f V"
    , Vrms_thy)

```

Scilab code Exa 5.11 Calculate the different parameters of 3 phase star connected

```

1 // 5.11
2 clc;
3 R=15;
4 Vrms_input_phase=415/3^0.5;
5 VL=3^0.5*2^0.5*Vrms_input_phase*(1/(%pi)*(%pi/6-30*
    %pi/(180*4)+sind(60)/8))^0.5;
6 printf("\nRMS value of output voltage per phase=%f
    V" , VL)
7 Po=3*VL^2/R;
8 printf("\nPower output =%f W" , Po)
9 I_line=VL/R;
10 printf("\nLine Current =%f A" , I_line)
11 VA_input=3*Vrms_input_phase*I_line;
12 pf_input=Po/VA_input;
13 printf("\nInput Power Factor =%f lagging" ,
    pf_input)

```

Scilab code Exa 5.12 Calculate the different parameters of 3 phase star connected

```
1 // 5.12
2 clc;
3 R=15;
4 Vrms_input_phase=415/3^0.5;
5 VL=3^0.5*2^0.5*Vrms_input_phase*(1/(%pi)*(%pi/6-60*
    %pi/(180*4)+sind(120)/8))^0.5;
6 printf("\nRMS value of output voltage per phase=%.2f
    V", VL)
7 Po=3*VL^2/R;
8 printf("\nPower output =%.1f W", Po)
9 I_line=VL/R;
10 printf("\nLine Current =%.2f A", I_line)
11 VA_input=3*Vrms_input_phase*I_line;
12 pf_input=Po/VA_input;
13 printf("\nInput Power Factor =%.3f lagging",
    pf_input)
```

Chapter 6

Cycloconverters

Scilab code Exa 6.1 Find the input voltage SCR rating and Input Power Factor

```
1 // 6.1
2 clc;
3 Vo_max=250;
4 Vm=Vo_max*%pi*2^0.5/(3*sin(%pi/3));
5 Vrms=Vm/2^0.5;
6 printf("RMS value of input voltage =%.1f V", Vrms)
7 I=50;
8 Irms=I*2^0.5/3^0.5;
9 PIV=3^0.5*Vm;
10 Irms_input=(I^2/3)^0.5;
11 Po=Vo_max*I*0.8;
12 Pi_per_phase=1/3*Po;
13 pf_input=Pi_per_phase/(Irms_input*Vrms)
14 printf("\nInput power factor =%.3f lagging",
pf_input)
```

Scilab code Exa 6.2 Find RMS value of output voltage for firing angle 30 and 45 de

```
1 // 6.2
2 clc;
3 Vo_max=250;
4 alph=30;
5 Vo=Vo_max*cosd(alph);
6 printf("RMS value of output voltage for firing angle
    30 degree =%.1f V", Vo)
7 alph=45;
8 Vo=Vo_max*cosd(alph);
9 printf("\nRMS value of output voltage for firing
    angle 45 degree =%.2f V", Vo)
```

Scilab code Exa 6.3 Find RMS value of output voltage for firing angle 0 and 30 deg

```
1 // 6.3
2 clc;
3 Vrms=230;
4 alph=0;
5 Vo=6*2^0.5*Vrms/(%pi*2^0.5)*sin(%pi/6)*cosd(alph);
6 printf("RMS value of output voltage for firing angle
    0 degree =%.2f V", Vo)
7 alph=30;
8 Vo=6*2^0.5*Vrms/(%pi*2^0.5)*sin(%pi/6)*cosd(alph);
9 printf("\nRMS value of output voltage for firing
    angle 30 degree =%.1f V", Vo)
```

Chapter 7

Applications of Thyristors

Scilab code Exa 7.1 Find the value of Voltage which will turn On the crowbar

```
1 //7.1
2 clc;
3 Vzb=14.8;
4 Vt=0.85;
5 V=Vzb+Vt;
6 printf("The value of Voltage which will turn On the
crowbar=%.2f V",V)
```

Scilab code Exa 7.2 Find the value of input voltage

```
1 //7.2
2 clc;
3 Rth=50*15/(50+15);
4 I=20*10^-3;
5 Vzb=14.8;
6 Vt=0.85;
7 V=Rth*I; // Voltage drop across the thevenin's
resistance
```

```
8 Vi=V+Vzb+Vt;  
9 printf("The value of input voltage Vi=%f V",Vi)
```

Scilab code Exa 7.3 Find the value of R and C

```
1 // 7.3  
2 clc;  
3 V=200;  
4 I=4*10^-3;  
5 R=V/I;  
6 printf("Resistance=%f ohm", R)  
7 Vc=0;  
8 RL=V/10;  
9 tq=15*10^-6;  
10 C=tq/(RL *log(2))*10^6;  
11 printf("\nCapacitance=%f uF", C)
```

Scilab code Exa 7.4 Find Duty cycle and Ratio for different output powers

```
1 // 7.4  
2 clc;  
3 V=230;  
4 R=60;  
5 Po_max=V^2/R;  
6 disp('When power output is 400')  
7 Po=400;  
8 Duty_cycle=Po/Po_max;  
9 printf("Duty cycle=%f", Duty_cycle)  
10 Ton=0.4537;  
11 T=1;  
12 Toff=1-Ton;  
13 Ratio=Ton/Toff;
```

```
14 printf("\nRatio of Ton and Toff when power output is  
        400=%f", Ratio)  
15 disp('When power output is 700')  
16 Po=700;  
17 Duty_cycle=Po/Po_max;  
18 printf("Duty cycle=%f", Duty_cycle)  
19 Ton=0.794;  
20 T=1;  
21 Toff=1-Ton;  
22 Ratio=Ton/Toff;  
23 printf("\nRatio of Ton and Toff when power output is  
        700=%f", Ratio)
```

Scilab code Exa 7.5 Find RMS value of output voltage

```
1 // 7.5  
2 clc;  
3 V=230;  
4 Ton=12;  
5 Toff=19;  
6 Duty_cycle=Ton/(Ton+Toff);  
7 printf("Duty cycle=%f", Duty_cycle)  
8 Vrms_output=V*Duty_cycle^0.5;  
9 printf("\nRMS output voltage=%f V", Vrms_output)
```

Scilab code Exa 7.6 Find the power supplied to heater for different firing angles

```
1 // 7.6  
2 clc;  
3 Vin=230;  
4Vm=2^0.5*Vin;  
5 alph=90;  
6 R=50;
```

```

7 VL=Vm*(1/(2*pi)*(%pi-90*pi/180+sind(180)/2))^0.5;
8 Po=VL^2/R;
9 printf("Power supplied when firing angle is 90
degree =%.2f W", Po)
10 alph=120;
11 R=50;
12 VL=Vm*(1/(2*pi)*(%pi-120*pi/180+sind(240)/2))^0.5;
13 Po=VL^2/R;
14 printf("\nPower supplied when firing angle is 120
degree =%.2f W", Po)

```

Scilab code Exa 7.7 Find the firing angles when different powers are supplied to h

```

1 // 7.7
2 clc;
3 V=230;
4 R=10;
5 Pmax=V^2/R;
6 P=2645;
7 VL=(P*R)^2;
8 //VL=Vm*(1/(2*pi)*(%pi-alph*pi/180+sind(2*alph)/2)
    )^0.5;
9 //on solving
10 alph=90;
11 printf("Firing angle when 2645 W Power is supplied =
    %.0f degree", alph)
12 P=1587;
13 VL=(P*R)^2;
14 //VL=Vm*(1/(2*pi)*(%pi-alph*pi/180+sind(2*alph)/2)
    )^0.5;
15 //on solving
16 alph=108.6;
17 printf("\nFiring angle when 2645 W Power is supplied
    =%.1f degree", alph)

```

Scilab code Exa 7.8 Find the current rating and peak inverse voltage

```
1 // 7.8
2 clc;
3 disp('For triac')
4 P=20000;
5 V=400;
6 I=P/(V*3^0.5);
7 printf("Current rating of traic=%f A",I)
8 PIV=2^0.5*V;
9 printf("\nPIV of traic=%f V",PIV)
10 disp('When two thyristors are connected in
    antiparallel')
11 I=I/2^0.5; //since each thyristor will conduct for
    half cycle
12 printf("Current rating =%f A",I)
13 PIV=2^0.5*V;
14 printf("\nPIV =%f V",PIV)
```

Scilab code Exa 7.9 Find firing angle and power factor of converter in the armature

```
1 // 7.9
2 clc;
3 Vm=230*2^0.5;
4 Vf=2*Vm/%pi;
5 Rf=200;
6 If=Vf/Rf;
7 T=50;
8 Kt=0.8;
9 Ia=T/(Kt*If);
10 w=2*pi*900/60;
11 Vb=Kt*w*If;
```

```

12 Ra=0.3;
13 Va=Vb+Ia*Ra;
14 alph_a=acosd(Va*%pi/Vm-1)
15 printf("Firing angle of converter in the armature
        circuit=%f degree",alph_a)
16 Po_a=Va*Ia;
17 Iin=Ia*((%pi-alph_a*pi/180)/%pi)^0.5;
18 VA_input=Iin*230;
19 pf=Po_a/VA_input;
20 printf("\npower factor of converter in the armature
        circuit=%f lagging",pf)

```

Scilab code Exa 7.10 Find the torque developed and motor speed

```

1 // 7.10
2 clc;
3 Vm=230*2^0.5;
4 Vf=2*Vm/%pi;
5 alph_a=%pi/4;
6 Va=(2*Vm/%pi)*cos(alph_a);
7 Rf=200;
8 If=Vf/Rf;
9 Kt=1.1;
10 Ia=50;
11 T=Ia*(Kt*If);
12 printf("Torque of motor=%f Nm", T)
13 Ra=0.25;
14 Vb=Va-Ia*Ra-2;
15 w=Vb/(Kt*If);
16 N=w*60/(2*%pi);
17 printf("\nSpeed of motor=%f rpm", N)

```

Scilab code Exa 7.11 Find armature current and Firing angle of the semi converter

```

1 // 7.11
2 clc;
3 Vm=675*2^0.5;
4 Ia1=30;
5 N1=350;
6 N2=500;
7 Ia2=Ia1*N2/N1;
8 printf("Armature current of the semi converter=%f
A", Ia2)
9 Va1=(1+cos(90.5*pi/180))*Vm/pi;
10 Eb1=Va1-Ia1*(0.22+0.22);
11 Eb2=Eb1*Ia2*N2/(Ia1*N1);
12 Va2=Eb2+Ia2*(0.22+0.22);
13 alph_a=acosd(Va2*pi/Vm-1);
14 printf("\nFiring angle of the semi converter=%f
degree", alph_a)

```

Scilab code Exa 7.12 Find the firing angle of converter in the armature circuit and power back to source.

```

1 // 7.12
2 clc;
3 Vm=230*2^0.5;
4 Eg=-131.9
5 Ia=50;
6 Ra=0.25;
7 Va=Eg+Ia*Ra+2;
8 alph_a=acosd(Va*pi/(2*Vm))
9 printf("Firing angle of converter in the armature
circuit=%f degree", alph_a)
10 Po=abs(Va*Ia);
11 printf("\npower back to source=%f W", Po)

```

Scilab code Exa 7.13 Find the firing angle of converter in the armature circuit and power back to source.

```

1 // 7.13
2 clc;
3 Vm=400*2^0.5/(3^0.5);
4 Vf=3*3^0.5*Vm/%pi;
5 Rf=250;
6 If=Vf/Rf;
7 Kt=1.33;
8 Ia=50;
9 w=2*%pi*1200/60;
10 Vb=Kt*w*If;
11 Ra=0.3;
12 Va=Vb+Ia*Ra;
13 alph_a=acosd(Va/Vf);
14 printf("Firing angle of converter in the armature
        circuit=%.3f degree",alph_a)

```

Scilab code Exa 7.14 Find the input power speed and torque of separately excited d

```

1 // 7.14
2 clc;
3 V=500;
4 Ia=200;
5 Ra=0.1;
6 Pi=V*Ia*0.5;
7 printf("Input power=%.0 f W" , Pi)
8 Va=0.5*500;
9 Eb=Va-Ia*Ra;
10 If=2;
11 Kt=1.4;
12 w=Eb/(Kt*If)
13 N=w*60/(2*%pi)
14 printf("\nSpeed=%.2 f rpm" , N)
15 T=Kt*If*Ia;
16 printf("\nTorque=% .0 f N-m" , T)

```

Scilab code Exa 7.15 Find the average voltage power dissipated and motor speed of

```
1 //7.15
2 clc;
3 Rb=7.5;
4 Ra=0.1;
5 Kt=1.4;
6 Ia=120;
7 If=1.6;
8 Duty_cycle=0.35;
9 Vavg=Rb*Ia*(1-Duty_cycle);
10 printf("Average voltage across chopper=%f V", Vavg
    )
11 Pb=Rb*Ia^2*(1-Duty_cycle);
12 printf("\nPower dissipated in breaking resistance=%
    .0f W", Pb)
13 Eb=Vavg+Ia*Ra;
14 w=Eb/(Kt*If);
15 N=w*60/(2*pi);
16 printf("\nSpeed=%f rpm", N)
```

Scilab code Exa 7.16 Find the speed for different values of torque

```
1 //7.16
2 clc;
3Vm=220*2^0.5;
4 alph=90;
5 Va=3*3^0.5*Vm*(1+cosd(alph))/(2*pi);
6 Kt=2;
7 Ra=0.72;
8 disp('For armature current of 5A')
9 Ia=5;
```

```

10 T=Ia*Kt;
11 printf("\nTorque=%f N-m", T)
12 Eb=Va-Ia*Ra;
13 w=Eb/(Kt);
14 N=w*60/(2*pi);
15 printf("\nSpeed=%f rpm", N)
16 disp('For armature current of 10A')
17 Ia=10;
18 T=Ia*Kt;
19 printf("\nTorque=%f N-m", T)
20 Eb=Va-Ia*Ra;
21 w=Eb/(Kt);
22 N=w*60/(2*pi);
23 printf("\nSpeed=%f rpm", N)
24 disp('For armature current of 20A')
25 Ia=20;
26 T=Ia*Kt;
27 printf("\nTorque=%f N-m", T)
28 Eb=Va-Ia*Ra;
29 w=Eb/(Kt);
30 N=w*60/(2*pi);
31 printf("\nSpeed=%f rpm", N)
32 disp('For armature current of 30A')
33 Ia=30;
34 T=Ia*Kt;
35 printf("\nTorque=%f N-m", T)
36 Eb=Va-Ia*Ra;
37 w=Eb/(Kt);
38 N=w*60/(2*pi);
39 printf("\nSpeed=%f rpm", N)
40 disp('For armature current of 50A')
41 Ia=50;
42 T=Ia*Kt;
43 printf("\nTorque=%f N-m", T)
44 Eb=Va-Ia*Ra;
45 w=Eb/(Kt);
46 N=w*60/(2*pi);
47 printf("\nSpeed=%f rpm", N)

```

```
48 disp('For armature current of 60A')
49 Ia=60;
50 T=Ia*Kt;
51 printf("\nTorque=%f N-m", T)
52 Eb=Va-Ia*Ra;
53 w=Eb/(Kt);
54 N=w*60/(2*pi);
55 printf("\nSpeed=%f rpm", N)
```

Scilab code Exa 7.17 Find the speed at no load and firing angle

```
1 // 7.17
2 clc;
3 Vm=400*2^0.5;
4 alph=30;
5 Vavg=3*3^0.5*Vm/(2*pi*3^0.5)*(1+cosd(alph));
6 I=5;
7 R=0.1;
8 Eb=Vavg-I*R;
9 N=Eb/0.3;
10 printf("Speed at no load=%f rpm", N)
11 N=1600;
12 Eb=N*0.3;
13 I=50;
14 V=Eb+I*R;
15 alph=acosd(3^0.5*2*pi*V/(Vm*3*3^0.5)-1)
16 printf("\nFiring angle =%f degree", alph)
```

Scilab code Exa 7.18 Find the motor speed

```
1 // 7.18
2 clc;
3 Vdc=2*2^0.5*230/pi;
```

```

4 TL=25;
5 Kt=0.25;
6 Ia=(TL/Kt)^0.5;
7 w=(Vdc-1.5*Ia)/(Kt*Ia);
8 N=w*60/(2*pi);
9 printf("Motor speed=%f rpm",N)

```

Scilab code Exa 7.19 Find the load torque stator applied voltage and rotor current

```

1 //7.19;
2 clc;
3 p=4
4 f=50;
5 ns=2*f*60/p;
6 TL_1300=40*(1300/1440)^2;
7 printf("Load torque=%f Nm",TL_1300)
8 n=1300;
9 s=(ns-n)/ns;
10 r2s=0.08*2^2; // in book r2'=r2s
11 x2s=0.12*2^2;
12 I2s=(TL_1300*2*pi*s*25/(3*r2s))^0.5;
13 I2=2*I2s;
14 printf("\nRotor current=%f A",I2)
15 r1=0.64;
16 x1=1.1;
17 V1=I2s*((r1+r2s/s)^2+(x1+x2s)^2)^0.5;
18 Vstator=3^0.5*V1;
19 printf("\nStator applied voltage=%f V",Vstator)

```

Scilab code Exa 7.20 Find the load torque stator applied voltage and rotor current

```

1 //7.20
2 clc;

```

```

3 r2s=0.32;
4 r1=0.64;
5 x2s=0.48;
6 x1=1.1;
7 s=r2s/(r1^2+(x1+x2s)^2)^0.5;
8 printf("\nSlip=%f ",s)
9 V1=400/3^0.5;
10 Tmax=1.5*V1^2/(2*pi*25)*(1/(r1+(r1^2+(x1+x2s)^2)^0.5))
11 printf("\nMaximum Torque=%f Nm",Tmax)
12 n=25*(1-s);
13 N=n*60;
14 printf("\nSpeed=%f rpm",N)
15 disp('at 25 Hz')
16 x1=0.55;
17 x2s=0.24;
18 s=r2s/(r1^2+(x1+x2s)^2)^0.5;
19 printf("\nSlip=%f ",s)
20 V1=0.5*400/3^0.5;
21 Tmax=1.5*V1^2/(2*pi*12.5)*(1/(r1+(r1^2+(x1+x2s)^2)^0.5))
22 printf("\nMaximum Torque=%f Nm",Tmax)
23 n=12.5*(1-s);
24 N=n*60;
25 printf("\nSpeed=%f rpm",N)

```

Scilab code Exa 7.21 Find the starting torques at different frequencies

```

1 // 7.21
2 clc;
3 r2s=0.32;
4 r1=0.64;
5 x2s=0.48;
6 x1=1.1;
7

```

```
8 V1=400/3^0.5;
9 Tstarting=3*V1^2*r2s/(2*pi*25)*(1/((r1+r2s)^2+(x1+
    x2s)^2))
10 printf("\nStarting Torque=%f Nm",Tstarting)
11
12 disp('at 25 Hz')
13 x1=0.55;
14 x2s=0.24;
15 V1=0.5*400/3^0.5;
16 Tstarting=3*V1^2*r2s/(2*pi*12.5)*(1/((r1+r2s)^2+(x1
    +x2s)^2))
17 printf("\nStarting Torque=%f Nm",Tstarting)
```

Chapter 8

Integrated circuits and operational amplifiers

Scilab code Exa 8.1 Find dc currents and voltages

```
1 // 8.1
2 clc;
3 Vcc=12;
4 Re=3.8*10^3;
5 Rc=4.1*10^3;
6 Ie=(Vcc-0.7)/Re*10^3;
7 printf("Ie=%3f mA",Ie)
8 Ic=0.5*Ie;
9 printf("\nIc=%3f mA",Ic)
10 Vo=Vcc-Ic*Rc*10^-3;
11 printf("\nVo=%1f V",Vo)
```

Scilab code Exa 8.2 Calculate the different parameters of differential amplifier

```
1 // 8.2
2 clc;
```

```

3 Vcc=12;
4 Re=1*10^6;
5 Rc=1*10^6;
6 Ie=(Vcc-0.7)/Re*10^3;
7 re=25*2/Ie;
8 printf("re=%f ohm",re)
9 Vgd=Rc/(2*re);
10 printf("\nVoltage gain for the differential input=%
    .1f ",Vgd)
11 Vi=2.1*10^-3;
12 Vo_Ac=Vgd*Vi;
13 printf("\nAC output voltage=%f V",Vo_Ac)
14 Beta=75;
15 Zi=2*Beta*re;
16 printf("\nInput impedance=%f ohm",Zi)
17 Rc=1*10^6;
18 RE=10^6;
19 CMG=Rc/(re+2*RE);
20 printf("\nCommon mode gain=%f ",CMG)
21 CMRR=Vgd/CMG;
22 printf("\nCommon mode rejection ratio=%f ",CMRR)

```

Scilab code Exa 8.3 Find the closed loop gain output and error voltage

```

1 // 8.3
2 clc;
3 open_loop_gain=100000;
4 FF=0.01;
5 Closed_loop_gain=open_loop_gain/(1+open_loop_gain*FF
    );
6 printf("Closed loop gain=%f",Closed_loop_gain)
7 Vi=2*10^-3;
8 output=Vi*Closed_loop_gain;
9 printf("\nOutput=%f V",output)
10 Error_voltage=output/open_loop_gain*10^6;

```

```
11 printf("\nError voltage=%f uV",Error_voltage)
```

Scilab code Exa 8.4 Find the closed loop gain output and error voltage

```
1 // 8.4
2 clc;
3 open_loop_gain=15000;
4 FF=0.01;
5 Closed_loop_gain=open_loop_gain/(1+open_loop_gain*FF
    );
6 printf("Closed loop gain=%f",Closed_loop_gain)
7 Vi=2*10^-3;
8 output=Vi*Closed_loop_gain;
9 printf("\nOutput=%f V",output)
10 Error_voltage=output/open_loop_gain*10^6;
11 printf("\nError voltage=%f uV",Error_voltage)
```

Scilab code Exa 8.5 Find the input and output impedances

```
1 // 8.5
2 clc;
3 Av=100000;
4 beta=0.01;
5 Zi=2*10^6;
6 Closed_loop_input_imped=Zi*(1+Av*beta)*10^-6;
7 printf("Closed loop input impedance=%f Mega-ohm",
    Closed_loop_input_imped)
8 Zo=75;
9 Closed_loop_output_imped=Zo/(1+Av*beta);
10 printf("\nClosed loop output impedance=%f ohm",
    Closed_loop_output_imped)
```

Scilab code Exa 8.6 Find closed loop gain and desensitiviy

```
1 //8.6
2 clc;
3 Av=100000;
4 beta=0.001;
5 Closed_loop_gain=Av/(1+Av*beta);
6 printf("\nClosed loop gain=%f ",Closed_loop_gain)
7 Desensitivity=(1+Av*beta);
8 printf("\nDesensitivity=%f ",Desensitivity)
```

Scilab code Exa 8.7 Find the closed loop gain and upper cut off frequency

```
1 //8.7
2 clc;
3 f_unity=10^6;
4 Av=100000;
5 open_loop_upper_cutoff_f=f_unity/Av;
6 printf("open loop upper cutoff frequency=%f Hz",
       open_loop_upper_cutoff_f)
7 disp('when beta=0.001')
8 beta=0.001;
9 Closed_loop_gain=Av/(1+Av*beta);
10 printf("\nClosed loop gain=%f ",Closed_loop_gain)
11 upper_cutoff_frequency=f_unity/Closed_loop_gain;
12 printf("\nUpper cutoff frequency=%f Hz",
       upper_cutoff_frequency)
13 disp('when beta=0.01')
14 beta=0.01;
15 Closed_loop_gain=Av/(1+Av*beta);
16 printf("\nClosed loop gain=%f ",Closed_loop_gain)
17 upper_cutoff_frequency=f_unity/Closed_loop_gain;
```

```
18 printf("\nUpper cutoff frequency=%f Hz" ,  
         upper_cutoff_frequency)  
19 disp('when beta=0.1')  
20 beta=0.1;  
21 Closed_loop_gain=Av/(1+Av*beta);  
22 printf("\nClosed loop gain=%f " ,Closed_loop_gain)  
23 upper_cutoff_frequency=f_unity/Closed_loop_gain;  
24 printf("\nUpper cutoff frequency=%f Hz" ,  
         upper_cutoff_frequency)
```

Scilab code Exa 8.8 Find the slew rate

```
1 //8.8  
2 clc;  
3 Imax=10*10^-6;  
4 C=4000*10^-12;  
5 Slew_rate=Imax/C;  
6 printf("Slew rate=%f V/s" , Slew_rate)
```

Scilab code Exa 8.9 Find the slew rate distortion of the op amp

```
1 //8.9  
2 clc;  
3 f=10*10^3;  
4 Vp=6  
5 Initial_slope_of_sine_wa=2*pi*f*Vp*10^-6;  
6 printf("Initial slope of sine wave= %.5f V/us" ,  
       Initial_slope_of_sine_wa)  
7 disp('Since slew rate of the amplifier is 0.4V/us ,  
      there is no slew rate distortion')
```

Scilab code Exa 8.10 Find the slew rate distortion of the op amp and amplitude of

```
1 // 8.10
2 clc;
3 f=10*10^3;
4 Vp=10;
5 Initial_slope_of_sine_wa=2*pi*f*Vp*10^-6;
6 printf("Initial slope of sine wave= %.3f V/us",
    Initial_slope_of_sine_wa)
7 disp('Since slew rate of the amplifier is 0.5V/us,
        so slew rate distortion will occur')
8 Sr=0.5*10^6;
9 Vp=Sr/(2*pi*f);
10 printf("Amplitude of the input signal=% .2f V",Vp)
```

Scilab code Exa 8.11 Find the different parameters of inverting amplifier

```
1 // 8.11
2 clc;
3 Rf=100*10^3;
4 R1=1000;
5 Gain=-Rf/R1;
6 printf("Closed loop gain=% .0f", Gain)
7 Av=100000;
8 Zo=75;
9 f_unity=10^6;
10 beta=R1/(R1+Rf);
11 Z_closed=Zo/(1+Av*beta);
12 printf("\nClosed loop output impedance=% .6f ohm",
    Z_closed)
13 closed_loop_upper_cut_f=f_unity*beta;
14 printf("\nClosed loop upper cutoff frequency=% .0f
        Hz", closed_loop_upper_cut_f)
15 closed_loop_input_impe=1000;
16 printf("\nClosed loop input impedance=% .0f ohm",
```

```
closed_loop_input_impe)
```

Scilab code Exa 8.12 Find the different parameters of non inverting amplifier

```
1 // 8.12
2 clc;
3 R2=100*10^3;
4 R1=100;
5 Zin=2*10^6;
6 Zo=75;
7 Gain=(R1+R2)/R1;
8 printf("Closed loop voltage gain=%0.0 f", Gain)
9 Av=100000;
10
11 beta=R1/(R1+R2);
12 Z_closed=Zin*(1+Av*beta)*10^-6;
13 printf("\nClosed loop input impedance=%0.1 f mega-ohm"
       , Z_closed)
14
15 closed_loop_output_impe=Zo/(1+Av*beta);
16 printf("\nClosed loop output impedance=%0.3 f ohm",
       closed_loop_output_impe)
```

Scilab code Exa 8.13 Find the different parameters of ac amplifier

```
1 // 8.13
2 clc;
3 R1=1000;
4 R2=100000;
5 Avf=(R1+R2)/R1;
6 printf("Closed loop gain=%0.0 f", Avf)
7 beta=R1/(R1+R2);
8 f_unity=100000;
```

```

9 f2=f_unity*beta;
10 printf("\nUpper cut off frequency=%f Hz", f2)
11 disp('Critical frequencies')
12 C1=10^-6;
13 R3=150*10^3;
14 fc=1/(2*pi*R3*C1);
15 printf("\nCritical frequency when R is 150 Kohm=%f
Hz", fc)
16 R3=15*10^3;
17 fc=1/(2*pi*R3*C1);
18 printf("\nCritical frequency when R is 15 Kohm=%f
Hz", fc)
19 R3=1*10^3;
20 fc=1/(2*pi*R3*C1);
21 printf("\nCritical frequency when R is 1 Kohm=%f
Hz", fc)
22 disp('The lower cutt off frequency is the highest of
the above three critical frequencies i.e.159.15
Hz')

```

Scilab code Exa 8.14 Find the output voltage

```

1 //8.14
2 clc;
3 Rf=50*10^3;
4 R1=10*10^3;
5 R2=R1;
6 R3=R1;
7 V1=0.5;
8 V2=1.5;
9 V3=0.2;
10 Vo=-Rf*((V1/R1)+(V3/R3)+(V2/R2));
11 printf("Output voltage=%f V", Vo)

```

Scilab code Exa 8.17 Find the output voltage

```
1 //8.17
2 clc;
3 R1=50*10^3;
4 R=10*10^3;
5 Vs1=4.5;
6 Vs2=5;
7 Vo=R1/R*(Vs2-Vs1);
8 printf("Output voltage=%f V", Vo)
```

Scilab code Exa 8.18 Find CMRR in dB

```
1 //8.18
2 clc;
3 Vcom=0.5*(2+2);
4 Acom=5*10^-3/Vcom;
5 CMRR=20*log10(50/Acom);
6 printf("CMRR=%f dB", CMRR)
```

Scilab code Exa 8.21 Find the different parameters of high pass filter

```
1 //8.21
2 clc;
3 R2=5.6*10^3;
4 R1=1*10^3;
5 Avf=1+R2/R1;
6 printf("Mid band Gain=%f", Avf)
7 Vin=1.6;
```

```
8 Vo=Avf*Vin;
9 printf("\nOutput voltage=%f mV", Vo)
10 R=1000;
11 C=0.001*10^-6;
12 fc=1/(2*pi*R*C);
13 printf("\nCutt off frequency=%f Hz", fc)
14 Gain=0.707*Avf;
15 printf("\nGain=%f", Gain)
```

Scilab code Exa 8.22 Find the different parameters of low pass filter

```
1 //8.22
2 clc;
3 R2=5.6*10^3;
4 R1=10*10^3;
5 Avf=1+R2/R1;
6 printf("Mid band Gain=%f", Avf)
7 Vin=1.1;
8 Vo=Avf*Vin;
9 printf("\nOutput voltage=%f mV", Vo)
10 R=10000;
11 C=0.001*10^-6;
12 fc=1/(2*pi*R*C);
13 printf("\nCutt off frequency=%f Hz", fc)
14 Vo=0.707*Avf;
15 printf("\nOutput voltage=%f mV", Vo)
```

Chapter 9

Number systems

Scilab code Exa 9.1 Convert decimal number into equivalent binary number

```
1 // 9.1
2 clc;
3 x=10;
4 disp('The binary number is ')
5 a=dec2bin(x);
6 disp(' ',a)
```

Scilab code Exa 9.2 Convert decimal number into equivalent binary number

```
1 // 9.2
2 clc;
3 x=25;
4 disp('The binary number is ')
5 a=dec2bin(x);
6 disp(' ',a)
```

Scilab code Exa 9.3 Convert binary number into equivalent decimal number

```
1 // 9.3
2 clc;
3 a='101110';
4 disp('The decimal no. is ')
5 x=bin2dec(a);
6 disp(' ',x)
```

Scilab code Exa 9.4 Convert decimal number into equivalent binary number

```
1 // 9.4
2 clc;
3 x=15;
4 disp('The binary number of decimal 15 is ')
5 a=dec2bin(x);
6 disp(' ',a)
7 x=31;
8 disp('The binary number of decimal 31 is ')
9 a=dec2bin(x);
10 disp(' ',a)
```

Scilab code Exa 9.5 Calculate the subtraction of two binary numbers

```
1 // 9.5
2 clc;
3 a='11001';
4 b=bin2dec(a);
5 c='10001';
6 f=bin2dec(c);
7 d=b-f;
8 s=dec2bin(d);
9 disp('Subtraction of two binary numbers=')
```

```
10 disp(s)
```

Scilab code Exa 9.6 Calculate the subtraction of two binary numbers

```
1 // 9.6
2 clc;
3 a='1010';
4 b=bin2dec(a);
5 c='0111';
6 f=bin2dec(c);
7 d=b-f;
8 s=dec2bin(d);
9 disp('Subtraction of two binary numbers=')
10 disp(s)
```

Scilab code Exa 9.7 Express the decimals in 16 bit signed binary system

```
1 // 9.7
2 clc;
3 a=8;
4 b=dec2bin(a);
5 disp(b)
6 disp('The 16 bit signed binary number of +8=0000
      0000 0000 1000')
7 disp('The 16 bit signed binary number of -8=1000
      0000 0000 1000')
8 a=165;
9 b=dec2bin(a);
10 disp(b)
11 disp('The 16 bit signed binary number of +165=0000
      0000 1010 0101')
12 disp('The 16 bit signed binary number of -165=1000
      0000 1010 0101')
```

Scilab code Exa 9.8 Calculate the twos complement representation

```
1 // 9.8
2 clc;
3 a='0001 1111';
4 disp(a)
5 disp('Since the MSB is 0 so this is a positive
       number and its 2 s complement representation is')
6 b=bin2dec(a);
7 disp(b)
8 a='1110 0101';
9 disp(a)
10 disp('Since the MSB is 1 so this is a negative
        number and its 2 s complement representation is')
11 c=bin2dec(a);
12 xc= bitcmp (c ,8);
13 b=xc+1;
14 disp(b)
15 a='1111 0111';
16 disp(a)
17 disp('Since the MSB is 1 so this is a negative
        number and its 2 s complement representation is')
18 c=bin2dec(a);
19 xc= bitcmp (c ,8);
20 b=xc+1;
21 disp(b)
```

Scilab code Exa 9.9 Find the largest positive and negative number for 8 bits

```
1 // 9.9
2 clc;
```

```
3 disp('The largest 8 bit positive number is +127 and  
      is represented in binary as')  
4 a='0111 1111';  
5 disp(a)  
6 disp('The largest 8 bit negative number is -128 and  
      is represented in binary as')  
7 a='1000 0000';  
8 disp(a)
```

Scilab code Exa 9.10 Calculate addition and subtraction of the numbers

```
1 // 9.10  
2 clc;  
3 c=24;  
4 xc= bitcmp (c ,8);  
5 A=xc+1;  
6 B=16;  
7 Ans=A+B;  
8 a=dec2bin(Ans)  
9 disp(a)  
10 disp('Since the MSB is 1 so the number is negative  
       and equal to -8')  
11  
12 Ans=A-B;  
13 a=dec2bin(Ans)  
14 disp(a)  
15 disp('Since the MSB is 1 so the number is negative  
       and equal to -40')
```

Scilab code Exa 9.11 Calculate addition and subtraction of the numbers

```
1 // 9.11  
2 clc;
```

```

3 c=60;
4 xc= bitcmp (c ,8);
5 A=xc+1;
6 d=28;
7 xd= bitcmp (d ,8);
8 B=xd+1;
9 Ans=B+A;
10 a=dec2bin(Ans)
11 disp(a)
12 disp('Since the MSB is 1 so the number is negative
      and equal to -88')
13 Ans=B-A;
14 a=dec2bin(Ans ,8)
15 disp(a)
16 disp('Since the MSB is 0 so the number is positive
      and equal to +32')

```

Scilab code Exa 9.12 Convert decimal number into equivalent binary number

```

1 // 9.12
2 clc;
3 q =0;
4 b =0;
5 s =0;
6 a =0.6875;    // accepting the decimal input from
                 user
7 d = modulo (a ,1) ;
8 a = floor ( a ) ;
9 while (a >0)
10 x = modulo (a ,2) ;
11 b = b + (10^ q ) * x ;
12 a = a /2;
13 a = floor ( a ) ;
14 q = q +1;
15 end

```

```

16  for i =1:10
17  // for fractional part
18 d = d *2;
19 q = floor ( d ) ;
20 s = s + q /(10^ i ) ;
21 if d >=1 then
22 d =d -1;
23 end
24 end
25 m=b+s;
26 printf("Equivalent binary number=%.4 f" ,m)

```

Scilab code Exa 9.13 Convert decimal number into equivalent binary number

```

1 // 9.13
2 clc;
3 q =0;
4 b =0;
5 s =0;
6 a =0.634;    // accepting the decimal input from user
7 d = modulo (a ,1) ;
8 a = floor ( a ) ;
9 while (a >0)
10 x = modulo (a ,2) ;
11 b = b + (10^ q ) * x ;
12 a = a /2;
13 a = floor ( a ) ;
14 q = q +1;
15 end
16 for i =1:10
17 // for fractional part
18 d = d *2;
19 q = floor ( d ) ;
20 s = s + q /(10^ i ) ;
21 if d >=1 then

```

```

22 d =d -1;
23 end
24 end
25 m=b+s;
26 printf("Equivalent binary number=%.7f",m)

```

Scilab code Exa 9.14 Convert decimal number into equivalent binary number

```

1 // 9.14
2 clc;
3 clear;
4 q =0;
5 b =0;
6 s =0;
7 a =39.12; // accepting the decimal input from user
8 d = modulo (a ,1) ;
9 a = floor ( a ) ;
10 while (a >0)
11 x = modulo (a ,2) ;
12 b = b + (10^ q ) * x ;
13 a = a /2;
14 a = floor ( a ) ;
15 q = q +1;
16 end
17 for i =1:10
18 // for fractional part
19 d = d *2;
20 q = floor ( d ) ;
21 s = s + q /(10^ i ) ;
22 if d >=1 then
23 d =d -1;
24 end
25 end
26 m=b+s;
27 printf("Equivalent binary number=%.7f",m)

```

Scilab code Exa 9.15 Find the addition of binary numbers

```
1 // 9.15
2 clc;
3 a= '1011010101';
4 d=bin2dec(a);
5 c= '100011010';
6 b=bin2dec(c);
7 e=d+b;
8 f=dec2bin(e);
9 disp('addition of binary numbers =')
10 disp(f)
```

Scilab code Exa 9.16 Convert binary number into equivalent decimal number

```
1 // 9.16
2 clc;
3 p =1;
4 q =1;
5 z =0;
6 b =0;
7 w =0;
8 f =0;
9 bin =11001.001011; // binary input
10 d = modulo (bin ,1) ;
11 d= d *10^10;
12 a = floor ( bin ) ;
13 while (a >0)
14 r = modulo (a ,10) ;
15 b(1,q) = r ;
16 a=a /10;
```

```

17 a= floor ( a ) ;
18 q = q +1;
19 end
20 for m =1: q -1
21 c=m -1;
22 f=f+b(1,m) *(2^ c);
23 end
24 while (d >0)
25 e = modulo (d ,2)
26 w (1 , p ) = e
27 d = d /10;
28 d = floor ( d )
29 p = p +1;
30 end
31 for n =1: p -1
32 z = z + w (1 , n ) *(0.5) ^ (11 - n ) ;
33 end
34 z = z *10000;
35 z = round ( z ) ;
36 z = z /10000;
37 x=f+z;
38 printf (" Equivalent decimal number=% .6f " ,x)

```

Scilab code Exa 9.17 Convert hexadecimal number into equivalent decimal number

```

1 //9.17
2 clc;
3 a='8A3';
4 disp('The decimal no. is ')
5 x=hex2dec(a);
6 disp(' ',x)

```

Scilab code Exa 9.18 Convert decimal number into equivalent hexadecimal number

```
1 // 9.18
2 clc;
3 a=268;
4 disp('The hexa decimal no. is ')
5 x=dec2hex(a);
6 disp(' ',x)
```

Scilab code Exa 9.19 Convert decimal number into equivalent hexadecimal number

```
1 // 9.19
2 clc;
3 a=5741;
4 disp('The hexa decimal no. is ')
5 x=dec2hex(a);
6 disp(' ',x)
```

Scilab code Exa 9.20 Convert hexadecimal number into equivalent decimal number

```
1 // 9.20
2 clc;
3 a='D70';
4 disp('The decimal no. is ')
5 x=hex2dec(a);
6 disp(' ',x)
```
