

Scilab Textbook Companion for
Modern Electronic Instrumentation And
Measurement Techniques
by A. D. Helfrick And W. D. Cooper¹

Created by
Abhijith C D
B.E
Electronics Engineering
National Institute of Engineering
College Teacher
M.s. Vijaykumar
Cross-Checked by
TechPassion

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Modern Electronic Instrumentation And Measurement Techniques

Author: A. D. Helfrick And W. D. Cooper

Publisher: Dorling Kindersly Pvt. Ltd. India

Edition: 1

Year: 2009

ISBN: 978-81-317-0888-0

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Measurement and Error	5
2 Systems of Units of Measurement	22
4 Electromechanical Indicating Instruments	27
5 Bridge Measurements	42
6 Electronic Instruments for Measuring Basic Parameters	51
7 Oscilloscopes	60
9 Signal Analysis	62
11 Transducers as Input Elements to Instrumentation Systems	66
12 Analog and Digital Data Acquisition Systems	68
14 Fiber Optics Measurements	70

List of Scilab Codes

Exa 1.1	To find Average voltage Range of error	5
Exa 1.2	To find Total resistance	6
Exa 1.3	To find voltage drop across resistor	7
Exa 1.4	To find sum with range of doubt	8
Exa 1.5	To find difference with range of doubt	9
Exa 1.6	To find difference with range of doubt	10
Exa 1.7	To find Apparent and actual resistance	11
Exa 1.8	To find Apparent and actual resistance	13
Exa 1.9	To find Arithmetic mean and deviation from mean	14
Exa 1.10	To find Average deviation	16
Exa 1.11	To find Std deviation and Probable error	17
Exa 1.12	To find Limiting error	18
Exa 1.13	To find the maximum error	19
Exa 1.14	To find limiting error	20
Exa 2.1	To convert area in metre to feet	22
Exa 2.2	To convert flux density to different units	23
Exa 2.3	To convert velocity to a different unit	23
Exa 2.4	To convert density to a different unit	24
Exa 2.5	To convert speed limit to a different unit	25
Exa 4.1	To find Shunt resistance required	27
Exa 4.2	To design Ayrton shunt	28
Exa 4.3	To design multirange dc voltmeter	30
Exa 4.4	To design multirange dc voltmeter	31
Exa 4.5	To find voltage reading and Error	33
Exa 4.6	To find the value of unknown resistor	35
Exa 4.7	To find the scale error	36
Exa 4.8	To find shunt and current limiting resistor	38

Exa 4.9	To find multiplier resistor	39
Exa 4.10	To find voltmeter sensitivity on AC range . .	40
Exa 5.1	To find deflection caused by the given unbalance	42
Exa 5.2	To check the capability of detecting unbalance	43
Exa 5.3	To find the unknown impedance	45
Exa 5.4	To find the unknown impedance	47
Exa 5.5	To balance the unbalanced bridge	48
Exa 6.1	To find the form factor and error	51
Exa 6.2	To find the form factor and error	52
Exa 6.3	To find the maximum time	54
Exa 6.4	To find the distributed capacitance	55
Exa 6.5	To find the self capacitance	56
Exa 6.6	To find percentage error	57
Exa 6.7	To find percentage error	58
Exa 7.1	To find minimum distance	60
Exa 9.1	To find dynamic range of spectrum analyser	62
Exa 9.2	To find minimum detectable signal	63
Exa 9.3	To find dynamic range and total frequency display	64
Exa 11.1	To find change in resistance	66
Exa 12.1	To find percentage error	68
Exa 14.1	To find acceptance angle and numerical aperture	70
Exa 14.2	To find loss in the fiber	71
Exa 14.3	To find current developed in photodiode . .	72
Exa 14.4	To find elapsed time	73

Chapter 1

Measurement and Error

Scilab code Exa 1.1 To find Average voltage Range of error

```
1 // To find Average voltage Range of error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1–1 in Page 3
7
8
9 clear; clc; close;
10
11 // Given data
12 E_1 = 117.02; // Voltage observed by 1st observer is
   117.02V
13 E_2 = 117.11; // Voltage observed by 2nd observer is
   117.11V
14 E_3 = 117.08; // Voltage observed by 3rd observer is
   117.08V
15 E_4 = 117.03; // Voltage observed by 4th observer is
   117.03V
16
```

```

17 // Calculations
18 E_av = (E_1+E_2+E_3+E_4)/4;
19 printf("(a) The average voltage , E_av = %0.2f V\n"
      ,E_av);
20
21 E_max = max (E_1,E_2,E_3,E_4); // Maximum value
      among the 4 nos
22 E_min = min (E_1,E_2,E_3,E_4); // Minimum value
      among the 4 nos
23
24 range_1 = E_max - E_av; // Range calculated using
      two different formulae
25 range_2 = E_av - E_min; // Range calculated using
      two different formulae
26
27 avg_range = (range_1+range_2)/2
28 printf("(b) The average range of error = +/- %0.2f
      V" ,avg_range);
29
30 // Result
31 // (a) The average voltage , E_av = 117.06 V
32 // (b) The average range of error = +/- 0.05 V

```

Scilab code Exa 1.2 To find Total resistance

```

1 // To find Total resistance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-2 in Page 4
7

```

```

8
9 clear; clc; close;
10
11 // Given data
12 R_1 = 18.7; // The first resistance is 18.7ohm
13 R_2 = 3.624; // The second resistance is 3.624ohm
14
15 // Calculations
16 R_T = R_1 + R_2; // formula to calculate total
                     resistance in series
17 printf("The total resistance connected in series =
         %0.3f ohm\n",R_T);
18 printf("As one of the resistance is accurate to only
         tenths of an ohm, The result should be reduced
         to the nearest tenth. \n Hence ")
19 printf("the total resistance is = %0.1f ohm",R_T);
20
21 //Result
22 // The total resistance connected in series = 22.324
                     ohm
23 // As one of the resistance is accurate to only
                     tenths of an ohm, The result should be reduced to
                     the nearest tenth.
24 // Hence the total resistance is = 22.3 ohm

```

Scilab code Exa 1.3 To find voltage drop across resistor

```

1 // To find voltage drop across resistor
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India

```

```

6 // Example 1–3 in Page 4
7
8
9 clear; clc; close;
10
11 // Given data
12 I = 3.18; //Current flowing through the resistor =
13 // 3.18A
13 R = 35.68; // The value of resistor = 35.68ohm
14
15 // Calculations
16 E = I*R;
17 printf("The voltage drop across the resistor = %0.4f
18 // volts",E);
18 disp('Since there are 3 significant figures involved
19 // in the multiplication , the result can be written
20 // only to a max of 3 significant figures');
19 printf("Hence the voltage drop across the resistor =
21 // %0.0f volts",E);
20
21 //Result
22 // The voltage drop across the resistor = 113.4624
23 // volts
23 // Since there are 3 significant figures involved in
24 // the multiplication , the result can be written
24 // only to a max of 3 significant figures
24 // Hence the voltage drop across the resistor = 113
25 // volts

```

Scilab code Exa 1.4 To find sum with range of doubt

```

1 // To find sum with range of doubt
2 // Modern Electronic Instrumentation And Measurement

```

Techniques

```
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1–4 in Page 5
7
8
9 clear; clc; close;
10
11 // Given data
12 // let N_1 = X_1 +/− Y_1
13 //      N_2 = X_2 +/− Y_2
14 X_1 = 826;
15 Y_1 = 5;
16 X_2 = 628;
17 Y_2 = 3;
18
19 // Calculations
20 X = (X_1 + X_2);
21 Y = (Y_1 + Y_2);
22 printf("SUM = %d +/− %d\n", X, Y);
23 %doubt = Y/X*100;
24 printf("The percentage range of doubt = +/−%0.2f%%" ,
    %doubt);
25
26 // Result
27 // SUM = 1454 +/− 8
28 // The percentage range of doubt = +/−0.55%
```

Scilab code Exa 1.5 To find difference with range of doubt

```
1 // To find difference with range of doubt
2 // Modern Electronic Instrumentation And Measurement
```

Techniques

```
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1–5 in Page 5
7
8
9 clear; clc; close;
10
11 // Given data
12 // let N_1 = X_1 +/− Y_1
13 //      N_2 = X_2 +/− Y_2
14 X_1 = 826;
15 Y_1 = 5;
16 X_2 = 628;
17 Y_2 = 3;
18
19 // Calculations
20 X = (X_1 - X_2);
21 Y = (Y_1 + Y_2);
22 printf("Difference = %d +/− %d\n", X, Y);
23 %doubt = Y/X*100;
24 printf("The percentage range of doubt = +/−%0.2f%%" ,
    %doubt);
25
26 // Result
27 // Difference = 198 +/− 8
28 // The percentage range of doubt = +/−4.04%
```

Scilab code Exa 1.6 To find difference with range of doubt

```
1 // To find difference with range of doubt
2 // Modern Electronic Instrumentation And Measurement
```

Techniques

```
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1–6 in Page 5
7
8
9 clear; clc; close;
10
11 // Given data
12 // let N_1 = X_1 +/− Y_1
13 //      N_2 = X_2 +/− Y_2
14 X_1 = 462;
15 Y_1 = 4;
16 X_2 = 437;
17 Y_2 = 4;
18
19 // Calculations
20 X = (X_1 - X_2);
21 Y = (Y_1 + Y_2);
22 printf("Difference = %d +/− %d\n", X, Y);
23 %doubt = Y/X*100;
24 printf("The percentage range of doubt = +/−%0.2f%%" ,
    %doubt);
25
26 // Result
27 // Difference = 25 +/− 8
28 // The percentage range of doubt = +/−32.00%
```

Scilab code Exa 1.7 To find Apparent and actual resistance

```
1 // To find Apparent and actual resistance
2 // Modern Electronic Instrumentation And Measurement
```

Techniques

```
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-7 in Page 6
7
8
9 clear; clc; close;
10
11 // Given data
12 I_T = 5*(10^-3); // Reading of the milliammeter in
ampere
13 V_T = 100; // Reading of the voltmeter in volt
14 sensitivity = 1000; // sensitivity of voltmeter in
ohm/volt
15 scale = 150; // scale of the voltmeter
16
17 // Calculations
18 R_T = V_T / I_T; // formula to calculate total
circuit resistance
19 printf("(a) The apparent circuit resistance
neglecting the resistance of milliammeter , R_T =
%d ohm\n",R_T);
20
21 R_V = sensitivity * scale; // calculating resistance
of voltmeter
22 R_X = (R_T * R_V)/(R_V - R_T); // effective circuit
resistance due to loading effect
23 printf("(b) The actual circuit resistance with the
loading effect of voltmeter , R_X = %0.2f ohm\n",
R_X);
24
25 percentage_error = (R_X - R_T)*100/ R_X;
26 // %error = (actual-apparent)/ actual
27 printf("(c) The percentage error due to loading
effect of voltmeter = %0.2f%%",percentage_error);
28
29 // result
```

```
30 // (a) The apparent circuit resistance neglecting  
    the resistance of milliammeter , R_T = 20000 ohm  
31 // (b) The actual circuit resistance with the  
    loading effect of voltmeter , R_X = 23076.92 ohm  
32 // (c) The percentage error due to loading effect  
    of voltmeter = 13.33%  
33  
34  
35 // The result shown in the textbook is printed  
    incorrectly and does not match with the correct  
    result
```

Scilab code Exa 1.8 To find Apparent and actual resistance

```
1 // To find Apparent and actual resistance  
2 // Modern Electronic Instrumentation And Measurement  
    Techniques  
3 // By Albert D. Helfrick , William D. Cooper  
4 // First Edition Second Impression , 2009  
5 // Dorling Kindersly Pvt. Ltd. India  
6 // Example 1–8 in Page 7  
7  
8  
9 clear; clc; close;  
10  
11 // Given data  
12 I_T = 800*(10^-3); // Reading of the milliammeter in  
    ampere  
13 V_T = 40; // Reading of the voltmeter in volt  
14 sensitivity = 1000; // sensitivity of voltmeter in  
    ohm/volt  
15 scale = 150; // scale of the voltmeter  
16
```

```

17 // Calculations
18 R_T = V_T / I_T; // formula to calculate total
                     circuit resistance
19 printf("(a) The apparent circuit resistance
           neglecting the resistance of milliammeter , R_T =
           %0.2f ohm\n",R_T);
20
21 R_V = sensitivity * scale; // calculating resistance
                               of voltmeter
22 R_X = (R_T * R_V)/(R_V - R_T); // effective circuit
                                   resistance due to loading effect
23 printf("(b) The actual circuit resistance with the
           loading effect of voltmeter , R_X = %0.2f ohm\n",
           R_X);
24
25 percentage_error = (R_X - R_T)*100/ R_X;
26 // %error = (actual-apparent)/ actual
27 printf("(c) The percentage error due to loading
           effect of voltmeter = %0.2f%%",percentage_error);
28
29 //result
30 // (a) The apparent circuit resistance neglecting
           the resistance of milliammeter , R_T = 50.00 ohm
31 // (b) The actual circuit resistance with the
           loading effect of voltmeter , R_X = 50.02 ohm
32 // (c) The percentage error due to loading effect
           of voltmeter = 0.03%
33
34
35 // The result shown in the textbook is printed
           incorrectly and does not match with the correct
           result

```

Scilab code Exa 1.9 To find Arithmatic mean and deviation from mean

```
1 // To find Arithmatic mean and deviation from mean
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-9 in Page 9
7
8
9 clear; clc; close;
10
11 // Given data
12 // Independent current measurements taken by six
   observers
13 I_1 = 12.8*(10^-3);
14 I_2 = 12.2*(10^-3);
15 I_3 = 12.5*(10^-3);
16 I_4 = 13.1*(10^-3);
17 I_5 = 12.9*(10^-3);
18 I_6 = 12.4*(10^-3);
19
20 // Calculations
21 arithmatic_mean = (I_1 +I_2 +I_3 +I_4 +I_5 +I_6)/6;
22 printf("(a) The arithmetic mean of the observations
   =%0.5f A",arithmatic_mean);
23
24 d_1 = I_1 - arithmatic_mean;
25 d_2 = I_2 - arithmatic_mean;
26 d_3 = I_3 - arithmatic_mean;
27 d_4 = I_4 - arithmatic_mean;
28 d_5 = I_5 - arithmatic_mean;
29 d_6 = I_6 - arithmatic_mean;
30
31 //deviation calculated using the formula d_n = x_n -
   arithmatic_mean
32 disp('(b) The deviations from the mean are: ' );
```

```

33 printf("d_1 = %0.5f A\n d_2 = %0.5f A\n d_3 = %0.5f
A\n d_4 = %0.5f A\n d_5 = %0.5f A\n d_6 = %0.5f A
\n",d_1, d_2, d_3, d_4, d_5, d_6);
34
35 // Result
36 // (a) The arithmetic mean of the observations
// =0.01265 A
37 // (b) The deviations from the mean are:
38 // d_1 = 0.00015 A
39 // d_2 = -0.00045 A
40 // d_3 = -0.00015 A
41 // d_4 = 0.00045 A
42 // d_5 = 0.00025 A
43 // d_6 = -0.00025 A

```

Scilab code Exa 1.10 To find Average deviation

```

1 // To find Average deviation
2 // Modern Electronic Instrumentation And Measurement
// Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1–10 in Page 10
7
8
9 clear; clc; close;
10
11 // Given data
12 // These are the data found out from the example_1–9
13 d_1 = 0.000150;
14 d_2 = -0.000450;
15 d_3 = -0.000150;

```

```

16 d_4 = 0.000450;
17 d_5 = 0.000250;
18 d_6 = -0.000250;
19
20 // Calculation
21 D = (abs(d_1) +abs(d_2) +abs(d_3) +abs(d_4) +abs(d_5)
     ) +abs(d_6))/6;
22 printf("The average deviation , D = %0.2e A",D);
23
24 //Result
25 // The average deviation , D = 2.83e-004 A

```

Scilab code Exa 1.11 To find Std deviation and Probable error

```

1 // To find Std deviation and Probable error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-11 in Page 14
7
8
9 clear; clc; close;
10
11 // Given data
12 // let the 10 resistance measurements in ohm be
   taken as elements of matrix
13 x = [101.2 101.7 101.3 101.0 101.5 101.3 101.2 101.4
      101.3 101.1];
14
15 // Calculations
16 arithmetic_mean = mean(x);

```

```

17 sigma = stdev(x);
18 probable_error = 0.6745 * sigma;
19 printf("(a) The arithmetic mean of the readings =
    %0.1f ohm\n", arithmetic_mean);
20 printf("(b) The standard deviation of the readings
    = %0.1f ohm\n", sigma);
21 printf("(c) The probable error of the readings = %0
    .4f ohm", probable_error);
22
23 //Result
24 // (a) The arithmetic mean of the readings = 101.3
      ohm
25 // (b) The standard deviation of the readings = 0.2
      ohm
26 // (c) The probable error of the readings = 0.1349
      ohm

```

Scilab code Exa 1.12 To find Limiting error

```

1 // To find Limiting error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-12 in Page 14
7
8
9 clear; clc; close;
10
11 // Given data
12 scale = 150;
13 percentage_accuracy = 1/100; // accuracy of 1% full

```

```

        scale reading
14 V = 83; //voltage measured by instrument = 83 volt
15
16 //Calculations
17 limiting_error = percentage_accuracy * scale;
18 printf("The magnitude of the limiting error = %0.1f
      V\n",limiting_error);
19
20 percentage_error = limiting_error/V * 100;
21 printf("The percentage limiting error = %0.2f
      percent",percentage_error);
22
23 //Result
24 // The magnitude of the limiting error = 1.5 V
25 // The percentage limiting error = 1.81 percent

```

Scilab code Exa 1.13 To find the maximum error

```

1 // To find the maximum error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-13 in Page 15
7
8
9 clear; clc; close;
10
11 // Given data
12 // For the given tolerence of 0.1%
13 // highest value of resistor is 1.001 times the
   nominal value

```

```

14 // lowest value of resistor is 0.999 times the
    nominal value
15
16 //Calculations
17 V_out_max = 1.001 * 1.001/ 0.999;
18 V_out_min = 0.999 * 0.999/ 1.003;
19 total_var = 0.1 * 3; // total variation of the
    resultant voltage is sum of tolerences
20 printf("The total variation of the resultant voltage
        = +/- %0.1f %%",total_var);
21
22 //Result
23 // The total variation of the resultant voltage =
        +/- 0.3 %

```

Scilab code Exa 1.14 To find limiting error

```

1 // To find limiting error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1–14 in Page 16
7
8
9 clear; clc; close;
10
11 // Given data
12 // let I = X_1 +/- Y_1
13 //      R = X_2 +/- Y_2
14 X_1 = 2.00;
15 Y_1 = 0.5;

```

```

16 X_2 = 100;
17 Y_2 = 0.2;
18
19 // Calculations
20 P_1 = ((1+0.005)^2)*(1+0.002);
21 printf("For the worst possible combination of the
           values of current and resistance ,\nThe highest
           power dissipation becomes,\n");
22 printf("P = %0.3f (I^2)*R Watts\n",P_1);
23 P_2 = ((1-0.005)^2)*(1-0.002);
24 printf("For the lowest power dissipation.\nP = %0.3f
           (I^2)*R Watts\n",P_2)
25 lim_error = 2 * Y_1 + Y_2;
26 printf("The limiting error = +/- %0.1f%%",lim_error)
      ;
27
28 // Result
29 // For the worst possible combination of the values
   // of current and resistance ,
30 // The highest power dissipation becomes ,
31 // P = 1.012 (I^2)*R Watts
32 // For the lowest power dissipation .
33 // P = 0.988 (I^2)*R Watts
34 // The limiting error = +/- 1.2%

```

Chapter 2

Systems of Units of Measurement

Scilab code Exa 2.1 To convert area in metre to feet

```
1 // To convert area in metre to feet
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-1 in Page 29
7
8 clear; clc; close;
9
10 // Given data
11 A_m = 5000; // area in metre^2 unit
12
13 // Calculation
14 A_ft = A_m * (1/0.3048)^2; // As 1ft = 0.3048m
15 printf("The area in feet = %d sq. ft", round(A_ft));
16
17 //Result
18 // The area in feet = 53820 sq. ft
```

Scilab code Exa 2.2 To convert flux density to different units

```
1 // To convert flux density to different units
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-2 in Page 29
7
8 clear; clc; close;
9
10 // Given data
11 B_cm = 20; // flux density in maxwell/sq.cm
12
13 // Calculations
14
15 B_in = B_cm *2.54^2; // converting to lines/sq.inch
16 printf("The flux density in lines/sq.in = %d lines/(
   in^2)",B_in);
17
18 //Result
19 // The flux density in lines/sq.in = 129 lines/(in
   ^2)
```

Scilab code Exa 2.3 To convert velocity to a different unit

```

1 // To convert velocity to a different unit
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-3 in Page 29
7
8 clear; clc; close;
9
10 // Given data
11 c_s = 2.997925 * 10^8; // velocity in m/s
12
13 // Calculations
14 c_hr = 2.997925 *10^8* 1/10^3* 3.6*10^3; // velocity
   in km/hr
15 printf("The velocity of light in km/hr = %0.3e km/hr
   ",c_hr);
16
17 // Result
18 // The velocity of light in km/hr = 1.079e+009 km/hr

```

Scilab code Exa 2.4 To convert density to a different unit

```

1 // To convert density to a different unit
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-4 in Page 29
7
8 clear; clc; close;

```

```

9
10 // Given data
11 Density_ft = 62.5;
12
13 // Calculations
14 Density_in = 62.5 * (1/12)^3;
15 Density_cm = Density_in * 453.6 * (1/2.54)^3;
16 printf("(a) The density of water in lb/cubic inch = %f lb/(in^3).\n", Density_in);
17 printf("(b) The density of water in g/cubic cm = %f g/(cm^3).", Density_cm);
18
19 // Result
20 // (a) The density of water in lb/cubic inch = 0.036169 lb/(in^3).
21 // (b) The density of water in g/cubic cm = 1.001171 g/(cm^3).

```

Scilab code Exa 2.5 To convert speed limit to a different unit

```

1 // To convert speed limit to a different unit
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-5 in Page 30
7
8 clear; clc; close;
9
10 // Given data
11 speed_km = 60; // speed limit in km/hr
12

```

```
13 // Calculations
14 speed_m = 60 *10^3 *10^2 *(1/2.54) *(1/12)*(1/5280);
15 speed_ft = 37.3 *5280 *(1/(3.6*10^3));
16
17 printf("(a) The speed limit in m/hr = %0.1f mi/hr\n",
18      , speed_m);
19
20 // Result
21 // (a) The speed limit in m/hr = 37.3 mi/hr
22 // (b) The speed limit in ft/s = 54.7 ft/s
23
24
25 //The answer given in textbook is printed
// incorrectly and does not match with calculated
// answer
```

Chapter 4

Electromechanical Indicating Instruments

Scilab code Exa 4.1 To find Shunt resistance required

```
1 // To find Shunt resistance required
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-1 in Page 56
7
8
9 clear; clc; close;
10
11 // Given data
12 I_m = 1*(10^-3); //Full scale deflection of the
   movement in ampere
13 R_m = 100; //Internal resistance of the movement(the
   coil) in ohm
14 I = 100*(10^-3); //Full scale of the ammeter
   including the shunt in Ampere
15
```

```

16 // Calculations
17 I_s = I - I_m; // calculating current through shunt
18 R_s = I_m * R_m / I_s; //calculating shunt to be
   added
19 printf("The value of the shunt resistance required ,
   R_s = %0.2f ohm",R_s);
20
21 // Result
22 // The value of the shunt resistance required , R_s =
   1.01 ohm

```

Scilab code Exa 4.2 To design Ayrton shunt

```

1 // To design Ayrton shunt
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-2 in Page 57
7
8
9 clear; clc; close;
10
11 // Given data
12 I_1 = 1; //Full scale currents of the ammeter in amp
13 I_2 = 5;
14 I_3 = 10;
15 R_m = 50; //Internal resistance of the movement(the
   coil) in ohm
16 I_m = 1*(10^-3); //Full scale deflection of the
   movement in ampere
17

```

```

18 // Calculations
19 // On the 1-A range:
20 I_s1 = I_1 - I_m; // calculating current through
    shunt
21 // Using the eq.  $R_s = I_m * R_m / I_s$ 
22 //  $R_a + R_b + R_c = I_m * R_m / I_s$ ; // As  $(R_a + R_b + R_c)$  are parallel with  $R_m$ 
23
24 // On the 5-A range
25 I_s2 = I_2 - I_m;
26 //  $R_a + R_b = I_m * (R_c + R_m) / I_s$ ; // As  $(R_a + R_b)$  in parallel with  $(R_c + R_m)$ 
27
28 // On the 10-A range
29 I_s3 = I_3 - I_m;
30 //  $R_a = I_m * (R_b + R_c + R_m) / I_s$ ; // As  $R_a$  is parallel with  $(R_b + R_c + R_m)$ 
31
32
33 // Solving the 3 simultaneous linear equations
34 function y = rr(R);
35 y(1)= R(1) + R(2) + R(3) - (I_m * R_m / I_s1);
36 y(2)= R(1) + R(2) - (I_m * (R(3) + R_m) / I_s2);
37 y(3)= R(1) - (I_m * (R(2) + R(3) + R_m) / I_s3);
38 endfunction
39
40 answer = fsolve([0.1;0.1;0.1],rr);
41 R_a = answer([1]);
42 R_b = answer([2]);
43 R_c = answer([3]);
44
45 disp('The different resistors used for the ayrton
    shunt for different ranges are:');
46 printf("R_a = %f ohm\n",R_a);
47 printf("R_b = %f ohm\n",R_b);
48 printf("R_c = %f ohm",R_c);

```

```
49
50 //Result
51 // The different resistors used for the ayrton shunt
      for different ranges are:
52 // R_a = 0.005005 ohm
53 // R_b = 0.005005 ohm
54 // R_c = 0.040040 ohm
```

Scilab code Exa 4.3 To design multirange dc voltmeter

```
1 // To design multirange dc voltmeter
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-3 in Page 60
7
8
9 clear; clc; close;
10
11 // Given data
12 R_m = 100; // internal resistance of movement
13 I_fsd = 1*(10^-3); //full-scale current in Amp
14 V_1 = 10; //different ranges in volt
15 V_2 = 50;
16 V_3 = 250;
17 V_4 = 500;
18
19 // Calculations
20
21 //For the 10-V range
22 R_T = V_1 / I_fsd;
```

```

23 R_4 = R_T - R_m;
24 printf("The value of the resistance R_4 = %d ohm\n",
25 R_4);
26 //For the 50-V range
27 R_T = V_2 / I_fsd;
28 R_3 = R_T - (R_4 + R_m);
29 printf("The value of the resistance R_3 = %dk ohm\n"
30 ,R_3/1000);
31 //For the 250-V range
32 R_T = V_3 / I_fsd;
33 R_2 = R_T - (R_3 + R_4 + R_m);
34 printf("The value of the resistance R_2 = %dk ohm\n"
35 ,R_2/1000);
36 //For the 500-V range
37 R_T = V_4 / I_fsd;
38 R_1 = R_T - (R_2 + R_3 + R_4 + R_m);
39 printf("The value of the resistance R_1 = %dk ohm",
40 R_1/1000);
41 //Result
42 // The value of the resistance R_4 = 9900 ohm
43 // The value of the resistance R_3 = 40k ohm
44 // The value of the resistance R_2 = 200k ohm
45 // The value of the resistance R_1 = 250k ohm

```

Scilab code Exa 4.4 To design multirange dc voltmeter

```

1 // To design multirange dc voltmeter
2 // Modern Electronic Instrumentation And Measurement
   Techniques

```

```

3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-4 in Page 62
7
8
9 clear; clc; close;
10
11 // Given data
12 // This is a repitition of example_4-3 with
   sensitivity method
13 R_m = 100; // internal resistance of movement
14 I_fsd = 1*(10^-3); //full-scale current in Amp
15 V_1 = 10; //different ranges in volt
16 V_2 = 50;
17 V_3 = 250;
18 V_4 = 500;
19
20 //Calculations
21 S = 1/ I_fsd; // sensitivity in ohm/V
22 R_4 = (S * V_1)-R_m;
23 R_3 = (S * V_2)-(R_4 +R_m);
24 R_2 = (S * V_3)-(R_3 +R_4 +R_m);
25 R_1 = (S * V_4)-(R_2 +R_3 +R_4 +R_m);
26
27 printf("The value of the resistance R_4 = (%dohm/V *
   %dV)- %dohm = %d ohm\n",S,V_1,R_m,R_4);
28 printf("The value of the resistance R_3 = (%dohm/V *
   %dV)- %dohm = %dK ohm\n",S,V_2,(R_4+R_m),R_3
   /1000);
29 printf("The value of the resistance R_2 = (%dohm/V *
   %dV)- %dohm = %dK ohm\n",S,V_3,(R_3 +R_4 +R_m),
   R_2/1000);
30 printf("The value of the resistance R_1 = (%dohm/V *
   %dV)- %dohm = %dK ohm",S,V_4,(R_2 +R_3 +R_4 +R_m
   ),R_1/1000);
31
32 // Result

```

```
33 // The value of the resistance R_4 = (1000ohm/V *10V  
34 // )- 100ohm = 9900 ohm  
35 // The value of the resistance R_3 = (1000ohm/V *50V  
36 // )- 10000ohm = 40K ohm  
37 // The value of the resistance R_2 = (1000ohm/V *250  
38 // V)- 50000ohm = 200K ohm  
39 // The value of the resistance R_1 = (1000ohm/V *500  
40 // V)- 250000ohm = 250K ohm
```

Scilab code Exa 4.5 To find voltage reading and Error

```
1 // To find voltage reading and Error  
2 // Modern Electronic Instrumentation And Measurement  
// Techniques  
3 // By Albert D. Helfrick , William D. Cooper  
4 // First Edition Second Impression , 2009  
5 // Dorling Kindersly Pvt. Ltd. India  
6 // Example 4-5 in Page 62  
7  
8 clear; clc; close;  
9  
10 // Given data  
11 // resistances in series  
12 R_1 = 100 * 10^3;  
13 R_2 = 50 *10^3;  
14 // sensitivity of two voltmeters  
15 S_1 = 1000;  
16 S_2 = 20000;  
17 V = 50; // range of the voltmeters  
18 E = 150; // voltage of battery in volt  
19  
20 // Calculations  
21 //By voltage divider rule
```

```

22 V_true = R_2 /(R_1+R_2)*E;
23 printf("The true voltage across resistor R_2 = %d V\n",
24 //Reading of the first voltmeter
26 R_T1 = S_1 * V; // resistance of voltmeter =
27 sensitivity * range
27 R_p =(R_2 *R_T1)/(R_2 +R_T1)// effective parallel
resistance
28 R_c1 = R_1+R_p // The total circuit resistance
29 V_1 = 25*10^3/R_c1 *E;
30 printf("The reading of the first voltmeter = %d V\n",
V_1);
31 //Reading of the second voltmeter
33 R_T2 = S_2 * V; // resistance of voltmeter =
sensitivity * range
34 R_p =(R_2 *R_T2)/(R_2 +R_T2)
35 R_c2 = R_1 +R_p // The total circuit resistance
36 V_2 = 47.6*10^3/R_c2 *E;
37 printf("The reading of the second voltmeter = %0.2f
V\n",V_2);
38
39 %error_1 = (V_true - V_1)/V_true *100;
40 printf("The error in the reading due to voltmeter 1
=%d%%\n",%error_1);
41 %error_2 = (V_true - V_2)/V_true *100;
42 printf("The error in the reading due to voltmeter 2
=%0.2f%%",%error_2);
43
44 //Results
45 // The true voltage across resistor R_2 = 50 V
46 // The reading of the first voltmeter = 30 V
47 // The reading of the second voltmeter = 48.37 V
48 // The error in the reading due to voltmeter 1 =40%
49 // The error in the reading due to voltmeter 2 =3.26
%
50

```

```
51 //The answers are varying as approximation is not  
done
```

Scilab code Exa 4.6 To find the value of unknown resistor

```
1 // To find the value of unknown resistor  
2 // Modern Electronic Instrumentation And Measurement  
Techniques  
3 // By Albert D. Helfrick , William D. Cooper  
4 // First Edition Second Impression , 2009  
5 // Dorling Kindersly Pvt. Ltd. India  
6 // Example 4–6 in Page 64  
7  
8  
9 clear; clc; close;  
10  
11 // Given data  
12 S = 100; //Sensitivity of the voltmeter  
13 // Three ranges of the voltmeter  
14 V_1 = 50;  
15 V_2 = 150;  
16 V_3 = 300;  
17 V_p = 4.65; //Reading of the meter on its 50-V scale  
18 R_s = 100*10^3;  
19 E = 100; //emf applied in volt  
20 //Calculations  
21 R_V = S * V_1;  
22 R_p = ceil(V_p *R_s/ (E -V_p)); //R_p is the  
parallel resistance of R_x and R_v  
23 R_x = R_p *R_V/ (R_V -R_p);  
24 printf("The value of the unknown resistance R_x = %0  
.1e ohm", ceil(R_x));  
25
```

```
26 // Result
27 // The value of the unknown resistance R_x = 2.0 e
+005 ohm
```

Scilab code Exa 4.7 To find the scale error

```
1 // To find the scale error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-7 in Page 67
7
8
9 clear; clc; close;
10
11 // Given data
12 R_h = 2000; //The desired scale marking for the half
   scale deflection
13 E = 3; //The internal battery voltage in volt
14 I_fsd = 1 *(10^-3); //Current for full scale
   deflection in ampere
15 R_m = 50; //resistance of the basic movement in ohm
16
17 // Calculations
18 I_t = E / R_h; //Total battery current at FSD
19 I_2 = I_t - I_fsd; // Current through zero-adjust
   resistor R_2
20 R_2 = I_fsd * R_m/I_2;
21 R_p = R_2*R_m/(R_2 + R_m);
22 R_1 = R_h - R_p;
23 printf("(a) The value of R_1 and R_2 is")
```

```

24 printf("The value of zero-adjust resistor R2 =%0.1f
          ohm\n",R_2);
25 printf("The value of current-limiting resistor R1 =
          %0.1f ohm\n",R_1);
26
27 //At a 10% drop in battery voltage
28 E = 3- 0.3;
29 I_t = E / R_h; //Total battery current in A
30 I_2 = I_t - I_fsd; //Shunt current in A
31 R_2 = ceil(I_fsd * R_m/I_2);
32 R_p = R_2 *R_m/(R_2+R_m);
33 R_h = R_1 + R_p;
34 %error = (2000-2003.7)/2003.7*100;
35 printf("\n(b) The maximum value of R2 to compensate
          the drop in battery voltage = %d ohm\n",R_2);
36 printf("The true value of the half-scale mark on the
          meter is = %0.3f ohm\n",R_h);
37 printf("\n(c) The percentage error = %0.3f%%\n",
          %error);
38 disp('The negative sign indicates that the meter
          reading is low');

39
40 //Result
41 // (a) The value of R_1 and R_2 isThe value of zero
          -adjust resistor R2 =100.0 ohm
42 // The value of current-limiting resistor R1 =1966.7
          ohm
43
44 // (b) The maximum value of R2 to compensate the
          drop in battery voltage = 143 ohm
45 // The true value of the half-scale mark on the
          meter is = 2003.713 ohm
46
47 // (c) The percentage error = -0.185%
48
49 // The negative sign indicates that the meter
          reading is low

```

Scilab code Exa 4.8 To find shunt and current limiting resistor

```
1 // To find shunt and current limiting resistor
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-8 in Page 70
7
8
9 clear; clc; close;
10
11 // Given data
12 I_fsd = 10*(10^-3); // current for full scale
   deflection in ampere
13 R_m = 5; //internal resistance of the d' Arsonval
   movement in ohm
14 E = 3; //Battery voltage in volt
15 R_h = 0.5; //The desired scale marking for the half
   scale deflection in ohm
16
17 // Calculations
18 I_m = 0.5 * I_fsd; // Current for half scale
   deflection of movement
19 E_m = I_m * R_m; //The voltage across movement
20 I_x = E_m / R_h; // Voltage across unknown resistor
   R_x
21 I_sh = I_x - I_m; //As I_x = I_sh + I_m
22 R_sh = E_m / I_sh;
23 I_t = I_m + I_sh + I_x; //The total battery current
24 R_1 = (E - E_m)/I_t;
```

```

25 printf("(a) The value of the shunt resistor , R_sh =
26 %0.3f ohm\n",R_sh);
27 printf("(b) The value of the current limiting
28 resistor , R_1 = %0.2f ohm",R_1);
29 //Result
30 // (a) The value of the shunt resistor , R_sh =
31 // 0.556 ohm
32 // (b) The value of the current limiting resistor ,
33 R_1 = 29.75 ohm

```

Scilab code Exa 4.9 To find multiplier resistor

```

1 // To find multiplier resistor
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-9 in Page 79
7
8
9 clear; clc; close;
10
11 // Given data
12 R_m = 50; //Internal resistance of the movement in
   ohm
13 I_fsd = 1 *(10^-3); //current for full scale
   deflection in ampere
14 E_rms = 10; // AC voltage applied to input terminals
   in volt
15
16 // Calculation

```

```

17 disp('Assuming zero forward resistance and infinite
       reverse resistance');
18 E_dc = round(2 *sqrt(2)*E_rms/%pi);
19 R_t = E_dc / I_fsd; //Total circuit resistance
20 R_s = R_t - R_m; //Calculating multiplier resistor
21 printf("The value of the multiplier resistor , R_s =
       %d ohm",R_s);
22
23 //Result
24 // Assuming zero forward resistance and infinite
       reverse resistance
25 // The value of the multiplier resistor , R_s = 8950
       ohm

```

Scilab code Exa 4.10 To find voltmeter sensitivity on AC range

```

1 // To find voltmeter sensitivity on AC range
2 // Modern Electronic Instrumentation And Measurement
      Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-10 in Page 81
7
8
9 clear; clc; close;
10
11 // Given data
12 R_m = 100; //Internal resistance of the movement in
      ohm
13 R_sh = 100;
14 I_fsd = 1*(10^-3); //current for full scale
      deflection

```

```

15 R_D1 = 400;
16 R_D2 = 400;
17 E_rms = 10; //AC range of the voltmeter
18
19 //Calculations
20 disp('Assuming infinite reverse resistance');
21 I_t = 2 *I_fsd;
22 E_dc = 0.45 * E_rms;
23 R_t = E_dc / I_t;
24 R_p = R_m *R_sh/(R_m+R_sh);
25 R_s = R_t - (R_D1 + R_p);
26 printf("(a) The value of the multiplier resistor
           required , R_s = %d ohm\n",R_s);
27 S = R_t / E_rms;
28 printf("(b) The sensitivity of the voltmeter on ac
           range , S = %d ohm/V",S);
29
30 //Result
31 // Assuming infinite reverse resistance
32 // (a) The value of the multiplier resistor
           required , R_s = 1800 ohm
33 // (b) The sensitivity of the voltmeter on ac range
           , S = 225 ohm/V

```

Chapter 5

Bridge Measurements

Scilab code Exa 5.1 To find deflection caused by the given unbalance

```
1 // To find deflection caused by the given unbalance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-1 in Page 101
7
8
9 clear; clc; close;
10
11 // Given data
12 // Resistances of the 4 arms in ohm
13 R_1 = 1000;
14 R_2 = 100;
15 R_3 = 200;
16 R_4 = 2005;
17
18 E = 5; // battery EMF in volt
19 S_I = 10*(10^-3)/(10^-6); //Current sensitivity in m
   /A
```

```

20 R_g = 100; //Internal resistance of galvanometer in
               ohm
21
22 //Calculations
23
24 //Calculations are made wrt fig 5-3 in page 103
25 //Bridge balance occurs if arm BC has a resistance
      of 2000 ohm. The diagram shows arm BC has as a
      resistance of 2005 ohm
26
27 //To calculate the current in the galvanometer , the
      ckt is thevenised wrt terminals B and D.
28 //The potential from B to D, with the galvanometer
      removed is the Thevenin voltage
29
30 // E_TH = E_AD - E_AB
31
32 E_TH = E * ((R_2/(R_2+R_3)) - (R_1/(R_1+R_4)));
33 R_TH = ((R_2 * R_3/(R_2+R_3)) + (R_1 * R_4/(R_1+R_4
      )) );
34
35 //When the galvanometer is now connected to the
      output terminals , The current through the
      galvanometer is
36
37 I_g = E_TH /(R_TH +R_g);
38 d = I_g * S_I;
39 printf("The deflection of the galvanometer = %0.2f
      mm" ,(d*1000));
40
41 //Result
42 // The deflection of the galvanometer = 33.26 mm

```

Scilab code Exa 5.2 To check the capability of detecting unbalance

```
1 // To check the capability of detecting unbalance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-2 in Page 102
7
8
9 clear; clc; close;
10
11 // Given data
12 // Resistances of the 4 arms in ohm
13 R_1 = 1000;
14 R_2 = 100;
15 R_3 = 200;
16 R_4 = 2005;
17
18 E = 5; // battery EMF in volt
19 S_I = 1*(10^-3)/(10^-6); //Current sensitivity in m/
   A
20 R_g = 500; //Internal resistance of galvanometer in
   ohm
21
22
23
24
25 //Calculations
26
27 //Calculations are made wrt fig 5-3 in page 103
28 //Bridge balance occurs if arm BC has a resistance
   of 2000 ohm. The diagram shows arm BC has as a
   resistance of 2005 ohm
29
30 //To calculate the current in the galvanometer , the
   ckt is thevenised wrt terminals B and D.
```

```

31 //The potential from B to D, with the galvanometer
   removed is the Thevenin voltage
32
33 // E_TH = E_AD - E_AB
34
35 E_TH = E * ((R_2/(R_2+R_3)) - (R_1/(R_1+R_4)));
36 R_TH = ((R_2 * R_3/(R_2+R_3)) + (R_1 * R_4/(R_1+R_4
   ))));
37
38 //When the galvanometer is now connected to the
   output terminals , The current through the
   galvanometer is
39
40 I_g = E_TH /(R_TH +R_g);
41 d = I_g * S_I;
42 printf("The deflection of the galvanometer = %0.3f
   mm",d*1000);
43 disp('Given that galvanometer is capable of
   detecting a deflection of 1mm');
44 disp('Hence looking at the result ,it can be seen
   that this galvanometer produces a deflection that
   can be easily observed');
45
46 //Result
47 // The deflection of the galvanometer = 2.247 mm
48 // Given that galvanometer is capable of detecting a
   deflection of 1mm
49
50 // Hence looking at the result ,it can be seen that
   this galvanometer produces a deflection that can
   be easily observed

```

Scilab code Exa 5.3 To find the unknown impedance

```

1 // To find the unknown impedance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-3 in Page 111
7
8
9 clear; clc; close;
10
11 // Given data
12 // The given polar forms in textbook is represented
   in rect form
13 Z_1 = 17.36482 +%i *98.48078;
14 Z_2 = 250;
15 Z_3 = 346.4102 +%i *200;
16
17 // Calculations
18 //The first condition for bridge balance is Z_1*Z_4
   = Z_2*Z_3
19 mod_Z_4 = (abs(Z_2) *abs(Z_3)/abs(Z_1));
20
21 //The second condition for bridge balance requires
   that sum of the phase angles of opposite arms be
   equal
22 theta_Z_4 = (atan(imag(Z_2),real(Z_2)) +atan(imag(
   Z_3),real(Z_3)) -atan(imag(Z_1),real(Z_1)))*180/
   %pi;
23
24 printf("The impedance of the unknown arm = %d ohm / -
   %d deg\n",mod_Z_4,theta_Z_4);
25 printf("Here the magnitude of impedance is 1000 and
   phase angle is 50 in degrees\n");
26 printf("The above value indicates that we are
   dealing with a capacitive element , possibly
   consisting of a series combination of a resistor
   and capacitance");

```

```
27
28 //Result
29 // The impedance of the unknown arm = 1000 ohm / -50 deg
30 // Here the magnitude of impedance is 1000 and phase angle is 50 in degrees
31 // The above value indicates that we are dealing with a capacitive element, possibly consisting of a series combination of a resistor and capacitance
```

Scilab code Exa 5.4 To find the unknown impedance

```
1 // To find the unknown impedance
2 // Modern Electronic Instrumentation And Measurement Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-4 in Page 112
7
8
9 clear; clc; close;
10
11 // Given data
12 // The notations are wrt to the figure 5-10 in page 109
13
14 //Arm AB
15 R_1 = 450;
16 //Arm BC
17 R_2 = 300;
18 C = 0.265 *(10^-6);
```

```

19 //Arm DA
20 R_3 = 200;
21 L = 15.9*(10^-3);
22 f = 1000;
23
24 // Calculations
25 w = 2*pi*f;
26 Z_1 = 450;
27 Z_2 = R_2 - %i *floor(1/(w*C));
28 Z_3 = R_3 + %i*ceil(w*L);
29
30 Z_4 = Z_1*Z_3/Z_2;
31 printf("The impedance of the unknown arm = %di ohm\n
", imag(Z_4));
32 printf("The result indicates that Z_4 is a pure
    inductance with an inductive reactance of 150 ohm
    at a frequency of 1 khz.\n")
33
34 L_ans = imag(Z_4)/w;
35 printf("The inductance present in the arm CD = %0.1
    fm H", L_ans*1000);
36
37 // Result
38 // The impedance of the unknown arm = 150i ohm
39 // The result indicates that Z_4 is a pure
    inductance with an inductive reactance of 150 ohm
    at a frequency of 1 khz.
40 // The inductance present in the arm CD = 23.9m H

```

Scilab code Exa 5.5 To balance the unbalanced bridge

```

1 // To balance the unbalanced bridge
2 // Modern Electronic Instrumentation And Measurement

```

Techniques

```
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-5 in Page 119
7
8
9 clear; clc; close;
10
11 // Given data
12 Z_1 = -1000*i;
13 Z_2 = 500;
14 Z_3 = 1000;
15 Z_4 = 100+500*i;
16
17 // The balance is not possible with this condition
   as theta_1+theta_4 will be slightly negative than
   theta_2+theta3
18 // Balance can be achieved by 2 methods:
19 disp('First option is to modify Z_1 so that its
   phase angle is decreased to less than 90deg by
   placing a resistor in parallel with the capacitor
   .')
20 // The resistance R_1 can be determined by the
   standard approach
21
22 // Calculations
23 Y_1 = Z_4/(Z_2*Z_3);
24 //Also ,
25 // Y_1 = (1/R) + %i/1000;
26 // equating both the equations and solving for R_1
27
28 R_1 = 1/(Y_1-(%i/1000));
29 printf("The value of the resistor R_1 in parallel
   with capacitor = %d ohm\n",R_1);
30
31 // It should be noted that the addition of R_1
   upsets the first balance condition as the
```

```

        magnitude of Z_1 is changed
32 // Hence the variable R_3 should be adjusted to
   compensate this effect
33
34 disp('The second option is to modify the phase angle
       of arm 2 or arm 3 by adding series capacitor');
35 Z_3_1 = Z_1 *Z_4/Z_2;
36 // substituting for the component values and solving
   for X_C yeilds
37
38 X_C = abs(1000- Z_3_1)/-%i;
39 printf("The value of the reactance of the capacitor
       used , X_C = %d ohm", imag(X_C));
40
41
42 //In this case the magnitude of the Z_3 is increased
   so that the first balance condition is changed
43 //A small adjustment of R_3 is necessary to restore
   balance
44
45 //Result
46 // First option is to modify Z_1 so that its phase
   angle is decreased to less than 90deg by placing
   a resistor in parallel with the capacitor.
47 // The value of the resistor R_1 in parallel with
   capacitor = 5000 ohm
48
49 // The second option is to modify the phase angle of
   arm 2 or arm 3 by adding series capacitor
50 // The value of the reactance of the capacitor used ,
   X_C = 200 ohm

```

Chapter 6

Electronic Instruments for Measuring Basic Parameters

Scilab code Exa 6.1 To find the form factor and error

```
1 // To find the form factor and error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-1 in Page 131
7
8
9 clear; clc; close;
10
11 // Given data
12 //let
13 E_m = 10; //Let the peak amplitude of the square
   wave be 10V
14 T = 1; //Let the time period of the square wave be 1
   s
15
16 function y= f(t),y=(E_m)^2 ,endfunction
```

```

17 E_rms = sqrt(1/T * intg(0,T,f));
18 printf("(a) The rms value of the square wave = %d V
19 \n",E_rms);
20 function x = ff(t),x =(E_m) ,endfunction
21 E_av = (2/T * intg(0,T/2,ff));
22 printf(" The average value of the square wave = %d
23 V\n",E_av);
24 k = E_rms/E_av;
25 printf(" The form factor of the square wave =%d\n",
26 k);
27 k_sine = 1.11;
28 k_square = 1;
29 %error = (k_sine - k_square)/k_square*100;
30 printf("(b) The percentage error in meter
31 indication = %d %%",%error);
32 //Result
33 // (a) The rms value of the square wave = 10 V
34 // The average value of the square wave = 10 V
35 // The form factor of the square wave =1
36 // (b) The percentage error in meter indication =
37 11 %

```

Scilab code Exa 6.2 To find the form factor and error

```

1 // To find the form factor and error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009

```

```

5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-2 in Page 132
7
8
9 clear; clc; close;
10
11 // Given data
12 E_m = 150; //Let the peak amplitude of the sawtooth
               wave be 150V
13 T = 3; //Let the time period of the sawtooth wave be
           3s
14 // e = 50*t; As seen from the figure 6-7b in page
           131
15
16 // Calculations
17 function y= f(t),y=(50*t)^2 ,endfunction
18 E_rms = sqrt(1/T * intg(0,T,f));
19 printf("(a) The rms value of the sawtooth wave = %d
           V \n",E_rms);
20
21 function x = ff(t),x =(50*t) ,endfunction
22 E_av = (1/T * intg(0,T,ff));
23 printf("The average value of the sawtooth wave = %d
           V\n",E_av);
24
25 k_st = E_rms/E_av;
26 printf("The form factor of the sawtooth wave =%0.3f\
           \n",k_st);
27
28 k_sine = 1.11;
29 r = k_sine/k_st;
30 printf("(b) The ratio of the two form factors = %0
           .3f\n",r);
31
32 printf("The meter indication is low by a factor of
           %0.3f\n",r);
33 %error = (r - 1)/1*100;
34 printf("The percentage error in meter indication =

```

```

    %0.1f %% ,%error);
35
36 // Result
37 // (a) The rms value of the sawtooth wave = 86 V
38 // The average value of the sawtooth wave = 75 V
39 // The form factor of the sawtooth wave =1.155
40 // (b) The ratio of the two form factors = 0.961
41 // The meter indication is low by a factor of 0.961
42 // The percentage error in meter indication = -3.9 %

```

Scilab code Exa 6.3 To find the maximum time

```

1 // To find the maximum time
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-3 in Page 144
7
8
9 clear; clc; close;
10
11 // Given data
12 R = 100*(10^3); // Value of resistance in ohm
13 C = 0.1*(10^-6); // The value of integrating
   capacitor in F
14 V_ref = 2; // The reference voltage in V
15 V_out = 10; // The maximum limit of the output in V
16
17 // Calculations
18 T = R*C;
19 printf("The integrator time constant = %0.3f s\n",T)

```

```

;
20 V_s = V_ref/T; //Unit is V/s
21 V = 1/V_s;
22 printf("Therefore the integrator output = %0.3f s/V"
, V)
23 disp('Therefore to integrate 10V');
24 T_max = V*V_out; //The max time the ref voltage can
be integrated
25 printf("The time required = %0.4f s", T_max);
26
27 //Result
28 // The integrator time constant = 0.010 s
29 // Therefore the integrator output = 0.005 s/V
30 // Therefore to integrate 10V
31 // The time required = 0.0500 s

```

Scilab code Exa 6.4 To find the distributed capacitance

```

1 // To find the distributed capacitance
2 // Modern Electronic Instrumentation And Measurement
Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-4 in Page 162
7
8
9 clear; clc; close;
10
11 // Given data
12 // Frequency measurements in Hz
13 f_1 = 2*10^6;
14 f_2 = 4*10^6;

```

```

15 // Value of tuning capacitor in F
16 C_1 = 460*10^-12;
17 C_2 = 100*10^-12;
18
19 // Calculations
20 C_d = (C_1 - (4*C_2))/3;
21 printf("C_d = %0.0E F\n", C_d);
22 printf(" i.e The value of the distributed capacitance
23 = %d pF", (C_d*10^12));
24
25 // Result
26 // C_d = 2E-011 F
27 // i.e The value of the distributed capacitance = 20
28 pF

```

Scilab code Exa 6.5 To find the self capacitance

```

1 // To find the self capacitance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-5 in Page 162
7
8
9 clear; clc; close;
10
11 // Given data
12 // Values of frequencies in Hz
13 f_1 = 2*10^6;
14 f_2 = 5*10^6;
15 // Values of the tuning capacitors in F

```

```

16 C_1 = 450*10^-12;
17 C_2 = 60*10^-12;
18
19 // Calculations
20
21 // Using the equation f = 1/(2*pi*sqrt(L*(C_2+C_d)))
22 ;
23 // Since f_2 = 2.5*f_1
24 // Equating & reducing the equations
25 // 1/(C_2 +C_d) = 6.25/(C_1 +C_d)
26
27 C_d = (C_1 -6.25*C_2)/5.25
28 printf("C_d = %0.2E F\n",C_d);
29 printf("i.e The value of the distributed capacitance
30 = %0.1f pF", (C_d*10^12));
31
32 // Result
33 // C_d = 1.43E-011 F
34 // i.e The value of the distributed capacitance =
35 14.3 pF

```

Scilab code Exa 6.6 To find percentage error

```

1 // To find percentage error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-6 in Page 163
7
8
9 clear; clc; close;

```

```

10
11 // Given data
12 R = 10; //Resistance of the coil in ohm
13 f = 1*10^6; //The oscillator frequency in Hz
14 C = 65*10^-12; //The value of resonating capacitor
15 in F
16 R_i = 0.02; //The value of the insertion resistor in
17 ohm
18
19 //Calculations
20 w = 2*%pi*f;
21 Q_e = 1/(w*C*R);
22 printf("The effective Q of the coil = %0.1f\n",Q_e);
23 Q_i = 1/(w*C*(R+R_i));
24 printf("The indicated Q of the coil = %0.1f\n",Q_i);
25 %error = (Q_e - Q_i)/Q_e*100;
26 printf("The percentage error is = %0.1f %%",%error);
27
28 // Result
29 // The effective Q of the coil = 244.9
30 // The indicated Q of the coil = 244.4
31 // The percentage error is = 0.2 %

```

Scilab code Exa 6.7 To find percentage error

```

1 // To find percentage error
2 // Modern Electronic Instrumentation And Measurement
3 // Techniques
4 // By Albert D. Helfrick , William D. Cooper
5 // First Edition Second Impression , 2009
6 // Dorling Kindersly Pvt. Ltd. India
7 // Example 6-7 in Page 163

```

```

8
9 clear; clc; close;
10
11 // Given data
12 R = 0.1; //Resistance of the coil in ohm
13 f = 40*10^6; //The frequency at resonance in Hz
14 C = 135*10^-12; //The value of tuning capacitor in F
15 R_i = 0.02; //The value of the insertion resistor in
16 ohm
17
18 // Calculations
19 w = 2*pi*f;
20 Q_e = 1/(w*C*R);
21 printf("The effective Q of the coil = %d\n", ceil(Q_e
));
22 Q_i = 1/(w*C*(R+R_i));
23 printf("The indicated Q of the coil = %d\n", ceil(Q_i
));
24 %error = (Q_e - Q_i)/Q_e*100;
25 printf("The percentage error is = %d %%", ceil(%error
));
26
27 // Result
28 // The effective Q of the coil = 295
29 // The indicated Q of the coil = 246
30 // The percentage error is = 17 %

```

Chapter 7

Oscilloscopes

Scilab code Exa 7.1 To find minimum distance

```
1 // To find minimum distance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 7-1 in Page 184
7
8
9 clear; clc; close;
10
11 // Given data
12 D = 4*10^-2; //Deflection on the screen in m
13 G = 100*100; // Deflection factor in V/m
14 E_a = 2000; //Accelarating potential in V
15
16 //Calculations
17 // wkt. L = 2*d*E_a/(G*I_d)
18
19 //Also L/D = I_d / d
20 //Therefore
```

```
21
22 L = sqrt(2*D*E_a/G);
23 printf("The distance from the deflection plates to
24      the oscilloscope tube screen = %0.3f m",L);
25 //Result
26 // The distance from the deflection plates to the
27 // oscilloscope tube screen = 0.126 m
```

Chapter 9

Signal Analysis

Scilab code Exa 9.1 To find dynamic range of spectrum analyser

```
1 // To find dynamic range of spectrum analyser
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 9-1 in Page 277
7
8
9 clear; clc; close;
10
11 // Given data
12 I_p = +25; //Third order intercept point in dBm
13 MDS = -85; //noise level in dBm
14
15 //Calculations
16
17 dynamic_range = 2/3*(I_p -MDS);
18 printf("The dynamic range of the spectrum analyser =
           %d dB",dynamic_range);
19
```

```
20 // Result
21 // The dynamic range of the spectrum analyser = 73
    dB
```

Scilab code Exa 9.2 To find minimum detectable signal

```
1 // To find minimum detectable signal
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 9–2 in Page 277
7
8
9 clear; clc; close;
10
11 // Given data
12 NF = 20; //Noise figure in dB
13 BW = 1*10^3; //Bandwidth in Hz
14
15 // Calculations
16 MDS = -114 +10* log10 ([BW/(1*10^6)]) +NF;
17 printf("The minimum detectable signal of the
   spectrum analyser = %d dBm",MDS);
18
19 // Result
20 // The minimum detectable signal of the spectrum
   analyser = -124 dBm
```

Scilab code Exa 9.3 To find dynamic range and total frequency display

```
1 // To find dynamic range and total frequency display
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 9–3 in Page 285
7
8
9 clear; clc; close;
10
11 // Given data
12 T = 4; //Sample window in s
13 f_s = 20*10^3; // sample frequency in Hz
14 N = 10; //no of bits
15
16 //Calculations
17 f_r = 1/T;
18 f_h = f_s/2;
19 R_d = 20*log10(2^N);
20
21 printf("The ratio of the spectral calculation = %0.2
      f Hz\n",f_r);
22 printf("The maximum calculated spectral frequency =
      %d Hz\n",f_h);
23 printf("The dynamic range = %d dB",R_d);
24
25 //Result
26 // The ratio of the spectral calculation = 0.25 Hz
27 // The maximum calculated spectral frequency = 10000
```

28 // The dynamic range = 60 dB

Chapter 11

Transducers as Input Elements to Instrumentation Systems

Scilab code Exa 11.1 To find change in resistance

```
1 // To find change in resistance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 11-1 in Page 317
7
8
9 clear; clc; close;
10
11 // Given data
12 K =2; //Gauge factor
13 s = 1050; //stress in kg/cm^2
14 E = 2.1*10^6; //modulus of elasticity of steel in kg
   /cm^2
15
16 // Calculations
17 strain = s/E; //Hooke's law
```

```
18 change_in_resistance = K*strain;
19 %change = change_in_resistance * 100;
20
21 printf("The change in resistance = %0.3f\n",
22       change_in_resistance);
22 printf("The percentage change in resistance = %0.1f
23      %%\n", %change);
24 // Result
25 // The change in resistance = 0.001
26 // The percentage change in resistance = 0.1 %
```

Chapter 12

Analog and Digital Data Acquisition Systems

Scilab code Exa 12.1 To find percentage error

```
1 // To find percentage error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 12-1 in Page 360
7
8
9 clear; clc; close;
10
11 // Given data
12 R = 1; //Resistance of the wire in ohm
13 R_L = 10*10^3; //Load resistance in ohm
14 I_supply = 50*10^-3; //power supply current in A
15 V_out = 1; //output of the amplifier in V
16
17 // Calculations
18 V_L = (V_out+(I_supply*R))*R_L/(2*R+R_L);
```

```
19 printf("The load voltage calculated = %0.2f\n", V_L);
20
21 %error = ceil((V_L -V_out)/V_L*100);
22 printf("The percentage error is about %d %%, which
23     is unacceptable in most systems", %error);
24 //Result
25 // The load voltage calculated = 1.05
26 // The percentage error is about 5 %, which is
27     unacceptable in most systems
```

Chapter 14

Fiber Optics Measurements

Scilab code Exa 14.1 To find acceptance angle and numerical aperture

```
1 // To find acceptance angle and numerical aperture
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-1 in Page 392
7
8
9 clear; clc; close;
10
11 // Given data
12 n_2 = 1.45; //Core index of refraction
13 n_1 = 1.47; //Cladding index of refraction
14
15 //Calculation
16 theta_c = acos(n_2/n_1);
17 theta_A = 2*asin(n_1*sin(theta_c));
18 NA = sqrt(n_1^2 -n_2^2);
19
20 printf("The critical angle of the fiber = %0.2f
```

```

        degree\n",theta_c*180/%pi);
21 printf("The acceptance angle of the fiber = %0.2f
        degree\n",theta_A*180/%pi);
22 printf("The numerical aperture of the fiber = %0.3f
        ",NA);
23
24 //Result
25 // The critical angle of the fiber = 9.46 degree
26 // The acceptance angle of the fiber = 27.97 degree
27 // The numerical aperture of the fiber = 0.242

```

Scilab code Exa 14.2 To find loss in the fiber

```

1 // To find loss in the fiber
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-2 in Page 393
7
8
9 clear; clc; close;
10
11 // Given data
12 NA_1 = 0.3; // numerical apertures of Source fiber
13 NA_2 = 0.242; //numerical apertures of receiving
   fiber
14
15 // Calculations
16 loss = 20*log10(NA_1/NA_2);
17 printf("The energy that is lost through the cladding
        of the receiving fiber = %0.2f dB",loss);

```

```
18
19 //Result
20 // The energy that is lost through the cladding of
   the receiving fiber = 1.87 dB
```

Scilab code Exa 14.3 To find current developed in photodiode

```
1 // To find current developed in photodiode
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-3 in Page 395
7
8
9 clear; clc; close;
10
11 // Given data
12 h = 6.63*10^-34; //Planck's constant
13 c = 3*10^8; //Speed of light in m/s
14 lambda = 1.3*10^-6; // photon wavelength in m
15 QE = 0.82; //Quantum efficiency
16 p = 75*10^-6; //Power in W
17 q = 1.6*10^-19; //Charge of an electron
18
19 //Calculations
20 e = h*c/lambda;
21 N = p/e;
22 N_QE= QE*N;
23 I = N_QE*q;
24 printf("The current developed in a PIN photodiode =
%0.2e A",I);
```

```
25
26 //Result
27 // The current developed in a PIN photodiode = 6.43e
   -005 A
```

Scilab code Exa 14.4 To find elapsed time

```
1 // To find elapsed time
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-4 in Page 401
7
8
9 clear; clc; close;
10
11 // Given data
12 n = 1.55; //index of refraction
13 c = 3*10^8; //speed of light in m/s
14 d = 1.4*10^3; //Distance in m
15
16 //Calculations
17 v = c/n;
18 t = d/v;
19 printf("t = %0.1e s",t);
20 disp('Since twice the time to reach the break is
      required for the reflection to arrive at the
      reflectometer , ')
21 printf("Hence the total elapsed time = %0.3e s",2*t)
   ;
22
```

```
23 // Result  
24 // t = 7.2e-006 s  
25 // Since twice the time to reach the break is  
// required for the reflection to arrive at the  
reflectometer ,  
26 // Hence the total elapsed time = 1.447e-005 s
```
