

Scilab Textbook Companion for
Network Analysis And Synthesis
by B. R. Gupta¹

Created by
Khan Salman Aafak
B.E (EXTC)
Electronics Engineering
Mumbai University
College Teacher
Chaya S Ravindra
Cross-Checked by
K. V. P. Pradeep

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Network Analysis And Synthesis

Author: B. R. Gupta

Publisher: S. Chand, New Delhi

Edition: 3

Year: 2009

ISBN: 81-219-3055-3

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Introduction to electronic circuits	5
2 single phase AC Circuits	24
3 Three Phase Circuits	88
4 network theorem	125
5 Network Theorem	144
7 Two Port Network	183
8 filter	192
9 Network Function	216

List of Scilab Codes

Exa 1.1	Resistance	5
Exa 1.2	Diameter	5
Exa 1.3	Alpha Rise in Temperature	6
Exa 1.4	Current	6
Exa 1.5	Power and Resistance	7
Exa 1.6	cost quantity of electricity number of electron rate of electrical energy	8
Exa 1.7	Power current voltage	8
Exa 1.11	Temperature coefficient	9
Exa 1.13	Resistance total power	9
Exa 1.14	Resistance	10
Exa 1.15	RESISTANCE CURRENT	10
Exa 1.16	ENERGY PERCENTAGE OF ENERGY	11
Exa 1.17	EMF	12
Exa 1.18	Inductance of Coil	12
Exa 1.19	Inductance	12
Exa 1.20	Resistance	13
Exa 1.21	Voltage Across Inductor	13
Exa 1.26	Inductor	14
Exa 1.27	Flux	14
Exa 1.28	Capacitor	14
Exa 1.29	Equivalent Capacitor	15
Exa 1.30	VLTAGE AND ENERGY	15
Exa 1.32	Current and Resistance	16
Exa 1.33	Introduction of Electric Circuits	16
Exa 1.34	Power	16
Exa 1.35	Resistance	17

Exa 1.36	change flux flux change voltage energy in inductor	17
Exa 1.37	Current	18
Exa 1.38	Current	19
Exa 1.39	Insulation resistance	19
Exa 1.40	Resistance	20
Exa 1.41	Resistance	20
Exa 1.42	Resistance	20
Exa 1.44	voltage	21
Exa 1.46	current	21
Exa 1.47	Resistance	21
Exa 1.48	Current	22
Exa 1.50	voltage	22
Exa 1.51	Power	22
Exa 1.52	equvalent inductance	23
Exa 1.53	equvalent resistance	23
Exa 2.1	average value RMS Value Form Factor Peak Factor RMS Value of sine wave	24
Exa 2.3	Form Factor Peak Factor	24
Exa 2.7	addition and substraction	25
Exa 2.8	ADDITION SUBSTRACTION MULTIPLICATION DIVISION	25
Exa 2.9	Rate of change of current	26
Exa 2.10	rms	27
Exa 2.11	INSTANTANEOUS VALUE	27
Exa 2.12	current	27
Exa 2.13	Average Value of Voltage	28
Exa 2.14	Effective Value Form Factor	28
Exa 2.15	Average Value Effective Value Form Factor .	29
Exa 2.16	ENERGY FORM FACTOR	29
Exa 2.17	RMS	30
Exa 2.20	Voltage	30
Exa 2.21	Voltage	30
Exa 2.22	Average	31
Exa 2.23	Average Energy	31
Exa 2.24	Current	32
Exa 2.25	VOLTAGE	32

Exa 2.26	Reading of moving coil Reading of hot wire	32
Exa 2.27	Total Power Power dissipated	32
	CURRENT POWER DISSIPATED INSTANTANEOUS CURRENT	33
Exa 2.28	FREQUENCY	34
Exa 2.29	Capacitive Reactance susceptance and current	34
Exa 2.30	Impedance Admittance Current Power Factor	
	Active power Reactive Power Apparent Power	34
Exa 2.31	Current Apparent Power Active Power . .	35
Exa 2.32	Active Power Current Voltage	36
Exa 2.33	Impedance Admittance Current Power Factor	
	Apparent Power Active Power Reactive	
	Power Voltage Across resistance and capacitance	37
Exa 2.34	Impedance Power Factor Power Consumed .	37
Exa 2.35	Maximum Charge and Energy	38
Exa 2.36	XL XC Current Power Factor Apparent Power	
	Active Power Reactive Power	39
Exa 2.37	active power impedance	40
Exa 2.38	Current Voltage	40
Exa 2.39	1 Power factor 2 Apparent Reactive Active Power	41
Exa 2.40	Voltage across v1 v2 Impedance Admittance Power factor	42
Exa 2.41	Impedance	43
Exa 2.42	Resistance Inductance	43
Exa 2.43	Power Factor	44
Exa 2.44	Resistance Capacitance	45
Exa 2.45	Power Inductance	46
Exa 2.46	P	46
Exa 2.47	RMS	47
Exa 2.49	current	47
Exa 2.51	Impedance admittance Current Power Factor	
	Apparent Power active Reactive Power . . .	48
Exa 2.52	Total Current power Factor	49
Exa 2.53	Inductance Frequency	49
Exa 2.54	Single Phase AC Circuits	50
Exa 2.55	Resistance	51

Exa 2.56	Current Power Factor	51
Exa 2.57	Total Current Impedance Admittance Power factor Apparent Power Active Power Reactive Power	52
Exa 2.58	Voltage Current power Factor Active Reac- tive Power	53
Exa 2.59	Total Current Shunt Capacitor	54
Exa 2.60	Conductance Susceptance Current Power fac- tor	55
Exa 2.61	admittance Impedance Total Current Power Factor Active Power	56
Exa 2.62	Current impedance Active Power TotalActive Power Power Factor Apparent Power Reactive Power	57
Exa 2.63	Current Power Factor	59
Exa 2.64	Current in branch Total Current	60
Exa 2.66	Power	60
Exa 2.67	Branch Impedance Total Impedance Branch Current Total Current	61
Exa 2.68	Total Power	62
Exa 2.69	Line Current Impedance Circuits Phase Angle	63
Exa 2.70	Current Impedance	64
Exa 2.71	Power Power Factor	64
Exa 2.72	Power Factor Total volts Active Reactive power Overall Power Factor	65
Exa 2.73	Inductance Capacitance	65
Exa 2.74	Current in each branch Total Current Power Factor Total apparent Active Reactive Total Current	66
Exa 2.75	Current Total Apparent Active Reactive Power Power Factor	67
Exa 2.76	magnitude Phase Angle Total Impedance . .	68
Exa 2.77	Power Factor	68
Exa 2.78	Voltage	69
Exa 2.79	Voltage	69
Exa 2.80	R1 X1 X2	70
Exa 2.81	Current in each branch Total Current Active Reactive Apparent Power	70

Exa 2.82	Resistance Capacitance	71
Exa 2.83	Active Reactive Apparent Power	72
Exa 2.84	Frequency	73
Exa 2.85	Current	74
Exa 2.86	Resonant Frequency Upper Lower Half Frequency Band Width Voltage	74
Exa 2.87	Inductance Q Current voltage	75
Exa 2.88	Resonant Frequency Rc	75
Exa 2.89	Resonant Frequency Q Band Width Out put Voltage	76
Exa 2.90	R L C	77
Exa 2.91	Current at resonance	77
Exa 2.92	frequency	77
Exa 2.93	Self Inductane Mutual Inductance voltage induce	78
Exa 2.94	Mutual Inductance EMF	78
Exa 2.95	Mutual Inductance	79
Exa 2.96	Mutual Inductance Coefficient Coupling	79
Exa 2.97	L1 L2 M K	80
Exa 2.98	L1 L2 M N2	80
Exa 2.99	M K	81
Exa 2.100	Self Inductance Mutual Inductance Coefficient of coupling	81
Exa 2.102	Equivalent Inductance	81
Exa 2.103	Equivalent Inductance	82
Exa 2.104	Self Inductance Total Inductance Energy	82
Exa 2.105	Self Inductance Mutual Inductance Turns of coil	83
Exa 2.106	Resonant Frequency Current	84
Exa 2.107	Average Value RMS Value	84
Exa 2.108	RMS	85
Exa 2.109	Real Power Reactive Power Power Factor	85
Exa 2.111	Total Power Factor Total Active and Reactive Power	86
Exa 2.112	impedance resistance reactance	86
Exa 2.113	Resonant Frequency Dynamic Resistance Band width	87

Exa 3.1	Line Current Total Volts Ampere Active Power	
	Reactive Power	88
Exa 3.2	Load Impedance Line Voltage	88
Exa 3.3	Line Current Active and Reactive Power . .	89
Exa 3.4	Current	90
Exa 3.5	line current active and reactive power . . .	90
Exa 3.6	Phase Current Line Current Total Active and Reactive Power	91
Exa 3.7	line currents	92
Exa 3.8	Line Current Neutral Current Total power . .	93
Exa 3.9	Line Current Neutral Current	94
Exa 3.10	Voltage Line Currents	94
Exa 3.11	Reading on wattmeter	96
Exa 3.12	Phase Current of delta and star Active Power Power Factor	96
Exa 3.13	Line voltage	97
Exa 4.14	Current voltage	98
Exa 3.15	Line Current Neutral Currents Reading of wattmeter	99
Exa 3.16	Power and Power factor	100
Exa 3.18	Power ouputs	100
Exa 3.19	Current Power factor Active Reactive Power	100
Exa 3.20	Load Impedance	101
Exa 3.21	Line current Volt ampere Active and Reactive Power	101
Exa 3.22	Phase Current Line Current Power Factor Ac- tive Powerand Reactive Power	102
Exa 3.23	impedance	102
Exa 3.24	Total Power and Power Factor	103
Exa 3.25	Line Current Total Power	103
Exa 3.26	current Power	104
Exa 3.27	Line Current and Total Power	105
Exa 3.28	Line Current Neutral Current Total power .	105
Exa 3.29	Line current	106
Exa 3.30	R and x	106
Exa 3.31	Voltmeter	107
Exa 3.32	Line currents	107
Exa 3.33	Neutral Current	108

Exa 3.34	Line Current Total Voltmeter Active and Reactive Power	108
Exa 3.35	Total Active Power Toal Reactive Power Voltmeter Line CurrentThree Phase Circuitsower factor	109
Exa 3.36	Phase current Total line current	110
Exa 3.37	current	110
Exa 3.39	Voltage	112
Exa 3.40	W1 and W2	113
Exa 3.41	Current	113
Exa 3.42	Za Zb Zc	114
Exa 3.43	Total Apparent active Reactive Power line Current Power factor	114
Exa 3.44	Power and Power Factor	115
Exa 3.45	Line Current	115
Exa 3.47	total votamperes Active and Reactive Power	116
Exa 3.48	voltage	117
Exa 3.49	Phase Current Line Current Total active and reactive Power W1 w2	117
Exa 3.50	Line current	118
Exa 3.51	Resistance reactance Power Factor	119
Exa 3.52	Line Current Power factor Active and Reactive Power	120
Exa 3.53	Current Active and Reactive Power	121
Exa 3.54	Voltage load impedance	121
Exa 3.55	Phase and Line Current	122
Exa 3.59	current	123
Exa 4.4	Numbers of trees	125
Exa 4.6	Currents	125
Exa 4.8	currents	126
Exa 4.9	current	127
Exa 4.10	Current	127
Exa 4.12	current	128
Exa 4.13	current	128
Exa 5.13	Current	129
Exa 4.14	current	129
Exa 4.16	current	130
Exa 4.17	voltage	130

Exa 4.19	currents	130
Exa 4.21	current and power	131
Exa 4.22	voltage	131
Exa 4.23	current	132
Exa 4.24	Current	132
Exa 4.25	Current	132
Exa 4.28	Current	133
Exa 4.29	Power	133
Exa 4.30	Current	134
Exa 4.32	Branch Current	134
Exa 4.36	Current	134
Exa 4.37	Current	135
Exa 4.38	Current	136
Exa 4.41	Voltage And Current	136
Exa 4.43	Node Voltage	137
Exa 4.44	Current	137
Exa 4.46	Current	138
Exa 4.47	V2	138
Exa 4.48	Voltage	139
Exa 4.49	Node Voltage	139
Exa 4.50	Voltage Vcd	140
Exa 4.51	Current	140
Exa 4.52	Voltage	141
Exa 4.56	Input Impedance	141
Exa 4.57	Primary and Secondary Current and voltage	141
Exa 4.58	current	142
Exa 4.62	I1 I2 Active and Reactive Power	142
Exa 5.1	Current	144
Exa 5.2	Voltage	145
Exa 5.3	Current	145
Exa 5.4	Current	147
Exa 5.6	Current	147
Exa 5.7	Power Total Power	148
Exa 5.8	Current	148
Exa 5.9	Deflection	149
Exa 5.10	Power dissipated	149
Exa 5.11	Voltage	150
Exa 5.12	Current	150

Exa 5.13	Current	151
Exa 5.14	Current	151
Exa 5.15	Current	152
Exa 5.16	Impedance	152
Exa 5.17	Impedance	152
Exa 5.18	Current and Resistance	153
Exa 5.19	RL Power	154
Exa 5.20	VOLTAGE	155
Exa 5.21	ZL Power	155
Exa 5.22	VOLTAGE	155
Exa 5.23	Vo	156
Exa 5.24	Voltage	157
Exa 5.25	Current	157
Exa 5.26	Current	158
Exa 5.27	Delta to Star	158
Exa 5.28	Total Impedance	159
Exa 5.29	Current	159
Exa 5.30	Current	160
Exa 5.31	Current	161
Exa 5.32	RL for Pmax	161
Exa 5.33	Current	162
Exa 5.34	Pmax Total Power RL	163
Exa 5.35	Thevenins equivalent circuits	163
Exa 5.36	maximum Power	164
Exa 5.37	Current	164
Exa 5.38	Current	165
Exa 5.39	RL and Pmax	166
Exa 5.40	R and Current	166
Exa 5.41	Current	167
Exa 5.42	Current	167
Exa 5.43	Current	168
Exa 5.44	current resistance	168
Exa 5.45	Current	169
Exa 5.46	Load Resistance	169
Exa 5.47	Thevenins and Nortan Equivalent	170
Exa 5.48	Current	170
Exa 5.49	current	171
Exa 5.50	Current	171

Exa 5.51	Resistance Power	172
Exa 5.52	Current	172
Exa 5.53	Vth Rth	173
Exa 5.54	Current	174
Exa 5.55	Current	174
Exa 5.56	Current	174
Exa 5.57	Current	175
Exa 5.58	Resistance	175
Exa 5.60	Current	176
Exa 5.62	Nortan equivalent	176
Exa 5.63	Thevenins Equivalent	177
Exa 5.64	ZL Power	177
Exa 5.65	Current	178
Exa 5.66	Change in current	178
Exa 5.67	Reciprocity Theorem	179
Exa 5.68	Equivalent Voltage	179
Exa 5.69	Current	180
Exa 5.70	Current	180
Exa 5.71	Current in R3	181
Exa 5.73	matrix	181
Exa 5.74	Reciprocity Theorem	181
Exa 7.2	Z Parameter	183
Exa 7.4	Z and Y Parameter	183
Exa 7.5	Z and Y Parameter	184
Exa 7.8	Current and Voltage	184
Exa 7.14	Y Parameter	185
Exa 7.16	Image Parameter	186
Exa 7.17	Insertion Loss	186
Exa 7.18	Impedance	187
Exa 7.20	Admittance Parameter	187
Exa 7.21	Ra Rb Rc	188
Exa 7.22	Z and Y Parameter	188
Exa 7.25	matrix	189
Exa 7.34	output Voltage	189
Exa 7.37	Y parameter	190
Exa 7.38	Impedance	190
Exa 7.42	Z Parameter	191
Exa 8.1	Frequency Impedance Attenuation Phase Shift	192

Exa 8.2	L and C	193
Exa 8.3	Impedance	193
Exa 8.4	L and C	194
Exa 8.5	Band Width	194
Exa 8.6	Circuits Parameter	195
Exa 8.7	inductance	195
Exa 8.8	m	196
Exa 8.9	m	196
Exa 8.10	L and C	197
Exa 8.11	L and C	198
Exa 8.12	L	198
Exa 8.13	C	198
Exa 8.14	L and C	199
Exa 8.15	cutt off Frequency	199
Exa 8.16	Cutt off Frequency Pass band	199
Exa 8.17	Cutt off Frequency Pass band	200
Exa 8.18	m	200
Exa 8.19	m and T	201
Exa 8.20	impedance	202
Exa 8.21	Inductance Capacitance	202
Exa 8.22	Resonant Frequency Band Width Cutt off Frequency	203
Exa 8.23	Cutt off Frequency	203
Exa 8.24	Output Voltage	204
Exa 8.25	Gain	204
Exa 8.26	Mid Band Gain	205
Exa 8.27	R2 Mid abnd Gain Cutt of Frequency	205
Exa 8.28	Mid abnd Output	206
Exa 8.29	Gain at mid band	206
Exa 8.30	Design a Filter	206
Exa 8.31	Resistance	207
Exa 8.32	Impedance	207
Exa 8.33	Attenuation	208
Exa 8.34	Resistance	208
Exa 8.35	Impedance	209
Exa 8.36	Resistance	209
Exa 8.37	Impedance	209
Exa 8.38	Resistance	210

Exa 8.39	N	210
Exa 8.40	N	211
Exa 8.41	L	211
Exa 8.42	D	212
Exa 8.43	L	212
Exa 8.45	design T	212
Exa 8.46	Design lattice attenuator	213
Exa 8.47	Impedance	213
Exa 8.48	Resistance	214
Exa 8.49	Design lattice attenuator	214
Exa 9.24	Resonant frequency Q band width Impedance	216
Exa 9.26	Resonant frequency Q	216
Exa 9.32	Q	217
Exa 9.37	Poles and Zero	218
Exa 9.38	R L G C	218
Exa 9.46	Ia	219
Exa 9.50	Current	219
Exa 9.56	C	219

Chapter 1

Introduction to electronic circuits

Scilab code Exa 1.1 Resistance

```
1 //CHAPTER1 EX 1-1 PG NO 17
2 L=5*10^-3; //length
3 B=2*10^-2; //breath
4 A=(5*10^-3)*(2*10^-2); //area
5 P=1.72*10^-5 ; //resistivity of copper
6 R=P*L/A; //resistance of copper
7 disp('i) resistance = '+string (R)+ ' ohm');
8 R=P*L/A; //resistance in ohm
```

Scilab code Exa 1.2 Diameter

```
1 //EXAMPLE 1-2 PG NO 18
2 R=0.69; //RESISTANCE
3 P=2.83*10^-8; //PRO
4 L=60; //LENGTH OF CABLE
5 a=(P*L)/R;
```

```

6 disp('i) a = '+string(a)+ ' m^2');
7 D=[(4*a)/pi]^0.5; //DIAMETER
8 disp('i) DIAMETER = '+string(D)+ ' mm');

```

Scilab code Exa 1.3 Alpha Rise in Temperature

```

1 //EXAMPLE 1-3 PG NO-18
2 A20=0.00393; //ALPHA 20
3 R30=1.3; //RESITANCE 30
4 A30=A20/(1+A20*(30-20)); //ALPHA 30
5 disp('i) Alpha30 (A30) = '+string(A30)+ ' ');
6 T=[((1.6/1.3)-1)/0.00378]; // THE RISE IN
    TEMPERATURE TO BE FIND where T=t-30
7 disp('ii) Resistance Temperature (t-30) = '+string(T)
    )+ ' degree celcious');

```

Scilab code Exa 1.4 Current

```

1 //EXAMPLE 1-4
    PG NO
        18-19
2 R1=2.22; //RESISTANCE
3 R2=0.6; //RESISTANCE
4 R3=3; //Resistance
5 R4=4;
6 R5=5;
7 R6=6;
8 R7=2;
9 R=R1+R2+R3;
10 disp('i) Resistance (R) is = '+string([R]) + '
    ohm ');
11 V=12; //VOLTAGE
12 I=V/R; // Current

```

```

13 disp('ii) CURRENT (I) is      = '+string ([I]) +' A
      ');
14 I3=I;

      //CURRENT THROUGH 3 ohm RESISTANCE
15 disp('iii) CURRENT (I3) is      = '+string ([I3]) +' A
      ');
16 I5=(I3*R4)/(R4+R5);           //CURRENT
      THROUGH 5 ohm RESISTANCE
17 disp('iv) CURRENT (I5) is      = '+string ([I5]) +' A
      ');
18 I4=(I3*R5)/(R4+R5);           //CURRENT
      THROUGH 4 ohm RESISTANCE
19 disp('v) CURRENT (I4) is      = '+string ([I4]) +' A
      ');
20 V1=1.236;                   //
      VOLTAGE ACROSS THREE PARALLEL RESISTANCE
21 I2=V1/R7;                   //
      current
22 disp('vi) CURRENT (I2) is      = '+string ([I2]) +' A
      ');
23 I1=V1;                      //
      CURRENT THROUGH 1 ohm RESISTANCE
24 disp('iv) CURRENT (I1) is      = '+string ([I1]) +' A
      ');
25 I6=V1/R6;                   //
      CURRENT THROUGH 6 ohm RESISTANCE
26 disp('vii) CURRENT (I6) is      = '+string ([I6]) +' A
      ');

```

Scilab code Exa 1.5 Power and Resistance

```

1 //EXAMPLE 1-5 PG NO-19
2 V1=230; //VOLTAGE ONE
3 P1=1000; //POWER
4 R=V1*V1/P1; //RESISTANCE OF HEATER
5 V2=210; //VOLTAGE TWO
6 P2=V2*V2/R; //POWER OF HEATER WHEN VOLTAGE IS
    210
7 R=(V1*V1)/P1 // Resistance
8 disp('i')RESISTANCE = '+string(R)+' ohm';
9 P2=(V2*V2)/R; //Power
10 disp('ii')POWER = '+string(P2)+' ohm';

```

Scilab code Exa 1.6 cost quantity of electricity number of electron rate of electr

```

1 //EXAMPLE 1-6 PG NO-19-20
2 I=12; //CURRENT
3 V=230; //VOLTAGE
4 P=1000; //POWER
5 T=3; //TIME
6 S=3600;
7 E=(I*V/P)*T; //ENERGY USED
8 Q=I*T*S; //QUANTITY OF ELECTRICITY USED
9 IC=6.24*10^18;
10 N.C=IC*Q; //NUMBER OF ELECTRON
11 R=I*V; //RATE OF ENERGY
12 disp('i') ENERGY = '+string(E)+' KWh';
13 disp('ii') QUANTITY = '+string(Q)+' C';
14 disp('iii') NUMBER OF ELECTRON = '+string(N.C)+' ';
15 disp('iiii') RATE OF ENERGY = '+string(R)+' W';

```

Scilab code Exa 1.7 Power current voltage

```

1 //Example 1_7 PG NO-20

```

```

2 I1=3;           //current
3 I2=1;           //current
4 R=4;            //Resistor
5 I=I1-I2;        //current through resistance
6 disp('i) Current Through resistance (I) = '+string (I)
      )+ ' A');
7 P=I*I*R;
8 disp('ii) Power dissipated in resistor (P) = '+string
      (P)+ ' W');
9 V=I*R;
10 disp('iii) voltage (V) = '+string (V)+ ' V');
11 P1=V*I1;        //power dissipated with 3A source
12 disp('iv) power dissipated with 3A source (P1) = '+
      string (P1)+ ' W');

```

Scilab code Exa 1.11 Temperature coefficient

```

1 //EXAMPLE 1-11
                           PG NO-21
2 R55=58;                  // resistance
3 R15=50;                  // Resistance
4 T1=55;                   //Temperature
5 T2=15;                   //Temperature
6 A15=[(R55/R15)-1]/(T1-T2); //alpha 15
7 disp('i) ALPHA (A15) = '+string (A15)+ ' ');
8 T3=0;
9 A2=A15/[1+A15*(T3-T2)]; //Alpha 2
10 disp('ii) ALPHA (A2) = '+string (A2)+ ' ');

```

Scilab code Exa 1.13 Resistance total power

```

1 //EXAMPLE 1-13   PG NO 21-22
2 R=10; //RESISTANCE

```

```
3 V=230; //VOLTAGE
4 P=(V*V)/R; //POWER
5 disp('i') POWER = '+string(P)+', W')
```

Scilab code Exa 1.14 Resistance

```
1 //EXAMPLE  
1-14  
  
PG NO-22  
  
2 R1=4; //Resistance  
3 R2=2; //Resistance  
4 R3=8; //Resistance  
5 RS=R1+R2; //  
    resistance When Point A&B is short circuit  
6 disp('i')resistance When Point A&B is short circuit  
    = '+string(RS)+', ohm');  
7 R0=R1+R2+R3;  
    //resistance When Point A&B is open circuit  
8 disp('i')resistance When Point A&B is open circuit  
    = '+string(R0)+', ohm');
```

Scilab code Exa 1.15 RESISTANCE CURRENT

```
1 //EXAMPLE 1-15  
PG NO-22  
  
2 I1=0.04; //CURRENT  
3 I2=0.01; //CURRENT  
4 V1=200; //VOLTAGE  
5 R=V1/I1; //Resistance  
6 disp('i')resistance (R) = '+string(R)+', ohm');  
7 V2=10; //VOLTAGE  
8 I3=50; //CURRENT
```

```

9 A=0.1;           //AMMETER RESISTANCE
10 R1=(V2/I3)-0.1;
11 disp('i)Resistance (R1) = '+string (R1)+ ' ohm');
12 V3=5000;
13 V4=250;
14 I=I3/V3;
15 disp('i)Current (I) = '+string (I)+ ' A');
16 R2=(V4-I3)/I;
17 disp('i)resistance (R2) = '+string (R2)+ ' ohm');

```

Scilab code Exa 1.16 ENERGY PERCENTAGE OF ENERGY

```

1 //EXAMPLE 1-16
                           PG NO-23
2 V=1;           //ASSUMING
3 t=1;           //ASSUMING
4 R1=30;          //RESISTANCE
5 R2=20;
6 R3=10;
7 E30=(V/R1)*t;          //ENERGY AT
                           30 ohm RESISTANCE
8 disp('i) ENERGY = '+string (E30)+ ' ');
9 E20=(V/R2)*t;          //ENERGY AT 20
                           ohm RESISTANCE
10 disp('ii) ENERGY = '+string (E20)+ ' ');
11 E10=(V/R3)*t;          //ENERGY AT
                           10 ohm RESISTANCE
12 disp('iii) ENERGY = '+string (E10)+ ' ');
13 TE=E30+E20+E10;          //TOTAL ENERGY
14 disp('iv) TOTAL ENERGY = '+string (TE)+ ' ');
15 PTE=(E30/TE)*100;          //PERCENTAGE OF
                           TOTAL ENERGY
16 disp('ii) PERCENTAGE OF TOTAL ENERGY = '+string (
                           PTE)+ '% ');

```

Scilab code Exa 1.17 EMF

```
1 //EXAMPLE 1-17  
    PG NO-23  
2 N=10^3;           //Number of Turns  
3 a=6.25*10^-4;    //Diameter  
4 l=0.25;  
5 L=(N*N*4*pi*10^-7*a)/(%pi*l);      //  
    INDUCTANCE  
6 disp('i')inductance = '+string(L)+ ' H');  
7 e=L*100;          //EMF  
8 disp('ii')EMF = '+string(e)+ ' V')
```

Scilab code Exa 1.18 Inductance of Coil

```
1 //EXAMPLE 1-18  
    PG NO-23  
2 E=0.05;           //ENERGY  
3 i=0.1;            //CURRENT  
4 L=2*E/i^2         //INDUCTANCE OF COIL  
5 disp('i')inductance = '+string(L)+ ' H')
```

Scilab code Exa 1.19 Inductance

```
1 //EXAMPLE 1-19          PG NO  
    23  
2 i=0.184;          // derivative of I  
3 e=0.16;  
4 L=e/i;             //Inductance  
5 disp('i')Inductance = '+string(L)+ ' H')
```

Scilab code Exa 1.20 Resistance

```
1 //EXAMPLE 1-20      PG NO-24
2 A=20*10^-6;
3 L=30;
4 P20=1.72*10^-8;
5 R20=P20*L/A;
6 X0=0.00426;
7 I=5;
8 X20=X0/[1+(X0*20)];
9 R55=R20*(1+X20*(55-20));
10 P=I*I*R55;
11 disp('i)RESISTANCE = '+string(R20)+' ohm');
12 disp('i) ALPHA 20(X20)= '+string(X20)+' ohm');
13 disp('i)RESISTANCE = '+string(R55)+' ohm')
14 disp('i)POWER = '+string(P)+' w')
```

Scilab code Exa 1.21 Voltage Across Inductor

```
1 //EXAMPLE 1-21          PG NO
-24
2 L=200*10^-3;           //INDUCTAR
3 t1=1;                  // di / dt=(-2e^-t+4e^-2t )
= -1.9*10^-7;
4 V=L*(-1.94*10^-7);    //VOLTAGE AT
TIME 1
5 disp('i)  Voltage = '+string(V) +'V ');
6 t2=0.1;                // di / dt=(-2
e^-t+4e^-2t )^2=0.216;
7 V1=L*0.5*(0.216);     //VOLTAGE AT
TIME 0.1
8 disp('ii)  Voltage = '+string(V1) +'V');
```

Scilab code Exa 1.26 Inductor

```
1 //EXAMPLE 1-26          PG NO 27
2 L1=(1.1-0.8)/0.75;           // Inductance
3 disp('i') Inductance = '+string(L1)+ ' H')
4 L2=3*L1;                   // Inductance
5 disp('ii') Inductance = '+string(L2)+ ' H')
```

Scilab code Exa 1.27 Flux

```
1 //EXAMPLE 1-27          PG NO27
2 L1=50*10^-3;                // Inductar
3 L2=100*10^-3;              // Inductar
4 X=(L1/L2);
5 disp('i')      (L1/L2) = '+string(X)+ ' '
6 //Q1+Q2=600;
7 Q11=200;                  // flux
8 Q22=400;                  // flux
9 disp('ii') Flux   Q11 = '+string(Q11)+ ' mWb';
10 disp('iii') Flux  Q22 = '+string(Q22)+ ' mWb');
```

Scilab code Exa 1.28 Capacitor

```
1 //EXAMPLE 1-28          PG NO-27
2 C1=60;                     //TWO CAPACITOR CONNECTED IN
3                         SERIES
3 EC=(C1*C1)/(C1+C1);       //
                         EQUIVALENT CAPACITOR
```

```
4 disp('i') Equivalent Cpacitor (EC) is = '+string  
      (EC) +' microF');
```

Scilab code Exa 1.29 Equivalent Capacitor

```
1 //EXAMPLE 1-29 PG NO  
    -27-28  
2 C1=12; //CAPACITOR  
3 C2=4; //CAPACITOR  
4 C3=8;  
5 C4=7;  
6 C1=(C1*C2)/(C1+C2); //CAPACITOR  
    IN SEREIS  
7 disp('i') Capacitor = '+string (C1)+ ' muF')  
8 C2=(C3*C4)/(C3+C4); //CAPACITOR  
    IN PARALLEL  
9 disp('i') Capacitor = '+string (C2)+ ' muF')
```

Scilab code Exa 1.30 VLTAGE AND ENERGY

```
1 //EXAMPLE 1-30 PG NO  
    -28  
2 Q=80*10^-4; //COULOMB CHARGR  
3 C=150*10^-6;  
4 C1=100*10^-6; //CAPACITANCE  
5 C2=50*10^-6;  
6 Va=Q/C1;  
7 Vb=Q/C2;  
8 E1=(0.5*C1*Va*Va)+(0.5*C2*Vb*Vb); //ENERGY  
9 E2=0.5*C*(Va+Vb)*(Va+Vb);  
10 disp('i') variable = '+string (Va)+ ' ohm')  
11 disp('i') variable = '+string (Vb)+ ' ohm')  
12 disp('i') energy = '+string (E1)+ ' J')
```

```
13 disp('i)energy = '+string(E2)+' J')
```

Scilab code Exa 1.32 Current and Resistance

```
1 //EXAMPLE 1-32 PG NO-29
2 V=10; //VOLTAGE
3 R1=2;
4 R2=8; //RESISTANCE
5 I1=V/(R1+R2); //CURRENT
6 I2=1.25; //CURRENT THROUGH SECOND BRANCH
7 R=V/I2-5;
8 disp('i)CURRENT = '+string(I1)+' A')
9 disp('ii)RESISTANCE = '+string(R)+' ohm')
```

Scilab code Exa 1.33 Introduction of Electric Circuits

```
1 //EXAMPLE 1-33 PG NO-29-30
2 R1=29980; //RESISTANCE
3 I1=9.99; //current
4 R2=20;
5 I2=0.01; // current
6 r=20*0.01/9.99; // resistance
7 disp('i)resistance = '+string(r)+' ohm')
```

Scilab code Exa 1.34 Power

```
1 //Example 1-34 PG
    NO-30
2 V=20; //VOLTAGE
3 R1=5; //Resistance
```

```

4 X=7.5;
5 P=(20/(R1+X))^2*(X);                                //Power
6 disp('i') Power (P) is      = '+string (P) + ' W ');

```

Scilab code Exa 1.35 Resistance

```

1 //EXAMPLE 1-35
          PG NO 30-31
2 I1=4;                                     //Current
3 I2=6;                                     //Current
4 V=110;                                    //Voltage
5 Vab1=V-(6+4)*2;
6 VB=80;
7 VC=50;
8 R11=(Vab1-VB)/I1;
9 R12=(Vab1-VC)/I2;
10 Vab2=V-(-2+20)*2;                         //Voltage
11 R21=(VB-Vab2)/2;                          //Resistance
12 R22=(Vab2-VC)/20;                         //Resistance
13 I=(V-VB)/2;                               //Current
14 R=(VB-VC)/I;                             //Resistance
15 disp('i) variable = '+string (Vab1)+ ' ohm')
16 disp('ii) resistance = '+string (R11)+ ' ohm')
17 disp('iii) resistance = '+string (R12)+ ' ohm')
18 disp('iv) variable = '+string (Vab2)+ ' ohm')
19 disp('v) resistance = '+string (R21)+ ' ohm')
20 disp('vi) resistance = '+string (R22)+ ' ohm')
21 disp('vii) resistance = '+string (R) + ' ohm')
22 disp('viii) Current = '+string (I) + ' A')

```

Scilab code Exa 1.36 change flux flux change voltage energy in inductor

```

1 //EXAMPLE 1-36      PG NO-31

```

```

2 T=0.99425;      //TIME
3 disp('i)Time = '+string (T)+ ' seconds')
4 X=0.37;          //DERAVATIVES OF 'I' W.R.T
5 disp('ii)(di\dt) = '+string (X)+ ' A\sec'
6 LI=0.63;         //CURRENT
7 dli=0.37;        // deravatives of 'SI' w.r.t
8 disp('iii)(dsi\dt) = '+string (dli)+ ' Wb-turns\sec'
9 VL=dli;
10 disp('iv)(VL) = '+string (VL)+ ' V'
11 Ri=0.63;
12 VR=Ri;
13 disp('v)VR = '+string (VR)+ ' V'
14 E=0.5*LI*LI;    //ENERGY
15 disp('vi)ENERGY stored in magnetic field = '+string
(E)+ ' J')
16 E1=LI*X;        //ENERGY STORED IN MAGNETIC FIELD
17 H=Ri*Ri;        //HEAT
18 disp('vii) Rate of Energy stored in magnetic field =
'+string (E1)+ ' W'
19 disp('viii)Rate of dissipation of heat in resistor =
'+string (H)+ ' W')
20 disp('ix)Rate of supply of battery energy = '+string
(Ri)+ ' W')

```

Scilab code Exa 1.37 Current

```

1 T=2000;          //TEMPERATURE
2 T1=15;           //ROOM TEMPERATURE
3 V=220;           //VOLTAGE
4 P=40;            //POWER
5 A15=0.005;
6 R=V*V/P;         //RESISTANCE
7 R15=R/(1+A15*(T-T1));   //RESISTANCE AT TIME OF
SWITCHING
8 I=V/R15;         //CURRENT

```

```
9 disp('i) resistance = '+string (R)+' ohm')
10 disp('ii) resistance = '+string (R15)+' ohm')
11 disp('iii) current = '+string (I)+' A')
```

Scilab code Exa 1.38 Current

```
1 //EXAMPLE 1-38 PG NO-32
2 F=50; //Frequency
3 W=2*%pi*F;
4 disp('i)W = '+string (W)+' rad/sec');
5 t=0.0025; //time
6 Vm=10;
7 A1=0.01;
8 A2=0.005;
9 i=[(A2*Vm^2)/2]+0.0707;
10 disp('ii) Current = '+string (i)+' A')
```

Scilab code Exa 1.39 Insulation resistance

```
1 //EXAMPLE 1-39 PG NO-32-33
2 V=440; // voltage
3 V1=5; // voltage
4 R=40; // resistance
5 V2=220;
6 V3=100;
7 Rv=(V3*R)/[V2-V3]; // insulation
    resistance
8 disp('i) Resistance (Rv) = ' + string (Rv) +' Kohm')
9 Ri=[Rv*(V-V1)]/V1; //insulation
    resistance
10 disp('iii) Resistance (Ri) = '+string (Ri) +' Kohm')
```

Scilab code Exa 1.40 Resistance

```
1 //EXAMPLE 1-40 PG  
2 P=1.72*10^-8; NO-33  
3 t=0.03; //PRO  
4 R=[(4*P)/(%pi*t)]*0.47; //Resistance  
5 disp('i') Resistance = '+string(R) +' ohm')
```

Scilab code Exa 1.41 Resistance

```
1 //EXAMPLE 1-41 PG  
2 P=1.72*10^-8; NO-33  
3 t=0.03; //PRO  
4 R=[(P*%pi)/(4*t*0.47)];  
5 disp('i') Resistance = '+string(R) +' ohm')
```

Scilab code Exa 1.42 Resistance

```
1 //EXAMPLE 1-42 PG NO-34  
2 P=100; //pro  
3 L=0.5; //inductance  
4 r1=0.15; //radius  
5 r2=0.075; //radius  
6 R=[100/(2*%pi*L)]*(0.731); //resistance  
7 disp('i') Resistance = '+string(R) +' ohm')
```

Scilab code Exa 1.44 voltage

```
1 //EXAMPLE 1-44 PG NO-36
2 R1=12; // Resistance
3 R2=0.2; // Resistance
4 R3=15;
5 V1=[-(R2*R3)+R1]/3; // voltage drop
6 disp('i') VOLTAGE = '+string(V1)+' V');
```

Scilab code Exa 1.46 current

```
1 //EXAMPLE 1-46 PG NO37
2 A=[85 -25;-25 135]; // Finding current
3 B=[60;100];
4 X=A\B; // current
5 disp('i')CURRENT = '+string(X)+' A')
6 I1=0.977;
7 I2=0.922; //WE HAVE FOUNDED I1 and I2
8 I3=I1-I2;
9 disp('ii')CURRENT = '+string(I3)+' A')
```

Scilab code Exa 1.47 Resistance

```
1 //EXAMPLE 1-48 PG NO-39-40
2 R1=4; // Resistance
3 R2=4; // Resistance
4 R3=8; // Resistance
5 RA=(R1*R2)/(R1+R2+R3);
6 disp('i')RESISTANCE = '+string(RA)+' ohm');
7 RB=(R1*R3)/(R1+R2+R3);
8 disp('ii')RESISTANCE = '+string(RB)+' ohm');
9 RC=(R2*R3)/(R1+R2+R3);
10 disp('iii')RESISTANCE = '+string(RC)+' ohm')
```

Scilab code Exa 1.48 Current

```
1 //EXAMPLE 1-48 PG NO-39-40
2 R1=6.8; // Resistance
3 R2=15;
4 R3=10;
5 RA=(R1*R2)/(R1+R2+R3);
6 disp('i')RESISTANCE = '+string(RA) +' ohm';
7 RB=(R1*R3)/(R1+R2+R3);
8 disp('ii')RESISTANCE = '+string(RB) +' ohm';
9 RC=(R2*R3)/(R1+R2+R3);
10 disp('iii')RESISTANCE = '+string(RC) +' ohm')
```

Scilab code Exa 1.50 voltage

```
1 //EXAMPLE 1-50 PG NO-45
2 TR=17/6; //TOTAL RESISTANCE
3 V=40; //VOLTAGE
4 I=5; //CURRENT
5 Vs=(TR*I)-V;
6 disp('i')VOLTAGE = '+string(Vs) +' V')
```

Scilab code Exa 1.51 Power

```
1 //EXAMPLE 1-51 PG NO-45-46
2 TR=2.05; //TOTAL RESISTANCE
3 V=2; //VOLTAGE
4 P=V^2/TR; //Power
5 disp('i')POWER = '+string(P) +' W')
```

Scilab code Exa 1.52 equivalent inductance

```
1 //EXAMPLE 1-52      PG NO-46
2 L1=1;
3 L2=1;
4 L3=1;           //INDUCTANCE
5 DL1=[(L1*L2)+(L2*L3)+(L3*L1)]/(L1*L2*L3);
6 disp('i')DELTA INDUCTANCE = '+string(DL1)+ ' H')
7 L4=1.5;
8 L5=1.5;          // Inductance
9 L6=1.5;
10 L=[L4*(L5+L6)]/[L4+L5+L6];
11 disp('ii')INDUCTANCE = '+string(L)+ ' H')
```

Scilab code Exa 1.53 equivalent resistance

```
1 //EXAMPLE 1-53      PG NO-46-47
2 R1=200;          //RESISTANCE
3 R2=50;
4 R3=30;
5 R4=20;
6 Rab=[R1*(R2+R3+R4)]/(R1+R2+R3+R4);           //
   equivalent   resistance
7 disp('i')RESISTANCE = '+string(Rab)+ ' ohm')
```

Chapter 2

single phase AC Circuits

Scilab code Exa 2.1 average value RMS Value Form Factor Peak Factor RMS Value of s

```
1 //EXAMPLE-2-1 EXAMPLE
      -59
2 t=0.5;
3 x=115;
4 z=310.6           //time
5 A.V=0.2*x;    //average value
6 R.M.S=(1/10)*z;          //rms value
7 F=R.M.S/A.V;        //form factor
8 P.F=60/R.M.S;      //peak factor
9 S=60/(2)^0.5;       //rms value of
                      sine wave
10 disp('i)R.M.S = '+string (R.M.S)+ ' V')
11 disp('i) average value = '+string (A.V)+ ' V')
12 disp('i)form factor = '+string (F)+ ' ')
13 disp('i) peak factor = '+string (P.F)+ ' ')
14 disp('i)sine wave = '+string (S)+ ' V')
```

Scilab code Exa 2.3 Form Factor Peak Factor

```

1      //EXAMPLE 2-3    PG NO-59-60
2 Vm=1;
3 AV1=0.318*Vm;           // avegare value
4 RMS1=0.5*Vm;           //RMS value
5 FF1=RMS1/AV1;           //Form Factor
6 PF1=Vm/RMS1;           //Peak Factor
7 AV2=0.637*Vm;           //Average value
8 RMS2=0.707*Vm;           //RMS value
9 FF2=RMS2/AV2;           //Form Factor
10 PF2=Vm/RMS2;           //Peak Factor
11 disp('i)Form Factor = '+string(FF1)+')
12 disp('i)peak Factor = '+string(PF1)+')
13 disp('i)Form Factor = '+string(FF2)+')
14 disp('i)PEAK Factor = '+string(PF2)+')

```

Scilab code Exa 2.7 addition and substraction

```

1          //EXAMPLE 2-7          PG NO
2          64-65
3 V1=24.15+%i*6.47;           //VOLTAGE
4 V2=7.5+;%i*12.99;           //VOLTAGE
5 X=V1+V2;                   //ADITION fo v1&v2
6 disp('i)ADITION is in rectangular form = '+string
(X)+ ' V')
7 X1=V1-V2;                   //subsractio of
                               v1&v2
8 disp('i)substration is in rectangular form = '+
      string (X1)+ ' V')

```

Scilab code Exa 2.8 ADDITION SUBSTRACTION MULTIPLICATION DIVISION

```

1          //EXAMPLE 2-8          PG
2          NO-65

```

```

2 A=3+%i*1;
3 B=4+%i*3;
4 X=A+B; //ADDITION
5 Y=A-B; //SUBTRACTION
6 Z=A*B; //MULTIPLICATION
7 U=A/B; //DIVISION
8 V=A^4;
9 P=B^(1/3);
10 disp('ii') ADDITION (A+B) is in polar form = '+
      string (X) +' ohm ');
11 disp('ii') SUBTRACTION (A-B) is in polar form =
      '+string (Y) +' ohm ');
12 disp('ii') MULTIPLICATION (A*B) is in polar form
      = '+string (Z) +' ohm ');
13 disp('ii') DIVISION (A/B) is in polar form =
      '+string (U) +' ohm ');
14 disp('ii') SQUARE OF A(A^4) is in polar form =
      '+string (V) +' ohm ');
15 disp('ii') CUBE ROOT OF B (B^(1/3)) is in polar
      form = '+string (P) +' ohm ');

```

Scilab code Exa 2.9 Rate of change of current

```

1 //EXAMPLE 2-9
                           PG NO-65
2 t1=0.0025; //time
3 t2=0.005; //time
4 t3=0.01; //time
5 i1=10*314.16*cos(314.16*t1); //
      i1 is derivatives of i wrt t;
6 disp('i') Current = '+string (i1)+'A ');
7 i2=10*314.16*cos(314.16*t2);
8 disp('ii') Current = '+string (i2)+'A ');
9 i3=10*314.16*cos(314.16*t3);
10 disp('iii') Current = '+string (i3)+'A ');

```

Scilab code Exa 2.10 rms

```
1 //EXAMPLE 2-10 PG NO-66
2 I1=5; //current
3 I2=7.071; //current
4 RMS=(I1*I1+I2*I2)^0.5; //resultant
    rms value
5 disp('i') RMS = '+string(RMS) +'A')
```

Scilab code Exa 2.11 INSTANTANEOUS VALUE

```
1 //EXAMPLE 2-11 PG NO-66
2 W=314.16;
3 PV=14.14; //PEAK VALUE
4 t=0.0025; //TIME
5 i=PV*sin(W*t); //CURRENT
6 T=0.0175; //TOTAL TIME
7 I=PV*sin(W*T);
8 disp('ii') Currnt (i) is = '+string(i) + ')
;
9 disp('ii') Currnt (I) is = '+string(I) + ')
;
```

Scilab code Exa 2.12 current

```
1 //EXAMPLE 2-12 PG NO-66-67
2 W1=80*%pi; //womega
3 W2=100*%pi;
4 PV=14.14; //peak value
```

```

5 t1=0.025;           //time
6 t2=0.05;
7 t3=0.075;
8 I1=PV*( cos(80*pi*t1)+cos(100*pi*t1));
    //current
9 I2=PV*( cos(80*pi*t2)+cos(100*pi*t2));
    //current
10 I3=PV*( cos(80*pi*t3)+cos(100*pi*t3));
    //current
11 disp('ii')    Currnt (I) is = '+string(I1) +' A'
    );
12 disp('ii')    Currnt (I) is = '+string(I2) +' A
    );
13 disp('ii')    Currnt (I) is = '+string(I3) +' A
    );

```

Scilab code Exa 2.13 Average Value of Voltage

```

1 //EXAMPLE 2-13          PG NO-67
2 T=20*10^-3;           //TIME PERIOD
3 Ta=300*10^-3;         //TOTAL AREA
4 A=(Ta)/T;             //AVERAGE VALUE
5 disp('ii')    AVERAGE VALUE (A) is = '+string(A)
    +' V ');

```

Scilab code Exa 2.14 Effective Value Form Factor

```

1 //EXAMPLE 2-14          PG NO-67
2 Ta=5;                 //TOTAL AREA
3 T=20*10^-3;           //TIME
4 Av=Ta/T;              //AVERAGE VALUE
5 Ev=[Av]^0.5;          //EFFECTIVE VALUE
6 FF=Ev/15;             //FORM FACTOR

```

```

7 disp('ii) AVERAGE VALUE (Av) is = '+string (Av
     ) + ' ');
8 disp('ii) EFFECTIVE VALUE (Ev) is = '+string (
     Ev) + ' V ');
9 disp('ii) FORM FACTOR (FF) is = '+string (FF)
     + ' ');

```

Scilab code Exa 2.15 Average Value Effective Value Form Factor

```

1 Eav=50;                                //in volts
2 T=2;                                     //time
3 E=[(1/T)*2500*2.66]^0.5;                //energy
   //integrate ('0','t',2)=2.66
4 disp('i) Energy = '+string (E)+ 'V ');
5 FF=E/Eav;                               //form
   factor
6 disp('i) Form Factor = '+string (FF)+ ' ');

```

Scilab code Exa 2.16 ENERGY FORM FACTOR

```

1                                         //EXAMPLE 2-16          PG
                                         NO 68
2 Eav=2.5;                                //AVERAGE ENERGY
3 E=8.333;
4 disp('i) ENERGY (E) is = '+string (sqrt(E)) +
     V ');
5 FF=sqrt(E)/Eav;
6 disp('ii) Form Factor (FF) is = '+string (FF)
     + ' ');

```

Scilab code Exa 2.17 RMS

```
1 //EXAMPLE 2-17          PG NO-69
2 I1=10;                  //CURRENT
3 I2=-4;
4 I3=2;
5 I4=0;
6 T=8;                   //TIME
7 Irms=[(I1*I1*2)+{I2*I2*2}+{I3*I3*2}+{I4*I4*2})/T
   ]^0.5;                //RMS
8 disp('i')  CURRENT R.M.S (Irms) is = '+string(
   Irms) +' A');
```

Scilab code Exa 2.20 Voltage

```
1 //EXAMPLE 2-20          PG NO-70
2 T=0.03;                 //TIME
3 // (1000*integrate('0','t',0.01,0.01))^2=-0.333
4 //100*integrate('0.01','t',0.02,0.02)=-1
5 //integrate('0.02','','',0.03,0.03)]=0
6 V=(-0.33-1)/T;
7 disp('i') Voltage (V) is = '+string(V) +' V ');
8 disp('i') Square Root of Voltage (V) is = '+
   string(sqrt(-V)) +' seconds');
```

Scilab code Exa 2.21 Voltage

```
1 //EXAMPLE 2-21          PG NO-70
2 T=0.05;                 //TIME
3 // (400*integrate('0','t',0.025,)) ^2=--0.8333
4 //100*integrate('0.01','t',0.02,0.02)=-1.738
```

```

5 V=(-0.833-1.738*10^-86)/T;
6 disp('i) Voltage (V) is = '+string (V) +' V ');
7 disp('i) Square Root of Voltage (V) is = '+
      string (sqrt(-V)) +' seconds ');

```

Scilab code Exa 2.22 Average

```

1 //EXAMPLE 2-22 PG NO-70-71
2 A=%pi/2;
3 // integrate(wt)=%pi/6
4 Eavg=1/A*(%pi+%pi)/6;
5 disp('i) Average Energy (Eavg) is = '+string (
    Eavg) +' Em ');

```

Scilab code Exa 2.23 Average Energy

```

1 //EXAMPLE 2-23 PG NO-71
2 A=%pi/2;
3 // [integrate('0',wt,%pi
// /3)]^2=%pi/9
4 // integrate('%pi/3',wt,%pi
// /2)=%pi/6;
5 E=1/A*[(%pi/9)+(%pi/6)];
6 disp('i) Energy (E) is = '+string (E) +' ');
7 disp('ii) Square Energy (E) is = '+string (sqrt(
    E)) +' ');
8 FF=[sqrt(E)*3]/2;
9 disp('iii) FORM FACTOR (FF) is = '+string (FF)
    +' ');

```

Scilab code Exa 2.24 Current

```
1 //EXAMPLE 2-24 PG NO 71
2 // integration of is=1008sinQ^2=0.5
3 I=150 //CURRENT
4 disp('i) CURRENT (I^2) is = '+string(I) +' A '
      );
5 disp('ii) CURRENT (I) is = '+string(sqrt(I)) +
      ' A');
```

Scilab code Exa 2.25 VOLTAGE

```
1 //EXAMPLE 2-25 PG NO-72
2 V1=50+%i*0;
3 V2=37.5-%i*64.95;
4 X=V1+V2; //ADDITION OF V1&V2
5 disp('ii) ADDITION (X) is in polar form = '+
      string(X) +' V');
```

Scilab code Exa 2.26 Reading of moving coil Reading of hot wire Total Power Power

```
1 //EXAMPLE 2-26 PG NO-72
2 V=200;
3 R=100;
4 R1=500;
5 R2=0.9009; // resistance
6 RMS1=V/(R+R); //RMS
7 disp('ii) CURRENT R.M.S in forward (R.M.S.1) is
      = '+string(RMS1) +' A ');
8 RMS2=-V/(R+R1);
9 disp('ii) CURRENT R.M.S in Backward (R.M.S.2) is
      = '+string(RMS2) +' A ');
10 I1=RMS1*R2; // Current
```

```

11 disp('ii) Average CURRENT in forward (I1) is      =
      '+string(I1) +' A ');
12 I2=RMS2*R2;
13 disp('ii) Average CURRENT in Backward (I2) is
      = '+string(I2) +' A ');
14 A=[I1+I2]/2;                                     //Ammeter
15 disp('ii) Reading of moving coil ammeter (A) is
      = '+string(A) +' A ');
16 H.A=[0.5*[RMS1+(RMS2)^2]]^0.5;                //
      HOT AMMETER
17 disp('ii) Reading of hot wire ammeter (H.A) is
      = '+string(H.A) +' A ');
18 P=0.5*[(RMS1*V)+(RMS2*RMS2*600)];            //
      /POWER
19 disp('ii) TOTAL AVERAGE POWER (P) is      = '+
      string(P) +' W ');
20 P1=0.5*[(RMS1*R)+(RMS2*RMS2*R1)];
21 disp('ii) TOTAL POWER dissipated in rectifier (P)
      ) is      = '+string(P1) +' W ');

```

Scilab code Exa 2.27 CURRENT POWER DISSIPATED INSTANTANEOUS CURRENT

```

1           //EXAMPLE 2-27 PG NO 74
2 F=50
3 V=230;          //voltage
4 R=20;           //resistance
5 I=V/R;          //current
6 P=V*I;          //power
7 Im=I*1.414;    //Maximum current
8 W=2*pi*F;
9 disp(' current is      = '+string(I) +' A ');
10 disp(' POWER is      = '+string(P) +' W ');
11 disp(' MAXIMUM CURENT is      = '+string(Im) +' A ');
12 disp(' W is      = '+string(W) +' ');

```

Scilab code Exa 2.28 FREQUENCY

```
1      //EXAMPLE 2-28 PG NO-76
2 F=50;    //Frequency
3 L=0.2;   //inductance
4 XL1=500;
5 XL=(2*%pi*F*L);
6 f=XL1/(2*%pi*L);           //FREQUENCY
7 disp(' XL  is  = '+string(XL)+ ' ohms');
8 disp(' frequency  is  = '+string(f)+ ' Hz');
```

Scilab code Exa 2.29 Capacitive Reactance susceptance and current

```
1      //EXAMPLE 2-29 PG NO=77-78
2 V=230;
3 F=50;        //Frequency
4 C=10*10^-6;  //Capacitor
5 Xc=1/(%pi*2*F*C);
6 Bc=1/Xc;
7 I=V/Xc;          //susceptance current
8 disp(' Xc  is  = '+string(Xc)+ ' ohms');
9 disp(' Bc  is  = '+string(Bc)+ ' siemens');
10 disp(' Current  is  = '+string(I)+ ' A');
```

Scilab code Exa 2.30 Impedance Admittance Current Power Factor Active power Reacti

```
1      //EXAMPLE 2-30      PG NO
2 V=230+%i*0;
```

```

3 F=50;
4 L=0.03;
5 R=20;
6 XL=2*pi*F*L;
7 disp('i) INDUCTANCE (XL) is in polar form = '+
      string(XL) +' ohm ');
8 Z=R+%i*XL;
9 disp('ii) IMPEDANCE (Z) is in polar form = '+
      string(Z) +' ohm ');
10 Y=1/Z;
11 disp('iii) ADMITTANCE (Y) is in polar form = '+
      string(Y) +' siemens ');
12 I=V/Z;
13 disp('iv) CURRENT (I) is in polar form = '+
      string(I) +' A ');
14 Vr=I*R;
15 disp('v) VOLTAGE (Vr) is in polar form = '+
      string(Vr) +' V ');
16 VL=%i*XL*I;
17 disp('vi) VOLTAGE (VL) is in polar form = '+
      string(VL) +' V ');
18 Q=25.23; //TETA
19 PF=cos(Q);
20 disp('vi) POWER FACTOR (PF) is = '+string(PF)
      +' lagging ');
21 P=V*I*cos(Q); //ACTIVE POWER
22 disp('vi) ACTIVE POWER (P) is in polar form = ,
      +string(P) +' W ');
23 q=V*I*sin(Q);
24 disp('vi) REACTIVE POWER (q) is in polar form =
      '+string(q) +' W ');
25 S=230*10.4;
26 disp('vi) APPARENT POWER (S) is in polar form =
      '+string(S) +' VA ');

```

Scilab code Exa 2.31 Current Apparent Power Active Power

```
1 //EXAMPLE 2-31 PG NO=82
2 Z1=20.15+%i*15.18;
3 Z2=6.99+%i*17.29;
4 Z=Z1+Z2;                                //impedance
5 V=230+%i*0;
6 I=V/Z;                                    //Current
7 PF=0.64;                                  //Power Factor
8 S=V*I;                                    //Apparent Power
9 P=S*PF;                                   //Active Power
10 disp(' Impedance is in rectangular form = '+string(
      Z)+ ' ohm');
11 disp(' current is in rectangular form = '+string(
      I)+ ' A');
12 disp(' S is in rectangular form = '+string(S)+ ' VA');
13 disp(' POWER is in rectangular form = '+string(P)+ ' W');
```

Scilab code Exa 2.32 Active Power Current Voltage

```
1 //EXAMPLE 2-32      PG NO-83
2 cos30=0.866;
3 sin30=0.5;
4 E1=141.42+%i*0;
5 E2=144.566+%i*11.976;
6 V=E1+141.42*(cos30 * sin30 );
7 disp('1) Voltage is in rectangular form = '+
      string(V)+ ' W');
8 Z=8+%i*6;                                //IMPEDANCE
9 I=V/Z;
10 disp('1) Current is in rectangular form = '+string(
      I)+ ' A');
11 P=I*V*0.743;
```

```
12 disp(' POWER is in rectangular form = '+string(P)
+ ' W');
```

Scilab code Exa 2.33 Impedance Admittance Current Power Factor Apparent Power Active Power

```
1 //EXAMPLE 2-33 PG NO-84-85
2 V=230+%i*0; //Voltage
3 F=50; //Frequency
4 C=10^-4; //Capacitor
5 R=10; //Resistance
6 XC=1/[2*pi*F*C]; //Capacitor
7 disp('i) CAPACITOR (XC) is in polar form = '+
    string(XC) +' ohm ');
8 Z=R-%i*XC; //Impedance
9 disp('ii) IMPEDANCE (Z) is in polar form = '+
    string(Z) +' ohm ');
10 Y=1/Z; //Admittance
11 disp('iii) ADMITTANCE (Y) is in polar form = '+
    string(Y) +' siemens ');
12 I=V/Z; //current
13 disp('iv) CURRENT (I) is in polar form = '+
    string(I) +' A ');
14 Vr=I*R; // Voltage
15 disp('v) VOLTAGE (Vr) is in polar form = '+
    string(Vr) +' V ');
16 VC=%i*XC*I //Voltage
17 disp('vi) VOLTAGE (VL) is in polar form = '+
    string(VC) +' V');
```

Scilab code Exa 2.34 Impedance Power Factor Power Consumed

```
1 //EXAMPLE 2-34 PG NO
-85
```

```

2 V=80+%i*60;                                // voltage
3 I=-4+%i*10;                                 // current
4 Z=V/I;                                       // Impedance
5 PF=0.26;                                     // power factor
6 P=V*I*PF;                                    // Power
7 disp(' IMPEDANCE    is in rectangular form = '+string
      (Z)+ ' ohm');
8 disp(' POWER    is in rectangular form    = '+string(P)
      + ' W');

```

Scilab code Exa 2.35 Maximum Charge and Energy

```

1 //EXAMPLE-2-35          PG
      NO-86
2 Vr=100;                                     //VOLTAGE
3 P=300;                                       //POWER
4 I=P/Vr;                                      //CURRENT
5 V=240;                                       //voltage
6 F=50;                                         //frequency
7 Z=V/I;                                       //IMPEDANCE
8 R=Vr/I;
9 Xc=[Z^2-R^2]^0.5;
10 C=1/[2*pi*Xc];                            //CAPACITOR
11 Vc=[(V*V)-(Vr*Vr)]^0.5;
12Vm=sqrt(2)*Vc;
13 Qm=(sqrt(2)*Vc)*(C);                      //CHARGE
14 Em=0.5*[Xc*Vm*Vm];                        //MAXIMUM ENERGY
15 disp('i) CURRENT (I) is = '+string(I) +' A ')
     );
16 disp('ii) IMPEDANCE (Z) is = '+string(Z) +' ohm ');
17 disp('iii) RESISTANCE (R) is = '+string(R) +' ohm ');
18 disp('i) CAPACITOR (Xc) is = '+string(Xc) +' ohm ');

```

```

19 disp('i') CAPACITOR (C) is      = '+string (C) +' F
   ') ;
20 disp('i') VOLTAGE (Vc) is      = '+string (Vc) +' V
   ') ;
21 disp('i') MAXIMUM VOLTAGE (Vm) is      = '+string (Vm
   ) +' V ') ;
22 disp('i') MAXIMUM CHARGE (Qm) is      = '+string (Qm)
   +' C ') ;
23 disp('i') MAXIMUM ENERGY (Em) is      = '+string (Em)
   +' J ') ;

```

Scilab code Exa 2.36 XL XC Current Power Factor Apparent Power Active Power Reacti

```

1 //EXAMPLE 2-36      PG NO-87
2 F=50;           //FREQUENCY
3 L=0.2;          //INDUCTANCE
4 C=150*10^-6;    //CAPACITOR
5 R=20;
6 V=230;
7 XL=2*pi*L*F;
8 disp('i') INDUCTANCE (XL) is      = '+string (XL) +' ohm ') ;
9 XC=1/(2*pi*F*C)
10 disp('i') CAPACITOR (Xc) is      = '+string (XC) +' ohm ') ;
11 Z=R+%i*(XL-XC)
12 disp('i') IMPEDANCE (Z) is      in polar form = '+
   string (Z) +' ohm ') ;
13 I=V/Z;          //CURRENT
14 disp('i') CURRENT (I) is      in polar form = '+
   string (I) +' ohm ') ;
15 AP=V*I;          //APPARENT POWER
16 disp('i') Apparent Power (AP) is      in polar form = '+
   string (AP) +' VA ') ;
17 P=V*I*0.433;      //active power

```

```

18 disp('i) ACTIVE POWER (P) is in polar form = '
      +'string (P) +' W ');
19 Q=V*I*0.9013; //Reactive Power
20 disp('i) Reactive Power (Q) is in polar form =
      +'string (Q) +' vars ');

```

Scilab code Exa 2.37 active power impedance

```

1 //EXAMPLE 2-37 PG NO-88
2 Xc=4;
3 XL=6;
4 R=2; //RESISTANCE
5 v=8.48+%i*30;;
6 Z=R+%i*(XL-Xc); //IMPEDANCE
7 V=v;
8 I=V/Z; //CURRENT
9 VL=%i*I*XL;
10 Vc=-%i*I*Xc;
11 P=V*I*0.707; //ACTIVE POWER
12 disp('i) Active Power = '+string(P)+' W');
13 disp('ii) Impedance = '+string(Z)+' ohm');
14 disp('iii) Current is = '+string(I)+' A');
15 disp('iv) VL is = '+string(VL)+' V');
16 disp('v) Vc is = '+string(Vc)+' V');

```

Scilab code Exa 2.38 Current Voltage

```

1 //EXAMPLE 2-38 PG N0-88-89
2 Z=12-%i*5;
3 V=100; //VOLTAGE
4 I=V/Z; //CURRENT
5 disp('i) CURRENT (I) is in polar form = '+
      string (I) +' A ');

```

```

6 Z1=4+%i*3;
7 Z2=6-%i*8;                                //impedance
8 V1=I*Z1;
9 disp('i') voltage (V1) is in polar form = '+
      string (V1) +' V ');
10 V2=I*Z2;                                 //voltage
11 disp('i') voltage (V2) is in polar form = '+
      string (V2) +' V ');
12 V3=2*I;                                 //voltage
13 disp('i') voltage (V3) is in polar form = '+
      string (V3) +' V ');
14 P=V*I*0.9230;                           //ACTIVE POWER
15 disp('i') Active Power (P) is in polar form = '+
      string (P) +' W ');

```

Scilab code Exa 2.39 1 Power factor 2 Apparent Reactive Active Power

```

1          //EXAMPLE-2-39      PG NO-89
2 V=7.07;
3 I=4.24;
4 W=500;
5 S=V*I;
6 cosQ=0.6428;
7 sinQ=0.766;
8 P=S*cosQ;                            //ACTIVE POWER
9 Q=S*sinQ;                            //REACTIVE POWER
10 Z=V/I;                               //IMPEDANCE
11 R=Z*cosQ;                            //RESISTANCE
12 Xc=Z*sinQ;                           //Xc
13 C=1/(W*Xc);                          //CAPACITOR
14 P2 =S*(cosQ-1);                     //NEGATIVE PEAK POWER
15 P3 =S*(cosQ+1);                     //POSITIVE PEAK POWER
16 P1=(P3 +P2)/2;                      // POWER
17 S1=(P3-P1);                         // apparent power
18 disp(' S is = '+string(S)+ ' VA');

```

```

19 disp(' ACTIVE POWER is = '+string(P)+' W');
20 disp(' REACTIVE POWER is = '+string(Q)+' VAr');
21 disp(' IMPEDANCE is = '+string(Z)+' ohm');
22 disp(' RESISTANCE is = '+string(R)+' ohm');
23 disp(' Xc is = '+string(Xc)+' ohm');
24 disp(' CAPACITOR is = '+string(C)+' F');
25 disp(' POWER CURVE is = '+string(P2)+' W');
26 disp(' POWER CURVE is = '+string(P3)+' W');
27 disp(' POWER is = '+string(P1)+' W');
28 disp(' S is = '+string(S1)+' VA');

```

Scilab code Exa 2.40 Voltage across v1 v2 Impedance Admittance Power factor

```

1 //EXAMPLE 2-40 PG NO
          -89-90
2 V1=52.33-%i*34.15878;
3 Z1=7.5-%i*9.999;           //IMPEDANCE
4 Z2=3.488+%i*12;           //IMPEDANCE
5 Z3=11.99+;%i*5;
6 V2=[Z2/Z1]*V1;
7 disp('i) voltage (V2) is in polar form = '+
      string(V2)+', V ');
8 V3=[Z3/Z1]*V1;             //voltage
9 disp('ii) voltage (V3) is in polar form = '+
      string(V3)+', V ');
10 V=V1+V2+V3;               //total voltage
11 disp('i) voltage (V) is in polar form = '+
      string(V)+', V ');
12 Z=Z1+Z2+Z3;               //Total Impedance
13 disp('i) IMPEDANCE (Z) is in polar form = '+
      string(Z)+', V ');
14 Y=1/Z;                     //Admittance
15 disp('i) Y (Y) is in polar form = '+string(Y)
      +', ohm ');

```

Scilab code Exa 2.41 Impedance

```
1 //EXAMPLE 2-41    PG NO-90
2 F1=50;                      //frequency
3 W=(2*%pi*F1);
4 L=1;                        //inductar
5 C=10^-6;                    //capacitor
6 XL1=W*L;
7 Xc1=1/(W*C);
8 Z1=XL1-Xc1;
9 F2=1000;
10 XL2=(2*%pi*F2*L);
11 Xc2=1/(2*%pi*F2*C);
12 Z2=(XL2-Xc2);             //impedance
13 disp(' IMPEDANCE(Z1) is = '+string(Z1)+ ' ohm');
14 disp(' IMPEDANCE(Z2) is = '+string(Z2)+ 'ohm');
15 disp(' XL1 is = '+string(XL1)+ ' ohm');
16 disp(' Xc1 is = '+string(Xc1)+ ' ohm');
17 disp(' XL2 is = '+string(XL2)+ ' ohm');
18 disp(' Xc2 is = '+string(Xc2)+ ' ohm');
```

Scilab code Exa 2.42 Resistance Inductance

```
1 //EXAMPLE 2-42    PG NO-90
2 F=50;                      //frequency
3 C=100*10^-6;               //capacitor
4 W=(2*%pi*F);
5 Xc=1/(W*C);
6 R=19.1;                     //resistance
7 XL=25.46;                  //inductance
8 L=XL/(2*%pi*F);
9 disp(' Xc is = '+string(Xc)+ ' ohms');
```

```
10 disp(' INDUCTANCE is = '+string(L)+ ' H');
```

Scilab code Exa 2.43 Power Factor

```
1 //EXAMPLE 2-43 PG NO  
-91  
2 R1=6; //RESISTANCE  
3 R2=3; //RESISTANCE  
4 R3=8; //RESISTANCE  
5 Z1=7; //IMPEDANCE  
6 Z2=5; //IMPEDANCE  
7 Z3=10; //IMPEDANCE  
8 V=7;  
9 I=1;  
10 PF1=R1/Z1; //POWER FACTOR  
11 disp('i) Power Factor (PF1) is = '+string(PF1  
) +' );  
12 PD1=V*I*0.857; //POWER dissipated  
13 disp('i) Power Dissipated (PD1) is = '+string  
(PD1) +' W );  
14 PF2=R2/Z2;  
15 disp('iii) Power Factor (PF2) is = '+string (PF2) +' W );  
16 PD2=Z2*PF2;  
17 disp('i) Power Dissipated (PD2) is = '+string  
(PD2) +' W );  
18 PF3=R3/Z3;  
19 disp('iii) Power Factor (PF3) is = '+string (PF3) +' W );  
20 PD3=Z3*PF3;  
21 disp('i) Power Dissipated (PD3) is = '+string  
(PD3) +' W );  
22 A=[Z1^2-R1^2]^0.5;  
23 disp('i) REACTANCE OF COIL (A) is = '+string (A) +' ohm );
```

```

24 B=[Z2^2-R2^2]^0.5;
25 disp('i')    REACTANCE OF COIL (B) is      = '+string (
      B) +' ohm ';
26 C=[Z3^2-R3^2]^0.5;
27 disp('i')    REACTANCE OF COIL (C) is      = '+string (
      C) +' ohm ';
28 TR=R1+R2+R3;
                                //  

      TOTAL RESISTANCE
29 disp('i')    TOTAL RESISTANCE (TR) is      = '+string (
      TR) +' ohm ';
30 TRC=A+B+C;
                                //  

      TOTAL RACTANCE
31 disp('i')    TOTAL REACTANCE (TRC) is      = '+string (
      TRC) +' ohm ';
32 TI=[TR^2+TRC^2]^0.5;
                                //TOTAL  

      IMPEADNCE
33 disp('i')    TOTAL IMPEDANCE (TI) is      = '+string (
      TI) +' ohm ';
34 PF=TR/TI;
                                //  

      POWER FACTOR
35 disp('i')    POWER FACTOR (PF) is      = '+string (PF)
      +' lagging ';

```

Scilab code Exa 2.44 Resistance Capacitance

```

1                                     //EXAMPLE   2-44          PG
                                         NO 91-92
2 R=20;                               //Resistance
3 V=125;                             //VOLTAGE
4 I=2.2;                            //CURRENT
5 Z=V/I;                            //IMPEDANCE

```

```

6 disp('i) Impedance is = '+string(Z)+');
7 F=50; //FREQUENCY
8 XC=53.18
9 C=1/[2*pi*F*XC]; //CAPACITANCE
10 disp('ii) Capacitor is = '+string(C)+' F');

```

Scilab code Exa 2.45 Power Inductance

```

1 //EXAMPLE 2-45 PG NO-92
2 I=10; //CURRENT
3 R=5; //RESISTANCE
4 P=I*I*R; //POWER
5 IL=250; //IRON LOSS
6 Z=20;
7 r=5;
8 F=50;
9 W=2*pi*F;
10 p1=750;
11 v=200; // voltage
12 L=(Z*Z-r*r)^0.5/W; // inductance
13 cosQ=p1/(v*I);
14 disp(' power is = '+string(P)+' W')
15 disp(' inductance is = '+string(L)+' H');
16 disp(' cos Q is = '+string(cosQ)+' lagging');

```

Scilab code Exa 2.46 P

```

1 //Example 2-46 PG NO-92
2 Z=50+%i*49.95; //IMPEDANCE
3 V=283; //VOLTAGE
4 T=1; //ASSUMING
5 i=(V/70.675)*[sin(100*pi-44.97)];

```

```

6 disp('i) Current (i) is in polar form = '+
      string (i) +' A');
7 P=(V/sqrt(2))*(4/sqrt(2))*(0.707);
8 disp('ii) POWER (P) is      = '+string (P) +' W ')
;

```

Scilab code Exa 2.47 RMS

```

1 //EXAMPLE 2-47 PG NO 92
2 V=100/sqrt(2); //VOLTAGE
3 F=100; //FREQUENCY
4 L=0.018; //INDUCTANCE
5 XL=2*pi*F*L;
6 disp('i) INDUCTANCE (XL) is in polar form = '+
      string (XL) +' ohm ');
7 I=V/[(11.3+%i*11.3)]; //current
8 disp('ii) CURRENT (I) is in polar form = '+
      string (I) +' A ');
9 VR=I*10; //voltage
10 disp('i) Voltage Across Resister (VR) is      = '+
      string (VR) +' V ');

```

Scilab code Exa 2.49 current

```

1 //EXAMPLE 2-49 PG NO-93
2 K=0.35; //CONSTANT
3 L1=0.1; //INDUCTANCE
4 L2=0.2; //INDUCTANCE
5 M=K*(L1*L2)^0.5;
6 V=125; //VOLTAGE
7 F=50; //FREQUENCY
8 L=0.2; // TOTAL INDUCTANCE
9 I=V/(2*pi*F*L); //CURRENT

```

```

10 disp(' M is = '+string(M)+ ' H');
11 disp(' current is = '+string(I)+ ' A');

```

Scilab code Exa 2.51 Impedance admittance Current Power Factor Apparent Power active reactive power

```

1 //example 2-51 pg no-94
2 V=230+%i*0; //VOLTAGE
3 F=50; //FREQUENCY
4 C=10^-4; //CAPACITOR
5 R=10; //RESISTANCE
6 cos(72.56)=0.299;
7 XC=1/[2*pi*F*C];
8 disp('i) INDUCTANCE (XC) is = '+string(XC) +
      ' ohm ');
9 Z=R-%i*XC; // impedance
10 disp('i) IMPEDANCE (Z) is in rectangular form =
      '+string(Z) + ' ohm ');
11 Y=1/Z; // admittance
12 disp('i) ADMITTANCE (Y) is in rectangular form =
      '+string(Y) + ' ohm ');
13 I=V/Z; //CURRENT
14 disp('i) CURRENT (I) is in rectangular form =
      '+string(I) + ' A ');
15 PF=0.299; //POWER FACTOR
16 disp('i) POWER FACTOR (PF) is = '+string(PF) +
      ' leading ');
17 S=V*I; //APPARENT POWER
18 disp('i) APPARENT POWER (S) is IN rectangular
      FORM = '+string(S) + ' VA ');
19 P=V*I*0.3; //ACTIVE POWER
20 disp('i) ACTIVE POWER (P) is in rectangular form
      = '+string(P) + ' W ');
21 Q=V*I*-0.1315; //REACTIVE POWER
22 disp('i) REACTIVE POWER (Q) is in rectangular
      form = '+string(Q) + ' vars ');

```

```

23 Vr=I*R;
24 disp('i') VOLTAGE (Vr) is in rectangular form =
    '+string (Vr) +' );
25 Vc=-%i*I*XC;
26 disp('i') VOLTAGE (Vc) is = '+string (Vc) +' );

```

Scilab code Exa 2.52 Total Current power Factor

```

1 // EXAMPLE 2-53      PG NO-96
2 W=1000;
3 L=0.02;
4 XL=W*L;
5 Z=4.85;
6 V=(100/1.414);
7 I=(20.62/1.414);
8 cos(14.06)=0.97;    //
9 P=V*I*0.97;
10 z=1.18;
11 Leq=z/W;
12 disp(' XL is = '+string(XL)+ ' ohms ');
13 disp(' POWER is = '+string(P)+ ' W');
14 disp(' Leq is = '+string(Leq)+ ' H');

```

Scilab code Exa 2.53 Inductance Frequency

```

1 //EXAMPLE 2-53      PG NO=97
2 R=15;                  //RESISTANCE
3 V=240+%i*0;            //VOLTAGE
4 I=22.1;
5 Ir=V/R;                //CURENT
6 disp('i') CURRENT (Ir) is = '+string (Ir) + ' A
    ');

```

```

7 IL=[I^2-Ir^2]^0.5;
8 disp('i') CURRENT (IL) is = '+string(IL) +' A
   );
9 XL=V/IL;
10 disp('i') INDUCTANCE (XL) is = '+string(XL) +' ohm ';
11 L=XL/[2*pi*50];
12 disp('i') INDUCTANCE (L) is = '+string(L) +' H ';
13 IL1=[34^2-Ir^2]^0.5;
14 disp('i') INDUCTANCE (IL1) is = '+string(IL1)
   +' A ');
15 F=8/[2*pi*0.05];
16 disp('i') FREQUENCY (F) is = '+string(F) +' Hz ';

```

Scilab code Exa 2.54 Single Phase AC Circuits

```

1 //EXAMPLE 2-54 PG NO-98
2 C=159*10^-6;           //capacitor
3 F=50;                  //frequency
4 Xc=1/(2*pi*F*C);
5 Z=8.94;                //impedance
6 V=100;                 //voltage
7 I=V/Z;                 //Current
8 PF=0.894;              //power factor
9 S=V*I;
10 P=V*I*PF;
11 Q=V*I*(-0.447);
12 disp(' CURRENT is = '+string(P)+' A');
13 disp(' APPARENT POWER is = '+string(S)+' VA');
14 disp(' active power is = '+string(P)+' W');
15 disp(' reactive power is = '+string(Q)+' vars');

```

Scilab code Exa 2.55 Resistance

```
1 //EXAMPLE 2-55      PG NO-99
2
3 Q=72.4;
4 tan(Q)=3.1524;
5 W=3000;
6 C=35*10^-6;
7 Xc=1/[W*C];
8 R=3.1524*Xc
9 disp('i') CAPACITOR (XC) is = '+string(Xc) +' ohm ');
10 disp('i') RESISTANCE (R) is = '+string(R) +' ohm');
```

Scilab code Exa 2.56 Current Power Factor

```
1 //EXAMPLE 2-56      PG NO-99-100
2 V=230+%i*0;
3 R=15+%i*0;
4 L=%i*7.5;
5 Ir=V/R;
6 Z1=-%i*12
7 disp('i') CURRENT (Ir) is = '+string(Ir) +' A ');
8 IL=V/L;
9 disp('i') INDUCTANCE CURRENT (IL) is = '+string(IL) +' A );
10 Ic=V/Z1;
11 disp('i') CAPACITOR CURRENT (Ic) is = '+string(Ic) +' A );
12 I=Ir+IL+Ic;
```

```

13 disp('i')      CURRENT (I) is      = '+string (I) +' A
      ');
14 Z=V/I;
15 disp('i')      IMPEDANCE (Z) is      = '+string (Z) +' A
      ');
16 PF=0.8;
17 Leq=7.2/[2*%pi*50];
18 disp('i')      EQUIVALENT CURRENT (Ieq) is      = '+
      string (Leq) +' H ');

```

Scilab code Exa 2.57 Total Current Impedance Admittance Power factor Apparent Power

```

1 //EXAMPLE 2-57    PG N0-100-101
2 V=240+%i*0;
3 R=400+%i*0;
4 Z1=%i*50;
5 Z2=-%i*40;
6 IR=V/R;
7 disp('i')      CURRENT (IR) is      = '+string (IR) +' A
      ');
8 IL=V/Z1;
9 disp('i')      CURRENT (IL) is      = '+string (IL) +' A
      ');
10 IC=V/Z2;
11 disp('i')      CURRENT (IC) is      = '+string (IC) +' A
      ');
12 I=IR+IL+IC;
13 disp('i')      CURRENT (I) is      = '+string (I) +' A '
      );
14 Z=V/I;
15 disp('i')      IMPEDANCE (Z) is      = '+string (Z) +' ohms
      ');
16 Y=1/Z;
17 disp('i')      ADMITTANCE (Y) is      = '+string (Y) +' ohm
      ';

```

```

18 S=V*I;
19 disp('i) APPARENT POWER (S) is = '+string (S) +
      ' VA ');
20 P=V*I*0.448;
21 disp('i) ACTIVE POWER (P) is = '+string (P) +
      ' W ');
22 Q=V*I*-0.94;
23 disp('i) REACTIVE POWER (Q) is = '+string (Q) +
      ' vars ');

```

Scilab code Exa 2.58 Voltage Current power Factor Active Reactive Power

```

1 //EXAMPLE 2-58 PG NO
           -101-102
2 Z1=2+%i*3;
3 Z2=1-%i*5;
4 Z3=4+%i*2;
5 Zeq=[Z2*Z3]/[Z2+Z3];
6 disp('i) IMPEDANCE EQUVALENT (Zeq) is = '+
      string (Zeq) +' ohms ');
7 Z=Z1+Zeq;
8 disp('i) TOTAL IMPEDANCE (Z) is = '+string (Z) +
      +' ohm ');
9 V=10;
10 R=5.65+%i*1.588;
11 I=V/R;
12 disp('i) CURRENT (I) is = '+string (I) +' A ')
      ;
13 VBC=I*Zeq;
14 disp('i) VOLTAGE (VBC) is = '+string (VBC) +
      ' V ');
15 I2=VBC/Z2;
16 disp('i) CURRENT (I2) is = '+string (I2) +' A ')
      ;
17 I3=VBC/Z3;

```

```

18 disp('i) CURRENT (I3) is in polar form = '+
      string(I3) +' A ');
19 S=V*I;
20 disp('i) APPARENT POWER (S) is in polar form = ,
      +string(S) +' VA ');
21 P=V*I*0.963;
22 disp('i) ACTIVE POWER (P) is in polar form = +
      string(P) +' W ');
23 Q=V*I*-0.27;
24 disp('i) REACTIVE POWER (Q) is in polar form = ,
      +string(Q) +' vars ');

```

Scilab code Exa 2.59 Total Current Shunt Capacitor

```

1 //EXAMPLE 2-59 PG NO-103
2 C1=15.5*10^3;
3 L=1000;
4 V=230;
5 PL1=10;           //active load power
6 PL2=6;           //active load power
7 QL1=7.5;         //reactive load power
8 QL2=8;           //reactive load power
9 P=PL1+PL2;       //total active power
10 Q=QL1+QL2;      //total reactive power
11 AP=(P*P+Q*Q)^0.5; //total apparent power
12 I=(AP*L)/V;     //TOTAL CURRENT
13 Ic=(C1/V);
14 Xc=V/Ic;
15 K=16;
16 C=1/(2*pi*50*Xc);
17 I1=(L*K)/V;
18 disp(' total active power is = '+string(P)+ ' KW');
19 disp(' total reactive power is = '+string(Q)+ ' K var
      ');
20 disp(' total apparent power is = '+string(AP)+ ' KVA'

```

```

);
21 disp(' total current(I) is = '+string(P)+ ' A');
22 disp(' Ic is = '+string(P)+ ' A');
23 disp(' Xc is = '+string(Xc)+ ' ohm');
24 disp(' capacitor is = '+string(C)+ ' F');
25 disp(' current(I1) is = '+string(I1)+ ' A');

```

Scilab code Exa 2.60 Conductance Susceptance Current Power factor

```

1 //EXAMPLE 2-60 PG NO-103-104
2 Z1=6+%i*8;
3 V=230; // VOLTAGE
4 Y1=1/Z1;
5 disp('i) ADMITTANCE (Y1) is = '+string(Y1) +' siemens ');
6 G1=0.06;
7 B1=-0.08;
8 Z2=4-%i*3;
9 Y2=1/Z2;
10 disp('ii) ADMITTANCE (Y2) is = '+string(Y2) +' siemens ');
11 G2=0.16;
12 B2=0.12;
13 TL=G1+G2; //TOTAL CONDUCTANCE
14 disp('iii) TOTAL CONDUCTANCE (TL) is = '+string(TL) +' siemens ');
15 TS=B1+B2; //TOTAL SUSCEPTANCE
16 disp('iv) TOTAL SUSCEPTANCE (TS) is = '+string(TS) +' siemens ');
17 I1=V*Y1; // CURRENT
18 disp('v) CURRENT (I1) is = '+string(I1) +' A ');
19 I2=V*Y2;
20 disp('vi) CURRENT (I2) is = '+string(I2) +' A ');

```

```

21 TI=I1+I2; //TOTAL CURRENT
22 disp('vii) TOTAL CURRENT (TI) is = '+string(TI
    ) +' A ');
23 PF=cos(degree(10.3));
24 disp('i) POWER FACTOR (PF) is = '+string(PF) +
    ' leading ');

```

Scilab code Exa 2.61 admittance Impedance Total Current Power Factor Active Power

```

1 //EXAMPLE 2-61 PG NO
      -104-105
2 V=100+%i*0;
3 Zab=1.6+%i*7.2;
4 Yab=1/Zab;
5 disp('i) ADMITTANCE (Yab) is in polar form = '+
      string(Yab) +' siemens');
6 Zcd=4+%i*3;
7 Ycd=1/Zcd;
8 disp('i) ADMITTANCE (Ycd) is in polar form = '+
      string(Ycd) +' siemens');
9 Zef=6-%i*8;
10 Yef=1/Zef;
11 disp('i) ADMITTANCE (Yef) is in polar form = '+
      string(Yef) +' siemens');
12 Ybg=Yef+Ycd;
13 disp('i) ADMITTANCE (Ybg) is in polar form = '+
      string(Ybg) +' siemens');
14 Zbg=1/Ybg;
15 disp('i) IMPEDANCE (Zbg) is in polar form = '+
      string(Zbg) +' ohms');
16 TZ=1.6+%i*7.2+4.4+%i*0.8;
17 disp('i) TOTAL IMPEDANCE (TZ) is in polar form =
      '+string(TZ) +' ohms');
18 TI=V/TZ;
19 disp('i) TOTAL CURRENT (TI) is in polar form =

```

```

        '+string (TI) +' A ');
20 Icd=TI*[Zef/(Zcd+Zef)]
21 disp('i) CURRENT (Icd) is in polar form = '+
      string (Icd) +' A ');
22 Ief=TI*[Zcd/(Zcd+Zef)];
23 disp('i) CURRENT (Ief) is in polar form = '+
      string (Ief) +' A ');
24 Pab=TI*TI*1.6;
25 disp('i) POWER (Pab) is in polar form = '+
      string (Pab) +' W ');
26 Pcd=Icd*Icd*4;
27 disp('i) POWER (Pcd) is in polar form = '+
      string (Pcd) +' W ');
28 Pef=Ief*Ief*6;
29 disp('i) POWER (Pef) is in polar form = '+
      string (Pef) +' W ');
30 TP=Pab+Pcd+Pef;
31 disp('i) TOTAL POWER (TP) is in polar form = '+
      string (TP) +' W ');

```

Scilab code Exa 2.62 Current impedance Active Power TotalActive Power Power Factor

1	//EXAMPLE 2-62	PG NO
		–105–106
2 Z1=24+%i*18;		
3 Z2=24-%i*10;		
4 Z3=2-%i*0.148;		
5 R1=24;		
6 R2=24;		
7 R3=32;		
8 R4=16;		
9 V=2;		
10 v1=128.3;		
11 I=2;		
12 I3=32+%i*24;		

```

13 I4=16-%i*30;
14 Z=Z1+Z2;
15 disp('i) IMPEDANCE (Z) is in polar form = '+
      string (Z) +' ohms ');
16 I1=[Z2/(Z1+Z2)]*Z3;
17 disp('i) CURRENT (I1) is in polar form = '+
      string (I1) +' ohms ');
18 I2=[Z1/(Z1+Z2)]*Z3;
19 disp('i) CURRENT (I2) is in polar form = '+
      string (I2) +' ohms ');
20 P1=I1*I1*R1;
21 disp('i) POWER (P1) is in polar form = '+string
      (P1) +' W ');
22 P2=I2*I2*R2;
23 disp('i) POWER (P2) is in polar form = '+string
      (P2) +' W ');
24 P3=V*V*R3;
25 disp('i) POWER (P3) is in polar form = '+string
      (P3) +' W ');
26 P4=V*V*R4;
27 disp('i) POWER (P4) is in polar form = '+string
      (P4) +' W ');
28 P=P1+P2+P3+P4;
29 disp('i) TOTAL POWER (P) is in polar form = '+
      string (P) +' W ');
30 V1=I1*Z1;
31 disp('i) VOLTAGE (V1) is in polar form = '+
      string (V1) +' V ');
32 V2=V1;
33 disp('i) VOLTAGE (V2) is in polar form = '+
      string (V2) +' V ');
34 V3=I3*Z3;
35 disp('i) VOLTAGE (V3) is in polar form = '+
      string (V3) +' V ');
36 V4=I4*Z3;
37 disp('i) VOLTAGE (V4) is in polar form = '+
      string (V4) +' V ');
38 V=V1+V4+V3;

```

```

39 disp('i%') VOLTAGE (V) is in polar form = '+
      string (V) +' V ');
40 S=v1*I;
41 disp('i') Apparent Power (S) is      = '+string (S)
      +' VA ');
42 Q=S*0.0726;
43 disp('i') Reactive Power (Q) is      = '+string (Q) +
      ' Var ');

```

Scilab code Exa 2.63 Current Power Factor

```

1 //EXAMPLE 2-63    PG NO
                  -106-107
2 Z1=14+%i*48;
3 Z2=30+%i*40;
4 Z3=24+%i*70;
5 V=230+%i*0;
6 Y1=1/Z1;
7 disp('i') ADMITTANCE (Y1) is in polar form = '+
      string (Y1) +' siemens');
8 Y2=1/Z2;
9 disp('ii') ADMITTANCE (Y2) is in polar form = '+
      string (Y2) +' siemens');
10 Y3=1/Z3;
11 disp('iii') ADMITTANCE (Y3) is in polar form = '+
      string (Y3) +' siemens');
12 Y=Y1+Y2+Y3;
13 disp('i') ADMITTANCE (Y) is in polar form = '+
      string (Y) +' siemens');
14 Z13=29.763+%i*21.62;
15 Z14=10-%i*24;
16 X=Z13+Z14;
17 Y=18+%i*80;
18 A=8-%i*6;
19 disp('i') IMPEDANCE (X) is in polar form = '+

```

```

        string (X) + ' ohm') ;
20 Z=[{X*Y}/{X+Y}]+A ;
21 disp('i) IMPEDANCE (Z) is in polar form = '+
      string (Z) + ' ohm') ;
22 I=V/Z ;
23 disp('vi) CURRENT (I) is = '+string (I) +' A ')
      ;
24 S=V*I ;
25 disp('i) Apparent Power (S) is = '+string (S)
      +' VA ') ;
26 P=V*I*0.989 ;
27 disp('i) Active Power (P) is = '+string (P) +' W ')
      ;
28 Q=V*I*0.146 ;
29 disp('i) Reactive Power (Q) is = '+string (Q) +' Var ')
      ;

```

Scilab code Exa 2.64 Current in branch Total Current

```

1 ZA=15+%i*15.708 ;
2 ZB=20+%i*0 ;
3 V=200+%i*0 ;
4 IA=V/ZA ;
5 disp('i) CURRENT (IA) is = '+string (IA) +' A ')
      ;
6 IB=V/ZB ;
7 disp('ii) CURRENT (IB) is = '+string (IB) +' A ')
      ;
8 I=IA+IB ;
9 disp('vi) TOTAL CURRENT (I) is = '+string (I) +' A ')
      ;

```

Scilab code Exa 2.66 Power

1 //EXAMPLE 2-66 PG NO
 -108

```

2 I=15;
3 Z1=10+%i*15
4 Z2=6-%i*8;
5 I1=[I*Z2]/(Z1+Z2);
6 disp('ii) CURRENT (I1) is in polar form = '+
      string(I1) +' A ');
7 I2=(I*Z1)/(Z1+Z2);
8 disp('ii) CURRENT (I2) is in polar form = '+
      string(I2) +' A ');
9 P1=8.59^2*10;
10 disp('ii) Power (P1) is in polar form = '+
       string(P1) +' W ');
11 P2=15.49^2*6;
12 disp('ii) Power (P2) is in polar form = '+string
      (P2) +' W ');

```

Scilab code Exa 2.67 Branch Impedance Total Impedance Branch Current Total Current

1 //EXAMPLE 2-67 PG NO
 -108-109

```

2 Z1=5;
3 V=100+%i*200;
4 I1=16; //CURRENT
5 P1=I1*I1*Z1;
6 disp('i) POWER (P1) is = '+string (P1) +' W ');
7 P2=5000-P1;
8 disp('ii) POWER (P2) is = '+string (P2) +' W ')
      ;
9 Q1=-69.02;
10 cos(-69.02)=0.35;
11 Z2=Z1/0.358;
12 disp('iii) IMPEDANCE (Z2) is in polar form = '+
      string (Z2) +' ohms ');

```

```

13 X1=Z2*-0.933;
14 disp('i') (X1) is in polar form = '+string (X1)
    + ' ohms ');
15 Z3=5-%i*13.04;
16 I1=V/Z3;
17 disp('ii') CURRENT (I1) is in polar form = '+
    string (I1) + ' A ');
18 P3=3720;
19 I2=P3/(223.6*0.8);
20 disp('ii') CURRENT (I2) is in polar form = '+
    string (I2) + ' A ');
21 z2=8.6+%i*6.45;
22 I3=V/z2;
23 disp('ii') CURRENT (I3) is in polar form = '+
    string (I3) + ' A ');
24 I=I1+I3;
25 disp('ii') CURRENT (I) is in polar form = '+
    string (I) + ' A ');
26 Z=V/I;
27 disp('iii') IMPEDANCE (Z) is in polar form = '+
    string (Z) + ' ohms ')

```

Scilab code Exa 2.68 Total Power

```

1 //EXAMPLE 2-68
                  PG NO-109-110
2 V=100;
3 Y1=0.16+%i*0.12;
4 Y2=-%i*0.15;
5 I1=V*Y1;
6 disp('i') CURRENT (I1) is in polar form = '+
    string (I1) + ' A ');
7 I2=V*Y2;
8 disp('ii') CURRENT (I2) is in polar form = '+
    string (I2) + ' A ');

```

```

9 P=(V*I1*0.8)+(V*I2*0);
10 disp('iii) Power (P) is in polar form = '+string
      (P) +' W ');
11 I=I1+I2;
12 disp('ii) CURRENT (I) is in polar form = '+
      string (I) +' A ');

```

Scilab code Exa 2.69 Line Current Impedance Circuits Phase Angle

```

1                                //EXAMPLE 2-69    PG NO-110
2 F=50;
3 L=0.6;
4 R=100;
5 XL=(%pi*2*F*L)
6 disp('i) INDUCTANCE (XL) is      = '+string (XL) +
      ohm ');
7 V=230+%i*0;
8 IR=V/R;
9 disp('ii) CURRENT (IR) is in polar form = '+
      string (IR) +' A ');
10 IL=V/(0+%i*XL);
11 disp('iii) CURRENT (IL) is in polar form = '+
      string (IL) +' A ');
12 I=IR+IL;
13 disp('iv) CURRENT (I) is in polar form = '+
      string (I) +' A ');
14 P=V*I*cos(degree(27.9));
15 disp('v) POWER (P) is in polar form = '+string (
      P) +' W ');
16 Z=V/I;
17 disp('vi) IMPEDANCE (Z) is      = '+string (Z) +
      ohm ');
18 LEQ=41.39/(2*%pi*F);
19 disp('ii) INDUCTANCE (LEQ) is      = '+string (LEQ)
      +' H ');

```

Scilab code Exa 2.70 Current Impedance

```
1 //EXAMPLE 2-70      PG NO-110-111
2 ZA=-%i*227.36;           //IMPEDANCE
3 ZB=-%i*795.77;          //IMPEDANCE
4 ZC=500;                  //IMPEDANCE
5 V=230+%i*0;             //VOLTAGE
6 IA=V/ZA;                //CURRENT
7 disp('i) CURRENT (IA) is in polar form = '+
      string(IA) +' A ');
8 IB=V/ZB;
9 disp('i) CURRENT (IB) is in polar form = '+
      string(IB) +' A ');
10 IC=V/ZC;
11 disp('i) CURRENT (IC) is in polar form = '+
      string(IC) +' A ');
12 I=IA+IB+IC;
13 disp('i) CURRENT (I) is in polar form = '+string(
      I) +' A ');
14 P=V*I*0.334;
15 disp('i) POWER (P) is in polar form = '+string(
      P) +' W ');
16 Z=V/I;
17 disp('vi) IMPEDANCE (Z) is      = '+string(Z) +' 
      ohm');
```

Scilab code Exa 2.71 Power Power Factor

```
1 //EXAMPLE 2-71  PG NO-111
2 V=240;
3 cos (degree(62.74))=0.458;
```

```

4 Pm=V*2*0.458;
5 disp('i') POWER (Pm) is in rectangular form = '+
      string (Pm) +' W ');
6 I=(2*0.458+1.5)-%i*(2*0.89);
7 disp('i') CURRENT (I) is in rectangular form = '+
      string (I) +' A ')
8 P=V*3*0.805
9 disp('i') Power (P) is in rectangular form = '+
      string (P) +' W ')

```

Scilab code Exa 2.72 Power Factor Total volts Active Reactive power Overall Power

```

1 //EXAMPLE 2-72    PG NO 111
2 P.F=0.5;
3 cosQ=0.5;
4 sinQ=0.866;
5 V=552;
6 I=2.3;
7 v=240;
8 PF1=0.89;
9 P=v*I*PF1;
10 Q=(V*V-P*P)^0.5;
11 disp(' ACTIVE POWER is = '+string(P)+' W');
12 disp(' REACTIVE POWER is = '+string(Q)+' vars ');

```

Scilab code Exa 2.73 Inductance Capacitance

```

1 //EXAMPLE 2-73    PG NO-112
2 R=44.074;
3 V=230;
4 I=3.05;
5 Z=V/I;
6 Y=2.475;

```

```

7 X=(Z*Z-R*R)^0.5;
8 L=X/(2*pi*50)
9 Xc=V/Y;
10 C=1/(2*50*Xc*pi);
11 disp(' impedance is = '+string(Z)+' ohm');
12 disp(' X is = '+string(X)+' W');
13 disp(' inductance is = '+string(L)+'H ');
14 disp(' Xc is = '+string(Xc)+' ohm');
15 disp(' Capacitor is = '+string(C)+' F');

```

Scilab code Exa 2.74 Current in each branch Total Current Power Factor Total apparent power

```

1 //EXAMPLE 2-74 PG NO-112
2 ZA=10+%i*7.226; //IMPEDANCE
3 ZB=5+%i*10.99; //IMPEDANCE
4 V=200+%i*0; //VOLTAGE
5 IA=V/ZA; //CURRENT
6 disp('i) CURRENT (IA) is in polar form = '+
      string(IA) +' A ');
7 IB=V/ZB;
8 disp('ii) CURRENT (IB) is in polar form = '+
      string(IB) +' A ');
9 I=IA+IB;
10 disp('iii) CURRENT (I) is in polar form = '+
       string(I) +' A ');
11 S=V*I;
12 disp('i) Apparent Power (S) is = '+string(S) +
      ' VA ');
13 P=V*I*0.63;
14 disp('i) Active Power (P) is = '+string(P) +
      ' W ');
15 Q=V*I*0.775;
16 disp('i) Reactive Power (Q) is = '+string(Q) +
      ' Var ');

```

Scilab code Exa 2.75 Current Total Apparent Active Reactive Power Power Factor

```
1 //EXAMPLE 2-75    PG NO-113
2 V=100+%i*0;
3 R=3+%i*2;
4 I=V/R;
5 disp('i') CURRENT (I) is in polar form = '+string
(I) +' A ')';
6 ZA=10+%i*8;
7 ZB=9-%i*6;
8 ZC=3+%i*2;
9 IB=I*[ZA/(ZA+ZB)];
10 disp('i') CURRENT (IB) is in polar form = '+
string (IB) +' A ')';
11 IA=I*[ZB/(ZA+ZB)];
12 disp('i') CURRENT (IA) is in polar form = '+
string (IA) +' A ')';
13 Z=[(ZA*ZB)/{ZA+ZB}]+ZC;
14 disp('vi') IMPEDANCE (Z) is      = '+string (Z) +
ohm ';
15 V1=I*Z;
16 disp('vi') VOLTAGE (V1) is      = '+string (V1) +' V ';
);
17 S=V1*I;
18 disp('i') Apparent Power (S) is      = '+string (S) +
' VA ';
19 P=V1*I*0.984;
20 disp('i') Active Power (P) is      = '+string (P) +' W ';
21 Q=[S^2-P^2]^0.5;
22 disp('i') Reactive Power (Q) is      = '+string (Q) +
' Var ';
```

Scilab code Exa 2.76 magnitude Phase Angle Total Impedance

```
1 Z1=8+%i*10;
2 Z2=7+%i*9;
3 Z3=5-%i*2;
4 Z={Z1*Z2}/{Z1+Z2};
5 disp('vi') IMPEDANCE (Z) is      in polar form = '+
      string (Z) +' ohm ');
6 TZ=Z+Z3;
7 disp('vi') TOTAL IMPEDANCE (TZ) is      = '+string (
      TZ) +' ohm ';
```

Scilab code Exa 2.77 Power Factor

```
1 //EXAMPLE 2-77      PG NO
      -114
2 R=sqrt(2.5^2-1.724^2)-0.69;
3 disp('i') Resistance (R) is      = '+string (R) +' 
      ohm ');
4 R1=sqrt(2.5^2-1.92^2)-0.384;
5 disp('ii') Resistance (R1) is      = '+string (R1) +' 
      ohm ');
6 r=5;
7 PF=(0.69+R)/2.5;
8 disp('iii') Power Factor (PF) is      = '+string (PF)
      +' lagging ');
9 r1=10;
10 PF1=(0.384+R1)/2.5;
11 disp('iv') Power Factor (PF1) is      = '+string (
      PF1) +' lagging ';
```

Scilab code Exa 2.78 Voltage

```
1 //EXAMPLE 2-78 PG NO-114-115
2 I=10;
3 L1=0.0318; //INDUCTANCE
4 L2=0.0191;
5 F=50; //FREQUENCY
6 C=398*10^-6; //CAPACITOR
7 XL1=[2*pi*F*L1];
8 disp('i') INDUCYANCE (XL1) is = '+string(XL1)
      + ' ohm ';
9 XL2=[2*pi*F*L2];
10 disp('ii') INDUCYANCE (XL2) is = '+string(XL2)
      + ' ohm ';
11 XC=1/[2*pi*F*C];
12 disp('iii') CAPACITOR (XC) is = '+string(XC) +
      ohm ';
13 Z1=5+%i*6;
14 Z2=7-%i*8;
15 Z3=8+%i*9.99;
16 Z=[(Z1*Z2)/(Z1+Z2)]+Z3;
17 disp('iv') IMPEDANCE (Z) is in polar form = '+
      string(Z) + ' ohm ';
18 VAB=I*Z;
19 disp('i') VOLTAGE (VAB) is in polar form = '+
      string(VAB) + ' V '
```

Scilab code Exa 2.79 Voltage

```
1 //EXAMPLE 2-79
2 PG NO-115
2 I2=10+%i*0;
```

```

3 Z1=7-%i*8;
4 Z2=5+%i*6
5 V=I2*Z1;
6 disp('i) VOLTAGE (V) is in polar form = '+string
      (V) +' V ');
7 I1=V/Z2;
8 disp('i) CURRENT (I1) is in polar form = '+
      string (I1) +' A ')
9 I=I2-%i*13.44;
10 disp('i) CURRENT (I) is in polar form = '+string
      (I) +' A ')
11 VAB=15.57*18.52;
12 disp('i) VOLTAGE (VAB) is in polar form = '+
      string (VAB) +' V ')

```

Scilab code Exa 2.80 R1 X1 X2

```

1 //EXAMPLE 2-80
          PG NO
          -115-16
2 I=12+%i*0;
3 X2=13.33;
4 R=10+%i*13.33;
5 V=I*R;
6 disp('i) VOLTAGE (V) is in polar form = '+string
      (V) +' V ')
7 V1=30-%i*27.67;
8 Z1=10.6165+%i*1.5;
9 R1=V1/Z1;
10 disp('i) RESISTANCE (R1) is in polar form = '+
      string (R1) +' ohm ')

```

Scilab code Exa 2.81 Current in each branch Total Current Active Reactive Apparent

```

1 //EXAMPLE 2-81 PG NO
-116-117
2 Z1=10+%i*10;
3 Z2=20+%i*0;
4 Z3=20-%i*0.2;
5 V=100+%i*0;
6 I1=V/Z1;
7 disp('i) CURRENT (I1) is in polar form = '+
      string(I1) +' A ')
8 I2=V/Z2;
9 disp('i) CURRENT (I2) is in polar form = '+
      string(I2) +' A ')
10 I3=V/Z3;
11 disp('i) CURRENT (I3) is in polar form = '+
      string(I3) +' A ')
12 I=I1+I2+I3;
13 disp('i) CURRENT (I) is in polar form = '+string(
      I) +' A ')
14 S=V*I;
15 disp('i) Apparent Power (S) is in polar form =
      '+string(S) +' VA ');
16 P=V*I*0.95;
17 disp('i) Active Power (P) is in polar form = '+
      string(P) +' W ');
18 Q=[S^2-P^2]^0.5;
19 disp('i) Reactive Power (Q) is in polar form =
      '+string(Q) +' Var ');

```

Scilab code Exa 2.82 Resistance Capacitance

```

1 //EXAMPLE 2-82 PG NO-117
2 Z1=4+%i*314.16; //Impedance
3 I1=1/Z1; //CURRENT
4 disp('i) Current (I1) is = '+string(I1) +' A
');

```

```

5 I2=I1+%i*90;                                //CURRENT
6 disp('ii)      Current (I2) is      = '+string(I2) +' 
     A ');
7 Z2=1/I2;                                     //IMPEDANCE
8 disp('i)      Impedance (Z2) is      = '+string(Z2) +' 
     ohm ');
9 R=310.16;                                    //RESISTANCE
10 Xc=310.16;
11 F=50;
12 C=1/(2*pi*F*Xc);
13 disp('i)      Capacitor (C) is      = '+string(C) +'   F
     ');

```

Scilab code Exa 2.83 Active Reactive Apparent Power

```

1                                         //EXAMPLE 2-83      PG NO
                                         -117-118
2 V=125+%i*0;
3 I1=5+%i*0;
4 I2=1.2+%i*1.964;
5 Z2=V/I2;
6 disp('iv)      IMPEDANCE (Z2) is      in polar form      = '+
     string(Z2) +' ohm ');
7 R=28.26;
8 XC=46.43;
9 F=50;
10 C=1/[2*pi*F*XC];
11 disp('iv)      CAPACITOR (C) is      in polar form      = '+
     string(C) +' F ');
12 I=I1+I2;
13 disp('iv)      CURRENT (I) is      in polar form      = '+
     string(I) +' A ');
14 S=V*I;
15 disp('i)      Apparent Power (S) is      in polar form      = 
     '+string(S) +' VA ');

```

```

16 P=S*0.953;
17 disp('i) Active Power (P) is in polar form = '+
      string (P) +' W ');
18 Q=S*0.302;
19 disp('i) Reactive Power (Q) is in polar form =
      '+string (Q) +' Var ');

```

Scilab code Exa 2.84 Frequency

```

1 //EXAMPLE 2-84
          PG NO
          121-122
2 L=0.01;           // Inductance
3 C=0.04*10^-6;    // Capacitor
4 Fo=1/[2*%pi*(sqrt(L*C))];
5 disp('i) Resonant Frequency (Fo) is = '+string
      (Fo) +' Hz ');
6 Z=50;
7 R=Z;
8 V=100;
9 Io=V/R;
10 disp('ii) Current (Io) is = '+string (Io) +' A
       ');
11 Fc=(1/(2*pi))*[(1/(L*C))-(R^2/(2*L^2))]^.5;
12 disp('iii) Cutt Frequency (Fc) is = '+string (
      Fc) +' Hz ');
13 Z1=50-%i*2.5;
14 Xc=1/[2*pi*Fc*C];
15 disp('iv) Xc (Xc) is = '+string (Xc) +' ');
16 Vc=[100/Z1]*Xc;
17 disp('v) VOLTAGE (Vc) is = '+string (Vc) +' V
       ');
18 FL=1/[(2*pi)*[(L*C)-[(R^2*C^2)/2]]^.5];
19 disp('vi) Frequency (FL) is = '+string (FL) +' Hz
       ');

```

```

20 Z2=50+%i*2.5;
21 VL=[100/Z2]*(2*%pi*FL*0.1);
22 disp('i) VOLTAGE (VL) is = '+string(VL)+')';

```

Scilab code Exa 2.85 Current

```

1 //example 285 pg no-126
2 I1=0.707;
3 I2=0.707;
4 db=20*log10(0.707);
5 disp(' Ration in db is = '+string(db));

```

Scilab code Exa 2.86 Resonant Frequency Upper Lower Half Frequency Band Width Volt

```

1 //EXAMPLE 2-86 PG NO 126
2 L=0.5; // inductance
3 C=40*10^-6; //capacitor
4 Wo=1/(L*C)^0.5;
5 R=10; // resistance
6 V=100; // voltage
7 Fo=Wo/(2*pi); //frequency
8 Q=(Wo*L)/R;
9 W2=233.6; //frequency
10 W1=213.6; //frequency
11 B.W=W2-W1; //Band width
12 Io=V/R; //current at resonance
13 Io1=0.707*Io; //current at half power points
14 V1=Q*V; //voltage across inductance at
             resonance
15 disp(' frequency is = '+string(Wo)+', rad/sec');
16 disp(' frequency is = '+string(Fo)+', Hz');
17 disp(' Q is = '+string(Q)+');

```

```

18 disp(' BAND WIDTH is = '+string(B.W)+ ' rad/sec');
19 disp(' current at resonance is = '+string(Io)+ ' A');
20 disp(' current at half power points is = '+string(
    Io1)+ ' A');
21 disp(' voltage across inductance at resonance is =
    '+string(V1)+ ' V');

```

Scilab code Exa 2.87 Inductance Q Current voltage

```

1 //EXAMPLE 2-87      PG NO-127
2 Wo=1000;
3 C=20*10^-6;
4 R=2;
5 V=10;
6 L=1/((Wo^2)*C);
7 Q=(Wo*L)/R;
8 I=V/R;
9 Vr=I*R;
10 VL=Q*V;
11 Vc=Q*V;
12 disp(' INDUCTANCE is = '+string(L)+ ' H');
13 disp(' Q is = '+string(Q)+ ' ');
14 disp(' CURRENT(I) is = '+string(I)+ ' A');
15 disp(' VOLTAGE ACROSS RESISTANCE is = '+string(Vr)+',
    V');
16 disp(' VOLTAGE ACROSS INDUCTANCE is = '+string(VL)+',
    V');
17 disp(' VOLTAGE ACROSS CAPACITANCE is = '+string(Vc)+',
    V');

```

Scilab code Exa 2.88 Resonant Frequency Rc

```

1 //EXAMPLE 2-88  PG NO-130

```

```

2 L=10^-3;           //INDUCTANCE
3 C=20*10^-6;       //CAPACITOR
4 Rc=4;             //CAPACITOR RESISTANCE
5 RL=6;              //LOAD RESISTANCE
6 Wo=(1/(L*C)^0.5)*(((RL*RL)-(L/C))/((Rc*Rc)-(L/C)))
^0.5;
7 disp(' Wo is = '+string(Wo)+' rad/sec');

```

Scilab code Exa 2.89 Resonant Frequency Q Band Width Out put Voltage

```

1      //example 2-89 pg no-134
2 L=8*10^-3;           //INDUCTANCE
3 C=16*10^-9;
4 Wo=1/[L*C]^0.5;
5 R=10;                //RESISTANCE
6 Fo=Wo/(2*pi);       //FREQUENCY
7 Q=(Wo*L)/R;
8 Rp=((R*R)+(Wo*Wo*L*L))/R
9 Vo1=100;
10 B.W1=Wo/Q;
11 R2=10*10^3;
12 R3=60*10^3;
13 LR=(Rp*R2)/R3;
14 Q1=(Q*LR)/Rp
15 Vo2=16.666;
16 B.W2=Wo/Q1;
17 disp(' Wo is = '+string(Wo)+' rad/sec');
18 disp(' Q is = '+string(Q)+');
19 disp(' Rp is = '+string(Rp)+' ohm');
20 disp('BAND WIDTH 1 is = '+string(B.W1)+' rad/sec');
21 disp('Load resistance is = '+string(LR)+' ohm');
22 disp(' Q1 is = '+string(Q1)+');
23 disp('BAND WIDTH2is = '+string(B.W2)+' rad/sec');

```

Scilab code Exa 2.90 R L C

```
1 //EX 2-90 PG NO-135
2 R=20;           //RESISTANCE
3 Vc=250;         //VOLTAGE
4 I=1;            //CURRENT
5 F=50;           //FREQUENCY
6 W=2*pi*F;
7 C=1/(W*50);    //CAPACITOR
8 L=1/(W*W*C);   //INDUTANCE
9 disp( 'W is = '+string(W)+ ' ');
10 disp( 'CAPACITANCE(C) is = '+string(C)+ ' F');
11 disp( 'INDUCTANCE(L) is = '+string(L)+ ' H');
```

Scilab code Exa 2.91 Current at resonance

```
1 //EXAMPLE 2-91 PG NO-135
2 L=10*10^-6;      //INDUCTANCE
3 R=1;             //RESISTANCE
4 C=10^4*10^-12;   //CAPACITOR
5 V=100;           //VOLTAGE
6 Z=L/(C*R);      //IMPEDANCE
7 I=V/Z;           //CURRENT
8 disp( 'IMPEDANCE is = '+string(Z)+ ' ohm');
9 disp( 'CURRENT is = '+string(I)+ ' A');
```

Scilab code Exa 2.92 frequency

```
1 //EXAMPL2-92 PG NO-136
```

```

2 L=0.5;
3 R=25;
4 C=10^-6;
5 Wo = ((L- (R*R*C))/(5*10^-6*(0.5*0.5)))^0.5;
6 Q=(Wo*L)/R;
7 B.W=Wo/Q;
8 disp('FREQUENCY is = '+string(Wo)+' rad/sec');
9 disp('Q is = '+string(Q));
10 disp('band width is = '+string(B.W)+' rad/sec');

```

Scilab code Exa 2.93 Self Inductane Mutual Inductance voltage induce

```

1 //EXAMPLE 2-93 PG NO-139
2 N1=100;
3 Q1=0.05*10^-3;
4 I1=5;
5 L1=0.01;
6 L2=0.01;
7 K=0.6;
8 i=1000;      // (di/dt=20/0.02)
9 M=K*((L1*L2)^0.5);
10 V=M*i;
11 disp('mutual induction is = '+string(M)+' H');
12 disp('voltage induce is = '+string(V)+' v');

```

Scilab code Exa 2.94 Mutual Inductance EMF

```

1 //EXAMPLE 2.94      PG NO-139-140
2 L=0.6;    //LENGTH
3 a=20*10^-4;    //AREA
4 MU=(4*pi*10^-7);
5 R=L/(MU*a);
6 N1=1500;

```

```

7 N2=500;
8 i=250;
9 M=(N1*N2)/R;
10 e=M*(i);
11 disp('R = '+string(R)+ ' ');
12 disp('mutual induction is = '+string(M)+ ' H');
13 disp('E.M.F INDUCE is = '+string(e)+ ' V');

```

Scilab code Exa 2.95 Mutual Inductance

```

1 //EXAMPLE 2-95      PG NO
-140
2 L=1.5;           //INDUCTANCE
3 a=(2000*0.01);
4 R=L/(4*pi*10^-7*a);          //RESISTANCE
5 disp('i) Resistance (R) is = '+string (R) +
      ohm ');
6 N1=30;
7 N2=600;
8 M=(N1*N2)/R;
9 disp('ii) M (M) is = '+string (M) + ' H ');
10 e=M*(10/0.01);
11 disp('iii) e (e) is = '+string (e) + ' V ');

```

Scilab code Exa 2.96 Mutual Inductance Coefficient Coupling

```

1 //EXAMPLE-2.96    PG NO-140
2 M=0.125;
3 L1=0.2;
4 L2=0.15;
5 K=M/((L1*L2)^0.5)
6 disp('i) K = '+string (K)+ ' ');

```

Scilab code Exa 2.97 L1 L2 M K

```
1 //EXAMPLE-2.97 PG  
NO-140  
2 N1=500; //NUMBER OF TURN  
3 N22=1500;  
4 N12=500  
5 Q1=0.6*10^-3; //FLUX OF COIL  
6 I1=5; //CURRENT  
7 Q12=0.3*10^-3;  
8 L1=(N1*Q1)/I1  
9 K=Q12/Q1;  
10 L2=(N22/N12)*L1;  
11 M=K*((L1*L2)^0.5);  
12 disp('i') L1 = '+string (L2)+ ' );  
13 disp('ii') K = '+string (K)+ ' H');  
14 disp('iii') L2 = '+string (L2)+ ' H');  
15 disp('i') M = '+string (M)+ ' H ' );
```

Scilab code Exa 2.98 L1 L2 M N2

```
1 // example -2.98 pg no-141  
2 L1=37.5*10^-3;  
3 M=63.75*10^-3;  
4 K=0.85;  
5 N1=250;  
6 L2=((M/K)^2)/L1;  
7 N2=250/((L1/L2)^0.5);  
8 disp('i') L2 = '+string (L2)+ ' );  
9 disp('i') N2 = '+string (N2)+ ' );
```

Scilab code Exa 2.99 M K

```
1 //EXAMPLE 2-99 PG  
NO -141  
2 L1=6.8;  
3 L2=4.5;  
4 C1=19.6;  
5 C2=3;  
6 M=(C1-C2)/4;  
7 disp('i') M (M) is = '+string (M) +' mH');  
8 K=M/sqrt(L1*L2);  
9 disp('ii') K (K) is = '+string (K) +'');
```

Scilab code Exa 2.100 Self Inductance Mutual Inductance Coefficient of coupling

```
1 //example 2.100 pg no  
-141  
2 L1=15;  
3 L2=35;  
4 M=10;  
5 K=M/((L1*L2)^0.5); // coefficient of  
coupling  
6 disp('i') COEFFICIENT OF CUPLING (K) = '+string (K)+',')
```

Scilab code Exa 2.102 Equivalent Inductance

```
1 //EXAMPLE 2-102 PG  
NO-142
```

```

2 L1=0.3;
3 L2=0.8; //INDUCTANCE
4 K=0.7;
5 M=K*sqrt(L1*L2);
6 disp('i) M (M) is = '+string(M) +' H ');
7 Lp=[(L1*L2)-M^2]/[L1+L2-(2*M)];
8 disp('ii) Lp (Lp) is = '+string(Lp) +' H ');

```

Scilab code Exa 2.103 Equivalent Inductance

```

1 // Example 2-103 pg no-142
2 L1=10;
3 L2=5;
4 L3=6;
5 M12=2;
6 M23=1;
7 M13=1;
8 X=1 // X=di/dt
9 V1=(L1*X)+(M12*X)+(M13*X);
10 V2=(M12*X)+(L2*X)+(M23*X);
11 V3=(-M13*X)+(-M23*X)+(L3*X);
12 V=V1+V2+V3;
13 Ls=L1+L2+L3+(2*M12)-(2*M23)-(2*M13);
14 disp('i) V1 = '+string(V1) +' ')
15 disp('ii) V2 = '+string(V2) +' ')
16 disp('iii) V3 = '+string(V3) +' ')
17 disp('iv) V = '+string(V) +' ')
18 disp('v) equivlent indutance (Ls) = '+string(Ls) +' mH')

```

Scilab code Exa 2.104 Self Inductance Total Inductance Energy

```

1 // Example -2.104 pg no-143

```

```

2 L=38.5*10^-3;
3 La=100*10^-3;
4 Lb=53.8*10^-3;
5 C=0.3; //CAPACITOR
6 i=3;
7 M=(C*L);
8 E1=(0.5*La*(3^2)); //energy in series aiding
connection
9 E2=(0.5*Lb*(i^2)); //ENERGY IN SERIES OPPOSING
CONNECTION
10 disp('i') M = '+string(M)+ ' H'
11 disp('i') ENERGY aiding = '+string(E1)+ ' J'
12 disp('i') ENERGY opposing = '+string(E2)+ ' J'

```

Scilab code Exa 2.105 Self Inductance Mutual Inductance Turns of coil

```

1 //EXAMPLE-2.105 PG-NO143
2 N1=250; //number of turn
3 I1=2; //current
4 Q1=0.3*10^-3; //phi
5 L1=(N1*Q1)/I1;
6 V2=63.75;
7 K=0.85;
8 x=10^3; //x=di/dt
9 M=V2/x;
10 L2=((V2/K)^2)/((37.5*10^-3)^0.5);
11 Q12=0.255*10^-3;
12 y=1.275*10^-7; //y=dQ12/dt
13 N2=V2/y
14 ;
15 disp('i') L1 = '+string(L1)+ ' Tesla '
16 disp('ii') M = '+string(M)+ ' '
17 disp('iii') L2 = '+string(L2)+ ' '
18 disp('iv') N2 = '+string(N2)+ ' '

```

Scilab code Exa 2.106 Resonant Frequency Current

```
1 //EXAMPLE-2.106 PG NO
   -144
2 Fo=35.59;      // frequency in HZ
3 V=50;
4 R=100;
5 I=V/R;
6 L=0.5;
7 XL=(2*%pi*Fo*L);
8 V.I=XL*L;      //VOLTAGE ACROSS INDUCTION
9 XC=XL;
10 Q=XC/R;
11 S=L/Q;
12 W2=323.55;    //UPPER HALF FREQUENCY
13 W1=123.65;    //LOWER HAL FREQUENCY
14 B.W=W2-W1;    // BAND WIDTH
15 disp('i) INDUCTION = '+string(XL)+ ' ohm ');
16 disp('i)VOLTAGE ACROSS INDUCTION = '+string(V.I)+ ' V ');
17 disp('i) Q = '+string(Q)+ ' ');
18 disp('i) FREQUENCY = '+ string(S)+ ' ohm ');
19 disp('i) BAND WIDTH = ' +string(B.W) + ' rad/sec ' );
```

Scilab code Exa 2.107 Average Value RMS Value

```
1 //EXAMPLE 2-107 PG
   NO-145
2 Vm=100;
3 RMS=Vm/{sqrt(3)};
4 disp('i) RMS (RMS) is = '+string(RMS) +'');
```

```

5 AVG=50;
6 FF=RMS/AVG;
7 disp('ii) Form Factor (FF) is = '+string(FF)
     +'');

```

Scilab code Exa 2.108 RMS

```

1 //EXAMPLE 2-108 PG NO-146
2 I1=(100/1.414)^2;
3 I2=(10/1.414)^2;
4 R.M.S=(I1+I2)^0.5;
5 disp('R.M.S VALUE is = '+string(R.M.S)+ ' A');

```

Scilab code Exa 2.109 Real Power Reactive Power Power Factor

```

1 //EXAMPLE 2-109 PG NO
      -146
2 V=200;
3 I=10;
4 W=314;
5 Z=V/I;
6 disp('i) IMPEDANCE (Z) is = '+string(Z) +' ohm ');
7 R=Z*0.707;
8 disp('ii) RESISTANCE (R) is = '+string(R) +' ohm ');
9 XC=Z*0.707;
10 disp('iv) INDUCTANCE (XC) is = '+string(XC) +' ohm ');
11 C=1/(W*XC);
12 disp('iv) CAPACITOR (C) is = '+string(C) +' F');
13 P=V*I*0.707;

```

```

14 disp('i) Active Power (P) is in polar form = '+
      string (P) +' W ');
15 Q=V*I*0.707;
16 disp('i) Reactive Power (Q) is in polar form =
      '+string (Q) +' Var ');

```

Scilab code Exa 2.111 Total Power Factor Total Active and Reactive Power

```

1 //EXAMPLE 2-111 PG
NO-147
2 VCB=2.49-%i*12.50;
3 R=4+%i*2;
4 I1=VCB/R;
5 disp('i) CURRENT (I1) is in polar form = '+
      string (I1) +' A ');
6 I2=2.5+%i*0;
7 I=I1+I2;
8 disp('i) CURRENT (I) is in polar form = '+string
      (I) +' A ');
9 VAC=11.8-%i*0.12;
10 VCB=2.5-%i*12.5;
11 VAB=VAC+VCB;
12 disp('i) VOLTAGE (VAB) is in polar form = '+
      string (VAB) +' V ')

```

Scilab code Exa 2.112 impedance resistance reactance

```

1 //EXAMPLE 2-112 PG NO-148
2 I=5;
3 R=25;
4 Z=50;
5 Z1=40;
6 R1=[Z^2-R^2-1600]/50;

```

```

7 disp('i) RESISTANCE (R1) is = '+string (R1) +' ohm ')
8 X1=[1600-R1^2]^0.5;
9 disp('ii) INDUCTANCE (X1) is = '+string (X1) +' ohm ')
10 Pc=I*I*R1;
11 disp('iii) Power (Pc) is = '+string (Pc) +' W ');
12 P=I*I*(R+R1);
13 disp('iv) Power (P) is = '+string (P) +' W ');

```

Scilab code Exa 2.113 Resonant Frequency Dynamic Resistance Band width

```

1 //example -2.113 pg no -149
2 Wo=9.798*10^3;
3 Fo=1559.39;
4 C=2;
5 R=10*10^-6;
6 L=10^-3;
7 D.R=L/(C*R); //DYNAMIC RESISTANCE
8 Q=(1/C)*((L/R)^0.5);
9 B.W=Wo/Q; //BAND WIDTH
10 disp('i) DYNAMIC RESISTANCE = '+string (D.R)+ ' ohm ');
11 disp('ii) Q = '+string (Q)+ ' ');
12 disp('iii) BAND WIDTH = '+string (B.W)+ ' rad/sec ');

```

Chapter 3

Three Phase Circuits

Scilab code Exa 3.1 Line Current Total Volts Ampere Active Power Reactive Power

```
1 //EXAMPLE 3-1 PG NO-172
2 VL=400;
3 Vp=400/sqrt(3);
4 Z=8-%i*10;
5 IL=Vp/Z;
6 S=sqrt(3)*(VL*IL);
7 P=S*(cos(-51.34));
8 Q=S*(sin(-51.34));
9 Von=230.94+%i*0;
10 Vbn=-115.47-%i*99.99
11 disp('i) RMS = '+string(S)+'A')
```

Scilab code Exa 3.2 Load Impedance Line Voltage

```
1 //EXAMPLE 2-32 PG NO 173
2 Vp=400; //Peak voltage
3 VL=400;
4 Z=8-%i*10; //Impedance
```

```

5 Ip=VL/12.81;
6 IL=sqrt(3)*Ip;
7 S=sqrt(3)*VL*IL;
8 P=S*cos(-51.34);
9 Q=S*sin(-51.34);
10 Vab=Vp+%i*0;
11 Vbc=-200-%i*346.410;
12 Vca=-200+%i*346;
13 Iab=Vab/Z;
14 Ibc=Vbc/Z;
15 Ica=Vca/Z;
16 Ia=Iab-Ibc;
17 Ib=Ibc-Iab;
18 Ic=Ica-Ibc;
19 disp('i) Peak current = '+string(Ip)+'A ')
20 disp('i) S = '+string(S)+'VA ')
21 disp('i) Active Power = '+string(P)+'W ')
22 disp('i) Reactive power = '+string(Q)+'Vars ')
23 disp('i) Iab is in reactance form = '+string(Iab)
+ 'A ')
24 disp('i) Ibc is in reactance form = '+string(Ibc)
+ 'A ')
25 disp('i) Ica is in reactance form= '+string(Ica)
+ 'A ')
26 disp('i) Ia is in reactance form = '+string(Ia)+'
A ')
27 disp('i) Ib is in reactance form = '+string(Ib)+'
A ')
28 disp('i) Ic is in reactance = '+string(Ic)+'A ')

```

Scilab code Exa 3.3 Line Current Active and Reactive Power

```

1 //EXAMPLE 3.3 PG NO 174
2 Zy=3+%i*5.196;
3 Zeq=2.55+%i*2.916;
```

```

4 Vp=230.94;
5 IL=59.61;
6 Ip=59.61;
7 VL=400;
8 cos(48.83)=0.658;
9 sin(48.83)=0.7527;
10 S=sqrt(3)*VL*IL;
11 P=sqrt(3)*VL*IL*0.658;
12 Q=sqrt(3)*VL*IL*0.7527;
13 disp('i) S = '+string(S)+'VA')
14 disp('i) Active power = '+string(P)+'W')
15 disp('i) Reactive power = '+string(Q)+'Vars')

```

Scilab code Exa 3.4 Current

```

1 //EXAMPLE 3-4 PG NO-174
2 V=220;
3 Im=15.75+%i*21;
4 Z=5.33-%i*4;
5 LI=V/(sqrt(3)*Z);
6 TLI=LI+Im;
7 cos(-17.16)=0.955;
8 PF=sqrt(3)*0.955*V*32.42;
9 disp('i) Line current = '+string(LI)+'A');
10 disp('i) TOTAL line current = '+string(TLI)+'A');
11 disp('i) Power Factor = '+string(PF)+'W');

```

Scilab code Exa 3.5 line current active and reactive power

```

1 //EXAMPLE 3-5 PG NO-175
2 Pm=6000;
3 Qm=8000;

```

```

4 Z=16-%i*12;
5 V=220;
6 PC=V/Z;
7 PL=3*V*11*0.799;
8 QL=3*V*11*(-0.6);
9 P=Pm+PL;
10 Q=Qm+QL;
11 PF=cos(1/tan(Q/P));
12 IL=P/(sqrt(3)*V*0.9555);
13 disp('i) Phase current = '+string(PC)+'A ');
14 disp('i) PL = '+string(PL)+'W ');
15 disp('i) QL = '+string(QL)+'Vars ');
16 disp('i) Active power = '+string(P)+'W ');
17 disp('i) Reactive Power = '+string(Q)+'Vars ');
18 disp('i) Power factor = '+string(PF)+'lagging ')
;
19 disp('i) line current (IL) = '+string(IL)+'A ');

```

Scilab code Exa 3.6 Phase Current Line Current Total Active and Reactive Power

```

1 //EXAMPLE 3-6 PG NO-175
2 Vac=100+%i*0;
3 Vcb=-50-%i*86.6;
4 Vba=-50+%i*86.6;
5 Zac=6+%i*8;
6 Rcb=20+%i*0;
7 Zba=4-%i*3;
8 Zcb=20+%i*0;
9 Iac=Vac/Zac;
10 disp('i) CURRENT (Iac) is in rectangular form =
    '+string(Iac)+', A ');
11 Icb=Vcb/Zcb;
12 disp('i) CURRENT (Icb) is in rectangular form =
    '+string(Icb)+', A ');
13 Iba=Vba/Zba;

```

```

14 disp('i) CURRENT (IbA) is in rectangular form =
      '+string(Iba) +' A ');
15 Ia=Iac-Iba;
16 disp('i) CURRENT (Ia) is in rectangular form = ,
      '+string(Ia) +' A ');
17 Ic=Icb-Iac;
18 disp('i) CURRENT (Ic) is in rectangular form = ,
      '+string(Ic) +' A ');
19 Ib=Iba-Icb;
20 disp('i) CURRENT (Ib) is in rectangular form =
      '+string(Ib) +' A ');
21 Pac=Vac*Iac*0.6;
22 disp('iv) Power (Pac) is in rectangular form =
      '+string(Pac) +' W ');
23 Pcb=Vcb*Icb;
24 disp('iv) Power (Pcb) is in rectangular form =
      '+string(Pcb) +' W ');
25 Pba=Vba*Iba*0.8;
26 disp('iv) Power (Pba) is in rectangular form = ,
      '+string(Pba) +' W ');
27 Qac=100*20*0.8;
28 disp('iv) Reactive Power (Qac) is in rectangular
      form = '+string(Qac) +' vars ');
29 Qba=100*20*-0.6
30 disp('iv) Reactive Power (Qba) is in rectangular
      form = '+string(Qba) +' vars ');
31 P=600+500+1600;
32 disp('iv) Power (P) is = '+string(P) +' W ');
33 Q=800-1200;
34 disp('iv) Power (Q) is = '+string(Q) +' vars
      ');

```

Scilab code Exa 3.7 line currents

```

2 Vab=400+%i*0;
3 Vbc=-200-%i*346.410;
4 R=100;
5 Ica=0;
6 Iab=Vab/R;
7 disp('i) CURRENT (Iab) is in rectangular form = '
      +'string (Iab) +' A ');
8 Ibc=Vbc/R;
9 disp('i) CURRENT (Ibc) is in rectangular form = '
      +'string (Ibc) +' A ');
10 Ia=Iab-Ica;
11 disp('i) CURRENT (Ia) is in rectangular form = '
      +'string (Ia) +' A ');
12 Ib=Ibc-Iab;
13 disp('i) CURRENT (Ib) is in rectangular form = '
      +'string (Ib) +' A ');
14 Ic=Ica-Ibc;
15 disp('i) CURRENT (Ic) is in rectangular form = '
      +'string (Ic) +' A ');

```

Scilab code Exa 3.8 Line Current Neutral Current Total power

```

1 //EXAMPLE 3-8    PG NO-177
2 Za=10-%i*8;
3 Zb=12+%i*0;
4 Zc=8+%i*10;
5 Van=230.94+%i*0;
6 Vbn=-115.47-%i*200;
7 Vcn=-115.47+%i*200;
8 Ia=Van/Za;
9 disp('i) CURRENT (Ia) is in rectangular form = '
      +'string (Ia) +' A ');
10 Ib=Vbn/Zb;
11 disp('ii) CURRENT (Ib) is in rectangular form = '
      +'string (Ib) +' A ');

```

```

12 Ic=Vcn/Zc;
13 disp('iii) CURRENT (Ic) is in rectangular form =
      '+string(Ic) +' A ');
14 In=Ia+Ib+Ic;
15 disp('iv) CURRENT (In) is in rectangular form =
      '+string(In) +' A ');
16
17 P=(230.94*18.028*0.78)+(230.94*19.245)
     +(230.94*18.028*0.62)
18
19 disp('v) POWER (P) is in rectangular form = '+
      string(P) +' W ');

```

Scilab code Exa 3.9 Line Current Neutral Current

```

1 //EXAMPLE 3-9
          PG NO
          -178-179
2 Z1=10+%i*0;
3 Z2=13+%i*7.5;
4 Z3=-13+%i&7.5;
5 Z4=8.66-%i*5;
6 X=[Z1+Z2 Z3;Z3 Z2+Z4];
7 Z5=-104+%i*180.13;
8 Z6=280+%i*0;
9 Y=[Z5 Z3;Z6 Z2+Z4];
10 I1=det(Y/X);
11 disp('i) Current (I1) is = '+string(I1) +' A
      ');

```

Scilab code Exa 3.10 Voltage Line Currents

1

//EXAMPLE 3-10
-180

PG NO

```
2 Za=6+%i*0;
3 Zb=5.26+%i*3;
4 Zc=3.535+%i*3.535;
5 Van=230.94+%i*0;
6 Vcn=-115.47-%i*200;
7 Vbn=-115.47+%i*200;
8 Ya=1/Za;
9 disp('i) admittance (Ya) is in rectangular form =
  '+string (Ya) +' siemens ');
10 Yb=1/Zb;
11 disp('i) admittance (Yb) is in rectangular form
  = '+string (Yb) +' siemens ');
12 Yc=1/Zc;
13 disp('i) admittance (Yc) is in rectangular form =
  '+string (Yc) +' siemens ');
14 Von=[(Van*Ya)+(Vbn*Yb)+(Vcn*Yc)]/(Ya+Yb+Yc);
15 disp('i) Voltage (Von) is in rectangular form =
  '+string (Von) +' V');
16 Vao=Van-Von;
17 disp('i) Voltage (Vao) is in rectangular form =
  '+string (Vao) +' V');
18 Vbo=Vbn-Von;
19 disp('i) Voltage (Vbo) is in rectangular form =
  '+string (Vbo) +' V');
20 Vco=Vcn-Von;
21 disp('i) Voltage (Vco) is in rectangular form =
  '+string (Vco) +' V');
22 Ia=Vao*Ya;
23 disp('i) CURRENT (Ia) is in rectangular form =
  '+string (Ia) +' A ');
24 Ib=Vbo*Yc;
25 disp('i) CURRENT (Ib) is in rectangular form =
  '+string (Ib) +' A ');
26 Ic=Vco*Yc;
27 disp('i) CURRENT (Ic) is in rectangular form =
  '+string (Ic) +' A ');
```

Scilab code Exa 3.11 Reading on wattmeter

```
1 //EXAMPLE 3-11 PG NO-181
2
3 Vrn=230.94+%i*0;
4 Vyn=-115.47-%i*200;
5 Vbn=-115.47+%i*200;
6 Yr=-%i*0.05;
7 Yy=%i*0.05;
8 Yb=0.05;
9 Von=[(Vrn*Yr)+(Vyn*Yy)+(Vbn*Yb)]/(Yr+Yy+Yb);
10 disp('i) Voltage (Von) is in rectangular form = '+string(Von) +' V');
11 Vyo=Vyn-Von;
12 disp('i) Voltage (Vyo) is in rectangular form = '+string(Vyo) +' V');
13 Iy=Vyo*Yy;
14 disp('iii) CURRENT (Iy) is in rectangular form = '+string(Iy) +' A');
```

Scilab code Exa 3.12 Phase Current of delta and star Active Power Power Factor

```
1 //EXAMPLE 3-12 PG NO-181-182
2 Vp=400;
3 Zp=10+%i*24;
4 Zpy=6-%i*8;
5 Ip=Vp/Zp;
6 disp('i) CURRENT (Ip) is in rectangular form = '+string(Ip) +' A ');
7 Ipy=[Vp/sqrt(3)]/Zpy;
8 disp('ii) CURRENT (Ipy) is in rectangular form = '+string(Ipy) +' A');
```

```

9 Rp=10;
10 Rpy=6;
11 Xp=24;
12 Xpy=-8;
13 P1=3*Ip*Ip*Rp;
14 disp('iii') Power (P1) is = '+string (P1) +' W
');
15 P2=Ipy*Ipy*3*Rpy;
16 disp('iv') Power (P2) is = '+string (P2) +' W '
);
17 Q1=3*Ip*Ip*Xp;
18 disp('v') Power (Q1) is = '+string (Q1) +' W ')
;
19 Qy=3*Ipy*Ipy*Xpy;
20 disp('vi') Power (Qy) is = '+string (Qy) +' W '
);
21 P=P1+P2;
22 disp('vii') Power (P) is = '+string (P) +' W ')
;
23 Q=Q1+Qy;
24 disp('viii') Power (Q) is = '+string (Q) +' W '
);
25 S=P+%i*Q;
26 disp('ix') Power (S) is = '+string (S) +' W ');
27 LI=S/[sqrt(3)*Vp];
28 disp('x') CURRENT (LI) is in rectangular form =
'+string (LI) +' A ');

```

Scilab code Exa 3.13 Line voltage

```

1 //EXAMPLE 3-13
          PG NO 182
2 VRY=375.877+%i*136.80;
3 disp('i') LINE VOLTAGE (VRY) is in rectangular form
= '+string (VRY) +' V ');

```

```

4 VYB=-69.45-%i*393.923;
5 disp('ii) LINE VOLTAGE (VYB) is in rectangular
      form = '+string(VYB) +' V ');
6 VBR=-306.41+%i*257.11;
7 disp('iii) LINE VOLTAGE (VBR) is in rectangular
      form = '+string(VBR) +' V ');
8 VYR=-VRY;
9 disp('i) LINE VOLTAGE (VYR) is in rectangular form
      = '+string(VYR) +' V ');
10 VRB=69.45+%i*393.923;
11 disp('i) LINE VOLTAGE (VRB) is in rectangular form
      = '+string(VRB) +' V ');
12 VBY=306.41-%i*257.11;
13 disp('i) LINE VOLTAGE (VBY) is in rectangular form
      = '+string(VBY) +' V ');

```

Scilab code Exa 4.14 Current voltage

```

1 //EXAMPLE 3-14 PG NO 182-183
2 X=[400+%i*0 -6+-%i*0,-200--%i*346.410 6--%i*0];
3 Y=[12+-%i*0 -6+-%i*0,-6+-%i*0 6--%i*8];
4 I1=52.31--%i*7.120;
5 I2=37.957--%i*14.23;
6 Ia=I1;
7 disp('i) CURRENT (Ia) is in rectangular form = '
      +string(Ia) +' A ');
8 Ib=I2-I1;
9 disp('i) CURRENT (Ib) is in rectangular form = '
      +string(Ib) +' A ');
10 IC=-I2;
11 disp('i) CURRENT (Ic) is in rectangular form = '
      +string(IC) +' A ');
12 Z1=6+-%i*0;
13 Vao=Ia*Z1;
14 disp('i) VOLTAGE (Vao) is in rectangular form = 
```

```

        '+string (Vao) +' V ');
15 Vbo=Ib*Z1;
16 disp('i) VOLTAGE (Vbo) is in rectangular form =
        '+string (Vbo) +' V ');
17 Vco=IC*(-%i*8);
18 disp('i) VOLTAGE (Vco) is in rectangular form =
        '+string (Vco) +' V ');

```

Scilab code Exa 3.15 Line Current Neutral Currents Reading of wattmeter

```

1 //EXAMPLE 3-15 PG NO-185-186
2 Van=230.94+%i*0;
3 Vbn=-115.47-%i*200;
4 Vcn=-115.47+%i*200;
5 V1=10*10^3;
6 Ia=V1/Van;
7 disp('i) CURRENT (Ia) is in rectangular form =
        '+string (Ia) +' A ');
8 V2=4*10^3;
9 Ic=V2/Van;
10 disp('i) CURRENT (Ic) is in rectangular form =
        '+string (Ic) +' A ');
11 V3=6*10^3;
12 Ib=V3/Van;
13 disp('i) CURRENT (Ib) is in rectangular form =
        '+string (Ib) +' A ');
14 In=(Ia+Ib+Ic);
15 disp('i) CURRENT (In) is in rectangular form =
        '+string (In) +' A ');
16 W1=[V1+V2+V3]/2;
17 disp('iv) Power (W1) is in rectangular form =
        '+string (W1) +' W ');

```

Scilab code Exa 3.16 Power and Power factor

```
1 //example -3.16      pg no-186
2 W1=5920;
3 W2=2610;
4 P=8530;
5 tanQ=(1.732*(W2-W1))/(W1+W2);
6 cosQ=0.83;
7 P.F=cosQ;
8 disp('i) tanQ = '+string(tanQ)+');
9 disp('ii) POWER FACTOR = '+string(P.F)+');
```

Scilab code Exa 3.18 Power outputs

```
1 //Example 3.18          pg no-186-187
2 cosQ=0.8;
3 sinQ=0.6;
4 VL=10000;
5 V=5000*10^3;           //VOLTAGE
6 P.F=0.9;              //POWER FACTOR
7 IL=V/(1.732*VL*cosQ);
8 I1=IL*cosQ;           //ACTIVE COMPONENT
9 I2=IL*sinQ;           //REACTIVE COMPONENT
10 P=1.732*(VL*IL*P.F)
11 disp('i) IL = '+string(IL)+' A');
12 disp('i) ACTIVE COMPONENT = '+string(I1)+' A');
13 disp('i) REACTIVE COMPONENT = '+string(I2)+' A');
14 disp('i) P = '+string(P)+' KW');
```

Scilab code Exa 3.19 Current Power factor Active Reactive Power

```
1 //EXAMPLE 3.19          PG NO-187
2 VL=230;
```

```

3 VP=VL/1.732;
4 IL=13.279;
5 COSQ=0.8;
6 SINQ=0.6;
7 P=(1.732*VL*IL*COSQ)
8 R.P=(1.732*VL*IL*SINQ)
9 VA=(1.732*VL*VP)
10 disp('i) POWER FACTOR = '+string(P)+' W');
11 disp('i) POWER FACTOR = '+string(R.P)+' var');
12 disp('i)TOTAL VA = '+string(VA)+' VA');

```

Scilab code Exa 3.20 Load Impedance

```

1 //Example 3.20 pg no-187
2 Ip=100; //LINE CURRENT
3 COSQ=0.787;
4 SINQ=0.617;
5 pi=3.14;
6 Vp=1100/1.732;
7 W=(2*pi*50)
8 Z=Vp/Ip;
9 R=Z*COSQ;
10 Xc=Z*SINQ
11 C=1/(W*Xc)
12 disp('i) Z = '+string(Z)+' ohm');
13 disp('ii) R = '+string(R)+' ohm');
14 disp('iii) Xc = '+string(Xc)+' ohm');
15 disp('iiii) capacitance (C) = '+string(C)+' F');

```

Scilab code Exa 3.21 Line current Volt ampere Active and Reactive Power

```

1 // EXAMPLE 3.21 PG NO-187
2 Ip=20;

```

```

3 IL=(1.732*Ip);
4 VL=400;
5 cos40=0.766;
6 sin40=0.642;
7 VA=(1.732*VL*IL);
8 p=(VA*cos40);
9 q=(VA*sin40);
10 disp('i) VA = '+string(VA)+ ' VA');
11 disp('ii) P = '+string(p)+ ' W');
12 disp('iii) Q = '+string(q)+ ' vars');

```

Scilab code Exa 3.22 Phase Current Line Current Power Factor Active Powerand React

```

1 //EXAMPLE 3.22 PG NO-188
2 Vp=230;
3 VL=230;
4 Z=8+%i*6;
5 Ip=Vp/Z;
6 disp('i) CURRENT (Ip) is in rectangular form = '
+string(Ip) +' A ');

```

Scilab code Exa 3.23 impedance

```

1 //EXAMPLE 3-23 PG NO-188
2 Za=8.66+%i*5;
3 Zc=8.48+%i*8.48;
4 Zb=11.50+%i*9.642;
5 VRn=254+%i*0;
6 VYn=-127.02-%i*220;
7 Vbn=-127.02+%i*220;
8 Yr=1/Za;
9 disp('i) admittance (Ya) is in rectangular form = '
+string(Yr) +' siemens ');

```

```

10 Yb=1/Zb;
11 disp('i) admittance (Yb) is in rectangular form =
    '+string (Yb) +' siemens ');
12 Yy=1/Zc;
13 disp('i) admittance (Yc) is in rectangular form =
    '+string (Yy) +' siemens ');
14
15 Von=[(VRn*Yr)+(Vbn*Yb)+(VYn*Yy)]/(Yr+Yb+Yy);
16
17 disp('i) Voltage (Von) is in rectangular form =
    '+string (Von) +' V');

```

Scilab code Exa 3.24 Total Power and Power Factor

```

1 //EXAMPLE 3-24 PG NO-189
2 W1=-1200;
3 W2=3400;
4 P=W1+W2;
5 disp('iv) Power (P) is = '+string (P) +' W ')
;
6 X=[sqrt (3)*(W2-W1)]/P;
7 disp('iv) (tan (Q)) is = '+string (X) +' ,
');

```

Scilab code Exa 3.25 Line Current Total Power

```

1 //EXAMPLE 3-25 PG NO
-189
2 Vac=240+%i*0;
3 Vcb=-120-%i*207.84;
4 Vba=-120+%i*207.84;
5 Zac=20+%i*0;
6 Zcb=12.99+%i*7.5;

```

```

7 Zba=0+%i*25;
8 Iac=Vac/Zac;
9 disp('i) CURRENT (Iac) is in rectangular form =
  '+string(Iac) +' A ');
10 Icb=Vcb/Zcb;
11 disp('i) CURRENT (Icb) is in rectangular form =
  '+string(Icb) +' A ');
12 Iba=Vba/Zba;
13 disp('i) CURRENT (Iba) is in rectangular form =
  '+string(Iba) +' A ');
14 Ia=Iac-Iba;
15 disp('i) CURRENT (Ia) is in rectangular form = ,
  '+string(Ia) +' A ');
16 Ib=Iba-Icb;
17 disp('i) CURRENT (Ib) is in rectangular form = ,
  '+string(Ib) +' A ');
18 Ic=Icb-Iac;
19 disp('i) CURRENT (Ic) is in rectangular form = ,
  '+string(Ic) +' A ');
20 P=(240*12)+(240*16*0.866)+(240*9.6*0);
21 disp('iv) Power (P) is      = ,'+string(P) +' W ')
  ;

```

Scilab code Exa 3.26 current Power

```

1 Vab=200+%i*0;
2 Vbc=-100-%i*173.20;
3 Vca=-100+%i*173.20;
4 Zac=31+%i*59;
5 Zcb=30-%i*40;
6 Zba=80+%i*60;
7 Iab=Vab/Zac;
8 disp('i) CURRENT (Iac) is in rectangular form =
  '+string(Iab) +' A ');
9 Ibc=Vbc/Zcb;

```

```

10 disp('i) CURRENT (Icb) is in rectangular form = 
      '+string (Ibc) +' A ');
11 Ica=Vca/Zba;
12 disp('i) CURRENT (Iba) is in rectangular form = 
      '+string (Ica) +' A ');
13 Ia=Iab-Ica;
14 disp('i) CURRENT (Ia) is in rectangular form = ,
      '+string (Ia) +' A ');
15 Ib=Ibc-Iab;
16 disp('i) CURRENT (Ib) is in rectangular form = ,
      '+string (Ib) +' A ');
17 Ic=Ica-Ibc;
18 disp('i) CURRENT (Ic) is in rectangular form = ,
      '+string (Ic) +' A ');
19 P=(200*3*0.46)+(200*4*0.6)+(200*2*0.8);
20 disp('iv) Power (P) is      = '+string (P) +' W')
      ;

```

Scilab code Exa 3.27 Line Current and Total Power

```

1 //EXAMPLE-3.27    PG NO-190-191
2 Zr=4;
3 Zy=5;
4 VL=400;
5 IL=103.1;
6 Q=36.6    //Q=TETA
7 COSQ=0.8028;
8 P=(1.732*VL*IL*COSQ)
9 disp('i) P = '+string (P)+ ' W');

```

Scilab code Exa 3.28 Line Current Neutral Current Total power

1 //EXAMPLE 3-28 PG NO-191

```

2 Van=230.94+%i*0;
3 Vbn=-115.47-%i*200;
4 Vcn=-115.47+%i*200;
5 Za=12-%i*16;
6 Zb=12+%i*0;
7 Zc=8+%i*6;
8 Ia=Van/Za;
9 disp('i) CURRENT (Ia) is in rectangular form = '
+string(Ia) +' A ');
10 Ib=Vbn/Zb;
11 disp('i) CURRENT (Ib) is in rectangular form = '
+string(Ib) +' A ');
12 Ic=Vcn/Zc;
13 disp('i) CURRENT (Ic) is in rectangular form = '
+string(Ic) +' A ');
14 NI=-(Ia+Ib+Ic);
15 disp('i)NEUTRAL CURRENT (NI) is in rectangular
form = '+string(NI) +' A ');
16 P=(230.95*11.55*0.6)+(230.95*19.25*1)
+(230.95*23.095*0.8);
17 disp('iv) Power (P) is = '+string(P) +' W ')
;
```

Scilab code Exa 3.29 Line current

```

1 //Example -3.29      PG NO-191-192
2 IL=12.55;
3 V=460;
4 Z=V/(1.732*IL)
5 disp('i) Z = '+string(Z)+ ' ohm');
```

Scilab code Exa 3.30 R and x

```

1 //EXAMPLE 3-30 PG NO-192
2 R=8*0.866; //cos30=0.866
3 disp('i') Resistance (R) is = '+string (R) +' ohm ';
4 X=8*0.5;
5 disp('ii') X (X) is = '+string (X) +' ohm ');

```

Scilab code Exa 3.31 Voltmeter

```

1 //EXAMPLE -3.31 PG NO -193
2 Zr=3333.33;
3 Vry=200;
4 X=16666.66;
5 Y=346.40; //Y=(300-j173.2)
6 I=Y/X;
7 R.V=I*Zr;
8 disp('i') I = '+string (I)+ '<-29.99 A';
9 disp('ii') READING OF VOLTMETER = '+string (R.V)+'
<-30 degree V');

```

Scilab code Exa 3.32 Line currents

```

1 //EXAMPLE 3-32 PG NO-193
2 Vry=400+%i*0;
3 Vy=-200-%i*346.41;
4 Vbr=-200+%i*346.410;
5 I1=14.74-%i*7.3;
6 I2=2.105-%i*10.94;
7 Ir=I1;
8 disp('i') CURRENT (Ir) is in rectangular form =
+string (Ir) +' A ');
9 Iy=I2-I1;

```

```

10 disp('i) CURRENT (Iy) is in rectangular form = '
      +string (Iy) +' A ');
11 Ib=-I2;
12 disp('i) CURRENT (Ib) is in rectangular form = '
      +string (Ib) +' A ');
13 Pr=16.45*16.45*10;
14 disp('i) Power (Pr) is      = '+string (Pr) +' W ');
15 Py=Iy*Iy*20;
16 disp('i) Power (Py) is in rectangular form = '+
      string (Py) +' W ');
17 Pb=11.24*11.24*25;
18 disp('i) Power (Pb) is in rectangular form = '+
      string (Pb) +' W ');
19 Vro=-(Ir*10);
20 disp('i) VOLTAGE (Vro) is in rectangular form = '
      '+string (Vro) +' V ');
21 Vrn=200-%i*115.475;
22 disp('i) VOLTAGE (Vrn) is in rectangular form = '
      '+string (Vrn) +' V ');
23 Von=Vro+Vrn;
24 disp('i) VOLTAGE (Von) is in rectangular form = '
      '+string (Von) +' V ');

```

Scilab code Exa 3.33 Neutral Current

```

1 //EXAMPLE 3-33          PG NO-194
2 Z1=8-%i*6;
3 Z2=3.6-%i*4.8;
4 In=-(Z1+Z2);
5 disp('i) CURRENT (In) is in rectangular form = '
      +string (In) +' A ');

```

Scilab code Exa 3.34 Line Current Total Voltmeter Active and Reactive Power

1 //EXAMPLE 3-34 PG NO
 -194

```

2 Vp=230.94;
3 Van=230.94+%i*0;
4 Vbn=-115.47-%i*200;
5 Vcn=-115.47+%i*200;
6 Z=8-%i*10;
7 Ia=Van/Z;
8 disp('i) CURRENT (Ia) is in rectangular form = ',  

      '+string(Ia) +, A ');
9 Ib=Vbn/Z;
10 disp('ii) CURRENT (Ib) is in rectangular form =  

      '+string(Ib) +, A ');
11 Ic=Vcn/Z;
12 disp('iii) CURRENT (Ic) is in rectangular form =  

      '+string(Ic) +, A ');
13 S=sqrt(3)*400*18.03;
14 disp('iv) APPARENT POWER (S) is = '+string(S)  

      +' VA ');
15 P=S*0.62;
16 disp('v) Power (P) is = '+string(P) +' W ');
17 Q=S*-0.8;
18 disp('vi) Power (Q) is = '+string(Q) +' vars  

      ');

```

Scilab code Exa 3.35 Total Active Power Toal Reactive Power Voltmetter Line Current

```

1 //EXAMPLE -3.35 PG NO-195
2 I.P=163.44; //POWER INPUT
3 T.A.P=253.44; //TOTAL ACTIVE POWER
4 R.P=122.58; //REACTIVE POWER INDUCTION MOTOR
5 L=40; //REACTIVE POWER OF SPECIAL LOAD
6 T.P=R.P+L; //TOTAL REACTIVE POWER
7 S=301.1; //P+JQ
8 X=T.A.P/S; //OVERALL POWER FACTOR

```

```

9 IL=S*10^3/(1.732*400)
10 disp('i')TOTAL REACTIVE POWER      = '+string (T.P)+'
```

Kvar')

```

11 disp('i') S      = '+string (S)+'
```

KVA')

```

12 disp('i')OVERALL POWER FACTOR (x) = '+string (X)+'
```

lagging')

```

13 disp('iiii')LOAD CURRENT (IL)    = '+string (IL)+'
```

A')

Scilab code Exa 3.36 Phase current Total line current

```

1 //EXAMPLE-3.36      PG NO -195
2 Vp=400/(3)^0.5;
3 R.p=162.58*10^3;
4 Ipc=R.p/(3*Vp);
5 IL=365.82;
6 Xc=Vp/Ipc;
7 pi=3.14;
8 C=1/(2*pi*50*Xc)
9 disp('i') Ipc = '+string (Ipc)+'
```

A')

```

10 disp('ii') Xc = '+string (Xc)+'
```

ohm')

```

11 disp('i') CAPACITANCE = '+string (C)+'
```

F')

Scilab code Exa 3.37 current

```

1 //EXAMPLE 3-37
2 PG NO-196-197
3 Vry=450+%i*0;
4 Vyb=-225-%i*389.711;
5 Vbr=-225+%i*389.711;
6 Vrn=225-%i*130;
7 Vyn=-225-%i*130;
8 Vbn=0+%i*259.8;
```

```

8 Z1=10.60+%i*10.60;
9 Z2=5+%i*8.66;
10 Z3=2.6+%i*1.5;
11 Z4=12.21+%i*4.44;
12 Iry=Vry/Z1;
13 disp('i) CURRENT (Iry) is in rectangular form =
  '+string(Iry) +' A ');
14 Iyb=Vyb/Z2;
15 disp('i) CURRENT (Iyb) is in rectangular form =
  '+string(Iyb) +' A ');
16 Ibr=Vbr/Z3;
17 disp('i) CURRENT (Ibr) is in rectangular form =
  '+string(Ibr) +' A ');
18 I1=Iry-Ibr;
19 disp('i) CURRENT (I1) is in rectangular form = ,
  '+string(I1) +' A ');
20 I2=Iyb-Iry;
21 disp('i) CURRENT (I2) is in rectangular form = ,
  '+string(I2) +' A ');
22 I3=Ibr-Iyb;
23 disp('i) CURRENT (I3) is in rectangular form = ,
  '+string(I3) +' A ');
24 I4=Vrn/Z4;
25 disp('i) CURRENT (I4) is in rectangular form = ,
  '+string(I4) +' A ');
26 I5=Vyn/Z4;
27 disp('i) CURRENT (I5) is in rectangular form = ,
  '+string(I5) +' A ');
28 I6=Vbn/Z4;
29 disp('i) CURRENT (I6) is in rectangular form = ,
  '+string(I6) +' A ');
30 I7=Vbn/(3+%i*4);
31 disp('i) CURRENT (I7) is in rectangular form = ,
  '+string(I7) +' A ');
32 IR=I1+I4;
33 disp('i) CURRENT (IR) is in rectangular form = ,
  '+string(IR) +' A ');
34 IY=I1+I4;

```

```

35 disp('i) CURRENT (IY) is in rectangular form = '
      +string (IY) +' A ');
36 IB=I3+I6+I7;
37 disp('i) CURRENT (IB) is in rectangular form = '
      +string (IB) +' A ');
38 IN=-(I7);
39 disp('i) CURRENT (IN) is in rectangular form = '
      +string (IN) +' A ');

```

Scilab code Exa 3.39 Voltage

```

1 VAB=400+%i*0;
2 VBC=-200-%i*346.41;
3 VCA=400+%i*0;
4 Z1=300-%i*398;
5 IAB=VAB/Z1;
6 disp('i) CURRENT (IAB) is in rectangular form = '
      +string (IAB) +' A ');
7 VAD=IAB*300;
8 disp('ii) VOLTAGE (VAD) is in rectangular form = '
      +string (VAD) +' V ');
9 VDA=-VAD;
10 disp('iii) VOLTAGE (VDA) is in rectangular form = '
      +string (VDA) +' V ');
11 VDC=VDA-VCA;
12 disp('iv) VOLTAGE (VDC) is in rectangular form = '
      +string (VDC) +' VA ');
13 VAC=400+%i*0;
14 VCB=-200-%i*346.41;
15 VBA=-200+%i*346.410;
16 IAB1=-(VAC)/Z1;
17 disp('v) CURRENT (IAB1) is in rectangular form = '
      +string (IAB1) +' A ');
18 VAD1=IAB1*300;
19 disp('vi) VOLTAGE (VAD1) is in rectangular form = '

```

```

        '+string (VAD1) +' V ');
20 VDA=-VAD;
21 disp('vii) VOLTAGE (VAAD) is in rectangular form
      = '+string (VDA) +' V ');
22 VDC=VDA+VAC;
23 disp('viii) VOLTAGE (VDC) is in rectangular form
      = '+string (VDC) +' V ');

```

Scilab code Exa 3.40 W1 and W2

```

1      //EXAMPLE-3.40      PG NO-199
2 Vry=200;
3 Vbr=200;
4 Vbn=115.47;
5 I1=10;    //10-j12
6 W1=200*I1;
7 X1=173.2;
8 X2=26.66;
9 W2=X1*X2;
10 disp('i)WATTMETERS (W2)     = '+string (W2)+ ' W')

```

Scilab code Exa 3.41 Current

```

1      //      CHAPTER -3 EXAMPLE NO 3.41      PG NO-200
2 Vp=230.94;
3 Xa=100+%i*155;
4 Ia=Vp/Xa;
5 COSQ=0.542;
6 P=COSQ;
7 disp('i) (Ia)     = '+string (Ia)+ ' A')

```

Scilab code Exa 3.42 Za Zb Zc

```
1 Van=254+%i*0;
2 Vbn=-127.02-%i*220;
3 Vcn=-127.02+%i*220;
4 Ib=0-%i*10;
5 Ic=0+%i*20;
6 Ia=-(Ib+Ic);
7 disp('i) CURRENT (Ia) is in rectangular form = '
      +string(Ia) +' A ');
8 Von=-173.20+%i*100;
9 Vao=Van-Von;
10 disp('i) VOLTAGE (Vao) is in rectangular form =
      '+string(Vao) +' V ');
11 Vbo=Vbn-Von;
12 disp('i) VOLTAGE (Vbo) is in rectangular form =
      '+string(Vbo) +' V ');
13 Vco=Vcn-Von;
14 disp('i) VOLTAGE (Vco) is in rectangular form =
      '+string(Vco) +' V ');
15 Za=Vao/Ia;
16 disp('i) IMPEDANCE (Za) is in rectangular form =
      '+string(Za) +' ohm ');
17 Zb=Vbo/Ib;
18 disp('i) IMPEDANCE (Zb) is in rectangular form =
      '+string(Zb) +' ohm ');
19 Zc=Vco/Ic;
20 disp('i) IMPEDANCE (Zc) is in rectangular form =
      '+string(Zc) +' ohm ');
```

Scilab code Exa 3.43 Total Apparent active Reactive Power line Current Power factor

```
1 //example -3.43    pg no -200-201
2 Ip=11<36.87;
3 PL=5808;
```

```

4 QL=4356;
5 Pm=6000;
6 Qm=8000;
7 P=PL+Pm;
8 Q=Qm-QL;
9 S=((P*P)+(Q*Q))^.5;
10 X=P/S;      //POWER FACTOR
11 disp('i)ACTIVE POWER (P) = '+string(P)+' W')
12 disp('i)REACTIVE POWER (Q) = '+string(Q)+' vars(
    inductive)')
13 disp('i)APPARENT POWER (S) = '+string(S)+' A')
14 disp('i)power factor (X) = '+string(X)+' lagging
')

```

Scilab code Exa 3.44 Power and Power Factor

```

1 //EXAMPLE 3.44 PG NO-201
2 W1=800;
3 W2=-400;
4 P=W1+W2;
5 x=(1.723*(W2-W1))/(W1+W2)    //tanQ=x
6 Q=-79.10;
7 y=0.189;
8 P=y      //POWER FACTOR
9 disp('i)tanQ (x) = '+string(x)+')
10 disp('i) POWER factor (P) = '+string(P)+')

```

Scilab code Exa 3.45 Line Current

```

1                               //EXAMPLE 3-45    PG NO-201-202
2 Vab=0+%i*212;
3 Vbc=-183.6-%i*106;
4 Vca=183.6-%i*106;

```

```

5 Za=10+%i*0;
6 Zb=10+%i*10;
7 Zc=0-%i*20;
8 Zab=[(Za*Zb)+(Zb*Zc)+(Za*Zc)]/Zc;
9 disp('i) IMPEDANCE (Zab) is in rectangular form =
    '+string(Zab) +' ohm ');
10 Zbc=[(Za*Zb)+(Zb*Zc)+(Za*Zc)]/Za;
11 disp('i) IMPEDANCE (Zbc) is in rectangular form =
    '+string(Zbc) +' ohm ');
12 Zca=[(Za*Zb)+(Zb*Zc)+(Za*Zc)]/Zb;
13 disp('i) IMPEDANCE (Zca) is in rectangular form =
    '+string(Zca) +' ohm ');
14 Iab=Vab/Zab;
15 disp('i) CURRENT (Iab) is in rectangular form =
    '+string(Iab) +' A ');
16 Ibc=Vbc/Zbc;
17 disp('i) CURRENT (Ibc) is in rectangular form =
    '+string(Ibc) +' A ');
18 Ica=Vca/Zca;
19 disp('i) CURRENT (Ica) is in rectangular form =
    '+string(Ica) +' A ');
20 Ia=Iab-Ica;
21 disp('i) CURRENT (Ia) is in rectangular form =
    '+string(Ia) +' A ');
22 Ib=Ibc-Iab;
23 disp('i) CURRENT (Ib) is in rectangular form =
    '+string(Ib) +' A ');
24 Ic=Ica-Ibc;
25 disp('i) CURRENT (Ic) is in rectangular form =
    '+string(Ic) +' A ');

```

Scilab code Exa 3.47 total votamperes Active and Reactive Power

1 //EXAMPLE 3-47 PG NO
-202-203

```

2 Vab=212;
3 Vbc=212;
4 Vca=212;
5 Iab=10;
6 IbC=5;
7 Ica=7.07;
8 P=[(Vab*Iab*0.707)+(Vbc*Ibc*0.707)+(212*7.07*0)];
9 disp('i) ACTIVE POWER (P) is = '+string(P) +' W
');
10 Q=[(Vab*Iab*0.707)+(Vbc*Ibc*-0.707)+(212*7.07*-1)]
11 disp('ii) REACTIVE POWER (Q) is = '+string(Q) +' vars ');
12 S=[P^2+(Q^2)]^0.5;
13 disp('i) APPARENT POWER (S) is = '+string(S) +' VA ');

```

Scilab code Exa 3.48 voltage

```

1 //EXAMPLE 3-48 PG NO-202-203
2 Vao=186.7-%i*87.06;
3 Vco=-38.5+%i*292.48;
4 Vbo=-(Vao+Vco);
5 disp('i) VOLTAGE (Vbo) is in rectangular form =
  '+string(Vbo) +' V ');
6 Vab=Vao-Vbo;
7 disp('i) VOLTAGE (Vab) is in rectangular form =
  '+string(Vab) +' V ');
8 Van=201-%i*37.51;
9 Von=Van-Vao;
10 disp('i) VOLTAGE (Von) is in rectangular form =
  '+string(Von) +' V ');

```

Scilab code Exa 3.49 Phase Current Line Current Total active and reactive Power W1

```

1 //EXAMPLE 3-49 PG NO-203-204
2 Vab=400+%i*0;
3 Vbc=-200-%i*346.41;
4 Vca=-200+%i*346.410;
5 Z1=%i*10;
6 Z2=-%i*20;
7 Z3=10;
8 Iab=Vab/Z1;
9 disp('i) CURRENT (Iab) is in rectangular form =
  '+string(Iab) +' A ');
10 Ibc=Vbc/Z2;
11 disp('ii) CURRENT (Ibc) is in rectangular form =
  '+string(Ibc) +' A ');
12 Ica=Vca/Z3;
13 disp('iii) CURRENT (Ica) is in rectangular form =
  '+string(Ica) +' A ');
14 Ia=Iab-Ica;
15 disp('iv) CURRENT (Ia) is in rectangular form =
  '+string(Ia) +' A ');
16 Ib=Ibc-Iab;
17 disp('v) CURRENT (Ib) is in rectangular form =
  '+string(Ib) +' A ');
18 Ic=Ica-Ibc;
19 disp('vi) CURRENT (Ic) is in rectangular form =
  '+string(Ic) +' A ');
20 P=Ica*Z3;
21 disp('vii) ACTIVE POWER (P) is in rectangular form
  = '+string(P) +' W ');
22 Q=(Iab^2*Z3)-(Ibc^2*20);
23 disp('viii) REACTIVE POWER (Q) is in rectangular
  form = '+string(Q) +' vars ');
24 S=[P^2+Q^2]^0.5;
25 disp('i) APPARENT POWER (S) is in rectangular form
  = '+string(S) +' VA ');

```

Scilab code Exa 3.50 Line current

```
1 //EXAMPLE 3-50 PG NO-204
2 I1=13.12-%i*9.15;
3 I2=-6.80-%i*19.55;
4 IaA=I1;
5 disp('i) CURRENT (IaA) is in rectangular form =
  '+string(IaA) +' A ');
6 IbB=I2-I1;
7 disp('i) CURRENT (IbB) is in rectangular form =
  '+string(IbB) +' A ');
8 IcC=-I2;
9 disp('i) CURRENT (IcC) is in rectangular form =
  '+string(IcC) +' A ');
```

Scilab code Exa 3.51 Resistance reactance Power Factor

```
1 //EXAMPLE 3-51 PG NO
-205
2 R1=1.5;
3 X=2.396;
4 X1=sqrt(X^2-R1^2);
5 disp('i) X1 is = '+string(X1) +'ohm ');
6 IL=100;
7 Ip=IL/1.732;
8 disp('ii) Peak Current = '+string(Ip) +' A ');
9 R2=4.5;
10 Z=7.1878;
11 X2=sqrt(Z^2-R2^2)
12 disp('iii) X2 is = '+string(X2) +'ohm ');
13 PF=R2/(Z);
14 disp('vi) Power Factor is = '+string(PF) +' ')
```

Scilab code Exa 3.52 Line Current Power factor Active and Reactive Power

```
1 //EXAMPLE 3-52    PG NO-205-206
2 Vp=230.94;
3 R=20+%i*30;
4 V=400;
5 IL=Vp/R;
6 disp('i) CURRENT (IL) is in rectangular form = ', '+string (IL) +' A ');
7 PF=0.555;
8 P=sqrt(3)*V*IL*PF;
9 disp('ii) ACTIVE POWER (P) is in rectangular form = '+string (P) +' W ');
10 Q=sqrt(3)*V*IL*56.289;
11 disp('iii) REACTIVE POWER (Q) is in rectangular form = '+string (Q) +' vars ');
12 S=sqrt(3)*V*IL;
13 disp('iv) APPARENT POWER (S) is in rectangular form = '+string (S) +' VA ');
14 Ip=3.698;
15 Z=V/Ip;
16 disp('i) IMPEDANCE (Z) is in rectangular form = '+string (Z) +' ohm ');
17 R1=Z*0.555;
18 disp('i) RESISTANCE (R1) is in rectangular form = '+string (R1) +' ohm ');
19 Xc=Z*0.83;
20 disp('i) INDUCTANCE (Xc) is in rectangular form = '+string (Xc) +' ohm ');
21 C=Xc/(2*%pi*50);
22 disp('i) CAPACITOR (C) is in rectangular form = '+string (C) +' F ');
```

Scilab code Exa 3.53 Current Active and Reactive Power

```
1 //EXAMPLE 3-53 PG NO-206-207
2 HP=2000;
3 Vp=2200;
4 E=0.93;
5 MI=(HP*735.5)/E;
6 disp('i) MOTOR INPUT (MI) is in rectangular form
    = '+string(MI) +' W ');
7 Ip=MI/[3*Vp*0.85];
8 disp('i) CURRENT (Ip) is in rectangular form = ,
    +string (Ip) +' A ');
9 AC=Ip*0.85;
10 disp('i) ACTIVE CURRENT (AC) is in rectangular
    form = '+string (AC) +' A ');
11 RC=(Ip^2-AC^2)^0.5;
12 disp('i) REACTIVE CURRENT (RC) is in rectangular
    form = '+string (RC) +' A ');
13 LC=sqrt(3)*Ip;
14 disp('i) LINE CURRENT (LC) is in rectangular form
    = '+string (LC) +' A ');
15 ALC=LC*0.85;
16 disp('i) ACTIVE LINE CURRENT (ALC) is in
    rectangular form = '+string (ALC) +' A ');
17 RLC=(LC^2-ALC^2)^0.5;
18 disp('i) REACTIVE LINE CURRENT (RLC) is in
    rectangular form = '+string (RLC) +' A ');
```

Scilab code Exa 3.54 Voltage load impedance

```
1 //EXAMPLE 3-54 PG NO
-207-208
```

```

2 Van=161.66+%i*0;
3 Vbn=-80.83-%i*140;
4 Vcn=-80.83+%i*140;
5 Z1=10+%i*0;
6 Z2=8.66+%i*5;
7 Z3=8.66-%i*5;
8 YA=1/Z1;
9 disp('i) ADMITTANCE (YA) is in rectangular form =
    '+string(YA) +' siemens ');
10 YB=1/Z2;
11 disp('ii) ADMITTANCE (YB) is in rectangular form
    = '+string(YB) +' siemens ');
12 YC=1/Z3;
13 disp('iii) ADMITTANCE (YC) is in rectangular form
    = '+string(YC) +' siemens ');
14 Von=-[(Van*YA)+(Vbn*YB)+(Vcn*YC)]/[YA+YB+YC];
15 disp('iv) VOLTAGE (Von) is in rectangular form =
    '+string(Von) +' V ');
16 Vao=Van-Von;
17 disp('v) VOLTAGE (Vao) is in rectangular form =
    '+string(Vao) +' V ');
18 Vbo=Vbn-Von;
19 disp('vi) VOLTAGE (Vbo) is in rectangular form =
    '+string(Vbo) +' V ');
20 Vco=Vcn-Von;
21 disp('vii) VOLTAGE (Vco) is in rectangular form =
    '+string(Vco) +' V ');

```

Scilab code Exa 3.55 Phase and Line Current

```

1 //EXAMPLE 3-55
          PG NO-208-209
2 Vab=400+%i*0;
3 Vbc=-220-%i*381.05;
4 Vca=-220+%i*381.05;

```

```

5 Z1=0+%i*25;
6 Z2=13+%i*7.5;
7 Z3=20+%i*0;
8 IAB=Vab/Z1;
9 disp('i) CURRENT (IAB) is in rectangular form =
    '+string (IAB) +' A ');
10 IBC=Vbc/Z2;
11 disp('i) CURRENT (IBC) is in rectangular form =
    '+string (IBC) +' A ');
12 ICA=Vca/Z3;
13 disp('i) CURRENT (ICA) is in rectangular form =
    '+string (ICA) +' A ');
14 IA=IAB-ICA;
15 disp('i) CURRENT (IA) is in rectangular form =
    '+string (IA) +' A ');
16 IB=IBC-IAB;
17 disp('i) CURRENT (IB) is in rectangular form =
    '+string (IB) +' A ');
18 IC=ICA-IBC;
19 disp('i) CURRENT (IC) is in rectangular form =
    '+string (IC) +' A ');

```

Scilab code Exa 3.59 current

```

1 //EXAMPLE 3-59 PG NO 267
2 V2=240-%i*14.35;
3 V1=240+%i*0;
4 VL=233.73-%i*8.938;
5 R1=0.6+%i*0.8;
6 R2=0.5+%i*0.866;
7 I1=(V1-VL)/R1;
8 I2=(V2-VL)/R2;
9 R3=16+%i*12;
10 I3=(VL/R3);
11 disp('i) current(I1) is in polar form = '+string (

```

```
I1)+'A ') ;  
12 disp('i) current(I2) is in polar form = '+string (I2)+'A ') ;  
13 disp('i) current(I3) is in polar form = '+string (I3)+'A ') ;
```

Chapter 4

network theorem

Scilab code Exa 4.4 Numbers of trees

```
1 //EXAMPLE 4-4 PG NO-224
2 A=[1 1 0 0 0 1;0 -1 1 -1 0 0;-1 0 -1 0 -1 0];
3 A1=[1 0 -1;1 -1 0;0 1 -1;0 -1 0;0 0 -1;1 0 0];
4 det(A*A1)=A*A1;
5 disp('i) Numbers of trees ([A*A^T]) is = '+
      string (det(A*A1)) +'');
```

Scilab code Exa 4.6 Currents

```
1 // EXAMPLE 4-6 PG NO-228
2 I1=-2.59*10^-3;
3 I2=-1.45*10^-3;
4 IR1=I1;
5 disp('i) CURRENT (IR1) is from A to B = '+
      string (IR1) +' A ');
6 IR2=I2;
7 disp('ii) CURRENT (IR2) is from B to E = '+
      string (IR2) +' A');
```

```

8 IR3=I1-I2;
9 disp('iii) CURRENT (IR1) is      from B to C = '+
      string (IR3) +' A ');
10 IR4=I1;
11 disp('vi) CURRENT (IR4) is      from C to F = '+
      string (IR4) +' A ');
12 IR5=I2;
13 disp('v) CURRENT (IR1) is      from D to C = '+
      string (IR5) +' A ');

```

Scilab code Exa 4.8 currents

```

1                                //EXAMPLE 4-8
                                         PG
                                         NO-230-231
2 V=25;
3Vm=0.64;
4Vn=3.05;
5R1=5;
6R2=9.64
7I1=(V-R2)/R1
8 disp('i) CURRENT (I1) is      = '+string (I1) +' A ');
9I2=R2/4;
10 disp('ii) CURRENT (I2) is      = '+string (I2) +' A ');
11 I3=(R2-Vn)/10;
12 disp('iii) CURRENT (I3) is      = '+string (I3) +' A ');
13 I4=(10-Vn)/8;
14 disp('vi) CURRENT (I4) is      = '+string (I4) +' A ');
15 I5=Vn/2;
16 disp('v) CURRENT (I5) is      = '+string (I5) +' A ');

```

Scilab code Exa 4.9 current

```
1 //EXAMPLE 4-9 PG NO-232-233
2 X=[40 -8 -20;-8 18 -6;-20 -6 36];
3 Y=[24 -8 -20;0 18 -6;0 -6 36];
4 Z=[40 24 -20;-8 0 -6;-20 0 36];
5 U=[40 -8 24;-8 18 0;-20 -6 0]
6 I1=det(Y/X);
7 disp('CURRENT = '+string((I1))+' A');
8 I2=det(Z/X);
9 disp(' CURRENT is = '+string(I2)+' A');
10 I3=det(U/X);
11 disp(' CURRENT is = '+string(I3)+' A');
12 IR3=I2;
13 disp(' CURRENT is = '+string(IR3)+' A');
14 IR4=0;
15 disp(' CURRENT is = '+string(IR4)+' A');
16 IR5=I1-I3;
17 disp(' CURRENT is = '+string(IR5)+' A');
18 IR6=I3;
19 disp(' CURRENT is = '+string(IR6)+' A');
```

Scilab code Exa 4.10 Current

```
1 //EXAMPLE 4-11 PG
2 I1=-1.28;
3 I2=-0.83;
4 I3=0.84;
5 IR1=-I1; //CURRENT
6 THROUGH 2.2 RESISTANCE
```

```

6 disp('i) Current (IR1) is = '+string(IR1) +
     A from B to A ');
7 IR2=-I1+I2; //CURRENT
   THROUGH 4.7 RESISTANCE
8 disp('ii) Current (IR2) is = '+string(IR2) +
     ' A from C to B ');
9 IR3=-I2+I3; //CURRENT
   THROUGH 6.8 RESISTANCE
10 disp('iii) Current (IR3) is = '+string(IR3)
      +' A from C to D ');

```

Scilab code Exa 4.12 current

```

1 //Example 4-12 PG NO234-235
2 VA=60.866;
3 VB=19.13;
4 R=60;
5 I60=(VA-VB)/R;
6 disp(' CURRENT is = '+string(I60)+ ' A');

```

Scilab code Exa 4.13 current

```

1 //Example 4-13 PG NO-235
2 X=[1 -0.5 2;-0.5 3.5 -4;-0.5 -1 0];
3 X1=[2 -0.5 -0.5;-4 3.5 -1;0 -1 2.5 ];
4 X2=[1 -0.5 -0.5;-0.5 3.5 -1;-0.5 -1 2.5];
5 V=det([X1-X]/X2); //V=VA-VC
6 disp('i) VOLTAGE (V) is = '+string(V) + ' V '
);
7 I2=0.5*1.566;
8 disp('i) Current (I2) is = '+string(I2) + ' A
');

```

Scilab code Exa 5.13 Current

```
1 //EXAMPLE 5-13 PG NO-305
2 Z1=10+%i*0;
3 Z2=-%i*5;
4 Z3=3+%i*4;
5 Z4=3-%i*4;
6 Z5=10+%i*2.5;
7 VTH=(Z1*Z2)/(Z3+Z2);
8 ZTH=2+((20-%i*15)/(3-%i*1));
9 ZL=VTH/(ZTH+Z5);
10 disp('i) VOLTAGE (VTH) is = '+string(VTH)+ 'V');
11 disp('i) IMPEDANCE (ZTH) is = '+string(ZTH)+ 'ohm
      ');
12 disp('i) IMPEDANCE (ZL) is = '+string(ZL)+ 'A');
```

Scilab code Exa 4.14 current

```
1 //EXAMPLE 4-14 PG NO-236
2 VA=61.38;
3 R1=60;
4 R2=110;
5 R3=25;
6 V1=120;
7 V2=40;
8 V3=60;
9 I120=(V1-VA)/R1;
10 disp(' CURRENT is = '+string(I120)+ ' A');
11 I40=(VA+V2)/R2;
12 disp(' CURRENT is = '+string(I40)+ ' A');
13 I60=(VA-V3)/R3;
14 disp(' CURRENT is = '+string(I60)+ ' A');
```

Scilab code Exa 4.16 current

```
1 //EXAMPLE 4-16          PG NO
   -236-237;
2 VA=1.96;
3 VB=3.2;
4 IBA=(VB-VA)/2;
5 disp(' CURRENT is = '+string(IBA)+ ' A');
```

Scilab code Exa 4.17 voltage

```
1 //EXAMPLE 4-17          PG NO-237
2 A=8.08;           //POTENTIAL
3 B=7.942;          //POTENTIAL
4 VAB=A-B;          //POTENTIAL DIFFERENCE
5 disp(' POTENTIAL DIFFERENCE is = '+string(VAB)+ ' V')
   ;
```

Scilab code Exa 4.19 currents

```
1 //EXAMPLE 4-19
   PG NO-236
2 i1=11.06;
3 i2=5.34;
4 i3=1.907;
5 IPR=i2-i3;
6 disp(' CURRENT is = '+string(IPR)+ ' A');
7 IRS=i2;
8 VRS=IRS*10^-3*15*10^3;
```

```
9 disp( ' VOLTAGE is = '+string(VRS)+ ' A' );
```

Scilab code Exa 4.21 current and power

```
1 //EXAMPLE 4-21 PG NO  
-239  
2 I1=4.46;  
3 I2=9.46;  
4 I3=10;  
5 I4=6.22;  
6 V1=110.8;  
7 IAB=I1  
8 disp( ' CURRENT is = '+string(IAB)+ ' A' );  
9 ICD=I2;  
10 disp( ' CURRENT is = '+string(ICD)+ ' A' );  
11 IFE=I3-I1;  
12 disp( ' CURRENT is = '+string(IFE)+ ' A' );  
13 IDE=I2-I4;  
14 disp( ' CURRENT is = '+string(IDE)+ ' A' );  
15 IHG=I4;  
16 disp( ' CURRENT is = '+string(IHG)+ ' A' );  
17 I5=5*V1  
18 disp( ' CURRENT is = '+string(I5)+ ' A' );
```

Scilab code Exa 4.22 voltage

```
1 //EXAMPLE 4-22 PG  
NO-39-240  
2 R1=50;  
3 R2=20;  
4 R3=10;  
5 V1=50;  
6 V2=100;
```

```
7 V=[(V1/R1)+(V2/R2)]/[(1/50)+(1/20)+(1/10)];  
8 disp(' Voltage is = '+string(V)+ ' V');
```

Scilab code Exa 4.23 current

```
1 //EXAMPLE 4-23 PG NO-240  
2 I1=-3/19;  
3 V=12.632;  
4 I6=I1+1;  
5 disp(' CURRENT is = '+string(I6)+ ' A');
```

Scilab code Exa 4.24 Current

```
1 //EXAMPLE 4-24 PG NO  
-240-241  
2 I1=9;  
3 I2=2.5;  
4 I3=2;  
5 IR3=I2-I3;  
6 disp(' CURRENT is = '+string(IR3)+ ' A');  
7 V=13.5;  
8 disp(' VOLTAGE is = '+string(V)+ ' V');
```

Scilab code Exa 4.25 Current

```
1 //EXAMPLE 4-25 PG  
NO-241  
2 //31-15I1-(I1-I2)+10V1=0  
3 // -10V1-(I2-I1)-4I2=0;  
4 //V1=31-5I1;
```

```
5 I1=5;
6 disp('i) Current (I1) is = '+string(I1) +' A
     ');
7 I2=-11;
8 disp('ii) Current (I2) is = '+string(I2) +' A
     ');
```

Scilab code Exa 4.28 Current

```
1 //EXAMPLE 4-28
    PG NO-243
2 I1=1.42;
3 I2=1.683;
4 I3=0.325;
5 Iba=I2-I1;
6 disp(' CURRENT is = '+string(Iba)+ ' A');
7 Ibd=I1-I3;
8 disp(' CURRENT is = '+string(Ibd)+ ' A');
9 Iac=I2;
10 disp(' CURRENT is = '+string(Iac)+ ' A');
11 Icd=I3;
12 disp(' CURRENT is = '+string(Icd)+ ' A');
```

Scilab code Exa 4.29 Power

```
1 //EXAMPLE 4-29
    PG
    NO-243
2 I1=2;                      //CURRENT
3 R=3;                      //RESISTANCE
4 P=I1*I1*R;                //POWER
5 disp(' POWER is = '+string(P)+ ' W');
```

Scilab code Exa 4.30 Current

```
1 //EXAMPLE 4-30 PG NO  
-244  
2 I3=-0.882;  
3 I=-I3;  
4 disp(' CURRENT is = '+string(I)+ ' A');

---


```

Scilab code Exa 4.32 Branch Current

```
1 //EXAMPLE 4-32 PG NO-245-246  
2 Vb=4.55;  
3 Vc=2.57;  
4 Vd=3.165;  
5 Iab=2*(-Vb+9);  
6 disp(' CURRENT is = '+string(Iab)+ ' A');  
7 Ida=2*Vd;  
8 disp(' CURRENT is = '+string(Ida)+ ' A');  
9 IbC=Vb-Vc;  
10 disp(' CURRENT is = '+string(Ibc)+ ' A');  
11 Idc=Vd-Vc;  
12 disp(' CURRENT is = '+string(Idc)+ ' A');  
13 Ibd=5*(Vb-Vd);  
14 disp(' CURRENT is = '+string(Ibd)+ ' A');  
15 Ica=Vc;  
16 disp(' CURRENT is = '+string(Ica)+ ' A');

---


```

Scilab code Exa 4.36 Current

//EXAMPLE 4-36 PG
NO-250-251

```

1
2 I1=0.3;
3 I2=-1.1;
4 V1=2*I1;
5 disp(' VOLTAGE is = '+string(V1)+' V');
6 V2=2*I2;
7 disp(' VOLTAGE is = '+string(V2)+' V');
8 V3=-5;
9 disp(' VOLTAGE is = '+string(V3)+' A');
10 V4=-(2*I1)+4;
11 disp(' VOLTAGE is = '+string(V4)+' V');
12 V5=2.8;
13 IAB=V4/2;
14 disp(' CURRENT is = '+string(IAB)+' A');
15 IAD=V5/2;
16 disp(' CURRENT is = '+string(IAD)+' A');
17 IAC=-V3/2;
18 disp(' CURRENT is = '+string(IAC)+' A');
19 IDB=V1/2;
20 disp(' CURRENT is = '+string(IDB)+' A');
21 IDC=-V2/2;
22 disp(' CURRENT is = '+string(IDC)+' A');
23 I=IAB+IAD+IAC-2;
24 disp(' CURRENT is = '+string(I)+' A');
```

Scilab code Exa 4.37 Current

//EXAMPLE 4-37 PG
NO-251-252

```

1
2 I1=5;
3 I2=2;
4 I3=1;
5 IAB=I1;
6 disp(' CURRENT is = '+string(IAB)+' A');
```

```
7 IBE=I1-I2;
8 disp(' CURRENT is = '+string(IBE)+ ' A');
9 IBC=I2;
10 disp(' CURRENT is = '+string(IBC)+ ' A');
11 ICE=I2+I3;
12 disp(' CURRENT is = '+string(ICE)+ ' A');
13 IDC=I3;
14 disp(' CURRENT is = '+string(IDC)+ ' A');
```

Scilab code Exa 4.38 Current

```
1 //EXAMPLE 4-38
PG NO
-252-253
2 VB=15;
3 VC=6;
4 V=20;
5 IAB=(V-VB)/1;
6 disp(' CURRENT is = '+string(IAB)+ ' A');
7 IBE=VB/IAB;
8 disp(' CURRENT is = '+string(IBE)+ ' A');
9 IBC=(VB-VC)/4.5;
10 disp(' CURRENT is = '+string(IBC)+ ' A');
11 ICE=VC/2;
12 disp(' CURRENT is = '+string(ICE)+ ' A');
13 IDC=1;
14 disp(' CURRENT is = '+string(IDC)+ ' A');
```

Scilab code Exa 4.41 Voltage And Current

```
1 //EXAMPLE-4-41
PG NO-254
2 I2=0.5;
```

```

3 I3=1.5;
4 R=11/3;
5 V=I3*R;
6 disp(' VOLTAGE is = '+string(V)+' V');
7 R1=20/9;
8 Req=(R*R1)/(R+R1);
9 disp(' RESISTANCE is = '+string(Req)+' ohm');
10 I=V/Req;
11 disp(' CURRENT is = '+string(I)+' A');

```

Scilab code Exa 4.43 Node Voltage

```

1 //EXAMPLE 4-43 PG NO
-256-257
2 X=[3 -1 -2;6 -1 -2;6 -5 -16];
3 disp('i) Ditermenent X is = '+string(det(X))
+ ' ');
4 X1=[0 -1 -2;80 -1 -2;40 -5 -16];
5 V1=X1/X;
6 disp('ii) Ditermenent V1 is = '+string(det(
V1)) +' V ');
7 X2=[3 0 -2;6 80 -2;6 40 -16];
8 V3=X2/X;
9 disp('iii) Ditermenent V3 is = '+string(det(
V3)) +' V ');
10 X3=[3 -1 0;6 -1 80;6 -5 40];
11 V4=X3/X;
12 disp('iv) Ditermenent V4 is = '+string(det(
V4)) +' V ');

```

Scilab code Exa 4.44 Current

```

1 //EXAMPLE 4-44 PG NO 257
2 // 6I1+14I2=20 I1-I2=-6
3 I1=-3.2;
4 I2=2.8;
5 disp('i) Current(I1) is = '+string(I1)+ ' A
');
6 disp('ii) Current (I2) is = '+string(I2)+ '
A ');

```

Scilab code Exa 4.46 Current

```

1 //EXAMPLE 4-46 PG NO
-258-259
2 X1=[10 -104-%i*200;0 205+%i*150];
3 X2=[200+%i*200 -104-%i*200;-104-%i*200 205+%i*150];
4 I1=det(X1/X2);
5 disp(' Current is in polar form= '+string(I1)+ ' A')
;
6 X3=[200+%i*200 10;-104-%i*200 0];
7 X4=[200+%i*200 -104-%i*200;-104-%i*200 205+%i*150];
8 I2=det(X3/X4);
9 disp(' Current is in polar form = '+string(I2)+ ' A')
;
10 V=10; //VOLTAGE
11 P=V*5.1*10^-2; //POWER
12 disp(' POWER is = '+string(P)+ ' W');
```

Scilab code Exa 4.47 V2

```

1 //EXAMPLE 4-47 PG
NO259-260
2 I2=0;
```

```

3 x=%i*1500;
4 y=30+%i*30;
5 V2=x/y; //VOLTAGE
6 disp(' VOLTAGE is in polar form = '+string(V2)+ ' V'
);

```

Scilab code Exa 4.48 Voltage

```

1 //EXAMPLE 4-48 PG NO
-260
2 Vm=63.43+%i*33.38;
3 V=100+%i*0;
4 V1=0+%i*50
5 R1=5+%i*0;
6 R2=8+%i*6;
7 R3=12+%i*16;
8 I1=(V-Vm)/R1;
9 disp('i) Current (I1) is = '+string(I1) +' A
');
10 I2=(V1-Vm)/R2;
11 disp('ii) Current (I2) is = '+string(I2) +' A
');
12 I3=(Vm)/R3;
13 disp('iii) Current (I3) is = '+string(I3) +' A
');
```

Scilab code Exa 4.49 Node Voltage

```

1 //EXAMPLE 4-49 PG NO
260-261
2 Vm=[10 -0.25;%i*25 0.75+%i*0.5]/[0.45-%i*0.5
-0.25;-0.25 0.75+%i*0.5];
```

```

3 disp('i) Voltage (Vm) is = '+string(det(Vm))
      + ' V');
4 Vn=[0.45-%i*0.5 10;-0.25 0.75+%i*0.5]/[0.45-%i*0.5
      10;-0.25 0.75+%i*0.5];
5 disp('ii) Voltage (Vn) is = '+string(det(Vn))
      + ' V');

```

Scilab code Exa 4.50 Voltage Vcd

```

1 //EXAMPLE 4-50 PG NO
      261-262
2 I1=(17.32+%i*10)/(10+%i*10);
3 VCA=I1*5;
4 disp('i) VOLTAGE (VCA) is = '+string(VCA) +
      ' V');
5 I2=(35.35-%i*35.35)/(5-%i*5);
6 VBD=(-I2)*5;
7 disp('ii) VOLTAGE (VBD) is = '+string(VBD) +
      ' V');
8 VCD=VCA+VBD;
9 disp('iii) VOLTAGE (VCD) is = '+string(VCD) +
      ' V');

```

Scilab code Exa 4.51 Current

```

1 //EXAMPLE 4-51 PG
      NO-262
2 X1=[14+%i*6 -%i*10 20+%i*0; -%i*10 24+%i*6 -8.66+%i
      *5; -%i*10 -(4-%i*4) 0];
3 X2=[14+%i*6 -%i*10 -%i*10; -%i*10 24+%i*6 -(4-%i*4)
      ; -%i*10 -(4-%i*4) (34-%i*4)]
4 I3=det(X1/X2);

```

```
5 disp('i) Current (I3) is = '+string(I3) + ' A  
') ;
```

Scilab code Exa 4.52 Voltage

```
1 //EXAMPLE 4-52 PG NO-263  
2 X=[(6+%i*2) (100+%i*0);(-6-%i*3.32) 0];  
3 X1=[(6+%i*2) (-6-%i*3.32); (-6-%i*3.32) (16+%i*12)  
];  
4 I2=det(X/X1);  
5 disp('i) Current (I2) is = '+string(I2) + ' A  
');  
6 V=10*I2;  
7 disp('ii) VOLTAGE (V) is = '+string(V) + ' V  
');
```

Scilab code Exa 4.56 Input Impedance

```
1 //EXAMPLE 4-56 PG NO-265  
2 I1=5.92-%i*4.833;  
3 V=12+%i*0;  
4 Z=V/I1;  
5 disp('i) Input Impedance (Z) is = '+string(Z  
)+ ' ohm ' );
```

Scilab code Exa 4.57 Primary and Secondary Current and voltage

```
1 //EXAMPLE 4-57 PG  
N 265-266
```

```

2 Z1=[200 +%i*4;0 5+;%i*10];
3 Z2=[2+;%i*5 %i*4;%i*4 5+;%i*10];
4 I1=det(Z1/Z2);
5 disp('i) Current (I1) is = '+string(I1)+', A
');
6 Z3=[2+;%i*5 %i*4;%i*4 5+;%i*10];
7 Z4=[2+;%i*5 %i*4;%i*4 5+;%i*10];
8 I2=det(Z3/Z4);
9 disp('ii) Current (I2) is = '+string(I2)+',
A ');

```

Scilab code Exa 4.58 current

```

1
2 // Example : 4.58
3
4 v1=233.73-%i*8.934;
5 vs=240+%i*0;
6 r1=0.6+;%i*0.8;
7 i1=(vs-v1)/r1;
8 disp('the value of I1 is = '+string(i1)+', Amp');
9 r2=0.5+;%i*0.866;
10 vs1=239.5-%i*14.359;
11 i2=(vs1-v1)/r2;
12 disp('the value of I1 is = '+string(i2)+', Amp');
13 r3=16+;%i*12;
14 il=i1/r3;
15 disp('the value of I1 is = '+string(il)+', Amp');

```

Scilab code Exa 4.62 I1 I2 Active and Reactive Power

1 //EXAMPLE 4-61 PG NO
-267-268

```
2 I1=0.05-%i*6.49;
3 I2=0.040+%i*0.02;
4 R1=100;
5 R2=4+%i*200;
6 Vab=(R1*I2)-[R2*(I1-I2)];
7 disp('i) VOLTAGE (Vab) is = '+string(Vab)+ ' V
');
```

Chapter 5

Network Theorem

Scilab code Exa 5.1 Current

```
1      //EXAMPLE 5-1  PG NO-294
2 TR1=32;
3 R1=20;
4 R2=30;
5 R3=20;
6 V=32;
7 Ir11=V/TR1;
8 Ir12=Ir11*(R1/(R1+R2));
9 Ir13=Ir11*(R2/(R1+R3));
10 TR2=40;
11 I#r2=R3/TR2;
12 I#r1=(R3/TR2)*I#r2;
13 I#r3=(R3/TR2)*I#r1;
14 Ir3=Ir13+I#r3;
15 Ir1=Ir11-I#r1;
16 Ir2=Ir12-I#r2;
17 disp('i) current (Ir3) is = '+string (Ir3)+'A ');
18 Ir3=Ir13+I#r3;
19 disp('i) current (Ir1) is = '+string (Ir1)+'A ');
20 Ir1=Ir11-I#r1;
21 disp('i) current (Ir2) is = '+string (Ir2)+'A ');
```

```
22 Ir2=0.5-0.4;
```

Scilab code Exa 5.2 Voltage

```
1 //EXAMPLE 5-2 PG NO-295
2 Vab1=7.059;
3 Vab2=2.353;
4 Vab=Vab1+Vab2;
5 disp('i') Votage(Vab) is = '+string(Vab)+'V');
```

Scilab code Exa 5.3 Current

```
1 //EXAMPLE 5-3 PG NO-296
2 TR1=(90/14); //TOTAL RESISTANCE
3 R1=8;
4 R2=6;
5 R3=3;
6 E1=10; //VOLTS
7 IR11=E1*(1/TR1); //
    Current in resistance one
8 IR12=IR11*(R1/(R1+R2)); //
    resistance Two
9 IR13=IR11*(R2/(R1+R2)); //
    resistance one
10 IR14=0;
11 TR2=10; //TOTAL RESISTANCE
12 IR23=TR2/E1;
13 IR21=IR23*(R2/(R2+R3));
14 IR22=IR23*(R3/(R2+R3));
15 IR24=0;
16 IR34=(10/12);
17 IR32=TR2/(R2+(R3*R1/11));
18 IR31=IR32*(R1/(R1+R3));
```

```

19 IR33=IR32*(R3/(R1+R3));
20 IR1=(14-6-8)/9;
21 IR2=(8+3-11)/9;
22 IR3=(6+3)/9-1;
23 IR4=IR34+0+0;
24 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR11)+'V ');
25 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR12)+'V ');
26 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR13)+'V ');
27 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR14)+'V ');
28 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR21)+'V ');
29 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR22)+'V ');
30 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR23)+'V ');
31 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR24)+'V ');
32 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR31)+'V ');
33 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR32)+'V ');
34 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR33)+'V ');
35 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR34)+'V ');
36 disp('i) CURRENT IN RESISTANCE ONE is = '+string
      (IR1)+'V ');
37 disp('i) CURRENT IN RESISTANCE TWO is = '+string
      (IR2)+'V ');
38 disp('i)CURRENT IN RESISTANCE THREE is = '+
      string (IR3)+'V ');
39 disp('i) CURRENT IN RESISTANCE FOUR is = '+string
      (IR4)+'' );

```

Scilab code Exa 5.4 Current

```
1
2 E1=100+%i*0;
3 E2=43.30+%i*25
4 Z1=1+%i*3;
5 Z2=1-%i*3;
6 Z3=2+%i*4;
7 Z4=3-%i*3
8 Z5=1+%i*5;
9 Z6=2-%i*8;
10 Iab1=E1/((Z1+Z2)+((Z3*Z4)/(Z3+Z4)));
11 I2=E2/((Z5-Z6)+((Z3*Z1+Z2)/(Z3+Z1+Z2)));
12 Iab2=(I2*Z3)/(Z3+Z1+Z2)
13 disp('i) CURRENT (Iab1) is = '+string(Iab1)+ 'A '
);
14 disp('i) CURRENT (I2) is = '+string(I2)+ 'A ');
15 disp('i) CURRENT (Iab2) is = '+string(Iab2)+ 'A '
);
```

Scilab code Exa 5.6 Current

```
1 //EXAMPLE      5-6      PG NO=299-300
2 TZ1=54.90+%i*85;
3 Z1=40+%i*0;
4 Z2=250-%i*132.625;
5 Z3=0-%i*132.625;
6 IR1=[Z1/TZ1]*[Z3/Z2];
7 disp(' CURRENT is in polar form = '+string(IR1)+ 'A '
);
8 TZ2=173.64+%i*48.84;
9 Z4=20+%i*0;
```

```

10 Z5=250+%i*377;
11 Z6=0+%i*377;
12 IR2=[Z4/TZ2]*[Z6/Z5];
13 disp(' CURRENT is in polar form = '+string(IR2)+'A')
);
14 IR=[IR1^2+IR2^2]^0.5;
15 disp(' CURRENT is in polar form = '+string(IR)+'A')
;
```

Scilab code Exa 5.7 Power Total Power

```

1 //EXAMPLE 5-7 PG NO-300
2 IR1=0.185; // current
3 IR2=0.0924; // current
4 R=250; // Resistance
5 P1=IR1*IR1*R; //POWER
6 P2=IR2*IR2*R; //POWER
7 P=P1+P2; //POWER
8 disp('i) POWER (P1) is = '+string(P1)+'W');
9 disp('i) POWER (P2) is = '+string(P2)+'W');
10 disp('i) POWER (P) is = '+string(P)+'W');
```

Scilab code Exa 5.8 Current

```

1 //EXAMPLE 5-8 PG NO-301
2 Vcb=40/7;
3 Vth=-6.2857;
4 RTH=9.4286;
5 R=10;
6 I=-Vth/[R+RTH];
7 disp(' CURRENT is in polar form = '+string(I)+'A');
```

Scilab code Exa 5.9 Deflection

```
1 //EXAMPLE 5-9 PG NO-302
2 V=10; // Voltage
3 S=0.5*10^-5;
4 R1=2500;
5 R2=1050;
6 R3=200;
7 R4=500;
8 Van=(V/(R1+R4))*R4;
9 Vbn=(V/(R2+R3))*R3;
10 VTH=Van-Vbn;
11 RTH=((R1*R4)/(R1+R4))+((R2*R3)/(R2+R3));
12 I=VTH/(RTH+100);
13 GD=I/S; // Galvonater
    Deflection
14 disp('i) voltage (Van) is = '+string(Van)+')';
15 disp('i) Voltage (Vbn) is = '+string(Vbn)+')';
16 disp('i) Voltage (VTH) is = '+string(VTH)+')';
17 disp('i) Resistance (RTH) is = '+string(RTH)+'
    ohms ');
18 disp('i) CURRENT (I) is = '+string(I)+')';
19 disp('i) Galvoneter Deflection (GD) is = '+string
    (GD)+')';
```

Scilab code Exa 5.10 Power dissipated

```
1 //EXAMPLE 5-10 PG NO-303
2 I1=(58/21);
3 R1=2;
4 R2=5;
5 R3=15;
```

```

6 VTH=R1+I1;                                //Thevenins Voltage
7 RTH=(1*(R2+R3))/(1+(R2+R3));           //Thevenins
     resistance
8 I=VTH/(10+RTH);                         //CURRENT
9 P=I*I*10;                                 //POWER
10 disp('i) Thevenins voltage (VTH) is = '+string(
      VTH)+'V ');
11 disp('i) Thevenins resistance (RTH) is = '+
      string(RTH)+'ohm ');
12 disp('i) current (I) is = '+string(I)+'A ');
13 disp('i) power (P) is = '+string(P)+'W ');

```

Scilab code Exa 5.11 Voltage

```

1                                         //EXAMPLE 5-11
                                         PG NO-303
2 X=8+%i*8;                               //X=I1/V1;
3 X1=0+%i*30/25+%i*80;                  //X1=Va/V1;
4 V1=[20*(25+%i*80)]/(0+%i*30);
5 disp(' VOLTAGE is in polar form = '+string(V1)+'V')
;
```

Scilab code Exa 5.12 Current

```

1                                         //EXAMPLE 5-12    PG NO304-305
2 I2=0.411+%i*0;
3 VTH=5+%i*0-(I2*5);
4 ZTH=1/(1+(1/2)+(1/5));
5 Iab=VTH/(ZTH+(2+%i*2));
6 disp('i) VOLTAGE (VTH) is in polar form = '+
      string(VTH)+'V ');
7 disp('i) IMPEDANCE (ZTH) is      in polar form = '+
      string(ZTH)+'ohms ');

```

```
8 disp('i) Current (Iab) is in polar form = '+  
      string (Iab)+'A');
```

Scilab code Exa 5.13 Current

```
1 //EXAMPLE 5-13 PG NO-305  
2 Z1=10+%i*0;  
3 Z2=-%i*5;  
4 Z3=3+%i*4;  
5 Z4=3-%i*4;  
6 Z5=10+%i*2.5;  
7 VTH=(Z1*Z2)/(Z3+Z2);  
8 ZTH=2+((20-%i*15)/(3-%i*1));  
9 ZL=VTH/(ZTH+Z5);  
10 disp('i) VOLTAGE (VTH) is = '+string (VTH)+'V');  
11 disp('i) IMPEDANCE (ZTH) is = '+string (ZTH)+'ohm');  
12 disp('i) IMPEDANCE (ZL) is = '+string (ZL)+'A');
```

Scilab code Exa 5.14 Current

```
1 //EXAMPLE 5-14 PG NO-306  
2 V1=120;  
3 V2=65;  
4 R1=40;  
5 R2=60;  
6 IN=(V1/R1)+(V2/R2);  
7 RN=(R1*R2)/(R1+R2);  
8 IRL=IN*(RN/(RN+11));  
9 disp('i) Current (IN) is = '+string (IN)+'A');  
10 disp('i) Current (RN) is = '+string (RN)+'ohms')  
     ;  
11 disp('i) Current (IRL) is = '+string (IRL)+'A');
```

Scilab code Exa 5.15 Current

```
1 //EXAMPLE 5-15 PG NO-306
2 I2=-0.67;
3 R1=8;
4 R2=2;
5 R3=5;
6 RN=R1+((R2*R3)/(R2+R3));
7 I=-I2*(RN/(10+RN));
8 disp('i) Resistance (RN) is = '+string(RN)+'ohm
      ');
9 disp('i) Current3 (I) is = '+string(I)+'A');
```

Scilab code Exa 5.16 Impedance

```
1 //EXAMPLE 5-16 PG NO-307
2 Z1=2.828+%i*2.828;
3 Z2=0+%i*2.5;
4 R=10;
5 Z3=3+%i*4;
6 IN=Z1+Z2;
7 ZN=(R*Z3)/(R+Z3);
8 disp('i) current (IN) is = '+string(IN)+'A');
9 disp('i) impedance (ZN) is = '+string(ZN)+'ohms
      ');
```

Scilab code Exa 5.17 Impedance

```
1 //EXAMPLE 5-17 PG NO-307-308
```

```

2 Z1=60+%i*0;
3 Z2=15.6-%i*9;
4 Z3=10.42-%i*6;
5 Z4=25.98-%i*15;
6 Z5=11.92-%i*1.4;
7 I=2.5*10^-3;
8 Vab=((Z1*Z2)/(Z3+Z2));
9 ZTH=(Z3*Z2)/(Z3+Z2);
10 Vax=I*Z3*10^3;
11 Vxy=Vab-Z4;
12 Zxy=ZTH+Z3;
13 IN=Z5/(Zxy*10^3);
14 ZN=Zxy;
15 disp('i) Voltage (Vab) is = '+string(Vab)+'V');
16 disp('i) Impedance (ZTH) is = '+string(ZTH)+'K
    ohms ');
17 disp('i) Voltage (Vax) is = '+string(Vax)+');
18 disp('i) Voltage (Vxy) is = '+string(Vxy)+'V');
19 disp('i) Impedance (Zxy) is = '+string(Zxy)+'K
    ohms ');
20 disp('i) Current (IN) is = '+string(IN)+'A ');
21 disp('i) Impedance (ZN) is = '+string(ZN)+'K
    ohms ');

```

Scilab code Exa 5.18 Current and Resistance

```

1 //example 5-18 pg no-308-309
2 V=120;
3 R1=1200;
4 R2=400;
5 Vab=(V*R1)/(R1+R2);
6 Rab=(R1*R2)/(R1+R2);
7 IN=40/450;
8 RN=450;
9 disp('i) Voltage (Vab) is = '+string(Vab)+'V')

```

```

;
10 disp('i) Resistance (Rab) is = '+string (Rab)+'
      ohms ');
11 disp('i) Current (IN) is = '+string (IN)+' mA');
12 disp('i) Resistance (RN) is = '+string (RN)+'
      ohms ');

```

Scilab code Exa 5.19 RL Power

```

1 //EXAMPLE -19 PG NO-312
2 V=360;
3 R1=150;
4 R2=30;
5 Pm=900;
6 RL=25;
7 VTH=(V*R1)/(R1+R2);
8 RTH=(R1*R2)/(R1+R2);
9 TR=30+((R1*RL)/(R1+RL));           // total resistance
10 I=V/TR;                           // Current supplied
      by battery
11 P=V*7;                            // Power supplied by
      battery
12 %PL=Pm*100/P                      // Percentage of
      power delivered to load
13 disp('i) Voltage (VTH) is = '+string (VTH)+'V ');
14 disp('i) Resistance (RTH) is = '+string (RTH)+'
      ohms ');
15 disp('i) Total resistance (TR) is = '+string (TR)
      +' ohms ');
16 disp('i) Current (I) is = '+string (I)+' A ');
17 disp('i) power (P) is = '+string (P)+' W ');
18 disp('i) Percentage of power (%PL) is = '+string
      (%PL)+' % ');

```

Scilab code Exa 5.20 VOLTAGE

```
1 //EXAMPLE 5-20 PG NO -313
2 Z1=5+%i*0;
3 Z2=4-%i*3;
4 Z3=3+%i*3;
5 Z4=%i*3;
6 VTH=((Z1)/(3(((Z4*Z2)/(Z3-Z4)))))*(Z4/(Z3-Z4))*(-Z4);
7 disp('i) Voltage (VTH) is = '+string(VTH)+ 'V');
```

Scilab code Exa 5.21 ZL Power

```
1 //EXAMPLE 5-21 PG NO -313-314
2 Z1=8.66+%i*5;
3 Z2=%i*1;
4 VTH=Z1-(Z1-1)*0.9;
5 ZTH=Z2+((9*1)/(9+1));
6 I=VTH/((0.9+%i*1)+(0.9-%i*1));
7 P=1.02^2*0.9;
8 disp('i) Voltage (VTH) is = '+string(VTH) +' V ');
9 disp('i) Impedance(ZTH) is = '+string(ZTH) +' ');
10 disp('i) Current (I) is = '+string(I) +'A ');
11 disp('i) Power (VTH) is = '+string(P) +' W');
```

Scilab code Exa 5.22 VOLTAGE

```

1 //EXAMPLE 5-22 PG NO-315-316
2 I1=100;
3 I2=80;
4 I3=5;
5 R1=100;
6 R2=50;
7 R3=200;
8 IN=I1+I2-I3;
9 X=1/R1+1/R2+1/R3; // 1/RN=X
10 RN=X;
11 VTH=IN*RN;
12 RTH=RN
13 disp('i) Voltage (VTH) is = '+string(IN) +'V');
14 disp('i) Voltage (VTH) is = '+string(1/RN) +'V'
);
15 disp('i) Voltage (VTH) is = '+string(VTH) +'V')
;
16 disp('i) Voltage (VTH) is = '+string(RTH) +'V')
;
```

Scilab code Exa 5.23 Vo

```

1 //EXAMPLE 5-23 PG -NO 316-317
2 V11=-5;
3 V12=5;
4 V13=0;
5 G1=1/2200;
6 G2=1/3300;
7 G3=1/1500;
8 V01=((V11*G1)+(V12*G2)+(V13*G3))/(G1+G2+G3);
9 V21=-5;
10 V22=10;
11 V23=0;
12 V02=((V21*G1)+(V22*G2)+(V23*G3))/(G1+G2+G3);
13 disp('i) Voltage (V01) is = '+string(V01) +'V')
```

```
14 disp('i) Voltage (V02) is = '+string (V02) +'V')  
;
```

Scilab code Exa 5.24 Voltage

```
1 Z1=10+%i*0;  
2 Z2=99.33-%i*49.09222;  
3 Z3=20+%i*0;  
4 Z4=10+%i*20;  
5 Z5=20.03+%i*30.03;  
6 Z6=15+%i*20;  
7 Z7=89.32-%i*49.105;  
8 IN=Z1+Z2-Z3;  
9 ZN=1/((1/Z4)+(1/Z5)+(1/Z6));  
10 VTH=(Z7/1000)*ZN;  
11 ZTH=ZN  
12 disp('i) Current (IN) is in rectangular form =  
      '+string (IN) +'V');  
13 disp('i) Impedance (1/ZN) is in rectangular form  
      = '+string (1/ZN) +'V');  
14 disp('i) Voltage (VTH) is in rectangular form =  
      '+string (VTH) +'V');  
15 disp('i) Impedance (ZTH) is in rectangular form  
      = '+string (ZTH) +'ohm');
```

Scilab code Exa 5.25 Current

```
1 //EXAMPLE 5-25  
          PG NO  
          -318-319  
2 I1=4.4-%i*1.012;                                //
```

Current

```

3 I2=I1*[(%i*5)/(3+%i*9)];
4 Z1=1;
5 I11=[I2/[10*%i*5]]*[%i*5/10+%i*5];
6 disp(' Current is in polar form = '+string(I1)+'A')
    ;
7 disp(' Current is in polar form = '+string(I2)+'A')
    ;
8 disp(' Current is in polar form = '+string(I11)+'A'
    );
9 I12=I1-I11;
10 disp(' Current is in polar form = '+string(I12)+'A'
    );

```

Scilab code Exa 5.26 Current

```

1 //EXAMPLE      5-26      PG NO-319-320
2 Z1=70.71+%i*70.71;
3 Z2=10+%i*5;
4 Z3=-%i*5;
5 Z4=%i*5;
6 Z5=5-%i*5;
7 X1=[Z2 Z3 Z1,Z3 10 0,0 Z4 0];
8 X2=[Z2 Z3 0,Z3 10 Z4,0 Z4 Z5];
9 X3=[0 Z3 0,0 10 Z4,Z1 Z4 Z5];
10 X4=[Z2 Z3 0,Z3 10 Z4,0 Z4 Z5];
11 I3=X1/X2;
12 I1=X3/X4;
13 disp('i) Current (I3) is in polar = '+string (I3
    ) +' A ');
14 disp('i) Current (I1) is in polar = '+string (I1
    ) +' A ');

```

Scilab code Exa 5.27 Delta to Star

```

1      //EXAMPLE 5-27    PG NO-321
2 Z1=(6-%i*2.41);           //Impedance
3 Z2=(0-%i*9.64);           //Impedance
4 Z3=4+%i*0;                //Impedance
5 Z4=2+%i*0;                //Impedance
6 Z5=0-%i*2.41;             //Impedance
7 Za=Z2/Z1;                 //Impedance
8 Zb=(Z3*Z4)/Z1;            //Impedance
9 Zc=(Z4*Z5)/Z1;            //Impedance
10 disp('i) Impedance (Za) is in polar = '+string
     (Za) +' ohms ');
11 disp('ii) Impedance (Zb) is in polar = '+string
     (Zb) +' ohms ');
12 disp('iii) Impedance (Zc) is in polar = '+string
     (Zc) +' ohms ');

```

Scilab code Exa 5.28 Total Impedance

```

1      //EXAMPLE 5-28    PG NO-322
2 Z1=0.6-%i*1.2;
3 Z2=0.6-%i*1.2;
4 Z3=1.2+%i*0.6;
5 Z=Z1+(((Z2+3)*(Z3+%i*3))/(Z2+3+Z3+%i*3));
6 disp('i) Impedance (Z) is in polar = '+string (Z
     ) +' ohms ');

```

Scilab code Exa 5.29 Current

```

1      //EXAMPLE 5-29    PG NO 323
2 V1=5;                      //Voltage
3 V2=0.05;                    //Voltage
4 R1=100;                     //Resistance
5 R2=1000;                    //Resistance

```

```

6 R3=85;
7 R4=880;;
8 I1=0.00266; //Current
9 I2=0.02676; //Current
10 Va=V1-R1*I2;
11 Vb=V1-R2*I1;
12 VTH=Va-Vb;
13 RTH=((R1*R3)/(R1+R3))+(R2*R4)/(R2+R4)
14 I=(0.016)/(RTH+20);
15 disp('i) Voltage (Va) is in polar = '+string(Va
    ) +' V ');
16 disp('i) Voltage (Vb) is in polar = '+string(Vb
    ) +' V ');
17 disp('i) Voltage (VTH) is in polar = '+string(
    VTH) +' V ');
18 disp('i) Resistance (RTH) is in polar = '+string(
    (RTH) +' ohms ');
19 disp('i) Current (I) is = '+string(I) +' A ')
;
```

Scilab code Exa 5.30 Current

```

1 //EXAMPLE 5-30 PG NO 324-325
2 V=25; //Voltage
3 R1=50; //RESISTANCE
4 R2=35; //RESISTANCE
5 R3=60; //RESISTANCE
6 R4=10;
7 VTH=V-(R1*(R2/R3)); //THEVENINS VOLTAGE
8 RTH=(R1*R4)/R3;
9 I40=- (VTH/(40+RTH));
10 V40=40*I40;
11 disp('i) Impedance (VTH) is = '+string(VTH) +
    ' V ');
12 disp('i) Impedance (RTH) is = '+string(RTH) +
    '
```

```

        ohm ') ;
13 disp('i) Impedance (I40) is      = '+string (I40) +
     A ')';
14 disp('v) Impedance (V40) is      = '+string (V40) +
     V ');

```

Scilab code Exa 5.31 Current

```

1 //EXAMPLE 5-31    PG NO-326;
2 V=25;
3 R1=50;
4 R2=40;
5 R3=10;
6 I=(V/(R1+((R2*R3)/(R2+R3))))*(R3/(R2+R3));
7 disp('i) Current (I) is      = '+string (I) +' A ');

```

Scilab code Exa 5.32 RL for Pmax

```

1 //EXAMPLE 5-32    PG NO=326
2 V1=60;           //VOLTAGE
3 V2=50;           //VOLTAGE
4 V3=100;          //VOLTAGE
5 R1=60;           //RESISTANCE
6 R2=30;           //RESISTANCE
7 R3=40;           //RESISTANCE
8 VTH=V2+(R2*(2/3))-(R1*1);
9 RTH=((R1*R2)/(R1+R2))+((R1*R3)/(R1+R3));
10 RL=RTH;
11 I=VTH/(RTH+RTH);           //CURRENT
12 P=(I*I)*RL;                //POWER
13 disp('i) Voltage (VTH) is      = '+string (VTH) +' V
     ');

```

```

14 disp('i) Resistance (RTH) is      = '+string (RTH) +' '
      );
15 disp('i) Load Resistance (RL) is      = '+string (RL)
      +' ohm ');
16 disp('i) Current (I) is      = '+string (I) +' A ');
17 disp('i) Power (P) is      = '+string (I) +' W ');

```

Scilab code Exa 5.33 Current

```

1           //EXAMPLE 5-33    PG NO=327
2 R1=15;      //RESISTANCE
3 R2=8;       //RESISTANCE
4 R3=12;      //RESISTANCE
5 R4=10;
6 R5=5.14;;
7 R6=7.429;
8 R7=32.74;
9 V=60;
10 Ra=(R1*R2)/(R1+R2+R3);
11 Rb=(R3*R2)/(R1+R2+R3);
12 Rc=(R1*R3)/(R1+R2+R3);
13 TR=R4+R5+((R6*R7)/(R6+R7));          //TOTAL RESISTANCE
14 I=V/TR
15 disp('i) Resistance (Ra) is      = '+string (Ra) +' 
      ohms ');
16 disp('i) Resistance (Rb) is      = '+string (Rb) +' 
      ohms ');
17 disp('i) Resistance (Rc) is      = '+string (Rc) +' 
      ohms ');
18 disp('i) Total Resistance (TR) is      = '+string (TR)
      +' ohms ');
19 disp('i) Current (I) is      = '+string (I) +' A ');

```

Scilab code Exa 5.34 Pmax Total Power RL

```
1 //EXAMPLE 5-34 PG NO-327-328
2 V=10;
3 R1=1;
4 R2=2;
5 R3=8.5;
6 VTH=V*(R1/R2); //Thevenins
    Voltage
7 RTH=R2+((R1*R1)/(R1+R1))+R2; //Thevenins
    Resistance
8 Pmax=(5/9)^2*RTH;
9 TR=R1+((R1*R3)/(R1+R3)); //Total Resistance
10 TP=V*(V/TR); //Total Power
11 disp('i) Voltage (VTH) is = '+string(VTH) +' V
');
12 disp('i) Resistance (RTH) is = '+string(RTH) +' ohms ');
13 disp('i) Power (Pmax) is = '+string(Pmax) +' W
');
14 disp('i) Total resistance (TR) is = '+string(TR) +' ohms ');
15 disp('i) Total Power (TP) is = '+string(TP) +' W');
```

Scilab code Exa 5.35 Thevenins equivalent circuits

```
1 //EXAMPLE 5-35 PG NO-328-329
2 Va=6; //VOLTAGE at PONT A
3 Vb=-3; //VOLTAGE at POINT B
4 VTH=Va-Vb;
5 R1=1;
6 R2=2;
7 R3=3;
8 RTH=((R2*R3)/(R2+R3))+((R1*R3)/(R1+R3));
```

```
9 disp('i) Voltage (VTH) is      = '+string (VTH) +' V
      ');
10 disp('i) Resistance (RTH) is   = '+string (RTH) +' ohm');
```

Scilab code Exa 5.36 maximum Power

```
1 //EXAMPLE 5-36
          PG NO
          =329
2 I1=-10;           //CURRENT
3 Vpc=15;
4 I2=7.5;
5 Vqc=I2*I1;
6 disp(' Voltage is      = '+string(Vqc) +'V');
7 Vpq=Vpc-Vqc;
8 disp(' Voltage is      = '+string(Vpq) +'V');
9 RTH=1.406;
10 Pmax=[I2/(2*RTH)]^2*RTH;
11 disp(' Power is      = '+string(Pmax) +'W');
```

Scilab code Exa 5.37 Current

```
1 //EXAMPLE 5-37
          PG
          NO-330-331
2 R=8;
3 R1=12.67;
4 R2=4;
5 R3=10;
6 R4=3.077;
7 R5=13.077;
```

```

8 R50=9.9;                                //RESISTANCE AT 50 V
    BATTERY
9 V=50;                                     //VOLTAGE
10 I1=V/R50;                                 //CURRENT
11 I=I1*[R/(R+R1)]; 
12 disp(' Current is (I1) = '+string(I1)+'A');
13 disp(' Current is (I) = '+string(I)+'A');
14 R100=R+[(R2*(R3+R4))/(R2+R3+R4)];
15 disp(' Resistance at 100 (R100) is = '+string(R100)
      )+'ohm');
16 I2=100/R100;
17 disp(' Current is (I2) = '+string(I2)+'A');
18 I3=[(I2*R2)/(R2+R5)];
19 disp(' Current is (I3) = '+string(I3)+'A');
20 I10=I3-I;
21 disp(' Current is (I10) = '+string(I10)+'A');

```

Scilab code Exa 5.38 Current

```

1 //EXAMPLE   5-38   PG   NO-331
2 R1=100;
3 R2=4;
4 R3=8;
5 R4=50;
6 R5=5;
7 VTH=(R1*((R2)/(R2+R3)))-((R3*R4)/(R3+R5));
8 RTH=((R3*R5)/(R3+R5))+((R2*R3)/(R2+R3));
9 I=VTH/(10+RTH);
10 disp('i) Voltage (VTH) is = '+string(VTH) +' V
      ');
11 disp('i) Resistance (RTH) is = '+string(RTH) +' ohm ');
12 disp('i) Current (I) is = '+string(I) +' A ');

```

Scilab code Exa 5.39 RL and Pmax

```
1 //EXAMPLE 5-39    PG NO-331
2 V=36;
3 R1=5;
4 R2=11;
5 R3=6;
6 VTH=V*(R1/R2);
7 RTH=(R1*R3)/(R1+R3);
8 R=RTH;
9 Pmax=(VTH/(2*RTH))^2*(RTH);
10 disp('i) Voltage (VTH) is = '+string(VTH) +' V
      ');
11 disp('i) Resistance (RTH) is = '+string(RTH) +' ohm
      ');
12 disp('i) Maximum Power (Pmax) is = '+string(
      Pmax) +' W');
```

Scilab code Exa 5.40 R and Current

```
1 //EXAMPLE 5-40    PG NO-331-332
2 R1=3;
3 R2=2;
4 R3=12;
5 R4=4;
6 R5=8;
7 V=10;
8 R=R3/(R1/R2);
9 TR=R4+((R2*R5)/(R2+R5))+((R1*R3)/(R1+R3));
10 I=V/TR;
11 Ir=I*(R2/(R5+R2));
```

```

12 disp('i) Resistance (R) is      = '+string (R) +' ohm ');
13 disp('i) Total Resistance (TR) is      = '+string (TR) +' ohm ');
14 disp('i) Current (I) is      = '+string (I) +' A ');
15 disp('i) Current (Ir) is      = '+string (Ir) +' A ';

```

Scilab code Exa 5.41 Current

```

1 //EXAMPLE 5-41 PG NO-332-333
2 VTH=10;
3 V=10;
4 R1=10;
5 R2=10;
6 R3=16.67;
7 R4=50;
8 R5=5.56;
9 R6=3.33;
10 RTH=V+R5+(((R1+R3)*(R4+R6))/(R1+R3+R4+R6));
11 I=(V/RTH)-0.4;
12 disp('i) Resistance (RTH) is      = '+string (RTH) +' ohm ');
13 disp('i) Current (I) is      = '+string (I) +' A ')
;
```

Scilab code Exa 5.42 Current

```

1 //EXAMPLE 5-42 PG NO-333
2 V=100;           // Voltage
3 RTH=0;           // Resistance
4 Iab=V/20;        // Current

```

```

5 disp('i) Current (Iab) is      = '+string(Iab) +' A
');
6 Iab=V/20;

```

Scilab code Exa 5.43 Current

```

1 //EXAMPLE 5-43 PG NO-333
2 Vab=38;           //Voltage
3 R1=12;
4 R2=6;
5 RTH=(R1*R2)/(R1+R2);
6 Iab=Vab/(RTH+3);
7 disp('i) Resistance (RTH) is      = '+string(RTH) +' ohm ');
8 disp('i) Current (Iab) is      = '+string(Iab) +' A
');
```

Scilab code Exa 5.44 current resistance

```

1 //EXAMPLE 5-44 PG NO-333-334
2 I1=1.6;
3 I2=0.8;
4 VTH=6*I2;           // ((R1*R2)/(R1+R2))
5 R1=3;
6 R2=9;
7 R3=6;
8 R4=3;
9 RTH=((((R1*R2)/(R1+R2))+R1)*R3)/(((R1*R2)/(R1+R2))+R1+R2);
10 IN=VTH/RTH;
11 RN=RTH;
```

```

12 disp('i) Voltage (VTH) is      = '+string (VTH) +' V
      ');
13 disp('i) Resistance (RTH) is   = '+string (RTH) +' ohm ';
14 disp('i) Current (IN) is       = '+string (IN) +' A '
      );
15 disp('i) Resistance (RN) is   = '+string (RN) +' ohm ';

```

Scilab code Exa 5.45 Current

```

1 //EXAMPLE5-45 PG NO-334-335
2 R1=10;
3 R2=5;
4 V=15;
5 Vb=9;
6 Va=(V*R2)/(R1+R2);
7 Vba=Vb-Va;
8 RTH=(R1*R2)/(R1+R2);
9 VTH=Vba;
10 Iba=VTH/(RTH+Vba);
11 disp('i) Voltage (Va) is      = '+string (Va) +' V '
      );
12 disp('i) Voltage (Vba) is     = '+string (Vba) +' V
      ');
13 disp('i) Voltage (VTH) is      = '+string (VTH) +' V
      ');
14 disp('i) Resistance (RTH) is   = '+string (RTH) +' ohms ';
15 disp('i) Current (Iba) is       = '+string (Iba) +' A
      ');

```

Scilab code Exa 5.46 Load Resistance

```

1 //EXAMPLE 5-46    PG NO-335
2 R1=1;
3 R2=1;
4 R3=3;
5 RTH=R1+((R2*R3)/(R2+R3));
6 RL=R3/(RTH+RTH);
7 P=RL^2*RTH;
8 disp('i) Resistance (RTH) is      = '+string(RTH) +' ohms ');
9 disp('i) Resistance (RL) is      = '+string(RL) +' A ');
10 disp('i) Power (P) is      = '+string(P) +' W ');

```

Scilab code Exa 5.47 Thevenins and Nortan Equivalent

```

1 //EXAMPLE 5-47    PG NO-336
2 V=5;           //VOLTAGE
3 R1=2;
4 R2=1;
5 VTH=R1+((V-R1)/3);
6 RTH=R2+((R1*R2)/(R1+R2));
7 IN=((V*0.5)/(R1+0.5))+((R1/RTH)*(R1/VTH))
8 disp('i) Voltage (VTH) is      = '+string(VTH) +' V ');
9 disp('i) Resistance (RTH) is      = '+string(RTH) +' ohm ');
10 disp('i) Current (IN) is      = '+string(IN) +' A ';

```

Scilab code Exa 5.48 Current

```

1 //EXAMPLE 5-48          PG NO-336-337
2 V=24;

```

```

3 R1=4;
4 R2=4;
5 Iab=V/(R1+R2);
6 IDb=6;
7 Iba=( IDb/(R1+R2))*R1;
8 Ibc=Iab+Iba;
9 IDB=Ibc;
10 disp('i) CURRENT (Iab) is = '+string(Iab) +' A
      ');
11 disp('i) CURRENT (Iba) is = '+string(Iba) +' A
      ');
12 disp('i) CURRENT (Ibc) is = '+string(Ibc) +' A
      ');
13 disp('i) CURRENT (IDB) is = '+string(IDB) +' A
      ');

```

Scilab code Exa 5.49 current

```

1 //EXAMPLE 5-49 PG NO-337-338
2 V1=120;
3 V2=65;
4 R1=20;
5 R2=30;
6 VTH=V1-((V1-V2)/(R1+R2))*R1;
7 RTH=(R1*R2)/(R1+R2);
8 disp('i) Voltage (VTH) is = '+string(VTH) +' V
      ');
9 disp('i) Resistance (RTH) is = '+string(RTH) +' ohms
      ');

```

Scilab code Exa 5.50 Current

```

1 //EXAMPLE - 5-50 PG NO-338

```

```

2 V1=240;
3 V2=140;
4 V=40;
5 R1=2;
6 R2=8;
7 R3=30;
8 VTH=((V1/V)*R3)-V2;
9 RTH=R1+((R3*(R1+R2))/V)+0.5;
10 I=VTH/(RTH+V2);
11 disp('i) Voltage (VTH) is = '+string(VTH) +' V
      ');
12 disp('i) Reesistance (RTH) is = '+string(RTH) +
      ' ohms ');
13 disp('i) CURRENT (I) is = '+string(I) +' A ');

```

Scilab code Exa 5.51 Resistance Power

```

1 //EXAMPLE 5-51      PG NO-338
2 I=10;           //CURRENT
3 R1=1;
4 R2=1;
5 R3=1;
6 VTH=(I*R1)/(R1+R2+R3);
7 RTH=(R1*(R1+R2))/(R1+R2+R3);
8 P=(VTH/(RTH+RTH))^2*(RTH);
9 disp('i) Voltage (VTH) is = '+string(VTH) +' V
      ');
10 disp('i) Resistance (RTH) is = '+string(RTH) +
      ' ohms ');
11 disp('i) Power (P) is = '+string(P) +' W ');

```

Scilab code Exa 5.52 Current

```

1 //EXAMPLE 5-52 PG NO-339
2 R1=2;
3 R2=4;
4 R3=2;
5 V=0.389;           //VOLTAGE
6 I1=3.89;          //CURRENT
7 TR=((R1*R2)/(R1+R2))+R2;    //TOTAL RESISTANCE
8 I=V/TR;           //CURRENT
9 TI=I1+I;          //TOTAL CURRENT
10 disp('i) Total resistance (TR) is = '+string(TR)
      +' ohms ');
11 disp('i) Current (I) is = '+string(I) +' A ');
12 disp('i) Total current (TI) is = '+string(TI) +
      ' A ');

```

Scilab code Exa 5.53 Vth Rth

```

1 //EXAMPLE 5-53 PG NO-339
2 R1=16;
3 R2=8;
4 R3=12;
5 Rd=(R1*R2)/(R1+R2+R1);
6 Rb=Rd;
7 Rc=(R1*R1)/(R1+R1+R2);
8 V=180;
9 VTH=[180/(R1+Rd+Rc)]*Rc;
10 RTH=R3+[((Rc*(R1+Rd)))/(R1+Rc+Rd)]+Rd;
11 disp('i) Resistance (Rd) is = '+string(Rd) +
      ' ohms ');
12 disp('i) Resistance (RC) is = '+string(Rc) +
      ' ohms ');
13 disp('i) Voltage (VTH) is = '+string(VTH) +' V
      ');
14 disp('i) Resistance (RTH) is = '+string(RTH) +
      ' ohms ');

```

Scilab code Exa 5.54 Current

```
1 //EXAMPLE 5-54 PG NO-340
2 V1=48; //VOLTAGE
3 V2=16; //VOLTAGE
4 R1=12;
5 R2=4;
6 R3=4;
7 I=(V1-V2)/(R1+R2+R3);
8 disp('i) Current (I) is = '+string(I)+ ' A');
```

Scilab code Exa 5.55 Current

```
1 //EXAMPLE 5-55 PG NO
-340-341
2 I1=1.2; // Current
3 I2=0.3; // Current
4 I=I1+I2;
5 disp(' Current is = '+string(I)+ 'A');
```

Scilab code Exa 5.56 Current

```
1 //EXAMPLE 5-56 PG NO-341
2 VTH=15; //THEVENINS VOLTAGE
3 R1=4;
4 R2=6;
5 I4=VTH/(R1+R2); //CURRENT
THROUGH 4 ohms Resistance
```

```
6 disp('i) CURRENT (I4) is      = '+string(I4) +' A '
);
```

Scilab code Exa 5.57 Current

```
1 //EXAMPLE 5-57          PG NO-341-342
2 R1=22;
3 R2=33;
4 R3=10;
5 R4=15;
6 V=24;
7 TR=[(R1+R2)*(R3+R4)]/(R1+R2+R3+R4);
8 I=V/TR;
9 disp('i) Total Resistance (TR) is      = '+string(TR
    ) +' Kohms ');
10 disp('ii) CURRENT (I) is      = '+string(I) +' A ')
;
```

Scilab code Exa 5.58 Resistance

```
1 //EXAMPLE 5-57          PG NO-341-342
2 R1=22;
3 R2=33;
4 R3=10;
5 R4=15;
6 V=24;
7 TR=[(R1+R2)*(R3+R4)]/(R1+R2+R3+R4);
8 I=V/TR;
9 disp('i) Total Resistance (TR) is      = '+string(TR
    ) +' Kohms ');
10 disp('ii) CURRENT (I) is      = '+string(I) +' A ')
;
```

Scilab code Exa 5.60 Current

```
1 //EXAMPLE 5-60 PG NO-343
2 V=60; //VOLTAGE
3 R1=3;
4 R2=4;
5 R3=1.5;
6 R4=2.5;
7 IAB=12;
8 IBC=6;
9 ICD=6;
10 IBD=6;
11 VAB=36;
12 VBC=9;
13 VCD=15;
14 VBD=24;
15 VkIk=VAB*IAB+VBC*IBC+VCD*ICD+VBD*IBD-V*IAB
16 disp('ii') SUBMISSION OF VkIk (VkIk) is = '+
      string(VkIk) + '');
```

Scilab code Exa 5.62 Norton equivalent

```
1 //EXAMPLE 5-62 PG NO
   -344-345
2 Z1=16+%i*0;
3 Z2=2+%i*1;
4 Z3=3-%i*1;
5 R=4;
6 I=Z1/[Z2+[(R*Z3)/(R+Z3)]];
7 disp(' Current is = '+string(I)+'A');
8 IN=[I*Z3]/(R+Z3);
9 disp(' Current is = '+string(IN)+'A');
```

```
10 ZN=[[Z3*Z2]/5]+R;
11 disp(' Impedance is = '+string(ZN)+'A');
```

Scilab code Exa 5.63 Thevenins Equivalent

```
1 //EXAMPLE 5-63 PG NO-345
2 IN=1.638-%i*0.614;
3 Z1=15+%i*0;
4 Z2=3-%i*1;
5 Z3=2+%i*1;
6 VTH=(Z1*Z2)/(Z3+Z2);
7 ZN=5.4+%i*0.21;
8 VTH1=IN*ZN
9 disp(' ii) Voltage (VTH) is = '+string(VTH) +' V ');
10 disp(' ii) Voltage (VTH) is = '+string(VTH) +' V');
```

Scilab code Exa 5.64 ZL Power

```
1 //EXAMPLE 5-64 PG NO-345-346
2 Z1=4+%i*6;
3 R1=1;
4 V=100;
5 ZTH=(Z1*R1)/(Z1+R1);
6 Pmax=[100/(ZTH+ZTH)]^2*[0.93*cos(-6.11)]
7 disp(' i) IMPEDANCE (ZTH) is = '+string(ZTH) +' ohms ');
8 disp(' ii) POWER (Pmax) is = '+string([Pmax]) +' W');
```

Scilab code Exa 5.65 Current

```
1           //EXAMPLE 5-65          PG NO-346
2 V1=5;
3 G1=1;
4 V2=5;
5 G2=(1/2);
6 V3=10;
7 G3=(1/4);
8 EV=(V1*G1+V2*G2+V3*G3)/(G1+G2+G3);           //
   EQUIVALENT VOLTAGE
9 ER=1/(G1+G2+G3);
10 I=(EV*ER)/(EV+ER);
11 disp('i) Euivalent Resistance (EV) is = '+string
      (EV) +' V ');
12 disp('ii) Equivalent Resistance (ER) is = '+
      string (ER) +' ohms ');
13 disp('ii) CURRENT (I) is = '+string (I) +' A ')
;
```

Scilab code Exa 5.66 Change in current

```
1 Z1=12.99+%i*7.5;
2 Z2=4-%i*3;
3 Z3=6+%i*8;
4 I1=Z1/Z2;
5 Z=Z3-Z2
6 I=(I1*Z)/Z3;
7 disp('ii) CURRENT (I1) is in polar form = '+
      string (I1) +' A ');
8 disp('i) IMPEDANCE (Z) is in polar form = '+
      string (Z) +' V ');
9 disp('ii) CURRENT (I) is in polar form = '+string
      (I) +' A ');
;
```

Scilab code Exa 5.67 Reciprocity Theorem

```
1 //EXAMPLE 5-67 PG NO-347-348
2 V=10; //VOLTAGE
3 R1=3;
4 R2=4.91; //RESISTANCE
5 I1=V/R1; //CURRENT
6 Isc1=1.11;
7 I2=V/R2;
8 Isc2=1.11;
9 disp('ii) CURRENT (I1) is = '+string(I1) +' A
');
10 disp('ii) CURRENT (I2) is = '+string(I2) +' A
');
```

Scilab code Exa 5.68 Equivalent Voltage

```
1 //EXAMPLE 5-68 PG NO-348
2 V1=3;
3 V2=0.75;
4 R1=1;
5 R2=0.75;
6 V=V1+V2;
7 R=R1+R2;
8 disp('ii) Voltage (V) is = '+string(V) +' V ')
;
9 disp('ii) Resistance (R) is = '+string(R) +' ohms
');
```

Scilab code Exa 5.69 Current

```
1 //EXAMPLE 5-69      PG NO-349
2 V=24;                      //VOLTAGE
3 R1=0.1;
4 R2=6;
5 R3=5;
6 I=V/[R1+(R3*R2)/(R3+R2)];
7 I1=I*(R3/(R2+R3));
8 I2=I*(R2/(R2+R3));
9 VTH=-(I1*2)-(-2*I2);
10 RTH=2.533;
11 IAB=VTH/(RTH+1);
12 disp('ii) CURRENT (I) is = '+string(I) +' A')
13 ;
13 disp('ii) CURRENT (I1) is = '+string(I1) +' A
14 ');
14 disp('ii) CURRENT (I2) is = '+string(I2) +' A
14 ');
15 disp('ii) Voltage (VTH) is = '+string(VTH) +' V
15 ');
16 disp('ii) CURRENT (IAB) is = '+string(IAB) +' A
16 ');
```

Scilab code Exa 5.70 Current

```
1 //EXAMPLE 5-70      PG NO-350
2 R1=2;
3 R2=3;
4 R3=6;
5 I4=R2*(R1/R3);           //CURRENT THROUGH 4
   OHMS RESISTANCE
6 TI=I4+I4;                //TOTAL CURRENT
7 disp('ii) CURRENT (I4) is = '+string(I4) +' A
7');
```

```
8 disp('ii') CURRENT (TI) is      = '+string (TI) +' A  
' );
```

Scilab code Exa 5.71 Current in R3

```
1 //EXAMPLE 5-71      PG NO=350-351  
2 R1=5;  
3 R2=4;  
4 R3=10;  
5 R=R1*R2/(R1+R2);  
6 I=(R*R3)/(R+R3);  
7 disp('ii') Resitance (R) is      = '+string (R) +'  
    ohms ' );  
8 disp('ii') CURRENT (I) is      = '+string (I) +' A ' )  
    ;
```

Scilab code Exa 5.73 matrix

```
1 X=[4 2 ;2 4 ];  
2 B=[20;10];  
3 X=B  
4 disp(' Current is      = '+string(X)+'A');
```

Scilab code Exa 5.74 Reciprocity Theorem

```
1 R1=15;  
2 V=20          //RESISTANCE  
3 I1=V/R1;  
4 I2=I1*(1/2);  
5 R2=15;
```

```
6 I1=V/R2;
7 I2=I1*(1/2);
8 disp('ii) CURRENT (I1) is      = '+string(I1) +' A
      ');
9 disp('ii) CURRENT (I2) is      = '+string(I2) +' A
      ');
10 disp('ii) CURRENT (I1) is     = '+string(I1) +' A
      ');
11 disp('ii) CURRENT (I2) is     = '+string(I2) +' A
      ');
```

Chapter 7

Two Port Network

Scilab code Exa 7.2 Z Parameter

```
1 //EXAMPLE 7-2
    PG NO
    -437-438
2 Z11=99+%i*99;
3 Z12=-%i*100;
4 Z21=20-%i*102.26;
5 Z22=90.06-%i*120;
6 Z1=Z11-Z12;
7 disp('i) Impedance (Z1) is in rectangular form =
    '+string(Z1) +'ohm ');
8 Z2=Z22-Z12;
9 disp('ii) Impedance (Z2) is in rectangular form =
    '+string(Z2) +'ohm ');
10 Z3=Z21-Z12;
11 disp('iii) Impedance (Z3) is in rectangular form
    = '+string(Z3) +'ohm ');
```

Scilab code Exa 7.4 Z and Y Parameter

```

1 //EXAMPLE 7-4 PG NO
    438-439
2 Z11=-0.4;
3 Z21=0.4;
4 Z12=-3.2;
5 Z22=1.2;
6 Z=[Z11 Z12;Z21 Z22];
7 X=det(Z);
8 disp(' delta is = '+string(X) +' ');
9 Y=[(Z22/X) (-Z12/X);(-Z21/X) (Z11/X)];
10 disp(' ADMITTANCE is = '+string(Y) +' ');

```

Scilab code Exa 7.5 Z and Y Parameter

```

1 //EXAMPLE 7-5 PG NO
    -439-440
2 Z11=-0.4;
3 Z21=-3.2;
4 Z12=0.4;
5 Z22=1.2;
6 Z=[Z11 Z12;Z21 Z22];
7 X=det(Z);
8 disp(' delta is = '+string(X) +' ');
9 Y=[(Z22/X) (-Z12/X);(-Z21/X) (Z11/X)];
10 disp(' ADMITTANCE is = '+string(Y) +' ');

```

Scilab code Exa 7.8 Current and Voltage

```

1 //EXAMPLE
    7-8
        PG
    NO-442
2 Y11=0.5;

```

```

3 Y21=-0.1;
4 Z1=0.1;
5 Z2=0.9;
6 Z=(Z1*Z2)/(Z1+Z2);
7 disp('i) Impedance (Z) is in rectangular form =
      '+string (Z) +'mho ');
8 I1=10*Z;
9 disp('ii) Current (I) is in rectangular form =
      '+string (I1) +'A ');
10 V11=I1/I1;
11 disp('i) VOLTAGE (V11) is in rectangular form =
      '+string (V11) +'V ');

```

Scilab code Exa 7.14 Y Parameter

```

1 //EXAMPLE 7-14 PG
NO469-470
2 Y11a=0.86;
3 Y11b=1.5;
4 Y12a=-0.57;
5 Y12b=-0.5;
6 Y21a=-0.57;
7 Y21b=-0.5;
8 Y22a=0.714;
9 Y22b=2.5;
10 Y11=Y11a+Y11b;
11 disp('i) IMPEDANCE (Y11) is = '+string (Y11) +
      mho ');
12 Y12=Y12a+Y12b;
13 disp('i) IMPEDANCE (Y12) is = '+string (Y12) +
      mho ');
14 Y21=Y21a+Y21b;
15 disp('i) IMPEDANCE (Y21) is = '+string (Y21) +
      mho ');
16 Y22=Y22a+Y22b;

```

```
17 disp('i) IMPEDANCE (Y22) is = '+string(Y22) +'  
mho');
```

Scilab code Exa 7.16 Image Parameter

```
1 //EXAMPLE 7-16 PG NO-473  
2 Zoc1=40;  
3 Zsc1=36.67;  
4 Zi1=sqrt((Zoc1*Zsc1));  
5 disp('i) IMPEDANCE (Zi1) is = '+string(Zi1) +'  
ohm');  
6 Zoc2=30;  
7 Zsc2=27.5;  
8 Zi2=sqrt((Zoc2*Zsc2));  
9 disp('ii) IMPEDANCE (Zi2) is = '+string(Zi2) +'  
ohm');  
10 TETA=1/tanh(0.9167);  
11 disp('iii) (TETA) is = '+string(TETA) +' degree  
'');
```

Scilab code Exa 7.17 Insertion Loss

```
1 //EXAMPLE 7-17 PG  
NO-474-475  
2 R=600; //RESISTANCE  
3 I1=1/1200.13;  
4 disp(' Current is = '+string(I1)+ 'A');  
5 I2=1/3793.54;  
6 disp(' Current is = '+string(I2)+ 'A');  
7 P20=23984.9;  
8 P2=2400;  
9 IL=10*log10(P20/P2);  
10 disp(' Insertion Loss is = '+string(IL)+ 'dB');
```

Scilab code Exa 7.18 Impedance

```
1 //EXAMPLE 7-18 PG NO  
-477-478  
2 Ra=7;  
3 Rb=3;  
4 Rc=3;  
5 A=(Ra+Rb)/Rb;  
6 disp(' A is = '+string(A));  
7 B=Ra+Rc+[(Ra*Rc)/Rb];  
8 disp(' B is = '+string(B));  
9 C=1/Rb;  
10 disp(' C is = '+string(C));  
11 D=(Rb+Rc)/Rb;  
12 disp(' D is = '+string(D));  
13 Z11=[(A*B)/(C*D)]^0.5;  
14 disp(' Impedance is = '+string(Z11)+'ohm');  
15 Z12=[(B*D)/(A*C)]^0.5;  
16 disp(' Impedance is = '+string(Z12)+'ohm');  
17 Q=1/cosh(2.62);  
18 Y12=-(1/17);  
19 disp(' Admittance is = '+string(Y12)+' siemens');
```

Scilab code Exa 7.20 Admittance Parameter

```
1 Zoc1=2.923;  
2 Zsc1=1.80;  
3 Zi1=sqrt((Zoc1*Zsc1));  
4 disp('i) IMPEDANCE (Zi1) is = '+string (Zi1) +' ohm');  
5 Zoc2=4.77;
```

```

6 Zsc2=2.95;
7 Zi2=sqrt((Zoc2*Zsc2));
8 disp('ii) IMPEDANCE (Zi2) is = '+string(Zi2)+'
      ohm ');
9 TETA=1/tanh(0.619);
10 disp('iii) (TETA) is = '+string(TETA)+' degree
      ');

```

Scilab code Exa 7.21 Ra Rb Rc

```

1 //EXAMPLE 7-21 PG NO-481
2 Rb=0.05;
3 C=0.09;
4 Ra=1/[C-(Rb)];
5 disp('i) RESISTANCE = '+string(Ra)+' ohm');
6 C1=0.07;
7 Rc=1/(C1-Rb);
8 disp('ii) RESISTANCE = '+string(Rc)+' ohm');

```

Scilab code Exa 7.22 Z and Y Parameter

```

1 //EXAMPLE 7-22 PG NO
-482
2 Z11=4;
3 Z21=3;
4 Z12=3;
5 Z22=5;
6 Z=[Z11 Z12;Z21 Z22];
7 X=det(Z);
8 disp(' delta is = '+string(X)+'));
9 Y=[(Z22/X) (-Z12/X);(-Z21/X) (Z11/X)];
10 disp(' ADMITTANCE is = '+string(Y)+'));

```

Scilab code Exa 7.25 matrix

```
1 //EXAMPLE 7_25 PG  
NO-484-485  
2 A1=4/3;  
3 A2=5/3;  
4 B1=11/3;  
5 B2=2;  
6 C1=1/3;  
7 C2=2;  
8 D1=5/3;  
9 D2=3;  
10 A=A1+A2;  
11 B=B1+B2;  
12 C=C1+C2;  
13 D=D1+D2;  
14 X=(A*D)-(B*C);  
15 disp(' X is = '+string(X));  
16 Z=[A1 B1;C1 D1]*[A2 B2; C2 D2];  
17 disp(' ABCD MATRIX is = '+string(Z));
```

Scilab code Exa 7.34 output Voltage

```
1 //EXAMPLE 7-34 PG NO  
-489-490  
2 h21=0.98;  
3 h22=0.3*10^-6;  
4 I1=(h22+(1/10^4))/h21;  
5 disp('i) Current (I1) is = '+string(I1)+ ' A  
' );
```

Scilab code Exa 7.37 Y parameter

```
1 //EXAMPLE 7-37 PG NO  
438-439  
2 Z11=3.25;  
3 Z21=0.75;  
4 Z12=-0.75;  
5 Z22=1.75;  
6 Z=[Z11 Z12;Z21 Z22];  
7 X=det(Z);  
8 disp(' delta is = '+string(X));  
9 Y=[(Z22/X) (-Z12/X);(-Z21/X) (Z11/X)];  
10 disp(' ADMITTANCE is = '+string(Y));
```

Scilab code Exa 7.38 Impedance

```
1 //EXAMPLE 7-38 PG NO  
-493  
2 R1=4; //RESISTANCE  
3 R2=4; //RESISTANCE  
4 R3=8/9; //RESISTANCE  
5 Z10=[R1*(R3+R2)]/[R1+R2+R3];  
6 disp(' Impedance is (Z10) = '+string(Z10)+ 'ohm');  
7 Z20=[R1*(R3+R2)]/[R1+R2+R3];  
8 disp(' Impedance is (Z20) = '+string(Z20)+ 'ohm');  
9 Z1S=[R1*R3]/[R1+R3];  
10 disp(' Impedance is (Z1S) = '+string(Z1S)+ 'ohm');  
11 Z2S=[R1*R3]/[R1+R3];  
12 disp(' Impedance is (Z2S) = '+string(Z2S)+ 'ohm');
```

Scilab code Exa 7.42 Z Parameter

```
1 //EXAMPLE7-42 PG  
NO-495-496  
2 Z11=2/3;  
3 Z22=Z11;  
4 Z12=1/3;  
5 Z21=Z12;  
6 A=Z11/Z21;  
7 disp(' A is (A) = '+string(A)+'ohm'));  
8 Z=[Z11 Z12;Z21 Z22]  
9 X=det(Z);  
10 disp(' Determinant is (X) = '+string(X));  
11 B=X/Z21;  
12 disp(' B is (B) = '+string(B)+'ohm'));  
13 C=1/Z21;  
14 disp(' C is (C) = '+string(C)+'mho'));  
15 D=Z22/Z21;  
16 disp(' D is (D) = '+string(D)+'mho'));
```

Chapter 8

filter

Scilab code Exa 8.1 Frequency Impedance Attenuation Phase Shift

```
1 //EXAMPLE 8-1 PG N0-510
2 L=0.02; //INDUCTANCE
3 C=4*10^-6; //CAPACITOR
4 Z=200;
5 Fc=1/(%pi*(L*C)^0.5);
6 Z0=(L/C)^0.5;
7 Z1=(%i*2)*%pi*Z*L;
8 Z2=1/(%i*2*%pi*Z*C);
9 Z0*(%pi)=[(4*Z1*Z2*Z2)/(Z1+4*Z2)]^0.5
10 F1=2000;
11 Z11=%i*%pi*F1*L;
12 Z22=1/(%i*%pi*F1*C);
13 Z01=[(4*Z11*Z22*Z22)/(Z1+4*Z22)]^0.5;
14 disp('ii) POWER (Pmax) is = '+string([Z1]) +' W ');
15 disp('ii) POWER (Pmax) is = '+string([Z2]) +' W ');
16 disp('ii) POWER (Pmax) is = '+string([Z0*(%pi)])
17 disp('ii) POWER (Pmax) is = '+string([Z11]) +' W ');
```

```

18 disp('ii) POWER (Pmax) is      = '+string([Z22]) + '
    W ');
19 disp('ii) POWER (Pmax) is      = '+string([Z01]) + '
    W ');

```

Scilab code Exa 8.2 L and C

```

1           //example 8-2    pg no -511
2 Ro=600;
3 Fc=940;
4 L=Ro/(%pi*Fc);
5 C=1/(%pi*Ro*Fc);
6 disp('ii) INDUCTANCE (L) is      = '+string([L]) + '
    H ')
7 disp('ii) CAPACITOR (C) is      = '+string([C]) + '
    F ')

```

Scilab code Exa 8.3 Impedance

```

1 L=0.015;                      //INDUCTANCE
2 C=0.5*10^-6;                  //CAPACITOR
3 Z=200;
4 Fc=1/(4*%pi*(L*C)^0.5);
5 Z0=(L/C)^0.5;
6 Z2=(%i*2)*%pi*Z*L;
7 Z1=1/(%i*2*%pi*Z*C);
8 F1=2000;
9 Z01=[(Z1*Z2)/(1+(Z1/(4*Z2)))]^0.5;
10 A=8.147;
11 disp('ii) Impedance (Z0) is      = '+string([Z0]) + '
    W ');
12 disp('ii) FREQUENCY is      = '+string([Fc]) + '   HZ
    ');

```

```

13 disp('ii) Impedance(Z1) is      = '+string([Z1]) +' 
      W ');
14 disp('ii) Impedance(Z2) is      = '+string([Z2]) +' 
      W ');
15 disp('ii) Impedance(Z01) is     = '+string([Z01]) +' 
      W ');
16 disp('ii) ALPHA is           = '+string([A]) +' ');

```

Scilab code Exa 8.4 L and C

```

1 //EXAMPLE -8-4    PG NO-514-515
2 Ro=3000;
3 Fc=2000;
4 L=Ro/(4*pi*Fc);
5 C=1/(4*pi*Fc*Ro);
6 disp('i) INDUCTANCE (L) is      = '+string([L]) +' 
      H ')
7 disp('ii) CAPACITOR (C) is      = '+string([C]) +' 
      F ')

```

Scilab code Exa 8.5 Band Width

```

1 //EXAMPLE 8-5    PG NO-517
2 C1=1;
3 C2=50;
4 X=1000;          //X=1/(2*pi*(L1*C1)^0.5)
5 Y=X*2*(C1/C2)^0.5; //Y=(Fc2-Fc1)
6 disp('ii) Frequency (Fc2-Fc1) is      = '+string([Y
]) +' Hz ')

```

Scilab code Exa 8.6 Circuits Parameter

```
1 //EXAMPLE 8-7 PG NO-519
2 Ro=100;
3 Fc2=5000;
4 Fc1=500;
5 L1=Ro/[2*pi*(Fc2-Fc1)];
6 disp('ii) INDUCTANCE (L1/2) is = '+string([L1
/2]) +' H ')
7 C1=(Fc2-Fc1)/(2*pi*Ro*Fc1*Fc2)
8 disp('ii) CAPACITOR (2*C1) is = '+string([2*C1
]) +' F ')
9 L2=[Ro*(Fc2-Fc1)]/(4*pi*Fc1*Fc2);
10 disp('ii) INDUCTANCE (L2) is = '+string([L2]) +
,' H ')
11 C2=1/(%pi*(Fc2-Fc1));
12 disp('ii) CAPACITOR (C2) is = '+string([C2]) +
,' F ')


---


```

Scilab code Exa 8.7 inductance

```
1 //EXAMPLE 8-7 PG NO-519
2 Fc1=1000;
3 Fc2=3000;
4 Ro=100;
5 L1=[(Ro*(Fc2-Fc1))/(2*pi*Fc2*Fc1)]
6 disp('i) INDUCTANCE (L1/2) is = '+string([L1])
 +' H ')
7 C1=1/[2*pi*(Fc2-Fc1)];
8 disp('ii) CAPACITOR (C1) is = '+string(C1) +
,' F ')
9 L2=Ro/[4*pi*(Fc2-Fc1)];
10 disp('iii) INDUCTANCE (L2) is = '+string([L2]) +
,' H ')
11 C2=(Fc2-Fc1)/(%pi*Ro*Fc1*Fc2)
```

12 **disp**('ii) CAPACITOR (C2) is = '+**string** ([C2]) +'
F')

Scilab code Exa 8.8 m

```
1 // EXAMPLE 8-8 PG NO-523
2 Ro=600;
3 Fc=2500;
4 L=Ro/(%pi*Fc);
5 C=1/(%pi*Ro*Fc);
6 disp('i) INDUCTANCE (L) is = '+string ([L]) +' H')
7 disp('ii) CAPACITOR (C) is = '+string ([C]) +' F')
8 Fo=2600;
9 m=sqrt(1-(Fc/Fo)^2)
10 disp('iii) (m) is = '+string (m) +' ')
11 L1=[(1-m*m)/4*m]*L;
12 disp('iv) INDUCTANCE (L1) is = '+string ([L1]) +' H')
13 L2=0.5*m*L;
14 disp('ii) INDUCTANCE (L2) is = '+string ([L2]) +' H')
15 C1=m*C;
16 disp('ii) CAPACITOR (C1) is = '+string (C1) +' F')
```

Scilab code Exa 8.9 m

```
1 //EXAMPLE 8-9 PG NO-525
2 Ro=600;
3 Fc=3000;
4 L=Ro/(4*%pi*Fc);
```

```

5 disp('i) INDUCTANCE (L) is      = '+string ([L]) +' H ')
6 C=1/(4*pi*Fc*Ro);
7 disp('ii) CAPACITOR (C) is      = '+string ([C]) +' F ')
8 Fo=2700;
9 m=sqrt(1-(Fo/Fc)^2);
10 disp('iii) (m) is      = '+string ([m]) +' ');
11 X=(2*C)/m;
12 disp('iv) X (X) is      = '+string ([X]) +' F ');
13 Y=L/m;
14 disp('v) Y     is      = '+string ([Y]) +' H ');
15 Z=(4*m*C)/(1-m^2); //Z
    =4mC/1-m^2
16 disp('vi) Z     (Z) is      = '+string ([Z]) +' F ');
17 Z1=(4*m*L)/(1-m^2); //Z1=4mL/1-m^2
18 disp('vii) (Z1) is      = '+string ([Z1]) +' H ')
19 X1=(2*L)/m;
20 disp('viii) X1     (X1) is      = '+string ([X1]) +' H ')
21 Y1=C/m;
22 disp('ix) Y1     is      = '+string ([Y1]) +' F ')

```

Scilab code Exa 8.10 L and C

```

1 //EXAMPLE 8-10                               PG NO- 529
2 Ro=100;
3 Fc=1000;
4 L=Ro/Fc*%pi;
5 disp('i) INDUCTANCE (L) is      = '+string ([L]) +' H ')
6 C=1/(%pi*Ro*Fc)
7 disp('ii) CAPACITOR (C) is      = '+string ([C]) +' F ')

```

Scilab code Exa 8.11 L and C

```
1 //EXAMPLE 8-11      PG NO-529-530
2 Ro=500;
3 Fc=1000;
4 L=Ro/(%pi*Fc);
5 disp('i') INDUCTANCE (L) is = '+string (L) +' H
')
6 C=1/(%pi*Ro*Fc);
7 disp('i') CAPACITOR (C) is = '+string (C) +' F
')
```

Scilab code Exa 8.12 L

```
1 //EXAMPLE 8-12      PG NO-530
2 Fc=1000;
3 C=0.05*10^-6;
4 L=1/(%pi*%pi*Fc*Fc*C)
5 disp('i') INDUCTANCE (L) is = '+string ([L]) +' H
')
```

Scilab code Exa 8.13 C

```
1 //EXAMPLE 8-13      PG NO-530
2 Fc=2000;
3 L=0.05;
4 C=1/(16*%pi*%pi*Fc*Fc*L)
5 disp('i') CAPACITOR (C) is = '+string (C) +' F
')
```

Scilab code Exa 8.14 L and C

```
1 //EXAMPLE 8-14    PG NO-530
2 Ro=600;
3 Fc=20000;
4 L=Ro/(4*%pi*Fc);
5 C=1/(4*%pi*Ro*Fc);
6 disp('i) INDUCTANCE (L) is = '+string(L) +' H
')
7 disp('ii) CAPACITOR (C) is = '+string(C) +' F
')
```

Scilab code Exa 8.15 cutt off Frequency

```
1 //EXAMPLE 8-15    PG NO-531
2 L=50*10^-3;
3 C=0.2*10^-6;
4 Ro=(L/C)^0.5;
5 Fc=1/[%pi*(L*C)^0.5];
6 disp('i) RESISTANCE (Ro) is = '+string(Ro) +' ohm ')
7 disp('ii) FREQUENCY (Fc) is = '+string(Fc) +' Hz
')
```

Scilab code Exa 8.16 Cutt off Frequency Pass band

```
1 //EXAMPLE 8-16    PG NO-531
2 C=0.2*10^-6;
3 L=50*10^-3;
```

```

4 Ro=(L/C)^0.5;
5 Fc=1/[4*%pi*(L*C)];
6 disp('Hi) RESISTANCE (Ro) is = '+string(Ro)+'
      ohm ')
7 disp('Hi) FREQUENCY (Fc) is = '+string(Fc)+'
      Hz ')

```

Scilab code Exa 8.17 Cutt off Frequency Pass band

```

1 //EXAMPLE 8-18
          PG NO
          -533-534
2 Z1=%i*413.05;           //Impedance
3 Z2=%i*334.45;           //Impedance
4 Zoc=(Z1/2)-Z2;
5 disp('i) Impedance (Zoc) is = '+string([Zoc])
      +' ohm ');
6 Zsc=(Z1/2)+[((Z1*-Z2)/2)/(-Z2+(Z1/2))];
7 disp(' ii) Impedance (Zsc) is = '+string([Zsc])
      +' ohm ');
8 Zo=(Zoc*Zsc)^0.5;
9 disp(' ii) Impedance (Zo) is = '+string([Zo]) +
      +' ohm ');

```

Scilab code Exa 8.18 m

```

1 //EXAMPLE 8-18    PG NO-533
2 Ro=600;
3 Fc=1000;
4 L1=Ro/(%pi*Fc);
5 C2=1/(%pi*Ro*Fc);
6 Fo=1050;
7 m=[1-(Fc/Fo)]^0.5;

```

```

8 X=(0.5*m*L1);
9 Y=[(1-m*m)/4*m]*L1;
10 Z=m*C2;
11 A=(m*L1)/2;
12 B=[(1-m*m)/(2*m)]*L1;
13 C=(m*C2)/2;
14 disp('i) INDUCTAR (L1) is = '+string(L1) +' H ')
15 disp('ii) CAPACITOR (C2) is = '+string(C2) +' F ')
16 disp('iii) CONSTANT (m) is = '+string(m) +' ')
17 disp('iv) (X) is = '+string(X) +' H ')
18 disp('v) (y) is = '+string(Y) +' H ')
19 disp('vi) (Z) is = '+string(Z) +' F ')
20 disp('vii) (A) is = '+string(A) +' H ')
21 disp('viii) (B) is = '+string(B) +' H ')
22 disp('x) (C) is = '+string(C) +' F ')

```

Scilab code Exa 8.19 m and T

```

1 //EXAMPLE 8-19
          PG NO
          -534-535
2 Ro=600;           // characteristics
          Impedance
3 Fc=1000;          // cutt of
          frequency
4 L=Ro/(4*pi*Fc);
5 disp('i) Inductance is = '+string([L]) +' H ')
;
6 C=1/[4*pi*Fc*Ro];
7 disp('ii) Capacitance is = '+string([C]) +' F
');
8 m=0.2;

```

```

9 X=(2*C)/m;                                //X=2C/m;
10 disp('iii') X is = '+string ([X]) +' F ');
11 Y=L/m;                                     Y=L/m;
12 disp('iv') Y is = '+string ([Y]) +' H ');
13 Z=(4*m*C)/[1-m^2];
14 disp('v') Z is = '+string ([Z]) +' F ');
15 m1=0.6;
16 X1=(2*C)/m1;                             //X=2C/m;
17 disp('iii') X is = '+string ([X1]) +' F ');
18 Y1=(2*L)/m1;                            Y1=L/m1;
19 disp('iv') Y is = '+string ([Y1]) +' H ');
20 Z1=(2*m1*C)/[1-m1^2];
21 disp('v') Z is = '+string ([Z1]) +' F ');

```

Scilab code Exa 8.20 impedance

```

1 //EXAMPLE 8-20    PG NO-535
2 Ro=450;
3 Fc=20000;
4 L=Ro/(4*pi*Fc);
5 C=1/(4*pi*Fc*Ro);
6 Z1=Ro/(2*pi*Fc);
7 disp('i') IMPEDANCE (Z1) is = '+string (Z1) +' );

```

Scilab code Exa 8.21 Inductance Capacitance

```

1 //EXAMPLE 8-21    PG NO-536-537
2 Ro=600;                                //RESISTANCE
3 Fc=10000;                               //FREQUENCY
4 F=25000;
5 L=Ro/(4*pi*Fc);
6 C=1/(4*pi*Fc*Ro);
7 Z=Ro*[1-(Fc/F)^2]^0.5;

```

```

8 Zo=Ro/[1-(Fc/F)^2]^0.5;
9 disp('i) INDUCTAR (L) is      = '+string (L) +' H ')
10 disp('ii) CAPACITOR (C) is    = '+string (C) +' F
     ')
11 disp('i) IMPEDANCE (Z) is     = '+string (Z) +' ohm
     ')
12 disp('ii) IMPEDANCE (Zo) is   = '+string (Zo) +' ohm
     ')

```

Scilab code Exa 8.22 Resonant Frequency Band Width Cutt off Frequency

```

1 //EXAMPLE 8-22          PG NO-537-538
2 L=60*10^-3;
3 C=150*10^-9;
4 Fo=1/[2*pi*(L*C)^0.5];
5 disp('ii) FREQUENCY (Fo) is      = '+string (Fo) +' Hz ')
6 R=670;
7 B.W=R/L;
8 disp('ii) BAND WIDTH (B.W) is     = '+string (B.W) +
     ' rad/sec ')
9 FL=Fo-(1777.22/2);
10 disp('ii) Lower Cut of Frequency (FL) is      = '+
      string (FL) +' Hz ')
11 Fu=Fo+(1777.22/2);
12 disp('ii) Upper Cut of Frequency (Fu) is      = '+
      string (Fu) +' Hz ')

```

Scilab code Exa 8.23 Cutt off Frequency

```

1 //EXAMPLE 8-23          PG NO-538
2 L=160*10^-3;
3 C=0.022*10^-6;

```

```

4 Fc=1/[%pi*(L*C)^0.5];
5 Zo=(L/C)^0.5;
6 disp('ii) Cut of Frequency (Fc) is = '+string (
    Fc) +' Hz ')
7 disp('ii) IMPEDANCE (Zo) is = '+string (Zo) +' ohm ')

```

Scilab code Exa 8.24 Output Voltage

```

1 //EXAMPLE 8-24 PG NO-541-542
2 Avf=1.56
3 Vo=2.262*10^-3;
4 R=15*10^3;
5 F=0.707;
6 C=0.002*10^-6;
7 Fc=1/(2*%pi*R*C);
8 disp('ii) Cut of Frequency (Fc) is = '+string (
    Fc) +' Hz ')
9 Vo1=F*Vo;
10 A=20*log(1.56);
11 disp('ii) Out Put Voltage (Vo1) is = '+string (
    Vo1) +' V ')

```

Scilab code Exa 8.25 Gain

```

1 //EXAMPLE 8-25 PG NO-542
2 Fc=4000;
3 R=10*10^3;
4 C=1/[2*%pi*Fc*R];
5 disp('i) CAPACITOR (C) is = '+string (C) +' F '
    )
6 Avf=1.586;
7 R1=15000

```

```
8 R2=[Avf -1]*R1;
9 disp('ii) RESISTANCE (R2) is = '+string (R2) +' ohm ')
```

Scilab code Exa 8.26 Mid Band Gain

```
1 //EXAMPLE-8-26 PG NO-543
2 R=15.86;
3 R1=10;
4 MA=R/R1;
5 disp('i) mid band gain = '+string (MA)+ '');
```

Scilab code Exa 8.27 R2 Mid abnd Gain Cutt of Frequency

```
1 //EXAMPLE 8-27 PG NO-545
2 R2=0.586;
3 M.G=1+0.586; //MID BAND GAIN
4 R=10^3;
5 C=0.02*10^-6;
6 Fc=1/(2*pi*R*C); //Cut OFF
    Frequency
7 G.Fc=0.707*M.G;
8 M.B.O=M.G*1.4;
9 disp('ii) Cut off Frequency (Fc) is = '+string
    (Fc) +' ')
10 disp('ii) Gain at cutt of frequency (G.Fc) is =
    '+string (G.Fc) +' ')
11 disp('ii) Mid band out Put (M.B.O) is = '+string
    (M.B.O) +' mV ')
```

Scilab code Exa 8.28 Mid abnd Output

```
1 //EXAMPLE-8-28 PG NO  
-545-546  
2 Avf=1.586;  
3 R1=10;  
4 R2=[Avf -1]*R1;  
5 Fc=5000;  
6 R=2000;  
7 C=1/[2*pi*R*Fc]  
8 disp('ii) Resistance (R2) is = '+string (R2) +'  
Kohm ')  
9 disp('ii) CAPACITOR (C) is = '+string (C) +' F  
)
```

Scilab code Exa 8.29 Gain at mid band

```
1 //EXAMPLE 8-29 PG NO-547-548  
2 R1=10000;  
3 Fc1=8000;  
4 C1=1/[2*pi*R1*Fc1];  
5 R4=15;  
6 R3=8.79;  
7 Fc2=4000;  
8 R2=20000;  
9 C2=1/[2*pi*R2*Fc2];  
10 disp('ii) CAPACITOR (C1) is = '+string (C1) +'  
F ')  
11 disp('ii) CAPACITOR (C2) is = '+string (C2) +'  
F ')
```

Scilab code Exa 8.30 Design a Filter

```

1 //EXAMPLE 8-30      PG NO-548
2 R1=10000;
3 Fc1=40000 ;
4 C1=1/[R1*Fc1*2*pi];
5 disp('ii) CAPACITOR (C1) is = '+string (C1) +' F ');
6 Fc2=8000;
7 R2=5000;
8 C2=1/[R2*Fc2*2*pi];
9 disp('ii) CAPACITOR (C2) is = '+string (C2) +' F ');

```

Scilab code Exa 8.31 Resistance

```

1 //EXAMPLE 8-31      PG NO-550
2 N=100;
3 Ro=450;
4 R1=Ro*[(N-1)/(N+1)];
5 R2=Ro*[2*N/{N^2-1}];
6 disp('ii) Resistance (R1) is = '+string (R1) +' ohm ');
7 disp('ii) Resistance (r2) is = '+string (R2) +' ohm ');

```

Scilab code Exa 8.32 Impedance

```

1 //EXAMPLE 8-32      PG NO-550
2 Zoc=200;
3 Zsc=187.5;
4 Zo=[Zoc*Zsc]^0.5;
5 R1=50;
6 R2=150;
7 R3=193.65;

```

```
8 N=[R1+R2+R3]/R1;
9 D=20*log10(N)
10 disp('ii) IMPEDANCE (Zo) is = '+string(Zo) +' ohm ');
11 disp('ii) (N) is = '+string(N) +', ');
12 disp('ii) (D) is = '+string(D) +', dB');
```

Scilab code Exa 8.33 Attenuation

```
1 //EXAMPLE 8-34 PG NO-551
2 N=2.985;
3 Ro=175;
4 R1=Ro*[(N-1)/(N+1)];
5 R2=Ro*[(2*N)/(N^2-1)];
6 disp('ii) Resistance (R1) is = '+string(R1) +' ohm ');
7 disp('ii) Resistance (R2) is = '+string(R2) +' ohm');
```

Scilab code Exa 8.34 Resistance

```
1 //EXAMPLE 8-34 PG NO-551
2 N=2.985;
3 Ro=175;
4 R1=Ro*[(N-1)/(N+1)];
5 R2=Ro*[(2*N)/(N^2-1)];
6 disp('ii) Resistance (R1) is = '+string(R1) +' ohm ');
7 disp('ii) Resistance (R2) is = '+string(R2) +' ohm');
```

Scilab code Exa 8.35 Impedance

```
1 //EXAMPLE 8-35      PG NO-552
2 R1=200;
3 R2=200;
4 R3=100;
5 Zoc=[R1*(R2+R3)/(R1+R2+R3)];
6 disp('i) IMPEDANCE (Zoc) is = '+string(Zoc) +' ohm ');
7 Zsc=(R1*R3)/(R1+R3);
8 disp('ii) IMPEDANCE (Zsc) is = '+string(Zsc) +' ohm ');
9 Zo=[Zoc*Zsc]^0.5;
10 disp('iii) IMPEDANCE (Zo) is = '+string(Zo) +' ohm ');
11 N=2.618;
12 D=20*log10(N)
13 disp('ii) (D) is = '+string(D) +' dB');
```

Scilab code Exa 8.36 Resistance

```
1 //EXAMPLE 8-36      PG NO-552-553
2 N=31.622;
3 Ro=700;
4 R1=Ro*[(N^2-1)/(2*N)];
5 R2=Ro*[(N+1)/(N-1)];
6 disp('i) RESISTANCE (R1) is = '+string(R1) +' ohm ');
7 disp('ii) RESISTANCE (R2) is = '+string(R2) +' ohms');
```

Scilab code Exa 8.37 Impedance

```

1 //EXAMPLE 8-37 PG NO-553
2 R1=657.08;
3 R2=44.316;
4 Zoc=R1+R2;
5 Zsc=R1+[(R1*R2)/(R1+R2)];
6 Zo=[Zoc*Zsc]^0.5;
7 N=[R2+R1+Zo]/R2;
8 disp('i) impedance (Zoc) is = '+string(Zoc)
      +' ohm ');
9 disp('ii) impedance (Zsc) is = '+string(Zsc) +
      ' ohm ');
10 disp('iii) impedance (Zo) is = '+string(Zo) +
      ' ohm ');
11 disp('iv) (N) is = '+string(N) + ')';

```

Scilab code Exa 8.38 Resistance

```

1 //EXAMPLE 8-38 PG NO-554
2 N=5.6234;
3 Ro=450;
4 R1=Ro*[(N^2-1)/(2*N)];
5 R2=Ro*[(N+1)/(N-1)];
6 disp('i) RESISTANCE (R1) is = '+string(R1) +
      ' ohm ');
7 disp('ii) RESISTANCE (R2) is = '+string(R2) +
      ' ohm ');

```

Scilab code Exa 8.39 N

```

1 //EXAMPLE 8-39 PG NO-554
2 R1=250;
3 R2=750;
4 Zoc=[R1*(R1+R2)]/{R1+R2+R1};

```

```

5 Zsc=[(R1*R2)/(R1+R2)];
6 Zo=[Zoc*Zsc]^0.5;
7 disp('i) impedance (Zoc) is = '+string(Zoc)
      +' ohm ');
8 disp('ii) impedance (Zsc) is = '+string(Zsc) +
      ' ohm ');
9 disp('iii) impedance (Zo) is = '+string(Zo) +
      ' ohm ');

```

Scilab code Exa 8.40 N

```

1 //EXAMPLE 8-40 PG NO-554-555
2 R1=459.089;
3 R2=22500';
4 Zoc=[R1*(R1+R2)]/{R1+R2+R1};
5 Zsc=[(R1*R2)/(R1+R2)];
6 Zo=[Zoc*Zsc]^0.5;
7 disp('i) impedance (Zoc) is = '+string(Zoc)
      +' ohm ');
8 disp('ii) impedance (Zsc) is = '+string(Zsc) +
      ' ohm ');
9 disp('iii) impedance (Zo) is = '+string(Zo) +
      ' ohm ');

```

Scilab code Exa 8.41 L

```

1 //EXAMPLE 8-41 PG NO-557
2 N=7.943;
3 Z=300; //IMPEDANCE
4 R1=[(N-1)/N]*Z;
5 R2=Z/(N-1);
6 disp('i) RESISTANCE (R1) is = '+string(R1) +
      ' ohm ');

```

```
7 disp('i i) RESISTANCE (R2) is = '+string (R2) +
      ' ohm ');
```

Scilab code Exa 8.42 D

```
1 //EXAMPLE 8-43 PG NO-557
2 Z1=450;
3 Z2=300;
4 R1=[Z1*(Z1-Z2)]^0.5;
5 R2=[(Z1*Z2*Z2)/(Z1-Z2)]^0.5;
6 disp('i i) RESISTANCE (R1) is = '+string (R1) +
      ' ohm ');
7 disp('i i) RESISTANCE (R2) is = '+string (R2) +
      ' ohm');
```

Scilab code Exa 8.43 L

```
1 //EXAMPLE 8-43 PG NO-557
2 Z1=450;
3 Z2=300;
4 R1=[Z1*(Z1-Z2)]^0.5;
5 R2=[(Z1*Z2*Z2)/(Z1-Z2)]^0.5;
6 disp('i i) RESISTANCE (R1) is = '+string (R1) +
      ' ohm ');
7 disp('i i) RESISTANCE (R2) is = '+string (R2) +
      ' ohm');
```

Scilab code Exa 8.45 design T

```
1 //EXAMPLE 8-45 PG NO-559-560
```

```

2 N=5.6234;
3 R1=500;
4 R2=R1/(N-1);
5 R3=R1*(N-1);
6 disp('i') RESISTANCE (R2) is = '+string (R2) +
    ohm ');
7 disp('ii') RESISTANCE (R3) is = '+string (R3) +
    ohm ');

```

Scilab code Exa 8.46 Design lattice attenuator

```

1 //EXAMPLE 8-46 PG NO-560-561
2 N=7.0795;
3 Z1=450;
4 R1=Z1*[(N-1)/(N+1)];
5 R2=Z1*[(N+1)/(N-1)];
6 disp('ii') RESISTANCE (R1) is = '+string (R1) +
    ohm ');
7 disp('ii') RESISTANCE (R2) is = '+string (R2) +
    ohm ');

```

Scilab code Exa 8.47 Impedance

```

1 //EXAMPLE 8-47 PG NO-561
2 R1=175;
3 R2=350;
4 Zoc=R1+R2;
5 Zsc=R1+[(R1*R2)/(R1+R2)];
6 Zo=[Zoc*Zsc]^0.5;
7 N=[R1+R2+Zo]/R2;
8 AT=20*log10(2.618);
9 disp('i') impedance (Zoc) is = '+string (Zoc)
    + ' ohm ');

```

```

10 disp('ii) impedance (Zsc) is      = '+string (Zsc) +' 
    ohm ');
11 disp('iii) impedance (Zo) is      = '+string (Zo) +' 
    ohm ');
12 disp('iv)   (N) is      = '+string (N) +' ')
13 disp('v) attenuation (AT) is      = '+string (AT) +' 
    dB ')

```

Scilab code Exa 8.48 Resistance

```

1                                //EXAMPLE  8-48    PG NO-561
2 R=300;
3 N=31.62;
4 R1=[(N-1)/N]*R;
5 R2=R/(N-1);
6 disp('i)   RESISTANCE (R1) is      = '+string (R1) +' 
    ohm ');
7 disp('ii)  RESISTANCE (R2) is      = '+string (R2) +' 
    ohm ');

```

Scilab code Exa 8.49 Design lattice attenuator

```

1                                //EXAMPLE  8-49    PG NO-562
2 Ro=500;
3 N=10;
4 RA=Ro*[(N-1)/(N+1)];
5 RB=Ro*[(N+1)/(N-1)];
6 R1=Ro*[(N-1)/(N+1)];
7 R2=Ro*[(2*N)/(N^2-1)];
8 disp('ii)   RESISTANCE (RA) is      = '+string (RA) +' 
    ohm ');
9 disp('ii)   RESISTANCE (RB) is      = '+string (RB) +' 
    ohm ');

```

```
10 disp('i i) RESISTANCE (R1) is = '+string (R1) +
     ' ohm ');
11 disp('i i) RESISTANCE (R2) is = '+string (R2) +
     ' ohm');
```

Chapter 9

Network Function

Scilab code Exa 9.24 Resonant frequency Q band width Impedance

```
1 //EXAMPLE 9-24
2 L=20;                                PG NO-608-609
3 R=2*L;                                //INDUCTANCE
4 disp('i) Resistance (R) is      = '+string ([R]) + '
      ohm ');
5 Wo=sqrt(101);
6 disp('ii) Wo (Wo) is      = '+string ([Wo]) + ' rad/
      sec ');
7 Q=(Wo*L)/R;
8 disp('iii) Q   is      = '+string ([Q]) + ' ');
9 BW=Wo/Q;
10 disp('iv) BANDWIDTH (BW) is     = '+string ([BW]) + '
      rad/sec ');
```

Scilab code Exa 9.26 Resonant frequency Q

```
1 //EXAMPLE 9-26
```

PG NO

-609-610

```
2 C=10^-6;
3 X=5*10^6;
4 L=1/(C*X);
5 disp('i) INDUCTAR (L) is = '+string([L]) +' H
');
6 R=10*L;
7 disp('ii) Resistance (R) is = '+string([R]) +' ohm
');
8 W=2.236*10^3;
9 Q=(W*L)/R;
10 disp('iii) (Q) is = '+string([Q]) +' ;
11 BW=W/Q;
12 disp('iv) Band Width (BW) is = '+string([BW]) +
' rad/sec ');
```

Scilab code Exa 9.32 Q

```
1 // Example 9-32 PG
NO 618-619
2 P1=1-%i*50;
3 P2=1+%i*150;
4 Z1=0+%i*50;
5 I=[0.2*Z1]/[P1*P2];
6 disp('i) Current (I) is = '+string([I]) +' A
');
7 L=5; //INDUCTAR
8 R=10; //RESISTANCE
9 C=2*10^-5;
10 Wo=1/sqrt(L*C);
11 disp('ii) Wo (Wo) is = '+string([Wo]) +' rad/
sec ';
12 Q=(Wo*L)/R;
13 disp('iii) Q (Q) is = '+string([Q]) +' );
```

```

14 BW=Wo/Q;
15 disp('ii) Band Width (BW) is = '+string ([BW]) +
      ' rad/sec ');

```

Scilab code Exa 9.37 Poles and Zero

```

1 //EXAMPLE 9-37 PG NO
2 C=1/8.5; //623-624
3 Capacitor
4 L=1/(17*C); //Inductar
5 disp('ii) Inductar (L) is = '+string ([L]) +' H
6 R=2*L; //Resistance
7 disp('ii) Resistance (R) is = '+string ([R]) +' ohm
8

```

Scilab code Exa 9.38 R L G C

```

1 //EXAMPLE 9-38 PG NO
2 C=1/9; //CAPACITOR =624-625
3 X=2; //R/L=X
4 Y=6-X; //G/C
5 G=4*C;
6 disp('i) G (G) = '+string (G)+ ' ohm ')
7 L=0.9;
8 R=1.8;

```

Scilab code Exa 9.46 Ia

```
1 //EXAMPLE 9-46 PG NO  
630-631  
2 ZA=5+%i*3;  
3 YA=1/ZA;  
4 disp('ii) Admittance (YA) is = '+string ([YA]) +' siemens');  
5 V=100; //VOLTAGE  
6 IA=V*YA;  
7 disp('ii) Current (IA) is = '+string ([IA]) +' A');

---


```

Scilab code Exa 9.50 Current

```
1 //EXAMPLE 9-50 PG NO-632  
2 I1=17.39-%i*4.66; //CURRENT  
3 I2=9+%i*15.68; //CURRENT  
4 I3=-%i*10.95; //CURRENT  
5 I=I1+I2+I3;  
6 disp('i)CURRENT (I) = '+string (I)+' A')

---


```

Scilab code Exa 9.56 C

```
1 //example 9-56 pg no-636  
2 Z1=8.05+%i*2.156; //IMPEDANCE  
3 XL=2.155;  
4 W=5000;  
5 L=XL/W;  
6 disp('i)INDUCTANCE (L) = '+string (L)+ ' H')  
7 Z2=4.166-%i*7.216; //IMPEDANCE  
8 Xc=7.216;
```

```
9 C=1/[W*Xc];
10 disp('ii)CAPACITOR (C) = '+string (C)+ ' F')
11 D=11.708; //DIAMETER
12 XL1=12.81;
13 L1=XL1/W;
14 disp('i) INDUCTANCE (L1) = '+string (L1)+ ' H')
```
