

Scilab Textbook Companion for  
Electronic Instrumentation And Measurements  
by D. A. Bell<sup>1</sup>

Created by  
Dhiraj N.v  
B.E (pursuing)  
Electronics Engineering  
The National Institute Of Engineering  
College Teacher  
M.S Vijaykumar  
Cross-Checked by  
TechPassion

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Electronic Instrumentation And Measurements

**Author:** D. A. Bell

**Publisher:** Oxford Publications, New Delhi

**Edition:** 2

**Year:** 2010

**ISBN:** 9780198065555

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 units Dimensions and Standards</b>	<b>5</b>
<b>2 Measurement Errors</b>	<b>7</b>
<b>3 Electromechanical Instruments</b>	<b>12</b>
<b>4 analog electronic volt ohm milliammeter</b>	<b>24</b>
<b>5 Digital instrument Basics</b>	<b>30</b>
<b>6 Digital voltmeters and frequency meters</b>	<b>36</b>
<b>7 Low High and Precise Resistance Measurements</b>	<b>38</b>
<b>8 Inductance and capacitance Measurements</b>	<b>44</b>
<b>9 Cathode Ray Oscilloscopes</b>	<b>54</b>
<b>11 signal generators</b>	<b>63</b>
<b>12 instrument calibration</b>	<b>68</b>
<b>16 Laboratory power supplies</b>	<b>72</b>

# List of Scilab Codes

Exa 1.1	Flux density . . . . .	5
Exa 1.2	temparature conversion . . . . .	5
Exa 2.1	resistance at a given temparature . . . . .	7
Exa 2.2	error in sum voltage . . . . .	8
Exa 2.3	error in difference voltage . . . . .	8
Exa 2.4	power dissipated and accuracy . . . . .	9
Exa 2.5	average voltage and deviation . . . . .	9
Exa 2.6	standard deviation and probable error . . . .	10
Exa 3.1	torque on the coil . . . . .	12
Exa 3.2	voltage and megohm sensitvity . . . . .	12
Exa 3.3	total current through the ammeter . . . . .	13
Exa 3.4	shunt resistance . . . . .	14
Exa 3.5	ammeter range . . . . .	15
Exa 3.6	multiplier resistance and applied voltage . .	15
Exa 3.7	multiplier resistances . . . . .	15
Exa 3.8	multiplier resistance . . . . .	16
Exa 3.9	pointer indication for the voltmeter . . . . .	17
Exa 3.10	sensitivity of the voltmeter . . . . .	18
Exa 3.11	value of given resistances . . . . .	18
Exa 3.12	calculate the value of $R_l$ . . . . .	19
Exa 3.13	percentage error . . . . .	20
Exa 3.14	instrument indication and resistance scale .	21
Exa 3.15	to find the resistance . . . . .	22
Exa 3.16	ohmeter indication and the resistance . . . .	23
Exa 4.1	meter current and voltage input resistance .	24
Exa 4.2	meter circuit voltage and currents . . . . .	25
Exa 4.3	meter reading and gate source voltage . . . .	26
Exa 4.4	suitable resistance values . . . . .	27

Exa 4.5	value of resistance and voltage at output . . . . .	27
Exa 4.6	resistance scale marking . . . . .	28
Exa 4.7	value of R3 and deflection . . . . .	28
Exa 5.1	high and low output voltages . . . . .	30
Exa 5.2	collector and base voltage . . . . .	31
Exa 5.3	supply current required . . . . .	32
Exa 5.4	out put frequency . . . . .	32
Exa 5.5	number of clock pulses counted . . . . .	33
Exa 5.6	number of output bits required . . . . .	34
Exa 5.7	output voltage of DAC . . . . .	34
Exa 6.1	maximum time and suitable frequency . . . . .	36
Exa 6.2	measurement accuracy . . . . .	36
Exa 6.3	determine the measured frequency . . . . .	36
Exa 6.4	percentage measurement error . . . . .	37
Exa 7.1	Caption find the resistance . . . . .	38
Exa 7.2	ammeter and ohmeter indications . . . . .	39
Exa 7.3	accuracy . . . . .	39
Exa 7.4	find the resistance . . . . .	40
Exa 7.5	accuracy upper and lower values . . . . .	41
Exa 7.6	minimum change . . . . .	41
Exa 7.7	ratio of resistances . . . . .	42
Exa 7.8	volume and surface leakage resistance . . . . .	43
Exa 8.1	components and connections . . . . .	44
Exa 8.2	range of capacitance . . . . .	45
Exa 8.3	resistance capacitance and dissipation factor	45
Exa 8.4	resistance capacitance and dissipation factor	46
Exa 8.5	parallel resistance and capacitance . . . . .	47
Exa 8.6	find the resistance . . . . .	48
Exa 8.7	inductance resistance and Q factor . . . . .	48
Exa 8.8	inductance resistance and Q factor . . . . .	49
Exa 8.9	find the inductance and resistance . . . . .	50
Exa 8.10	find the capacitance and resistance . . . . .	51
Exa 8.11	determine the q factor . . . . .	51
Exa 8.12	coil inductance and resistance . . . . .	52
Exa 9.2	peak to peak voltage and time period . . . . .	54
Exa 9.3	amplitude frequency and phase difference . . . . .	55
Exa 9.4	pulse amplitude frequency raise and fall time	56
Exa 9.5	longest pulse width . . . . .	57

Exa 9.6	shortest pulse width . . . . .	57
Exa 9.7	raise time . . . . .	58
Exa 9.8	terminal oscilloscope voltage and frequency .	59
Exa 9.9	find the capacitance . . . . .	59
Exa 9.10	find the frequency . . . . .	60
Exa 9.11	find the frequency . . . . .	60
Exa 9.12	minimum time per sensitivity . . . . .	61
Exa 9.13	raise time . . . . .	61
Exa 11.1	maximum and minimum output frequencies	63
Exa 11.2	find the resistor values . . . . .	64
Exa 11.3	find the output frequency . . . . .	65
Exa 11.4	output square wave frequency . . . . .	65
Exa 11.5	output pulse width and the capacitance . .	66
Exa 12.1	accuracy . . . . .	68
Exa 12.2	error and correction figure . . . . .	69
Exa 12.4	resistance voltage and current . . . . .	69
Exa 12.5	maximum voltage and instrument resolution	70
Exa 16.1	load effects and line regulation . . . . .	72
Exa 16.2	maximum and minimum output voltage . .	73

# Chapter 1

## units Dimensions and Standards

Scilab code Exa 1.1 Flux density

```
1 // Example 1-1 in page 8
2 // Given data
3 clc;
4 phi=500*10^-8; // one maxwell=10^-8 Wb, phi=total
      flux
5 Area=(2.54*10^-2)^2; // area in m^2, cross section is
      one inch and 1inch=2.54cm
6 // Calculation
7 B=phi/Area; //flux density(B) in tesla
8 printf("total flux density=%f mT",B*1000);
9 // Result
10 // the toatal flux density is 7.75 mT
```

---

### Scilab code Exa 1.2 temparature conversion

```
1 //example 1-2 in page 8
2 clc;
3 //given data
4 body_temp=98.6; //human body temperature is 98.6
      degree fahrenheit
5 //calculations
6 cel_temp=(body_temp-32)/1.8; //temperature in celsius
7 kel_temp=cel_temp+273.15; // temperature in kelvin
8 printf("celsius temperature=%0.0f degree celsius \n",
       cel_temp);
9 printf("kelvin temperature=%0.2f K" ,kel_temp);
10 //result
11 //the celsius temperature=37 degree celsius
12 //the kelvin temperature=310.15 K
```

---

# Chapter 2

## Measurement Errors

Scilab code Exa 2.1 resistance at a given temparature

```
1
2 //example 2-1 in page 16
3 clc;
4 //given data
5 Rmin=1.14; // minimum resistance 1.14 k-ohm
6 Rmax=1.26 // maximum resistance 1.26 k-ohm
7 R=1.2; //stated value
8 dT=75-25; //change in temperature from 25 to 75
    degree celsius
9 // calculation
10 ab=Rmax-R; //Absolute maximum error
11 abmin=Rmin-R; // Absolute minmum error
12 T=(ab/1.2)*100; // Tolerance
13 Rlarge=R+ab; //largest resistance possible at 25
    degree celsius
14 dR_per_C=(1.26/10^6)*500; // resistance change per
    degree celsius dR_per_C
15 dR=dR_per_C*dT; // total resistance increase
16 R_75=Rlarge+dR; //maximum resistance at 75 degree
    celsius
17 printf("Percentage Tolerance to be stated=+- %d
```

```
    percent \n",T);
18 printf("Maximum resistance at 75 degree celsius=% .4 f
      K-ohm" ,R_75);
19 // result
20 // Tolerance=5%
21 //maximum resistance at 75 degree celsius=1.2915
      kohm
```

---

### Scilab code Exa 2.2 error in sum voltage

```
1 //example 2-2 in page 20
2 clc;
3 //given data
4 V1=100; //stated voltage one
5 V2=80; //stated voltage two
6 e1=(1/100)*V1; //absolute error of v1
7 e2=(5/100)*V2; //absolute error of v2
8 //calculation
9 e=e1+e2; //absolute error for the sum of the voltages
10 E=V1+V2; // sum voltage
11 emax=(e/E)*100; //maximum percentage error
12 printf("E=%d V +/- %.1 f percent" ,E ,emax);
13 // result
14 //E=180 V +/- 2.8 percent
```

---

### Scilab code Exa 2.3 error in difference voltage

```
1
2 //example 2-2 in page 20
```

```
3 clc;
4 //given data
5 V1=100; //stated voltage one
6 V2=80; //stated voltage two
7 e1=(1/100)*V1; //absolute error of v1
8 e2=(5/100)*V2; //absolute error of v2
9 //calculation
10 e=e1+e2; //absolute error for the sum of the voltages
11 E=V1-V2; // difference voltage
12 emax=(e/E)*100; //maximum percentage error
13 printf("E=%d V +/- %d percent",E,emax);
14 //result
15 //E=20 V +/- 25 percent
```

---

### Scilab code Exa 2.4 power dissipated and accuracy

```
1
2 //Theory problem
```

---

### Scilab code Exa 2.5 average voltage and deviation

```
1
2 // example 2-5 in page 25
3 clc;
4 //given data
5 V=[1.001 1.002 0.999 0.998 1.000]; // 5 digital
     voltmeters reading in volts
6 //calculation
7 Vav=sum(V)/5; // average of 5 readings in volts
```

```

8 D=abs(V-Vav); //deviation of each reading from the
    average voltage
9 Dav=sum(D)/5; //average of deviation in volts
10 printf("Average measured voltage=%d V\n",Vav);
11 printf("Average deviation=%f V",Dav);
12 //result
13 //the Average measured voltage=1 V
14 //The Average deviation=0.0012 V

```

---

### Scilab code Exa 2.6 standard deviation and probable error

```

1 //To determine the standard deviation and probable
   measurement
2 //example 2-6 in page 26
3 clc;
4 //given data
5 V=[1.001 1.002 0.999 0.998 1.000]; // 5 digital
   voltmeters readings in matrix V in volts
6 //calculation
7 Vavg=sum(V)/5; // average of 5 readings in volts
8 D=abs(V-Vavg); //deviation of each reading from the
   average in volts
9 D1=D.*D;// get the square of each deviation
10 x=sum(D1); // sum of the squares of the deviation
11 sigma=sqrt(x/5); // standard deviation in volts
12 printf("standard deviation=%f V\n",sigma);
13 eP=0.6745*0.0014; //probable error in volts and sigma
   =0.0014 V
14 printf("probable error=%f mV",eP*1000);
15 //result
16 //standard deviation=0.0014 V
17 //probable error=0.94 V

```

---



# Chapter 3

## Electromechanical Instruments

Scilab code Exa 3.1 torque on the coil

```
1 // To find the Torque on the coil
2 // example3-1 in page 37
3 clc;
4 //Given data
5 N=100; //Number of turns
6 B=0.2; //Magnetic flux density of 0.2 tesla
7 D=0.01; l=0.015; //diameter and length of the coil
// in meters
8 I=.001; // current=1 mA
9 //calculation
10 T=B*l*I*N*D; // torque in N-m
11 printf("Torque=%f N-m",T);
12 //result
13 //Torque=0.000003 N-m
```

---

Scilab code Exa 3.2 voltage and megohm sensitivity

```

1 //To find the voltage sensitivity and Megohm
   sensitivity
2 // Example3–2 in page 39
3 clc;
4 //Given data
5 Is=(1*10^-6)/(10^-3); // current sensitivity in A/m
6 R=1000; // critical damping resistance of 1 kohm
7 //calculation
8 Vs=R*Is;//voltage sensitivity in mV/mm
9 Rs=Vs/Is;// megohm sensitivity i M-ohm
10 printf("Voltage sensitivity=%d mV/mm\n",Vs);
11 printf("megohm sensitivity=%d M-ohm",Rs/1000);
12 //result
13 //Voltage sensitivity=1 mV/mm
14 //Megohm sensitivity=1 Kohm

```

---

### Scilab code Exa 3.3 total current through the ammeter

```

1 //example 3–3 in page 41
2 clc;
3 //Given Data
4 A=[ 'a' 'b' 'c'];
5 m=0;
6 Rm=99; //coil resistance in ohm
7 IM=0.1e-3; //FSD(IM)=0.1 mA
8 Rs=1; //shunt resistance in ohm
9 //calculation
10 n=2; //initialisation
11 while n>0.25,
12     n=n/2;
13     Im=IM*n;
14     Vm=Im*Rm; // Meter voltage in volts
15     Is=Vm/Rs; //current throught the shunt resistance

```

```

                in ampere
16     I=Im+Is; // total current through the ammeter I=
           Im+Is in ampere
17     m=m+1;
18     printf("(%) current through the ammeter at %.2f
           FSD=%f mA\n",A(m),n,I*1000);
19 end

```

---

### Scilab code Exa 3.4 shunt resistance

```

1 // To find the Shut resistance of the ammeter
2 // example 3-4 in paage 43
3 clc;
4 //Given data
5 A=[ 'b' 'a' ];
6 Im=100*10^-6; // FSD(Im) in ampere
7 Rm=1000; // Coil resistance is 1 K-ohm
8 // calculation
9 I=10; // FSD initialisation
10 m=0;
11 while I>0.1,
12     I=I/10;
13     Vm=Im*Rm; //voltage across the meter in volts
14     Is=I-Im; //current through shunt resistance in
           ampere
15     Rs=Vm/Is; //shunt resistance in ohm
16     m=m+1;
17     printf("(%) shunt resistance value for %.1f A
           FSD is %f ohm\n",A(m),I,Rs);
18 end

```

---

### **Scilab code Exa 3.5 ammeter range**

```
1 // Theory problem
```

---

### **Scilab code Exa 3.6 multiplier resistance and applied voltage**

```
1  
2 // Theory
```

---

### **Scilab code Exa 3.7 multiplier resistances**

```
1 // To find the required multiplier resistance for  
    the two given circuits  
2 //Example3-7 in page 49  
3 clc;  
4 //Given data  
5 V=[10 50 100]; // voltage ranges in volt  
6 Im=50e-6; // FSD=50 micro-A  
7 Rm=1700; // coil resistance in ohm  
8 //calculation  
9 printf("for circuit as in figure 3-16(a)\n");  
10 for n=1:3  
11     R=(V(n)/Im)-Rm;
```

```

12     printf("R%d=%.4f M ohm\n",n,R/10^6);
13 end
14 printf("for circuit as in figure 3-16(b)\n");
15 R=zeros(1,3);
16 for n=1:3
17     R(n)=(V(n)/Im)-Rm-R(1)-R(2);
18     printf("R%d=%.4f M ohm \n",n,R(n)/10^6);
19 end
20 //result
21 // for circuit as in figure 3-16(a)
22 //R1=198300 ohm
23 //R2=998300 ohm
24 //R3=1998300 ohm
25 //for circuit as in figure 3-16(b)
26 //R1=198300 ohm
27 //R2=800000 ohm
28 //R3=1000000 ohm

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 3.8 multiplier resistance

```

1 // To find the required multiplier resistance for
   the two given circuits
2 //Example3-7 in page 49
3 clc;
4 //Given data
5 V=[10 50 100];// voltage ranges in volt
6 Im=50e-6;// FSD=50 micro-A
7 Rm=1700;// coil resistance in ohm
8 //calculation
9 printf("for circuit as in figure 3-16(a)\n");

```

```

10 for n=1:3
11     R=(V(n)/Im)-Rm;
12     printf("R%d=%f M ohm\n",n,R/10^6);
13 end
14 printf("for circuit as in figure 3-16(b)\n");
15 R=zeros(1,3);
16 for n=1:3
17     R(n)=(V(n)/Im)-Rm-R(1)-R(2);
18     printf("R%d=%f M ohm \n",n,R(n)/10^6);
19 end

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 3.9 pointer indication for the voltmeter

```

1
2 // example 3-9 in page 53
3 clc;
4 //given data
5 A=['a' 'b'];
6 Rm=1e+3; // coil resistance of 1 k ohm
7 Rs=890.7e+3; //multiplier resistance in ohm
8 Vf=0.7; //voltage drop across the diode in volt
9 //calculation
10 m=0; // reference to indicate a and b respectively
11 for n=75:-25:50 //voltages 50 and 75 volts
12     Iav=(0.637)*(((1.414*n)-2*Vf)/(Rs+Rm)); //
13         average current through pmcc instrument in
14         ampere
15     m=m+1;
16     printf("(%c),\nIav for %d V is %.2f micro-A\n",A
17     (m),n,Iav*10^6);

```

```
15     printf(" pointer indication for %d V is %.2f FSD\
n",n,10000*Iav);
16 end
```

---

### Scilab code Exa 3.10 sensitivity of the voltmeter

```
1 //To find the sensitivity
2 //example 3-10 in page 54
3 clc;
4 //given data
5 Im=157e-6; // peak current=157 micro ampere
6 Vrms=100; // FSD rms voltage in volt
7 //calculation
8 Irms=0.707*Im; //FSD rms current
9 R=Vrms/Irms; // total circuit resistance
10 S=R/Vrms; //sensitivity
11 printf("sensitivity=%d K-ohm/volt\n",S/1000);
12 //result
13 //sensitivity=9 k-ohm/Volt
```

---

### Scilab code Exa 3.11 value of given resistances

```
1 //To find resistance Rs and Rsh in the given ciruit
2 // example 3-10 in page 55
3 clc;
4 //data given
5 Iav=50e-6; //average current through PMCC instrument
    =50 micro ampere
6 Rm=1700; // coil resistance in ohm
```

```

7 Vf=0.7; // diode forward drop in volts
8 If=100e-6; // forward current = 100 micro-ampere
9 Vrms=50; // ac rms voltage in volts
10 // calculation
11 Im=Iav/(0.5*0.637); //peak current in ampere
12 Ifp=(100/20)*If; //at 20% of FSD, diode peak current(
    If) must be at least 100 micro ampere; therefore,
    at 100% of FSD,
13 Ishp=Ifp-Im; // peak current through Rsh in ampere
14Vm=Im*Rm; // peak voltage in volts
15 Rsh=Vm/Isph;
16 Rs=(1.414*Vrms-Vm-Vf)/Ifp;
17 printf("Rsh=%d ohm\n",Rsh);
18 printf("Rs=%f K-ohm\n",Rs/1000);
19 //result
20 //Rsh=778 ohm
21 //Rs=139.5 K-ohm

```

---

### Scilab code Exa 3.12 calculate the value of $R_l$

```

1 //To find the the resistance  $R_l$ 
2 // example 3-12 in page 58
3 clc;
4 // Given data
5 Iav=1e-3; // Average current through the PMCC = 1 mA
6 Ip=250e-3; // primary current= 250 mA
7 Rm=1700; // coil resistance in ohm
8 Ns=500; // number of secondary turns
9 Np=4; //number of primary turns
10 Vf=0.7; //diode forward drop in volts
11 Rs=20e+3; //  $Rs=20$  k ohm
12 //calculation
13 Im=Iav/0.637; //peak current

```

```

14 Em=(Im*(Rs+Rm))+(2*Vf); //secondary peak voltage
15 Es=Em*0.707; //secondary rms voltage
16 Irms=1.11*Iav; // RMS meter current
17 Is=Ip*(Np/Ns); //transformer rms secondary current
18 Il=Is-Irms; //current through Rl
19 Rl=Es/Il;
20 printf("Rl=%f K-ohm\n",Rl/1000);
21 //result
22 //Rl=28.2 K-ohm

```

---

### Scilab code Exa 3.13 percentage error

```

1
2 //Given Data
3 clc;
4 Im=100e-6; // FSD=100 micro amps
5 e=1; // specified accuracy
6 //calculation
7 for n=1:2
8     I=Im/n; //indicated current
9     Ie=(e/100)*Im; //error current
10    Imax=I+Ie; //actual measured maximum current
11    Imin=I-Ie; //actual measured minimum current
12    eI=(Ie/I)*100; //Percentage error in the measured
                      currrent
13    printf("At %.1f FSD\n",1/n);
14    printf("Actual measured current=%d to %d micro-A\n",
           Imin*(1e+6),Imax*(1e+6));
15    printf("error=(+/-)%d persent of measured current\n"
           ,eI);
16    printf("\n");
17 end
18 //result

```

```

19 // At 1.000000 FSD
20 //Actual measured current=99 to 101 micro-A
21 //error=(+/-)1 percent of measured current
22
23 //At 0.500000 FSD
24 //Actual measured current=49 to 51 micro-A
25 //error=(+/-)2 percent of measured current

```

---

### Scilab code Exa 3.14 instrument indication and resistance scale

```

1
2 // example 3-14 in page 61
3 clc;
4 //Given Data
5 Eb=1.5; //battery rating in volts
6 Im=100e-6; // FSD=100 micro ampere
7 R=15e+3; // R1+Rx=15 K-ohm
8 //calculation
9 printf("meter indication when Rx=0 is %d micro-A (FSD)\n", (Eb/R+0)*10^6); // here Rx=0
10 for n=0.25:0.25:0.75 //FSD's in ampere at which
    resistance Rx should be calculated
11     Rx=(Eb/(n*Im))-R; // resistance in ohm
12     printf("Rx for %.2f FSD=% .0f K-ohm \n", n, Rx
        /1000);
13 end
14 //result
15 // meter indication when Rx=0 is 100 micro A (FSD)
16 //Rx for 0.25 FSD=45 K-ohm
17 //Rx for 0.5 FSD=15 K-ohm
18 //Rx for 0.75 FSD=5 K-ohm

```

---

### Scilab code Exa 3.15 to find the resistance

```
1
2 //example3-15 in page 63
3 clc;
4 //Given data
5 R1=15e+3; // resistance R1=15 K-ohm
6 Rm=50; // coil resistance in ohm
7 R2=50; // resistance R2 in ohm
8 Im=50e-6; // FSD=50 micro-ampere
9 //calculations
10 printf("at Rx=0 & Eb=1.3 V,\n");
11 Rx=0; Eb=1.3;
12 Ib=Eb/(Rx+R1);
13 I2=Ib-Im;
14Vm=Im*Rm;
15 R21=Vm/I2; // the resistance R2 in ohm
16 printf("R2=%f ohm\n",R21);
17 for Eb=1.5:-0.2:1.3, // To find Rx
18     Vm=0.5*Im*Rm;
19     if Eb==1.3
20         R2=R21;
21     end
22     I2=Vm/R2;
23     Ib=I2+Im*0.5;
24     Rx=(Eb/Ib)-R1;
25     printf("At 0.5 FSD with Eb=%f V,\n",Eb);
26     printf("Rx=%d K-ohm \n",Rx/1000);
27 end
28 //result
29 //at Rx=0 & Eb=1.3 V
30 //R2=68.181818 ohm
```

```
31 //At 0.5 FSD with Eb=1.5V,  
32 //Rx=15 K-ohm  
33 //At 0.5 FSD with Eb=1.3 V,  
34 //Rx=15 K-ohm
```

---

### Scilab code Exa 3.16 ohmeter indication and the resistance

```
1  
2 // example 3-16 in page65  
3 clc;  
4 //Given data  
5 //the equivalent circuit is derived as shown in the  
fig3-24 from the R X 1 range ohmmeter circuit  
6 E=1.5; // battery rating in volts  
7 //calculation  
8 for Rx=0:24:24, //Rx in ohm  
9     Ib=E/(Rx+14+((10*(9990+2875+3820))  
         /(9990+2875+3820)));  
10  
11     Im=Ib*(10/(10+9990+2875+3820)); // meter current  
12     printf("meter current when Rx=%d ohm is %.2f  
         micro-A\n", Rx, Im*1e+6);  
13 end
```

---

# Chapter 4

## analog electronic volt ohm milliammeter

Scilab code Exa 4.1 meter current and voltage input resistance

```
1 // To find the meter current and the voltmeter  
    resistance  
2 //example 4-1 in page 88  
3 clc;  
4  
5 //given data  
6 Vcc=20; //Vcc in volts  
7 R=9.3e+3; // R=Rs+Rm=9.3 K-ohm  
8 Im=1e-3' // Im=1 mA  
9 hfe=100;  
10 E=10; // E in volts  
11 Vb=0.7; // voltage drop across base in volts  
12  
13 // calculation  
14 Ve=E-Vb;// emitter voltage in volts  
15 printf("meter current=%d mA\n",Ve*1000/R);  
16 Ib=Im/hfe;// base current  
17 printf("input resistance with transistor = %d M-ohm\n",E/(Ib*1000000));
```

```

18 printf("input resistance with out transistor = %.1f
K-ohm\n",R/1000);
19 //result
20 //meter current = 1 mA
21 //input resistance with transistor = 1 M-ohm
22 //input resistance with out transistor = 9300 ohm

```

---

### Scilab code Exa 4.2 meter circuit voltage and currents

```

1 // To find currents I2 and I3 and calculate the
   meter circuit voltage in the given circuit
2 //example 4-2 in page 89
3 clc;
4 //Given data
5 R2=3.9e+3; //resistance R2=R3=3.9 K-ohm
6 R3=R2;
7 Vcc=12; //Vcc in volt
8 Vee=-12; // Vee in volt
9 Vbe=0.7; // voltage drop across the base-emitter
10 Vp=0; // base voltage of transistor 2
11 //calculation
12 VR2=0-Vbe-Vee;
13 VR3=VR2;
14 I2=VR2/R2;
15 I3=I2;
16 printf("I2=I3=% .1f mA\n",I2*1000);
17 for E=1:-0.5:0.5// voltage applied to the base of
   transistor 1 in volts
18     Ve1=E-Vbe; // emitter voltage of transistor 1
19     Ve2=Vp-Vbe; // emitter voltage of transistor 2
20     V=Ve1-Ve2; // voltage difference b/w the two
       emitters
21     printf("when E=% .1f V,\n",E);

```

```

22     printf(" circuit voltage (V)=%f V\n",v);
23 end
24 //result
25 //I2=I3=2.9 mA
26 //when E=1.0 V,
27 //circuit voltage (V)=1.0 V
28 //when E=0.5 V,
29 //circuit voltage (V)=0.5 V

```

---

### Scilab code Exa 4.3 meter reading and gate source voltage

```

1
2 // example 4-3 in page 93
3 clc;
4 //Given data
5 Range=10; //range in volts
6 Ra=800e+3; Rb=100e+3; Rc=60e+3; Rd=40e+3; // given
    resistance values in ohm
7 E=7.5; //battery voltage in volts
8 Vgs=-5; // gate source voltage in volts
9 Vp=5; // base voltage of transistor 2 in volts
10 R=1e+3; // R=Rs+Rm=1 K-ohm
11 Im=1e-3; //FSD=1 mA
12 Vbe=0.7 //base emitter voltage in volt
13 //calculation
14 Eg=E*((Rc+Rd)/(Ra+Rb+Rc+Rd)); //gate voltage
15 Vs=Eg-Vgs; //souce voltage
16 Ve1=Vs-Vbe; // emitter voltage of transistor 1
17 Ve2=Vp-Vbe; //emitter voltage of transistor 2
18 V=Ve1-Ve2; // voltage difference b/w the two emitters
19 I=V/R;
20 P=I/Im; //P% of full scale
21 printf("THE METER READING=%f V\n",P*Range);

```

```
22 // result  
23 //THE METER READING=7.500000 V
```

---

#### Scilab code Exa 4.4 suitable resistance values

```
1 // to determine the resistance values for the  
    circuit in the figure4-7  
2 //example 4-4 in page 97  
3 clc;  
4 //Given data  
5 E=20e-3; //maximum input voltage = 20 mV  
6 Ib=0.2e-6; //op-amp input current 0.2 micro amps  
7 Im=100e-6; //FSD=100 micro amps  
8 Rm=10e+3; // coil resistance in 10 k-ohm  
9 //As I4>>Ib select  
10 I4=1000*Ib; // current in ampere  
11 // at full scale Im=100 micro-A  
12 Vout=Im*Rm;  
13 printf("R3=%d ohm\n",E/I4);  
14 printf("R4=%f K-ohm\n", (Vout-E)/(1000*I4));  
15 //result  
16 //R3=100 ohm  
17 //R4=4900 ohm
```

---

#### Scilab code Exa 4.5 value of resistance and voltage at output

```
1  
2 //example 4-5 in page 98  
3 clc;
```

```

4 // data given
5 E=1; // E=1 V
6 Im=1e-3; //FSD=1 mA
7 Rm=100; // Rm in ohm
8 //calculation
9 R3=E/Im;
10 printf("R3=%d K-ohm\n",R3/1000);
11 printf("Vout=%f V\n",Im*(R3+Rm));
12 //result
13 //R3=1 K-ohm
14 //Vout=1.1 V

```

---

### Scilab code Exa 4.6 resistance scale marking

```

1
2 // example 4-6 in page 100
3 clc;
4 // data give
5 Eb=1.5; // Full scale voltage in volts
6 R1=1e+3;//R1=1 K-ohm
7 //calculation
8 for n=1:2
9     E=Eb*(n/3); // 1/3rd and 2/3rd value of full
                  scale
10    Rx=R1/((Eb/E)-1);
11    printf(" at %d/3 FSD, Rx=%d ohm\n",n,Rx)
12 end

```

---

### Scilab code Exa 4.7 value of R3 and deflection

```

1
2 // example 4-7 in page 107
3 clc;
4 // Given data
5 Iav=1e-3; //for , FSD the average meter current is 1
    mA
6 Rm=1.2e+3; // coil resistance 1.2 K-ohm
7 E=100e-3; // ac input rms voltage=100 mV
8 //calculations
9 Ip=(2/0.637)*Iav; // peak current for half wave
    rectifier
10 Ep=E/0.707; // input peak voltage
11 R3=Ep/Ip;
12 printf("R3=%d ohm\n\n",R3);
13 printf("When E=50 mV,\n");
14 Ep=(50e-3)/0.707;
15 Ip=Ep/R3;
16 printf("meter deflection=Iav=%f mA\n", (0.637/2)*Ip
    *1000); //half scale

```

---

# Chapter 5

## Digital instrument Basics

Scilab code Exa 5.1 high and low output voltages

```
1 // to find the high and low output voltage values
2 // example 5-1 in page 120
3 clc;
4 //Given data
5 Vcc=5; // DC source in volts
6 Io=1e-3; // output current= 1mA
7 R1=1e+3; //R1=1K-ohm
8 Vi=0; //lowest input voltage
9 Vd=0.7; // silicon-diode drop in volts
10 //calculation
11 printf("High output voltage=%d V\n",Vcc-(Io*R1));
12 printf("low output voltage=%f V\n",Vi+Vd);
13 //result
14 //High output voltage=4 V
15 //low output voltage=0.7 V
```

---

### Scilab code Exa 5.2 collector and base voltage

```
1 // To find the collector and base voltages
2 // example 5-2 in page 121
3 clc;
4 // Given data
5 R1=15e+3; R2=27e+3; Rc1=2.7e+3; R11=R1; R21=R2; // resistance values in Ohm where R11=R1' and R21=R2'
6 Vc2=0.2;// collector voltage of on transistor in volt
7 Vce=Vc2;// collector-emitter saturation voltage in volt
8 Vbb=-5;//dc power supply in volt
9 Vcc=5;//dc power supply in volt
10 //calculations
11 Vr1r2=Vc2-Vbb;//voltage across Ri and R2 in volt
12 Vr1=(R1/(R1+R2))*Vr1r2;// voltage across R1 resistor in volt
13 Vb1=Vc2-Vr1;// base voltage
14 printf("Vb1=%f V\n",Vb1);
15 //with Q1 off
16 Vrc1=(Rc1/(Rc1+R11+R21))*(Vcc-Vbb);
17 Vc1=Vcc-Vrc1;// collector voltage in volt
18 printf("Vc1=%f V",Vc1);
19 //result
20 //Vb1=-1.657143 V
21 //Vc1=4.395973 V
```

---

### Scilab code Exa 5.3 supply current required

```
1 //example 5-3 in page 124
2 clc;
3 // Given data
4 // 3(1/2) digit display
5 If1=20e-3; //forward current per segment of led=20 mA
6 If2=300e-6; //forward current per segment of lcd
7 //calculations
8 for n=1:2
9     if n==1
10        I=If1;
11    else I=If2;
12    end
13    It=3*7*I+2*I; // each digit has 7 segments and
14    // there are three digits with a half digit that
15    // has 2 segments
16    printf("case %d,\n Total current=%.0f mA\n",n,It
17    *1000);
18 end
19 // result
20 // case 1,
21 //Total current=0.460000 A
22 //case 2,
23 //Total current=0.006900 A
```

---

### Scilab code Exa 5.4 out put frequency

```

1 // to find the out put frequency in fig 5-10
2 // example 5-4 in page 130
3 clc;
4 //Given data
5 To=1e-6;// oscillator time period=1 micro-second
6 N=16;// modulus number of the counter = 16
7 n=3;// number of counters
8 //calculations
9 T=To*(N^n); //out put time period
10 printf("output frequency=%d hertz",1/T); //output
    frequency
11 //result
12 //output frequency=244 hertz

```

---

### Scilab code Exa 5.5 number of clock pulses counted

```

1 //To find the number of pulses counted
2 //example5-5 in page 131
3 clc;
4 //data given
5 Vr=1.25;//peak voltage of ramp in volts
6 tr=125e-3;//time period of the ramp=1.25 ms
7 T=1/(1e+6);// frequency =1 Mhz and time period of
    the clock pulses is 1/f
8 for Vi=0.75:(0.9-0.75):0.9,// analog input voltages
    for which clock pulses has to b found
9     t1=(tr/Vr)*Vi;//time period of the comparator
        high out put
10    N=t1/T;// pulses counted
11    printf("number of pulses counted for Vi=%.2f V
        are %d\n",Vi,N/100);
12 end
13 // result

```

```
14 //number of pulses counted for Vi=0.750000 V are 750
15 //number of pulses counted for Vi=0.900000 V are 900
```

---

### Scilab code Exa 5.6 number of output bits required

```
1 // example 5-6 in page 133
2 clc;
3 //Given data
4 //error should be less thsn 1%
5 // for less than 1% error count>=100
6 n=6;
7 N=0;
8 while(N<100)
9 N=(2^n)-1; //count value
10 if(N<100)
11 n=n+1; //increment n and check weather N has exceeded
100
12 end
13 end
14 printf("for less 1percent error ,use n=%d\n",n);
15 //end
16 // for less 1percent error ,use n=7
```

---

### Scilab code Exa 5.7 output voltage of DAC

```
1
2 // example 5-7 in page 135
3 clc;
4 //Given data
```

```
5 D=8; C=0; B=2; A=0; //corresponding analog input  
    voltages for the digital input 1-0-1-0  
6 Vi=10; //input voltage in volts  
7 //calculation  
8 Vo=(D+C+B+A)*Vi/16; // output voltage  
9 printf("out put voltage=%f V",Vo);  
10 //result  
11 //out put voltage=6.25 V
```

---

# Chapter 6

## Digital voltmeters and frequency meters

Scilab code Exa 6.1 maximum time and suitable frequency

1 // Theory Problem

---

Scilab code Exa 6.2 measurement accuracy

1  
2 // Theory Problem

---

Scilab code Exa 6.3 determine the measured frequency

1 // Theory Problem

---

**Scilab code Exa 6.4 percentage measurement error**

1 //THEORY PROBLEM

---

# Chapter 7

## Low High and Precise Resistance Measurements

Scilab code Exa 7.1 Caption find the resistance

```
1 // To find the value of measured Resistance R
2 // example 7-1 in page 165
3 clc;
4 // Given data
5 I=0.5; //measured current in amps
6 V=500; // voltmeter indication in volts
7 Ra=10; //ammeter resistance in ohms
8 //calculation
9 R=(V/I)-Ra; // measured resistance
10 printf("The value of R=%d ohm",R);
11 //result
12 // The value of R=990 ohm
```

---

### Scilab code Exa 7.2 ammeter and ohmeter indications

```
1 // To find the ammeter and ohmeter indication for
   the circuit 7-1(a)
2 // example 7-2 in page 166
3 clc;
4 //Data given
5 V=1000; S=10e+3; // voltmeter range and sensitivity
   in volt and ohm/volt
6 R=990; // the resistance measured
7 E=500; // supply voltage in volts
8 Ra=10; // ammeter resistance in ohm
9 //calculation
10 Rv=V*S; // voltmeter resistance
11 R1=(R*Rv)/(R+Rv); // as voltmeter is connected in
   parallel with the measured resistance , the
   equivalent resistance is the parallel combination
   of both resistances
12 Ev=(E*R1)/(R1+Ra); // voltmeter reading using voltage
   divider formula
13 I=Ev/R1; // ammeter reading
14 printf("voltmeter reading=% .0f V\nAmmeter reading=%
   .1f A\n",Ev,I);
15 //result
16 //voltmeter reading=495 V
17 //Ammeter reading=0.5 A
```

---

### Scilab code Exa 7.3 accuracy

```
1 // To determine which of the circuits 7-1(a) or 7-2(
   b) has greater accuracy
2 // example 7-3 in page 166
3 clc;
```

```

4 //Data given
5 V1=495; I1=0.5; // voltmeter and ammeter reading in
   volt and ampere respectively of circuit 7-1(a)
6 V2=500; I2=0.5; // voltmeter and ammeter reading in
   volt and ampere respectively of circuit 7-1(b)
7 //calculation
8 printf("R from circuit 7-1(a)=%d ohm\nR from circuit
   7-1(b)=%d ohm\n",V1/I1,V2/I2);
9 printf("thus circuit 7-1(a) gives the more accurate
   result");
10 //result
11 //R from circuit 7-1(a)=990 ohm
12 //R from circuit 7-1(b)=1000 ohm
13 //thus circuit 7-1(a) gives the more accurate result

```

---

#### Scilab code Exa 7.4 find the resistance

```

1 // to calculate the value of Resistance R
2 // example 7-4 in page 169
3 clc;
4 // data given
5 P=3.5e+3; Q=7e+3; S=5.51e+3; // resistance values of
   the wheatstone bridge arms in ohm
6 //calculation
7 R=S*P/Q;// equation for balancng condition
8 printf("R=%f K-ohm\n",R/1000);
9 S=[1e+3 8e+3];// adjusting s from 1 t0 8 K-ohm
10 for n=1:2
11     R=S(n)*P/Q;
12     printf("when S=%d K-ohm,\n",S(n)/1000);
13     printf("R=%d ohm\n",R);
14 end
15 // result

```

```
16 //Measurement range is from 500 ohm to 4000 ohm
```

---

### Scilab code Exa 7.5 accuracy upper and lower values

```
1 // To calculate the accuracy of the measured value  
    of resistance and to find the upper and lower  
    values  
2 // example 7-5 in page 169  
3 clc;  
4 //Data given  
5 R=2.755e+3; //measured value of R in ohm  
6 E=[0.05 0.05 0.1] // percentage errors of the  
    resistances P Q and S respectivly  
7 //calculation  
8 Re=sum(E); // percentage error in R  
9 Rmax=R+((Re/100)*R); //upper limit of resistance R in  
    ohm  
10 Rmin=R-((Re/100)*R); // lower limit of resistance R  
    in ohm  
11 printf("the upper and lower limits of R are %.4f K-  
    ohm and %.4f K-ohm respectively",Rmax/1000,Rmin  
    /1000);  
12 //result  
13 // the upper and lower limits of R are 2.760510 K-  
    ohm and 2.749490 K-ohm respectively
```

---

### Scilab code Exa 7.6 minimum change

```

1 // to calculate the minimum change detectable by the
   bridge
2 // example 7-6 in page 172
3 clc;
4 //Given data
5 P=3.5e+3; Q=7e+3; S=4e+3; R=2e+3; // bridge arm
   resistances in ohm
6 Eb=10; // supply voltage in volt
7 Ig=1e-6; //galvano meter reading in ampere
8 rg=2.5e+3; //galvanometer resistance=2.5 K-ohm
9 //calculations
10 r=((P*R)/(P+R))+((Q*S)/(Q+S)); // internal resistance
    of the bridge in ohm
11 dVR=Ig*(r+rg); // open-circuit galvano meter voltage
    i,e VR-VS in volt
12 VR=Eb*R/(R+P); // voltage across resistance R in volt
13 VP=Eb-(VR+dVR); //voltage across resistance P in volt
14 IR=VP/P; // current through P which is equal to
    current through R in ampere
15 dR=((VR+dVR)/IR)-R; //Change in R value that the
    device can detect in ohm
16 printf("the minimum change in R which is detected by
    the bridge is %f ohm\n",dR);
17 //result
18 // the minimum change in R which is detected by the
    bridge is 5.466141 ohm

```

---

### Scilab code Exa 7.7 ratio of resistances

```

1 // to determinr the required ratio of R/P
2 // example 7-7 in page 176
3 clc;
4 // Given data

```

```
5 S=0.1; Q=0.15; // resistances in ohm
6 //calculation
7 r=S/Q; // here R/P=S/Q
8 printf("the required ratio is %d/%d", (S*100), (Q*100)
      );
9 //result
10 // the required ratio is 10/15
```

---

### Scilab code Exa 7.8 volume and surface leakage resistance

```
1 // to find the volume resistance and the surface
   leakage resistance
2 // example 7-8 in page 180
3 clc;
4 //Data given
5 Is=5e-6;// surface current in ampere
6 Iv=1.5e-6;// volume current in ampere
7 E=10000;// supply voltage in volt
8 // calculation
9 printf("volume resistance=%0.1e ohm\n",E/Iv);
10 printf("surface leakage resistance=%0.1e ohm",E/(Is-
    Iv));
11 //result
12 //volume resistance=6.7e+009 ohm
13 //surface leakage resistance=2.9e+009 ohm
```

---

# Chapter 8

## Inductance and capacitance Measurements

Scilab code Exa 8.1 components and connections

```
1 // To find the components and connections
2 // example 8-1 in page 194
3 clc;
4 // Given data
5 C=0.005e-6; Rs=8e+3; f=1e+3; // the circuits
// capacitance , resistance and measurement frequency
// in farad , ohm and hertz respectively
6 ohm_meter_reading=134e+3;// in ohm
7 //calculation
8 Xs=1/(2*pi*f*C); //series inductive reactance in ohm
9 Rp=(Rs*Rs+Xs*Xs)/Rs; // parallel resistance in ohm
10 Xp=(Rs*Rs+Xs*Xs)/Xs; // parallel inductive reactance
// in ohm
11 Cp=1/(2*pi*f*Xp); // parallel capacitance in farad
12 printf("Rp=%d K-ohm\nXp=%f K-ohm\nCp=%f micro-F"
, Rp/1000, Xp/1000, Cp*1000000);
13 //result
```

```
14 // since the measured terminal resistance is 134 k-
    ohm, the circuit must consist of a 0.005 micro-
    farad capacitor connected in parallel with a 134
    kilo-ohm resistor. For a series connected circuit.
        the terminal resistance would be much higher
        than 134 K-ohm
```

---

### Scilab code Exa 8.2 range of capacitance

```
1 // to find the range of Cx in fig 8-5
2 // example 8-2 in page 199
3 clc;
4 // data given
5 C1=0.1e-6; //standard capacitance in micro farad
6 r=[100/1 1/100]; // range of the ratio R3/R4
7 Cx=C1*r; // range of Cx
8 printf("The range of Cx is from %.3f micro-F to %d
         micro-F",Cx(2)*10^6,Cx(1)*10^6);
9 //result
10 //The range of Cx is from 0.001 micro-F to 10 micro-
    F
```

---

### Scilab code Exa 8.3 resistance capacitance and dissipation factor

```
1 // to find the capacitance , resistance and the
    dissipation factor
2 // example 8-3 in page 202
3 clc;
4 //Given data
```

```

5 f=100; // frequency in Hz
6 C1=0.1e-6; // satndard capacitance in farad
7 R=[125 0 10e+3 14.7e+3]; // resistances R1,R3 and R4
    values in ohms as R2 is not used it is take as 0
    for convinence
8 //calculation
9 Cs=C1*(R(3)/R(4)); //series capacitance
10 Rs=R(1)*R(4)/R(3); // series resistance
11 D=2*pi*f*Cs*Rs; // dissipation factor
12 printf("Cs=% .3 f micro-F\nRs=% .1 f ohm\nD=% .3 f" ,Cs
        *10^6 ,Rs ,D);
13 //result
14 //Cs=0.068 micro-F
15 //Rs=183.8 ohm
16 //D=0.008

```

---

### Scilab code Exa 8.4 resistance capacitance and dissipation factor

```

1 // To find the resistance ,capacitance and
    dissipation factors
2 // example 8-4 in page 204
3 clc;
4 //Given Data
5 f=100; // frequency in Hz
6 C1=0.1e-6; // satndard capacitance in farad
7 R=[375e+3 0 10e+3 14.7e+3]; // resistances R1,R3 and
    R4 values in ohms as R2 is not used it is take as
    0 for convinence
8 //calculation
9 Cp=C1*(R(3)/R(4)); //parallel capacitance in farad
10 Rp=R(1)*R(4)/R(3); // parallel resistance in ohm
11 D=1/(2*pi*f*Cp*Rp); // dissipation factor
12 printf("Cp=% .3 f micro-F\nRp=% .1 f K-ohm\nD=% .1 e\n" ,

```

```

        Cp*10^6 , Rp/1000 , D) ;
13 // result
14 // Cp=0.068027 micro-F
15 //Rp=551.250000 K-ohm
16 //D=0.042441

```

---

### Scilab code Exa 8.5 parallel resistance and capacitance

```

1 // to calculate the equivalent parallel capacitance
   and resistance
2 // example 8-5 in page 204
3 clc;
4 //Given dATA
5 R3=10e+3; // resistance R3 in ohm
6 f=100; //frequency in hertz
7 Cs=0.068e-6; Rs=183.8; // series capacitance in
   farad and resistance in ohm
8 //Calculation
9 Xs=1/(2*pi*f*Cs); // series capacitive reactance in
   ohm
10 Rp=(Rs*Rs+Xs*Xs)/Rs; //equivalent parallel resistance
   in ohm
11 Xp=(Rs*Rs+Xs*Xs)/Xs; //equivalent parallel capacitive
   reactance in ohm
12 Cp=1/(2*pi*f*Xp); // equivalent capacitance in farad
13 R4=Cs*R3/Cp; // parallel resistance in ohm
14 R1=R3*Rp/R4; // parallel resistance in ohm
15 printf("Rp=%f M-ohm\nCp=%f Micro-F\nR1=%f M-
   ohm\nR4=%f K-ohm",Rp/10^6,Cp*10^6,R1/10^6,R4
   /1000);
16 // result
17 //Rp=2.98 M-ohm
18 //Cp=0.068 Micro-F

```

```
19 //R1=2.03 M-ohm  
20 //R4=14.7 K-ohm
```

---

### Scilab code Exa 8.6 find the resistance

```
1 // To find the resistance R1 and R3 in fig 8-8  
2 // example 8-6 in page 207  
3 clc;  
4 // Given data  
5 R4=5e+3; L1=100e-3; Ls=500e-3; Rs=270; R3=1e+3; //  
    resistances in ohm and inductances in henry  
6 //calculation  
7 printf("R3=%d K-ohm\n",R4*L1/(Ls*1000));  
8 printf("R1=%d ohm",Rs*R3/R4);  
9 //result  
10 //R3=1 K-ohm  
11 //R1=54 ohm
```

---

### Scilab code Exa 8.7 inductance resistance and Q factor

```
1 // to find the resistance inductance and the Q  
    factor of the inductor  
2 // example 8-7 in page 209  
3 clc;  
4 // given data  
5 // it is a maxwell's induction bridge  
6 C3=0.1e-6; R1=1.26e+3; R4=500; R3=470; //  
    capacitance and resistor values in farad and ohm  
7 f=100; // frequency =100 Hz
```

```

8 // calculation
9 printf("Ls=%d mH\n", C3*R1*R4*1000); // here Ls=C3*R1*
   R4
10 printf("Rs=%.2f K-ohm\n", R1*R4/(R3*1000)); // here Rs=
    R1*R4/R3
11 printf("Q=%.2f", (2*pi*f*C3*R1*R4)/(R1*R4/R3)); // Q=
    w*Ls/Rs
12 // result
13 //Ls=63 mH
14 //Rs=1.34 K-ohm
15 //Q=0.03

```

---

### Scilab code Exa 8.8 induactance resistance and Q factor

```

1 // to find the resistance inductance and the Q factor
   of the inductor
2 // example 8-8 in page 210
3 clc;
4 // given data
5 // it is a maxwell's induction bridge
6 C3=0.1e-6; R1=1.26e+3; R4=500; R3=75; // capacitance
   and resistor values in farad and ohm
7 f=100; // frequency =100 Hz
8 //calculation
9 printf("Lp=%d mH\n", C3*R1*R4*1000); // here Lp=C3*R1*
   R4
10 printf("Rp=%.1f K-ohm\n", R1*R4/(R3*1000)); // here Rp=
    R1*R4/R3
11 printf("Q=%d", (R1*R4/R3)/(2*pi*f*C3*R1*R4)); // Q=Rs
    /(w*Lp)
12 // result
13 //Lp=63 mH
14 //Rp=8.4 K-ohm

```

15 //Q=212

---

### Scilab code Exa 8.9 find the inductance and resistance

```
1 // to find series equivalent inductance and
   resistance and find R1 and R3 for maxwell circuit
2 // example 8-9 in page 211
3 clc;
4 printf("part a,\n");
5 //Data Given
6 Lp=63e-3; Rp=8.4e+3; f=100; // the parallel
   inductance in henry and resistace in ohm with 100
   hertz frequency
7 //calculation
8 Xp=2*pi*f*Lp; //parallel inductive reactance in ohm
9 Rs=(Rp*Xp*Xp)/(Xp*Xp+Rp*Rp); // series resistance in
   ohm
10 printf("Rs=%f ohm\n",Rs); // equivalent series
    resistance in ohm
11 Xs=(Rp*Rp*Xp)/(Xp*Xp+Rp*Rp); // series inductive
    reactance in ohm
12 Ls=Xs/(2*pi*f); // equivalent series inductance in
   henry
13 printf("Ls=%f mH\n",Ls*1000);
14 printf("part b,\n");
15 //Data given
16 C3=0.1e-6; R4=500; // capacitance in farad and
   resistance in ohm of maxwell bridge
17 //calculation
18 R1=Ls/(C3*R4); //resistance in ohm
19 printf("R3=%f M-ohm", (R1*R4)/(Rs*10^6));
20 printf("\nR1=%f K-ohm", R1/1000);
21 //result
```

```
22 // part a,  
23 //Rs=0.187 ohm  
24 //Ls=63 mH  
25 // part b,  
26 //R3=3.38 M-ohm  
27 //R1=1.26 K-ohm
```

---

**Scilab code Exa 8.10 find the capacitance and resistance**

```
1 // to find Cx and Rx of figure 8-7 for new balance  
2 // example 8-10 in page 214  
3 clc;  
4 //Data given  
5 C1=0.1e-6; R3=10e+3; R4=14.66e+3; R1=369.3e+3; //  
    bridge capacitance and resistance in farad and  
    ohm respectively  
6 Rp=553.1e+3; Cp=0.068e-6;// parallel resistance in  
    ohm and capacitance in farad  
7 //calculations  
8 Cx=(C1*R3/R4)-Cp; // here Cx+Cp = C1*R3/R4 in farad  
9 printf("Cx=%d pF\n",Cx*10^12);  
10 R=R1*R4/R3; // let R=Rx parallel with Rp in ohm  
11 Rx=1/((1/R)-(1/Rp)); // Rx in ohm  
12 printf("Rx=%f M-ohm\n",Rx/10^6);  
13 //result  
14 //Cx=212 pF  
15 //Rx=26 M-ohm
```

---

**Scilab code Exa 8.11 determine the q factor**

```

1 // to determine the Q factor
2 // example 8-11 in page 221
3 clc;
4 //Data given
5 E=100D-3; R=[5 10]; XC=100; XL=XC; // supply
    resistance , capacitive reactance and inductive
    reactance respectively for the fig 8-17, all in
    ohm
6 //calculation
7 for n=1:2
8     I=E/R(n); // current in ampere
9     V=I*XC; // VL=VC=V and XC=XL, voltage in volts
10    Q=V/E; // Q factor
11    printf(" for %d st coil ,\n",n);
12    printf(" voltmeter indication=%d V\n",V);
13    printf("Q=%d\n",Q);
14 end
15 //result
16 //for 1 st coil ,
17 //voltmeter indication=2 V
18 //Q=20
19 //for 2 st coil ,
20 //voltmeter indication=1 V
21 //Q=10

```

---

### Scilab code Exa 8.12 coil inductane and resistance

```

1 // To Determine the coil inductance and the
    resistance
2 // example 8-12 in page 225
3 clc;
4 // Data given
5 f=1.25e+6; C=147D-12; Q=98; // frequency in hertz ,

```

```
    Capacitance in farad and Q factor of the Q metre
6 //calculation
7 L=1/((2*pi*f)^2*C); // inductance in henry
8 printf(" inductance=%f micro-henry\n",L*10^6);
9 printf("R=%f ohm", (2*pi*f*L)/Q);
10 //result
11 //inductance=110 micro-henry
12 //R=8.8 ohm
```

---

# Chapter 9

## Cathode Ray Oscilloscopes

Scilab code Exa 9.2 peak to peak voltage and time period

```
1 // to find the peak to peak voltage and the time
   period for the sweep generator circuit in fig 9-7
2 // example 9-2 in page 243
3 clc;
4 // Given Data
5 R3=4.2e+3; C1=0.25D-6; Vb1=4.9; Vbe=0.7; //resistance
   in ohm, capacitance in farad and voltages in
   volt respectively
6 UL=2; // UTP,LTP=(+/-)2 V
7 //Calculation
8 dV=2*UL; //peak-peak voltage in volt
9 Ic1=(Vb1-Vbe)/R3; //current in ampere
10 T=dV*C1/Ic1; // time period in seconds
11 printf("peak-peak voltage=%d V p-to-p\n",dV);
12 printf("time period=%d ms",T*1000);
13 //result
14 //peak-peak voltage=4 V p-to-p
15 //time period=1 ms
16 x=linspace(0,1,100);
```

```

17 y=4*x-2;
18 plot(x,y);
19 xlabel('Time period in ms');
20 ylabel('voltage in V');
21 set(gca(),"grid",[1 1]);

```

---

### Scilab code Exa 9.3 amplitude frequency and phase difference

```

1 // to find the amplitude ,frequency and the phase
   difference b/w two waveforms in the figure 9–20
2 // example 9–3 in page 256
3 clc;
4 //Data Given
5 x=[ 'A' 'B'];
6 V=200D-3; // volatge/division=200mV
7 T=0.1D-3; //time/division=0.1ms
8 one_cycle=360; // one cycle=360 degree
9 Vd=[6 2.4]; // vertical divisions of A and B
   respectively
10 Hd=[6 7]; // horizontal divisions of A and B
   respectively
11 //calculation
12 for n=1:2
13     Vp=Vd(n)*V; // V peak-to-peak
14     Tp=T*Hd(n); // time period
15     f=1/Tp; //frequency
16     printf("V peak-peak of wave from %c=%f V\n",x(
17         n),Vp);
17     printf("frequency of wave form %c=%f Hz\n",x(n
18         ),f);
18 end
19 phase_diff=Hd(2)-Hd(1);
20 phase_diff=one_cycle*phase_diff/6; // here one cycle

```

```
    makes 6 horizontal divisions
21 printf("phase difference=%d degree",phase_diff);
22 //result
23 //V peak-peak of wave from A=1.20 V
24 //frequency of wave form A=1667 Hz
25 //V peak-peak of wave from B=0.48 V
26 //frequency of wave form B=1429 Hz
27 //phase difference=60 degree
```

---

#### Scilab code Exa 9.4 pulse amplitude frequency raise and fall time

```
1 // to find the pulse amplitude ,frequency ,rise time
   and fall time of fig9-22
2 // example 9-3 in page 259
3 clc;
4 // Data given
5 Vpd=2; // voltage/division=2 V
6 Hpd=5D-6; // time/division=5 micro seconds per
   division
7 Vd=4; // number of vertical divisions
8 Hd=5.6 // number of horizontal divisions
9 // calculation
10 printf("Pulse amplitude=%d V\n",Vd*Vpd);
11 printf("frequency=%f kHz\n", (1/(Hd*Hpd))/10^3);
12 printf("raise time=%f micro-s\n fall time=%d micro-
   s",0.5*Hpd*10^6,10^6*0.6*Hpd);
13 //result
14 //Pulse amplitude=8 V
15 //frequency=35.7 kHz
16 //raise time=2.5 micro-s
17 //fall time=3.0 micro-s
```

---

### Scilab code Exa 9.5 longest pulse width

```
1 // to find the longest pulse width
2 // example 9-5 in page 261
3 clc;
4 //Given data
5 Ri=10e+6;// input resistance in ohm
6 Cc=0.1e-6;// coaxial cable capacitance in farad
7 //calculation
8 printf("pulse width=%f s",Ri*Cc/10); // here pulse
    width=tuo/10 seconds
9 //result
10 //pulse width=0.1 s
```

---

### Scilab code Exa 9.6 shortest pulse width

```
1 // to find the shortest pulse width that can be
    displayed
2 // example 9-6 in page 262
3 clc;
4 //DATA GIVEN
5 Rs=3.3e+3; Ci=15D-12; // source resistance in ohm and
    input capacitance in farad
6 //calculation
7 printf("shortest pulse width=%f micro-second",10*
    Rs*Ci*2.2*10^6); //here shortest pulse width =10*
    tuo in seconds where tuo is the rise time imposed
    by the oscilloscope
```

```
8 // result
9 // shortest pulse width=1.089 micro-second
```

---

### Scilab code Exa 9.7 raise time

```
1 //to find the raise time of the displayed waveform
2 // example 9-7 in page 262
3 clc;
4 //Data given
5 Rs=3.3e+3; Ci=15D-12; //source resistance in ohm and
   input capacitance in farad
6 tri=[109e-9 327e-9]; //input raise times in seconds
   for which trd is to be determined
7 //calculations
8 tuo=2.2*Rs*Ci;//tuo is the rise time in seconds
   imposed by the oscilloscope
9 for n=1:2
10    trd=sqrt(tri(n)^2+tuo^2); // displayed raise
      time in seconds
11    printf("the displayed raise time for input pulse
      raise time %d ns=%d ns\n",tri(n)*10^9,trd
      *10^9);
12 end
13 //result
14 //the displayed raise time for input pulse raise
   time 109 ns=154 ns
15 //the displayed raise time for input pulse raise
   time 327 ns=344 ns
```

---

### Scilab code Exa 9.8 terminal oscilloscope voltage and frequency

```
1 //to find the terminal oscilloscope voltage and its
   frequency
2 // exmaple 9-8 in page 264
3 clc;
4 //Data given
5 Vs=1; //supply voltage in volt
6 Rs=600; //source resistance in ohm
7 Ri=1e+6;//input resistance in ohm
8 Ci=30D-12;//input parallel capacitance in farad
9 Ccc=100D-12;//coaxial cable capacitance in farad
10 f=100; // signal frequency in hertz
11 //calculation
12 Vi=Vs*Ri/(Rs+Ri); // input voltage in volts
13 Xc=1/(2*pi*f*(Ci+Ccc)); //capacitive reactance in
   ohm for total capacitance
14 printf("the input terminal voltage at 100 Hz =%.4f V
   \n",Vi);
15 printf("when Vi=(Vs-3 dB),\n");
16 f=1/(2*pi*(Ci+Ccc)*Rs); // frequency in hertz
17 printf("frequency=% .2f MHz",f/10^6);
18 //result
19 //the input terminal voltage at 100 Hz =0.9994 V
20 //when Vi=(Vs-3 dB),
21 //frequency =2.04 MHz
```

---

### Scilab code Exa 9.9 find the capacitance

```
1 // to find the capacitance to compensate a probe and
   input capacitance
2 //example 9-9 in page 267
3 clc;
```

```

4 //data given
5 Ci=30D-12; // input capacitance in farad
6 Ccc=100D-12; // coaxial cable capacitance in farad
7 R1=9e+6; Ri=1e+6; // resistances in ohm
8 //calculation
9 C2=Ccc+Ci; // capacitance in farad
10 C1=C2*Ri/R1; // capacitance in farad
11 printf("C1=%f pF\n",C1*10^12);
12 printf("The probe input capacitance as seen from the
    source=%d pF", (C1*C2)*10^12/(C1+C2))
13 //result
14 //C1=14.4 pF
15 //The probe input capacitance as seen from the
    source=13 pF

```

---

### Scilab code Exa 9.10 find the frequency

```

1 // to find the frequency
2 // example 9-10 in page 268
3 clc;
4 // data given
5 C=13D-12; Rs=600; // input capacitance in farad and
    source resistance in ohm
6 //calculation
7 printf("frequency=%f MHz", 1/(2*pi*C*Rs*10^6));
8 //result
9 //frequency =20.4 MHz

```

---

### Scilab code Exa 9.11 find the frequency

```
1 // to determine the frequency
2 // example 9-11 in page 269
3 clc;
4 // Data Given
5 C=3.5D-12; Rs=600; // capacitance in farad and
// source resistance in ohm
6 //calculation
7 printf("frequency=%f MHz", 1/(2*pi*C*Rs*10^6));
8 //result
9 //frequency=75.8 MHz
```

---

### Scilab code Exa 9.12 minimum time per sensitivity

```
1 // to find the minimum time/division sensitivity
2 // example 9-12 in page 278
3 clc;
4 //Data Given
5 f=50e+6;// frequency of the waveform in hertz
6 //calculation
7 T=1/f;//time period in seconds
8 printf("using the five times magnifier ,\n");
9 printf("minimum time/div setting=%d ns/div",5*(T/4)
    *10^9); // here one cycle occupies 4 horizontal
    divisions
10 //result
11 //using the five times magnifier ,
12 //minimum time/div setting=25 ns/div
```

---

### Scilab code Exa 9.13 raise time

```

1 // to determine the raise time displayed waveform
2 // example9-13 in page 279
3 clc;
4 // Data given
5 fH=[20e+6 50e+6]; // upper cut-off frequency in hertz
6 tri=21D-9; // input raise time in seconds
7 // calculation
8 for n=1:2
9     tro=0.35/fH(n); // tro is the raise time in
10    seconds
10    trd=sqrt(tri^2+tro^2); // trd is the fall time in
11    seconds
11    printf(" for fH=%d MHz,\n trd=%d ns\n",fH(n)/10^6,
12    trd*10^9);
12 end
13 //result
14 //for fH=20 MHz,
15 //trd=27 ns
16 //for fH=50 MHz,
17 //trd=22 ns

```

---

# Chapter 11

## signal generators

Scilab code Exa 11.1 maximum and minimum output frequencies

```
1 // to calculate the maximum and minimum output
   frequencies of oscillator in fig 11-1
2 // example 11-1 in page 317
3 clc;
4 // Data Given
5 R=[5e+3 500]; // resistance R2 and R1 all in ohm
6 C1=300D-9; C2=C1; // Capacitance=300 nF
7 // calculation
8 f=['f(min)' 'f(max)'];
9 for n=1:2
10    printf("%s=%d Hz\n",f(n),1/(2*pi*C1*R(n))); //
           frequency in hertz
11 end
12 // result
13 // f(min)=106 Hz
14 // f(max)=1061 Hz
```

---

### Scilab code Exa 11.2 find the resistor values

```
1 //to find the resistor values in fig 11-3
2 // example 11-2 in page 319
3 clc;
4 //data given
5 Vi=5; //input sine wave voltage in volt
6 VR3=[0.1 1]; // range of voltage across resistor R3
    in volt
7 IB=500D-9; // input current to the op-amp in ampere
8 //calculation
9 V=Vi-VR3(1); // with R1 and R2 in the circuit , V=VR1+
    VR2 in volt
10 I3=100D-6; // as I3>>IB , select I3=100 micro ampere
11 R3=VR3(1)/I3; // resistance in ohm
12 R=V/I3; //R=R1+R2 in ohm
13 //with R2 switched off the circuit
14 I3=VR3(2)/R3; // current in ampere
15 VR1=Vi-VR3(2); // voltage in volt
16 R1=VR1/I3; // here I3=I1 , resistance in ohm
17 R2=R-R1; // resistance in ohm
18 printf("R1=%d K-ohm\nR2=%d K-ohm\nR3=%d K-ohm" , R1
    /1000 , R2/1000 , R3/1000);
19 //result
20 //R1=4 K-ohm
21 //R2=45 K-ohm
22 //R3=1 K-ohm
```

---

### Scilab code Exa 11.3 find the output frequency

```
1 // to find the output frequency of the circuit 11-8
2 // example 11-3 in page 326
3 clc;
4 // Data given
5 Vcc=15; // supply voltage=15 V
6 C1=0.1D-6; // capacitance in farad
7 R1=1e+3; R2=10e+3; // resistances in ohm
8 utp=3; ltp=-3; // upper and lower trigger points in
      volt
9 //calculation
10 a=['For contact at top of R1' 'For R1 contact at 10%
      from bottom'];
11 V3=Vcc-1; // voltage in volt
12 dV=utp-ltp; //change in voltage in volt
13 V1=[V3 10*V3/100]; // V1 when R1 is at the top and 10%
      % from the bottom of R1 in volt
14 for n=1:2
15     I2=V1(n)/R2; // current in ampere
16     t=C1*dV/I2; // time in seconds
17     f=1/(2*t); // frequency in hertz
18     printf("%s,\nfrequency=%.2f Hz\n",a(n),f);
19 end
20 //result
21 //For contact at top of R1,
22 //frequency=1166.67 Hz
23 //For R1 contact at 10% from bottom ,
24 //frequency=116.67 Hz
```

---

### Scilab code Exa 11.4 output square wave frequency

```

1 // to find the out put square wave frequency in
11-14
2 // example 11-4 in page 332
3 clc;
4 //Data given
5 Vcc=12; //supply voltage (+/-)12 V
6 R=10^3*[20 6.2 5.6]; //resistance R1, R2 and R3 all
in ohm
7 C1=0.2D-6; // capacitance=0.2 micro farad
8 // calculation
9 Vo=Vcc-1; // out put voltage = (+/-)(Vcc-1) in volt
10 utp=Vo*R(3)/(R(2)+R(3)); // upper trigger point in
volt
11 ltp=-utp; // lower trigger point in volt
12 t=C1*R(1)*log((Vo-ltp)/(Vo-utp)); // time in seconds
13 printf("out put frequency=%d Hz",1/(2*t));
14 //result
15 //out put frequency=121 Hz

```

---

### Scilab code Exa 11.5 output pulse width and the capacitance

```

1 // to find the output pulse width and capacitance
      for the given pulse width in figure 11-15
2 // example 11-5 in page 334
3 clc;
4 //data given
5 Vcc=10; //supply voltage in Volt
6 Vee=10; // supply voltage in volt
7 VB=1; // base voltage in volt
8 R=1e+3*[22 10]; //resistances R1 in ohm and R2 in ohm
9 C=[100D-12 0.01D-6]; //capacitance C1 in farad and C2
      in farad
10 //calculation

```

```

11 Vop=Vcc-1; // positive output voltage in volt
12 Von=-(Vee-1); // negative output voltage in volt
13 PW=C(2)*R(2)*log((Vop-Von)/VB); //pulse width in
    seconds
14 printf("PULSE WIDTH=%d micro-sec\n",PW*10^6);
15 PW=6e-3; //to calculate C2 for PW=6 ms
16 C2=PW/(R(2)*log((Vop-Von)/VB)); // capacitance in
    farad
17 printf("For pulse width of 6 ms,\nC2=%f micro-F",C2*10^6);
18 //result
19 //PULSE WIDTH=289 micro-sec
20 //For pulse width of 6 ms,
21 //C2=0.2 micro-F

```

---

# Chapter 12

## instrument calibration

Scilab code Exa 12.1 accuracy

```
1 //to find the accuracy as a percentage of reading  
    and percentage of full scale  
2 // example 12-1 in page 355  
3 clc;  
4 // Data given  
5 r=[10 50]; //scale readings  
6 c=[-0.5 1.7]; // respective correction  
7 f=100; //full scale reading  
8 //calculation  
9 for n=1:2  
10     pr=c(n)*100/r(n); // accuracy as a percentage of  
        reading  
11     pf=c(n)*100/f; //accuracy as a percentage of full  
        scale  
12     printf("accuracy as a percentage of reading for  
        scale reading %d= %.1f percent\n",r(n),pr);  
13     printf("accuracy as a percentage of full scale=   
        %.1f percent\n",pf);  
14 end
```

```
15 // result
16 //accuracy as a percentage of reading for scale
    reading 10= -5.0
17 //accuracy as a percentage of full scale= -0.5
18 //accuracy as a percentage of reading for scale
    reading 50= 3.4
19 //accuracy as a percentage of full scale= 1.7
```

---

### Scilab code Exa 12.2 error and correction figure

```
1 // to find the wattmeter error and the correction
   figure
2 // example 12-2 in page 357
3 clc;
4 //Data given
5 V=114; // measured voltage in volt
6 P=120; // indicated power in watt
7 I=1; // current in ampere
8 //calculation
9 cf=V*I-P; // here power = v*i , capacitance in farad
10 e=cf*100/P; //percentage error
11 printf("correction figure=%d W\n",cf);
12 printf("wattmeter error=%d percent",e);
13 //result
14 //correction figure=-6 W
15 //wattmeter error=-5 percent
```

---

### Scilab code Exa 12.4 resistance voltage and current

```

1 // to find the resistance . , voltage and current in
fig 12-8
2 //examole 12-4 in page364
3 clc;
4 // Data given
5 V=1.0190; // the standard cell voltage in volt , VBC=
VB2=V
6 VB1=3; // terminal voltage of battery B1 in volt
7 RAB=100; l=100D-2; //resistance in ohm and length
in meter of the wire AB
8 lBC=50.95D-2; //length of BC in meter
9 //calculation
10 printf("At calibiration ,\n");
11 VAB=l*V/lBC; // voltage accross AB in volt where V/
lBC is the volatge per unit length
12 I=VAB/RAB; // current in ampere
13 printf("current through AB=%d mA\n",I*1000);
14 R1=(VB1-VAB)/I; // resistance in ohm
15 printf("Resistance R1=%d ohm\n\n",R1); // R=V/I ohm
16 printf("Vx=%f V\n",94D-2*V/lBC); //volatge Vx in
volt when null is obtained at 94.3cm
17 printf("\nR2=%d K-ohm", (VB1+V)/(20D-6*1000)); // R2
in ohm to limit the standard cell current to a
maximum of 20 micro-A
18 //result
19 //At calibiration ,
20 //current through AB=20 mA
21 //Resistance R1=50
22
23 //Vx=1.88 V
24
25 //R2=200 K-ohm

```

---

### Scilab code Exa 12.5 maximum voltage and instrument resolution

```
1 // to find the maximum measurable voltage and the
   instrument resolution
2 // example 12-5 in page 367
3 clc;
4 // Data given
5 V=1.0190; // Standard cell voltage V=VR3=VB2 in volt
6 R13=100; R3=509.5; R4=290.5; // R13 is the slider
   resistance and resistance R3 and R4 all in ohm
7 R=100; // resistances R6 through R12 in ohm
8 l=100D-2; // length of the sliding wire in meter
9 // calculation
10 VAE=(V/R3)*(R3+R4); // maximum measurable voltage in
   volt where I1=V/R3
11 printf("Maximum measurable voltage=%f V\n",VAE);
12 I2=VAE/(8*R); // current I2 in ampere
13 VAB=I2*R13; // voltage across R13 in volt
14 Vpl=VAB/l; // slide wire voltage per unit length in
   volt/meter
15 printf("instrument resolution=(+/-)%f mV",Vpl)
16 // result
17 //Maximum measurable voltage=1.6 V
18 //instrument resolution=(+/-)0.2 mV
```

---

# Chapter 16

## Laboratory power supplies

Scilab code Exa 16.1 load effects and line regulation

```
1 //to find the source & load effects and load & line
   regulation
2 // example 16-1 in page 423
3 clc;
4 //Data Given
5 Es=[12 11.95]; // change in Dc power supply when ac
   drops by 10%
6 Eo=[12 11.9]; // change in output voltage when load
   current goes from zero to maximum
7 //calculation
8 printf("source effect=%d mV\n", (Es(1)-Es(2))*1000);
9 printf("line regulation=% .2f percent\n", (Es(1)-Es(2))
   )*100/Es(1));
10 printf("load effect=%d mV\n", (Eo(1)-Eo(2))*1000);
11 printf("line regulation=% .2f percent\n", (Eo(1)-Eo(2))
   )*100/Eo(1));
12 //result
13 //source effect=50 mV
14 //line regulation=0.42 percent
```

```
15 //load effect=99 mV  
16 //line regulation=0.83 percent
```

---

### Scilab code Exa 16.2 maximum and minimum output voltage

```
1 // to find the maximum and minimum output voltages  
    in the fig 16-8(b)  
2 // example 16-2 in page 428  
3 clc;  
4 //Data given  
5 Vz=6; R=1000*[0 5.6 5.6 3]; // zener voltage and the  
    resistance values  
6 A=['when the moving contact is at the bottom of R4'  
    '0' '0' 'when the moving contact is at the top of  
    R4'];  
7 //calculation  
8 for n=1:3:4  
9     I3=Vz/(R(3)+R(n));  
10    Eo=I3*sum(R);  
11    printf("%s,Eo=%.1f V\n",A(n),Eo);  
12 end  
13 //result  
14 //when the moving contact is at the bottom of R4,Eo  
    =15.2 V  
15 //when the moving contact is at the top of R4,Eo=9.9  
    V
```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)