

Scilab Textbook Companion for  
Engineering Basics  
by T. Thyagarajan<sup>1</sup>

Created by  
Qureshi Mehtab Alam Niyaz Ahmed  
B.E (EXTC)  
Electronics Engineering  
Mumbai University  
College Teacher  
S. Chaya Ravindra  
Cross-Checked by  
Banda Nawaz

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Engineering Basics

**Author:** T. Thyagarajan

**Publisher:** New Age International , New Delhi

**Edition:** 3

**Year:** 2000

**ISBN:** 81-224-1274-2

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 concept of electric current and laws	5
2 Magnetic Current	11
3 Electromagnetism	18
4 Ac circuit	23
5 Electrical Machine	40

# List of Scilab Codes

Exa 1.1	specific resistance . . . . .	5
Exa 1.2	resistance . . . . .	5
Exa 1.3	resistance and current . . . . .	6
Exa 1.4	resistance . . . . .	6
Exa 1.5	resistance . . . . .	7
Exa 1.6	resistance . . . . .	7
Exa 1.7	current . . . . .	7
Exa 1.9	current . . . . .	8
Exa 1.10	resistance of coil . . . . .	8
Exa 1.11	power . . . . .	8
Exa 1.12	Bill amount . . . . .	9
Exa 1.18	resistance . . . . .	9
Exa 1.19	resistance . . . . .	10
Exa 2.1	flux density . . . . .	11
Exa 2.2	Magnetic field strength . . . . .	11
Exa 2.3	reluctance current and . . . . .	12
Exa 2.4	relative permeability . . . . .	12
Exa 2.5	mmf . . . . .	12
Exa 2.6	magnetising force relative permeability mag- netic flux density . . . . .	13
Exa 2.7	Magnetising Current . . . . .	14
Exa 2.8	number of amperes turns . . . . .	14
Exa 2.9	ampere turns . . . . .	15
Exa 2.10	exciting current . . . . .	16
Exa 2.11	hysteris loop . . . . .	16
Exa 3.1	emf induced . . . . .	18
Exa 3.2	emf induced . . . . .	18
Exa 3.3	inductance of the coil . . . . .	19

Exa 3.4	self inductance . . . . .	19
Exa 3.5	inductance and emf induced . . . . .	19
Exa 3.6	inductance and emf induced . . . . .	20
Exa 3.7	inductance and emf induced . . . . .	21
Exa 3.8	mutual inductance and emf induced . . . . .	21
Exa 3.9	energy stored . . . . .	22
Exa 3.10	force . . . . .	22
Exa 4.1	voltage and current factors . . . . .	23
Exa 4.2	voltage equation . . . . .	23
Exa 4.3	voltage and time . . . . .	24
Exa 4.12	power dissipated . . . . .	24
Exa 4.13	inductive reactance . . . . .	25
Exa 4.15	current . . . . .	25
Exa 4.16	inductance and current . . . . .	26
Exa 4.17	voltage and current . . . . .	26
Exa 4.18	current . . . . .	26
Exa 4.19	capacitance current . . . . .	27
Exa 4.20	frequency . . . . .	27
Exa 4.21	phase angle . . . . .	28
Exa 4.22	voltage and current . . . . .	28
Exa 4.23	voltage . . . . .	29
Exa 4.24	resistance . . . . .	29
Exa 4.25	inductance . . . . .	30
Exa 4.27	voltage across choking coil . . . . .	30
Exa 4.28	time equation for v and i . . . . .	31
Exa 4.29	current and voltage . . . . .	31
Exa 4.30	voltage across R and C . . . . .	32
Exa 4.31	resistance and capacitance . . . . .	32
Exa 4.32	capacitance . . . . .	33
Exa 4.33	voltage across RLC . . . . .	33
Exa 4.34	current and voltage . . . . .	34
Exa 4.35	maximum current . . . . .	35
Exa 4.36	frequency response . . . . .	35
Exa 4.37	current voltage and power . . . . .	35
Exa 4.38	current and power . . . . .	36
Exa 4.40	voltage and current . . . . .	37
Exa 4.41	power absorbed . . . . .	38
Exa 4.42	power absorbed . . . . .	38

Exa 4.43	power factor . . . . .	39
Exa 5.1	determine the emf induced in the coil . . . . .	40
Exa 5.2	emf induced in coil . . . . .	40
Exa 5.3	speed . . . . .	41
Exa 5.4	induced emf . . . . .	41
Exa 5.5	emf induced . . . . .	42
Exa 5.6	emf induced . . . . .	42
Exa 5.7	back emf . . . . .	43
Exa 5.8	power . . . . .	43
Exa 5.9	speed . . . . .	43
Exa 5.10	speed of rotor . . . . .	44
Exa 5.11	torque . . . . .	44
Exa 5.12	number of turns and current . . . . .	45
Exa 5.13	flux density . . . . .	45
Exa 5.14	current . . . . .	46
Exa 5.15	efficiency . . . . .	46
Exa 5.16	speed and emf . . . . .	47
Exa 5.17	speed . . . . .	47
Exa 5.18	poles speed frequency . . . . .	48
Exa 5.19	induced emf . . . . .	48

# Chapter 1

## concept of electric current and laws

Scilab code Exa 1.1 specific resistance

```
1 //find the specific resistance of the material
2 L =12 //meter
3 A=0.01*10^-4 //m^2
4 R=0.2 //ohm
5 p=R*A/L //specific resistance
6 disp('value of specific resistance='+string(p)+'
      ohm -meter')
```

---

Scilab code Exa 1.2 resistance

```
1
2 //resistance at 40 degree
3 a0=0.0043
4 t1=27
5 t2=40
6 R1=1.5
```



```
7 R2=R1*(1+a0*t2)/(1+a0*t1)
8 disp('value of resistance='+string(R2)+ ' ohm')
```

---

### Scilab code Exa 1.3 resistance and current

```
1
2 //find the total R.I.V
3 R1=5
4 R2=10
5 R3=15
6 V=120
7 R=R1+R2+R3
8 I=V/R
9 V1=I*R1
10 V2=I*R2
11 V3=I*R3
12 disp('Voltage V3='+string(V3)+' volts ', 'Voltage
      V2='+string(V2)+' volt ', 'Voltage V1='+string(V1)
      +' volts')
```

---

### Scilab code Exa 1.4 resistance

```
1
2 //find the equivalent resistance of series parallel
  combination
3 Rab=(2*4)/(2+4)
4 Rbc=(6*8)/(6+8)
5 Rac=Rab+Rbc
6 disp('resistance across AC='+string(Rac)+' ohms')
```

---

### Scilab code Exa 1.5 resistance

```
1
2 //find the equivalent resistance of series parallel
   combination
3 Rab=4
4 Rbc=(12*8)/(12+8)
5 Rcd=(3*6)/(3+6)
6 Rad=Rab+Rbc+Rcd
7 disp('resistance across AC='+string(Rad)+' ohms'
   )
```

---

### Scilab code Exa 1.6 resistance

```
1
2 //what resistance must be connected in parallel
3 R1=8
4 R2=48/2//R1*R2/R1+R2
5 disp('R2='+string(R2)+' ohms')
```

---

### Scilab code Exa 1.7 current

```
1
2 //calculate the current I1.I2
3 I=12
4 R1=6
5 R2=8
6 I1=I*R2/(R1+R2)
7 I2=I*R1/(R1+R2)
8 disp('I1='+string(I1)+' amps' , 'I2 ='+string(I2)+
   ' amps')
```

---

### Scilab code Exa 1.9 current

```
1
2 //find how current divide in circuit
3 R1=0.02
4 R2=0.03
5 I1=(10*R2)/(R1+R2)
6 I2=(10*R1)/(R1+R2)
7 disp('I2='+string(I2)+' amps' , 'I1='+string(I1)
      + ' amps')
```

---

### Scilab code Exa 1.10 resistance of coil

```
1
2 //what is the resistance of each coil
3 V=200
4 I=25
5 P1=1500
6 R1=(V*I)/P1
7 R=V/I //total resistance
8 R2=R*R1/(R1-R)
9 disp('R2='+string(R2)+' ohms')
```

---

### Scilab code Exa 1.11 power

```
1
2 //what is the resistance of each coil
3 V=100
4 P=1500
```

```

5 R=(V^2/P)/2
6 Ra=R
7 Rb=R
8 Rc=R
9 R1=((Ra*Rc)/(Ra+Rc))+Rb
10 I=V/R1
11 I1=(I*Ra)/(Ra+Rc)
12 I2=(I*Ra)/(Ra+Rc)
13 Pa=I*I*Ra
14 Pb=I1*I1*Rb
15 Pc=I2*I2*Rc
16 disp('Pc=' + string(Pc) + ' watts ', 'Pb=' + string(Pb)
      + ' watts ', 'Pa=' + string(Pa) + ' watts ')

```

---

#### Scilab code Exa 1.12 Bill amount

```

1
2 //determine the energy consume in a house in the
   month
3 L=3600//six lamp 1000 watt each for six days
4 H=3000//one haeter
5 M=735.5//single phase motor
6 F=2400//four fans 75W
7 T=L+H+M+F//total energy consumed in watt
8 TE=T*30/1000
9 C=0.9//cost of energy
10 B=TE*0.9//Bil amount
11 disp('B= ' + string(B) + ' ')

```

---

#### Scilab code Exa 1.18 resistance

```

1
2 //convert the delta circuit

```

```

3 Rry=4
4 Ryb=1
5 Rbr=5
6 Rr=(Rbr*Rry)/(Rry+Rbr+Ryb)
7 Ry=(Rry*Ryb)/(Rry+Rbr+Ryb)
8 Rb=(Rbr*Ryb)/(Rry+Rbr+Ryb)
9 disp('Rb=' + string(Rb) + ' ohms ' , 'Ry=' + string(Ry) +
      ' ohms ' , 'Rr=' + string(Rr) + ' ohms ')

```

---

### Scilab code Exa 1.19 resistance

```

1
2 //convert star circuit
3 Rr=2
4 Ry=0.67
5 Rb=1
6 Rry=(Rr*Ry)+(Ry*Rb)+(Rb*Rr)/Rb
7 Ryb=(Rr*Ry)+(Ry*Rb)+(Rb*Rr)/Rr
8 Rbr=(Rr*Ry)+(Ry*Rb)+(Rb*Rr)/Ry
9 disp('Rbr=' + string(Rbr) + ' ohms ' , 'Ryb=' + string(Ryb)
      + ' ohms ' , 'Rry=' + string(Rry) + ' ohms ')

```

---

## Chapter 2

# Magnetic Current

Scilab code Exa 2.1 flux density

```
1
2 //determine the flux density
3 F=0.5e-3; //webers
4 A=4*10^-4; //meter^2
5 B=F/A;
6 disp('flux density is = '+string(B)+' Wb/m^2');
```

---

Scilab code Exa 2.2 Magnetic field strength

```
1
2 //determine the magnetic field strength at the
   centre of solinoid
3 I=2; //amp
4 L=50e-2; //meter
5 N=100; //turns
6 H=(N*I)/L;
7 disp('magnetic field strength=' +string(H)+' AT/m');
```

---

### Scilab code Exa 2.3 reluctance current and

```
1
2 //calculate the reluctance and current
3 A=5e-4
4 N=250
5 l=50e-2
6 F=700e-6
7 u=380
8 S=1/(4*%pi*10^-7*A*u)
9 I=F*S/N
10 disp('current='+string(I)+'amps' , 'reluctance =' +
      string(S)+'AT/Wb')
```

---

### Scilab code Exa 2.4 relative permeability

```
1
2 //determine the value of relative permeability of
  iron
3 D=15e-2
4 l=%pi*15e-2
5 N=450
6 I=2
7 B=1.2
8 u=B/(4*%pi*10^-7*N*I*l)
9 disp('value of relative permeability='+string(u)+'
      ')
```

---

### Scilab code Exa 2.5 mmf

```

1
2 //calculate the mmf
3 l=1.5
4 u=1600
5 B=1.2
6 H1=B*l/(4*pi*10^-7*u)
7 la=1e-3
8 ua=1
9 H2=B*la/(4*pi*10^-7*ua)
10 H=H1+H2
11 disp('total amprs turns =' + string(H) + ' AT' , 'amprs
      turns=' + string(H2) + ' AT', 'amprs turns=' + string(
      H1) + ' AT')

```

---

Scilab code Exa 2.6 magnetising force relative permeability magnetic flux density

```

1
2 //calculate the magnetising force relative
  permeability
3 A=5e-4
4 l=25e-2
5 N=100
6 I=2
7 F=0.3e-3
8 H=(N*I)/l
9 u=(F*l)/(N*I*A*4*3.14*10^-7)
10 B=(u*H*4*3.14*10^-7)
11 I1=5
12 F1=0.58e-3
13 H1=(N*I1)/l
14 u1=(F1*l)/(N*I*A*4*3.14*10^-7)
15 B1=(u1*H*4*3.14*10^-7)
16 disp('flux density B1=' + string(B1) + ' Wb/m^2' , '
      flux density B =' + string(B) + ' Wb/m^2' )

```

---



### Scilab code Exa 2.7 Magnetising Current

```
1
2 //calculate the magnetising current
3 A=0.01
4 l=2e-3
5 u=1
6 F=800e-6
7 B=F/A//flux
8 H=B/(4*3.14*10^-7*u)
9 N=(H*l)
10 L=150e-2
11 v=600
12 f=9.6e-4
13 N1=(f*L)/(v*A*4*pi*10^-7)
14 N2=N1+N
15 n=200
16 M=N2/n
17 disp( 'Magnetising current = '+string(M)+' A' , '
      Total amps turns= '+string(N2)+' AT' , 'amps
      turn iron= '+string(N1)+' AT' , 'amps turn for
      air= '+string(N)+' AT' )
```

---

### Scilab code Exa 2.8 number of amperes turns

```
1
2 //find the number of amprs turns required
3 A=25e-4
4 F=1.2e-3
5 u=1 //air path
6 l=0.25e-2
7 N=(F*l/(4*pi*10^-7*A*u))*2 // for two air gaps
```

```

8 v=2000 // iron path
9 L=50e-2
10 N1=(F*L)/(v*A*4*%pi*10^-7)
11 N2=N+N1
12 disp( 'total amps turns = '+string(N2)+' AT'
        , 'amps turn for air= '+string(N1)+' AT'
        , 'amps turn for air= '+string(N)+' AT' )

```

---

### Scilab code Exa 2.9 ampere turns

```

1
2 //calculate the circuit current
3 u=1//for air gap
4 F=1.5e-3//flux
5 A=9e-4 //area
6 B=F/A
7 H=B/(4*3.14*10^-7*u)
8 l=4e-3//air gap
9 S=H*l//amps turns in air gap
10 l=4e-3//air gap
11 u1=800// for iron gap
12 A1=750e-6
13 B1=F/A1
14 H1=B1/(4*3.14*10^-7*u1)
15 l1=270e-3
16 S1=H1*l1
17 u2=1000//for P,Q,R
18 H2=B/(4*3.14*10^-7*u2)
19 Ip=135e-3
20 Iq=270e-3
21 Ir=135e-3
22 S2=H2*(Ip+Iq+Ir)//amps turns
23 TNn=S+S1+S2
24 TN=4000
25 EI=TNn/TN

```

```
26 disp('exciting current= ' +string(EI)+' amps' )
```

---

### Scilab code Exa 2.10 exciting current

```
1
2 //calculate the total amprers turns
3 u=1//for air gap
4 F=1.2e-3//flux
5 A=10e-4 //area
6 B=F/A
7 H=B/(4*3.14*10^-7*u)
8 l=0.2e-3// air gap
9 S=H*l//amps turns in air gap
10 l1=15e-2//air gap
11 A1=8e-4
12 H1=450
13 S1=H1*l1
14 F1=0.6e-3
15 B1=F1/A1
16 H2=140
17 S2=H2*30e-2
18 TN=500
19 TAN=S+S1+S2
20 EI=TAN/TN
21 disp('exciting current =' +string(EI)+'amps' )
```

---

### Scilab code Exa 2.11 hysteresis loop

```
1
2 //calculate the hysteresis loss
3 A=50//area of hysteresis
4 H=200
5 B=0.2
```

```
6 f=50
7 D=10// density
8 M=1000// mass
9 V=M/D// velocity is mass /density
10 HL=A*H*B// .....j/m^2/cycle
11 HL1=A*H*B*10^-4// .....j/cycle
12 HL2=A*H*B*50*1e-4// .....j/s
13
14 disp('Hysteresis loop = '+string(HL2)+' j/s')
```

---

# Chapter 3

## Electromagnetism

Scilab code Exa 3.1 emf induced

```
1
2 //calculate the emf induced in the coil
3 N=200
4 F1=1e-3
5 F2=3e-3
6 F3=F2-F1
7 t=0.1
8 e=N*F3/t //neglecting negative sign
9 disp('induced emf= ' +string(e)+' volts')
```

---

Scilab code Exa 3.2 emf induced

```
1
2 //calculate the emf induced in a long wire
3 B=1.2; //weber/meter ^2... flux density
4 V=4; //meter/second.. velocity of conductor
5 l=2; //meter... length of
6 e=(B*V*l*1) //sin90=1
```

```
7 disp('emf induced in the conductor='+string(e)+' volt
      ');
```

---

### Scilab code Exa 3.3 inductance of the coil

```
1
2 //find the inductance of the coil
3 N=1500; // number of turns
4 I=10; //amp... current in coil
5 F=.5*10^-3; //weber... flux
6 L=N*I/I;
7 disp('inductance of coil='+string(L)+' henry');
```

---

### Scilab code Exa 3.4 self inductance

```
1
2 //P3.4 calculate its self induction
3
4 Ur=1;
5 N=400;
6 l=30e-2;
7 A=5e-4;
8 U0=4e-7*%pi;
9 S=1/(U0*Ur*A);
10 L=N^2/S;
11 disp('Self inductance is = '+string(L)+' henry', 'S =
      '+string(S));
```

---

### Scilab code Exa 3.5 inductance and emf induced

```

1
2 //calculat the inductance and emf induced in the
   coil
3 u=1 //air core torroidal ring
4 D=25e-2
5 l=3.14*D
6 N=500
7 d=4e-2 //cross sectional diameter
8 A=(3.14*d*d)/4 //cross sectional area
9 s=1/(4*3.14*10^-7*u*A)
10 L=N^2/s // self inductance
11 dI=10
12 dt=50e-3
13 e=(L*dI)/dt
14 disp('Induced emf=' +string(e)+' volts' , '
      Inductance = ' +string(L)+' henry' )

```

---

**Scilab code Exa 3.6** inductance and emf induced

```

1
2 //calculate the induced emf in the coil
3 A=4e-4 //cross sectional is a squar side
4 u=1 //air core torroidal ring
5 D=25e-2
6 l=3.14*D
7 N=500
8 d=4e-2 //cross sectional diameter
9 s=1/(4*3.14*10^-7*u*A)
10 L=N^2/s // self inductance
11 dI=10
12 dt=50e-3
13 e=(L*dI)/dt
14 disp('Induced emf=' +string(e)+' volts' , '
      Inductance = ' +string(L)+' henry' )

```

---

### Scilab code Exa 3.7 inductance and emf induced

```
1
2 //calculate the induced emf in coil
3 di=5
4 dt=0.05
5 L=5.029e-4
6 di1=400
7 dt1=1
8 e=L*di/dt
9 e1=L*di1/dt1
10 disp('Induced emf=      '+string(e1)+' volts' , '
      Induced emf=      '+string(e)+' volts')
```

---

### Scilab code Exa 3.8 mutual inductance and emf induced

```
1
2 ////calculate the mutual inductance between the two
   coil
3 N1=50
4 N2=400
5 A=150e-4
6 l=200e-2
7 u=2500
8 s=1/(4*3.14*10^-7*A*u)
9 M=(N1*N2)/s
10 dI1=24
11 dt=0.03
12 eM2=M*dI1/dt
13 disp('induced emf=      '+string(eM2)+' volts' , '
      Mutual inductance=  '+string(M)+' henry' , 's=
      '+string(s)+' AT/Wb')
```



---

**Scilab code Exa 3.9** energy stored

```
1
2 //find the energy stored in it
3 L=0.5
4 I=2
5 E=0.5*L*I*I
6 disp('Energy stored= ' +string(E)+' joule')
```

---

**Scilab code Exa 3.10** force

```
1
2 //determine the pull between poles and keeper
3 A=15e-4
4 B=1.2
5 U=1
6 F=2*B*B*A/(2*4*3.14*10^-7)
7 disp('Total force=' +string(F)+' N')
```

---

# Chapter 4

## Ac circuit

Scilab code Exa 4.1 voltage and current factors

```
1
2 //
3 //i=40sin 314t
4 //i=Imsin wt
5 Im=40
6 w=314
7 Iav=Im/1.414
8 Irms=Im*2/3.14
9 f=w/(2*3.14)
10 Ff=Irms/Iav
11 Pf=Im/Irms
12 disp('peak factor='+string(Pf)+ ' ', 'form
      factor='+string(Ff)+ ' ', 'frequency =' +string
      (f)+ ' ')
```

---

Scilab code Exa 4.2 voltage equation

```
1
```

```

2 //determine the voltage sin wave
3 f=50
4 V=50
5 Vm=V*1.414
6 w=2*3.14*f
7 t=(0:0.1:5*%pi)';
8 plot2d1('onn',t,[5*sin(t)])
9 disp('voltage equation v=70.7 sin(314)t')

```

---

#### Scilab code Exa 4.3 volatage and time

```

1
2 //determine the time taken to reach the intantaneous
   of 150
3 f=50
4 Vr=200
5 Vm=Vr*1.414
6 t=2.5e-3
7 w=2*3.14*f*t
8 v=Vm*sind(w*180/%pi)
9 v1=150 //v1=Vmsimwt
10 t=1/18000*asind(150/282.8)
11 disp('voltage equation='+string(v)+' volts ', ' ',
      'time='+string(t)+' seconds ')

```

---

#### Scilab code Exa 4.12 power dissipated

```

1
2 //determine the power dissipated in resistance
3 //v=200 sind 314t
4 Vm=200;
5 o=314; //@=omega
6 //i=50 sind 314t

```

```
7 Im=50
8 o=314
9 R=Vm/Im
10 I=Im/1.414
11 P=(I*I*R)
12 disp('power dissipated in resistance='+string(P)+'
        watts')
```

---

#### Scilab code Exa 4.13 inductive reactance

```
1
2 //determine the inductive reactance of the coil
3 L=0.25;//henry .... inductance
4 f=50;//hertz ... frequency
5 X=2*3.14*f*L
6 disp('value of inductive reactance='+string(X)+'ohms
        ');
```

---

#### Scilab code Exa 4.15 current

```
1
2 //calculate the current flowing through the coil
3 L=0.05
4 V=230
5 f=60
6 X=(2*%pi*f*L)
7 I=V/X
8 disp(' the current flowing through the coil='+string
        (I)+'amps')
```

---

#### Scilab code Exa 4.16 inductance and current

```
1
2 //determine the value of inductance
3 I=5;//amp
4 V=200;//volt
5 f=50;//hertz
6 X=V/I;
7 L=40/(2*%pi*50);
8 disp('the value of inductive reactance='+string(X)+
      'ohms' , 'value of inductors='+string(L)+'
      henry');
```

---

#### Scilab code Exa 4.17 voltage and current

```
1
2 //write the time equation for voltage and current
3 Vrms=150
4 Vm=2*1.414*Vrms
5 f=50
6 L=0.2
7 X=2*3.14*f*L
8 Im=Vm/X
9 disp('current equation i=212.132 sin(314)t' , '
      voltage equation v=3.376 sin(314t-90)' , ' Im= '+
      string(Im)+ ' ')
```

---

#### Scilab code Exa 4.18 current

```
1
2 //calculate the current
3 C=25e-6;
4 V=200
```

```

5 f=60 //frequency half
6 f2=120 //frequency doubled
7 Xc=1/(2*%pi*f*C)
8 Xc=1/(2*%pi*f2*C)
9 I=V/Xc
10 disp('frequency half='+string(f)+'hz' , 'frequency
      douled='+string(f2)+'hz')

```

---

#### Scilab code Exa 4.19 capacitance current

```

1
2 //determine the value of capacitance nd current
3 Xc=25
4 V=200
5 f=50
6 C=1/(2*%pi*f*Xc)
7 I=V/Xc
8 disp('the value of capacitance =' +string(C)+'farad ',
      'the value of current='+string(I)+'amps')

```

---

#### Scilab code Exa 4.20 frequency

```

1
2 //find the frquency
3 Vrms=110
4 c=15e-6
5 I=0.518
6 Xc=Vrms/I
7 f=1/(2*%pi*Xc*c)
8 disp('value of frequency='+string(f)+'hz')

```

---

### Scilab code Exa 4.21 phase angle

```
1
2 //calculate the value of current
3 R=10; //ohms
4 L=0.02; //henry
5 V=250; //volt
6 f=50; //hertz
7 X=(2*%pi*f*L)
8 Z=sqrt(R^2+X^2)
9 I=V/Z
10 coso=R/Z
11 o=acosd(coso)
12 disp('phase angle='+string(o)+'degree', 'current
      flowing through coil='+string(I)+'amp')
```

---

### Scilab code Exa 4.22 voltage and current

```
1
2 //find the inductance impd, curent ,power factr ,
   voltage .power
3 R=50; //ohms
4 L=0.5; //henry
5 V=200; //volt
6 f=50; //hertz
7 X=(2*%pi*f*L)
8 Z=sqrt(R^2+X^2)
9 I=V/Z
10 coso=R/Z
11 sino=R/Z
12 o=acosd(coso)
13 o1=asind(sino)
14 Vr=I*R
15 Vl=I*X
16 AP=V*I*coso
```

```

17 RP=V*I*sino
18 APP=V*I;
19 //disp('Apprent power='+string(AP)+'degree'' phase
    angle='+string(o)+'degree', 'crnt flowing
    through coil='+string(I)+'amp')
20 disp('The time equation of current = 1.711 sin(314t
    -72.34)')

```

---

#### Scilab code Exa 4.23 voltage

```

1
2 //determine the supply voltage
3 R=15; //ohms
4 L=0.15; //henry
5 I=20; //ampss
6 f=50; //hertz
7 X=2*%pi*50*0.15
8 Z=sqrt(R^2+X^2)
9 V=I*Z
10 disp('supply voltage = '+string(V)+'volts');

```

---

#### Scilab code Exa 4.24 resistance

```

1
2 //determine the supply voltage
3 V=200; //ohms
4 L=0.4; //henry
5 I=0.5; //ampss
6 f=50; //hertz
7 Z=V/I
8 X=2*%pi*f*L
9 R=sqrt(Z^2+X^2)
10 disp('Resistance = '+string(R)+'ohms')

```



---

Scilab code Exa 4.25 inductance

```
1
2 //determine the inductance of the coil
3 R=6
4 V=250; //volts
5 I=1.5; //amps
6 Z=V/I; //impedance
7 f=60; //hetrz
8 X=sqrt(Z^2-R^2)
9 L=X/(2*%pi*f)
10 disp('inductance of coil='+string(L)+ 'henry')
```

---

Scilab code Exa 4.27 voltage across choking coil

```
1
2 //determine the inductance of the coil and voltage
  across each element
3 I=7
4 V=200
5 f=50
6 R=10
7 r=1.5 //rasistance choke coil
8 V1=I*R
9 V3=I*r
10 V2=sqrt(V^2-(V1+V3)^2)
11 X=V2/I //inductive reactance
12 L=X/(2*%pi*f)
13 V4=sqrt(V2^2+V3^2) ///voltage across choking coil
14 disp('voltage across choking coil='+string(V4)+'
  volts' , 'inductor='+string(L)+'henry')
```

---

Scilab code Exa 4.28 time equation for v and i

```
1
2 4.28 //voltage across R$C
3 C=15e-6; //farad ..
4 R=100; //ohms
5 V=100; //volts
6 f=50; //hertz
7 Xc=1/(2*%pi*f*C);
8 Z=sqrt(R^2+(Xc^2));
9 I=V/Z;
10 coso=R/Z;
11 sino=R/Z
12 o=acosd(coso);
13 o=asind(sino)
14 Vr=I*R;
15 Vc=I*Xc;
16 AP=V*I*coso
17 RP=V*I*sino
18 APP=V*I;
19 disp('The time equation of current i = (0.426)1.414
      sin(314t-64.34)', 'Apparent power =' +string(APP)
      ) + 'vars ', 'ACTIVE POWER =' +string(AP) +
      ' watts ' )
```

---

Scilab code Exa 4.29 current and voltage

```
1
2 //determine the frequency
3 R=30; //ohms
4 L=0.5; //henry
5 f=50; //hertz
```

```

6 X=(2*%pi*f*L)
7 Z=R+%i*X
8 V=86.6+%i*50
9 I=V/Z
10 disp('current = '+string(I)+ 'A')

```

---

#### Scilab code Exa 4.30 voltage across R and C

```

1
2 //find the equation of voltage and current
3 C=10e-6;//farad..
4 R=300;//ohms
5 //i=2 sin 314t
6 V=100;//volts
7 f=50;//hertz
8 Xc=1/(2*%pi*f*C);
9 Z=sqrt(R^2+(Xc^2));
10 Im=2
11 Vm=2*Z
12 coso=R/Z;
13 o=acosd(coso);
14 disp('The time equation of voltage Vr = 600sin(314t
      )' , 'The time equation of voltage Vc = 636sin(
      wt-90)')

```

---

#### Scilab code Exa 4.31 resistance and capacitance

```

1
2 //calculate the value of RESISTANCE AND CAPACITANCE
3 I=2.5;//amps
4 V=150;//volts
5 f=50;//hetz
6 Z=V/I;

```

```

7 P=100; //watt .. power
8 R=P/(I*I)
9 Xc=sqrt(Z^2-R^2)
10 C=1/(2*3.14*f*Xc); // capacitance
11 disp('find the value of capacitance='+string(C)+'
      farad ');

```

---

#### Scilab code Exa 4.32 capacitance

```

1
2 //determine the value of capacitance
3 V1=100; //volts
4 V=250; //volts
5 f=50; //hertz
6 P=500; //watt
7 I=P/V;
8 V2=sqrt(V^2-V1^2); //volts
9 Xc=V2/I;
10 C=1/(2*%pi*f*Xc);
11 disp('determine the value of capacitance='+string(C)
      +'farad ');

```

---

#### Scilab code Exa 4.33 voltage across RLC

```

1
2 //determine the ind.reactance nd capacitance nd
  voltage across R L C
3 R=25
4 C=20e-6
5 L=0.15
6 V=250
7 f=50
8 X=2*%pi*f*L

```

```

9 Xc=1/(2*%pi*f*C)
10 Z=sqrt(R^2+(X-Xc)^2)
11 I=V/Z
12 coso=R/Z
13 o=acosd(coso)
14 Vr=I*R
15 Vl=I*X
16 Vc=I*Xc
17 disp('Vr='+string(Vr)+'volts' , 'Vl='+string(Vl)+'
      volts' , 'Vc='+string(Vc)+'volts' , 'phase
      angle='+string(o)+'degree' , 'current='+string(I)
      )+'amps' , 'impedance='+string(Z)+'ohms' , '
      ind.reactance='+string(X)+'ohms' , 'ind
      capacitance='+string(Xc)+'ohms')

```

---

#### Scilab code Exa 4.34 current and voltage

```

1
2 //determine the current also V1 and V2
3 V=250
4 f=50
5 R1=10
6 L1=0.15
7 C1=10e-6
8 X1=2*%pi*f*L1
9 Xc1=1/(2*%pi*f*C1)
10 R2=8
11 L2=0.25
12 X2=2*%pi*f*L2
13 Z=sqrt((R1+R2)^2+[(X1+X2)-Xc1]^2)
14 I=V/Z
15 Z1=sqrt(R1^2+(X1-Xc1)^2)
16 V1=I*Z1
17 Z2=sqrt(R2^2+X2^2)
18 V2=I*Z2

```

```
19 disp('value of current='+string(I)+'amps' , 'v1='+  
    string(V1)+'volts' , 'V2='+string(V2)+'volts')
```

---

#### Scilab code Exa 4.35 maximum current

```
1  
2 //determine the value of max. current  
3 C=30e-6;//farad  
4 R=12;//ohms  
5 L=0.2;//henry  
6 V=200;//volt  
7 I=V/R  
8 f=1/(2*%pi*sqrt(L*C))  
9 disp('frequency='+string(f)+'hertz' , 'maximum crnt='+  
    string(I)+'amp')
```

---

#### Scilab code Exa 4.36 frequency response

```
1  
2 //calculate freq at resonance  
3 C=30*10^-6  
4 L=0.2  
5 R=12  
6 F= sqrt(1/(L*C)-R^2/(L*L))  
7 f=1/(2*3.14)*F  
8 disp(('freq at resonance='+string(f)+'hz'))
```

---

#### Scilab code Exa 4.37 current voltage and power

```
1
```

```

2 //determine the current also power nd power factor
3 V=200+%i*0
4 f=50
5 R1=30
6 L1=0.2
7 C1=10e-6
8 X1=2*%pi*f*L1
9 Z1=R1+%i*X1
10 R2=40
11 L2=0.12
12 X2=2*%pi*f*L2
13 Z2=R2+%i*X2
14 Z=(Z1*Z2)/(Z1+Z2)
15 I=V/Z
16 R=18.858 //calculating Z and I we get R and Z,I
17 Z=31.06
18 coso=R/Z
19 I=6.44
20 P=I^2*R
21 I1=(I*Z1)/(Z1+Z2)
22 I2=(I*Z1)/(Z1+Z2)
23 coso1=R1/Z1
24 P1=I1^2*R1
25 coso2=R2/Z2
26 P2=(I2)^2*R2
27 disp('P2 =' + string(P2) + ' watt' , 'P1 =' + string(P1) +
      ' watt' , 'Total power factr=' + string(coso) + ' '
      , 'Total power=' + string(P) + ' watt' , 'total
      current =' + string(I) + ' amps' , 'total impedance
      =' + string(Z) + ' ohms' )

```

---

Scilab code Exa 4.38 current and power

```

1
2 //determine the current also power nd power factor

```

```

3 V=200+%i*0
4 f=50
5 R1=10
6 X1=12
7 Z1=R1+%i*X1
8 R2=15
9 Xc2=20
10 Z2=R2-%i*Xc2
11 Z=(Z1*Z2)/(Z1+Z2)
12 I=V/Z//calculating Z and I we get R and Z,I
13 R=14.36
14 I=13.46
15 coso=R/Z
16 P=I*I*R
17 I1=(I*Z2)/(Z1+Z2)
18 I2=(I*Z1)/(Z1+Z2)
19 coso1=R1/Z1
20 P1=I1*I1*R1
21 coso2=R2/Z2
22 P2=I2*I2*R2
23 disp('P2 =' + string(P2) + ' watt' , 'P1 =' + string(P1) +
      ' watt' , 'Total power factr=' + string(coso) + ''
      , 'Total power=' + string(P) + ' watt' , 'total
      current =' + string(I) + ' amps' , 'total impedance
      Z =' + string(Z) + ' ohms' )

```

---

#### Scilab code Exa 4.40 voltage and current

```

1
2 //calculate the line currnt nd voltage
3 R=200
4 V1=440
5 f=50
6 V=V1/1.732//star connection
7 I=V/R

```



```

8 I1=I
9 coso=1
10 P=3*V*I*coso
11 Vp=440//delta connection
12 V1=440
13 I1=1.732*I
14 P1=3*Vp*I*coso
15 disp('active power='+string(P)+'watt' , 'active
      power='+string(P1)+'watt' )

```

---

#### Scilab code Exa 4.41 power absorbed

```

1
2 //calculate total power absrbed
3 R=15
4 L=0.25
5 f=50
6 X=2*%pi*f*L
7 Z=sqrt(R^2+X^2)
8 V1=400
9 V=V1/1.732 //in star connection
10 I=V/Z
11 I1=I
12 coso=R/Z
13 P=3*V*I1*coso
14 disp('total power absorbed='+string(P)+'watt')

```

---

#### Scilab code Exa 4.42 power absorbed

```

1
2 //calculate resistance nd reactance of circuit
3 P=15000; //power
4 V1=400; //line voltage

```

```

5 V=V1/1.732
6 I=35; //line current equal to phase current
7 Z=V/I
8 coso=15e3/(1.732*400*35)
9 R=Z*coso
10 X=sqrt(Z^2-R^2)
11 disp('reactance='+string(X)+'ohms' , 'resistance='+
      string(R)+'ohms')

```

---

#### Scilab code Exa 4.43 power factor

```

1
2 //calculate power factor
3 W1=5000 //W1=V*L*cos(30+o)
4 W2=3000 //W2=V*L*cos(30-o)
5 o=atand (1.732*(W1-W2)/(W1+W2))
6 disp('power factor='+string(o)+' ')

```

---

# Chapter 5

## Electrical Machine

Scilab code Exa 5.1 determine the emf induced in the coil

```
1
2 //P5.1 determine the induced emf in the armature
3 P=4; //poles
4 A=2; //wave wound
5 N=50; //number of slots
6 SperCondctr=24; //slots/conductor
7 Z=SperCondctr*N; //total conductor
8 N=600; //rpm.... speed of armature
9 F=10e-3; //webers.... flux/poles
10 E=F*Z*N*P/(60*A); //emf induced
11 disp('e.m.f induced is = '+string(E)+' volts');
```

---

Scilab code Exa 5.2 emf induced in coil

```
1
2 //P5.2 determine the induced emf in the armature
3 P=4; //poles
4 A=4; //wave wound
```

```

5 N=50; //number of slots
6 SperCondctr=24; //slots/conductor
7 Z=SperCondctr*N; //total conductor
8 N=600; //rpm.... speed of armature
9 F=10e-3; //webers .... flux/poles
10 E=F*Z*N*P/(60*A); //emf induced
11 disp('e.m.f induced is = '+string(E)+' volts');

```

---

### Scilab code Exa 5.3 speed

```

1
2 //determine the speed
3 P=6; //poles
4 A=2; //wave wound
5 Z=780; //armature conductors
6 F=12*10^-3; //webers .. flux/poles
7 E=400; //voltage
8 N=(E*60*2)/(F*Z*P);
9 N2=(E*60*6)/(F*Z*P);
10 disp('determine the speed='+string(N)+'rpm ',
       'determine the speed (A=P=6)='+string(N2)+'rpm ');

```

---

### Scilab code Exa 5.4 induced emf

```

1
2 //determine the emf induced
3 R=0.05;
4 Rs=100;
5 V=250;
6 P=10000;
7 I=P/V;
8 Is=V/Rs;
9 Ia=I+Is;

```

```
10 Eg=V+(R*Ia);
11 disp('emf induced='+string(Eg)+'volts');
```

---

#### Scilab code Exa 5.5 emf induced

```
1
2 //calculate the emf induced in the armature
3 I1=200
4 V1=500
5 Ra=0.03
6 Rs=0.015
7 R=150
8 BCD=2 //one volt per brush
9 I=V1/R
10 Ia=I1+I
11 Eg=V1+(Ia*Ra)+(Ia*Rs)+BCD
12 disp('emf induced=          '+string(Eg)+'          volts');
```

---

#### Scilab code Exa 5.6 emf induced

```
1
2 //calculate the emf induced in the armature
3 I1=200
4 V1=500
5 Ra=0.03
6 Rs=0.015
7 Is=200 //for a short shunt generator I1=Ise
8 R=150
9 BCD=2 //one volt per brush
10 I=(V1+(Is*Rs))/R
11 Ia=I1+I
12 Eg=V1+(Ia*Ra)+(Ia*Rs)+BCD
13 disp('emf induced=          '+string(Eg)+'          volts');
```

---

**Scilab code Exa 5.7** back emf

```
1
2 //calculate the back emf induced on full load
3 Ra=0.5 //armature resistance
4 Rs=250 //shunt resistance
5 V1=250 //line volt
6 I1=40
7 Is=V1/Rs
8 Ia=I1-Is
9 Eb=V1-(Ia*Ra)
10 disp('emf induced=' +string(Eb)+' volts' );
```

---

**Scilab code Exa 5.8** power

```
1
2 //find the power developed in circiut
3 P1=20e3
4 V1=200
5 Ra=0.05
6 R=150
7 I=V1/R
8 I1=P1/V1
9 Ia=I1+I
10 Eg=V1+(Ia*Ra)
11 P=Eg*Ia
12 disp('power developed=' +string(P)+' watt');
```

---

**Scilab code Exa 5.9** speed

```

1
2 //calculate the speed of the machine when running
3 N1=1000 //speed of generator
4 E1=205.06 //emf generator
5 E2=195.06 //emf of motor
6 N2=(E2*N1)/E1 //speed of generator
7 disp('speed of motor='+string(N2)+'rpm')

```

---

#### Scilab code Exa 5.10 speed of rotor

```

1
2 //dtermine its speed when its take crnt 25 amps
3 V1=250
4 Ra=0.05
5 R=0.02
6 Ia=30
7 I1=30 // I1=Ia
8 N1=400
9 E1=V1-(Ia*Ra)-(Ia*R)
10 //E1=E2
11 I2=25
12 N2=(N1*E1*I1)/(E1*I2)
13 disp('speed of motor='+string(N2)+'rpm')

```

---

#### Scilab code Exa 5.11 torque

```

1
2 //find the torque whn its take scurnt 60amprs
3 V1=200
4 I1=60 //amprs
5 R=50
6 I=V1/R // amprs
7 Ia=I1-I //amprs

```

```

8 f=0.03 // flux
9 Z=700
10 P=4
11 A=2
12 T=(0.159*f*Z*Ia*P)/A
13 disp('Torque='+string(T)+'N-m')

```

---

**Scilab code Exa 5.12** number of turns and current

```

1
2 //calcute the num of prim turns and prim $sec
   current
3 KVA=50
4 E1=6000
5 E2=250
6 N2=52
7 N1=N2*E1/E2
8 I2=KVA*1000/E2
9 I1=KVA*1000/E1
10 disp('prim current I1 = '+string(I1)+' amps' ,
      'sec current I2 = '+string(I2)+' amps' , '
      prim num of turns N1 = '+string(N1)+' turns'
      )

```

---

**Scilab code Exa 5.13** flux density

```

1
2 //determine the emf induced in the secondry max
   value of flux density
3 f=50
4 N1=350
5 N2=800
6 E1=400

```



```

7 E2=(N2*E1)/N1
8 A=75e-4
9 Bm=E1/(4.44*f*A*N1)
10 disp('flux density='+string(Bm)+'wb/m^2')

```

---

#### Scilab code Exa 5.14 current

```

1
2 //find the magnetic nd iron loss component of
   current
3 E1=440
4 E2=200
5 I=0.2
6 coso=0.18
7 sino=sqrt(1-coso^2)
8 Iw=I*coso
9 Iu=I*sino
10 disp('Iw='+string(Iw)+'amps' , 'Iu='+string(Iu)+'
   amprs')

```

---

#### Scilab code Exa 5.15 efficiency

```

1
2 //calculate teh efficiency at loads
3 KVA=20
4 I1=350
5 C1=400
6 x=1
7 pf=0.8//at full load
8 pf1=0.4 //at half load
9 x1=0.5
10 op=KVA*1000*x
11 op1=KVA*1000*x1*pf1

```

```

12 T1=I1+(C1*x*x)
13 T11=I1+(C1*x1*x1)
14 ip=op+T1
15 ip1=op1+T11
16 %n=op/ip*100
17 %n1=op1/ip1*100
18 disp('efficiency at half load n = '+string(%n1)+'
      ', 'efficiency at full load n1 = '+string(
      %n)+' ')

```

---

#### Scilab code Exa 5.16 speed and emf

```

1
2 //calculate the synchronous speed ,slip ,frequency
  induced emf
3 f=50
4 p=4
5 Ns=120*f/p
6 N=1460
7 s=(Ns-N)/Ns
8 f1=(s*f)
9 disp('f1='+string(f1)+'hz ', 's='+string(s)+' ',
      ', 'Ns='+string(Ns)+'rpm ')

```

---

#### Scilab code Exa 5.17 speed

```

1
2 //determine the value of slip and speed of motor
3 P=6
4 f=50
5 Ns=120*f/P
6 f1=1.5
7 s=f1/f

```

```
8 N=Ns*(1-s)
9 disp('speed of motor='+string(N)+'RPM')
```

---

#### Scilab code Exa 5.18 poles speed frequency

```
1
2 //calculate the numbers of poles ,slip at full load ,
   frequency rotor ,speed of motor
3 Ns=1000
4 N=960
5 f=50
6 P=120*f/Ns// synchronous speed
7 s=(Ns-N)/Ns
8 f1=s*f
9 N=Ns*(1-0.08)//speed of motor at 8% slip
10 disp('speed of rotor='+string(N)+'RPM')
```

---

#### Scilab code Exa 5.19 induced emf

```
1
2 //calculate the induced emf per phase
3 f=50
4 P=16
5 N=160
6 S=6
7 n=N*S
8 Z=n/3
9 F=0.025
10 e=2.22*F*f*Z
11 disp('e='+string(e)+'volts')
```

---