

Scilab Textbook Companion for  
Electronic Instrumentation and Measurements  
by J. B. Gupta<sup>1</sup>

Created by  
Sabiya  
B.Tech  
Electronics Engineering  
Uttarakhand Tech. University  
College Teacher  
Mohd. Rijwan  
Cross-Checked by  
Lavitha Pereira

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Electronic Instrumentation and Measurements

**Author:** J. B. Gupta

**Publisher:** S. K. Katariya & Sons, New Delhi

**Edition:** 3

**Year:** 2010

**ISBN:** 81-89757-30-x

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 Units Dimensions and Standards</b>	<b>5</b>
<b>2 Measurement Errors</b>	<b>6</b>
<b>3 PMMC Instruments</b>	<b>24</b>
<b>4 Digital Meters</b>	<b>39</b>
<b>5 Digital Meters</b>	<b>44</b>
<b>6 Resistance Measurements</b>	<b>54</b>
<b>7 Inductance And Capacitance Measurements</b>	<b>64</b>
<b>8 Cathode Ray Oscilloscopes</b>	<b>86</b>
<b>10 Instrument Calibration And Recorders</b>	<b>96</b>

# List of Scilab Codes

Exa 1.1	Unit of resistance capacitance and inductance	5
Exa 2.1	Absolute error of measurement . . . . .	6
Exa 2.2	Error and correction . . . . .	6
Exa 2.3	True value of power . . . . .	7
Exa 2.4	Relative Error . . . . .	7
Exa 2.5	Limit of inductance . . . . .	8
Exa 2.6	Limiting error . . . . .	8
Exa 2.7	Range of the reading . . . . .	8
Exa 2.8	Limiting error . . . . .	9
Exa 2.9	Limiting error . . . . .	10
Exa 2.10	Addition of resistance . . . . .	10
Exa 2.12	Power dissipated . . . . .	11
Exa 2.13	Limiting error and power dissipation . . . .	12
Exa 2.14	Resolution of instrument . . . . .	12
Exa 2.15	Limiting error of the resulting capacitance .	13
Exa 2.16	Uncertainly in the combined resistance . . .	13
Exa 2.17	Magnitude of the resultant resistance . . . .	14
Exa 2.18	Power and limiting error of power . . . . .	15
Exa 2.19	Nominal power consumed and limiting error of power . . . . .	16
Exa 2.20	Nominal value of unknown resistance . . . .	17
Exa 2.21	Relative error in power factor . . . . .	17
Exa 2.22	Magnitude of unknown inductance . . . . .	18
Exa 2.23	Uncertainly in the measurement of Z . . . .	19
Exa 2.24	Standard Deviation . . . . .	20
Exa 2.25	Mean standard deviation . . . . .	20
Exa 2.26	Arithmetic mean average deviation . . . . .	21
Exa 3.1	Torque developed by the each coil . . . . .	24

Exa 3.2	Deflection . . . . .	24
Exa 3.3	Deflection produced by the 300 V . . . . .	25
Exa 3.4	Angle through which the coil turns . . . . .	26
Exa 3.5	Number of turns . . . . .	26
Exa 3.6	Current in the coil . . . . .	27
Exa 3.7	Current sensitivity voltage sensitivity megohm sensitivity . . . . .	27
Exa 3.8	Value of the shunt resistance . . . . .	28
Exa 3.9	Current range of instrument . . . . .	29
Exa 3.10	Main circuit current . . . . .	29
Exa 3.11	Necessary value of resistors . . . . .	30
Exa 3.12	Three ranges of ammeter . . . . .	31
Exa 3.13	Shunt resistance required . . . . .	32
Exa 3.14	Estimate the resistance . . . . .	33
Exa 3.15	Applied voltage . . . . .	33
Exa 3.16	Additional resistance required . . . . .	34
Exa 3.17	Instrument indication . . . . .	35
Exa 3.18	New resistance value . . . . .	37
Exa 4.1	Meter current voltmeter input . . . . .	39
Exa 4.2	Meter circuit voltage . . . . .	40
Exa 5.2	Analog output voltage . . . . .	41
Exa 4.4	Suitable value of R <sub>1</sub> and R <sub>f</sub> . . . . .	42
Exa 4.5	Value of R <sub>1</sub> . . . . .	42
Exa 4.6	Value of R <sub>2</sub> and meter deflection . . . . .	43
Exa 5.1	Resolution and Full scale output . . . . .	44
Exa 5.2	Analog output voltage . . . . .	45
Exa 5.3	Resolution and full scale output . . . . .	45
Exa 5.4	Value of V <sub>x</sub> . . . . .	46
Exa 5.5	Conversion time . . . . .	47
Exa 5.6	Time of conversion . . . . .	48
Exa 5.7	Maximum time upto which the reference volt- age can be integrated . . . . .	48
Exa 5.8	Possible error in volt . . . . .	49
Exa 5.9	Resolution of voltmeter . . . . .	49
Exa 5.10	Resolution of the instrument . . . . .	50
Exa 5.11	Time taken to read the unknown voltage . .	51
Exa 5.12	Display indication . . . . .	51
Exa 5.13	Frequency of the system . . . . .	52

Exa 5.14	Resolution of measurement . . . . .	52
Exa 5.15	Frequency of input signal . . . . .	53
Exa 6.1	Apparent resistance of the unknown resistor	54
Exa 6.2	Resulting error . . . . .	55
Exa 6.3	Value of unknown resistance and limits of possible error . . . . .	56
Exa 6.4	Value of unknown resistance . . . . .	57
Exa 6.5	Value of unknown resistance . . . . .	57
Exa 6.6	Dials required . . . . .	58
Exa 6.7	Limiting values of unknown resistance . . .	58
Exa 6.8	Magnitude and direction of current . . . . .	59
Exa 6.9	Sensitivity of the bridge . . . . .	59
Exa 6.10	Ratio of galvanometer sensitivities . . . . .	60
Exa 6.11	Smallest change in resistance . . . . .	61
Exa 6.12	Series resistance . . . . .	62
Exa 6.13	Maximum value of resistance . . . . .	62
Exa 6.14	Unknown resistance . . . . .	63
Exa 7.1	Balance the bridge under condition . . . . .	64
Exa 7.2	Whether or not the bridge is complete balance	65
Exa 7.3	Range of measurements of unknown capacitance . . . . .	66
Exa 7.4	Dissipation Factor . . . . .	67
Exa 7.5	Phase angle errors and unknown capacitance	67
Exa 7.6	Values of C <sub>1</sub> and r <sub>1</sub> and dissipation factor .	68
Exa 7.7	Resistive and capacitive component of unknown capacitor and dissipaiton factor . . . . .	69
Exa 7.8	Power factor of the specimen . . . . .	69
Exa 7.9	Variable capacitor and resistor required . . .	70
Exa 7.10	Equivalent parallel resistance and capacitance	71
Exa 7.11	Values of C <sub>1</sub> and r <sub>1</sub> and dissipation factor .	72
Exa 7.12	Resistance and inductance of coil . . . . .	73
Exa 7.13	Resistance and inductance of coil . . . . .	73
Exa 7.14	Resistance and inductance of inductor . . . .	74
Exa 7.15	Resistance and inductance of unknown inductor . . . . .	74
Exa 7.16	Resistance and inductance of AB . . . . .	75
Exa 7.17	Resistance and inductance of unknown inductor . . . . .	75

Exa 7.18	Resistance and inductance at balance condition . . . . .	76
Exa 7.19	Value of R and C . . . . .	76
Exa 7.20	Series equivalent inductance and resistance . . . . .	77
Exa 7.21	Resistance and inductance of choke coil . . . . .	78
Exa 7.22	Effective impedance of the specimen . . . . .	78
Exa 7.23	Value of L and C . . . . .	79
Exa 7.24	Resistive and reactive component of unknown impedance . . . . .	80
Exa 7.25	Self capacitance and inductance of the coil . . . . .	80
Exa 7.26	Self capacitance of the coil . . . . .	81
Exa 7.27	Value of self capacitance . . . . .	81
Exa 7.28	Effective inductance and resistance of unknown coil . . . . .	82
Exa 7.29	Percentage error introduced in the calculated value of Q . . . . .	83
Exa 7.30	Self capacitance of the radio coil . . . . .	83
Exa 7.31	Self capacitance of the coil and true and indicated values of Q . . . . .	84
Exa 8.1	Deflection sensitivity . . . . .	86
Exa 8.2	Maximum velocity of electrons . . . . .	87
Exa 8.3	Deflection sensitivity . . . . .	87
Exa 8.4	Required voltage . . . . .	88
Exa 8.5	Required deflecting voltage . . . . .	88
Exa 8.6	Charging current and time period . . . . .	89
Exa 8.7	RMS value of unknown ac voltage . . . . .	89
Exa 8.8	Ratio of frequencies of vertical and horizontal signals . . . . .	90
Exa 8.9	Frequency of vertical signal . . . . .	90
Exa 8.10	Frequency of vertical signal . . . . .	91
Exa 8.11	Mark to space ratio . . . . .	91
Exa 8.12	Phase angle for each trace . . . . .	92
Exa 8.13	Pulse duration . . . . .	93
Exa 8.14	Peak to peak amplitude of the signal and signal frequency . . . . .	93
Exa 8.15	Value of C <sub>1</sub> and input capacitance . . . . .	94
Exa 8.16	Signal frequency . . . . .	94
Exa 8.17	Minimum time division . . . . .	95

Exa 10.1	Instrument accuracy . . . . .	96
Exa 10.2	Wattmeter error . . . . .	97

# Chapter 1

## Units Dimensions and Standards

Scilab code Exa 1.1 Unit of resistance capacitance and inductance

```
1 // Exa 1.1
2 clc;
3 clear;
4 close;
5 // Given data
6 V_desh= 100; // in V
7 I_desh= 10; // in amp
8 R_desh= V_desh/I_desh; // in
9 disp(R_desh,"New unit of resistance will be equal to
    ( in      ) is : ")
10 C_desh= I_desh/V_desh; // in F
11 disp(C_desh,"New unit of capacitance will be equal
    to (in Farad) is : ")
12 L_desh= V_desh/I_desh; // in L
13 disp(L_desh,"New unit of inductance will be equal to
    (in Henrys) is : ")

---


```

# Chapter 2

## Measurement Errors

Scilab code Exa 2.1 Absolute error of measurement

```
1 // Exa 2.1
2 clc;
3 clear;
4 close;
5 // Given data
6 Am= 10.25; // in ohm
7 A= 10.22; // in ohm
8 del_A= Am-A; // in ohm
9 disp(del_A ,” Absolute error in ohm”)
```

---

Scilab code Exa 2.2 Error and correction

```
1 // Exa 2.2
2 clc;
3 clear;
4 close;
5 // Given data
6 Am= 6.7; // in A
```

```
7 A= 6.54; // in A
8 del_A= Am-A; // in A
9 disp(del_A,"Absolute error in A")
10 disp(-del_A,"Correction in A")
```

---

### Scilab code Exa 2.3 True value of power

```
1 // Exa 2.3
2 clc;
3 clear;
4 close;
5 // Given data
6 Am= 25.34; // in watt
7 del_A= -0.11; // in watt
8 A= Am-del_A;
9 disp(A,"True value in watt")
```

---

### Scilab code Exa 2.4 Relative Error

```
1 // Exa 2.4
2 clc;
3 clear;
4 close;
5 // Given data
6 Am= 205.3*10^-6; // in F
7 A= 201.4*10^-6; // in F
8 epsilon_o= Am-A;
9 epsilon_r= epsilon_o/A*100; // in %
10 disp(epsilon_r,"Percentage relative error")
```

---

### Scilab code Exa 2.5 Limit of inductance

```
1 // Exa 2.5
2 clc;
3 clear;
4 close;
5 // Given data
6 PerError= 5; // in %
7 epsilon_r= PerError/100;
8 Am=20; // in H
9 del_A= Am*epsilon_r;
10 // A= Am+del_A and A= Am-del_A
11 disp("Limiting value of inductance is : "+string(Am)
      +" + "+string(del_A)+" to "+string(Am)+" - "+
      string(del_A)+" in Henry")
```

---

### Scilab code Exa 2.6 Limiting error

```
1 // Exa 2.6
2 clc;
3 clear;
4 close;
5 // Given data
6 V=600; // in volt
7 A= 400; //in volt
8 epsilon_r= 2.5/100;
9 del_V= epsilon_r*V;
10 PerLimitError= del_V/A*100; // in %
11 disp(PerLimitError,"The percentage limiting error at
        400 volt (in positive and negetive)");
```

---

### Scilab code Exa 2.7 Range of the reading

```

1 // Exa 2.7
2 clc;
3 clear;
4 close;
5 // Given data
6 Am= 500; // in watt
7 epsilon_r= 1.5/100; // in neg and pos
8 // for positive value of epsilon_r
9 A1= Am*(1+epsilon_r); // in watt
10 // for positive value of epsilon_r
11 A2= Am*(1-epsilon_r); // in watt
12 disp("Range of reading of wattmeter is "+string(A2)+"
    " watt to "+string(A1)+" watt")

```

---

### Scilab code Exa 2.8 Limiting error

```

1 // Exa 2.8
2 clc;
3 clear;
4 close;
5 // Given data
6 epsilon_r= 1.5/100; // in neg and pos
7 A= 10; // in amp
8 del_A= epsilon_r*A; // in amp
9 // The magnitude of current being measured is 2.5 A.
    The relative error at this current is
10 A= 2.5; // in amp
11 epsilon_r= del_A/A;
12 // Hence, the current under measurement is between
    the limits of
13 Am= 2.5; // in amp
14 // for positive value of epsilon_r
15 A1= Am*(1+epsilon_r); // in amp
16 // for positive value of epsilon_r
17 A2= Am*(1-epsilon_r); // in amp

```

```
18 disp("Limiting values of current under measurement  
      are "+string(A2)+" amp to "+string(A1)+" amp")  
19 LimitingError= del_A/A*100; // in %  
20 disp(LimitingError,"Limiting Error in %")
```

---

### Scilab code Exa 2.9 Limiting error

```
1 // Exa 2.9  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 epsilon_r= 1/100;  
7 P=1000; // in watt  
8 del_P= epsilon_r*P; // in watt  
9 // The magnitude of the power being measured is 100  
   watts.  
10 PerLimitError= del_P/100*100; // in %  
11 disp(PerLimitError,"The percentage limiting error at  
      1000 watt ")
```

---

### Scilab code Exa 2.10 Addition of resistance

```
1 // Exa 2.10  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 // For positive value of error  
7 R1= 100+100*2/100; // in ohm  
8 R2= 200+200*2.5/100; // in ohm  
9 AddR1R2_pos= R1+R2; // in ohm  
10 // For negative value of error
```

```
11 R1= 100-100*2/100; // in ohm
12 R2= 200-200*2.5/100; // in ohm
13 AddR1R2_neg= R1+R2; // in ohm
14 disp("Values of R1+R2 in ohm are "+string(
    AddR1R2_neg)+" ohm to "+string(AddR1R2_pos)+" ohm
")
```

---

### Scilab code Exa 2.12 Power dissipated

```
1 // Exa 2.12
2 clc;
3 clear;
4 close;
5 // Given data
6 AV= 110.2; // true value of voltage in volt
7 AI= 5.3; // true value of current in amp
8 v= 0.2; // uncertainties in voltage in volt
9 i= 0.6; // uncertainties in current in amp
10 PLV= v/AV*100; // percentage limiting error to
    voltage drop
11 PLC= i/AI*100; // percentage limiting error to
    current
12 P= AV*AI; // in watt
13 disp(P,"The power dissipated in the resistor in watt
")
14 LE_P= (PLV+PLC); // limiting error in the power
    dissipation in pos and neg
15 disp(LE_P,"The limiting error in the power
    dissipation with pos and neg")
16 disp("Power dissipation")
17 disp(string(P-P*LE_P/100)+" to "+string(P+P*LE_P
    /100))
```

---

### Scilab code Exa 2.13 Limiting error and power dissipation

```
1 // Exa 2.13
2 clc;
3 clear;
4 close;
5 // Given data
6 AR= 100; // true value of resistance in ohm
7 AI= 2; // true value of current in amp
8 R= 0.2; // uncertainties in resistance in ohm
9 I= 0.01; // uncertainties in current in amp
10 PLR= R/AR*100; // percentage limiting error to
    resistance
11 PLC= I/AI*100; // percentage limiting error to
    current
12 P=AI^2*AR; // in watt
13 LE_P= 2*PLC+PLR; // limiting error in the power
    dissipation
14 disp("Power dissipation")
15 disp(string(P-P*LE_P/100)+" to "+string(P+P*LE_P
    /100))
```

---

### Scilab code Exa 2.14 Resolution of instrument

```
1 // Exa 2.14
2 clc;
3 clear;
4 close;
5 // Given data
6 FullScaleReading= 200; // in V
7 N= 100; // Number of division of scale
8 SD= FullScaleReading/N; // 1 scale division
9 Resolution = 1/5*SD; // in v
10 disp(Resolution,"Resolution in volt")
```

---

**Scilab code Exa 2.15 Limiting error of the resulting capacitance**

```
1 // Exa 2.15
2 clc;
3 clear;
4 close;
5 // Given data
6 // u= 150+2.4 miu F and 150-2.4 miu F
7 // v= 120+1.5 miu F and 120-1.5 miu F
8 y=150+120;
9 del_y = 2.4+1.5; // Pos and neg
10 disp(del_y,"Limiting error with pos and neg in miu F
    ")
11 RelLimError= del_y/y*100;// in %
12 disp(RelLimError,"Relative limiting error with pos
    and neg");
```

---

**Scilab code Exa 2.16 Uncertainly in the combined resistance**

```
1 // Exa 2.16
2 clc;
3 clear;
4 close;
5 // Given data
6 R1= 1; //in kohm
7 R1=R1*10^3; //in ohm
8 del_R1ByR1= 1;
9 del_R2ByR2= 1;
10 R2= 500; //in kohm
11 R= R1*R2/(R1+R2); //in ohm
12 // Let R= X/Y
13 X= R1*R2;
```

```

14 Y=R1+R2;
15 ErrorX= del_R1ByR1+del_R2ByR2; // with pos and neg
16 // ErrorY= del_R1/Y + del_R2/Y = R1/Y*del_R1ByR1 +
    R2/Y*del_R2ByR2
17 ErrorY= R1/Y*del_R1ByR1 + R2/Y*del_R2ByR2; // with
    pos and neg
18 PerError= ErrorX+ErrorY; // in % with pos and neg
19 disp(PerError,"Percentage error (maximum possible) in
    equivalent parallel resistance with pos and neg"
    )
20 Error= 333.33*PerError/100;
21 Error=ceil(Error);
22 disp(Error,"Error (maximum possible) in equivalent
    parallel resistance in ohm")

```

---

### Scilab code Exa 2.17 Magnitude of the resultant resistance

```

1 // Exa 2.17
2 clc;
3 clear;
4 close;
5 // Given data
6 R1= 200; //in ohm
7 R2= 100; //in ohm
8 R3= 50; //in ohm
9 del_R1ByR1= 5;
10 del_R2ByR2= 5;
11 del_R3ByR3= 5;
12 // Part (i) when the resistance are connected in
    series
13 Rse= R1+R2+R3; // in ohm
14 disp(Rse,"Equivalent resistance when connected in
    series in ohm");
15 LimError= R1/Rse*del_R1ByR1 + R2/Rse*del_R2ByR2 + R3
    /Rse*del_R3ByR3;

```

```

16 disp(LimError,"Relative limiting error of series
      resistances in percentage (with pos and neg)") ;
17 LimError= Rse*LimError/100; //relative limiting error
      of series equivalent resistance in ohm
18 disp(LimError,"Relative limiting error of series
      equivalent resistance in ohm")
19
20 // Part(ii) when the resistance are connected in
      parallel
21 Rp= R1*R2*R3/(R1*R2+R2*R3+R3*R1);
22 disp(Rp,"Equivalent resistance when connected in
      parallel in ohm")
23 // Let Rp= X/Y
24 X= R1*R2*R3;
25 Y=R1*R2+R2*R3+R3*R1;
26 y1= R1*R2;
27 y2= R2*R3;
28 y3= R3*R1;
29 ErrorX= del_R1ByR1 + del_R2ByR2 + del_R3ByR3;
30 Errory1= del_R1ByR1 + del_R2ByR2 ;
31 Errory2= del_R2ByR2 + del_R3ByR3 ;
32 Errory3= del_R3ByR3 + del_R1ByR1 ;
33 Errory= [ y1/Y*Errory1 + y2/Y*Errory2 + y3/Y*Errory3
      ];
34 LimError= ErrorX+Errory;
35 disp(LimError,"Percentage error (maximum possible)
      in equivalent parallel resistance in percentage")
36 LimError= Rp*LimError/100;
37 disp(LimError,"Error (maximum possible) in
      equivalent parallel resistance in ohm")

```

---

### Scilab code Exa 2.18 Power and limiting error of power

```

1 // Exa 2.18
2 clc;

```

```

3 clear;
4 close;
5 // Given data
6 epsilon_r= 1.5/100;
7 V=100; // in volt
8 I=150; // in mA
9 del_V= epsilon_r*V; // in volt
10 Vm= 70; // magnitude of voltage being measured in
    volt
11 PerLimError_V= del_V/Vm*100; // in %
12 del_I= epsilon_r*I; // in mA
13 Im= 80; // in mA
14 PerLimError_C= del_I/Im*100; // in %
15 P= Vm*Im/1000; // in watt
16 RelLimError_P= (PerLimError_V+PerLimError_C); // in %
17 disp(RelLimError_P,"Relative limiting error in power
    measurement in percentage")

```

---

Scilab code Exa 2.19 Nominal power consumed and limiting error of power

```

1 // Exa 2.19
2 clc;
3 clear;
4 close;
5 // Given data
6 E= 200; // in V
7 del_E_by_E= 1;
8 R=1000; // in ohm
9 del_R_by_R= 5;
10 P=E^2/R; // in watt
11 disp(P,"Normal power consumed in watt")
12 LimError= 2*del_E_by_E+del_R_by_R; // in %
13 disp(LimError,"Relative limiting error in
    measurement of power in percentage")
14 LimError= LimError*P/100; // in watt

```

```
15 disp(LimError,"Limiting error of power in watt")
```

---

### Scilab code Exa 2.20 Nominal value of unknown resistance

```
1 // Exa 2.20
2 clc;
3 clear;
4 close;
5 // Given data
6 R1= 500; // in ohm
7 R2= 615; // in ohm
8 R3= 100; // in ohm
9 delR1ByR1= 1;
10 delR2ByR2= 1;
11 delR3ByR3= 0.5;
12 // Part(i)
13 R4=R1*R2/R3; // in ohm
14 disp(R4,"Unknown resistance in ohm")
15 delR4ByR4= delR1ByR1+delR2ByR2+delR3ByR3;
16 disp(delR4ByR4,"Relative limiting error of unknown
    resistance in percentage")
17 LimError= R4*delR4ByR4/100;
18 disp(LimError,"Limiting error in ohms");
```

---

### Scilab code Exa 2.21 Relative error in power factor

```
1 // Exa 2.21
2 clc;
3 clear;
4 close;
5 // Given data
6 del_PbyP=0.5;
7 del_CbyC=1;
```

```

8 del_VbyV=1;
9 del_PFbyPF=del_PbyP + del_CbyC + del_VbyV;
10 disp(del_PFbyPF," Relative limiting error in
    percentage (with pos and neg)")
```

---

### Scilab code Exa 2.22 Magnitude of unknown inductance

```

1 // Exa 2.22
2 clc;
3 clear;
4 close;
5 // Given data
6 C=1; // in miu F
7 C=C*10^-6; // in F
8 P=1000; // in ohm
9 Q=2000; // in ohm
10 r=200; // in ohm
11 S=2000; // in ohm
12 del_C_by_C= 1;
13 del_P_by_P= 0.4;
14 del_Q_by_Q= 1;
15 del_r_by_r= 0.5;
16 del_S_by_S= 0.5;
17 Lx= C*P/S*(r*(Q+S)+Q*S); // in Henry
18 disp(Lx,"Unknown inductance in Henry")
19 // Let
20 u=Q+S; // in ohm
21 Error_u= Q/u*del_Q_by_Q + S/u*del_S_by_S; // in %
22 // Let v= r*(Q+S) = r*u
23 v= r*(Q+S);
24 Error_v= del_r_by_r + Error_u; // in %
25 // Let
26 x=Q*S;
27 Error_x= del_Q_by_Q + del_S_by_S; // in %
28 // Let y= r*(Q+S)+Q*S = v+x
```

```

29 y=v+x;
30 Error_y= v/y*Error_v + x/y*Error_x; // in %
31 del_Lx_by_Lx= del_C_by_C + del_P_by_P + del_S_by_S +
    Error_y; // in %
32 disp(del_Lx_by_Lx ,”Percentage error in inductance”)

```

---

### Scilab code Exa 2.23 Uncertainly in the measurement of Z

```

1 // Exa 2.23
2 clc;
3 clear;
4 close;
5 // Given data
6 R=100; // in ohm
7 del_R_by_R= 5;
8 L=2; // in Henry
9 del_L_by_L= 10;
10 omega= 2*pi*50;
11 // Let
12 u=R^2;
13 Error_u= 2*del_R_by_R;
14 // Let
15 v= omega^2*L^2;
16 Error_v= 2*del_L_by_L;
17 // Let
18 x= u+v;
19 Error_x= u/x*Error_u + v/x*Error_v; // in %
20 // Now
21 Z= x^(1/2);
22 Error_Z= 1/2*Error_x;
23 disp(Error_Z ,”The uncertainly in the measurement of
    Z in percentage”)

```

---

### Scilab code Exa 2.24 Standard Deviation

```
1 // Exa 2.24
2 clc;
3 clear;
4 close;
5 // Given data
6 x1= 49.7;
7 x2= 50.1;
8 x3= 50.2;
9 x4= 49.6;
10 x5= 49.7;
11 n=5;
12 x_bar= (x1+x2+x3+x4+x5)/5;
13 d1= x1-x_bar;
14 d2= x2-x_bar;
15 d3= x3-x_bar;
16 d4= x4-x_bar;
17 d5= x5-x_bar;
18 s= sqrt((d1^2+d2^2+d3^2+d4^2+d5^2)/(n-1));
19 disp(s,"Standard deviation")
```

---

### Scilab code Exa 2.25 Mean standard deviation

```
1 // Exa 2.25
2 clc;
3 clear;
4 close;
5 // Given data
6 x1= 41.7;
7 x2= 42;
8 x3= 41.8;
9 x4= 42;
10 x5= 42.1;
11 x6= 41.9;
```

```

12 x7= 42.5;
13 x8= 42;
14 x9= 41.9;
15 x10=41.8;
16 n=10;
17 // ( i )
18 x_bar= (x1+x2+x3+x4+x5+x6+x7+x8+x9+x10)/10;
19 disp(x_bar ,”Arithmetic mean”)
20 d1= x1-x_bar;
21 d2= x2-x_bar;
22 d3= x3-x_bar;
23 d4= x4-x_bar;
24 d5= x5-x_bar;
25 d6= x6-x_bar;
26 d7= x7-x_bar;
27 d8= x8-x_bar;
28 d9= x9-x_bar;
29 d10= x10-x_bar;
30 // ( ii )
31 sigma= sqrt((d1^2+d2^2+d3^2+d4^2+d5^2+d6^2+d7^2+d8
    ^2+d9^2+d10^2)/(n-1));
32 disp(sigma ,”Standard deviation”);
33
34 // ( iii )
35 r= 0.6745*sigma;
36 disp(r ,”Probable error of one reading”)

```

---

### Scilab code Exa 2.26 Arithmetic mean average deviation

```

1 // Exa 2.26
2 clc;
3 clear;
4 close;
5 // Given data
6 x1= 1.570;

```

```

7 x2= 1.597;
8 x3= 1.591;
9 x4= 1.562;
10 x5= 1.577;
11 x6= 1.580;
12 x7= 1.564;
13 x8= 1.586;
14 x9= 1.550;
15 x10=1.575;
16 n=10;
17 // (i)
18 x_bar= (x1+x2+x3+x4+x5+x6+x7+x8+x9+x10)/10;
19 disp(x_bar,"Arithmetic mean in gramme")
20 d1= x1-x_bar;
21 d2= x2-x_bar;
22 d3= x3-x_bar;
23 d4= x4-x_bar;
24 d5= x5-x_bar;
25 d6= x6-x_bar;
26 d7= x7-x_bar;
27 d8= x8-x_bar;
28 d9= x9-x_bar;
29 d10= x10-x_bar;
30
31 // (ii)
32 D= (abs(d1)+abs(d2)+abs(d3)+abs(d4)+abs(d5)+abs(d6)+
      abs(d7)+abs(d8)+abs(d9)+abs(d10))/n; // in gramme
33 disp(D,"Average deviation in gramme")
34
35 // (iii)
36 sigma= sqrt((d1^2+d2^2+d3^2+d4^2+d5^2+d6^2+d7^2+d8
      ^2+d9^2+d10^2)/(n-1)); // in gramme
37 disp(sigma,"Standard deviation in gramme");
38
39 // (iv)
40 V= sigma^2; // variance in gramme^2
41 disp(V,"Variance in gramme^2");
42

```

```
43 // (v)
44 r= 0.6745*sigma; // in gramme
45 disp(r,"Probable error gramme")
46
47 // (vi)
48 rm= r/sqrt(n-1); // in gramme
49 disp(rm,"Probable error of mean in gramme")
```

---

# Chapter 3

## PMMC Instruments

Scilab code Exa 3.1 Torque developed by the each coil

```
1 // Exa 3.1
2 clc;
3 clear;
4 close;
5 // Given data
6 N= 100;
7 A=4*3; // in cm^2
8 A=A*10^-4; // in m^2
9 i=20; // in mA
10 i=i*10^-3; // in A
11 B=0.05; // in T
12 T=N*i*B*A; // in Nm
13 disp(T,"Torque developed by the coil in Nm")
```

---

Scilab code Exa 3.2 Deflection

```
1 // Exa 3.2
2 clc;
```

```
3 clear;
4 close;
5 // Given data
6 N= 125;
7 A=4*2.5; // in cm^2
8 A=A*10^-4; // in m^2
9 i=25; // in mA
10 i=i*10^-3; // in A
11 B=0.06; // in T
12 Td=N*i*B*A; // in Nm
13 Tc_BY_theta= 25*10^-7; // in Nm/
14 // Formula Tc=Td
15 theta= Td/Tc_BY_theta; // in
16 disp(theta,"Deflection in degree")
```

---

### Scilab code Exa 3.3 Deflection produced by the 300 V

```
1 // Exa 3.3
2 clc;
3 clear;
4 close;
5 // Given data
6 N= 100;
7 B=6*10^-2; // in Wb/m^2
8 A=3*4; // in cm^2
9 A=A*10^-4; // in m^2
10 V=300; // in volt
11 R=12000; // in ohm
12 i= V/R; // in amp
13 Td=N*i*B*A; // in Nm
14 Tc_BY_theta= 25*10^-7; // in Nm/
15 // Formula Tc=Td
16 theta= Td/Tc_BY_theta; // in
17 disp(theta,"Deflection in degree")
```

---

### Scilab code Exa 3.4 Angle through which the coil turns

```
1 // Exa 3.4
2 clc;
3 clear;
4 close;
5 // Given data
6 d= 42; // in mm
7 d=d*10^-3; // in meter
8 r= 0.6; // in meter
9 // Formula d= 2*theta*r
10 theta= d/(2*r); // radian
11 theta= 180*theta/%pi; // in
12 disp(round(theta),"Angle through which coil turn in
    ");
```

---

### Scilab code Exa 3.5 Number of turns

```
1 // Exa 3.5
2 clc;
3 clear;
4 close;
5 // Given data
6 B=1.8*10^-3; // in Wb/m^2
7 K= 1.4*10^-7; // in Nm/radian
8 theta= 90; // in
9 theta=theta*%pi/180;
10 Tc= K*theta; // in N-m
11 i=5; // in mA
12 i=i*10^-3; // in amp
13 A=1.5*1.2; // in cm^2
14 A=A*10^-4; // in m^2
```

```
15 // Formula Tc= Td= B*i*A*N;  
16 N= Tc/(B*i*A);  
17 N=ceil(N);  
18 disp(N,"Number of turns is")
```

---

### Scilab code Exa 3.6 Current in the coil

```
1 // Exa 3.6  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 B=0.1; // in T  
7 C= 100*10^-7; // in Nm/radian  
8 theta= 120; // in  
9 theta=theta*pi/180;  
10 Tc= C*theta; // in N-m  
11 N=200; // number of turns  
12 A=2.5*2; // in cm^2  
13 A=A*10^-4; // in m^2  
14 // Formula Tc= Td= B*i*A*N;  
15 i= Tc/(B*A*N); // in amp  
16 disp(i*10^3,"Current in the coil in mA")
```

---

### Scilab code Exa 3.7 Current sensitivity voltage sensitivity megohm sensitivity

```
1 // Exa 3.7  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 d=150; // in mm  
7 i=2.5; // in micro amp
```

```

8 R=200; // in ohm
9 V= R*i; // in micro volt
10 r=2.5; // in meter
11 // Part(i)
12 Si= d/i; // in mm/micro amp
13 disp(Si,"Current sensitivity in mm/micro amp")
14
15 // Part(ii)
16 Sv= d/V; // in mm/micro volt
17 disp(Sv,"Voltage sensitivity in mm/micro volt")
18
19 // Part(iii)
20 So= 1/(1/60*10^-6); // in ohm/mm
21 So=So*10^-6; // in Mohm
22 disp(So,"Megohm sensitivity in Mohm/mm")
23
24 // Part(iv)
25 i=5; // in micro amp
26 d=60*i; // in mm
27 d=d*10^-3; // in meter
28 theta=d/(2*r); // in radian
29 disp(theta,"Deflection in radians")

```

---

### Scilab code Exa 3.8 Value of the shunt resistance

```

1 // Exa 3.8
2 clc;
3 clear;
4 close;
5 // Given data
6 Im= 50*10^-6; // in amp
7 Rm= 1000; // in ohm
8 I=1; // in amp
9 Rs= Rm/(I/Im-1); // in ohm
10 disp(Rs,"Resistance of ammeter shunt required in ohm"

```

” )

---

### Scilab code Exa 3.9 Current range of instrument

```
1 // Exa 3.9
2 clc;
3 clear;
4 close;
5 // Given data
6 Rm= 1.0; // in ohm
7 Rse= 4999; // in ohm
8 V=250; // full scale deflection voltage in volt
9 // Formula V= Im*(Rm+Rse)
10 Im= V/(Rm+Rse); // in amp
11
12 // Part(a)
13 Rs= 1/4999; // in ohm
14 Is= Im*Rm/Rs; // in amp
15 I= Im+Is; // in amp
16 disp(I,"Current range in amp")
17
18 // Part(b)
19 I=50; // in amp
20 N=I/Im;
21 Rs= Rm/(N-1); // in ohm
22 disp(Rs,"Required shunt resistance in ohm")
```

---

### Scilab code Exa 3.10 Main circuit current

```
1 // Exa 3.10
2 clc;
3 clear;
4 close;
```

```

5 // Given data
6 Im= 50; // in micro amp
7 Im=Im*10^-6; // in amp
8 Rm= 49; // in ohm
9 Rs= 1; // in ohm
10 Is= Im*Rm/Rs; // in amp
11 I= Im+Is; // in amp
12 // (i)
13 I1= I; // in amp
14 I2= I*0.5; // in amp
15 I3= I*0.1; // in amp
16 disp(I1*10^3,"Main circuit current at FSD in mA")
17 disp(I2*10^3,"Main circuit current at 0.5 FSD in mA"
      )
18 disp(I3*10^3,"Main circuit current at 0.1 FSD in mA"
      )

```

---

### Scilab code Exa 3.11 Necessary value of resistors

```

1 // Exa 3.11
2 clc;
3 clear;
4 close;
5 // Given data
6 Rm= 40; // in ohm
7 Im= 1; // in mA
8 // For switch at position 1 (lowest range of 10 mA)
9 I=10; // in mA
10 N1= I/Im;
11 R1= Rm/(N1-1); // in ohm
12 // For switch at position 2 (range of 20 mA)
13 I=20; // in mA
14 N2= I/Im;
15 R2= (R1+Rm)/N2; // in ohm
16 // For switch at position 3 (range of 30 mA)

```

```

17 I=30; // in mA
18 N3= I/Im;
19 R3= (R1+Rm)/N3; // in ohm
20 // For switch at position 4 (range of 40 mA)
21 I=40; // in mA
22 N4= I/Im;
23 R4= (R1+Rm)/N4; // in ohm
24 // For switch at position 5 (range of 50 mA)
25 I=50; // in mA
26 N5= I/Im;
27 R5= (R1+Rm)/N5; // in ohm
28 r1= R1-R2; // in ohm
29 r2= R2-R3; // in ohm
30 r3= R3-R4; // in ohm
31 r4= R4-R5; // in ohm
32 r5= R5; // in ohm
33 disp("Resistance of the various sections of the
        Ayrtons shunt in ohm are: ")
34 disp(r1);
35 disp(r2);
36 disp(r3);
37 disp(r4);
38 disp(r5);

```

---

### Scilab code Exa 3.12 Three ranges of ammeter

```

1 // Exa 3.12
2 clc;
3 clear;
4 close;
5 // Given data
6 Rm= 1000; // in ohm
7 Im= 1; // in mA
8 Im=Im*10^-3; // in amp
9 r3=0.05; // in ohm

```

```

10 r2=0.45; // in ohm
11 r1=4.5; // in ohm
12 // For switch at contact 1
13 Rm1= Rm; // in ohm
14 Rs1= r1+r2+r3; // in ohm
15 I1= Im*(Rm1/Rs1+1); // in A
16 I1=I1*10^3; // in mA
17 I1=round((I1/10))*10;
18
19 disp(I1,"Ammeter range at contact 1 in mA")
20 // For switch at contact 2
21 Rm2= Rm+r1; // in ohm
22 Rs2= r2+r3; // in ohm
23 I2= Im*(Rm2/Rs2+1); // in A
24 I2=round(I2);
25 disp(I2,"Ammeter range at contact 2 in A")
26
27 // For switch at contact 3
28 Rm3= Rm+r1+r2; // in ohm
29 Rs3= r3; // in ohm
30 I3= Im*(Rm3/Rs3+1); // in A
31 I3=round(I3);
32 disp(I3,"Ammeter range at contact 3 in A")

```

---

### Scilab code Exa 3.13 Shunt resistance required

```

1 // Exa 3.13
2 clc;
3 clear;
4 close;
5 // Given data
6 Rm= 10; // in ohm
7 Im= 50; // in mA
8 Im=Im*10^-3; // in amp
9 V=750; // in volt

```

```

10 R= V/I_m-R_m; // in ohm
11 disp(R,"External resistance in ohm")
12 // Part(ii)
13 I=100; // in A
14 N=I/I_m;
15 R_s= R_m/(N-1); // in ohm
16 disp(R_s,"Shunt resistance required in ohm")

```

---

#### Scilab code Exa 3.14 Estimate the resistance

```

1 // Exa 3.14
2 clc;
3 clear;
4 close;
5 // Given data
6 T_c= 120*10^-6; // in N-m
7 B= 0.5; // in wb/m^2
8 N=100;
9 A= 4*3; // in cm^2
10 A=A*10^-4 // in m^2
11 R_m=0;
12 V= 100*1;
13 // Formula T_c= T_d = B*I*N*A
14 I= T_c/(B*N*A); // in amp
15 R= V/I-R_m; // in ohm
16 disp(R,"External required resistance in ohm")

```

---

#### Scilab code Exa 3.15 Applied voltage

```

1 // Exa 3.15
2 clc;
3 clear;
4 close;

```

```

5 // Given data
6 Im= 0.2*10^-3; // in amp
7 Rm= 10; // in ohm
8 V=100; // in volt
9 R= V/Im-Rm; // in ohm
10 disp(R*10^-3,"External required resistance in kohm")
11 Im1= 0.75*Im; //in amp
12 V1= Im1*(R+Rm); // in volt
13 disp(V1,"Applied voltage at instrument current 0.75
    FSD in volt");
14
15 Im2= 0.5*Im; //in amp
16 V2= Im2*(R+Rm); // in volt
17 disp(V2,"Applied voltage at instrument current 0.5
    FSD in volt");
18
19 Im3= 0.25*Im; //in amp
20 V3= Im3*(R+Rm); // in volt
21 disp(V3,"Applied voltage at instrument current 0.25
    FSD in volt");
22
23 Im4= 0.1*Im; //in amp
24 V4= Im4*(R+Rm); // in volt
25 disp(V4,"Applied voltage at instrument current 0.1
    FSD in volt");

```

---

### Scilab code Exa 3.16 Additional resistance required

```

1 // Exa 3.16
2 clc;
3 clear;
4 close;
5 // Given data
6 CS= 0.1*10^-3; // current sensitivity in amp
7 VS= 1/CS; // voltage sensitivity in ohm/volt

```

```

8 VS= VS*10^-3; // in kohm/volt
9 Rm=500; // in ohm
10 Rm=Rm*10^-3; // in kohm
11
12 // (i) 0-10 V range
13 V=10; // full scale delection voltage in volt
14 R_T= VS*V; // in kohm
15 R1= R_T-Rm; // in kohm
16 disp(R1,"Additional required resistance at 0-10 V
range in kohm")
17
18 // (ii) 0-50 V range
19 V=50; // full scale delection voltage in volt
20 R_T= VS*V; // in kohm
21 R2= R_T-R1-Rm; // in kohm
22 disp(R2,"Additional required resistance at 0-50 V
range in kohm")
23
24 // (i) 0-100 V range
25 V=100; // full scale delection voltage in volt
26 R_T= VS*V; // in kohm
27 R3= R_T-R1-R2-Rm; // in kohm
28 disp(R3,"Additional required resistance at 0-100 V
range in kohm")
29
30 // (i) 0-500 V range
31 V=500; // full scale delection voltage in volt
32 R_T= VS*V; // in kohm
33 R4= R_T-R1-R2-R3-Rm; // in kohm
34 disp(R4,"Additional required resistance at 0-500 V
range in kohm")

```

---

### Scilab code Exa 3.17 Instrument indication

```
1 // Exa 3.17
```

```

2 clc;
3 clear;
4 close;
5 // Given data
6 E= 1.5; // in V
7 R1addRm= 10; // addition of R1 and Rm in kohm
8 Rx= 0;
9 R=R1addRm+Rx; // in kohm
10 R=R*10^3; // in ohm
11 I= E/R; //meter FSD current in amp
12
13 // At 0.8 FSD
14 Im= 0.8*I; // in amp
15 R= E/Im; // in ohm
16 R=R*10^-3; // in kohm
17 Rx= R-R1addRm; // in kohm
18 disp(Rx,"Unknown resistance at 0.8 FSD in k ")
19
20 // At 0.5 FSD
21 Im= 0.5*I; // in amp
22 R= E/Im; // in ohm
23 R=R*10^-3; // in kohm
24 Rx= R-R1addRm; // in kohm
25 disp(Rx,"Unknown resistance at 0.5 FSD in k ")
26
27 // At 0.25 FSD
28 Im= 0.25*I; // in amp
29 R= E/Im; // in ohm
30 R=R*10^-3; // in kohm
31 Rx= R-R1addRm; // in kohm
32 disp(Rx,"Unknown resistance at 0.25 FSD in k ")
33
34 // At 0.1 FSD
35 Im= 0.1*I; // in amp
36 R= E/Im; // in ohm
37 R=R*10^-3; // in kohm
38 Rx= R-R1addRm; // in kohm
39 disp(Rx,"Unknown resistance at 0.1 FSD in k ")

```

---

### Scilab code Exa 3.18 New resistance value

```
1 // Exa 3.18
2 clc;
3 clear;
4 close;
5 // Given data
6 Rm= 50; // in ohm
7 R1= 10; // in kohm
8 R1=R1*10^3; // in ohm
9 R2= 50; // in ohm
10 Im_FSD= 100*10^-6; // meter FSD current in amp
11
12 // At 0.5 FSD , with 1.5 V
13 E=1.5; // in volt
14 Im= 0.5*Im_FSD; // in amp
15Vm= Im*Rm; // in volt
16 I0= Vm/R2; // in amp
17 I=I0+Im; // in amp
18 Rx= E/I-R1; // in ohm
19 Rx=Rx*10^-3; // in kohm
20 disp(Rx,"Unknown resistance at 0.5 FSD with 1.5 V in
kohm")
21 // With E= 1.25 V and Rx=0
22 E=1.25; // in volt
23 Rx=0;
24 I=E/(R1+Rx); // in amp
25 I0=I-Im_FSD; // in amp
26 Vm= Im_FSD*Rm; // in volt
27 R2= Vm/I0; // in ohm
28 disp(R2,"Zero adjuster resistance in ohm")
29
30 // At 0.5 FSD , with 1.25 V
31 E=1.25; // in volt
```

```
32 Im= 0.5*Im_FSD; // in amp
33 Vm= Im*Rm; // in volt
34 I0= Vm/R2; //in amp
35 I=I0+Im; // in amp
36 Rx= E/I-R1; // in ohm
37 Rx=Rx*10^-3; //in kohm
38 disp(Rx,"Unknown resistance at 0.5 FSD with 1.25 V
in kohm")
```

---

# Chapter 4

## Digital Meters

Scilab code Exa 4.1 Meter current voltmeter inpur

```
1 // Exa 4.1
2 clc;
3 clear;
4 close;
5 // Given data
6 V_CC= 12; // in volt
7 V_BE=0.7; //in volt
8 Rsm=4.3; //value o Rs+Rm in kohm
9 I=1; //in mA
10
11 // Part (i)
12 V= 5; //in volt
13 V_E= V-V_BE; // in volt
14 Im= V_E/Rsm; // in mA
15 I_E=Im; // in mA
16 disp(Im,"Meter Current in mA")
17
18 // Part(ii)
19 h_FE= 100;
20 Im=Im*10^-3; //in amp
21 I_B= Im/h_FE; // in amp
```

```

22 Rin= V/I_B; // in ohm
23 disp(Rin*10^-3,"Input resistance with transistor in
      kohm")
24 // without transistor
25 Rin= Rsm;
26 disp(Rin,"Input resistance without transistor in
      kohm")
27
28 // Part(iii)
29 V=2.5; // in volt
30 V_E= V-V_BE; // in volt
31 I_m= V_E/Rsm; // in mA
32 I_E=I_m; // in mA
33 disp(I_m,"Meter current when the dc input voltage is
      2.5 volt in mA")

```

---

### Scilab code Exa 4.2 Meter circuit voltage

```

1 // Exa 4.2
2 clc;
3 clear;
4 close;
5 // Given data
6 V_CC= 12; // in volt
7 V_BE=0.7; // in volt
8 R_E1=3.3; // in kohm
9 V_EE= -12; // in volt
10 // Part (a) when V=0
11 V= 0; // in volt
12 V_E1= V-V_BE-V_EE; // in volt
13 I_E1= V_E1/R_E1; // in mA
14 disp(I_E1,"emitter current when input voltage is
      zero volt , in mA")
15
16 // Part (b)

```

```

17 // Part (i) when V=2 volt
18 V= 2; //in volt
19 V_P=0;
20 V_E1= V-V_BE; // in volt
21 V_E2= V_P-V_BE; // in volt
22 Vm= V_E1-V_E2; // in volt
23 disp(Vm,"Meter circuit voltage when input voltage is
2 volt , in volt")
24
25 // Part (ii) when V=1 volt
26 V= 1; //in volt
27 V_P=0;
28 V_E1= V-V_BE; // in volt
29 V_E2= V_P-V_BE; // in volt
30 Vm= V_E1-V_E2; // in volt
31 disp(Vm,"Meter circuit voltage when input voltage is
1 volt , in volt")

```

---

### Scilab code Exa 5.2 Analog output voltage

```

1 // Exa 5.2
2 clc;
3 clear;
4 close;
5 // Given data
6 V_REF= -5; // in volt
7 V_A= -5; // in volt
8 V_C=V_A; // in volt
9 V_D=V_C; // in volt
10 V_B= 0;
11 Vout= -1*(V_A+V_B/2+V_C/4+V_D/8);
12 disp(Vout,"Output voltage in volt");

```

---

### Scilab code Exa 4.4 Suitable value of R1 and Rf

```
1 // Exa 4.4
2 clc;
3 clear;
4 close;
5 // Given data
6 Im= 200; // in micro A
7 Im=Im*10^-6; // in amp
8 Rm= 5; // in kohm
9 Rm=Rm*10^3; // in ohm
10 I_B= 0.5; // in micro amp
11 I_B=I_B*10^-6; // in amp
12 V=25; // in mV
13 V=V*10^-3; // in volt
14 Vout= Im*Rm; // in volt
15 I= 500*I_B; // in amp
16 R1= V/I; // in ohm
17 disp(R1,"Resistor in ohm")
18 Rf= (Vout-V)/I; // in ohm
19 disp(Rf*10^-3,"Feedback resistor in kohm")
```

---

### Scilab code Exa 4.5 Value of R1

```
1 // Exa 4.5
2 clc;
3 clear;
4 close;
5 // Given data
6 Im= 1; // in mA
7 Im=Im*10^-3; // in amp
8 Rm= 100; // in ohm
9 V=1.2; // in volt
10 R1= V/Im; // in ohm
11 disp(R1*10^-3,"Resistance in kohm")
```

```
12 Vout= Im*(Rm+R1); // in volt
13 disp(Vout ,”Output voltage in volt”)
```

---

### Scilab code Exa 4.6 Value of R2 and meter deflection

```
1 // Exa 4.6
2 clc;
3 clear;
4 close;
5 // Given data
6 Vrms=120; // in mV
7 Iav= 1.25; // in mA
8 I_max= 1/0.318*Iav; // in mA
9 Vmax= sqrt(2)*Vrms; // in mV
10 R2= Vmax/I_max; // in ohm
11 disp(R2 ,”Value of R2 in ohm”)
12 // when input voltage is 60 volt
13 Vrms=60; // in mV
14 Vmax= sqrt(2)*Vrms; // in mV
15 I_max= Vmax/R2; // in mA
16 Iav= I_max*0.318; // in mA
17 disp(Iav ,”Average value of meter current in mA”)
```

---

# Chapter 5

## Digital Meters

Scilab code Exa 5.1 Resolution and Full scale output

```
1 // Exa 5.1
2 clc;
3 clear;
4 close;
5 // Given data
6 V_REF= 10; // in volt
7 w2= V_REF/2; // The second MSB weight in volt
8 disp(w2,"The second MSB weight in volt")
9 w3= V_REF/4; // The third MSB weight in volt
10 disp(w3,"The third MSB weight in volt")
11 w4= V_REF/8; // The forth MSB weight in volt
12 disp(w4,"The forth MSB weight in volt")
13
14 // (i)
15 r_DAC= w4; // resolution of the DAC in volt
16 disp(r_DAC,"Resolutio of the DAC in volt");
17
18 //(ii)
19 FSO= V_REF+w2+w3+w4; //full scale output in volt
20 disp(FSO," Full scale output in volt")
21
```

```
22 // (iii)
23 FSO_R= FSO/4; // full scale output when the feedback
    resistor is made one fourth of R in volt
24 disp(FSO_R ,”The full scale output when the feedback
    resistor is made one fourth of R i volt”)
```

---

### Scilab code Exa 5.2 Analog output voltage

```
1 // Exa 5.2
2 clc;
3 clear;
4 close;
5 // Given data
6 V_REF= -5; // in volt
7 V_A= -5; // in volt
8 V_C=V_A; // in volt
9 V_D=V_C; // in volt
10 V_B= 0;
11 Vout= -1*(V_A+V_B/2+V_C/4+V_D/8);
12 disp(Vout ,”Output voltage in volt”);
```

---

### Scilab code Exa 5.3 Resolution and full scale output

```
1 // Exa 5.3
2 clc;
3 clear;
4 close;
5 // Given data
6 D=16;
7 D1= D/2; // first MSB output in volt
8 disp(D1 ,”First MSB output in volt”);
9 D2= D/4; // second MSB output in volt
10 disp(D2 ,”Second MSB output in volt”);
```

```

11 D3= D/8;// third MSB output in volt
12 disp(D3,"Third MSB output in volt");
13 D4= D/16;// fourth MSB output in volt
14 disp(D4,"Fourth MSB output in volt");
15 D5= D/32;// fifth MSB output in volt
16 disp(D5,"Fifth MSB output in volt");
17 D6= D/64;// sixth MSB (LSB) output in volt
18 disp(D6,"Sixth MSB (LSB) output in volt");
19 disp(D6,"The resolution is equal to the weight of
the LSB in volt . ")
20 // Full scale output occurs for a digital input of
111111
21 FSO= D1+D2+D3+D4+D5+D6;// in volt
22 disp(FSO,"Full scale output occurs for a digital
input of 111111 in volt")
23 // The output voltage for a digital input of 101011
24 D0=16;
25 D1=16;
26 D2=0;
27 D3=16;
28 D4=0;
29 D5=16;
30 Vout= ( D0*2^0 + D1*2^1 + D2*2^2 + D3*2^3 + D4*2^4 +
D5*2^5 )/64;// in volt
31 disp(Vout,"The output voltage for digital input of
101011 in volt")

```

---

#### Scilab code Exa 5.4 Value of Vx

```

1 // Exa 5.4
2 clc;
3 clear;
4 close;
5 // Given data
6 R=100;// in kohm

```

```

7 R=R*10^3; //in ohm
8 C=1*10^-6; // in F
9 V_REF= 5; // in volt
10 t=0.2; // time taken to read unknown voltage in sec
11 T=R*C; // in sec
12 Vx= T/t*V_REF; // in volt
13 disp(Vx,"Unknown voltage in volt")

```

---

### Scilab code Exa 5.5 Conversion time

```

1 // Exa 5.5
2 clc;
3 clear;
4 close;
5 // Given data
6 // For an 8-bit converter reference voltage V_REF be
    taken as 100 V
7 V_REF= 100; // in volt
8 f=75*10^6; // in Hz
9 // For setting
10 D7=1;
11 Vout1= V_REF*2^7/2^8; // in volt
12 disp(Vout1,"Output voltage in volt")
13 // since 180-100 = 80 > 50; set D7=1
14
15 // For setting
16 D6=1;
17 Vout2= V_REF*2^6/2^8; // in volt
18 disp(Vout2,"Output voltage in volt")
19 // Hence for setting D7=1 and D6=1 output voltage
20 Vout3= Vout1+Vout2; // in volt
21 disp(Vout3,"Output voltage in volt")
22 // since 80>75; set D6=1
23 // For setting D5=1, D6=1 and D7=1
24 Vout4 = V_REF*2^5/2^8 + Vout1+ Vout2; // in volt

```

```
25 disp(Vout4,"Output voltage in volt")
26 disp(" All other digits will be set to zero or 1.
        Output will be accordingly indicated as a result
        of successive approximation. The Converted 8-bit
        digital form will be 1110010")
27 T=1/f; //in sec
28 disp(T*10^9,"Conversion time in ns")
```

---

### Scilab code Exa 5.6 Time of conversion

```
1 // Exa 5.6
2 clc;
3 clear;
4 close;
5 // Given data
6 N=8; // Number of bits
7 f=1*10^6; // in Hz
8 T=1/f;
9 Tc= N*T; // in second
10 disp(Tc*10^6,"Time of conversion in micro second")
```

---

### Scilab code Exa 5.7 Maximum time upto which the reference voltage can be integrated

```
1 // Exa 5.7
2 clc;
3 clear;
4 close;
5 // Given data
6 Vin= 2; // in volt
7 Vout= 10; // in volt
8 R=100; // kohm
9 R=R*10^3; // in ohm
10 C= 0.1; // in miu F
```

```

11 C=C*10^-6; // in F
12 // Vout= -1/(R*C)*integrate( 'Vin' , 't' ,0 ,t) = -Vin*t
   /(R*C)
13 t= Vout*R*C/Vin; // in sec
14 disp(t*10^3,"The maximum time upto which the
   reference voltage can be integrated in ms");

```

---

### Scilab code Exa 5.8 Possible error in volt

```

1 // Exa 5.8
2 clc;
3 clear;
4 close;
5 // Given data
6 n=3;
7 R=1/10^n;
8 fs1=1; // full scale range of 1 v
9 r1= fs1*R; // resolution for full scale range of 1 V
10 disp(r1,"Resolution for full scale range of 1 V")
11 fs2=10; // full scale range of 10 v
12 r2= fs2*R; // resolution for full scale range of 10 V
13 disp(r2,"Resolution for full scale range of 10 V")
14 // The display for 2 V reading on 10 V scale of
   3*1/2 digital meter would be 02.00 i.e
15 reading=2;
16 LSD= 5*R; // in volt
17 Total_pos_Error= reading*0.5/100+LSD; //in volt
18 disp(Total_pos_Error,"Total possible error in volt")

```

---

### Scilab code Exa 5.9 Resolution of voltmeter

```

1 // Exa 5.9
2 clc;

```

```

3 clear;
4 close;
5 // Given data
6 R= 1/10^4; // resolution
7 disp(R,"Resolution of voltmeter is : ")
8 reading1= 16.58;
9 reading2= 0.7254;
10 disp("There are 5 digit places in 4 display , so "+  

     string(reading1)+" would be displayed as 16.580 V  

     on a 10V range ")
11 disp(reading2,"Any reading up to 4th decimal can be  

     displayed . Hence "+string(reading2)+" will be  

     displayed as ")
12 R= 10*R;// resolution on 10 V range
13 format('v',6);
14 disp("Resolution of 10 V range is "+string(R)+" So")
15 disp(reading2,"0.7254 will be displayed as ")

```

---

### Scilab code Exa 5.10 Resolution of the instrument

```

1 // Exa 5.10
2 clc;
3 clear;
4 close;
5 // Given data
6 n=3;
7 R=1/10^n;
8 fs1=10; // full scale range of 10 v
9 r1= fs1*R;// resolution for full scale range of 10 V
10 disp(r1,"Resolution for full scale range of 10 V")
11 fs2=100;// full scale range of 100 v
12 r2= fs2*R;// resolution for full scale range of 100  

   V
13 disp(r2,"Resolution for full scale range of 100 V")
14 disp("The display of 14.53 V reading on 10 V scale

```

```
would be 14.53")
15 disp("The display of 14.53 V reading on 100 V scale
      would be 0145.3")
```

---

### Scilab code Exa 5.11 Time taken to read the unknown voltage

```
1 // Exa 5.11
2 clc;
3 clear;
4 close;
5 // Given data
6 Vmax= 255; // in volt
7 Vx= 180; // in volt
8 f=10; // in kHz
9 f=f*10^3; // in Hz
10 t= (Vmax-Vx)/(2*pi*f*Vmax); // time taken to read
      the unknown voltage in second
11 t=t*10^6; // in micro second
12 disp(t,"Time taken to read the unknown voltage in
      micro second");
```

---

### Scilab code Exa 5.12 Display indication

```
1 // Exa 5.12
2 clc;
3 clear;
4 close;
5 // Given data
6 f=2.5; // in kHz
7 f=f*10^3; // in Hz
8 // Part (i) when
9 t=0.1; // in sec
10 count= f*t;
```

```
11 disp(count,"When GATE ENABLE time is 0.1 sec then  
    the counter will count or display")  
12 // Part (ii) when  
13 t=1; // in sec  
14 count= f*t;  
15 disp(count,"When GATE ENABLE time is 1 sec then the  
    counter will count or display")  
16 // Part (iii) when  
17 t=10; // in sec  
18 count= f*t;  
19 disp(count,"When GATE ENABLE time is 10 sec then the  
    counter will count")
```

---

#### Scilab code Exa 5.13 Frequency of the system

```
1 // Exa 5.13  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 N=045; // unit less  
7 t=10; // in ms  
8 t=t*10^-3; // in sec  
9 f=N/t; // Hz  
10 f=f*10^-3; // in kHz  
11 disp(f,"Frequency in kHz")
```

---

#### Scilab code Exa 5.14 Resolution of measurement

```
1 // Exa 5.14  
2 clc;  
3 clear;  
4 close;
```

```
5 // Given data
6 totalPulse= 174; // unit less
7 t=100; //time period of total pulses in miu s
8 t=t*10^-6; // in sec
9 t1= t/totalPulse; // time period of one pulse in sec
10 f= 1/t1; // frequency in Hz
11 f=f*10^-6; // in MHz
12 disp(f,"Frequency in MHz");
13 resolution= totalPulse/t; // in sec
14 resolution=resolution*10^-6; // per micro sec
15 disp(resolution,"Resolution of measurement per micro
sec")
```

---

### Scilab code Exa 5.15 Frequency of input signal

```
1 // Exa 5.15
2 clc;
3 clear;
4 close;
5 // Given data
6 t=1/(2*10^6); // time of one cycle o 2MHz clock in
sec
7 N=500; // number of cycle
8 t1= N*t; // time of 1 cycle by the electronic counter
in sec
9 f= 1/t1; // in Hz
10 f=f*10^-3; // in kHz
11 disp(f,"Frequency of input signal in kHz")
```

---

# Chapter 6

## Resistance Measurements

Scilab code Exa 6.1 Apparant resistance of the unknown resistor

```
1 // Exa 6.1
2 clc;
3 clear;
4 close;
5 // Given data
6 V= 100; // in volt
7 I=5; // in mA
8 I=I*10^-3; // in amp
9 VS= 1000; // sensitivity of voltmeter in ohm
10 VR= 150; // voltmeter range in volt
11 Rv= VS*VR; // in ohm
12 // Part (i)
13 Rm= V/I; // in ohm
14 Rm= Rm*10^-3; // in kohm
15 disp(Rm,"Apparent value of unknown resistor in kohm")
);
16
17 // Part (ii)
18 Rx= V/(I*(1-V/(I*Rv))); // in ohm
19 Rx= Rx*10^-3; // in kohm
20 disp(Rx,"Actual value of unknown resistor in kohm")
```

```

21
22 // Part (iii)
23 epsilon_r= (Rm-Rx)/Rx*100; // in %
24 disp(epsilon_r,"Error percentage due to loading
    effect of voltmeter");

```

---

### Scilab code Exa 6.2 Resulting error

```

1 // Exa 6.2
2 clc;
3 clear;
4 close;
5 // Given data
6 V=38.4; // in volt
7 I=0.4; // in amp
8 ammeterRange= 1; // in amp
9 voltmeterRange= 50; // in volt
10 inst_acc= 1/2; // instrument accuracy in %
11 R= 100; // resistance in ohm
12
13 R_A= 2.5; // in ohm
14 R_V= 6000; // in ohm
15 Rx= sqrt(R_A*R_V); // in ohm
16 disp(Rx,"Value of unknown resistance in ohm")
17 disp("Since the unknown resistance is of value
        smaller than "+string(Rx)+" ohm, the voltmeter
        should be connected directly across the unknown
        resistance as it will give more accurate result")
18 Rm= V/I; // in ohm
19 Rx= V/(I*(1-V/(I*R_V))); // in ohm
20 ErrorAmmeter= inst_acc*ammeterRange/R; // Error in
    ammeter reading in amp
21 ErrorVoltmeter= inst_acc*voltmeterRange/R; // Error
    in voltmeter reading in volt
22 // Percentage error at 0.4 A reading

```

```

23 E1= ErrorAmmeter/0.4*100;//in %
24 // Percentage error at 38.4 V reading
25 E2= ErrorVoltmeter/38.4*100;//in %
26 //Error due to ammeter and voltmeter
27 E= sqrt(E1^2+E2^2);
28 //Absolute error due to ammeter and voltmeter
29 Error_ammeter_voltmeter= E/R*Rx;// in pos and neg
30 disp(Error_ammeter_voltmeter,"Absolute error due to
ammeter and voltmeter in ohm")
31 disp("So the resistance is specified as "+string(Rx-
Error_ammeter_voltmeter)+" to "+string(Rx+
Error_ammeter_voltmeter));

```

---

**Scilab code Exa 6.3 Value of unknown resistance and limits of possible error**

```

1 // Exa 6.3
2 clc;
3 clear;
4 close;
5 // Given data
6 V=120;// in volt
7 I=8;// in amp
8 R_A= 0.3;// in ohm
9 ammeterReading= 0.01;// in A
10 voltmeterReading= 0.1;// in V
11 AmmeterRange= 10;//in A
12 VoltmeterRange= 150;//in V
13 EA= 0.25;// constructional error of the ammeter in %
14 EV= 0.5;// constructional error of the voltmeter in
%
15
16 Rm= V/I;// in ohm
17 Rx= Rm-R_A;// in ohm
18 ErrorAmmeter= ammeterReading/AmmeterRange*100;// in
%
```

```
19 ErrorVoltmeter= voltmeterReading/VoltmeterRange*100;  
    // in %  
20 del_I= ErrorAmmeter+EA; // in %  
21 del_V= ErrorVoltmeter+EV; // in %  
22 // since R=V/I  
23 TotalError= del_I+del_V; // in % in neg and pos  
24 disp(TotalError,"Total systematic error in  
measurement in % (neg and pos)")  
25 disp("So the value of Rx is specified as "+string(Rx  
-Rx*TotalError/100)+" ohm to "+string(Rx+Rx*  
TotalError/100)+" ohm")
```

---

#### Scilab code Exa 6.4 Value of unknown resistance

```
1 // Exa 6.4  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 P=100; // in ohm  
7 Q=10; // in ohm  
8 S=46; // in ohm  
9 R= P*S/Q; // in ohm  
10 disp(R,"Unknown resistance in ohm")
```

---

#### Scilab code Exa 6.5 Value of unknown resistance

```
1 // Exa 6.5  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 S=6; // in ohm
```

```
7 AB= 25; // in cm
8 BC= 75; // in cm
9 R= S*AB/BC; // in ohm
10 disp(R,"Unknown resistance in ohm")
```

---

### Scilab code Exa 6.6 Dials required

```
1 // Exa 6.6
2 clc;
3 clear;
4 close;
5 // Given data
6 resistor= 5000; // in ohm
7 LVR1= resistor-resistor*0.1/100; // Limiting value of
      5000 ohm resistor in negative error
8 LVR2= resistor+resistor*0.1/100; // Limiting value of
      5000 ohm resistor in positive error
9 disp("Limiting value of 5000 ohm resistance is "+
      string(LVR1)+" ohm to "+string(LVR2)+" ohm")
10 disp("Thus dials of 1000 , 100 , 10 and 1 ohm would
      to be adjusted");
```

---

### Scilab code Exa 6.7 Limiting values of unknown resistance

```
1 // Exa 6.7
2 clc;
3 clear;
4 close;
5 // Given data
6 P=100; // in ohm
7 Q=100; // in ohm
8 S=230; // in ohm
9 R=P*S/Q; // in ohm
```

```

10 del_P_BY_P= 0.02; // in %
11 del_Q_BY_Q= 0.02; // in %
12 del_S_BY_S= 0.01; // in %
13 del_R_BY_R= del_P_BY_P + del_Q_BY_Q + del_S_BY_S; // in %
14 disp(del_R_BY_R,"Relative limiting error of unknown resistance in percentage")
15 disp("So limiting values of unknown resistance "+string(R-R*del_R_BY_R/100)+" ohm to "+string(R+R*del_R_BY_R/100)+" ohm")

```

---

### Scilab code Exa 6.8 Magnitude and direction of current

```

1 // Exa 6.8
2 clc;
3 clear;
4 close;
5 // Given data
6 P=1000; // in ohm
7 Q=1000; // in ohm
8 S=100; // in ohm
9 E=2; // in volt
10 Rg=50; // in ohm
11 R_desh= 101; // in ohm
12 R=Q*S/P; // in ohm
13 del_R= R_desh-R; // in ohm
14 E_Th= E*[(R+del_R)/(R+del_R+S)- P/(P+Q)]; // in volt
15 R_Th= [(R+del_R)*S/(R+del_R+S)+ P*Q/(P+Q)]; // in ohm
16 Ig= E_Th/(R_Th+Rg); // in amp
17 Ig=Ig*10^+6; // in micro amp
18 disp(Ig,"The galvanometer current in micro amp")

```

---

### Scilab code Exa 6.9 Sensitivity of the bridge

```

1 // Exa 6.9
2 clc;
3 clear;
4 close;
5 // Given data
6 P=100; // in ohm
7 Q=1000; // in ohm
8 S=2000; // in ohm
9 E=5; // in volt
10 Si= 5; // in mm/miuA
11 Rg=200; // in ohm
12 R_desh= 202; // in ohm
13 R=P*S/Q; // in ohm
14 del_R= R_desh-R; // in ohm
15 E_Th= E*[(R+del_R)/(R+del_R+S)- P/(P+Q)]; // in volt
16 R_Th= [(R+del_R)*S/(R+del_R+S)+ P*Q/(P+Q)]; // in ohm
17 Ig= E_Th/(R_Th+Rg); // in amp
18 Ig=Ig*10^+6; // in micro amp
19 theta= Si*Ig; // in mm
20 disp(theta," Deflection of the galvanometer in mm")
21 S_B= theta/del_R; // in mm/ohm
22 disp(S_B," Sensitivity of the bridge in mm/ohm")

```

---

### Scilab code Exa 6.10 Ratio of galvanometer sensitivities

```

1 // Exa 6.10
2 clc;
3 clear;
4 close;
5 // Given data
6 P=1000; // in ohm
7 Q=100; // in ohm
8 R=200; // in ohm
9 E=5; // in volt
10 Si1= 10; // in mm/miuA

```

```

11 Si2= 5; // in mm/miuA
12 Rg1= 400; // in ohm
13 Rg2= 100; // in ohm
14 S=R*Q/P; // in ohm
15 R_Th= R*S/(R+S)+ P*Q/(P+Q); // in ohm
16 // theta=Si1*E*S*del_R/((R+S)^2*(R_Th+Rg))
17 // RatioTheta21= theta2/theta1
18 RatioTheta21= Si2/Si1*(R_Th+Rg1)/(R_Th+Rg2);
19 disp(RatioTheta21,"Ratio of deflection on two
galvanometers")

```

---

### Scilab code Exa 6.11 Smallest change in resistance

```

1 // Exa 6.11
2 clc;
3 clear;
4 close;
5 // Given data
6 P=500; // in ohm
7 S=P;
8 Q=S;
9 R=P;
10 R_Th=R; // in ohm
11 Rg=100; // in ohm
12 E=10; // in volt
13 Ig= 1; // in nA
14 Ig=Ig*10^-9; // in amp
15 // Formula Ig= E_Th/(R_Th+Rg) and E_Th= E*del_R/(4*R
    ) so
16 // Ig= (E*del_R/(4*R))/(R_Th+Rg) and
17 del_R= Ig*(R_Th+Rg)*4*R/E; // in ohm
18 del_R= del_R*10^3; // in mohm
19 disp(del_R,"The smallest change in resistance in
mohm")

```

---

### Scilab code Exa 6.12 Series resistance

```
1 // Exa 6.12
2 clc;
3 clear;
4 close;
5 // Given data
6 R=200; // in ohm
7 S=R;
8 P=S;
9 Q=P;
10 r=2; // in ohm
11 E=24; // in volt
12 Power= 0.5; // in W
13 // Formula Power= I^2/R
14 I= sqrt(Power/R); // in A
15 disp(I,"Maximum power dissipation in amp")
16 V=I*2*R; // in volt
17 // Formula E= V+2*I*(r+R)
18 R= (E-V)/(2*I)-r; // in ohm
19 disp(R,"Series resistance in ohm")
```

---

### Scilab code Exa 6.13 Maximum value of resistance

```
1 // Exa 6.13
2 clc;
3 clear;
4 close;
5 // Given data
6 P=10000; // in ohm
7 Q=10; // in ohm
8 S=5; // in kohm
```

```

9 S=S*10^3; // in ohm
10 E=12; // in volt
11 R=P*S/Q; // in ohm
12 disp(R*10^-6,"The maximum value of resistance that
    can be measurement with the given argument in
    Mohm")
13 R_Th= R*S/(R+S)+ P*Q/(P+Q); // in ohm
14
15 // Part (ii)
16 theta= 2.5; // in mm
17 Rg=100; // in ohm
18 Si=100; // in mm/miuA
19 Si=Si*10^6; // in mm/amp
20 del_R= theta*(R_Th+Rg)*(R+S)^2/(Si*E*S); // in ohm
21 disp(del_R*10^-3,"Change in resistance in kohm")

```

---

### Scilab code Exa 6.14 Unknown resistance

```

1 // Exa 6.14
2 clc;
3 clear;
4 close;
5 // Given data
6 p=200.62; // in ohm
7 q=400; // in ohm
8 P=200.48; // in ohm
9 Q=400; // in ohm
10 S=100.03; // in micro ohm
11 S=S*10^-6; // in ohm
12 r=700; // in micro ohm
13 r=r*10^-6; // in ohm
14 X= P*S/Q+q*r/(p+q)*(P/Q-p/q); // in ohm
15 disp(X*10^+6,"Unknown resistance in micro ohm")

```

---

# Chapter 7

## Inductance And Capacitance Measurements

Scilab code Exa 7.1 Balance the bridge under condition

```
1 // Exa 7.1
2 clc;
3 clear;
4 close;
5 // Given data
6 Z1= 100; // in
7 theta1= 30; // in
8 Z2= 50; // in
9 theta2= 0; // in
10 Z3= 200; // in
11 theta3= -90; // in
12 Z4= 100; // in
13 theta4= 30; // in
14 if Z1*Z4 == Z2*Z3 then
15     disp("The first condition is satisfied")
16 end
17 if theta1+theta4 == theta2+theta3 then
18     disp("The second condition is also satisfied , So
          it is possible to balance the bridge under")
```

```

        the given condition")
19 else
20     disp("The second condition is not satisfied .")
21     disp("So balance is not possible under given
           condition")
22 end

```

---

**Scilab code Exa 7.2** Whether or not the bridge is complete balance

```

1 // Exa 7.2
2 clc;
3 clear;
4 close;
5 // Given data
6 Z1= 1000; // in
7 theta1= -90; // in
8 Z2= 500; // in
9 theta2= 0; // in
10 Z3= 1000; // in
11 theta3= 0; // in
12 R4= 100; // in
13 XL4= 500; // in
14 Z4=abs(R4+%i*XL4); // in
15 theta4= atand(imag(R4+%i*XL4),real(R4+%i*XL4)); // in

16 if theta1+theta4 == theta2+theta3 then
17     disp("The first conditon is satisfied .")
18 else
19 disp("Balance is not possible with given
           configuration")
20 end
21 // 1/Z1=1/R1+j*omega*C1      ( i )
22 // According to figure 1/Z1= R4/(Z2*Z3)+%i*XL4/(Z2*
           Z3)      ( ii )
23 // Comparing real and j-components of Eqn ( i ) and (

```

```

        ii )
24 R1= Z2*Z3/R4; // in
25 OmegaC1= Z2*Z3/XL4; // in
26 disp("Since X_C1 is already equal to "+string(
    OmegaC1)+" , the bridge can be balanced simply
    by placing a")
27 disp("resistance of "+string(R1)+" across the
    capacitor arm 1")
28 // Z3= R3-j*X_C3          (iii)
29 Z3= Z1*expm(%i*theta1*pi/180)*Z4*expm(%i*theta4*pi
    /180)/(Z2*expm(%i*theta2*pi/180)); //      (iv)
30 // Comparing real and j-components of Eqn (iii) and
    (iv)
31 R3= 1000; // in
32 XC3= 200; // in
33 disp("Since R3 is already of "+string(R3)+" , the
    bridge can be balanced simply by adding a")
34 disp("capacitor of reactance X_C3 of "+string(XC3)+""
    in series with the resistor R3 in arm 3.")

```

---

### Scilab code Exa 7.3 Range of measurements of unknown capacitance

```

1 // Exa 7.3
2 clc;
3 clear;
4 close;
5 // Given data
6 C2= 0.2;// in micro F
7 Ratio21= 10/1;// resistance ratio R2/R1
8 C1= C2*Ratio21;// in micro F
9 Ratio21_desh= 1/10;
10 C1_desh= C2*Ratio21_desh;// in micro F
11 disp("So range of measurement of unknown capacitance
    is "+string(C1_desh)+" micro F to "+string(C1)+""
    micro F")

```

---

### Scilab code Exa 7.4 Dissipation Factor

```
1 // Exa 7.4
2 clc;
3 clear;
4 close;
5 // Given data
6 R2= 5; // in ohm
7 R3= 2000; // in ohm
8 R4= 2950; // in ohm
9 C2= 0.5; // in micro F
10 C2=C2*10^-6; // in F
11 r2=0.4; // in ohm
12 f=450; // in Hz
13 omega= 2*%pi*f;
14 // Under Balance Condition Z1*Z4=Z2*Z3
15 // [r1+1/(j*omega*C1)]*R4= [r2+R2+1/(j*omega*C2)]*R3
16 // Equating the real parts we have , r1*R4= (r2+R2)*
    R3
17 r1= (r2+R2)*R3/R4; // in ohm
18 disp(r1,"Value of r1 in ohm")
19 // Equating imaginary parts we have R4/(j*omega*C1)=
    R3/(j*omega*C2)
20 C1= R4/R3*C2; // in F
21 disp(C1*10^6,"Value of C1 in micro F");
22 Tan_toh= omega*C1*r1;
23 disp(Tan_toh,"Dissipation Factor is")
```

---

### Scilab code Exa 7.5 Phase angle errors and unknown capacitance

```
1 // Exa 7.5
```

```

2 clc;
3 clear;
4 close;
5 // Given data
6 f=1000; //in Hz
7 R1=1000; // in ohm
8 R2=1000; // in ohm
9 R3=2000; // in ohm
10 R4=2000; // in ohm
11 C1=1*10^-6; //in F
12 r1= 10; // in ohm
13 omega=2*pi*f;
14 C2=C1*R1/R2; //in F
15 disp(C2*10^6,"Unknown capacitance in micro F ");
16
17 r2=(R2*(R3+r1)-R1*R4)/R1; //in ohm
18 del_1=omega*r1*C1; //in radian
19 del_1=del_1*180/pi; // in
20 disp(del_1,"Phase angle error1 in degree");
21 del_2=omega*r2*C2; //in radian
22 del_2=del_2*180/pi; // in degree
23 disp(del_2, "Phase angle error2 in degree");

```

---

### Scilab code Exa 7.6 Values of C1 and r1 and dissipation factor

```

1 // Exa 7.6
2 clc;
3 clear;
4 close;
5 // Given data
6 f=500; //in Hz
7 R2=4.8; //in ohm
8 R3=2*10^3; // in ohm
9 R4=2.85*10^3; //in ohm
10 C2=0.5*10^-6; //in F

```

```

11 r2= 0.4; // in ohm
12 omega=2*pi*f;
13 C1=C2*R4/R3; //in F
14 disp(C1*10^6,"Unknown capacitance in micro F ");
15 r1=(R3*(R2+r2))/R4; //in ohm
16 disp(r1," Resistance of unknown capacitance in ohm")
17 Tan_del_1= omega*C1*r1;
18 disp(Tan_del_1," Dissipation factor is ")

```

---

**Scilab code Exa 7.7 Resistive and capacitive component of unknown capacitor and di**

```

1 // Exa 7.7
2 clc;
3 clear;
4 close;
5 // Given data
6 f=50; //in Hz
7 R2=330*10^3; //in ohm
8 R3=15*10^3; // in ohm
9 R4=22*10^3; //in ohm
10 C2=0.12*10^-6; //in F
11 omega=2*pi*f;
12 R1= R2*R3/R4; // in ohm
13 disp(R1*10^-3," Resistive component of unknown
             resistance in kohm")
14 C1= C2*R4/R3; // in F
15 disp(C1*10^6,"Capacitive component of unknown
             capacitor in micro F")
16 D=1/(omega*C1*R1);
17 disp(D," Dissipation factor is ")

```

---

**Scilab code Exa 7.8 Power factor of the specimen**

```

1 // Exa 7.8
2 clc;
3 clear;
4 close;
5 // Given data
6 f=50; //in Hz
7 R4=309; //in ohm
8 R2=100; // in ohm
9 C3=109*10^-12; //in F
10 C4=0.5*10^-6; //in F
11 omega=2*pi*f;
12 Cx= C3*R4/R2; // in F
13 disp(Cx*10^12,"Equivalent series capacitance in
F ");
14 Rx= C4*R2/C3; // in ohm
15 // Power factor of the specimen
16 Tan_delta= omega*Cx*Rx;
17 disp(Tan_delta,"Power factor of the specimen is ")

```

---

### Scilab code Exa 7.9 Variable capacitor and resistor required

```

1 // Exa 7.9
2 clc;
3 clear;
4 close;
5 // Given data
6 f=50; //in Hz
7 R4=1000; //in ohm
8 C3=50*10^-12; //in F
9 delta=9; // in
10 epsilon_r= 2.3;
11 epsilon_0= 8.854*10^-12;
12 d= 0.3*10^-2; // in meter
13 A=314; // area of each electrode in square cm
14 A=A*10^-4; // in square meter

```

```

15 omega=2*pi*f;
16 C1= epsilon_r*epsilon_0*A/d; // in F
17 // Formula tan (delta)= 1/(omega*C1*R1)
18 R1= 1/(omega*C1*tand(delta)); // in ohm
19 C4= 1/(omega^2*C1*R1*R4); // in F
20 disp(C4*10^6,"Variable capacitor in micro F")
21 R2= C3*R4*(cosd(delta))^2/C1; // in ohm
22 disp(R2,"Variable resistance in ohm")
23
24 // Note: Calculation of R2 in the book is wrong

```

---

### Scilab code Exa 7.10 Equivalent parallel resistance and capacitance

```

1 // Exa 7.10
2 clc;
3 clear;
4 close;
5 format('v',7);
6 // Given data
7 f=25; // in kHz
8 f=f*10^3; // in Hz
9 R1=3.1*10^3; // in ohm
10 R2=25*10^3; // in ohm
11 R4=100*10^3; // in ohm
12 C1=5.2*10^-6; // in F
13 omega= 2*pi*f;
14 // From C3/C1= R2/R4-R1/R3
15 // C3= C1*(R2/R4-R1/R3) (i)
16 // and omega= 1/sqrt(R1*R3*C1*C3)
17 // R3= 1/(omega^2*R1*C1*C3), putting this value in (i)
18 C3= C1*R2/(R4*(1+R1^2*C1^2*omega^2)); // in F
19 disp(C3*10^12,"Equivalent capacitance in F ")
20 R3= 1/(omega^2*R1*C1*C3); // in ohm
21 disp(R3*10^-3,"Equivalent parallel resistance in

```

```
    kohm")  
22  
23  
24 // Note Evaluating the value of C3 in the book is  
    wrong.
```

---

### Scilab code Exa 7.11 Values of C1 and r1 and dissipation factor

```
1 // Exa 7.11  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 format('v',9);  
7 R2= 5; // in ohm  
8 R3= 2000; // in ohm  
9 R4= 2950; // in ohm  
10 C2= 0.5; // in miu F  
11 C2=C2*10^-6; // in F  
12 r2=0.4; // in ohm  
13 f=450; // in Hz  
14 omega= 2*%pi*f;  
15 // Under Balance Condition Z1*Z4=Z2*Z3  
16 // [r1+1/(j*omega*C1)]*R4= [r2+R2+1/(j*omega*C2)]*R3  
17 // Equating the real parts we have , r1*R4= (r2+R2)*  
    R3  
18 r1= (r2+R2)*R3/R4; // in ohm  
19 disp(r1,"Value of r1 in ohm")  
20 // Equating imaginary parts we have R4/(j*omega*C1)=  
    R3/(j*omega*C2)  
21 C1= R4/R3*C2; // in F  
22 disp(C1*10^6,"Value of C1 in micro F");  
23 Tan_toh= omega*C1*r1;  
24 disp(Tan_toh,"Dissipation Factor is")
```

---

### Scilab code Exa 7.12 Resistance and inductance of coil

```
1 // Exa 7.12
2 clc;
3 clear;
4 close;
5 // Given data
6 L1= 52.6; // in mH
7 r1= 28.5; // in ohm
8 R2= 1.68; // in ohm
9 R3= 80; // resistance in ohm
10 R4= 80; // resistance in ohm
11 r2= r1*R3/R4-R2; // in ohm
12 disp(r2,"Resistance of coil in ohm")
13 L2=L1*R3/R4; // in mH
14 disp(L2,"Inductance of coil in mH");
```

---

### Scilab code Exa 7.13 Resistance and inductance of coil

```
1 // Exa 7.13
2 clc;
3 clear;
4 close;
5 // Given data
6 L= 47.8; // in mH
7 R= 1.36; // in ohm
8 R2= 100; // in ohm
9 R3= 32.7; // in ohm
10 R4= 100; // in ohm
11 R1= R2*R3/R4-R; // in ohm
12 disp(R1,"Resistance of coil in ohm");
13 L1= R2/R4*L; // in mH
```

```
14 disp(L1," Inductance of coil in mH")
```

---

### Scilab code Exa 7.14 Resistance and inductance of inductor

```
1 // Exa 7.14
2 clc;
3 clear;
4 close;
5 // Given data
6 R2= 1000; // in ohm
7 R3= 1000; // in ohm
8 R4= 1000; // in ohm
9 C4= 0.5; // in miu F
10 C4= C4*10^-6; // in F
11 R1= R2*R3/R4; // in ohm
12 disp(R1," Resistance of inductor in ohm")
13 L1= C4*R2*R3; // in H
14 disp(L1," Inductance of inductor in H")
```

---

### Scilab code Exa 7.15 Resistance and inductance of unknown inductor

```
1 // Exa 7.15
2 clc;
3 clear;
4 close;
5 // Given data
6 r= 469; // in ohm
7 R2= 1000; // in ohm
8 R3= 218; // in ohm
9 R4= 1000; // in ohm
10 C= 10; // in miu F
11 C= C*10^-6; // in F
12 R1= R2*R3/R4; // in ohm
```

```
13 disp(R1," Resistance of inductor in ohm")
14 L1= C*R2/R4*(r*(R3+R4)+R3*R4); // in H
15 disp(L1," Inductance of inductor in H")
```

---

### Scilab code Exa 7.16 Resistance and inductance of AB

```
1 // Exa 7.16
2 clc;
3 clear;
4 close;
5 // Given data
6 r= 500; // in ohm
7 R2= 400; // in ohm
8 R3= 400; // in ohm
9 R4= 400; // in ohm
10 C= 2; // in miu F
11 C= C*10^-6; // in F
12 R= R2*R3/R4; // in ohm
13 disp(R," Resistance of AB in ohm")
14 L= C*R2/R4*(r*(R3+R4)+R3*R4); // in H
15 disp(L," Inductance of AB in H")
```

---

### Scilab code Exa 7.17 Resistance and inductance of unknown inductor

```
1 // Exa 7.17
2 clc;
3 clear;
4 close;
5 // Given data
6 r= 100; // in ohm
7 R2= 1000; // in ohm
8 R3= 500; // in ohm
9 R4= 1000; // in ohm
```

```
10 C= 3; // in micro F
11 C= C*10^-6; // in F
12 Rx= R2*R3/R4; // in ohm
13 disp(Rx,"Value of Rx in ohm")
14 Lx= C*R2/R4*(r*(R3+R4)+R3*R4); // in H
15 disp(Lx,"Value of Lx in H")
```

---

### Scilab code Exa 7.18 Resistance and inductance at balance condition

```
1 // Exa 7.18
2 clc;
3 clear;
4 close;
5 // Given data
6 R2= 1000; // in ohm
7 R3= 16800; //in ohm
8 R4= 833; //in ohm
9 C4= 0.38; // in miu F
10 C4= C4*10^-6; // in F
11 f= 50; // in Hz
12 omega=2*pi*f;
13 L1= R2*R3*C4/(1+(omega*C4*R4)^2); // in H
14 disp(L1,"Unknown inductance in H");
15 R1= R2*R3*R4*omega^2*C4^2/(1+(omega*C4*R4)^2); // in
    ohm
16 disp(R1,"Unknown resistance in ohm")
```

---

### Scilab code Exa 7.19 Value of R and C

```
1 // Exa 7.19
2 clc;
3 clear;
4 close;
```

```

5 // Given data
6 R1= 500; //in ohm
7 R2= 1000; // in ohm
8 R3= R2; //in ohm
9 L1= 0.18; // in H
10 f= 5000/(2*pi); // in Hz
11 omega= 2*pi*f;
12 // L1= R2*R3*C4/(1+(omega*C4*R4)^2) (i)
13 // and R1= R2*R3*R4*omega^2*C4^2/(1+(omega*C4*R4)^2) or R1= omega^2*R4*C4*L1
14 R4C4= R1/(omega^2*L1);
15 // From eq (i)
16 C4= L1*(1+(omega*R4C4)^2)/(R2*R3); // in F
17 disp(C4*10^6,"Value of C in micro F");
18 R4= R4C4/C4; // in ohm
19 disp(round(R4),"Value of R4 in ohm")

```

---

### Scilab code Exa 7.20 Series equivalent inductance and resistance

```

1 // Exa 7.20
2 clc;
3 clear;
4 close;
5 // Given data
6 R2= 1000; //in ohm
7 R3= 10000; // in ohm
8 R4= 2000; //in ohm
9 C4= 1*10^-6; // in F
10 omega= 3000; // radians/sec
11 L1= R2*R3*C4/(1+(omega*C4*R4)^2); // in H
12 disp(L1,"Equivalent inductance of the network in H")
13 R1= R2*R3*R4*omega^2*C4^2/(1+(omega*C4*R4)^2); // in
   ohm
14 disp(R1*10^-3,"Equivalent resistance of the network
   in kohm")

```

---

### Scilab code Exa 7.21 Resistance and inductance of choke coil

```
1 // Exa 7.21
2 clc;
3 clear;
4 close;
5 // Given data
6 R2= 2410; //in ohm
7 R3= 750; // in ohm
8 R4= 64.5; //in ohm
9 C4= 0.35*10^-6; // in F
10 r4= 0.4; // series resistance of capacitor in ohm
11 f=500; // in Hz
12 omega= 2*pi*f; // radians/sec
13 R4= R4+r4; // in ohm
14 R1= R2*R3*R4*omega^2*C4^2/(1+(omega*C4*R4)^2); // in
   ohm
15 disp(R1,"Resistance of the choke coil in ohm")
16 L1= R2*R3*C4/(1+(omega*C4*R4)^2); // in H
17 disp(L1,"Inductance of the choke coil in H")
18
19 // Note: Calculation of finding the value of L1 in
   the book is wrong
```

---

### Scilab code Exa 7.22 Effective impedance of the specimen

```
1 // Exa 7.22
2 clc;
3 clear;
4 close;
5 // Given data
```

```

6 R2= 834; // in
7 R3= 100; // in
8 C2= 0.124; // in F
9 C2= C2*10^-6; // in F
10 C4= 0.1; // in F
11 C4= C4*10^-6; // in F
12 L1= R2*R3*C4; // in H
13 f= 2; // in kHz
14 f= f*10^3; // in kHz
15 disp(L1*10^3,"The value of L1 in mH is : ")
16 R1= R3*C4/C2; // in
17 disp(R1,"The value of R1 in ohm is : ")
18 Z= R1+%i*2*%pi*f*L1; // in
19 disp(abs(Z),"The magnitude of effective impedance in
is : ")
20 disp(atand(imag(Z),real(Z)),"The angle of effective
impedance in degrees is : ")

```

---

### Scilab code Exa 7.23 Value of L and C

```

1 // Exa 7.23
2 clc;
3 clear;
4 close;
5 // Given data
6 fr= 2; // in MHz
7 fr=fr*10^6; // in Hz
8 C=230+8; // in pF
9 C=C*10^-12; // in F
10 // Formula fr= 1/(2*pi*sqrt(L*C))
11 L= 1/((2*pi*fr)^2*C); // in H
12 disp(L*10^6,"Value of L in H ")
13 // From the first set of data
14 fr= 1; // in MHz
15 fr=fr*10^6; // in Hz\

```

```
16 C= 1/((2*pi*fr)^2*L); // in F
17 disp(C*10^12,"Value of C in pF")
```

---

**Scilab code Exa 7.24 Resistive and reactive component of unknown impedance**

```
1 // Exa 7.24
2 clc;
3 clear;
4 close;
5 // Given data
6 C1= 208; // in pF
7 C1=C1*10^-12; // in F
8 Q1= 80;
9 C2= 184; // in pF
10 C2=C2*10^-12; // in F
11 Q2= 50;
12 f=165; // in kHz
13 f=f*10^3; // in Hz
14 omega= 2*pi*f; // in radians/sec
15 // Part (i)
16 Rm= 1/omega*(1/(C2*Q2)-1/(C1*Q1)); // in ohm
17 disp(Rm,"Resistive component of unknown impedance in
ohm")
18 // Part (ii)
19 Xm= 1/omega*(1/C2-1/C1); // in ohm
20 disp(round(Xm),"Reactive component of unknown
impedance in ohm")
```

---

**Scilab code Exa 7.25 Self capacitance and inductance of the coil**

```
1 // Exa 7.25
2 clc;
3 clear;
```

```

4 close;
5 // Given data
6 C1= 160*10^-12; // in F
7 C2= 36*10^-12; // in F
8 f1=250; // in kHz
9 f1=f1*10^3; // in Hz
10 f2=500; // in kHz
11 f2=f2*10^3; // in Hz
12 Cd= (C1-4*C2)/3; // in F
13 disp(Cd*10^12," Self Capacitance of the coil in F
")
14 // Formula f1= 1/(2*pi*sqrt(L*(C1+Cd)))
15 L= 1/((2*pi*f1)^2*(C1+Cd)); // in H
16 disp(round(L*10^6)," Self inductance of the coil in
H ");

```

---

#### Scilab code Exa 7.26 Self capacitance of the coil

```

1 // Exa 7.26
2 clc;
3 clear;
4 close;
5 // Given data
6 C1= 251*10^-12; // in F
7 C2= 50*10^-12; // in F
8 f1=3; // in MHz
9 f1=f1*10^6; // in Hz
10 f2=6; // in MHz
11 f2=f2*10^6; // in Hz
12 Cd= (C1-4*C2)/3; // in F
13 disp(Cd*10^12," Self Capacitance of the coil in pF")

```

---

#### Scilab code Exa 7.27 Value of self capacitance

```

1 // Exa 7.27
2 clc;
3 clear;
4 close;
5 // Given data
6 C1= 1530; // in pF
7 C2= 162; // in pF
8 f1=1; // in MHz
9 f1=f1*10^6; // in Hz
10 f2=3; // in MHz
11 f2=f2*10^6; // in Hz
12 // f1= 1/(2*pi*sqrt(L*(C1+Cd)))
13 // f1= 1/(2*pi*sqrt(L*(C2+Cd))) and f2= 3*f1 so
14 Cd= (C1-9*C2)/8; // in pF
15 disp(Cd," Self capacitance of the coil in pF")

```

---

### Scilab code Exa 7.28 Effective inductance and resistance of unknown coil

```

1 // Exa 7.28
2 clc;
3 clear;
4 close;
5 // Given data
6 f= 450; // in kHz
7 f=f*10^3; // in Hz
8 C=250; // in pF
9 C=C*10^-12; // in F
10 Rsh= 0.75; // in ohm
11 Q= 105;
12 omega= 2*pi*f; // in radians/sec
13 // Formula f= 1/(2*pi*sqrt(L*C))
14 L= 1/((2*pi*f)^2*C); // in H
15 disp(round(L*10^6)," Inductance of the coil in H ")
16 R= omega*L/Q-Rsh; // in ohm
17 disp(R," Resistance of the coil in ohm")

```

---

**Scilab code Exa 7.29** Percentage error introduced in the calculated value of Q

```
1 // Exa 7.29
2 clc;
3 clear;
4 close;
5 // Given data
6 f= 500; // in kHz
7 f=f*10^3; // in Hz
8 C=120; // in pF
9 C=C*10^-12; // in F
10 R= 5; // in ohm
11 r=0.02; // resistance used across the oscillatory
            circuit in ohm
12 omega= 2*%pi*f; // in radians/sec
13 Q_True= 1/(omega*C*R);
14 Q_indicated= 1/(omega*C*(R+r));
15 PerError= (Q_True-Q_indicated)*100/Q_True; // in %
16 disp(PerError," Percentage Error is ")
```

---

**Scilab code Exa 7.30** Self capacitance of the radio coil

```
1 // Exa 7.30
2 clc;
3 clear;
4 close;
5 // Given data
6 f1= 800; // in kHz
7 f1=f1*10^3; // in Hz
8 f2= 2.5; // in MHz
9 f2=f2*10^6; // in Hz
```

```

10 C1=95; // in pF
11 C1=C1*10^-12; // in F
12 // L= 1/(omega1^2*(C1+Cd)) (i)
13 // L= 1/(omega2^2*Cd) (ii)
14 // From eq(i) and eq(ii)
15 Cd= f1^2*C1/(f2^2-f1^2); // in F
16 disp(Cd*10^12," Self capacitance of the radio coil in
    pF");

```

---

**Scilab code Exa 7.31** Self capacitance of the coil and true and indicated values of

```

1 // Exa 7.31
2 clc;
3 clear;
4 close;
5 // Given data
6 f1= 1; // in MHz
7 f1=f1*10^6; // in Hz
8 f2= 2; // in MHz
9 f2=f2*10^6; // in Hz
10 C1=480; // in pF
11 C1=C1*10^-12; // in F
12 C2=90; // in pF
13 C2=C2*10^-12; // in F
14 R=10; // in ohm
15 omega1= 2*pi*f1; // in radians/sec
16 omega2= 2*pi*f2; // in radians/sec
17
18 // Part (i)
19 Cd= (C1-4*C2)/3; // in F
20 disp(Cd*10^12," Self capacitance of the coil in pF")
21
22 // Part(ii)
23 Q_indicated1= 1/(omega1*(C1+Cd)*R);
24 disp(Q_indicated1," Indicated or effective Q for

```

```
    first measurement")
25 Q_True1= 1/(omega1*C1*R);
26 disp(Q_True1,"True Q for first measurement is ");
27 Q_indicated2= 1/(omega2*(C2+Cd)*R);
28 disp(Q_indicated2,"Indicated or effective Q for
second measurement")
29 Q_True2= 1/(omega2*C2*R);
30 disp(Q_True2,"True Q for second measurement is");
```

---

# Chapter 8

## Cathode Ray Oscilloscopes

Scilab code Exa 8.1 Deflection sensitivity

```
1 // Exa 8.1
2 clc;
3 clear;
4 close;
5 // Given data
6 l=25; // in mm
7 l=l*10^-3; // in meter
8 d=5; // in mm
9 d=d*10^-3; // in meter
10 S= 20; // in cm
11 S= S*10^-2; // in meter
12 Va= 3000; // in volts
13 TraceLength= 10; // in cm
14 TraceLength=TraceLength*10^-2; // in meter
15 y=TraceLength/2;
16 Vd= 2*d*Va*y/(l*S); // in volts
17 Vrms= Vd/sqrt(2); // in volts
18 Vrms= floor(Vrms);
19 disp(Vrms,"RMS value of the sinusoidal voltage
    applied to the X-deflecting plates in volt");
20 DeflectionSensitivity= l*S/(2*d*Va); // in m/V
```

```
21 disp(DeflectionSensitivity*10^3,"Deflection  
Sensitivity in mm/V");
```

---

### Scilab code Exa 8.2 Maximum velocity of electrons

```
1 // Exa 8.2  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 Va= 1000; // in volts  
7 e= 1.6*10^-19; // in C  
8 m= 9.1*10^-31; // in kg  
9 MaxVel= sqrt(2*Va*e/m); // maximum velocity of  
electrons in m/s  
10 disp(MaxVel,"Maximum velocity of electrons in m/s")
```

---

### Scilab code Exa 8.3 Deflection sensitivity

```
1 // Exa 8.3  
2 clc;  
3 clear;  
4 close;  
5 // Given data  
6 l=20; // in mm  
7 l=l*10^-3; // in meter  
8 d=5; // in mm  
9 d=d*10^-3; // in meter  
10 S= 0.20; // in meter  
11 Va= 2500; // in volts  
12 DeflectionSensitivity= l*S/(2*d*Va); // in m/V  
13 disp(DeflectionSensitivity*10^3,"Deflection  
Sensitivity in mm/V");
```

---

### Scilab code Exa 8.4 Required voltage

```
1 // Exa 8.4
2 clc;
3 clear;
4 close;
5 // Given data
6 l=2.5; // in cm
7 l=l*10^-2; // in meter
8 d=1; // in cm
9 d=d*10^-2; // in meter
10 Va= 1000; // in volts
11 theta= 1; // in degree
12 // Formula tand(theta) = l*Vd/(2*d*Va)
13 Vd= 2*d*Va/l*tand(theta); // in volts
14 disp(Vd,"Voltage required across the deflection
plates in volts")
```

---

### Scilab code Exa 8.5 Required deflecting voltage

```
1 // Exa 8.5
2 clc;
3 clear;
4 close;
5 // Given data
6 l=2.5; // in cm
7 l=l*10^-2; // in meter
8 d=.5; // in cm
9 d=d*10^-2; // in meter
10 S= 20; // in cm
11 S= S*10^-2; // in meter
```

---

```

12 Va= 2500; // in volts
13 // Formula y = OC*AB/OB = (S*d/2)/(1/2)
14 y = (S*d/2)/(1/2); // in meter
15 disp(y*10^2,"Deflection in cm")

```

---

### Scilab code Exa 8.6 Charging current and time period

```

1 // Exa 8.6
2 clc;
3 clear;
4 close;
5 // Given data
6 R_E1= 5.6; // in kohm
7 C1= 0.2; // in miu F
8 V_B1= 6.3; // in volt
9 V_BE= 0.7; // in volt
10 TL= 2.5; // trigger level for the Schmitt trigger (
    UTP,LTP) in volt
11 del_V1= 2*TL; // in volt
12 I_C1= (V_B1-V_BE)/R_E1; // in mA
13 disp(I_C1,"Charging current in mA");
14 toh= del_V1*C1/I_C1; // in ms
15 disp(toh,"Time period in ms")

```

---

### Scilab code Exa 8.7 RMS value of unknown ac voltage

```

1 // Exa 8.7
2 clc;
3 clear;
4 close;
5 // Given data
6 L=10; // trace length in cm
7 DS= 5; // deflection sensitivity in V/cm

```

```
8 V_peakT0peak= L*DS; // in volt
9 V_peak= V_peakT0peak/2; // in volt
10 RMS= V_peak/sqrt(2); // RMS value of unknown as
    voltage in volt
11 disp(RMS,"AC voltage in volt")
```

---

#### Scilab code Exa 8.8 Ratio of frequencies of vertical and horizontal signals

```
1 // Exa 8.8
2 clc;
3 clear;
4 close;
5 // Given data
6 Y= 3; // Positive Y-peaks in pattern
7 X= 2; // Positive X-peaks in pattern
8 // Ratio of frequencies of vertical and horizontal
    signals
9 // f_y/f_x= omega_y/omega_x = Y/X
10 R= Y/X; //Ratio of frequencies
11 disp(R,"Ratio of frequencies of vertical and
    horizontal signals");
```

---

#### Scilab code Exa 8.9 Frequency of vertical signal

```
1 // Exa 8.9
2 clc;
3 clear;
4 close;
5 // Given data
6 Y= 2+1/2; // Positive Y-peaks in pattern
7 X= 1/2+1/2; // Positive X-peaks in pattern
8 f_h= 3 // frequency of horizontal voltage signal in
    kHz
```

```
9 f_yBYf_x= Y/X;
10 // frequency of vertical voltage signal= f_yBYf_x *
    f_h
11 f_v= f_yBYf_x * f_h; // frequency of vertical voltage
    signal in kHz
12 disp(f_v," frequency of vertical voltage signal in
    kHz");
```

---

#### Scilab code Exa 8.10 Frequency of vertical signal

```
1 // Exa 8.10
2 clc;
3 clear;
4 close;
5 // Given data
6 f_x= 1000; // in Hz
7 Y= 2; // points of tangency to vertical line
8 X= 5; // points of tangency to horizontal line
9 f_y= f_x*X/Y; // in Hz
10 disp(f_y," Frequency of vertical input in Hz")
```

---

#### Scilab code Exa 8.11 Mark to space ratio

```
1 // Exa 8.11
2 clc;
3 clear;
4 close;
5 // Given data
6 // Taking 1div= 1 cm for CRO wave displays
7 Mark= 0.4; // cm
8 Space= 1.6; // cm
9 SAC= 0.2; // signal amplitude control in V/div
10 TBS= 10; // time base control in micro/div
```

```

11 Amplitude= 2.15; // in cm
12 M_S_ratio= Mark/Space; // Mark to Space ratio
13 disp(M_S_ratio,"Mark to Space ratio ")
14 T= (Mark+Space)*TBS; // in micro sec
15 T=T*10^-6; // in sec
16 f=1/T; // in Hz
17 disp(f*10^-3,"Pulse frequency in kHz")
18 Mag= Amplitude*SAC; // Magnitude of pulse voltage in
    volt
19 disp(Mag,"Magnitude of pulse voltage in volt")

```

---

### Scilab code Exa 8.12 Phase angle for each trace

```

1 // Exa 8.12
2 clc;
3 clear;
4 close;
5 // Given data
6 // Part (a)
7 d_v0= 0;
8 Dv=6;
9 fie= asind(d_v0/Dv);
10 disp(fie,"Phase angle of first figure in degree")
11 // Part (b)
12 d_v0= 3;
13 Dv=6;
14 fie= asind(d_v0/Dv);
15 disp(fie,"Phase angle of second figure in degree")
16 // Part (c)
17 d_v0= 5;
18 Dv=5;
19 fie= asind(d_v0/Dv);
20 disp(fie,"Phase angle of third figure in degree")
21 // Part (d)
22 d_v0= 3;

```

```
23 Dv=5;
24 fie= asind(d_v0/Dv);
25 // since ellipse is in 2nd and fourth quartes so the
   valid value of phase angle
26 fie= 180-fie
27 disp(fie,"Phase angle of forth figure in degree")
```

---

### Scilab code Exa 8.13 Pulse duration

```
1 // Exa 8.13
2 clc;
3 clear;
4 close;
5 // Given data
6 f=2000; // in Hz
7 T=1/f; // in sec
8 D=0.2;
9 PulseDuration= D*T; // in sec
10 disp(PulseDuration*10^3,"Pulse duration in ms")
```

---

### Scilab code Exa 8.14 Peak to peak amplitude of the signal and signal frequency

```
1 // Exa 8.14
2 clc;
3 clear;
4 close;
5 // Given data
6 vertical_attenuation= 0.5; // in V/Div
7 TPD= 2; // time/Div control in micro sec
8 P= 4*vertical_attenuation; // peak-to-peak amplitude
   of the signal in V;
9 disp(P,"Peak-to-Peak amplitude of the signal in V")
10 T= 4*TPD; // in micro sec
```

```
11 T=T*10^-6; // in sec
12 f=1/T; // in Hz
13 disp(f*10^-3,"Frequency in kHz")
```

---

### Scilab code Exa 8.15 Value of C1 and input capacitance

```
1 // Exa 8.15
2 clc;
3 clear;
4 close;
5 // Given data
6 C_1N= 36; // in pF
7 C_2= 150; // in pF
8 R_1N= 1; // in M ohm
9 R_1= 10; // in M ohm
10 // R_1/(omega*(C_2+C_1N)) = R_1N/(omega*C_1)
11 C_1= R_1N*(C_2+C_1N)/R_1; // in pF
12 disp(C_1,"Value of C_1 in pF")
13 C_T= 1/(1/C_1+1/(C_2+C_1N)); // in pF
14 disp(C_T,"Value of C_T in pF")
```

---

### Scilab code Exa 8.16 Signal frequency

```
1 // Exa 8.16
2 clc;
3 clear;
4 close;
5 // Given data
6 C_1N= 36; // in pF
7 C_2= 150; // in pF
8 R_1N= 1; // in M ohm
9 R_1= 10; // in M ohm
10 R_source= 500; // in ohm
```

```
11 // R_1/(omega*(C_2+C_1N)) = R_1N/(omega*C_1)
12 C_1= R_1N*(C_2+C_1N)/R_1; // in pF
13 C_T= 1/(1/C_1+1/(C_2+C_1N)); // in pF
14 C_T= C_T*10^-12; // in F
15 f= 1/(2*pi*C_T*R_source);
16 disp(f*10^-6,"Signal Frequency in MHz")
```

---

### Scilab code Exa 8.17 Minimum time division

```
1 // Exa 8.17
2 clc;
3 clear;
4 close;
5 // Given data
6 f= 20; // in MHz
7 f=f*10^6; // in Hz
8 toh= 1/f; // in sec
9 toh=toh*10^9; // in ns
10 // For one cycle occupying 4 horizontal divisions ,
11 MTD= toh/4; // Minimum time/division in ns/division
12 // Using the 10 times magnifier to provide MTD
13 MTD_setting= 10*MTD; // minimum time/division setting
   in ns/division
14 disp(MTD_setting,"Minimum time/division setting in
   ns/division")
```

---

# Chapter 10

## Instrument Calibration And Recorders

Scilab code Exa 10.1 Instrument accuracy

```
1 // Exa 10.1
2 clc;
3 clear;
4 close;
5 // Given data
6 FullScale= 25; // in volt
7
8 VR= 5; // voltmeter reading in volt
9 Error= -0.25; // in volt
10 Error_Reading= Error/VR*100; // % of reading
11 disp(Error_Reading,"Error percentage of reading");
12 Error_FullScale= Error/FullScale*100; // % of full
    scale
13 disp(Error_FullScale,"Error percentage of full scale
    ")
14
15 VR= 10; // voltmeter reading in volt
16 Error= 0.25; // in volt
17 Error_Reading= Error/VR*100; // % of reading
```

```
18 disp(Error_Reading,"Error percentage of reading");
19 Error_FullScale= Error/FullScale*100; // % of full
    scale
20 disp(Error_FullScale,"Error percentage of full scale
    ")
21
22 VR= 20; // voltmeter reading in volt
23 Error= -0.4; // in volt
24 Error_Reading= Error/VR*100; // % of reading
25 disp(Error_Reading,"Error percentage of reading");
26 Error_FullScale= Error/FullScale*100; // % of full
    scale
27 disp(Error_FullScale,"Error percentage of full scale
    ")

---


```

### Scilab code Exa 10.2 Wattmeter error

```
1 // Exa 10.2
2 clc;
3 clear;
4 close;
5 // Given data
6 Pm=1250; // in watt
7 V=255; // in volt
8 I=4.8; // in amp
9 P=V*I; // in watt
10 AbsoluteError= Pm-P; // in watt
11 disp(AbsoluteError,"Absolute Error in watt");
12 PerError= AbsoluteError/Pm*100; // in %
13 disp(PerError,"Percentage Error")

---


```