

Scilab Textbook Companion for
Electronic Devices and Circuits
by J. Paul¹

Created by
S. Prashanth
BE
Electrical Engineering
BANNARI AMMAN INSTITUTE OF TECHNOLOGY, TAMIL NADU
College Teacher
Dr. V. Parthiban
Cross-Checked by
Chaya Ravindra

July 30, 2019

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Electronic Devices and Circuits

Author: J. Paul

Publisher: New Age International

Edition: 1

Year: 2003

ISBN: 812241415X

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Semiconductor Physics	5
2 Semiconductor Diodes	22
3 special semiconductor diodes	36
4 Bipolar Junction Transistor	40
5 BJT Amplifier	68
6 BJT at high frequency	90
7 Field Effect Transistor	94
8 FET Amplifier	99
9 Multistage Amplifier	103
10 Negative Feedback Amplifiers	108
11 Sinusoidal Oscillators	112
12 Power Electronic Devices	118

List of Scilab Codes

Exa 1.1	Minority carrier concentration	5
Exa 1.2	example 2	6
Exa 1.3	example 3	6
Exa 1.4	example 4	7
Exa 1.5	example 5	8
Exa 1.6	example 6	9
Exa 1.7	example 7	9
Exa 1.8	example 8	10
Exa 1.9	example 9	11
Exa 1.10	example 10	11
Exa 1.11	example 11	12
Exa 1.12	example 12	12
Exa 1.13	example 13	13
Exa 1.14	example 14	13
Exa 1.15	example 15	14
Exa 1.16	example 16	15
Exa 1.17	example 17	16
Exa 1.18	example 18	16
Exa 1.19	example 19	17
Exa 1.20	example 20	18
Exa 1.21	example 21	18
Exa 1.22	example 22	19
Exa 1.23	example 23	20
Exa 1.24	example 24	20
Exa 2.1	example 1	22
Exa 2.2	example 2	23
Exa 2.3	example 3	23
Exa 2.4	example 4	24

Exa 2.6	example 6	25
Exa 2.7	example 7	25
Exa 2.8	example 8	26
Exa 2.11	example 11	26
Exa 2.12	example 12	27
Exa 2.14	example 14	27
Exa 2.15	example 15	28
Exa 2.16	example 16	29
Exa 2.17	example 17	30
Exa 2.18	example 18	30
Exa 2.19	example 19	31
Exa 2.20	example 20	32
Exa 2.21	example 21	32
Exa 2.22	example 22	32
Exa 2.23	example 23	33
Exa 2.24	example 24	33
Exa 2.25	example 25	34
Exa 3.1	example 1	36
Exa 3.2	example 2	37
Exa 3.3	example 3	37
Exa 3.4	example 4	38
Exa 3.6	example 6	38
Exa 3.7	example 7	39
Exa 4.1	example 1	40
Exa 4.2	example 2	41
Exa 4.5	example 5	41
Exa 4.6	example 6	42
Exa 4.7	example 7	43
Exa 4.9	example 9	43
Exa 4.10	example 10	44
Exa 4.11	example 11	45
Exa 4.12	example 12	45
Exa 4.13	example 13	46
Exa 4.14	example 14	47
Exa 4.15	example 15	47
Exa 4.16	example 16	48
Exa 4.17	example 17	49
Exa 4.18	example 18	49

Exa 4.19	example 19	50
Exa 4.21	example 21	50
Exa 4.22	example 22	51
Exa 4.23	example 23	51
Exa 4.24	example 24	51
Exa 4.25	example 25	52
Exa 4.26	example 26	52
Exa 4.27	example 27	53
Exa 4.28	example 28	54
Exa 4.29	example 29	55
Exa 4.30	example 30	56
Exa 4.31	example 31	56
Exa 4.32	example 32	57
Exa 4.33	example 33	57
Exa 4.34	example 34	58
Exa 4.35	example 35	59
Exa 4.36	example 36	60
Exa 4.37	example 37	61
Exa 4.38	example 38	61
Exa 4.39	example 39	62
Exa 4.40	example 40	63
Exa 4.41	example 41	64
Exa 4.42	example 42	64
Exa 4.43	example 43	65
Exa 4.45	example 45	65
Exa 4.46	example 46	66
Exa 4.47	example 47	66
Exa 5.1	example 1	68
Exa 5.2	example 2	69
Exa 5.3	example 3	69
Exa 5.4	example 4	71
Exa 5.5	example 5	71
Exa 5.6	example 6	72
Exa 5.7	example 7	72
Exa 5.8	example 8	73
Exa 5.9	example 9	74
Exa 5.10	example 10	74
Exa 5.11	example 11	75

Exa 5.12	example 12	75
Exa 5.13	example 13	76
Exa 5.14	example 14	77
Exa 5.15	example 15	77
Exa 5.16	example 16	78
Exa 5.17	example 17	79
Exa 5.18	example 18	80
Exa 5.19	example 19	81
Exa 5.20	example 20	82
Exa 5.21	example 21	82
Exa 5.22	example 22	83
Exa 5.23	example 23	84
Exa 5.24	example 24	84
Exa 5.25	example 25	85
Exa 5.26	example 26	86
Exa 5.27	example 27	86
Exa 5.28	example 28	87
Exa 5.29	example 29	88
Exa 5.30	example 30	88
Exa 6.1	example 1	90
Exa 6.2	example 2	91
Exa 6.3	example 3	92
Exa 6.6	example 6	92
Exa 6.8	example 8	93
Exa 7.1	example 1	94
Exa 7.2	example 2	95
Exa 7.4	example 4	95
Exa 7.5	example 5	96
Exa 7.6	6	96
Exa 7.7	example 7	97
Exa 7.8	example 8	97
Exa 7.9	example 9	98
Exa 8.1	example 1	99
Exa 8.2	example 2	100
Exa 8.3	example 3	100
Exa 8.6	example 6	101
Exa 8.7	example 7	101
Exa 8.9	example 9	102

Exa 9.1	example 1	103
Exa 9.2	example 2	104
Exa 9.3	example	104
Exa 9.4	example 4	105
Exa 9.5	example 5	105
Exa 9.6	example 6	106
Exa 9.8	example 8	107
Exa 10.1	example 1	108
Exa 10.2	example 2	108
Exa 10.3	example 3	109
Exa 10.5	example 5	110
Exa 10.6	example 6	110
Exa 11.2	example 2	112
Exa 11.3	example 3	113
Exa 11.5	example 5	113
Exa 11.6	example 6	114
Exa 11.7	example 7	115
Exa 11.8	example 8	116
Exa 11.9	example 9	116
Exa 12.1	example 1	118
Exa 12.2	example 2	118
Exa 12.3	example 3	119
Exa 12.4	example 4	119
Exa 12.5	example 5	120
Exa 12.6	example 6	120
Exa 12.7	example 7	121
Exa 12.9	example 9	121
Exa 12.10	example 10	122
Exa 13.1	example 1	123
Exa 13.2	example 2	123
Exa 13.3	example 3	124
Exa 13.4	example 4	125
Exa 13.5	example 5	125
Exa 13.7	example 7	126
Exa 13.8	example 8	126
Exa 13.9	example 9	127
Exa 13.10	example 10	127

Chapter 1

Semiconductor Physics

Scilab code Exa 1.1 Minority carrier concentration

```
1 //pagenumber 24 example 1
2 clear
3 incaco=1.5*10^16;//cubic metre
4 resist=2*10^3;//ohm metre
5 dopcon=10^20;//metre
6 q=26*10^-3;//electron volt
7 //(1)
8 w=2.25*10^32/dopcon;
9 //(3)
10 shifer=q*log(dopcon/incaco);//shift in fermi level
11 ni=9*10^32;
12 //(3)
13 w1=ni/dopcon;
14 disp("minority concentration = "+string((w))+
    "per metre square");
15 disp("shift in fermi = "+string((shifer))+
    "voltage");
16 disp("minority concentration when n doubled = "+
    string((w1))+
    "per cubic metre");
```

Scilab code Exa 1.2 example 2

```
1 //pagenumber 25 example 2
2 clear
3 format(12)
4 numfre=7.87*10^28; //per cubic metre
5 molity=34.8; //square centimetre/velocity second
6 e=30; //volt per centimetre
7 //(1)
8 molity=molity*10^-4; q=1.6*10^-19;
9 conduc=numfre*q*molity;
10 //(2)
11 e=e*10^2;
12 veloci=(molity*e);
13 curden=conduc*e;
14 disp("conductivity = "+string((conduc))+ "second
    per metre");
15 disp("drift velocity = "+string((veloci))+ "metre
    per second");
16 disp("density = "+string((curden))+ "ampere per
    cubic metre");
```

Scilab code Exa 1.3 example 3

```
1 //pagenumber 26 example 3
2 clear
3 ni=2.5*10^13; //per square centimetre
```

```

4 moe=3800//square centimetre/velocity second
5 mo1=1800;//square centimetre/velocity second
6 num=4.51*10^22;//number of atoms
7 q=1.6*10^-19;
8 conduc=ni*q*(moe+mo1);
9 num=num/10^7;
10 impura=(ni^2)/num;
11 ni=5*10^14;
12 condu1=ni*q*moe;
13 disp("conductivity = "+string((conduc))+ "second
per centimetre");
14 disp("conductivity at extent of 1 impurity = "+
string((condu1))+ "second per centimetre");//there
is mistake in book as 3.04s/cm
15 conduc=num*q*mo1;
16 disp("conductivity acceptor to extent of 1 impurity
= "+string((conduc))+ "second per centimetre"
);

```

Scilab code Exa 1.4 example 4

```

1 //pagenumber 27 example 4
2 clear
3 ni=1.5*10^10;//per cubic centimetre
4 moe=1300;//square centimetre/velocity second
5 mo1=500;//square centimetre/velocity second
6 w=5*10^22;//atoms per cubic centimetre
7 q=1.6*10^-19;
8 //(a) conductivity intrinisc at 300kelvin
9 conduc=ni*q*(moe+mo1);//conductivity
10 u=((ni)/(5*10^14));
11 ni=5*10^14;
12 //(b)conductivity when donor atom added to extent of

```

```

    1 impurity
13  condu1=ni*q*moe;
14  disp("conductivity intrinisc at 300kelvin = "+
    string((conduc))+ "second per centimetre");
15  disp("conductivity when donor atom added to extent
    of 1 impurity = "+string((condu1))+ "second
    per centimetre");
16  //conductivity when acceptor added to extent of 1
    impurity
17  conduc=ni*q*mo1;
18  disp("conductivity when acceptor added to extent of
    1 impurity = "+string((conduc))+ "second per
    centimetre");

```

Scilab code Exa 1.5 example 5

```

1  //pagenumber 28 example 5
2  clear
3  ni=2.5*10^13; //per cubic centimetre
4  moe=3800; //square centimetre/velocity second
5  mo1=1800; //square centimetre/velocity second
6  w=4.5*10^22; //atoms per cubic centimetre
7  q=1.6*10^-19;
8  //(1) conductivity intrinisc at 300kelvin
9  conduc=ni*q*(moe+mo1);
10 u=10^6;
11 u=((w)/(u));
12 //(2) conductivity with donor impurity 1
13 condu1=u*q*moe;
14 disp("conductivity intrinisc at 300kelvin = "+
    string((conduc))+ "second per centimetre");
15 disp("conductivity with donor impurity 1 = "+
    string((condu1))+ "second per centimetre");

```

```

16 u=10^7;u=w/u;
17 //(3) conductivity with acceptor impurity 1
18 conduc=u*q*m01;
19 disp("conductivity with acceptor impurity 1 = "+
      string((conduc))+ "second per centimetre");
20 u=0.9*(w/10^6);
21 //(4) conductivity on both
22 conduc=u*q*moe;
23 disp("conductivity on both = "+string((conduc))+
      "second per centimetre");

```

Scilab code Exa 1.6 example 6

```

1 //pagenumber 29 example 6
2 clear
3 ferlev=0.3;//electron volt
4 u=300;//kelvin
5 u1=330;//kelvin
6 ferlev=ferlev*u1/u;
7 disp("fermi = "+string((ferlev))+ "electron volt"
      );
8 disp("fermi below the conduction band");

```

Scilab code Exa 1.7 example 7

```

1 //pagenumber 29 example 7
2 clear
3 ferlev=0.02;//electron volt
4 q=4;//donor impurity added

```

```

5 w=0.025; //electron volt
6 ferlev=-((log(q)-8))/40;
7 disp("fermi    =    "+string((ferlev))+ "electron volt"
      );

```

Scilab code Exa 1.8 example 8

```

1 //pagenumber 30 example 8
2 clear
3 area=1.5*10^-2; //centimetre square
4 w=1.6; //centimetre
5 resist=20; //ohm centimetre
6 durati=60*10^-6; //second in book given as mili
7 quanti=8*10^15; //photons per second
8
9
10 //(1) resistance at each photon gives a electron
    hole pair
11 up=1800; //centimetre square per velocity second
12 un=3800; //centimetre square per velocity second
13 q=1.6*10^-19; //coulomb
14 ni=2.5*10^13; //per cubic centimetre
15 sigma1=1/resist;
16 z1=3800;
17 z=-sigma1/q;
18 u=ni^2/up;
19 n=poly([(z1) z u], 'n');
20 roots(n);
21 n=7.847*10^13; //n>ni taken so it is admissible
22 p1=ni^2/n;
23 volume=w*area;
24 nchang=quanti*durati/volume;
25 pchang=nchang;

```



```

26 sigm11=q*((n+nchang)*un+(pchang+p1)*up);
27 resis1=1/sigm11;
28 r1=resis1*w/area;
29 disp("resistance = "+string((r1))+ "ohm"); //book
    only one resistance has been given

```

Scilab code Exa 1.9 example 9

```

1 //pagenumber 31 example 9
2 clear
3 moe=1350; //square centimetre/velocity second
4 mo1=450; //square centimetre/velocity second
5 ni=1.5*10^10; //per cubic centimetre
6 concn1=ni*(sqrt(mo1/moe)); //concentration
7 concne=((ni^2)/(concn1));
8
9
10 disp("concentration of electron = "+string((
    concn1))+ "per cubic centimetre");
11 disp("concentration of holes = "+string((concne)
    )+"per cubic centimetre");

```

Scilab code Exa 1.10 example 10

```

1 //pagenumber 32 example 10
2 clear
3 resist=0.12; //ohm metre
4 q=1.6*10^-19;

```

```

5 concn1=((1/resist)/(0.048*q)); //concentration of
  hole
6 concne=((1.5*10^16)^(2))/concn1; //concentration of
  electron
7 disp("concentration of hole    =    "+string((concn1))
  +"per cubic centimetre");
8 disp("concentration of electron  =    "+string((
  concne))+ "per cubic centimetre");

```

Scilab code Exa 1.11 example 11

```

1 //pagenumber 32 example 11
2 clear
3 resist=1*10^3; //ohm
4 w=20*10^-6; //wide metre
5 w1=400*10^-6; //long metre
6 mo1=500; //square centimetre/velocity second
7 q=1.6*10^-19;
8 conduc=(resist*w*4*10^-6)/w1;
9 concentration=((1)/(conduc*mo1*q));
10 disp("concentration of acceptor atoms    =    "+string
  ((concentration))+ "per cubic metre"); //correction
  in the book

```

Scilab code Exa 1.12 example 12

```

1 //pagenumber 32 example 12
2 clear
3 w=0.026;

```

```

4 moe=3800; //square centimetre/velocitysecond
5 mo1=1300; //square centimetre/velocitysecond
6 u=(moe*w);
7 u1=(mo1*w);
8 disp("dn constants = "+string((u))+ "square metre
      per second"); //correction in the book
9 disp("dp constants = "+string((u1))+ "square
      metre per second"); //correction in the book

```

Scilab code Exa 1.13 example 13

```

1 //pagenumber 33 example 13
2 clear
3 w=0.026*(3/2)*log(3)/2;
4 disp("distance of fermi level from center = "+
      string((w))+ " electron volt");

```

Scilab code Exa 1.14 example 14

```

1 //pagenumber 33 example 14
2 clear
3 up=1800; //centimetre square per velocity second
4 un=3800; //centimetre square per velocity second
5
6 //(1) resistivity is 45 ohm
7 q=1.6*10^-19; //coulomb
8 ni=2.5*10^13;
9 sigma1=(un+up)*q*ni;
10 resist=1/sigma1;

```

```

11 disp(" resistivity    =    "+string((resist))+ "    ohm
    centimetre");
12 disp(" resistivity equal to 45");
13 //(2) impurity added to extent of 1 atom per 10^9
14 n=4.4*10^22/10^9;
15
16 p1=ni^2/n;
17 sigma1=(n*un+p1*up)*q;
18 resist=1/sigma1;
19
20 disp(" resistivity    =    "+string((resist))+ "    ohm
    centimetre");
21 disp(" resistivity equal to 32.4");

```

Scilab code Exa 1.15 example 15

```

1 //pagenumber 34 example 15
2 clear
3 nd=4*10^14;//atoms per cubic centimetre
4 na=5*10^14;//atoms per cubic centimetre
5 //(1) concentration
6 ni=2.5*10^13;
7 np=ni^2;
8 //p1=n+10^14
9 z=1;
10 z1=10^14;
11 u=-ni^2;
12 n=poly([z z1 u], 'q');
13 roots(n);//n taken as
14 n=1.05*10^4;
15 disp(" concentration of the a free electrons    =    "+
    string((n)));
16 p1=n+10^14;

```

```

17 disp(" concentration of the a free holes = " +
      string((p1)));
18 //(2)
19 disp(" sample p");
20 a=ni^2/(300^3*exp(-(0.785/0.026)));
21 w=400; //kelvin
22 ni=sqrt(a*w^3*exp(-0.786/(8.62*10^-5*w)));
23 ni=((n)*(n+10^14))/10^3;
24 n=ni-0.05*10^15;
25 disp("n = " + string((n)) + " electrons per cubic
      centimetre");
26 p1=n+10^14;
27 disp("p = " + string((p1)) + " holes per cubic
      centimetre");
28
29
30 disp(" essentially intrinsic");

```

Scilab code Exa 1.16 example 16

```

1 //pagenumber 35 example 16
2 clear
3 w=300; //kelvin
4 conduc=300; //ohm centimetre inverse
5 u=1800;
6 p=conduc/(u*1.6*10^-19); //concentration holes
7 n=(2.5*10^13)^2/(p);
8 disp(" concentration of n = " + string((n)) + "
      electrons per cubic centimetre");
9
10 disp(" concentration of holes = " + string((p)) + "
      holes per cubic centimetre");

```

Scilab code Exa 1.17 example 17

```
1 //pagenumber 35 example 17
2 clear
3 nd=10^14; //atoms per cubic centimetre
4 na=5*10^13; //atoms per cubic centimetre
5 un=3800;
6 up=1800;
7 q=1.6*10^-19; //coulomb
8 resist=80; //ohm metre
9 e1=5; //volt per metre
10 w=nd-na;
11 ni=(un+up)*q*resist;
12 p1=poly([1 w -ni^2], 'q');
13 roots(p1); //p1=taken as 3.65*19^12
14 p1=3.65*10^12;
15 n=p1+w;
16 j=(n*un+p1*up)*q*e1;
17 disp("current density = "+string((j))+ " ampere
    per square centimetre");
```

Scilab code Exa 1.18 example 18

```
1 //pagenumber 36 example 18
2 clear
3 na=1*10^16; //per cubic centimetre
    correction in the book
4 ni=1.48*10^10; //per cubic centimetre
```

```

5 un=0.13*10^4;//centimetre square per velocity second
6 u=0.05*10^4;//centimetre square per velocity second
7 n=ni^2/na;
8 q=1/(1.6*10^-19*(un*n+(u*na)));
9 disp("resistivity    =    "+string((q))+ "ohm
centimetre");

```

Scilab code Exa 1.19 example 19

```

1 //pagenumber 37 example 19
2 clear
3 e1=750;//volt per metre
4 b=0.05;//metre square per velocity second
5 un=0.05;//metre square per velocity second
6 up=0.14;//metre square per velocity second
7 //(1) voltage
8 w=1.25*10^-2;//metre
9 v1=e1*w;
10 disp("voltage across sample    =    "+string((v1))+ "
voltage");
11 //(2) drift velocity
12 vd=un*e1;
13 disp("drift velocity    =    "+string((vd))+ "metre per
second");
14 //transverse force per coulomb
15 f1=vd*b;
16 disp("transverse force per coulomb    =    "+string((
f1))+ "newton per coulomb");
17 //(4) transverse electric field
18 e1=vd*b;
19 disp("transverse electric field    =    "+string((e1))
+"voltage per metre");
20 //(5) hall voltage

```

```

21 q=0.9*10^-2;
22 vh=e1*q;
23
24 disp(" hall voltage      =      "+string((vh))+ " volt");

```

Scilab code Exa 1.20 example 20

```

1 //pagenumber 37 example 20
2 clear
3 un=1300;//centimetre square per velocity second
4 //at 300kelvin
5 ni=1.5*10^10;
6 u=500;//centimetre square per velocity second
7 conduc=1.6*10^-19*1.5*10^10*(un+u);
8 q=1/conduc;
9 //impurity of 1 atom included per 10^5 atoms
10 disp(" resistivity at 300kelvin      =      "+string((q))+ "
      ohm centimetre");
11 n=5*10^22/10^5;
12 p=ni^2/n;
13 q=1/(1.6*10^-19*(un*n+(u*p)));
14
15
16 disp(" resistivity at impurity of 1 atom included per
      10^5 atoms      =      "+string((q))+ "ohm centimetre")
      ;

```

Scilab code Exa 1.21 example 21


```

1 //pagenumber 38 example 21
2 clear
3 n=4.4*10^22;
4 nd=n/10^7;
5 w=300; //kelvin
6 nc=4.82*10^15*w^(3/2)/1/sqrt(8);
7 ec_ef1=-0.026*log((nc/(nd)));
8 disp("ec-ef = "+string((ec_ef1)));
9 //(2) impurities included inratio 1 to 10^3
10 n=4.4*10^22;
11 nd=n/(10^3);
12 ec_ef1=-0.026*log(nc/nd);
13 disp("ec-ef = "+string((ec_ef1))+ "electron volt
      ef above ec");
14 q=log10(nd/nc)/log10(10);
15 disp("impurities included per germanium atoms =
      0.0002");

```

Scilab code Exa 1.22 example 22

```

1 //pagenumber 39 example 22
2 clear
3 n=5*10^22; //atoms per cubic centimetre
4 //(1) 1 atom per 10^6
5 m=0.8; //metre
6 na=n/10^6;
7 w=300; //kelvin
8 nv=4.82*10^15*(m)^(3/2)*w^(3/2);
9 ef_ec=0.026*log(nv/na);
10 disp("ef-ec = "+string((ef_ec))+ "electron volt")
    ;
11 //(2) impurity included 10*10^3 per atom
12 na=n/(10*10^3);

```

```

13 ef_ec=0.026*log(nv/na);
14 disp("ef-ec    =    "+string((ef_ec))+ "electron volt")
    ;
15 //(3) condition to concide ec=ef
16 na=4.81*10^15;
17 w=(nv/na)^(2/3);
18 disp("temperature    =    "+string((w))+ "kelvin");//
    correction in the book

```

Scilab code Exa 1.23 example 23

```

1 //pagenumber 40 example 23 //figure is not given in
    the book
2 clear
3 nd=10^7;//per cubic centimetre
4 na=10^17;//per cubic centimetre
5 voltag=0.1*3800*10^-4*1500*3*10^-3;
6 disp("hall voltage    =    "+string((voltag))+ "volt");
7 disp("remains the same but there change in polarity"
    );

```

Scilab code Exa 1.24 example 24

```

1 //pagenumber example 24
2 clear
3 vh=60*10^-3;//volt
4 w=6*10^-3;//metre
5 bz=0.1;//weber per metre square
6 i1=10*10^-6;//ampere

```

```
7 resist=300000*10^-2; //ohm metre
8 //(1)
9 //mobility
10 rh=vh*w/(bz*i1);
11 u1=rh/resist;
12 disp("mobilty = "+string((u1))+ "metre square per
      velocity second");
```

Chapter 2

Semiconductor Diodes

Scilab code Exa 2.1 example 1

```
1 //pagenumber 99 example 1
2 clear
3 q=0.01; //centimetre
4 sigma1=1; //ohm centimetre inverse
5 q1=0.01; //centimetre
6 sigm11=0.01; //ohm centimetre inverse
7 iratio=(0.0224^2*2.11*20)*3.6^2/((3.11*(4.3^2*10^-6)
      ^2*2.6*20*10^3));
8 for q=1:2
9     if q==1 then
10         un=3800;
11         up=1500;
12         q=1.6*10^-19;
13         ni=2.5*10;
14     else
15         q=1.6*10^-19;
16         up=500
17         un=1300;
18         ni=1.5*10
```

```

19 end
20
21     b=un/up;
22     sigmai=(un+up)*q*ni;
23 end
24 disp("ratio of reverse saturation current = " +
      string((iratio))); //correction in the book

```

Scilab code Exa 2.2 example 2

```

1 //pagenumber 100 example 2
2 clear
3 sigma1=0.01; //ohm centimetre inverse
4 area1=4*10^-3; //metre square
5 q=0.01*10^-2; //metre
6 un=1300;
7 up=500;
8 ni=1.5*10^15; //per cubic centimetre
9 sigma1=(un+up)*1.6*10^-19*ni;
10 iratio=(4*10^-10*0.026*sigma1^2*2.6*2/10^-4)/3.6^2;
11 disp("reverse current ratio = " + string((iratio))
      ); //correction in the book

```

Scilab code Exa 2.3 example 3

```

1 //pagenumber 100 example 3
2 clear
3 a=4*10^-4; //metre square
4 sigmap=1;

```

```

5 sigman=0.1;
6 de=0.15;
7 vtem=26*10^-3;
8 i=(a*vtem*((2.11)*(0.224))/((3.22)^(2)))*((1/de*
    sigman)+(1/de*sigmap));
9 disp("reverse saturation current = "+string(i)+"
    ampere"); //correction in the book

```

Scilab code Exa 2.4 example 4

```

1 //pagenumber 101 example 4
2 clear
3 w=0.9;
4 voltaf=0.05; // volt
5 revcur=10*10^-6; //ampere
6 //(1) voltage
7 volrev=0.026*(log((-w+1))); //voltage at which the
    reverse saturation current at saturate
8 resacu=((exp(voltaf/0.026)-1)/((exp(-voltaf/0.026)
    -1))); //reverse saturation current
9 disp("voltage at which the reverse saturation
    current at saturate = "+string((volrev))+
    " volt");
10 disp("reverse saturation current = "+string((
    resacu))+ " ampere");
11 u=0.1;
12 for q=1:3
13     reverc=revcur*(exp((u/0.026))-1)
14     disp("reverse saturation current "+string((u
        ))+" = "+string((revert))+ " ampere");
15     u=u+0.1;
16 end

```

Scilab code Exa 2.6 example 6

```
1 //pagenumber 103 example 6
2 clear
3 a=1*10^-6; //metre square
4 w=2*10^-6; //thick centimetre
5 re=16;
6 eo=8.854*10^-12;
7 c=(eo*re*a)/w;
8 disp(" capacitance = "+string(c)+" farad");
```

Scilab code Exa 2.7 example 7

```
1 //pagenumber 105 example 7
2 volbar=0.2; //barrier voltage for germanium volt
3 na=3*10^20; //atoms per metre
4 //(1) width of depletion layer at 10 and 0.1 volt
5
6 for q=[-10 -0.1 0.1]
7     w=2.42*10^-6*sqrt((0.2-(q)));
8     disp(" width of depletion layer at "+string((q))+
9         " = "+string((w))+ "metre"); //for -0.1 volt
10        correction in the book
11 end
12 //(d) capacitance
13 for q=[-10 -0.1]
14     capaci=0.05*10^-9/sqrt(0.2-q);
```

```
13     disp(" capacitance at "+string((q))+ " = " +
        string((capaci))+ " farad");
14 end
```

Scilab code Exa 2.8 example 8

```
1 //pagenumber 104 example 8
2 clear
3 p=2; //watts
4 voltaf=900*10^-3; //volt
5 i1=p/voltaf;
6 r1=voltaf/i1;
7 disp("maximum forward current = "+string(i1)+"
    ampere");
8
9
10 disp("forward diode resistance = "+string(r1)+"
    ohm");
```

Scilab code Exa 2.11 example 11

```
1 //pagenumber 108 example 11
2 clear
3 r=250; //ohm
4 c=40*10^-6; //farad
5 alpha1=180-atan(377*r*c);
6 disp("alpha = "+string(alpha1)+" degree");
```

Scilab code Exa 2.12 example 12

```
1 //pagenumber 109 example 12
2 clear
3 i1=0.1; //current in ampere
4 vms=40; //rms voltage in volts
5 c=40*10^-6; //capacitance in farad
6 r1=50; //resistance in ohms
7 ripple=0.0001;
8 induct=((1.76/c)*sqrt(0.472/ripple)); //inductance
9 outv=(2*sqrt(2)*vms)/3.14-i1*r1; //output voltage
10 disp("inductance    =    "+string(induct)+" henry"); //
    correction in the book
11 disp("output voltage    =    "+string(outv)+" volt");
```

Scilab code Exa 2.14 example 14

```
1 //pagenumber 109 example 14
2 clear
3 voltag=40; //voltage
4 i1=0.2; //ampere
5 c1=40*10^-6; //farad
6 c2=c1;
7 induct=2; //henry
8 //(1) ripple
9 vdc=2*sqrt(2)*voltag/3.14;
10 r1=vdc/i1;
11 induc1=r1/1130;
```

```

12 v1=voltag/(3*3.14^3*120^2*4*induct*c1);
13 disp(" ripple voltage    =    "+string((v1))+ " volt");
14 //(2) with two filter
15 v1=4*voltag/((3*3.14^5)*(16*120^2*induct^2*c1^2));
16 disp(" ripple voltage including filters    =    "+
      string((v1))+ " volt"); //correction in the book
17 //(3) ripple voltage
18 v1=4*voltag/(5*3.14*1.414*2*3.14*240*240*3.14*induct
      *c1);
19 v1=v1/20;
20 disp(" ripple voltage    =    "+string((v1))+ " volt");

```

Scilab code Exa 2.15 example 15

```

1 //pagenumber 111 example 15
2 clear
3 voltag=375; // volt
4 r1=2000; //ohm
5 induct=20; //henry
6 c1=16*10^-6; //farad
7 r11=100; //ohm
8 r=200; //ohm
9 //(1) voltage and ripple with load
10 disp(" voltage and ripple with load");
11 r=r+r11+400;
12 vdc=((2*sqrt(2)*voltag/3.14))/1.35;
13 ripple=r1/(3*sqrt(2)*(377)*induct*2);
14 disp(" vdc    =    "+string((vdc))+ " volt");
15 disp(" ripple    =    "+string((ripple)));
16 //(2) capacitance connected across load
17 disp(" capacitance connected across load");
18 vdc=sqrt(2)*voltag/(1+1/(4*(60)*r1*2*c1));
19 ripple=1/(4*sqrt(3)*(60)*r1*2*c1);

```

```

20 disp("vdc = "+string((vdc))+ " volt");
21 disp("ripple = "+string((ripple)));
22 //(3) filter containing two inductors and capacitors
    in parallel
23 disp("filter containing two inductors and capacitors
    in parallel");
24 vdc=250;//volt
25 ripple=0.83*10^-6/(2*induct*2*c1);//correction in
    the book
26 disp("vdc = "+string((vdc))+ " volt");
27 disp("ripple = "+string((ripple)));
28 //(4) two filter
29 disp("two filter");
30 vdc=250;
31 ripple=sqrt(2)/(3*16*3.14^2*60^2*induct*c1)^2;//
    correction in the book
32 disp("vdc = "+string((vdc))+ " volt");
33 disp("ripple = "+string((ripple)));
34 vdc=sqrt(2)*voltage/(1+(4170/(r1*16))+(r/r1));
35 ripple=3300/(16^2*2*20*r1);
36 disp("vdc = "+string((vdc))+ " volt");
37 disp("ripple = "+string((ripple)));

```

Scilab code Exa 2.16 example 16

```

1 //pagenumber 112 example 16
2 clear
3 capaci=4;//farad
4 induct=20;//henry
5 i1=50*10^-3;//ampere
6 resist=200;//ohm
7 maxvol=300*sqrt(2);
8 vdc=maxvol-((4170/capaci)*(i1))-(i1*resist);

```

```

9 ripple=(3300*i1)/((capaci^2)*(induct)*353);
10 disp(" output voltage    =    "+string((vdc))+ " volt");
11 disp(" ripple voltage    =    "+string((ripple)));

```

Scilab code Exa 2.17 example 17

```

1 //pagenumber 113 example 17
2 clear
3 voltag=25; // volt
4 c1=10*10^-6; //farad
5 i1=100*10^-3; //ampere
6 ripple=0.001;
7 w=754; //radians
8 //(1) inductance and resistance
9
10
11 r1=voltag/i1;
12 induct=40/(sqrt(2)*w^2*(c1));
13 disp(" inductance of filter    =    "+string((induct))+
      " henry"); //correction in the book
14 disp(" resistance of filter    =    "+string((r1))+ " ohm
      ");

```

Scilab code Exa 2.18 example 18

```

1 //pagenumber 113 example 18
2 clear
3 resacu=0.1*10^-12; //ampere
4 u=20+273; //kelvin

```

```

5 voltaf=0.55; // volt
6 w=1.38*10^-23;
7 q=1.6*10^-19;
8 for z=1:2
9     if z==2 then
10         u=100+273;
11         disp("current at 100celsius rise");
12     end
13     voltag=w*u/q;
14     i1=(10^-13)*(exp((voltaf/voltag))-1);
15     if z==2 then
16         i1=(256*10^-13)*((exp(voltaf/voltag)-1));
17     end
18     disp("current    =    "+string((i1))+ " ampere");
19 end

```

Scilab code Exa 2.19 example 19

```

1 //pagenumber 114 example 19
2 clear
3 na=10*22; //atoms per cubic metre
4 nd=1.2*10^21; //donor per cubic metre
5 voltag=1.38*10^-23*(273+298)/(1.6*10^-19); //
   correction in the book
6 voltag=0.026;
7 ni=1.5*10^16;
8 ni=ni^2;
9 v1=voltag*log((na*nd)/(ni));
10 disp("thermal voltage    =    "+string((voltag))+ " volt
   ");
11 disp("barrier voltage    =    "+string(abs(v1))+ " volt"
   ); //correction in the book

```

Scilab code Exa 2.20 example 20

```
1 //pagenumber 114 example 20
2 clear
3 i1=2*10^-7; //ampere
4 voltag=0.026; //voltage
5 i=i1*((exp(0.1/voltag)-1));
6 disp("current = "+string((i))+ " ampere");
```

Scilab code Exa 2.21 example 21

```
1 //pagenumber 115 example 21
2 clear
3 resacu=1*10^-6; //ampere
4 voltaf=150*10^-3; //voltage
5 w=8.62*10^-5;
6 voltag=0.026; //voltage
7 u=300; //kelvin
8 uw=u*w;
9 resist=(uw)/((resacu)*exp(voltaf/voltag));
10 disp("resistance at 150mvolt = "+string((resist)
    )+"ohm"); //correction in the book
```

Scilab code Exa 2.22 example 22

```

1 //pagenumber 115 example 22
2 clear
3 dopfac=1000;
4 w=300; //kelvin
5 q=0.026*log(dopfac);
6 disp("change in barrier    =    "+string((q))+ " volt");

```

Scilab code Exa 2.23 example 23

```

1 //pagenumber 116 example 23
2 clear
3 area12=1*10^-8; //metre square
4 volre1=-1; //reverse voltage
5 capac1=5*10^-12; //farad
6 volbu1=0.9; //voltage
7 voltag=0.5; //voltage
8 i1=10*10^-3; //ampere
9 durmin=1*10^-6; //ssecond
10 //(1) capacitance
11 capac1=capac1*sqrt((volre1-volbu1)/(voltag-volbu1));
12 disp("depletion capacitance    =    "+string((capac1))
      +" farad");
13 //(2) capacitance
14 capac1=i1*durmin/(0.026);
15
16 disp("capacitance    =    "+string((capac1))+ " farad");

```

Scilab code Exa 2.24 example 24

```

1 //pagenumber 116 example 24
2 quantg=4*10^22;//atoms per cubic centimetre
3 quants=5*10^22;//atoms per cubic centimetre
4 w=2.5*10^13;//per cubic centimetre
5 w1=1.5*10^10;//per cubic centimetre
6 for q=[quantg quants]
7     na=2*q/(10^8);
8     nd=500*na;
9     if q==quantg then
10         w=w;
11         voltag=0.026*log(na*nd/w^2);
12         disp("potential germanium = "+string((
            voltag))+ " volt");
13     end
14     if q==quants then
15         w=w1;
16         voltag=0.026*log(na*nd/w^2);
17         disp("potential silicon = "+string((
            voltag))+ " volt");
18     end
19
20 end

```

Scilab code Exa 2.25 example 25

```

1 //pagenumber 117 example 25
2 clear
3 u=0.05;//metre square per velocity second correction
   in the book
4 un=0.13;//metre square per velocity second
5 condun=20;//second per metre conductivity of n
   region
6 condup=1000;//second per metre conductivity of p

```



```
    region
7  p=condup/(1.6*10^-19*u);
8  no=condun/(1.6*10^-19*un);
9  disp("electrons density    =    "+string((no))+ " per
    cubic metre");
10 disp("holes density    =    "+string((p))+ " per cubic
    metre"); //others to find is not in the book
```

Chapter 3

special semiconductor diodes

Scilab code Exa 3.1 example 1

```
1 //pagenumber 138 example 1
2 clear
3 //zener diode
4 voltag=5.2;//volts
5 w=260*10^-3;//watts
6 appv=15;//voltsw1=50;//watts
7 imax=w/voltag*0.1;
8 //to maitain a constant voltage
9 imax1=(w/voltag)-imax;
10 resmin=(appv-voltag)/(w/voltag);
11 resmax=(appv-voltag)/imax1;
12 //load 50
13 resmax1=((9.8)/(45*10^-3))-50;
14 resmin1=((9.8)/(50*10^-3))-50;
15 res50=resmax1-resmin1;
16 disp("resistance range from "+string(resmin)+" to "+
       string(resmax)+"ohms");
17 disp("resistance range at 50 from "+string(resmin1)+
       " to "+string(resmax1)+"ohms");
```

Scilab code Exa 3.2 example 2

```
1 //pagenumber 139 example 2
2 clear
3 i1=20*10^-3;//ampere
4 i=30*10^-3;//ampere
5 v1=5.6;//volts
6 v=5.65;//volts
7 //condition
8 u=35*10^-3;//ampere
9 voltag=5*u+5.5;
10 disp("voltage drop = "+string(voltag)+" volts");
```

Scilab code Exa 3.3 example 3

```
1 //example 3 pagenumber 139
2 clear
3 v=4.3;//volt
4 q=4;//volt
5 dop=10^17;//per cubic centimetre
6 fi0=0.254*log(dop/(5.1*10^10));
7 fi01=0.407+q+0.55;
8 disp('fi0 = '+string(fi01));
```

Scilab code Exa 3.4 example 4

```
1 //example 4 pagenumber 140
2 clear
3 v1=20; // volt
4 i1=((v1)/(200+1))*10^-3;
5 disp('current = '+string(i1)+' ampere ');
6 //greater than 20
7 vone=16;
8 r=vone/i1;
9 r1=r-1*10^3;
10 r11=200*10^3-r1;
11 disp('resistance = '+string(r)+' ohm ');
12 disp("r1 = "+string((r1))+ "ohm");
13 disp("r2 = "+string((r11))+ "ohm");
```

Scilab code Exa 3.6 example 6

```
1 //example 6 pagenumber 142
2 clear
3 v1=150; // volt
4 vone=300 // volt
5 idmax=40*10^-3; // ampere
6 idmin=5*10^-3; // ampere
7 r=(vone-v1)/idmax;
8 imax=idmax-idmin;
9 disp('maximum current = '+string(imax)+' ampere ')
   ;
10 //minimum
11 zq=1;
12 while (zq<=2)
13     if zq==1 then
14         ione=25*10^-3;
```

```

15         i1=i0ne+idmin;
16         vmin=(i1*r)+v1;
17         disp('v1 minimum    =    '+string(vmin)+' volt '
18             );
19         else
20         i0ne=25*10^-3;
21         i1=i0ne+idmax;
22         vmin=(i1*r)+v1;
23         disp('v1 maximum    =    '+string(vmin)+' volt '
24             );
25     end
26     zq=zq+1;
27
28
29
30 end

```

Scilab code Exa 3.7 example 7

```

1 //example 7 pagenumber 142
2 clear
3 q=4.5*10^22; //atoms per cubic metre
4 na=q/(10^4);
5 eo=0.026*24.16;
6 e=1.6*10^-19;
7 W=sqrt((4*16*0.628)/(36*3.14*10^9*na*10^6*e));
8 disp('width    =    '+string(W)+' metre ');

```

Chapter 4

Bipolar Junction Transistor

Scilab code Exa 4.1 example 1

```
1 //page number 201 example 1
2 clear
3 alpha=0.98;
4 vbe=0.7;//base emitter voltage volt
5 ie=-4*10^-3;//emitter current
6 vc=12;//colector voltage volt
7 colr=3.3*10^3;//ohms
8 colCurrent=ie*(-alpha);
9 baseCurrent=0.02*ie;
10 vbn=vbe+(-4*10^-3*100);
11 i2=-vbn/(10*10^3);
12 i1=-(baseCurrent+i2);
13 vcn=(vc-((colCurrent+i1)*colr));
14 v1=vcn-0.9;
15 r1=v1/i1;
16 disp(" r1    =    "+string(abs(r1))+ "ohm");
```

Scilab code Exa 4.2 example 2

```
1 //pagenumber 202 example 2
2 clear
3 colvoltage=12; // volts
4 vbe=5; // volts
5 colcur=10*10^-3; // ampere
6 vce=5; // volts
7 beta1=50;
8 ib=colcur/beta1;
9 rb=(vbe-0.7)/ib;
10 rc=(12-vbe)/colcur;
11 //when 100ohm included
12 disp("rb = "+string(rb)+"ohm");
13 disp("rc = "+string(rc)+"ohm");
14 rb=(vce-0.7-(colcur+ib)*beta1)/ib;
15
16 disp("rb at emitter resistance 100ohm = "+string
      (rb)+"ohm"); //correction in the book
```

Scilab code Exa 4.5 example 5

```
1 //pagenumber 205 example 5
2 clear
3 //given
4 reveri=2*10^-6; //ampere at 25
5 icb=2*10^-6*2^5; //ampere at 75
6 basevoltage=5; // volt
```

```

7 // (1)
8 rb=(-0.1+basevoltage)/(icb);
9 disp("max resistance = "+string((rb))+ "ohm"); //
    correction in the book
10 // (2)
11 basevoltage=1;
12 rb=100*10^3;
13 reveri=(-0.1+basevoltage)/rb;
14 q=reveri/(2*10^-6);
15 w=q^10;
16 u=log(w)
17 t=25+(u/log((2)));
18 disp(" baseresistance = "+string((rb))+ "ohm");
19 disp(" temperature = "+string((t))+ "celsius");

```

Scilab code Exa 4.6 example 6

```

1 //pagenumber 205 example 6
2 clear
3 //given
4 vbe=0.8; //voltage
5 beta1=100;
6 vce=0.2; //voltage
7 rb=200*10^3; //ohm
8 bascur=(6-vbe)/rb;
9 colres=(10-vce)/(beta1*bascur);
10 disp("min resistance = "+string((colres))+ "ohm")
    ;

```

Scilab code Exa 4.7 example 7

```
1 //pagenumber 206 example 7
2 clear
3 beta1=100;
4 colres=3*10^3; //collector resistance //ohm
5 rb=8*10^3; //ohm
6 r1=500; //ohm
7 voltag=5; //voltage
8 //(1)
9 ib=(-voltage+0.7)/((1+beta1)*r1+(rb));
10 ic=beta1*ib;
11 vce=(-10-ic*(colres)+r1*(ib+ic));
12 vcb=vce+0.7;
13 //(2)
14 volmin=-0.2+abs(ib+ic)*r1;
15 re=-(0.7+rb*ib+voltage)/((1+(beta1))*ib);
16 disp("in saturation mode")
17 disp("vo = "+string((volmin))+ " volt");//
    correction in the book
18 disp("emitter resistance < "+string((re))+ "ohm")
    ;
```

Scilab code Exa 4.9 example 9

```
1 //example 9
2 clear
3 vcc=12; //voltage
4 rb=12*10^3; //ohm
5 colres=2*10^3; //ohm
6 beta1=100;
7 vb=0.7; //voltage
8 vce=0.1; //voltage
```

```

9
10 for q=1:2
11     if q==1 then
12         vbb=1;
13     else
14         vbb=12;
15     end
16     ib=(vbb-vb)/rb;
17     ic=beta1*ib;
18     ie=ic+ib;
19     vce=vcc-ic*colres;
20     if q==2 then
21         ic=(vcc-0.1)/colres;
22     end
23
24     disp("the operating point at vbb = "+string
          ((vbb))+ " volt ic = "+string((ic))+ " ampere
          vce = "+string((vce))+ " volt");
25 end
26 beta1=ic/ib;
27
28 disp("beta at saturation = "+string((beta1)));

```

Scilab code Exa 4.10 example 10

```

1 //example 10
2 clear
3
4
5
6 disp("rb/re<<1");

```

Scilab code Exa 4.11 example 11

```
1 //example 11
2 clear
3 vbe=0.65; // volt
4 colres=2*10^3; //ohm
5 voltag=10; // volt
6 i1=voltag/10;
7 q=(1.65-vbe)/(1*10^3);
8
9
10 disp(" current    =    "+string((q))+ " ampere");
```

Scilab code Exa 4.12 example 12

```
1 //example 12
2 clear
3 vcc=12; // volt
4 r1=10*10^3; //ohm
5 colres=1*10^3; //ohm
6 re=5*10^3; //ohm
7 rb=5*10^3; //ohm
8 beta1=100;
9 vbe=0.7; // volt
10 basvol=vcc*10/20;
11 ib=((basvol-vbe)/(rb+beta1*rb));
12 ic=beta1*ib;
13 vce=vcc-ic*(colres+re);
```

```
14 disp(" vce    =    "+string((vce))+ " volt");
15 disp(" collector current    =    "+string((ic))+ " ampere
    ");
```

Scilab code Exa 4.13 example 13

```
1 //example 13
2 clear
3 colres=330; //ohm
4 re=0.1*10^3; //ohm
5 vcc=12; //voltage
6 vce=0.2; //voltage
7 revcur=18*10^-3 //ampere
8 ib=0.3*10^-3; //ampere
9 stability=10;
10 beta1=100;
11 colres=0.330; //ohm
12 re=0.1*10^3; //ohm
13 vbe=0.2;
14 rb=((1+beta1)*re)/10-((1+beta1)*re)/(1-10.1);
15 vb=2+ib*rb;
16 w=vcc/vb;
17 q=w-1;
18 r1=1.2*10^3;
19 r=q*1.2*10^3;
20 disp(" r1    =    "+string((q))+ " times r2");
21 disp(" if r2 is 1200ohm");
22 disp(" r1    =    "+string((r))+ "ohm");
23
24 disp(" r2    =    "+string((r1))+ "ohm");
```

Scilab code Exa 4.14 example 14

```
1 //example 14
2 clear
3 alpha1=0.99;
4 ib=25*10^-6; //ampere
5 icb=200*10^-9; //ampere
6 beta1=alpha1/(1-alpha1);
7 ic=beta1*ib+(beta1+1)*icb;
8 disp("collector current = "+string((ic))+ " ampere
    ");
9 ie1=(ic-icb)/alpha1;
10 disp("emitter current = "+string((ie1))+ " ampere"
    );
11 ic=beta1*ib;
12 disp("collector current with ib = "+string((ic))
    + " ampere");
13 ie=ic/alpha1;
14 disp("emitter current = "+string((ie))+ " ampere")
    ;
15 w=(ie1-ie)/ie1;
16 disp("error = "+string((w)));
```

Scilab code Exa 4.15 example 15

```
1 //example 15
2 clear
3 vcc=26; //voltage
```

```

4 colres=20*103; //ohm
5 re=470; //ohm
6 beta1=45;
7 vce=8; //voltage
8 ib=(vcc-vce)/((1+beta1)*(colres+re));
9 ic=beta1*ib;
10 r1=((vcc-colres*(ib+ic)-re*(ib+ic)-(0.7)))/ib;
11 disp("resistance = "+string((r1))+ "ohm");
12 stability=(1+beta1)/(1+(beta1*re)/(re+colres));
13 disp("stability = "+string((stability))); //
    correction in the book

```

Scilab code Exa 4.16 example 16

```

1 //example 16
2 clear
3 vcc=1.5 //voltage in book should be changed as 1.5
4 colres=1.5*103; //ohm
5 emresi=0.27*103; //ohm
6 r1=2.7*103; //ohm
7 r=2.7*103; //ohm
8 beta1=45;
9 basre1=690; //ohm
10 voltag=r*vcc/(r+r1);
11 basres=(r*r1)/(r+r1);
12 vbe=0.2;
13 for q= 1:2
14     if q==2 then
15         disp("resistance = "+string((basre1))+
            "ohm");
16         basres=basres+basre1;
17     end
18     bascur=(((voltag+vbe)))/(basres+(45*(emresi)));

```

```

19     colcur=beta1*bascur;
20     vce=(vcc+colcur*colres+(bascur+colcur)*emresi);
21     disp(" current    =    "+string((colcur))+ " ampere")
        ;
22     disp(" vce      =    "+string((vce))+ " volt");
23 end

```

Scilab code Exa 4.17 example 17

```

1 //example 17
2 clear
3 beta1=25;
4 colres=2.5*10^3; //ohm
5 vcc=10; // volt
6 vce=-5; // volt
7 ic=-(vcc+vce)/colres;
8 ib=ic/beta1;
9 rb=vce/ib;
10 stability=(1+beta1)/((1+beta1)*((colres)/(colres+rb)
    ));
11 disp(" base resistance    =    "+string((rb))+ "ohm"); //
    correction in book
12 disp(" stability      =    "+string((stability)));

```

Scilab code Exa 4.18 example 18

```

1 //example 18
2 clear
3 therre=8; //celsius per watts

```

```

4 tepera=27; //celsius ambient temperature
5 potran=3; //watt
6 tejunc=tepera+(therre*potran);
7 disp("junction temperature = "+string((tejunc))+
      "celsius");

```

Scilab code Exa 4.19 example 19

```

1 //example.19
2 clear
3 ambtep=40; //celsius
4 juntep=160; //celsius
5 hs_a=8;
6 j_c=5;
7 c_a=85;
8 j_a=(j_c)+(c_a*hs_a)/(c_a+hs_a);
9 podiss=(juntep-ambtep)/j_a;
10 disp("dissipation = "+string((podiss))+ "watt");

```

Scilab code Exa 4.21 example 21

```

1 //example 21
2 clear
3 emicur=1*10^-3; //ampere
4 colcur=0.995*10^-3; //ampere
5 alpha1=colcur/emicur;
6 beta1=alpha1/(1-alpha1);
7 disp("alpha = "+string((alpha1)));
8 disp("beta = "+string((beta1)));

```

Scilab code Exa 4.22 example 22

```
1 //example 22
2 clear
3 beta1=100;
4 alpha1=beta1/(beta1+1);
5
6 disp("alpha    =    "+string((alpha1)));
```

Scilab code Exa 4.23 example 23

```
1 //example .23
2 rb=200*10^3;//ohm
3 rc=2*10^3;//ohm
4 vcc=20;//voltage
5 ib=(vcc)/(rb+200*rc);
6 ic=200*ib;
7 disp("ic    =    "+string((ic))+ " ampere"); //correction
    in book
```

Scilab code Exa 4.24 example 24

```
1 //example 24
```

```

2 clear
3 alpha1=0.98;
4 revcur=1*10^-6; //ampere
5 emicur=1*10^-3; //ampere
6 colcur=alpha1*emicur+revcur;
7 bascur=emicur-colcur;
8 disp(" collector current    =    "+string((colcur))+
      ampere");
9 disp(" base current    =    "+string((bascur))+
      ampere"
      ");

```

Scilab code Exa 4.25 example 25

```

1 //example 25
2 clear
3 colcur=100*10^-3; //ampere
4 ouresi=20; //ohm
5 r=200; //ohm
6 r1=100; //ohm
7 vcc=15; //voltage
8 basvol=((r1)/(r+r1))*vcc;
9 em1res=basvol/colcur;
10 vce=vcc-(ouresi+em1res)*colcur;
11 disp(" vce    =    "+string((vce))+
      " volt");
12 disp(" emitter resistance    =    "+string((em1res))+
      ohm");

```

Scilab code Exa 4.26 example 26

```

1 //example 26
2 colres=1*10^3; //ohm
3 beta1=50;
4 vbe=0.3; // volt
5 vcc=6; // volt
6 rb=10*10^3; //ohm
7 re=100; //ohm
8 em1cur=((vcc-vbe)*(beta1+1))/((rb+((beta1+1)*re)));
9 for q=1:2
10     if q==2 then
11         colres=1*10^3;
12         vce=vcc-(colres+re)*em1cur;
13         ic=vcc/(colres+re);
14         disp(" collector to emitter    =    "+string((
15             vce))+ " volt");
16         disp(" collector current      =    "+string((ic))
17             +" ampere");
18     end
19     if q==1 then
20         colres=50;
21         rb=100;
22         vce=vcc-(colres+rb)*em1cur;
23         disp(" emitter current      =    "+string((em1cur
24             ))+" ampere");
25         disp(" collector to emitter    =    "+string((
26             vce))+ " volt");
27     end
28 end

```

Scilab code Exa 4.27 example 27

```

1 //example 27
2 clear

```

```

3  beta1=99;
4  stability=5;
5  vbe=0.2; //voltage
6  colres=2.5*10^3; //ohm
7  vce=6; //voltage
8  ven=5.5; //voltage
9  vcc=15; //voltage
10 vcn=vce+ven;
11 colvol=vcc-vcn; //voltage across collector resistance
12 ic=colvol/colres;
13 ib=ic/beta1;
14 colre1=ven/ic;
15 rb=stability*colre1/(1-(stability/(1+beta1))); //
    correction in the book taken collector resistance
    as 3.13*10^3ohm but it is 3.93*10^3ohm
16 v1=(ib*rb)+(vbe)+((ib+ic)*colre1);
17 r=rb*vcc/v1;
18 r1=r*v1/(vcc-v1);
19 disp("resistance    =    "+string((colre1))+ "ohm");
20 disp("resistance r1    =    "+string((r))+ "ohm");
21 disp("resistance r2    =    "+string((r1))+ "ohm");

```

Scilab code Exa 4.28 example 28

```

1  //example 28
2  clear
3  beta1=50;
4  vbb=5; //voltage
5  rb=10*10^3; //ohm
6  colres=800; //ohm
7  re=1.8*10^3; //ohm
8  vcc=5; //voltage
9  ib=(0.7-vbb)/((rb)+(beta1+1)*re); //correction in

```

```

    book
10 re=beta1*ib;
11 ie=(ib+re);
12 vce=vcc-colres*re-re*ie;
13 vcb=(vce-0.7);
14 disp("base current    =    "+string((ib))+ " ampere");
15 disp("collector current =    "+string((re))+ " ampere
    ");
16 disp("emitter current  =    "+string((ie))+ " ampere")
    ;
17 disp("vcb    =    "+string((vcb))+ " volt"); // correction
    in book
18 disp("the collector base junction is reverse biased
    the transistor in active region");

```

Scilab code Exa 4.29 example 29

```

1 //example 29
2 clear
3 r=40*10^3; //ohm
4 r1=5*10^3; //ohm
5 colres=r1;
6 beta1=50;
7 em1res=1*10^3; //ohm
8 vcc=12; //voltage
9 rth=r*r1/(r+r1);
10 v1=r1*vcc/(r1+r);
11 bascur=(v1-0.3)/(rth+(beta1*em1res));
12 colcur=beta1*bascur;
13 vce=vcc-(colres+em1res)*colcur;
14 disp("collector current    =    "+string((colcur))+ "
    ampere");
15 disp("collector emitter voltage    =    "+string((vce))

```

```
)+" volt");
```

Scilab code Exa 4.30 example 30

```
1 //example 30
2 colcur=8*10^-3; //ampere
3 re=500; //ohm
4 vce=3; //voltage
5 beta1=80;
6 vcc=9; //voltage
7 ib=colcur/beta1;
8 rb=(vcc-(1+beta1)*(ib*re))/ib;
9 disp(" base resistance = "+string((rb))+ "ohm");
```

Scilab code Exa 4.31 example 31

```
1 //example 31
2 clear
3 vcc=10; //voltage
4 basres=1*10^6; //ohm
5 colres=2*10^3; //ohm
6 em1res=1*10^3; //ohm
7 beta1=100;
8 bascur=vcc/(basres+(beta1+1)*(em1res));
9 colcur=beta1*bascur;
10 em1cur=colcur+bascur;
11 disp(" base current = "+string((bascur))+ " ampere"
    );
```

```
12 disp(" collector current    =    "+string((colcur))+  
    ampere"); //correction in book  
13 disp(" emitter current    =    "+string((em1cur))+  
    ampere"); //correction in book
```

Scilab code Exa 4.32 example 32

```
1 //example 32  
2 alpha1=0.99;  
3 rebacu=1*10^-11; //ampere  
4 colres=2*10^3; //ohm  
5 vcc=10; //voltage  
6 bascur=20*10^-6; //ampere  
7 beta1=alpha1/(1-alpha1);  
8 i1=(1+beta1)*rebacu;  
9 colcur=beta1*bascur+i1;  
10 em1cur=-(bascur+colcur);  
11 vcb=vcc-colcur*colres;  
12 vce=vcb-0.7;  
13 disp(" collector current    =    "+string((colcur))+  
    ampere");  
14 disp(" emitter current    =    "+string((em1cur))+  
    ampere");  
15 disp(" collector emitter voltage    =    "+string((vce)  
    )+" volt");
```

Scilab code Exa 4.33 example 33

```
1 //pagenumber 220 example 33
```

```

2 clear
3 beta1=100;
4 revcur=20*10^-9; //ampere
5 colres=3*10^3; //ohm
6 rb=200*10^3; //ohm
7 vbb=5; //voltage
8 vcc=11; //voltage
9 em1res=2*10^3; //ohm
10 ib=(vbb-0.7)/rb;
11 ic=beta1*ib;
12 ie=ib+ic;
13 disp("base current = "+string((ib))+ " ampere");
14 disp("collector current = "+string((ic))+ " ampere
    ");
15 disp("emitter current = "+string((ie))+ " ampere")
    ;//question asked only currents
16 //2*10^3 ohm added to emitter
17 ib=- (0.7-vcc)/(rb+((1+beta1)*em1res));
18 ic=beta1*ib;
19 ie=ib+ic;
20 disp("base current = "+string((ib))+ " ampere");//
    correction in book
21 disp("collector current = "+string((ic))+ " ampere
    ");
22 disp("emitter current = "+string((ie))+ " ampere")
    ;//question asked only currents

```

Scilab code Exa 4.34 example 34

```

1 //pagenumber 221 example 34
2 clear
3 em1cur=2*10^-3; //ampere
4 v1=12; //voltage

```



```

5 vcc=12; // volt
6 format(12);
7 colres=5*10^3; //ohm
8 em1res=v1/em1cur;
9 colcur=em1cur;
10 voltag=colcur*colres; //ic*r
11 v1=vcc-(colres*colcur);
12 disp(" emitter current    =    "+string((em1cur))+
      " ampere");
13 disp(" collector current   =    "+string((colcur))+
      " ampere");
14 disp(" voltage           =    "+string((voltag))+ " volt");
15 disp(" vcb              =    "+string(abs(v1))+ " volt");
16 disp(" emitter resistance  =    "+string((em1res))+
      " ohm");

```

Scilab code Exa 4.35 example 35

```

1 //example 35
2 clear
3 vbb=4; // volt
4 ib=50*10^-6; //ampere
5 for q=[0 0.7 4 12];
6     if q==0 then
7         rb=(vbb-q)/ib;
8         disp(" resistance at "+string((q))+ " volt    "+
9             string((rb))+ " ohm");
10    elseif q==0.7
11        rb=(vbb-q)/ib;
12        disp(" resistance at "+string((q))+ " volt    "+
13            string((rb))+ " ohm");
14    elseif q==4
15        disp(" vbb at 12 volt");

```

```

14         q=0;
15         vbb=12;
16         rb=(vbb-q)/ib;
17         disp("resistance at "+string((q))+ "volt    "+
              string((rb))+ "ohm");
18     else
19         q=0.7;
20         vbb=12;
21         rb=(vbb-q)/ib;
22
23
24         disp("resistance at "+string((q))+ "volt    "+
              string((rb))+ "ohm");
25     end
26 end

```

Scilab code Exa 4.36 example 36

```

1 //example 36
2 clear
3 ic=5.2*10^-3; //ampere
4 ib=50*10^-6; //ampere
5 icb=2*10^-6; //ampere
6 beta1=(ic-icb)/(ib+icb);
7 disp("beta    =    "+string((beta1)));
8 ie=ib+ic;
9
10 disp("ie    =    "+string((ie))+ "ampere");
11 alpha1=(ic-icb)/ic;
12 disp("alpha    =    "+string((alpha1)));
13
14
15

```

```

16 ic=10*10^-3;//ampere
17 ib=(ic-(beta1+1)*(icb))/beta1;
18
19
20 disp("ib    =    "+string((ib))+ " ampere"); //correction
    in the book

```

Scilab code Exa 4.37 example 37

```

1 //example 37
2 clear
3 beta1=160;
4 vb=-0.8;//volt
5 re=2.5*10^3;//ohm
6 vcc=10;//volt
7 for q=[160 80]
8     ib=(vcc-vb)*10^2/((re)*(1+q)*400);
9     ic=q*ib;
10    colres=1.5*10^3;//ohm
11    disp("collector current at beta "+string((q))+
        =    "+string((ic))+ " ampere"); //correction
        in the book
12    ie=(1+beta1)*ib;
13    vce=-(vcc-colres*ic-re*ie);
14    disp("vce at beta "+string((q))+ " =    "+string
        ((vce))+ " volt"); //correction in the book
15 end

```

Scilab code Exa 4.38 example 38

```

1 //pagenumber 222 example 38
2 clear
3 vb=0.7; // volt
4 vce=7; // volt
5 ic=1*10^-3; //ampere
6 vcc=12; // volt
7 beta1=100;
8 colres=(vcc-vce)/ic;
9 ib=ic/beta1;
10 //rb
11 rb=(vcc-vb-ic*colres)/ib;
12 disp("rb    =    "+string((rb))+ " ohm");
13 //stability
14 stability=(1+beta1)/(1+beta1*(colres/(colres+rb)));
15 disp("stability    =    "+string((stability)));
16 //beta=50
17 beta1=50;
18 disp("new point");
19 ib=(vcc-vb)/(beta1*colres+rb);
20 ic=beta1*ib;
21 disp("ic    =    "+string((ic))+ " ampere");
22 vce=vcc-(ic*colres);
23 disp("vce    =    "+string((vce))+ " volt");

```

Scilab code Exa 4.39 example 39

```

1 //pagenumber 223 example 39
2 clear
3 vcc=16; // volt
4 colres=3*10^3; //ohm
5 re=2*10^3; //ohm
6 r1=56*10^3; //ohm
7 r2=20*10^3; //ohm

```

```

8 alpha1=0.985;
9 vb=0.3; // volt
10 // coordinates
11 beta1=alpha1/(1-alpha1);
12 v1=vcc*r2/(r1+r2);
13 rb=r2/(r1+r2);
14 ic=(v1-vb)/((rb/beta1)+(re/beta1)+re);
15 disp("new point");
16 disp("vce = "+string((v1))+ " volt");
17 disp("ic = "+string((ic))+ " ampere");

```

Scilab code Exa 4.40 example 40

```

1 //pagenumber 224 example 40
2 clear
3 vce=12; // volt
4 ic=2*10^-3; //ampere
5 vcc=24; // volt
6 vb=0.7; // volt
7 beta1=50;
8 colres=4.7*10^3; //ohm
9 //re
10 re=((vcc-vce)/(ic))-colres;
11 disp("re = "+string((re))+ " ohm");
12 //r1
13 ib=ic/beta1;
14 v1=ib*3.25*10^3+vb+(ib+1.5*10^3);
15 r1=3.25*18*10^3/2.23;
16 disp("r1 = "+string((r1))+ " ohm");
17 //r2
18 r2=26.23*2.23*10^3/(18-2.3);
19 disp("r2 = "+string((r2))+ " ohm");

```

Scilab code Exa 4.41 example 41

```
1 //pagenumber 225 example 41
2 clear
3 colres=3*10^3; //ohm
4 rb=150*10^3; //ohm
5 beta1=125;
6 vcc=10; // volt
7 v1=5; // volt
8 vb=0.7; // volt
9 ib=(v1-vb)/rb;
10 disp(" ib    =    "+string((ib))+ " ampere");
11 ic=beta1*ib;
12 ie=ic+ib;
13 disp(" ic    =    "+string((ic))+ " ampere");
14 disp(" ie    =    "+string((ie))+ " ampere");//
    correction in the book in question to find only
    currents
```

Scilab code Exa 4.42 example 42

```
1 //pagenumber 226 example 42
2 clear
3 beta1=50;
4 vb=0.6; // volt
5 vcc=18; // volt
6 colres=4.3*10^3; //ohm
7 ic=1.5*10^-3; // ampere
```

```

8 vce=10; // volt
9 stability=4;
10 r1=(vcc-vce)/ic;
11 re=r1-colres;
12 w=(beta1+1)*(stability)*re/(1+beta1-stability);
13 disp("re    =    "+string((re))+ "ohm");
14 disp("rb    =    "+string((w))+ "ohm"); // correction in
    the book

```

Scilab code Exa 4.43 example 43

```

1 //pagenumber 226 example 43
2 re=100; //ohm
3 beta1=100;
4 rb=1*10^3; //ohm
5 stability=(1+beta1)/(1+beta1*(re/(re+rb)));
6 r1=3.8//r2
7 disp("r1    =    3.8*r2"); // correction in the book not
    given in question

```

Scilab code Exa 4.45 example 45

```

1 //pagenumber 228 example 45
2 clear
3 icb=2*10^-6; //ampere
4 vbb=1; //voltage
5 r1=50*10^3; //ohm
6 //current increases every 10celsius rb at 75celsius
7 vb=-0.1; //voltage

```

```

8 icb=2^6*10^-6; //at 75 celsius
9 rb=(vb+vbb)/icb;
10 disp("rb at 75 celsius = "+string((rb))+ "ohm");
11 icb=(vb+vbb)/r1;
12 disp("icb = "+string((icb))+ "ampere");
13 w=(log10(icb*10^6)*20/log10(2))-25;
14 disp("temperature at which current till max = "+
      string((w))+ "celsius");

```

Scilab code Exa 4.46 example 46

```

1 //pagenumber 228 example 46
2 clear
3 vb=0.8; //voltage
4 beta1=100;
5 vce=0.2; //voltage
6 vcc=10; //voltage
7 rb=200*10^3; //ohm
8 //collector resistance
9 ib=(5-0.7)/rb;
10 colres=(vcc-vce)/(beta1*ib);
11 disp("min collector resistance = "+string((
      colres))+ "ohm");

```

Scilab code Exa 4.47 example 47

```

1 //pagenumber 229 example 47
2 clear
3 alpha1=0.98;

```



```

4  alph11=0.96;
5  vcc=24; // volt
6  colres=120; //ohm
7  ie=100*10^-3; // ampere
8  beta1=alpha1/(1-alpha1);
9  bet11=alph11/(1-alph11);
10 ib2=ie/(1+bet11);
11 ie1=-ib2;
12 disp(" ib2    =    "+string((ib2))+ " ampere");
13 disp(" ie1    =    "+string((ie1))+ " ampere");
14
15
16 ic2=bet11*ib2;
17 ib1=ib2/(1+beta1);
18 ic1=beta1*ib1;
19 disp(" ic2    =    "+string((ic2))+ " ampere");
20 disp(" ib1    =    "+string((ib1))+ " ampere");
21 disp(" ic1    =    "+string((ic1))+ " ampere");
22 ic=ic1+ic2;
23 vce=vcc-ic*colres;
24 ib=ib1;
25 w=ic/ib;
26 q=-ic/ie;
27 disp(" ic     =    "+string((ic))+ " ampere");
28 disp(" ic/ib  =    "+string((w)));
29 disp(" ic/ie  =    "+string((q))); //correction in the
    book
30 disp(" vce   =    "+string((vce))+ " volt");

```

Chapter 5

BJT Amplifier

Scilab code Exa 5.1 example 1

```
1 //pagenumber 283 example 1
2 clear
3 ic=1*10^-3; //ampere
4 vcc=5; // volt
5 colres=2*10^3; //ohm
6 r1=1.4*10^3; //ohm
7 re=100; //ohm
8 beta1=100;
9 rb=100; //ohm
10 v1=0.026;
11 c1=25*10^-6; //farad
12 g1=ic/v1;
13 freque=10*10^3; // hertz
14 xc=1/(2*freque*3.14*c1);
15 volgai=-beta1*colres/(r1+0.1*10^3+2.5*10^3);
16 disp("voltage gain = "+string((volgai)));
17 ri=(0.1+2.5)*10^3-imag((xc)*(1+beta1));
18 disp("input resistance = "+string((ri))+ "ohm");
19 //ce removed
```

```

20 volgai=-beta1*colres/((r1+0.1*10^3+2.5*10^3)
    +(101/1000)*10^3*100);
21 disp("ce removed");
22 disp("voltage gain = "+string((volgai)));
23 ri=(0.1+2.5)*10^3+100*101/1000*10^3;
24 disp("input resistance = "+string((ri))+ "ohm");

```

Scilab code Exa 5.2 example 2

```

1 //pagenumber 285 example 2
2 clear
3 ic=1.3*10^-3; //ampere
4 colres=2*10^3; //ohm
5 re=500; //ohm
6 v1=0.026; //voltage
7 beta1=100;
8 vcc=15; //voltage
9 c1=10*10^-6; //farad
10 ib=ic/beta1;
11 ri=0.01/ib;
12 volgai=beta1*colres*ib/0.01;
13 disp("voltage gain = "+string((volgai))+ "<180");
14 disp("voltage gain reduced ce removed");
15 disp("when cb is short circuited the voltage gain
    increased");

```

Scilab code Exa 5.3 example 3

```

1 //pagenumber 286 example 3

```

```

2 clear
3 colres=4*10^3; //ohm
4 r1=4*10^3; //ohm
5
6 rb=20*10^3; //ohm
7 r=1*10^3; //ohm
8 hie=1.1*10^3; //ohm
9
10 //current gain
11 ri=rb*hie/(rb+hie);
12 curgai=(1/2.04)*(rb/(rb+(hie)))*(-50*colres/(colres
    +(r1)));
13 disp("current gain    =    "+string((curgai)));
14 //voltage gain
15 volgai=curgai*r1/r;
16 disp("voltage gain    =    "+string((volgai)));
17 //transconductance
18 conduc=volgai/r1;
19 disp("transconductance    =    "+string((conduc))+
    "ampere per volt");
20 //transresistance
21 resist=volgai*r;
22 disp("transresistance    =    "+string((resist))+
    "ohm");
23 //input resistance
24 disp("input resistance    =    "+string((ri))+
    "ohm");
25 //output resistance
26 resist=40*10^3*colres/(40*10^3+colres);
27
28
29
30 disp("output resistance    =    "+string((resist))+
    "ohm");

```

Scilab code Exa 5.4 example 4

```
1 //pagenumber 287 example 4
2 clear
3 ib=20*10^-6;//ampere
4 beta1=500;
5 re=10;//ohm correction in the book
6 r1=4.7*10^2;//ohm correction in the book
7 ic=ib*beta1;
8 voltag=ic*r1;//voltage drop at 4.7*10^3ohm
9 vc=(10-voltag);
10 rb=(vc-0.6)/ib;
11 disp("rb = "+string((rb))+ "ohm");
12 //re included
13 voltag=ic*re;//voltage drop at re
14 vb=(0.6+voltag);
15 rb=(vc-vb)/ib;
16 disp("rb including emitter resistance = "+string
      ((rb))+ "ohm");
```

Scilab code Exa 5.5 example 5

```
1 //pagenumber 288 example 5
2 clear
3 av=12480;
4 fedbac=8;//decibel
5 volgai=20*log10(av);//gain without feedback
6 volga1=volgai-fedbac;
7 beta1=((av/5000)-1)/av;
8
9 disp("voltage gain with feedback = "+string((
      volga1))+ "decibel");
10 disp("beta = "+string((beta1)));
```

Scilab code Exa 5.6 example 6

```
1 //pagenumber 288 example 6
2 beta1=100;
3 r1=1.5*10^3; //ohm
4 vcc=10; //voltage
5 r=100*10^3; //ohm
6 vb=((vcc)/(r+10*10^3))*10*10^3;
7 ie=0.3/100;
8 ib=ie/beta1;
9 disp(" collector current    =    "+string((ie))+ " ampere
      ");
10 disp(" emitter current    =    "+string((ie))+ " ampere")
    ;
11 disp(" base current      =    "+string((ib))+ " ampere");
```

Scilab code Exa 5.7 example 7

```
1 //pagenumber 268 example 7
2 clear
3 hie=800; //ohm
4 he=50*10^-6; //mho
5 hfe=-55;
6 z1=2*10^3; //ohm
7 curgai=hfe/(1+he*z1);
8 zi=hie
9 volgai=curgai*z1/zi;
```

```

10 powgai=volgai*curgai;
11 //if hoe neglected
12 av=137.5;
13 hfe=-55;
14 w=((av-abs(volgai))*100)/abs(volgai);
15 ap=hfe*(-av);
16 w1=((ap-powgai)*100)/powgai;
17 disp("voltage gain = "+string((volgai)));
18
19
20 disp("power gain = "+string((powgai)));
21 disp("error without hoe = "+string((w)));
22 disp("error = "+string((w1)));

```

Scilab code Exa 5.8 example 8

```

1 //pagenumber 289 example 8
2 clear
3 rb=5*10^3;//ohm
4 vcc=20;//voltage
5 r=10*10^3;//ohm
6 colres=5*10^3;//ohm
7 vb=vcc*r/(r+r);
8 beta1=50;
9 v1=0.6;//voltage
10 ib=(vb-v1)/(1+beta1*colres);
11 ic=beta1*ib;
12 vc=vcc-ic*1*10^3;
13 vce=vc-rb*(ic+ib);
14 disp("emitter current = "+string((ic+ib))+
      "ampere");
15 disp("vc = "+string((vc))+ "voltage");
16 disp("collector emitter voltage = "+string((vce)

```

```
)+" volt");
```

Scilab code Exa 5.9 example 9

```
1 //pagenumber 290 example 9
2 clear
3 hib=25;//ohm
4 hfb=0.999;
5 hob=10^-6;//ohm
6 colres=10*10^3;//ohm
7 //voltage gain
8 curgai=hfb/(1+hob*colres);
9 zi=hib+hob*colres*curgai;
10 volgai=curgai*colres/(zi);
11 disp(" voltage gain    =    "+string((volgai)));//
    correction in the book
```

Scilab code Exa 5.10 example 10

```
1 //pagenumber 290 example 10
2 clear
3 re=1*10^3;//ohm
4 hie=100;//ohm
5 hfe=100;
6 //voltage gain
7 volgai=1/((1+(hie/(2*(1+hfe)*re))));
8 //ri
9 ri=(hie/2)+(1+hfe)*re;
10 disp(" voltage gain    =    "+string((volgai)));
```



```
11 disp("input resistance = "+string((ri))+ "ohm");
```

Scilab code Exa 5.11 example 11

```
1 //pagenumber 292 example 11
2 clear
3 beta1=90;
4 re=2*10^3; //ohm
5 rb=240*10^3; //ohm
6 vcc=20;
7 ib=(vcc-0.7)/(rb+(1+beta1)*(re));
8 ic=beta1*ib;
9 vce=vcc-(ib+ic)*re;
10 disp("emitter current = "+string((ib+ic))+
      "ampere");
11 disp("vce = "+string((vce))+ "volt");
```

Scilab code Exa 5.12 example 12

```
1 //pagenumber 292 example 12
2 clear
3 hfe=110;
4 hie=1.6*10^3; //ohm
5 hoe=20*10^-6; //ohm
6 colres=4.7*10^3; //ohm
7 hre=2*10^-4;
8 r1=470*10^3; //ohm
9 curgai=-hfe/(1+hoe*colres);
10 ri=hie+hre*curgai*colres;
```

```

11  volgai=curgai*colres/ri;
12  y1=hoe-((hfe*hre)/(hie+1*10^3))
13  z1=1/y1;
14  disp("voltage gain    =    "+string((volgai)));
15  disp("current gain    =    "+string((curgai)));
16  disp("impedance      =    "+string((z1))+ "ohm");
17  r0=z1*colres/(z1+colres);
18  curgai=-hfe;
19  ri=hie;
20  disp("parameters using approxmiate");
21  volgai=curgai*(colres)/ri;
22  disp("voltage gain    =    "+string((volgai)));//
    correction in the book
23  disp("current gain    =    "+string((curgai)));
24  disp("impedance      =    "+string((z1))+ "ohm");

```

Scilab code Exa 5.13 example 13

```

1  //pagenumber 293 example 13
2  clear
3  re=1*10^3;//ohm
4  hie=1000;//ohm
5  hfe=99;
6  //inptut resistance
7  ri=hie+((1+hfe)*(hie+1+hfe*re));
8
9
10 disp("input resistance    =    "+string((ri))+ "ohm");
    //correction in the book
11 //voltage gain
12 volgai=((1+hfe)*(1+hfe)*re)/ri;
13 disp("voltage gain    =    "+string((volgai)));
14

```

```

15
16 //current gain
17 curgai=-((1+hfe)*(1+hfe));
18
19
20 disp("current gain    =    "+string((curgai)));

```

Scilab code Exa 5.14 example 14

```

1 //pagenumber 294 example 14
2 clear
3 hie=2*10^3; //ohm
4 beta1=100;
5 colres=5*10^3; //ohm
6 volgai=beta1*colres/hie;
7 disp("voltage gain    =    "+string((volgai))+<180");
8 disp("input impedance  =    "+string((hie))+<ohm");
9 disp("current gain    =    "+string((beta1)));

```

Scilab code Exa 5.15 example 15

```

1 //pagenumber 294 example 15
2 clear
3 colres=4.7*10^3; //ohm
4 beta1=150;
5 r1=12*10^3; //ohm
6 vcc=15; //voltage
7 re=1.2*10^3; //ohm
8 rac=colres*r1/(colres+r1);

```

```

 9 r=2*10^3; //ohm
10 //voltage gain
11 volgai=beta1*rac/r;
12 disp("voltage gain = "+string((volgai)));
13 r1=75*10^3; //ohm
14 r2=7.5*10^3; //ohm
15 //input impedance
16 zin=(r1*r2)/(r1+r2);
17 zin=zin*r/(zin+r);
18 disp("input impedance = "+string((zin)));
19 //coordinates
20 vb=vcc*r2/(r1+r2);
21 ie=vb/re;
22 vce=vcc-((colres+re)*(ie));
23 disp("coordinates ic = "+string((ie))+ " ampere
      vce = "+string((vce))+ " volt");

```

Scilab code Exa 5.16 example 16

```

1 //pagenumber 296 example 16
2 clear
3 r1=2000; //ohm
4 r=900; //ohm
5 hie=1200; //ohm
6 hre=2*10^-4;
7 hfe=60;
8 hoe=25*10^-6; //ampere per volt
9 curgai=(hfe)/(1+hoe*r1);
10 disp("current gain = "+string((curgai)));
11 ri=hie+(curgai*r1);
12 disp("input impedance = "+string((ri))+ "ohm");
13 volgai=curgai*r1/ri;
14 disp("voltage gain = "+string((volgai)));

```

```

15 admita=1/ri;
16 admita=hoe-(-hfe*hre)/(hie+r);
17 r=1/admita;
18 disp(" output resistance = "+string((r))+ "ohm");

```

Scilab code Exa 5.17 example 17

```

1 //pagenumber 296 example 17
2 clear
3 hfe=60;
4 hie=500; //ohm
5 ic=3*10^-3; //ampere
6 zi=hie;
7 rb=220*10^3; //ohm
8 colres=5.1*10^3; //ohm
9 z=colres;
10 volgai=-hfe*colres/hie;
11 curgai=-hfe;
12 vcc=12; //voltage
13 ib=(vcc-0.6)/rb;
14 ie=hfe*ib;
15 re=0.026/ie;
16 zi=hfe*re;
17 z=colres;
18 volgai=-colres/re;
19 curgai=-hfe;
20 disp(" voltage gain = "+string((volgai)));
21 disp(" current gain = "+string((curgai)));
22 disp(" input impedance = "+string((zi))+ "ohm");
23 disp(" output impedance = "+string((z))+ "ohm");

```

Scilab code Exa 5.18 example 18

```
1 //pagenumber 297 example 18
2 clear
3 hie=3.2*10^3; //ohm
4 hfe=100;
5 r=40*10^3; //ohm
6 r1=4.7*10^3; //ohm
7 colres=4*10^3; //ohm
8 rb=r*r1/(r+r1);
9 zi=hie*rb/(hie+rb);
10 z=colres;
11 re=1.2*10^3; //ohm
12 volgai=-hfe*colres/hie;
13 disp("input impedance = "+string((zi))+ "ohm");
14 disp("output impedance = "+string((z))+ "ohm");
15 disp("voltage gain = "+string((volgai)));
16 curgai=-hfe*rb/(rb+hie);
17 disp("current gain = "+string((curgai)));
18 hie=833;
19 //(1) load open
20 vi=1;
21 ib=vi/hie;
22 volgai=hfe*ib*1.5*10^3;
23 //load closed
24 hoe=50;
25 r2=2*10^3; //ohm
26 ib=vi/(r2+hie);
27 vb=1.682;
28 ib=(vb-0.6)/(rb+(1+hfe)*(re));
29 ic=hfe*ib;
30 ie=ic+ib;
```

```

31 re=0.026/ie;
32 zi=rb*hfe*re/((rb)+(hfe*re));
33 disp("parameters in re");
34 disp("input impedance = "+string((zi))+ "ohm");
35 z=colres;
36 disp("output impedance = "+string((z))+ "ohm");
37 volgai=colres/(-re);
38 disp("voltage gain = "+string((volgai)));
39 curgai=-hfe*rb/(rb+hfe*re);
40 disp("current gain = "+string((curgai)));

```

Scilab code Exa 5.19 example 19

```

1 //pagenumber 299 example 19
2 clear
3 hfe=120;
4 hie=0.02; //ohm
5 r1=5.8*10^3; //ohm
6 r=27*10^3; //ohm
7 colres=1.5*10^3; //ohm
8 re=330*10^3; //ohm
9 vcc=10; //voltage
10 vb=vcc*r1/(r1+r);
11 rb=(r*r1)/(r+r1);
12 ib=(vb-0.7)/(rb+((1+hfe)*re));
13 volgai=-hfe*ib*2*10^3;
14 disp("voltage gain = "+string((volgai))); //
    correction in the book

```

Scilab code Exa 5.20 example 20

```
1 //pagenumber 300 example 20
2 clear
3 freque=6*10^6; //hertz
4 hfe=50;
5 r1=500; //ohm
6 g=0.04
7 rbb=100; //ohm
8
9
10 c1=10*10^-12; //farad
11 r=1000; //ohm
12 rbe=hfe/g;
13 ce=g/(2*3.14*freque);
14 c1=ce+c1*(1+g*r);
15 hie=rbb+rbe;
16 resist=(r1+rbb)*rbe/(r1+rbb+rbe);
17 frequ2=1/(2*3.14*resist*c1);
18 curgai=-hfe*r1/(r1+hie);
19 volgai=(-hfe*r)/(r1+hie);
20 q=volgai*frequ2;
21 disp("upper frequency voltage gain = "+string(
    abs(q))+ "hertz"); //correction in the book
22 q=curgai*frequ2;
23 disp("upper current gain = "+string(abs(q))+
    "hertz");
```

Scilab code Exa 5.21 example 21

```
1 //pagenumber 301 example 21
2 clear
3 hie=1*10^3; //ohm
```



```

4 hre=2*10^-4;
5 hoe=25*10^-6; //ampere per volt
6 hfe=50;
7 colres=1*10^3; //ohm
8 curgai=-hfe/(1+hoe*colres);
9 disp("current gain = "+string((curgai)));
10 ri=hie-hfe*hre/(hoe+1/colres);
11 disp("input resistance = "+string((ri))+ "ohm");
12 volgai=curgai*colres/ri;
13 disp("voltage gain = "+string((volgai)));
14 y1=hoe-((hfe*hre)/(hie+800));
15 r1=1/y1;
16 disp("output resistance = "+string((r1))+ "ohm");
17 // approximate
18 disp("approximate");
19 curgai=-hfe;
20 disp("current gain = "+string((curgai)));
21 ri=hie;
22 disp("input resistance = "+string((ri))+ "ohm");
23 volgai=-hfe*colres/hie;
24 disp("voltage gain = "+string((volgai)));

```

Scilab code Exa 5.22 example 22

```

1 //example 22
2 clear
3 rb1=7.5*10^3; //ohm
4 rb2=6.8*10^3; //ohm
5
6 rb3=3.3*10^3; //ohm
7 re=1.3*10^3; //ohm
8 colres=2.2*10^3; //ohm
9 beta1=120;

```

```

10 vcc=18; // volt
11 vb1=rb3*vcc/(rb3+rb2+rb1);
12 ie1=(vb1-0.7)/(re);
13 re1=0.026/ie1;
14 re2=0.026/ie1;
15 volgai=colres/re2;
16 disp(" voltage gain    =    "+string((volgai)));

```

Scilab code Exa 5.23 example 23

```

1 //pagenumber 302 example 23
2 clear
3 vcc=5; // volt
4 colres=250; //ohm
5 v1=5; // volt
6 rb=25*10^3; //ohm
7 beta1=200;
8 vbs=0.8; // volt
9 vcon=0.3; // volt
10 icon=(vcc-vcon)/colres;
11 ibon=icon/beta1;
12 ibs=(v1-vbs)/rb;
13 ic=(vcc-0.2)/colres;
14 beta1=ic/ibs;
15 disp(" forced beta    =    "+string((beta1)));

```

Scilab code Exa 5.24 example 24

```

1 //pagenumber 303 example 24

```

```

2 clear
3 vb=0.6; // volt
4 beta1=100;
5 ic=1*10^-3; // ampere
6 vce=2.5; // volt
7 re=300; // ohm
8 vcc=5; // volt
9 ib=ic/beta1;
10 ie=ic+ib;
11 ve=ie*re;
12 vce=vce+ve;
13 r3=(vcc-vce)/ic;
14 vb=ve+vb;
15 r1=(vcc-vb)/(vb/(10*10^3)+(ib));
16 disp("resistance r1 = "+string((r1))+ "ohm");
17 disp("resistance r3 = "+string((r3))+ "ohm");

```

Scilab code Exa 5.25 example 25

```

1 //pagenumber 304 example 25
2 clear
3 vce2=7.5; // volt
4 vb=0.7; // volt
5 beta1=200;
6 v1=25; // volt
7 r1=10*10^3; // ohm
8 vcc=15; // volt
9 i1=(vcc-vb)/r1;
10 r=(vcc-vce2)/i1;
11 z1=beta1*v1/i1;
12 z=v1/i1;
13 disp("input impedance q1 = "+string((z))+ "ohm");
    //correction in the book

```

```
14 disp("input impedance q2 = "+string((z1))+ "ohm")
    ;
```

Scilab code Exa 5.26 example 26

```
1 //pagenumber 305 example 26
2 clear
3 beta1=99;
4 r1=1*10^3; //ohm
5 g=beta1/r1;
6 r=r1*((r1+r1)/(100))/((r1+((r1+r1)/(100))));
7 disp("make input = 0");
8 disp("ground dc");
9
10
11 disp("output resistance = "+string((r))+ "ohm");
```

Scilab code Exa 5.27 example 27

```
1 //pagenumber 305 example 27
2 clear
3 ic=0.5*10^-3; //ampere
4 rb=100*10^3; //ohm
5 v1=0.026; //voltage
6 r1=50; //ohm
7 colres=1*10^3; //ohm
8 g=ic/v1;
9 volgai=g*colres;
```

```

10 disp("output resistance = "+string((colres))+
    ohm");
11 disp("input resistance very low");//not given in the
    book
12 disp("voltage gain = "+string((volgai)));

```

Scilab code Exa 5.28 example 28

```

1 //pagenumber 306 example 28
2 clear
3 re=4*10^3;//ohm
4 r1=4*10^3;//ohm
5 hie=1.1*10^3;//ohm
6 resist=10*10^3;//ohm
7 hfe=50;
8 rb=10*10^3;//ohm
9 r=1*10^3;//ohm
10 colres=5*10^3;//ohm
11 //(1) current gain
12 ri=rb*hie/(rb+hie);
13 curgai=(1/2.04)*((rb)/(rb+hie))*((-hfe*colres)/(
    colres+r1));
14 disp("current gain = "+string((curgai)));
15 //(2) voltage gain
16 volgai=curgai*r1/r;
17 disp("voltage gain = "+string((volgai)));
18 //(3) tranconductance
19 conduc=volgai/r1;
20 disp("transconductance = "+string((conduc))+
    ampere per volt");
21 //transresistance
22 resist=resist*volgai;
23 disp("transresistance = "+string((resist))+
    "ohm")

```

```

    );
24 disp("input resistance = "+string((ri))+ "ohm");
25 r=(40*10^3*colres)/(40*10^3+colres);
26 disp("output resistance = "+string((r))+ "ohm");

```

Scilab code Exa 5.29 example 29

```

1 //pagenumber 307 example 29
2 clear
3 beta1=500;
4 ib=20*10^-6; //ampere
5 re=100; //ohm
6 ic=beta1*ib;
7 vc=ic*0.47*10^3; //voltage drop across collector
   resistance
8 v1=(10-vc);
9 vb=v1-0.6;
10 rb=vc/ib;
11 disp("base resistance = "+string((rb))+ "ohm");
12 ve=re*ic;
13 disp("base resistance with re");
14 b=0.6+0.1;
15 rb=(v1-b)/ib;
16 disp("base resistance = "+string((rb))+ "ohm");

```

Scilab code Exa 5.30 example 30

```

1 //pagenumber 308 example 30
2 clear

```

```
3 beta1=100;
4 re=100; //ohm
5 vcc=10; //voltage
6 colres=1.5*10^3; //ohm
7 r=100*10^3; //ohm
8 r1=10*10^3; //ohm
9 vb=vcc*r1/(r1+r);
10 ie=0.3/re;
11 ib=ie/beta1;
12 disp("collector current = "+string((ie))+ " ampere
    ");
13 disp("base current = "+string((ib))+ " ampere");
14 disp("emitter current = "+string((ie))+ " ampere")
    ;
```

Chapter 6

BJT at high frequency

Scilab code Exa 6.1 example 1

```
1 //pagenumber 337 example 1
2 clear
3 colcur=10*10^-3; //ampere
4 vce=10; //voltage
5 hie=500; //ohm
6 hoe=4*10^-5;
7 hfe=100;
8 hre=1*10^-4;
9 fqu=50*10^6; //hertz
10 q=3*10^12; //farad
11 voltag=26*10^-3; //voltage
12 g=colcur/voltag;
13 gbe=g/hfe;
14 gbc=gbe*hre;
15 rbb=hie-260;
16 oucond=hoe-(1+hfe)*gbc;
17 cbe=g/(2*3.14*fqu);
18 rbc=1/gbc;
19 rce=1/oucond;
```



```

20 disp("transconductance g = "+string((g))+ " ampere
    /voltage");
21 disp("input conductance gbe = "+string((gbe))+ "
    ampere/voltage");
22 disp("feedback conductance gbc = "+string((gbc))
    +" ampere/voltage");
23 disp("base spread resistance rbb = "+string((rbb
    ))+"ohm");
24 disp("output conductance = "+string((oucond))+ "
    ampere/voltage");
25 disp("transition capacitance cbe = "+string((cbe
    ))+"farad");
26 disp("rbc = "+string((rbc))+ "ohm"); // correction
    as 2.6 mega ohm
27 disp("rce = "+string((rce))+ "ohm");

```

Scilab code Exa 6.2 example 2

```

1 //pagenumber 337 example 2
2 clear
3 colcur=5*10^-3; //ampere
4 vce=10; //voltage
5 hfe=100;
6 hie=600; //ohm
7 cugain=10;
8 fqu=10*10^6; //hertz
9
10 tracat=3*10^-12; //farad
11 voltag=26*10^-3; //voltage
12 fbeta1=(((hfe^2)/(cugain^2))-1)/fqu^2)^(1/2);
13 fbeta1=1/fbeta1;
14 fq1=hfe*fbeta1;
15 cbe=colcur/(2*3.14*fq1*voltag);

```

```

16 rbe=hfe/(colcur/voltag);
17 rbb=hie-rbe;
18 disp(" fbeta    =    "+string((fbeta1))+ " hertz");
19 disp(" f        =    "+string((fq1))+ " hertz");
20 disp(" cbe      =    "+string((cbe))+ " farad");
21 disp(" rbe      =    "+string((rbe))+ " ohm");
22 disp(" rbb      =    "+string((rbb))+ " ohm");

```

Scilab code Exa 6.3 example 3

```

1 //pagenumber 338 example 3
2 clear
3 w=1*10^-4; //centimetre
4 em1cur=2*10^-3; //ampere
5 q=47;
6 voltag=26*10^-3; // volt
7 cde=(em1cur*w^2)/(voltag*2*q);
8 fq1=(em1cur)/(2*3.14*cde*voltag);
9 disp(" cde      =    "+string((cde))+ " farad");
10 disp(" frequency =    "+string((fq1))+ " hertz");

```

Scilab code Exa 6.6 example 6

```

1 //pagenumber 339 example 6
2 clear
3 w=5*10^-4; //centimetre
4 em1cur=2*10^-3; //ampere
5 q=47;
6 voltag=26*10^-3; // volt

```

```

7 re=voltag/em1cur;
8 fq1=2*q/(w^2*2*3.14);
9 cde=(em1cur*w^2)/(voltag*2*q);
10 w=(w^2)/(2*q);
11 disp("re    =    "+string((re))+ "ohm");
12 disp("falphi  =    "+string((fq1))+ "hertz");
13 disp("cde    =    "+string((cde))+ "farad");
14
15
16 disp("w      =    "+string((w))+ "second");

```

Scilab code Exa 6.8 example 8

```

1 //pagenumber example 8
2 clear
3 w=10^-6; //centimetre
4 em1cur=4*10^-3; //ampere
5 voltag=26*10^-3; //volt
6 q=47;
7 cde=(em1cur*w^2)/(voltag*2*q);
8 fq1=(em1cur)/(2*3.14*cde*voltag);
9 disp("f      =    "+string((fq1))+ "hertz");
10 disp("cde    =    "+string((cde))+ "farad");//
    correction in book 0.0016pico farad

```

Chapter 7

Field Effect Transistor

Scilab code Exa 7.1 example 1

```
1 //pagenumber 370 example 1
2 clear
3 rd=12*10^3; //ohm
4 r=1*10^6; //ohm
5 resour=470; //ohm
6 vdd=30; //voltage
7 idss=3*10^-3; //ampere
8 vd=2.4; //voltage
9
10 vgs=[0.24 2.175 1.41];
11 vgs=roots(vgs);
12 vgs=0.7;
13 id=idss*((1-(vgs/vd)))^2;
14 vds=vdd-id*(rd+resour);
15 g=(2*idss/vd)*(1-((vgs/vd)));
16 volgai=-g*rd;
17 disp(" vgs    =    "+string((vgs))+ " volt");
18 disp(" id     =    "+string((id))+ " ampere");
19 disp(" vds    =    "+string((vds))+ " volt");
```

```
20 disp(" voltage gain = "+string((volgai)));
```

Scilab code Exa 7.2 example 2

```
1 //pagenumber 371 example 2
2 clear
3 idss=1*10^-3; //ampere
4 pinvol=1; //voltage
5 q=10; //voltage
6 rd=56*10^3; //ohm
7 vdd=24; //voltage
8 dracur=(vdd-q)/rd;
9 vgs=0.5;
10 r1=vgs/dracur;
11 disp("r1 = "+string((r1))+ "ohm");
```

Scilab code Exa 7.4 example 4

```
1 //pagenumber 372 example 4
2 clear
3 ids=4*10^-3; //ampere
4 vp=4; //voltage
5 r=1.3*10^3 //ohm
6 r1=200*10^3; //ohm
7 vdd=60; //voltage
8 drares=18*10^3; //ohm
9 soresi=4*10^3; //ohm
10 rth=(r*r1)/(r+r1);
11 vth=r1*(1-vdd)/(1500*10^3);
```

```

12 id=-2.25*10^-3;
13 vds=-vdd-(drares+soresi)*id;
14 disp("id    =    "+string(abs(id))+ " ampere");
15 disp("vds    =    "+string(abs(vds))+ " volt");

```

Scilab code Exa 7.5 example 5

```

1 //pagenumber 373 example 5
2 clear
3 idss=10*10^-3; //ampere
4 pinvol=-1; //voltage
5 ids=6.4*10^-3; //ampere
6 vgs=-(sqrt(ids/idss)-(1))*pinvol;
7 r=pinvol/ids;
8
9
10 disp("source resistance    =    "+string(abs(r))+ "ohm"
      );

```

Scilab code Exa 7.6 6

```

1 //pagenumber 374 example 6
2 clear
3 v1=2; //voltage
4 vgs=4; //voltage
5 voltag=5; //voltage
6 q=5*10^-3; //ampere per volt square
7 id=q*(vgs-v1);
8 durati=10^-7*log(4);

```

```
9
10 disp(" duration    =    "+string((durati))+ " second");
```

Scilab code Exa 7.7 example 7

```
1 //pagenumber 7 example 7
2 clear
3 idss=1*10^-3;//ampere
4 pinvol=-5;//volt
5 tracon=(2*idss)/abs(pinvol);
6 disp("max transconductance    =    "+string((tracon))+
      "mho");
```

Scilab code Exa 7.8 example 8

```
1 //pagenumber 376 example 8
2 clear
3 vdd=10;//volt
4 beta1=10^-4;//ampere per square volt
5 ids=0.5*10^-3;//ampere
6 voltag=1;//volt
7 vgs=(sqrt(ids/beta1)+(1));
8 rd=(vdd-vgs)/ids;
9
10 disp(" vgs    =    "+string((vgs))+ " volt");
11 disp(" rd    =    "+string((rd))+ " ohm");
```

Scilab code Exa 7.9 example 9

```
1 //pagenumber 376 example 9
2 clear
3 v1=2; //voltage
4 ids=4*10^-3; //ampere
5
6 rd=910; //ohm
7 r1=3*10^3; //ohm
8 r=12*10^6; //ohm
9 r11=8.57*10^6; //ohm
10 vdd=24; //voltage
11 vg=vdd*(r11/(r+(r11)));
12 id=3.39*10^-3;
13 vgsq=vg-id*r1;
14 vdsq=vdd-id*(rd+r1);
15 vdgq=vdsq-vgsq;
16 disp("point "+string(vdsq)+">" +string(v1)+"voltage");
17 disp("vds greater than 2voltage the point in pinch");
```

Chapter 8

FET Amplifier

Scilab code Exa 8.1 example 1

```
1 //pagenumber 399 example 1
2 clear
3 freque=5*10^3; //hertz
4 //(1)
5 g=2*10^-3; //ampere per volt
6 rd=10*10^3; //ohm
7 r1=30*10^3; //ohm
8 r12=r1*r1/(r1+r1);
9 volgai=-(g*r12*rd)/(r12+rd);
10 disp("voltage gain = "+string((volgai))); //
    correction r12 should be taken as 15*10^3ohm in
    book
11 //(2) capacitance included
12 c=0.025*10^-6; //farad
13 frequ1=1/((2*3.14*(((rd*r1)/(rd+r1))+r1))*c);
14 volgai=(volgai/(sqrt((1+(frequ1/freque)^2))));
15
16 disp("voltage gain = "+string((volgai)));
```

Scilab code Exa 8.2 example 2

```
1 //pagenumber 400 example 2
2 clear
3 rd=80*10^3; //ohm
4 r1=8*10^3; //ohm
5 rd12=5*10^3; //ohm
6 rd1=rd*r1/(rd+r1);
7 u=30;
8 volgai=-(u*rd1)/(rd1+rd12);
9
10 disp(" voltage gain    "+string((volgai)));
```

Scilab code Exa 8.3 example 3

```
1 //pagenumber 401 example 3
2 clear
3 r1=60*10^3; //ohm
4 volgai=-17.7;
5 rg=80*10^3; //ohm
6 volgai=((volgai*rg)/(1-volgai))/((rg/(1-volgai))+r1)
  ;
7 disp(" voltage gain    =    "+string((volgai)));
```

Scilab code Exa 8.6 example 6

```
1 //pagenumber 405 example 6
2 clear
3 vds=14; // volt
4 idq=3*10^-3; //ampere
5 vdd=20; // volt
6 g=2*10^-2;
7 rd=50*10^3; //ohm
8 vgs=-1.5; // volt
9 w=(vdd-vds)/idq;
10 r1=-vgs/idq;
11 r2=w-r1;
12 inpres=1/(1-(0.8*((r1)/(r1+r2))));
13 volgai=(r1+r2)/(r1+r2+(1/(g)));
14 disp("r1 = "+string((r1))+ "ohm");
15 disp("effective input resistance = "+string((
    inpres))+ "r3ohm");
16 disp("r2 = "+string((r2))+ "ohm");
17
18
19 disp("voltage gain = "+string((volgai))+ "av'");
```

Scilab code Exa 8.7 example 7

```
1 //pagenumber 405 example 7
2 clear
3 rg=40*10^3; //ohm
4 voltag=(1-6*50)*3.3*10^3/(5.3*10^3);
5
6 disp("output voltage = "+string((voltag))+ "volt"
    ); //correction in the book
```

Scilab code Exa 8.9 example 9

```
1 //pagenumber 406 example 9
2 clear
3 u=50;
4 rd=10*10^3; //ohm
5 cgs=5*10^-12; //farad
6 cgd=2*10^-12; //farad
7 cds=2*10^-12; //farad
8 freque=3; //decibel
9 g=u/rd;
10 volgai=-u*rd/(rd+rd);
11 req=rd*rd/(rd+rd);
12 frequ1=1/(2*3.14*cgd*req);
13 disp("voltage gain = "+string((volgai))); //
    correction in book
14 disp("frequency = "+string((frequ1))+ "hertz");
15 capac1=cgd*(1+g);
16 disp("output capacitance = "+string((capac1))+
    "farad");
17
18
19
20 disp("req = "+string((req))+ "ohm");
```

Chapter 9

Multistage Amplifier

Scilab code Exa 9.1 example 1

```
1 //pagenumber 424 example 1
2 clear
3 //(1) frequency
4 freque=100*10^3*sqrt(2^(1/3)-(1));
5 frequ2=100*10^3/sqrt(2^(1/3)-(1));
6 disp("frequency1    =    "+string((freque))+ " hertz");
7 disp("frequency2    =    "+string((frequ2))+ " hertz");
8 //(2) frequency
9 freq11=100*10^6; //hertz
10 freq12=150*10^6; //hertz
11 freq13=200*10^6; //hertz
12 freq21=100*10^3; //hertz
13 freq22=150*10^3; //hertz
14 freq23=200*10^3; //hertz
15 frequ1=sqrt(freq11^2+freq12^2+freq13^2);
16 disp("frequency    =    "+string((frequ1))+ " hertz");//
    correction in the book 269.25mega hertz
17 frequ1=1/sqrt((1/(freq21^2))+ (1/(freq22^2))+ (1/(
    freq23^2))));
```

```

18
19
20 disp("frequency    =    "+string((frequ1))+ "hertz"); //
    correction in the book

```

Scilab code Exa 9.2 example 2

```

1 //pagenumber 424 example 2
2 clear
3 freque=60; //hertz
4 frequ1=freque*0.484;
5 cb=1/(frequ1*2*3.14*10^3);
6 disp("coupling capacitance    =    "+string((cb))+"/r '
    ");

```

Scilab code Exa 9.3 example

```

1 //pagenumber 425 example 3
2 clear
3 g=10*10^-3; //ampere per volt
4 rd=5.5*10^3; //ohm
5 rg=1*10^6; //ohm
6 //(1) cb frequency 1decibel to 10hertz
7 ri=rg;
8 r1=(rd*8*10^3)/(rd+8*10^3);
9 cb=10^-6/(3.14*5.07);
10 disp("cb    =    "+string((cb))+ "farad");
11 //(2) cb
12 cb=(cb*(5)/(3.52));

```

```

13 disp("cb = "+string((cb))+ "farad");
14 //(3) gain
15 a1=g^2*(3.26^2);
16 disp("gain of each stage = "+string((a1)));//
    correction in the book

```

Scilab code Exa 9.4 example 4

```

1 //pagenumber 427 example 4
2 clear
3 freque=40*10^3;//hertz
4 frequ1=freque/0.507;
5 disp("upper frequency = "+string((frequ1))+
    hertz");
6 frequ1=freque/1.96;
7 disp("lower frequency = "+string((frequ1))+
    hertz");

```

Scilab code Exa 9.5 example 5

```

1 //pagenumber 427 example 5
2 clear
3 g=2.6*10^-3;//ampere per volt
4 rd=7.7*10^3;//ohm
5 rd1=12*10^3;//ohm
6 cb=0.005*10^-6;//farad
7 //(1) voltage gain
8 volgai=g*((1/rd)+1/rd1+1/(1*10^3));
9 volgai=(20*(log10(10.8)))*3;

```

```

10 disp("overall voltage gain = "+string((volgai))+
    decibel");//correction in the book
11 //(2) lower frequency
12 r=rd*rd1/(rd+rd1);
13 freque=1/((2*3.14)*(r+1*10^6)*cb);
14 disp("lower frequency of each = "+string((freque
    ))+" hertz");
15 //(3) overall lower frequency
16 freque=freque*1.96;
17 disp("lower frequency overall = "+string((freque)
    )+" hertz");

```

Scilab code Exa 9.6 example 6

```

1 //pagenumber 429 example 6
2 clear
3 hfe=50;
4 hie=1.1*10^3;//ohm
5 //(1) gain
6 r1=2*10^3;//ohm
7 volgai=-hfe*r1/(hie);
8 r11=25*10^3*hie/(25*10^3+hie);
9 r11=r1*r11/(r1+r11);
10 volga1=-hfe*r11/hie;
11 volgai=volgai*volga1;
12 disp("voltage gain = "+string((volgai)));
13 freque=20;//hertz
14 ri=25*10^3*hie/(25*10^3+hie);
15 cb=1/(2*3.14*(ri+r1)*(freque));
16 disp("cb = "+string((cb))+ "farad");
17 cb=1/(2*3.14*3.05*10^3*10/3.14);
18 disp("cb <= "+string((cb))+ "farad");

```

Scilab code Exa 9.8 example 8

```
1 //pagenumber 432 example 8
2 clear
3 theta1=atand(0.1);
4 disp("theta1 = "+string((theta1)));
5 disp("phase constant 10f1<=f<=0.1f11");
```

Chapter 10

Negative Feedback Amplifiers

Scilab code Exa 10.1 example 1

```
1 //pagenumber 467 example 1
2 clear
3 av=1000;
4 chvoga=0.001;//change in voltage gain
5 beta1=1/((chvoga)/(100/av))-1;
6 beta1=beta1/av;
7 fegain=(av)/(1+(av*(beta1)));
8 disp("reverse transmission    =    "+string((beta1)));
9
10 disp("gain with feedback    =    "+string((fegain)));
```

Scilab code Exa 10.2 example 2

```
1 //pagenumber 467 example 2
2 clear
```

```

3  voltag=36; //voltage
4  w=0.07; //harmonic distortion
5  inpvol=0.028; //voltage
6  beta1=0.012;
7  a=voltag/inpvol;
8  fegain=a/(1+beta1*a); //correction in book
9  volta1=fegain*inpvol;
10 disp("output voltage    =    "+string((volta1)));
11 //decrease of gain 9
12 inpvol=9*inpvol;
13
14
15
16 disp("input voltage    =    "+string((inpvol))+ " volt")
    ;

```

Scilab code Exa 10.3 example 3

```

1  //pagenumber 468 example 3
2  clear
3  volgain=2000; //voltage gain
4  outpower=20; //watts
5  inpsig=10*10^-3; //volts
6  fedbac=40; //decibel
7  fedgai=volgain/100;
8  outvol=volgain*inpsig; //output voltage
9  inpvol=outvol/fedgai; //required input
10 //10 second harmonic distortion
11 distor=(10/100);
12 disp("required input    =    "+string((inpvol))+ " volt"
    );
13
14

```

```
15
16 disp("harmonic distortion = "+string((distor)));
```

Scilab code Exa 10.5 example 5

```
1 //pagenumber 469 example 5
2 clear
3 fedgai=60; //decibel
4 outimp=10*10^3; //ohm
5 outim1=500; //ohm modified impedance
6 fedgai=1000;
7 fedbac=((outimp/outim1)-(1))/fedgai;
8 //10 change in gain
9 overga=1/((1+(fedgai*fedbac))/0.1); //over gain
10 disp("feedback factor = "+string((fedbac)));
11 disp("over gain = "+string((overga)));
```

Scilab code Exa 10.6 example 6

```
1 //pagenumber 470 example 6
2 clear
3 colres=4*10^3; //ohm
4 r=4*10^3; //ohm
5 basres=20*10^3; //ohm
6 r1=1*10^3; //ohm
7 hie=1.1*10^3;
8 hfe=50;
9 hoe=(40*10^3);
10 ri=basres*hie/(basres+hie);
```

```

11  curgai=((r1/(r1+ri))*((basres/(basres+hie))*((-hfe
      *colres)/(colres+r)));
12  volgai=curgai*r/r1;
13  tranco=volgai/r;
14  tranre=r1*volgai;
15  outres=hoe*colres/(hoe+colres);
16  disp("current gain    =    "+string((curgai)));
17  disp("voltage gain    =    "+string((volgai)));
18  disp("transconductance =    "+string((tranco))+
      "ampere per volt");
19  disp("transresistance  =    "+string((tranre))+
      "ohm");
20  disp("input resistance  =    "+string((ri))+
      "ohm");
21  disp("output resistance =    "+string((outres))+
      "ohm");

```

Chapter 11

Sinusoidal Oscillators

Scilab code Exa 11.2 example 2

```
1 //pagenumber 514 example 2
2 clear
3 macapa=900*10^-12; //farad
4 micapa=90*10^-12; //farad
5 r=100*10^3; //ohm
6 //(a) frequency range
7 fremin=1/(2*3.14*r*macapa);
8 disp("min frequency    =    "+string((fremin))+ " hertz"
9      );
9 fremax=1/(2*3.14*r*micapa);
10 disp("max frequency    =    "+string((fremax))+ " hertz"
11      );
11 //(b) r3
12 r=10*10^3; //ohm
13 r3=2*r;
14 disp("resistance r3    =    "+string((r3))+ " ohm");
```

Scilab code Exa 11.3 example 3

```
1 //pagenumber 516 example 3
2 clear
3 c1=0.004*10^-6; //farad
4 c2=0.03*10^-6; //farad
5 induct=4*10^-3; //henry
6 //min voltage
7 mivolt=c2/c1;
8 disp("min voltage   >=   "+string((mivolt))+ " volt");
9 //frequency
10 freque=((1/(2*3.14)))*sqrt((c1+c2)/(induct*c1*c2))
    ;
11 disp(" frequency   =   "+string((freque))+ " hertz");
```

Scilab code Exa 11.5 example 5

```
1 //pagenumber 517 example 5
2 clear
3 induct=500*10^-6; //henry
4 induc1=5000*10^-6; //henry
5 mutuin=300*10^-6; //henry
6 c1=150*10^-12; //farad
7 //(a) frequency
8 indcto=induct+induc1+2*mutuin;
9 freque=1/((2)*3.14*sqrt(indcto*c1));
10 //(b) condition
11 r=10*10^3; //ohm
```

```

12 conduc=8*10^-3; //ampere per volt
13 r1=50*10^3; //ohm
14 r'=r*r1/(r+r1);
15 volgai=conduc*r';
16 disp("frequency = "+string((freque))+ "hertz");
17 ratio1=(induc1+mutuin)/(induct+mutuin);
18 ratio1=ratio1*volgai;
19 disp("ratio1 greater than 1 so oscillations possible
      ");

```

Scilab code Exa 11.6 example 6

```

1 //pagenumber 518 example 6
2 clear
3 cgs=5*10^-12; //farad
4 cds=1*10^-12; //farad
5 conduct=10*10^-3; //ampere per volt
6 rd=50*10^3; //ohm
7 r=10*10^6; //ohm
8 induct=0.5; //henry
9 c1=0.05*10^-12; //farad
10 rse=1*10^3; //ohm
11 c=1*10^-12; //farad
12 //(1) c11
13 c11=(((cds*cgs)/(cds+cgs))+1)*c1)/(((cds*cgs)/(cds+
      cgs))+1+c1);
14 disp("resonating capacitance = "+string((c11))+
      " farad");
15 //(2) frequency
16 freque=((sqrt(2))/(2*3.14*sqrt(induct*c11)));
17 disp("resonant frequency = "+string((freque))+
      " hertz");
18 //(3) frequency parallel

```



```

19
20 freque=1/(2*3.14*sqrt(((induct*c*c1))/(c+c1)));
21 disp("parallel resonant frequency = "+string((
    freque))+ "hertz");
22 //frequency series
23 freque=1/((2*3.14*sqrt(induct*c1)));
24 disp("series resonant frequency = "+string((
    freque))+ "hertz");
25 qualit=((induct/c1)^(0.5))/rse;
26 disp("quality factor = "+string((qualit)));//
    correction in book
27 //(4) loop gain
28 abeta1=conduct*rd*cds/cgs;
29 disp("loop gain = "+string((abeta1)));
30 //(5)
31 w=r*(cgs+cds);
32 disp("bias = "+string((w))+ "second");

```

Scilab code Exa 11.7 example 7

```

1 //pagenumber 519 example 7
2 clear
3 c=200*10^-12;//farad
4 c1=1000*10^-12;//farad
5 induct=100*10^-6;//henry
6 //(1) frequency
7 ceq=(c*c1)/(c+c1);
8 freque=1/(2*3.14*(sqrt(induct*ceq)));
9 disp("frequency = "+string((freque))+ "hertz");//
    correction in the book
10 gaimin=c1/c;
11 disp("gain = "+string((gaimin)));

```

Scilab code Exa 11.8 example 8

```
1 //pagenumber 520 example 8
2 clear
3 induc1=0.4*10^-3; //henry
4 c=0.004*10^-6; //farad
5 freque=120*10^3; //hertz
6 induct=((1/(4*3.14^2*freque^2*c)))-induc1;
7 disp("inductance = "+string((induct))+ "henry");
```

Scilab code Exa 11.9 example 9

```
1 //pagenumber 520 example 9
2 clear
3 induct=0.33; //henry
4 c=0.065*10^-12; //farad
5 c1=1*10^-12; //farad
6 r=5.5*10^3; //ohm
7 //(1) series resonant frequency
8 freque=(1/(2*(3.14)))*sqrt(1/((induct)*c));
9 disp("frequency = "+string((freque))+ "hertz");
10 //(2) exceed of frequency
11 ratio1=sqrt((1+(c/c1)))
12 disp("ratio parallel series = "+string((ratio1))
    ); //correction in the book
13 //(3) quality factor
14 qualit=(1/r)*sqrt(induct/c);
15
```

```
16 disp("quality factor = "+string((qualit)));
```

Chapter 12

Power Electronic Devices

Scilab code Exa 12.1 example 1

```
1 //pagenumber 553 example 1
2 clear
3 slope1=130;
4 trivol=15; //voltage
5 d=0.5; //watts
6 ig=sqrt(d/slope1);
7 vg=slope1*ig;
8 r=(trivol-vg)/ig;
9
10 disp("source resistance = "+string((r))+ "ohm");
```

Scilab code Exa 12.2 example 2

```
1 //pagenumber 553 example 2
2 clear
```

```

3 latcur=50*10^-3; // ampere
4 durpul=50*10^-6; // second
5 induct=0.5; // henry
6 r=20; // ohm
7 voltag=100; // volt
8 w=induct/r;
9 inpcur=-(voltag/r)*((1)-exp(-durpul/w));
10 disp("current = "+string(abs(inpcur))+ " ampere");
11 disp("input current less than required current");

```

Scilab code Exa 12.3 example 3

```

1 //pagenumber 554 example 3
2 clear
3 latcur=4*10^-3; // ampere
4 induct=0.1; // henry
5 voltag=100; // volt
6 durmin=induct*latcur/voltag;
7 disp("min duration = "+string((durmin))+ " second"
);

```

Scilab code Exa 12.4 example 4

```

1 //pagenumber 554 example 4
2 clear
3 slope1=3*10^3;
4 egs=10; // volt
5 d=0.012; // watts
6 ig=sqrt(d/slope1);

```

```
7 vg=slope1*ig;
8 r=(egs-vg)/ig;
9
10 disp("source resistance = "+string((r))+ "ohm");
    //it is not given in the book
```

Scilab code Exa 12.5 example 5

```
1 //pagenumber 554 example 5
2 clear
3 slope1=16;
4 durmax=4*10^-6; //second
5 curmin=500*10^-3; //ampere
6 voltag=15; //voltage
7 //(1) resistance
8 vg=slope1*curmin
9 r=(voltag-vg)/curmin;
10 //(2)
11 d=vg*curmin;
12 freque=0.3/(d*durmax);
13 disp("resistance = "+string((r))+ "ohm");
14
15
16 disp("frequency = "+string((freque))+ "hertz");
```

Scilab code Exa 12.6 example 6

```
1 //pagenumber 555 example 6
2 clear
```

```

3 c1=20*10^-12; //farad
4 limcur=16*10^-3; //ampere
5 w=(limcur/c1)*10^-6; //convert second to microsecond
6 disp(" change of voltage    =    "+string((w))+ " volt
      per microsecond");

```

Scilab code Exa 12.7 example 7

```

1 //pagenumber 555 example 7
2 clear
3 ratcur=3000; //ampere
4 freque=50; //hertz
5 i=sqrt(ratcur^2/2);
6 disp(" current    =    "+string((i))+ " ampere");
7 i=((ratcur)/sqrt(2))^2/(2*freque);
8 disp(" current    =    "+string((i))+ " ampere square
      second");

```

Scilab code Exa 12.9 example 9

```

1 //pagenumber 556 example 9
2 clear
3 voltag=30; //voltage
4 w=0.51;
5 i1=10*10^-6; //ampere
6 v1=3.5; //voltage
7 curen1=10*10^-3; //ampere
8 freque=60; //hertz
9 tridun=50*10^-6; //second

```

```

10 pinvol=w*voltag+0.6;
11 r=(voltag-pinvol)/i1;
12 disp("max limit resistance    =    "+string((r))+ "ohm"
    );
13 r=(voltag-v1)/(curen1);
14 disp("min limit resistance    =    "+string((r))+ "ohm"
    );
15 capac1=0.5*10^-6; //farad
16 r=(1/freque)*(1/(capac1*log(1/(1-w))));
17 disp("resistance            =    "+string((r))+ "ohm");
18 rb2=10^4/(w*voltag);
19 rb1=tridun/capac1;
20 disp("rb1            =    "+string((rb1))+ "ohm");
21 disp("rb2            =    "+string((rb2))+ "ohm");
22 disp("peak voltage      =    "+string((pinvol))+ "volt");

```

Scilab code Exa 12.10 example 10

```

1 //pagenumber 557 example 10
2 clear
3 re=1*10^3; //ohm
4 i1=5*10^-3; //ampere
5
6 voltag=re*i1+2;
7 disp("voltage      =    "+string((voltag))+ "volt");
8
9
10 disp("this voltage makes to off");

```

Chapter 13

Cathode Ray Oscilloscope

Scilab code Exa 13.1 example 1

```
1 //pagenumber 578 example 1
2 clear
3 quanti=3*10^17;
4 voltag=10*10^3; // volt
5 distan=40*10^-3; //metre per minute
6 w=quanti*1.6*10^-19*voltag
7 w=w/60; //per second
8
9
10 disp("power to electrons    =    "+string((w))+ " watts"
      );
```

Scilab code Exa 13.2 example 2

```

1 //pagenumber 578 example 2
2 clear
3 sensit=5; // per centimetre
4 q=50*10^-6; //second per centimetre
5 petope=5.4; //centimetre
6 horiax=8.4; //centimetre
7 voltag=petope*sensit;
8 voltag=voltag/((2)*sqrt(2));
9 //one cycle
10 horiax=(horiax/2)*q;
11 freque=1/horiax;
12 disp("input voltage = "+string((voltag))+ " volt")
    ;
13 disp("frequency = "+string((freque))+ " hertz");
14
15
16 disp("vm1coswt vm2sinwt squaring and adding gives
    ellipse");

```

Scilab code Exa 13.3 example 3

```

1 //pagenumber 579 example 3
2 clear
3 voltag=1000; // volt
4 //(1) velocity
5 vx=sqrt(2*1.6*10^-19*(voltag)/(9.11*10^-31));
6 disp("velocity x = "+string((vx))+ " metre per
    second");
7 vox=1*10^5; //metre per second intial velocity
8 vx=sqrt((vox)+((2*1.6*10^-19*voltag)
    /(2.01*1.66*10^-27)));
9
10 disp("velocity x = "+string((vx))+ " metre per

```

```
second");
```

Scilab code Exa 13.4 example 4

```
1 //pagenumber 580 example 4
2 clear
3 voltag=2000; // volt
4 d=15; //centimetre
5 d1=3; //centimetre
6 r1=((d^2+d1^2)/(6))*10^-2; //centimetre to metre
7 vox=sqrt(2*1.6*10^-19*(voltag)/(9.11*10^-31));
8 b=vox/((1.6*10^-19*r1)/(9.11*10^-31));
9
10 disp("transverse magnetic field    =    "+string((b))+
      "weber per metre square");
```

Scilab code Exa 13.5 example 5

```
1 //pagenumber 581 example 5
2 clear
3 voltag=2000; // volt
4 d=2*10^-2; //metre
5 //(1) frequency
6 vx=sqrt(2*1.6*10^-19*(voltag)/(9.11*10^-31));
7 durati=d/vx;
8 freque=1/(2*durati);
9 disp("max frequency    "+string((freque))+ "hertz");
10 //(2)
11 durati=60*durati;
```

```
12 disp("duration electron between the plates = "+
    string((durati))+ "second"); //correction in book
```

Scilab code Exa 13.7 example 7

```
1 //pagenumber 582 example 7
2 clear
3 voltag=800; // volt
4
5
6 q=1.6*10^-19; //coulomb
7 m=9.11*10^-31; //kilogram
8 vox=sqrt(2*q*voltag/m);
9
10 disp("max velocity "+string((vox))+ "metre per
    second");
```

Scilab code Exa 13.8 example 8

```
1 //pagenumber 582 example 8
2 clear
3 voltag=2000; // volt
4 d=1.5*10^-2; //centimetre
5 d1=5*10^-3; //metre
6 distan=50*10^-2; //metre
7 //(1) velocity
8 vox=sqrt(2*1.6*10^-19*(voltag)/(9.11*10^-31));
9 //(2) sensitivity
10 defsen=distan*d/(2*d1*voltag);
```

```

11 //deflection factor
12 g=1/defsen;
13 disp(" velocity    =    "+string((vox))+ "metre per
    second");
14 disp(" sensitivity    =    "+string((defsen))+ "metre
    per volt");
15
16 disp(" deflection factor    =    "+string((g))+ " volt
    per metre"); //correction in the book

```

Scilab code Exa 13.9 example 9

```

1 //pagenumber 582 example 9
2 clear
3 voltag=2000; // volt
4 d=50*10^-3; //metre
5 //(1) velocity
6 vox=sqrt(2*1.6*10^-19*(voltag)/(9.11*10^-31));
7 disp(" velocity    =    "+string((vox))+ "metre per
    second");
8 //(2) fc
9 fc=vox/(4*d);
10
11 disp(" fc    =    "+string((fc))+ " hertz");

```

Scilab code Exa 13.10 example 10

```

1 //pagenumber 582 example 10
2 clear

```

```
3 y=2.5; // divisions
4 y1=1.25; // divisions
5 y=y1/y;
6 w=asind(y);
7 disp("phase angle = "+string((w))+ " degree");
```
