

Scilab Textbook Companion for
Basic Electronics
by A. P. Godse and U. A. Bakshi¹

Created by
Boston Shullai
engineering
Others
Sri Jayachamarajendra College of Engineering.
College Teacher
None
Cross-Checked by
Bhavani Jalkrish

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Basic Electronics

Author: A. P. Godse and U. A. Bakshi

Publisher: Technical Publications, Pune

Edition: 1

Year: 2006

ISBN: 8184310811

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
2 Semiconductor Devices	6
3 Diode applications	17
4 Transistors	42
5 Biasing methods	45
6 Power control Devices	59
7 Junction field effect transistors	63
8 Amplifiers	65
9 Oscillators	67
10 Introduction to Operational Amplifiers	75
11 Cathode Ray Oscilloscope CRO	93
12 Communication Systems	95
13 Number Systems	117

List of Scilab Codes

Exa 2.1	Dc reverse Resistance	6
Exa 2.2	Dynamic forward resistance	6
Exa 2.3	Current through the resistance	7
Exa 2.4	Forward current through the diode	8
Exa 2.5	Piece Wise linear characteristic of a Diode	8
Exa 2.6	Load resistance Rl	9
Exa 2.7	New supply voltage	10
Exa 2.8	Pn junction diode current	12
Exa 2.9	Maximum forward current	12
Exa 2.10	Forward voltage drop	13
Exa 2.11	Dynamic resistance	13
Exa 2.12	Maximum reverse recovery time	14
Exa 2.13	Derated power rating	14
Exa 2.14	Zener resistance	14
Exa 2.15	voltage across the terminal	15
Exa 2.16	maximum zener current	15
Exa 2.17	Zener diode current and power dissipation	16
Exa 3.1	RMS value of current output voltage efficiency	17
Exa 3.2	Dc output voltage	18
Exa 3.3	Dc voltage and load current	18
Exa 3.4	Average output voltage	19
Exa 3.5	1Power 2Percentage regulation 3efficiency of rectification and 4TUF	19
Exa 3.6	Peak to peak value of output voltage	20
Exa 3.7	1no load Dc voltage 2output voltage at 100mA 3percentage regulation	21
Exa 3.8	Input power from the transformer	21
Exa 3.9	1Average voltage 2efficiency	22

Exa 3.10	Load current and rms value of input current	22
Exa 3.11	resistance of the load and efficiency	23
Exa 3.12	1Dc load current 2Dc load voltage 3ripple voltage 4PIV ratings of the diode	24
Exa 3.13	Load voltage and ripple voltage	24
Exa 3.14	Average load current and efficiency	25
Exa 3.15	1Dc output voltage 2ripple factor 3efficiency 4PIV	25
Exa 3.16	1Average Dc voltage 2Average Dc current 3frequency of output wave forms	26
Exa 3.17	1Ripple voltage 2ripple factor	27
Exa 3.18	1Dc output voltage 2rms value of of ripple voltage 3ripple factor	27
Exa 3.19	Load voltage and ripple voltage	28
Exa 3.20	Value of capacitor C	29
Exa 3.21	Ripple factor	29
Exa 3.22	surge current	30
Exa 3.23	Rms value of ripple voltage and peak to peak voltage	30
Exa 3.24	Dc output voltage and ripple factor	31
Exa 3.25	Value of the capacitance needed	31
Exa 3.26	Ripple factor	32
Exa 3.27	minimum value of capacitor	32
Exa 3.28	Value of the capacitor required	33
Exa 3.29	1Average Dc current 2Average Dc voltage 3Ripple voltage	33
Exa 3.30	Load regulation	34
Exa 3.31	Percentage load regulation	34
Exa 3.32	Source regulation and percentage source regulation	35
Exa 3.33	Range of input voltage	35
Exa 3.34	design of zener diode	36
Exa 3.35	Minimum and maximum load current	37
Exa 3.38	Design of zener diode	38
Exa 3.39	Design of Voltage regulator	39
Exa 3.40	series resistance and diode current	39
Exa 3.41	Design of zener regulator	40
Exa 4.1	Base current	42

Exa 4.2	Dc current gain and voltage gain	42
Exa 4.3	Dc voltage gain and current gain	43
Exa 4.4	current gain and emitter current	43
Exa 5.1	Calculation of Ib Ic and Vce and the region of operation	45
Exa 5.2	Minimum and maximum values of Ic and Vce	47
Exa 5.3	Calculation of Q point values	48
Exa 5.4	Calculation of minimum and maximum values of Ic and Vce	48
Exa 5.5	Calculation of Vce and Ic	49
Exa 5.6	Determination of Ic Ve and Vce	50
Exa 5.7	Minimum and maximum values of Ic and Vce	51
Exa 5.8	Design of a fixed biased circuit	52
Exa 5.9	Design of Collector to base bias circuit . . .	52
Exa 5.10	Design of voltage divider bias circuit	53
Exa 5.11	Stability factor	54
Exa 5.12	Resistance Rb	55
Exa 5.13	Calculation of R1 and R3	56
Exa 5.14	Calculation of Re Vce and stability factor .	57
Exa 5.15	Determination of percent change in Q values	57
Exa 6.1	Finding of various ratings of SCR	59
Exa 6.2	Designing values of R1 R2 and R3	60
Exa 6.3	Frequency of oscillations	61
Exa 6.4	Frequency of oscillations	61
Exa 6.5	Range of Rt	62
Exa 7.1	Drain current	63
Exa 7.2	1maximum and minimum od output voltage 2voltage gain	64
Exa 8.1	Gain in dB scale	65
Exa 8.2	Maximum voltage gain	65
Exa 8.3	Gain of an amplifier	65
Exa 8.4	Gain of an amplifier	66
Exa 9.1	Frequency of oscillations	67
Exa 9.2	Design of an RC phase shift oscillator . . .	67
Exa 9.3	estimation of R and C	68
Exa 9.4	Frequency of oscillations	68
Exa 9.5	Value of capacitor C	69
Exa 9.6	Frequency of oscillation	69

Exa 9.7	value of inductance L	70
Exa 9.8	designing the value of inductor L	70
Exa 9.9	Frequency of oscillation	70
Exa 9.10	Range for the capacitor C	71
Exa 9.11	Range of capacitor C	72
Exa 9.12	1series resonant frequency 2parallel resonant frequency 3percentage that the parallel resonant frequency exceeds the series resonant frequency 4Q factor	72
Exa 9.13	Series and parallel resonant frequency	73
Exa 10.1	Output voltage	75
Exa 10.2	Input bias current and input offset current .	76
Exa 10.3	Values of two input bias current	76
Exa 10.4	Voltage gain	77
Exa 10.5	Output voltage and waveforms	77
Exa 10.6	Reading of output voltage on the voltmeter	79
Exa 10.7	Voltage gain and output waveforms	80
Exa 10.8	Feedback resistor R _f	81
Exa 10.9	Gain and output voltage	82
Exa 10.10	Closed loop gain and feedback resistance .	83
Exa 10.11	Output voltage V _o	84
Exa 10.12	Otuput voltage V _o	84
Exa 10.13	Output voltage V _o	86
Exa 10.14	Design of Scaling adder	86
Exa 10.15	Relation between R _f and R	87
Exa 10.16	Output voltage	87
Exa 10.17	Output voltage	88
Exa 10.18	Output voltage	89
Exa 10.19	Output voltage	89
Exa 10.20	Design of adder circuit	90
Exa 10.21	Design of an Opamp circuit	90
Exa 10.22	Output voltage	91
Exa 11.1	Amplitude and rms value of sinusoidal voltage	93
Exa 11.2	Rms voltage and frequency	94
Exa 12.1	Modulation index and percentage modulation	95
Exa 12.2	Lower and upper side band frequency	95
Exa 12.3	AM modulated waveform	96

Exa 12.4	1Modulation index 2sideband frequencies and amplitude 3bandwidth 4total power 5transmission efficiency	98
Exa 12.5	Total power	99
Exa 12.6	Power of each sidebands	99
Exa 12.7	Antenna current	100
Exa 12.8	modulation index	100
Exa 12.9	modulation index	100
Exa 12.10	modulation index and total radiated power	101
Exa 12.11	Carrier power	101
Exa 12.12	Frequencies	102
Exa 12.13	Total sideband power radiated	102
Exa 12.14	Current I	103
Exa 12.15	Current and percentage power swing	103
Exa 12.16	1Carrier frequency 2modulating frequency 3carrier power 4total power output 5peak power output	104
Exa 12.17	Equation of the wave and output wave form	105
Exa 12.18	Percentage power saving	106
Exa 12.19	frequency deviation and modulation index	107
Exa 12.20	Frequency deviation and modulation index	108
Exa 12.21	Maximum deviation and modulation index	109
Exa 12.22	Peak frequency deviation modulation index	109
Exa 12.23	1carrier and modulating frequency 2modulation index and maximum deviation 3Power dissipated	110
Exa 12.24	sketching the spectrum of the modulated FM wave	111
Exa 12.25	Percent modulation	112
Exa 12.26	Frequency deviation and carrier swing	113
Exa 12.27	1Carrier swing 2highest and lowest frequencies 3modulation index	114
Exa 12.28	1Frequency deviation 2carrier swing 3lowest frequency reached	114
Exa 12.29	modulation index	115
Exa 12.30	1Carrier swing 2frequency deviation 3carrier frequency 4modulation index	115

Exa 13.1	Represesntation of a number 98point72 in powers of 10	117
Exa 13.2	1101point101 in power of 2 and its decimal equivalent	117
Exa 13.3	567 in power of 8 and its decimal equivalent	118
Exa 13.4	3FD in power of 16 and its decimal equivalent	118
Exa 13.5	decimal equivalent of 231point23 with base 4	119
Exa 13.6	counting from 0 to 9 in radix 5	119
Exa 13.7	111101100 with base 2 to octal equivalent	119
Exa 13.8	634 with base 8 to binary equivalent	120
Exa 13.9	725point63 with base 8 to binary equivalent	120
Exa 13.10	1101100010011011 with base 2 to hexadecimal equivalent	121
Exa 13.11	3FD with base 16 to binary equivalent	122
Exa 13.12	5A9pointB4 with base 16 to binary equivalent	122
Exa 13.13	615 with base 8 to hexadecimal equivalent	123
Exa 13.14	25B with base 16 to octal equivalent	123
Exa 13.15	1101point1 with base 2 to decimal equivalent	124
Exa 13.16	475point25 with base 8 to decimal equivalent	124
Exa 13.17	9B2point1A with base 16 to decimal equivalent	125
Exa 13.18	3102point12 with base 4 to decimal equivalent	125
Exa 13.19	614point15 with base 7 to decimal equivalent	125
Exa 13.20	37 with base 10 to binary equivalent	126
Exa 13.21	214 with base 10 to octal equivalent	126
Exa 13.22	3509 with base 10 to hexadecimal equivalent	126
Exa 13.23	54 with base 10 to radix 4	127
Exa 13.24	point8125 with base 10 to binary equivalent	127
Exa 13.25	point95 with base 10 to binary equivalent	128
Exa 13.26	point640625 with base 10 to octal equivalent	128
Exa 13.27	point1289062 with base 10 to hexadecimal equivalent	129
Exa 13.28	24point6 with base 10 to binary equivalent	130
Exa 13.29	35point45 with base 10 to octal equivalent	131
Exa 13.30	22point46 with base 10 to hexadecimal equivalent	132
Exa 13.31	convert the given binary nos to dec hex and oct	135
Exa 13.32	2AC5pointD with base 16 to dec oct and bin	139

Exa 13.33	determination of the value of base x	141
Exa 13.34	1s complement of 1101	143
Exa 13.35	1s complement of 10111001	143
Exa 13.36	2s complement of 1001	143
Exa 13.37	2s complement of 10100011	144
Exa 13.38	7s complement of 612	144
Exa 13.39	8s complement of 346	145
Exa 13.40	15s complement of A9B	145
Exa 13.41	16s complement of A8C	145
Exa 13.42	binary addition	146
Exa 13.43	addition of 28 and 15 in binary	146
Exa 13.44	subtraction of 0101 from 1011	147
Exa 13.45	subtraction of 101011 from 111001 using 1s complement	147
Exa 13.46	subtraction of 111001 from 101011 using 1s complement	148
Exa 13.47	subtraction of 101011 from 111001 using 2s complement	149
Exa 13.48	subtraction of 111001 from 101011 using 2s complement	149
Exa 13.49	expression of the given decimal nos in 1s and 2s complement	150
Exa 13.50	decimal nos subtraction using 2s complement	151
Exa 13.51	binary nos subtraction using 1s and 2s complement	152
Exa 13.52	addition of octal nos	154
Exa 13.53	octal nos addition	155
Exa 13.54	octal nos addition	156
Exa 13.55	7s complement of 612	156
Exa 13.56	subtract 157 from 176 using 7s complement	157
Exa 13.57	subtract 243 from 153 using 7s complement	158
Exa 13.58	8s complement of 346	158
Exa 13.59	subtract 413 from 516 using 8s complement	159
Exa 13.60	subtract 451 from 316 using 8s complement	159
Exa 13.61	hexadecimal addition	160
Exa 13.62	hexadecimal addition	161
Exa 13.63	hexadecimal addition	162
Exa 13.64	15s complement of A9B	162

Exa 13.65	subtraction of 98F from B02 using 15s complement	163
Exa 13.66	subtraction of C14 from 69B using 15s complement	164
Exa 13.67	16s complement of A8C	164
Exa 13.68	subtraction of 972 from CB2 using 16s complement	165
Exa 13.69	subtraction of 854 from 3B7 using 16s complement	165
Exa 13.70	decimal addition in 8421BCD	166
Exa 13.71	decimal subtraction in 8421BCD using 9s complement method	171
Exa 14.1	Representation of the given boolean expression	175
Exa 14.2	Implementation of EXNOR gate using NAND gate	175
Exa 14.3	Implementation of EXNOR gate using NOR gate	176
Exa 14.4	Boolean Solutions	176
Exa 14.5	Boolean Solutions	177
Exa 14.6	Boolean Solutions	177
Exa 14.7	Boolean Solutions	177
Exa 14.8	Boolean Solutions	178
Exa 14.9	Boolean Solutions	178
Exa 14.10	Boolean Solutions	179
Exa 14.11	Boolean Solutions	179
Exa 14.12	Boolean Solutions	180
Exa 14.13	Boolean Solutions	180
Exa 14.14	Boolean Solutions	181
Exa 14.15	Boolean Solutions	182
Exa 14.16	Boolean Solutions	182
Exa 14.17	Boolean Solutions	183
Exa 14.18	Boolean Solutions	184
Exa 14.19	construction of the given logic circuit using AND OR and INVERTER logic	184
Exa 14.20	truth table of the given logic expression	185
Exa 14.21	simplification of the given logic expression	186
Exa 14.22	simplification of the given logic expression using Demorgans theorem	186

List of Figures

10.1 Output voltage and waveforms	79
10.2 Output voltage and waveforms	80
10.3 Voltage gain and output waveforms	81
10.4 Otuput voltage Vo	86
12.1 Equation of the wave and output wave form	106
12.2 sketching the spectrum of the modulated FM wave	112

Chapter 2

Semiconductor Devices

Scilab code Exa 2.1 Dc reverse Resistance

```
1 //Ex-2.1 Pg-2.18
2 clc;
3 clear;
4 Vf=0.2; //voltage in volts
5 Vr=60; //voltage in volts
6 If=60*10^(-3); //current in ampere
7 I0=0.025*10^(-3); //current in ampere
8 Rf=Vf/If; //forward resistance
9 Rr=Vr/I0; //reverse resistance
10 Rr=Rr*1e-6
11 printf("the equivalent resistance are Rf=%f ohm
           and Rr=%f M ohm",Rf,Rr)
```

Scilab code Exa 2.2 Dynamic forward resistance

```
1 //Chapter-2 Ex-2.2 Pg-2.18
2 clc
3 clear;
```

```

4 disp(" refer to the Figure -2.19 given ")
5 disp(" from the characteristics at point P, Vf=0.7V,
     If=60mA")
6 Vf=0.7;
7 If=0.06;
8 Rf=Vf/If; //DC forward resistance
9 printf("\n DC forward resistance Rf : %.2f ohm\n",Rf
      )
10 disp(" as the forward voltage changes from P to Q")
11 delta_Vf=0.77-.7;
12 delta_If=(120-60)*10^(-3);
13 rf=delta_Vf/delta_If; //dynamic forward resistance
14 printf("\n Dynamic forward resistance rf : %.3f ohm"
      ,rf)

```

Scilab code Exa 2.3 Current through the resistance

```

1 //Ex2_3 Pg-2-22
2 clc
3 clear;
4 disp(" Refer to the figure -2.24 shown ")
5 disp(" since Rf=0 The circuit becomes as shown in
     figure -2.24(a)")
6 V=10; //supply voltage
7 Rf=0; //forward resistance
8 Rl=1; //load resistance in k ohm
9 Vin=0.7; //cut in voltage
10 Il=(V-Vin)/Rl; //applying KVL to the loop
11 If=Il;
12 printf("\n \n current through the resistance Il=If =
     is %.1f mA",If)
13 Vl=Il*Rl;
14 printf("\n \n voltage across Rl is %.1f V",Vl)
15 Pd=If*Vin;
16 printf("\n \n diode power Pd = %.2f mW",Pd)

```

```
17 P1=I1*V1;
18 printf("\n \n load power P1 = %.2f mW",P1)
```

Scilab code Exa 2.4 Forward current through the diode

```
1 //EX2_4 PG-2.23
2 clc
3 disp("Refer the Figure -2.25 shown")
4 disp("When forward resistance Rf is neglected then")
5 disp("the diode behaves as a battery as shown in
Figure -2.25(a)")
6 Vf=0.7; //cut-in voltage
7 V=10; //supply voltage
8 Rl=500; //load resistance
9 If=(V-Vf)/Rl; //applying KVL to the circuit
10 If=If*1e3
11 printf("\n Forward current is %.2f mA\n",If)
12 disp("When forward resistance is Rf is 3.2 Ohm then")
13 disp("the equivalent circuit is as shown in fig
-2.25(b)")
14 Rf=3.2;
15 If=(V-Vf)/(Rl+Rf); //applying KVL to the circuit
16 If=If*1e3
17 printf("\n therefore Forward current is %.4f mA",If)
```

Scilab code Exa 2.5 Piece Wise linear characteristic of a Diode

```
1 //EX2_5 PG-2.23
2 clc
3 If=80e-3; //maximum forward current
4 Rf=0.4; //dynamic resistance
```

```

5 Vin=0.3; //cut-in voltage for germanium
6 disp("when forward current is zero then")
7 Vf=Vin; //voltage across the diode
8 printf(" voltage across the diode is %1.1f V\n",Vf)
9 disp("when forward current is 80mA then")
10 Vf=Vin+If*Rf;
11 printf(" voltage across the diode is %1.3f V",Vf)
12 clf()
13 x=[0 .1 .2 .3 .332]; //x-coordinate
14 y=[0 0 0 0 80]; //y-coordinate
15 plot2d(x,y)
16 xlabel('voltage across the diode (V)');
17 ylabel('current (mA)');
18 title('Piecewise linear characteristic')
19 xgrid(color("grey"));

```

Scilab code Exa 2.6 Load resistance Rl

```

1 //EX2_6 PG-2.28
2 clc
3 disp("Refer to the Figure:2.29 shown")
4 If=25e-3; //current at Q-point
5 disp("for Q point If=25mA, ie Iq=25mA")
6 disp("for If=0 A, Vf=Vin=3V at point B")
7 disp("Now we draw the graph")
8 disp("The coordinates are Q=(1V,25mA) B=(3V,0mA)")
9 clf()
10 x=[ 0 0.5 0.6 1 1.1 ]; //x-coordinate
11 y=[ 0 1 5 25 30 ]; //y-coordinate
12 plot(x,y,)
13 x1=[0.5 1 3]; //x-coordinate
14 y1=[ 31 25 0]; //y-coordinate
15 plot(x1,y1)
16 x2=[ 0 1];
17 y2=[25 25];

```

```

18 plot2d(x2,y2,style=6)
19 xlabel('Vf (volts)');
20 ylabel('If (mA)');
21 title("Piece-wise linear characteristic")
22 xgrid(color("red"));
23 disp("Q-point is denoted by the intersection of two
      lines as shown in the plot")
24 delta_If=10e-3; //from the graph plotted
25 delta_Vf=0.9; //from the graph plotted
26 s=delta_If/delta_Vf; //slope
27 disp("Therefore load resistance is the reciprocal of
      the slope ")
28 Rl=1/s; //load resistance
29 printf("\n required load resistance is %.0f ohm",Rl)

```

Scilab code Exa 2.7 New supply voltage

```

1 //EX2_7 PG-2.29
2 clc
3 Rl=150; //load resistance
4 If=35e-3; //current at which Q-point appears
5 disp("We draw the new DC load line in the plot")
6 s=-1/Rl; //slope
7 printf("\n slope is %f \n",s)
8 x=[ 0 0.5 1 1.1 1.15 ]; //x-coordinate
9 y=[ 0 1 25 35 40 ]; //y-coordinate
10 clf()
11 plot2d(x,y,style=2)
12 x1=[0 1.1 2.6 6.4 ]; //x-coordinate
13 y1=[42 35 25 0]; //y-coordinate
14 plot2d(x1,y1)
15 x2=[ 0 1 1.1]; //x-coordinate
16 y2=[35 35 35]; //y-coordinate
17 plot2d(x2,y2,style=5)
18 x3=[0 1 2.6]; //x-coordinate

```

```

19 y3=[25 25 25]; //y-coordinate
20 plot2d(x3,y3,style=4)
21 x4=[1.1 1.1 1.1];
22 y4=[ 0 10 35 ];
23 plot2d(x4,y4,style=6)
24 x5=[2.6 2.6];
25 y5=[0 25];
26 plot2d(x5,y5,style=7)
27 xlabel('Vf (volts)');
28 ylabel('If (mA)');
29 title("Piece-wise linear characteristic")
30 xgrid(color("gray"));
31 disp("The slope passes through the Q-point so the
      equation of the load ")
32 disp("line is If=(-Vf/Rl)+(Vin/Rl)")
33 disp("Now from the graph we can see that slope =(
      change in If)/(change in Vf)")
34 disp("For If=35 mA Vf=1.1 V")
35 disp("The coordinates are Q=(1.1V,35mA) C=(2.6V,25mA
      ) B=(6.4V,0mA)")
36 delta_If=10e-3;//change in If
37 delta_Vf=delta_If/abs(s);//change in Vf and we take
      only the magnitudeof the slope
38 printf("\n change in Vf is %1.1f V \n",delta_Vf)
39 disp("This is point C corresponding to If=35-10=35mA
      , as If is change by 10mA")
40 disp("and Vf=2.6V ")
41 disp("We join the Q-point and point C as shown in
      the plot to get the DC load")
42 disp(" line we extend the line to intersect point B
      ")
43 disp("the voltage at point B is the new supply
      voltage required")
44 printf("\n From the plot voltage at point B = 6.7 V"
      )

```

Scilab code Exa 2.8 Pn junction diode current

```
1 //EX2_8 PG-2.33
2 clc
3 V=0.22; //forward bias voltage
4 T=25+273; //room temperature in degree kelvin
5 I0=2e-3; //reverse saturation current
6 n=1; //for germanium diode
7 k=8.62e-5 //Boltzmann's constant
8 Vt=k*T;
9 I=I0*(exp(V/(n*Vt))); // diode current
10 printf("therefore the P-N junction diode current is
    %f A",I)
11 // in the book they have taken the approximate value
12 //hence the answer is slighty different. in the book
13 //Vt=0.02568(approx) whereas Vt=0.0256876(exact
    value)
```

Scilab code Exa 2.9 Maximum forward current

```
1 //EX2_9 PG-2.36
2 clc
3 P1=500e-3; //rated power rating of the diode
4 T1=27; //temperature in Degree Celsius
5 Df=4e-3; //Derating factor
6 disp("At temperature T=27 degree C")
7 disp("For silicon diode Vf=0.7 V is constant ")
8 Vf=0.7;
9 If1=P1/Vf;
10 printf("\n Therefore maximum forward current at T
        =27 degree C is %.4f A \n",If1)
11 disp("At temperature T=77 degree C")
```

```
12 T2=77; //temperature in degree celsius
13 P2=P1-(T2-T1)*Df; //rated power rating of the diode
   at T=77 degree C
14 If2=P2/Vf;
15 printf("\n Therefore maximum forward current at T=77
   degree C is %.4f A",If2)
```

Scilab code Exa 2.10 Forward voltage drop

```
1 //EX2_10 PG-2.37
2 clc
3 T1=27; //initial temperature
4 Vf1=0.7; //forward voltage
5 Vtc=-2.3e-3; //voltage temperature coefficient
6 disp("at T2=25 degree C")
7 T2=50;
8 Vf2=Vf1+((T2-T1)*Vtc)
9 printf("\n therefore forward voltage drop at 50
   degree C is %.4f V \n",Vf2)
10 disp("at T3=77 degree C")
11 T3=77;
12 Vf2=Vf1+((T3-T1)*Vtc)
13 printf("\n therefore forward voltage drop at 77
   degree C is %.3f V",Vf2)
```

Scilab code Exa 2.11 Dynamic resistance

```
1 //EX2_11 PG-2.38
2 clc
3 If=30e-3; //forward current
4 T1=25+273; //temperature in degree kelvin
5 disp("Therefore at a temperature of 25 Degree C ")
6 Rf=26e-3/If;
```

```
7 printf("\n dynamic resistance is %.3f ohm \n",Rf)
8 disp("Therefore at a temperature of 75 Degree C ")
9 T2=75+273 //Temperature in degree kelvin
10 Rf=Rf*(T2/T1);
11 printf("\n dynamic resistance is %.3f ohm",Rf)
```

Scilab code Exa 2.12 Maximum reverse recovery time

```
1 //EX2_12 PG-2.43
2 clc
3 Tf_min=1; //fall time in micro second
4 Trr_max=Tf_min/10
5 printf("the maximum recovery time is %.1f micro sec"
, Trr_max)
```

Scilab code Exa 2.13 Derated power rating

```
1 //EX2_13 PG-2.48
2 clc
3 PD_max=320e-3; //maximum power rating
4 T1=50; //temperature in degree celsius at which
        maximum power rating occurs
5 DF=2.3e-3; //Derating factor
6 disp("Therefore the derated power rating at a
        temperature T=100 Degree celsius")
7 T2=100;
8 PD=PD_max-DF*(T2-T1);
9 printf("\n is %.3f W",PD)
```

Scilab code Exa 2.14 Zener resistance

```
1 //EX2_14 PG-2.52
2 clc
3 Vzd=50e-3; //change in Vz
4 Izd=2.5e-3//change in Iz
5 Zz=Vzd/Izd; //zener resistance
6 printf("zener resistance Zz=%f ohm",Zz)
```

Scilab code Exa 2.15 voltage across the terminal

```
1 //EX2_15 PG-2.52
2 clc
3 rz=4; //zener diode resistance
4 Vz=5.1;
5 Iz=25e-3;
6 x=Iz*rz;
7 Vzz=Vz+x; //total terminal voltage across the diode
8 printf("Therefore total terminal voltage across the
diode Vz'=%fV",Vzz)
```

Scilab code Exa 2.16 maximum zener current

```
1 //EX2_16 PG-2.52
2 clc
3 Vz=6.8 //nominal voltage
4 Pd_max=500; //zener diode power loss in mW at 40
degree celsius
5 D=2.6; //Derating factor in mW/degree celsius
6 T1=40; //Temperature in degree celsius
7 Izm=Pd_max/Vz;
8 printf("At T=40 degree celsius maximum zener
current Izm=%f mA\n\n",Izm)
9 T2=100; //Temperature in degree celsius
10 delta_T=T2-T1; //change in temperature
```

```
11 Pd_derated=Pd_max-D*delta_T
12 Izm=Pd_derated/Vz;
13 printf(" At T=100 degree celsius maximum zener
           current Izm=%f mA\n\n",Izm)
```

Scilab code Exa 2.17 Zener diode current and power dissipation

```
1 //EX2_17 PG-2.52
2 clc
3 printf("Refer to the figure -2.51 shown\n")
4 printf(" We apply KVL across the circuit \n")
5 printf(" Therefore -Iz*R1-Vz+Vin = 0 \n")
6 Vin=15;
7 Vz=5.2;
8 R1=670;
9 Iz=(Vin-Vz)/R1;//zener diode current
10 Iz=Iz*1e3;//in mA
11 Pd=Vz*Iz;//power dissipation
12 printf("\n zener diode current Iz:%f mA\n power
           dissipation :%f mW ",Iz,Pd)
```

Chapter 3

Diode applications

Scilab code Exa 3.1 RMS value of current output voltage efficiency

```
1 //EX3_1 pg-3.14
2 clc
3 disp("Refer to the circuit diagram shown in figure
      -3.7")
4 Rf=75; //diode forward resistance
5 Rl=10e3; //load resistance
6 Rs=10; //transformer secondary resistance
7 Ep=230; //rms value of primary voltage
8 N2byN1=1/3; //turns ratio
9 Es=Ep*N2byN1; //rms value of secondary voltage
10 Esm=sqrt(2)*Es; //peak value of secondary voltage
11 Im=Esm/(Rs+Rf+Rl);
12 Im=Im*1e3;
13 printf("\n Therefore peak value of current is %.2f
      mA \n",Im)
14 Idc=Im/%pi;
15 printf("\n Average current is %.3f mA \n",Idc)
16 Irms=Im/2; //for half wave rectifier
17 printf("\n rms current is %.3f mA \n",Irms)
18 Idc1=Idc*1e-3;
19 Edc=Idc1*Rl;
```

```
20 printf("\n DC output voltage is %.2f V \n",Edc)
21 Pdc=Edc*Idc1;//Dc output power
22 Irms1=Irms*1e-3;
23 Pac=Irms1^2*(Rs+Rf+Rl); //AC output power
24 %n=Pdc/Pac*100; //efficiency
25 printf("\n Efficiency is %.2f %% \n",%n)
26 disp("Ripple factor for half wave rectifier is 1.21"
)
```

Scilab code Exa 3.2 Dc output voltage

```
1 //EX3_2 PG-3.15
2 clc
3 disp("Refer to the figure -3.8 shown")
4 Vin=0; //cut-in voltage for an ideal diode is zero
5 Rf=0; //forward resistance for an ideaal diode is
       zero
6 disp("For an ideal diode")
7Vm=15;
8 Vdc=-Vm/%pi;
9 printf("\n DC output voltage is %.2f V\n ",Vdc)
10 disp("-ve sign indicates that voltage is negative
      wrt ground")
11 disp("For a silicon diode Vin=0.7V ")
12 Vin=0.7;
13 Vdc=-(Vm-Vin)/%pi;
14 printf("\n DC output voltage is %.2f V\n ",Vdc)
15 disp("-ve sign indicates that voltage is negative
      wrt ground")
```

Scilab code Exa 3.3 Dc voltage and load current

```
1 //EX3_3 PG-3.16
```

```

2 clc
3 Rl=1; //load resistance in kohm
4 Vm=10;
5 disp("For an ideal diode Vin= 0V")
6 Vin=0; //for ideal diode
7 Rf=0; //for ideal diode
8 Edc=Vm/%pi;
9 Idc=Edc/Rl;
10 printf("\n Dc voltage is %.2f V and load current is
    %.2f mA \n",Edc ,Idc)
11 disp("For a silicon diode Vin=0.7 V")
12 Vin=0.7;
13 Edc=(Vm-Vin)/%pi;
14 Idc=Edc/Rl
15 printf("\n Dc voltage is %.2f V and load current is
    %.2f mA \n",Edc ,Idc)

```

Scilab code Exa 3.4 Average output voltage

```

1 //EX3_4 Pg3.16
2 clc
3 Esm=300; //peak rms voltage
4 Edc=Esm/%pi; //average output voltage
5 printf("\n average output voltage is %.3f V" ,Edc)

```

Scilab code Exa 3.5 1Power 2Percentage regulation 3efficiency of rectification and

```

1 //EX3_5 PG-3.28
2 clc
3 Es=30; //rms voltage
4 Rf=2;
5 Rs=8;
6 Rl=1e3; //in kohm

```

```

7 Esm=sqrt(2)*Es; //peak value of voltage
8 Im=Esm/(Rf+Rl+Rs); //peak value of current
9 Idc=2*Im/%pi; //average current for full wave
    rectifier
10 P=Idc^2*Rl;
11 printf(" Power delivered to the load is %.3f W \n",P
      )
12 Vdc_noload=2*Esm/%pi;
13 printf("\n Vnl=%f \n",Vdc_noload)
14 Vdc_fullload=Idc*Rl;
15 printf("\n Vfl=%.2f \n",Vdc_fullload)
16 %reg=(Vdc_noload-Vdc_fullload)/Vdc_fullload*100;
17 printf("\n percentage regulation is %f %% \n",%reg)
18 disp(" Efficiency of rectification =(DC output)/(AC
      output)")
19 x=(1+(Rf+Rs)/Rl)^(-1);
20 n=8/%pi^2*x*100;
21 printf("\n Efficiency of rectification is %.1f %% \n
      ",n)
22 Irms=Im/sqrt(2);
23 AC_rating=Es*Irms;
24 TUF=P/AC_rating;
25 printf("\n TUF of secondary is %.3f",TUF)
26 //The exact answer for percentage regulation is 1%
    not .97% as shown in the book ....
27 //because in the book it has rounded off the value
    27.009 to 27 only

```

Scilab code Exa 3.6 Peak to peak value of output voltage

```

1 //EX3_6 PG-3.29
2 clc
3 disp("Refer to the figure -3.16 shown")
4 Rl=100;
5 Idc=1; //maximum value of DC current in each diode

```

```

6 disp("We know Idc=Im/ pi for each diode")
7 Vm=%pi*Rl*Idc;
8 Vp=2*Vm;
9 printf("\n maximum peak to peak voltage is %.2f V" ,
Vp)

```

Scilab code Exa 3.7 1no load Dc voltage 2output voltage at 100mA 3percentage regul

```

1 //EX3_7 PG-3.30
2 clc
3 Rf=1;
4 Es=10;
5 Rs=5;
6 Esm=sqrt(2)*Es;
7 Edc_nl=2*Esm/%pi;
8 printf("Therefore o load DC output voltage is %.4f V
\n",Edc_nl)
9 Idc=100e-3;
10 disp("We know that Idc=2Im/ pi and Im=Esm/(Rf+rs+r1)")
11 Im=Idc*%pi/2;
12 Rl=Esm/Im-Rf-Rs; //load resistance
13 Edc.ol=Idc*Rl; //DC output voltage at 100mA
14 printf("\n DC output voltage at 100mA is %.4f V \n "
,Edc.ol)
15 %reg=(Edc_nl-Edc.ol)/Edc.ol*100;
16 printf("\n percentage regulation is %.2f %%",%reg)

```

Scilab code Exa 3.8 Input power from the transformer

```

1 //EX3_8 PG-3.31
2 clc
3 Pdc=500; //for half wave rectifier

```

```
4 %n=40.6; //maximum efficiency for half wave rectifier
5 disp(" We know that efficiency=Pdc/Pac ")
6 disp("for Half wave rectifier ")
7 Pac=Pdc/%n*100;
8 printf("\n AC input power is %.3f W \n",Pac)
9 disp("for Full wave rectifier ")
10 %n=81.2; //maximum efficiency for full wave rectifier
11 Pac=Pdc/%n*100;
12 printf("\n AC input power is %.3f W \n",Pac)
```

Scilab code Exa 3.9 Average voltage & efficiency

```
1 //EX3_9 PG-3.32
2 clc
3 Rf=10;
4 Rl=100;
5 Es=30; //transformer rms voltage
6 Esm=sqrt(2)*Es; //peak value of the voltage
7 Im=Esm/(Rf+Rl);
8 Idc=2*Im/pi;
9 Edc=Idc*Rl;
10 printf("Average voltage is %.2f V \n",Edc)
11 Pdc=Idc^2*Rl;
12 Irms=Im/sqrt(2); //rms value of the current
13 Pac=Irms^2*(Rf+Rl);
14 %n=Pdc/Pac*100;
15 printf("\n Efficiency is %.2f %% ",%n)
```

Scilab code Exa 3.10 Load current and rms value of input current

```
1 //EX3_10 PG-3.32
2 clc
3 Es=100; //rms value of current
```

```

4 Rf=50; //forward resistance
5 Rl=950;
6 Rs=0; //resistance of the transformer secondary which
       is assumed to be 0 ohm
7 Esm=sqrt(2)*Es;//peak value of the input voltage
8 Im=Esm/(Rs+Rl+Rf);
9 Irms=Im/sqrt(2);
10 printf("rms value of input current is %.4f A \n",
         Irms)
11 Idc=2*Im/pi;
12 printf("\n load value of current is %.4f A",Idc)

```

Scilab code Exa 3.11 resistance of the load and efficiency

```

1 //EX3_11 PG-3.38
2 clc
3 Rf=0.1;
4 Idc=10;
5 Rs=0;
6 Es=30; //rms value of input voltage
7 Esm=sqrt(2)*Es;//peak value of the input voltage
8 Im=Idc*pi/2; //DC output current
9 disp("We know that Im=Esm/(2Rf+Rs+Rl) for fullwave
       rectifier")
10 Rl=Esm/Im-2*Rf-0;
11 printf("\n Therefore load resistance is %.1f ohm \n",
         ,Rl)
12 Pdc=Idc^2*Rl; //Dc output power rating
13 Irms=Im/sqrt(2); //rms value of input current
14 Pac=Irms^2*(2*Rf+Rs+Rl); //Ac input power
15 %n=Pdc/Pac*100; //efficiency
16 printf("\n Therefore efficiency is %.2f %% \n",%n)

```

Scilab code Exa 3.12 1Dc load current 2Dc load voltage 3ripple voltage 4PIV rating

```
1 //EX3_12 PG-3.39
2 clc
3 Rl=5e3;
4 N1toN2=2; //transformer turns ratio
5 Ep=460; //rms value of primary voltage
6 Es=Ep/N1toN2;
7 Esm=sqrt(2)*Es; //peak value of the secondary voltage
8 Im=Esm/Rl; //We neglect forward diode resistance
9 Idc=2*Im/%pi;
10 printf("\n Therefore DC load current is %f A \n", Idc)
11 Edc=Idc*Rl;
12 printf("\n DC load voltage is %.3f V \n",Edc)
13 Rf=.482; //ripple factor for full bridge rectifier
14 Vrip=Rf*Edc; //ripple voltage
15 printf("\n Therefore ripple voltage is %.1f V \n", Vrip)
16 disp(" Peak value of bridge rectifier=PIV rating of each diode")
17 PIV=Esm;
18 printf("\n Therefore PIV rating of each diode is % .2f V",PIV)
```

Scilab code Exa 3.13 Load voltage and ripple voltage

```
1 //EX3_13 PG-3.40
2 clc
3 Ep=230; //rms value of primary voltage
4 N2toN1=1/15; //turns ratio
5 Rf=0; //diode is ideal
6 Rs=0; //transformer is ideal
7 Rl=50; //load resistance
8 Es=Ep*N2toN1; //rms value of primary voltage
```

```

9 Esm=sqrt(2)*Es; //peak value of input voltage
10 Im=Esm/(Rs+2*Rf+Rl);
11 Idc=2*Im/%pi;
12 Edc=Idc*Rl; //load voltage
13 printf("\n Therefore load voltage is %.1f V\n",Edc)
14 Rf=.482;//ripple factor for full wave rectifier
15 Vrip=Rf*Edc;//ripple voltage
16 printf("\n ripple voltage is %.4f V",Vrip)
17 //in the book the ripple voltage has been rounded
    off to
18 //6.6516V but the actual ans is 6.6539V

```

Scilab code Exa 3.14 Average load current and efficiency

```

1 //EX3_14 PG-3.40
2 clc
3 Rf=0;//diode forward resistance
4 Es=240;//rms value of supply voltage
5 Rl=48;//load resistance
6 Im=sqrt(2)*Es/(Rl+Rf);
7 Idc=2*Im/%pi;
8 printf(" Average load current is %.3f A \n",Idc)
9 Pdc=Idc^2*Rl;
10 Irms=Im/sqrt(2); //rms value of input current
11 Pac=Irms^2*Rl;
12 %n=Pdc/Pac*100;//efficiency
13 printf("\n Therefore efficiency is %.2f %% \n",%n)

```

Scilab code Exa 3.15 1Dc output voltage 2ripple factor 3efficiency 4PIV

```

1 //EX3_15 PG-3.41
2 clc
3 Es=100;//peak value of supply voltage

```

```

4 Rf=25; //diode forward voltage
5 Rl=950; //load resistance
6 Rt=(2*Rf)+Rl; //total resistance
7 Im=Esm/Rt;
8 Idc=2*Im/%pi;
9 Edc=Idc*Rl;
10 printf("\n DC output voltage is %f V \n",Edc)
11 Irms=Im/sqrt(2); //rms value of input current
12 x=(Irms/Idc)^2-1;
13 Rf=sqrt(x); //ripple factor;
14 printf("\n Therefore ripple factor is %.4f \n",Rf)
15 Pdc=Idc^2*Rl;
16 Pac=Irms^2*(2*Rf+Rl); //Ac input power
17 %n=Pdc/Pac*100; //efficiency
18 printf("\n Therefore efficiency is %.2f %% \n",%n)
19 disp("Peak value of bridge rectifier=PIV rating of
      each diode")
20 PIV=Esm;
21 printf("\n Therefore PIV rating of each diode is %.2
      f V",PIV)
22 //In the book the answer for Edc=57.5985V which is
      wrong because they have taken
23 //Rf=50 ohm instead of 25 ohm as given in the
      question similarly
24 //the efficiency=73.3417% in the book is wrong
25 //the correct answer for efficiency is 80.97%

```

Scilab code Exa 3.16 1Average Dc voltage 2Average Dc current 3frequency of output

```

1 //EX3_16 PG-42
2 clc
3 Rl=100; //load resistance
4 Es=230; //rms value of input voltage
5 Rf=0; //ideal diode resistance
6 Rs=0; //neglecting transformer resistance

```

```

7 f=50; //frequency of the supply
8 Esm=sqrt(2)*Es;//peak value of the input voltage
9 Edc=2*Esm/%pi;//as Rf=0 ohm
10 printf("\n Average DC voltage is %.0f V \n",Edc)
11 Im=Esm/Rl;
12 Idc=2*Im/%pi;
13 printf("\n Therefore DC load current is %.2f A \n",
Idc)
14 f=2*f;//frequency of output waveform
15 printf("\n frequency of output waveform is %.0f Hz",
f)

```

Scilab code Exa 3.17 1Ripple voltage 2ripple factor

```

1 //EX3_17 PG-3.56
2 clc
3 Edc=12;//output DC voltage
4 f=50;//frequency
5 Idc=50e-3;
6 C=100e-6;//filter capacitor
7 Rl=2e3;//load resistance
8 Vr=Edc/(2*f*C*Rl);//rms value of ripple voltage
9 printf("\n rms value of ripple voltage is %.1f V \n",
",Vr)
10 Rf=(4*sqrt(3)*f*C*Rl)^(-1)*100;//ripple factor
11 printf("\n ripple factor is %.2f %% \n",Rf)

```

Scilab code Exa 3.18 1Dc output voltage 2rms value of of ripple voltage 3ripple fa

```

1 //EX3_18 PG-3.56
2 clc
3 Es=120;//rms value of input voltage
4 f=50;//frequency

```

```

5 Idc=50e-3;
6 C=100e-6; // filter capacitor
7 Esm=sqrt(2)*Es;
8 Edc=Esm-Idc/(4*f*C);
9 printf("\n DC output voltage is %.4f V \n",Edc)
10 Vr=Idc/(4*sqrt(3)*f*C); //rms value of ripple voltage
11 printf("\n rms value of ripple voltage is %.4f V \n"
      ",Vr)
12 Rf=Vr/Edc;
13 printf("\n ripple factor is %f \n",Rf)

```

Scilab code Exa 3.19 Load voltage and ripple voltage

```

1 //EX3_19 PG-3.56
2 clc
3 Ep=230; //rms value of primary voltage
4 N1toN2=10; //turns ratio
5 Rl=50; //load resistance
6 f=50; //frequency of the supply in Hz
7 Es=Ep/N1toN2;//rms value of secondary voltage or the
     input voltage
8 Esm=sqrt(2)*Es;//peak value of input voltage
9 Im=Esm/(Rl);
10 Idc=2*Im/pi;
11 Edc=Idc*Rl; //load voltage
12 printf("\n Therefore load voltage is %.1f V \n",Edc)
13 Rf=.48; //ripple factor for full wave rectifier
     without filter
14 Vrip=Rf*Edc;//ripple voltage
15 printf("\n Ripple factor is 0.48")
16 printf("\n ripple voltage is %.4f V \n",Vrip)
17 disp("If the capacitor filter is used then")
18 C=470e-6; //filter capacitor
19 Edc=Esm-Idc/(4*f*C);
20 printf("\n new DC load voltage is %.2f V \n",Edc)

```

```

21 Rf=((4*sqrt(3)*f*C*Rl))^-1; // new ripple factor
22 Vrip=Rf*Edc; //new ripple voltage
23 printf("\n Ripple factor is %.4f",Rf)
24 printf("\n rms value of ripple voltage is %.4f V \n"
      ,Vrip)
25 // in the book the new ripple factor is 3.256e-3
      which is wrong
26 //the actual answer is 0.1228 hence the new ripple
      voltage is 3.4544V
27 // not 0.09156V as shown in the book

```

Scilab code Exa 3.20 Value of capacitor C

```

1 //EX3_20 PG-3.57
2 clc
3 Rf=.01; //ripple factor in percentage
4 Rl=2; //load resistance in kohm
5 f=50; //frequency
6 disp("the %ripple factor=Rf=((4*sqrt(3)*f*C*Rl))
      ^(-1)*100 ")
7 C=((4*sqrt(3)*f*Rf*Rl))^(-1)*100; //filter capacitor
8 printf("\n the filter capacitor is %.3f mF",C)

```

Scilab code Exa 3.21 Ripple factor

```

1 //EX3_21 PG-3.58
2 clc
3 Idc=100e-3; //average current
4 C=500e-6; //filter capacitor
5 Esm=18; //peak voltage
6 f=50; //frequency of the supply in Hz
7 Edc=Esm-Idc/(4*f*C);
8 Rl=Edc/Idc; //load resistance

```

```
9 Rf=(4*sqrt(3)*f*C*Rl)^(-1)*100; // ripple factor
10 printf("\n ripple factor is %.2f %% \n",Rf)
```

Scilab code Exa 3.22 surge current

```
1 //EX3_22 PG-3.58
2 clc
3 f=50; //frequency
4 C=1000e-6; //filter capacitor
5 Rl=500; //load resistance
6 Vrms=120; //rms value of voltage
7 T1=1e-3; //conduction period of diode ,T1=1ms
8 disp("conduction period of diode ,T1=1ms")
9 Esm=sqrt(2)*Vrms; //peak value of input voltage
10 disp("Edc=Esm-Idc/(2*f*C) and Idc=Edc/Rl")
11 Edc=Esm/(1+(2*Rl*f*C)^(-1)); //output dc voltage
12 Idc=Edc/Rl;
13 T=1/f;
14 //Idc*T=Ip*T1
15 //Ip is the surge current
16 Ip=Idc*T/T1;
17 printf("\n hence the diode should be rated for a
minimum surge\n current of %.2f A \n",Ip)
```

Scilab code Exa 3.23 Rms value of ripple voltage and peak to peak voltage

```
1 //EX3_23 PG-3.59
2 clc
3 Rf=0.1; //ripple factor
4 Edc=10;
5 Vrip=Rf*Edc; //rms value of voltage
6 printf("\n rms value of ripple voltage is %.0f V \n
",Vrip)
```

```
7 Vp_p=2*sqrt(2)*Vrip;
8 printf("\n peak to peak voltage is %.4f V ",Vp_p)
```

Scilab code Exa 3.24 Dc output voltage and ripple factor

```
1 //EX3_24 PG-3.59
2 clc
3 Es=230; //rms value of input voltage
4 f=50; //frequency
5 Idc=50e-6;
6 Rl=100; //load resistance
7 C=1000e-6; //filter capacitor
8 Esm=sqrt(2)*Es;
9 Edc=2*Esm/%pi;
10 printf("\n Therefore DC output voltage is %.2f V \n"
      ,Edc)
11 Idc=Edc/Rl;
12 disp("if the capacitor filter C=1000e-6 is use then
      ")
13 Rf=(4*sqrt(3)*f*C*Rl)^(-1); //ripple factor
14 printf("\n ripple factor is %.4f \n",Rf)
15 Edc=Esm-Idc/(4*f*C);
16 printf("\n Therefore new DC load voltage is %.4f V \
      ",Edc)
```

Scilab code Exa 3.25 Value of the capacitance needed

```
1 //EX3_25 Pg-3.60
2 clc
3 Es=230;
4 f=50 //frequency
5 Rf=.005; //ripple factor
6 Il=0.5; //average load current
```

```
7 Esm=sqrt(2)*Es; //peak value of input voltage
8 disp(" For a half wave rectifier Ripple factor=(2*
      sqrt(3)*f*C*Rl)^(-1)")
9 Edc=Esm/%pi //for half wave rectifier
10 Rl=Edc/I1;
11 C=(2*sqrt(3)*f*Rf*Rl)^(-1); //for half wave rectifier
12 C=C*1e3;
13 printf("\n Therefore capacitance required is %.3f
      mF",C)
```

Scilab code Exa 3.26 Ripple factor

```
1 //EX3_26 PG-3.60
2 clc
3 Rl=1000;
4 C=500e-3
5 f=50;
6 Rf=(4*sqrt(3)*f*C*Rl)^(-1); //ripple factor
7 Rf=Rf*1e6;
8 printf("\n ripple factor is %.2f 10^(-6) \n",Rf)
```

Scilab code Exa 3.27 minimum value of capacitor

```
1 //EX3_27 PG-3.60
2 clc
3 I1=12e-3; //load current
4 Es=200; //rms voltage
5 Rf=0.02; //ripple factor
6 Esm=sqrt(2)*Es; //peak value of input voltage
7 Edc=2*Esm/%pi;
8 Idc=I1;
9 Rl=Edc/Idc; //load resistance
10 f=50; //frequency of the supply in Hz
```

```

11 disp(" For a half wave rectifier Ripple factor=1/(2*
      sqrt(3)*f*C*Rl)")
12 C=(4*sqrt(3)*f*Rf*Rl)^(-1); // filter capacitor
13 printf("\n Therefore minimum value of capacitance
      required is %.3f microF",C*1e6)
14 //C=9.619 microF not 9.622 microF

```

Scilab code Exa 3.28 Value of the capacitor required

```

1 //EX3_28 PG-3.61
2 clc
3 Es=230; //rms voltage
4 f=50;
5 Il=10e-3; //load current
6 Rf=.01; //ripple factor
7 Esm=sqrt(2)*Es; //peak value of input voltage
8 Edc=2*Esm/pi; //for full wave
9 Rl=Edc/Il;
10 C=(4*sqrt(3)*f*Rf*Rl)^(-1); //for full wave rectifier
11 C=C*1e6;
12 printf("\n Therefore capacitance required is %.2f
      microF",C)

```

Scilab code Exa 3.29 1Average Dc current 2Average Dc voltage 3Ripple voltage

```

1 //EX3_29 PG-3.61
2 clc
3 Rl=2e3; //load resistance
4 Es=200; //rms voltage
5 f=50;
6 Esm=sqrt(2)*Es; //peak value of input voltage
7 Rf=0; //ideal diodes
8 Rs=0;

```

```

9 Ism=Esm/(Rf+Rs+Rl);
10 Idc=2*Ism/%pi;
11 printf("\n Therefore Average DC load current is %.2f
      A \n",Idc)
12 Edc=Idc*Rl;
13 printf("\n Therefore average DC voltage is %.0f V \n
      ",Edc)
14 Rf=0.48;//ripple factor
15 Vrip=Rf*Edc;// ripple voltage
16 printf("\n rms value of ripple voltage is %.1f V \n
      ",Vrip)
17 disp("if a filter capacitor C=500 microF is used
      then")
18 C=500e-6;//capacitor filter
19 Rf=(4*sqrt(3)*f*C*Rl)^(-1); //for full wave rectifier
20 Vrip=Rf*Edc;//new ripple voltage
21 printf("\n rms value of new ripple voltage is %.4f V
      \n ",Vrip)

```

Scilab code Exa 3.30 Load regulation

```

1 //EX3_30 PG-3.67
2 clc
3 Vnl=10;//no load output voltage
4 Vfl=9.8;//full output voltage
5 LR=Vnl-Vfl;//load regulation
6 %LR=(Vnl-Vfl)/Vfl*100;//percentage load regulation
7 printf("\n percentage load regulation is +%.2f %%",
      %LR)

```

Scilab code Exa 3.31 Percentage load regulation

```

1 //EX3_31 PG-3.67

```

```

2 clc
3 LR=3e-3; //load regulation
4 Vnl=15; //no load voltage or maximum voltage
5 Vfl=Vnl-LR; //full load voltage
6 %LR=(Vnl-Vfl)/Vfl*100; //percentage load regulation
7 printf("\n percentage load regulation is +%.2f %%" ,
       %LR)

```

Scilab code Exa 3.32 Source regulation and percentage source regulation

```

1 //EX3_32 PG-3.67
2 clc
3 Vhl=10+.3; //high line voltage
4 Vll=10-.3; //low line voltage
5 SR=Vhl-Vll; //source regulation
6 Vnom=10; //nominal load voltage
7 %SR=SR/Vnom*100; //percentage source regulation
8 printf("\n percentage source regulation is %.0f %%" ,
       %SR)

```

Scilab code Exa 3.33 Range of input voltage

```

1 //EX3_33 PG-3.70
2 clc
3 disp("Refer to the figure -3.45 shown")
4 Vz=6.1; //zener voltage
5 Iz_min=2.5e-3; //minimum zener current
6 Iz_max=25e-3; //maximum zener current
7 rZ=0; //ideal zener diode
8 R=2.2e3;
9 Rl=1e3; //loadd resistance
10 I1=Vz/Rl;
11 //For minimum input voltage (Vin_min)

```

```

12 Iz=Iz_min
13 I=Iz_min+Il;
14 Vin_min=Vz+I*R;
15 printf("\n minimum input voltage (Vin_min) is %.2f V
    \n",Vin_min)
16 //For maximum input voltage (Vin_max)
17 I=Iz_max+Il;
18 Vin_max=Vz+I*R;
19 printf("\n maximum input voltage (Vin_max) is %.2f V
    \n",Vin_max)
20 printf("\n range of input voltage is from %.3f V to
    %.2f V \n",Vin_min,Vin_max)

```

Scilab code Exa 3.34 design of zener diode

```

1 //EX3_34 PG-3.70
2 clc
3 Vo=5; //output voltage
4 Vin_min=12-3; //min input voltage
5 Vin_max=12+3; //max input voltage
6 Iz_min=10e-3; //minimum zener current
7 Il=20e-3; //load current
8 Pz=500e-3; //Zener wattage
9 Vz=Vo; //zener voltage
10 disp("Step1 : Maximum power dissipation correesponds
        to Iz_max")
11 Iz_max=Pz/Vz;
12 printf("\n maximum current that should flow through
        the zener diode is %.1f A \n",Iz_max)
13 disp ("Step2 : We know that Il is constant")
14 //for Vin_max , Iz=Iz_max
15 I=Il+Iz_max;
16 Rmin=(Vin_max-Vz)/I;
17 printf("\n minimum resistance required is %.2f ohm \
    \n",Rmin)

```

```

18 disp("Iz is maximum when R=Rminimum")
19 disp("Step3 : for calculation of Rmax I must be
      minimum ie I=Iz_min ")
20 I=Il+Iz_min
21 Rmax=(Vin_min-Vz)/I;
22 printf("\n maximum resistance required is %.2f ohm \
      n",Rmax)
23 printf("\n Thus R must be greater than %.2f ohm and
      less than \n %.2f ohm for proper regulation \n",
      Rmin,Rmax)

```

Scilab code Exa 3.35 Minimum and maximum load current

```

1 //EX3_35 PG-3.72
2 clc
3 disp("refer to the figure -3.47 shown")
4 Vz=10; //output voltage
5 Vin=20; //input voltage
6 Iz_max=25e-3; //maximum zener current
7 Iz_min=5e-3; //minimum zener current
8 R=300;
9 Rz=0; //zener resistance
10 I=(Vin-Vz)/R;
11 //for Il_min Iz=Iz_max
12 Il_min=I-Iz_max; //minimum load current
13 printf("\n minimum load current is %.2f mA \n",
      Il_min*1e3)
14 //for Il_max , Iz=Iz_min
15 Il_max=I-Iz_min; //maximum load current
16 printf("\n maximum load current is %.2f mA \n",
      Il_max*1e3)
17 Rl_min=Vz/Il_max; //minimum load resistance
18 printf("\n minimum load resistance is %.3f ohm \n",
      Rl_min)
19 // in the book in the question it given that Iz_max

```

```
=50mA  
20 //but during the solution Iz_max is taken as 25mA I  
    have taken Iz_max=25mA  
21 // in this program
```

This code can be downloaded from the website www.scilab.in This code
can be downloaded from the website www.scilab.in

Scilab code Exa 3.38 Design of zener diode

```
1 //EX3_38 Pg-3.75  
2 clc  
3 Vo=5;  
4 Il=20e-3;  
5 Pz=500e-3;  
6 Rl=Vo/Il;  
7 Il_min=Il; //minimum load current  
8 Il_max=Il; //maximum load current  
9 Iz_max=Pz/Vo; //maximum zener current  
10 Iz_min=5e-3; //minimum zener current  
11 V=12; //input DC voltage  
12 Vin_min=12-3; //min input voltage  
13 Vin_max=12+3; //max input voltage  
14 Rmax=(Vin_min-Vo)/(Il_max+Iz_min);  
15 printf("\n maximum resistance required is %.0f ohm \\\n", Rmax)  
16 Rmin=(Vin_max-Vo)/(Il_min+Iz_max);  
17 printf("\n minimum resistance required is %.2f ohm \\\n", Rmin)  
18 printf("\n So series resistance must be selected  
        between %.2f ohm to %.0f ohm \n", Rmin, Rmax)
```

Scilab code Exa 3.39 Design of Voltage regulator

```
1 //EX3_39 Pg-3.76
2 clc
3 Vo=10;
4 Il_min=0; //minimum load current
5 Il_max=10e-3; //maximum load current
6 Iz_max=50e-3; //maximum zener current
7 Iz_min=2e-3; //minimum zener current
8 Vin_min=20; //min input voltage
9 Vin_max=30; //max input voltage
10 R1_min=Vo/Il_max;
11 Rmax=(Vin_min-Vo)/(Il_max+Iz_min);
12 printf("\n maximum resistance required is %.2f ohm \
n",Rmax)
13 Rmin=(Vin_max-Vo)/(Il_min+Iz_max);
14 printf("\n minimum resistance required is %.0f ohm \
n",Rmin)
15 printf("\n So series resistance must be selected \
between %.0f ohm to %.2f ohm \n",Rmin,Rmax)
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 3.40 series resistance and diode current

```
1 //EX3_40 Pg-3.76
2 clc
3 Vo=24;
4 Il_min=0; //minimum load current
5 Pz=600e-3;
6 Vin=32; //input voltage
```

```

7 Iz_max=Pz/Vo;
8 Rmin=(Vin-Vo)/(Il_min+Iz_max);
9 printf("\n minimum resistance required is %.0f ohm \
n",Rmin)
10 printf("\n As Vin and Il are not changing R=Rmin=%.0
f ohm\n is sufficient to work as a regulator\n",
Rmin)
11 disp("For Rl=1200 ohm")
12 Rl=1200;
13 Il=Vo/Rl;
14 printf("\n load current is: %.2f A \n",Il)
15 R=Rmin
16 It=(Vin-Vo)/R;
17 Iz=It-Il;
18 printf("\n zener current is :%.3f A \n",Iz)
19 printf(" As Iz=Iz_min=%.3f A, the circuit will work
as a regulator",Iz)

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 3.41 Design of zener regulator

```

1 //EX3_41 PG-3.79
2 clc
3 Pd=400e-3;
4 Vz=8.1; //output voltage
5 Vo=Vz;
6 Zz=8;
7 Vin=15;
8 Izm=Pd/Vz;
9 Rmax=(Vin-Vz)/Izm;
10 printf("\n maximum series resistance is %.3f ohm \n"
,Rmax)
11 Iz_min=5e-3; //we select the minimum zener current

```

```

12 Il_max=Izm-Iz_min;//maximum load current
13 printf("\n maximum load current is %.7f A \n",Il_max
      )
14 Rl=Vz/Il_max;//load resistance
15 deltaVin=.1*Vin;//change in input voltage is equal
      to 10% of the original input voltage
16 R=Rmax;//series resistance
17 x=(Rl*Zz)/(Rl+Zz);
18 deltaVo=(deltaVin*x)/(R+x);
19 Sv=deltaVo/deltaVin;//voltage stability factor
20 printf("\n voltage stability factor is %.3f \n",Sv)
21 SR=deltaVo/Vo*100;// line regulation for a 10%
      change in Vin
22 printf("\n line regulation is %.4f %% \n",SR)
23 deltaIL=Il_max;
24 y=(R*Zz)/(R+Zz)
25 deltaVo=deltaIL*y;
26 LR=deltaVo/Vo*100;//load regulation
27 printf("\n load regulation is %.4f %% \n",LR)
28 z=(Rl*Zz)/(Rl+Zz)
29 RR=z/(R+z);//ripple rejection ratio
30 printf("\n ripple rejection ratio is %.3f \n",RR)
31 Ro=y;//output resistance
32 printf("\n output resistance is %.3f ohm \n",Ro)

```

This code can be downloaded from the website www.scilab.in

Chapter 4

Transistors

Scilab code Exa 4.1 Base current

```
1 //EX-4_1 PG-4.11
2 clc
3 Ie=12e-3; //emitter current
4 Ic=Ie/1.02; //collector current
5 Ib=Ie-Ic; //base current
6 printf("\n Therefore base current is %.0f microA \n"
, Ib*1e6)
```

Scilab code Exa 4.2 Dc current gain and voltage gain

```
1 //EX4_2 Pg-4.14
2 clc
3 printf("When beta_dc=50 ")
4 beta_dc=50;
5 alpha_dc=beta_dc/(1+beta_dc);
6 printf("\n alpha_dc=% .4 f \n\n" ,alpha_dc)
7 printf(" When beta_dc=190 ")
8 beta_dc=190;
```

```

9 alpha_dc=beta_dc/(1+beta_dc);
10 printf("\n alpha_dc=%f \n\n",alpha_dc)
11 printf(" When alpha_dc=0.995 ")
12 alpha_dc=0.995;
13 beta_dc=alpha_dc/(1-alpha_dc);
14 printf("\n beta_dc=%f \n\n",beta_dc)
15 printf(" When alpha_dc=0.9765 ")
16 alpha_dc=0.9765;
17 beta_dc=alpha_dc/(1-alpha_dc);
18 printf("\n beta_dc=%f \n",beta_dc)

```

Scilab code Exa 4.3 Dc voltage gain and current gain

```

1 //EX4_3 , Pg-4.15
2 clc
3 Ib=20e-6;
4 Ie=0.0064;
5 beta_dc=Ie/Ib-1;
6 alpha_dc=beta_dc/(1+beta_dc);
7 printf("\n beta_dc=%f \n \n alpha_dc=%f \n",
       beta_dc,alpha_dc)
8 Ic=beta_dc*Ib; //collector current
9 printf("\n collector current is %.3f mA \n",Ic*1e3)

```

Scilab code Exa 4.4 current gain and emitter current

```

1 //EX4_4 PG4.15
2 clc
3 Icbo=5e-6; //leakage current
4 Ic=20e-3; //collector current
5 Ie=Ic/0.996; //Ic=0.996 Ie
6 alpha_dc=Ic/Ie;
7 printf("\n alpha_dc=%f \n",alpha_dc)

```

```
8 disp("We know that Ic=alpha_dc*Ie+Icbo ")
9 disp(" Therefore emitter current is Ie=(Ic-Icbo)/
       alpha_dc")
10 Ie=(Ic-Icbo)/alpha_dc; //emitter current
11 Ie=Ie*1e3;
12 printf("\n emitter current is %.2f mA", Ie)
```

Chapter 5

Biasing methods

Scilab code Exa 5.1 Calculation of Ib Ic and Vce and the region of operation

```
1 //EX5_1 PG 5.4
2 clc
3 disp(" Refer to the figure -5.5 shown")
4 disp(" i) When Rb=300 kohm")
5 disp(" Base emitter junction is not reverse biased
")
6 disp(" Assume transistor is operating in active
region")
7 Rb=300e3;
8 Rc=2e3; //collector resistance
9 Vcc=10; //supply voltage
10 Vbe=0.7; //base emitter voltage
11 disp(" We know that Vcc=Ib*Rb+Vbe ")
12 Ib=(Vcc-Vbe)/Rb; //since Vcc=Ib*Rb+Vbe
13 printf("\n      base current Ib is : %.2f microA \n", Ib
*1e6)
14 Beta=100;
15 Ic=Beta*Ib; //coletor current in active region
16 printf("\n      Collector current is %.1f mA \n", Ic*1
e3)
17 disp(" Applying KVL around collector loop ie Vcc=
```

```

        Ic*Rc+Vce")
18 Vce=Vcc-Ic*Rc; // since Vcc=Ic*Rc+Vce
19 printf("\n      Now Vce= %.1f V \n\n",Vce)
20 printf("      Since Vce=3.8 V collector to base
           junction is reverse biased and we can say \n
           that our assumption that transistor is in active
           region is justified")
21 printf("\n\n ii) When Rb=150 kohm\n\n")
22 disp("      base emitter junction is not reverse biased
           ")
23 Rb=150e3;
24 disp("      assume transistor is operating in active
           region")
25 disp("      Applying KVL around base loop ie Vcc=Ib*Rb+
           Vbe")
26 Ib=(Vcc-Vbe)/Rb; // since Vcc=Ib*Rb+Vbe
27 printf("\n      base current Ib is : %.0f microA \n",Ib
           *1e6)
28 Ic=Beta*Ib; // collector current in active region
29 printf("\n      Collector current is %.1f mA \n",Ic*1
           e3)
30 disp("      Applying KVL around collector loop ie Vcc=
           Ic*Rc+Vce")
31 Vce=Vcc-Ic*Rc; // since Vcc=Ic*Rc+Vce
32 printf("\n      Therefore Vce= %.1f V \n\n",Vce)
33 printf("      Collector voltage Vce has to be +ve or
           zero but Vce=-2.4 V hence \n      transistor is not
           in active region but it is in saturation region\
           \n ")
34 Vbe_sat=0.8; //base saturation voltage
35 Vce_sat=0.2; //collector saturation voltage
36 disp("      Applying KVL around base loop ie Vcc=Ib*Rb+
           Vbe_sat")
37 Ib=(Vcc-Vbe_sat)/Rb; // since Vcc=Ib*Rb+Vbe_sat
38 printf("\n      base current Ib is : %.0f microA \n",Ib
           *1e6)
39 disp("      Applying KVL around collector loop ie Vcc=
           Ic*Rc+Vce_sat")

```

```

40 Ic=(Vcc-Vce_sat)/Rc // since Vcc=Ic*Rc+Vce_sat
41 printf("\n      Collector current is %.1f mA \n", Ic*1
        e3)
42 printf("      To justify transistor is in saturation
        then \n      Ib must be greater than (Ic/Beta)")
43 x=Ic/Beta
44 printf("\n\n      Now Ib=%f nA \n \n      (Ic/Beta
        )=%f microA \n", Ib*1e6, x*1e6)
45 if (Ib>x) then//x=(Ic/Beta)
46 disp("      Hence transistor in saturation region is
        satisfied ")
47 end

```

Scilab code Exa 5.2 Minimum and maximum values of Ic and Vce

```

1 //EX5_2 PG-5.6
2 clc
3 Vbe=0.7; //base emitter voltage for silicon
4 Vcc=12; //supply voltage
5 Rb=150e3;
6 Rc=2e3
7 hFE_min=50; //minimum voltage gain
8 hFE_max=60; //maximum voltage gain
9 Ib=(Vcc-Vbe)/Rb; //since Vcc=Ib*Rb+Vbe
10 printf("\n base current is %.8f A \n", Ib)
11 printf("\n for hFE_min=50")
12 Ic=hFE_min*Ib
13 printf("\n Ic=%f A \n", Ic*1e3)
14 Vce=Vcc-Ic*Rc
15 printf(" Vce=%f V \n", Vce)
16 printf("\n\n for hFE_max=60")
17 Ic=hFE_max*Ib
18 printf("\n Ic=%f A \n", Ic*1e3)
19 Vce=Vcc-Ic*Rc
20 printf(" Vce=%f V \n", Vce)

```

Scilab code Exa 5.3 Calculation of Q point values

```
1 //EX5_3 PG5.8
2 clc
3 disp("Refer to the figure -5.8 shown")
4 Vbe=0.7; //base emitter voltage for silicon
5 Vcc=12; //supply voltage
6 Rb=100e3;
7 Rc=10e3;
8 Beta=100; //voltage gain
9 Ib=(Vcc-Vbe)/((1+Beta)*Rc+Rb); //since Vcc=Ib*Rb+Vbe
10 printf("\n base current is %.2f microA \n", Ib*1e6)
11 Ic=Beta*Ib
12 printf("\n Ic=% .3f mA \n", Ic*1e3)
13 Vce=Vcc-(Ib+Ic)*Rc
14 printf("\n Vce=% .4f V \n", Vce)
```

Scilab code Exa 5.4 Calculation of minimum and maximum values of Ic and Vce

```
1 //EX5_4 PG-5.9
2 clc
3 Vbe=0.7; //base emitter voltage for silicon
4 Vcc=12; //supply voltage
5 Rb=150e3;
6 Rc=2e3
7 hFE_min=50;
8 hFE_max=60;
9 printf(" i) for hFE_min=50")
10 Beta=hFE_min; //minimum voltage gain
11 Ib=(Vcc-Vbe)/((1+Beta)*Rc+Rb); //since Vcc=Ib*Rb+Vbe
12 printf("\n      base current is %.2f microA \n", Ib*1e6
    )
```

```

13 Ic=Beta*Ib
14 printf(" Ic=%f mA \n", Ic*1e3)
15 Vce=Vcc-(Ib+Ic)*Rc
16 printf(" Vce=%f V \n", Vce)
17 printf("\n for hFE_max=60")
18 Beta=hFE_max; //maximum voltage gain
19 Ib=(Vcc-Vbe)/((1+Beta)*Rc+Rb); //since Vcc=Ib*Rb+Vbe
20 printf("\n base current is %f microA \n", Ib*1e6
)
21 Ic=Beta*Ib
22 printf(" Ic=%f mA \n", Ic*1e3)
23 Vce=Vcc-(Ib+Ic)*Rc
24 printf(" Vce=%f V \n", Vce)

```

Scilab code Exa 5.5 Calculation of Vce and Ic

```

1 //EX5_5 PG-5.11
2 clc
3 disp(" Refer to the figure -5.13 shown")
4 Vbe=0.7; //base emitter voltage for silicon
5 Vcc=10; //supply voltage
6 R1=10e3;
7 Rc=1e3;
8 R2=5e3;
9 Re=500;
10 Beta=100; //voltage gain
11 Vb=R2*Vcc/(R1+R2); //base voltage
12 printf("\n Vb=%f V\n", Vb)
13 Ve=Vb-Vbe; //emitter voltage
14 printf("\n Ve=%f V \n", Ve)
15 Ie=Ve/Re;
16 printf("\n Ie=%f mA \n", Ie*1e3)
17 Ib=5.26e-3/(1+Beta); //Ie=0.00526 A=5.26 mA
18 printf("\n Ib=%f microA \n", Ib*1e6)
19 Ic=Beta*Ib;

```

```

20 printf("\n Ic=%f mA \n",Ic*1e3)
21 disp("We apply KVL to the collector circuit")
22 disp("Vce=Vcc-Ic*Rc-Vce-Ie*Re=0")
23 Vce=Vcc-Ic*Rc-Ie*Re; //since Vcc-Ic*Rc-Vce-Ie*Re=0
24 printf("\n Vce=%f V \n",Vce)

```

Scilab code Exa 5.6 Determination of Ic Ve and Vce

```

1 //EX5_6 PG-5.12
2 clc
3 printf("Refer to the figure -5.13 shown in the
        question no 5.5\n")
4 //We must find the value of Ic ,Ve ,Vce using exact
        analysis
5 Vbe=0.7;//base emitter voltage for silicon
6 Vcc=10;//supply voltage
7 R1=10e3;
8 Rc=1e3;
9 R2=5e3;
10 Re=500;
11 Beta=100;//voltage gain
12 Vt=R2*Vcc/(R1+R2); //thevenin's voltage
13 printf("\n Vt=%f V\n",Vt)
14 Rb=R1*R2/(R1+R2);
15 printf("\n Rb=%f ohm \n",Rb)
16 Ib=(Vt-Vbe)/(Rb+(1+Beta)*Re);
17 printf("\n Ib=%f microA \n",Ib*1e6)
18 Ic=Beta*Ib;
19 printf("\n Ic=%f mA \n",Ic*1e3)
20 Vce=Vcc-Ic*Rc-(Ic+Ib)*Re; //since Vcc-Ic*Rc-Vce-Ie*Re
        =0
21 printf("\n Vce=%f V \n",Vce)
22 //the ans for Ve in the book is 2.648V whereas in
        output it is 2.638V because
23 // in the book the values has been rounded off so

```

that the final answer is

24 // 2.648V same is the case for Rb, Ib and Ic

Scilab code Exa 5.7 Minimum and maximum values of Ic and Vce

```
1 //EX5_7 PG-5.13
2 clc
3 Vbe=0.7; //base emitter voltage for silicon
4 Vcc=12; //supply voltage
5 R1=10e3;
6 R2=2e3
7 Re=470;
8 Rc=2e3
9 hFE_min=50;
10 hFE_max=60;
11 Vb=R2*Vcc/(R1+R2); //base voltage
12 printf("\n Vb=%.0f V\n",Vb)
13 Ve=Vb-Vbe; //emitter voltage
14 printf("\n Ve=%.1f V \n",Ve)
15 Ie=Ve/Re;
16 printf("\n Ie=%.2f mA \n",Ie*1e3)
17 printf("\n i) for hFE_min=50")
18 Beta=hFE_min;
19 Ib=Ie/(Beta+1);
20 Ic=Beta*Ib;
21 printf("\n Ic=%.3f mA \n",Ic*1e3)
22 Vce=Vcc-Ic*Rc-Ve;
23 printf(" Vce=%.3f V \n",Vce)
24 disp(" ii) for hFE_max=60")
25 Beta=hFE_max;
26 Ib=Ie/(Beta+1);
27 Ic=Beta*Ib;
28 printf(" Ic=%.3f mA \n",Ic*1e3)
29 Vce=Vcc-Ic*Rc-Ve;
30 printf(" Vce=%.2f V \n",Vce)
```

Scilab code Exa 5.8 Design of a fixed biased circuit

```
1 //EX5_8 PG-5.16
2 clc
3 disp("refer to the figure -5.17 shown")
4 Vbe=0.7; //base emitter voltage for silicon
5 Vcc=10; //supply voltage
6 Beta=100; //voltage gain
7 Vce=5; //colector to emitter voltage
8 Ic=5e-3; //collector current
9 disp("We apply KVL to the collector circuit ie Vcc-
      Vce-Ic*Rc=0")
10 Rc=(Vcc-Vce)/Ic; //since Vcc-Vce-Ic*Rc=0
11 printf("\n Rc=%f kohm \n",Rc*1e-3)
12 Ib=Ic/Beta; //base current
13 printf("\n Ib=%f microA \n", Ib*1e6)
14 disp("We apply KVL to the base circuit ie Vcc-Vbe-Ib
      *Rb=0")
15 Rb=(Vcc-Vbe)/Ib; //since Vcc-Vbe-Ib*Rb=0
16 printf("\n Rb=%f kohm \n", Rb*1e-3)
17 disp("the standard value of Rb=200k ohm")
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 5.9 Design of Collector to base bias circuit

```
1 //EX5_9 PG-5.17
2 clc
3 disp("refer to the figure -5.19 shown")
4 Vbe=0.7; //base emitter voltage for silicon
```

```

5 Vcc=16; // supply voltage
6 Beta=100; // voltage gain
7 Vce=5; // collector to emitter voltage
8 Ic=5e-3; // collector current
9 Ib=Ic/Beta; // base current
10 printf("\n Ib=%f microA \n", Ib*1e6)
11 Rc=(Vcc-Vce)/(Ic+Ib); // since Vcc-Vce-Ic*Rc=0
12 printf("\n Rc=%f kohm \n", Rc*1e-3)
13 disp("Rc=2 kohm standard value")
14 disp("We apply KVL to the input circuit ie Vce-Vbe-
    Ib*Rb=0")
15 Rb=(Vce-Vbe)/Ib; // since Vce-Vbe-Ib*Rb=0
16 printf("\n Rb=%f kohm \n", Rb*1e-3)
17 disp("the standard value of Rb=91 kohm")

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 5.10 Design of voltage divider bias circuit

```

1 //EX5_10 PG-5.18
2 clc
3 disp("Refer to the figure -5.20 shown")
4 Vbe=0.7; //base emitter voltage for silicon
5 Vcc=12; //supply voltage
6 Beta=100; //voltage gain
7 Vce=5; //collector to emitter voltage
8 Ve=3; //assumption
9 Ic=3e-3; //collector current
10 Ib=Ic/Beta; //base current
11 printf("\n Ib=%f microA \n", Ib*1e6)
12 Ie=Ic+Ib; //emitter current
13 printf("\n Ie=%f mA \n", Ie*1e3)
14 Re=Ve/Ie;
15 printf("\n Re=%f ohm \n", Re)

```

```

16 printf(" the standard value of Re=910 ohm")
17 Re=910; //standard value
18 Ve=Ie*Re;
19 printf("\n\n Ve=%f V \n",Ve)
20 Rc=(Vcc-Ve-Vce)/Ic
21 printf("\n Rc=%f ohm \n",Rc)
22 printf(" the lower side standard value is selected
           to reduce Ic*Rc and increase Vce ")
23 Vb=Ve+Vbe
24 printf("\n\n Therefore Vb=%f V \n",Vb)
25 I=10*Ib
26 printf("\n I=%f mA \n",I*1e3)
27 R2=Vb/I;
28 printf("\n R2=%f ohm \n",R2)
29 printf(" the standard value of R2=11 kohm\n")
30 disp("the lower side standard is selected to satisfy
       I>=10*Ib")
31 R2=11e3;
32 I=Vb/R2;
33 printf("\n I=%f mA \n",I*1e3)
34 R1=(Vcc-Vb)/(I+Ib)
35 printf("\n R1=%f kohm \n",R1*1e-3)
36 printf(" the standard value of R1=22kohm\n")
37 disp("The lowest standard value is selected to
       satisfy I>=10*Ib")

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 5.11 Stability factor

```

1 //EX5_11 PG-5.26
2 clc
3 //for base bias take the figure as shown the
   Example5.1

```

```

4 Beta=100;
5 S=1+Beta; // stability factor
6 printf("\n For base bias: stability factor=%f \n",
      S)
7 //for collector to base bias the figure as shown the
      Example5.3
8 Beta=100;
9 Rc=10e3;
10 Rb=100e3
11 S=(1+Beta)/(1+Beta*(Rc/(Rc+Rb)));
12 printf("\n For collector to base bias: stability
      factor=%f \n",S)
13 //for voltage divider bias take the figure as shown
      the Example5.5
14 Re=500;
15 R1=10e3;
16 R2=5e3;
17 Rb=R1*R2/(R1+R2); //R1 and R2 are in parallel
18 S=(1+Beta)/(1+Beta*(Re/(Re+Rb)));
19 printf("\n For voltage divider bias: stability
      factor=%f \n",S)

```

Scilab code Exa 5.12 Resistance Rb

```

1 //EX5_12 PG-5.28
2 clc
3 disp("Refer to the figure -5.25 shown")
4 Icbo1=2e-6; //at a temperature T1=25 degree celsius
5 Vbb=5;
6 Vbe=0.1
7 disp("Icbo doubles for every 10 degree Celsius")
8 T1=25; //temperature in degree celsius
9 T2=80; //temperature in degree celsius
10 Icbo2=Icbo1*2^((T2-T1)/10); //at a temperature T2=80
      degree celsius

```

```

11 printf("\n Therefore Icbo2=%f microA \n",Icbo2*1e6
      )
12 disp("Apply KVL to the base circuit Vbb=Vbe+Icbo2*Rb
      we get")
13 Rb=(Vbb-Vbe)/Icbo2;
14 printf("\n Rb=%f kohm \n",Rb*1e-3)

```

Scilab code Exa 5.13 Calculation of R1 and R3

```

1 //EX5_13 PG-5.29
2 clc
3 disp("Refer to the figure -5.26 shown")
4 Vcc=15; //supply voltage
5 Beta=100; //voltage gain
6 Vbe=0.6; //base emitter voltage
7 Ic=2e-3
8 Vce=3;
9 R4=600;
10 R2=10e3;
11 Ib=Ic/Beta;
12 Ie=Ic+Ib; //collector current
13 printf("\n Apply KVL to the collector side Vcc=Ic*R3
      +Vce+Ie*R4")
14 R3=(Vcc-Vce-Ie*R4)/Ic; //since Vcc=Ic*R3+Vce+Ie*R4
15 printf("\n Therefore R3=%f kohm \n",R3*1e-3)
16 printf("\n Apply KVL to the base side I*R2=Vbe+Ie*R4
      ")
17 I=(Vbe+Ie*R4)/R2; //since I*R2=Vbe+Ie*R4
18 printf("\n Therefore I=%f mA \n",I*1e3)
19 printf("\n Apply KVL to the potential divider side
      we get Vcc=(I+Ib)*R1+I*R2")
20 R1=(Vcc-I*R2)/(I+Ib); //since Vcc=(I+Ib)*R1+I*R2
21 printf("\n therefore R1=%f kohm \n",R1*1e-3)

```

Scilab code Exa 5.14 Calculation of R_e V_{ce} and stability factor

```
1 //EX5_14 PG-5.30
2 clc
3 disp("Refer to the figure -5.27 shown")
4 Vcc=12; //supply voltage
5 Beta=100; //voltage gain
6 Vbe=0.7; //base emitter voltage
7 Ic=2e-3;
8 Ib=Ic/Beta;
9 R1=50e3;
10 R2=5e3;
11 Rc=2e3;
12 disp("apply KVL to the potential divider side we get
      Vcc-(I+Ib)*R1-I*R2=0 we get")
13 I=(Vcc-R1*Ib)/(R1+R2); //since Vcc-(I+Ib)*R1-I*R2=0
14 Vb=R2*I;
15 Ie=Ib+Ic;
16 Re=(Vb-Vbe)/(Ib+Ic); //Vb=Vbe+Re*Ie
17 printf("\n Re=%f ohm \n",Re)
18 disp("Apply KVL to the collector side Vcc-Ic*Rc-Vce+
      Ie*Re=0")
19 Vce=Vcc-Ic*Rc-Ie*Re; //since Vcc-Ic*Rc-Vce+Ie*Re=0
20 printf("\n Therefore Vce=%f V \n",Vce)
21 Rb=R1*R2/(R1+R2); //R1 and R2 are in parallel
22 S=(1+Beta)/(1+Beta*(Re/(Re+Rb)));
23 printf("\n stability factor=%f \n",S)
```

Scilab code Exa 5.15 Determination of percent change in Q values

```
1 //EX5_15 PG-5.31
2 clc
```

```

3 disp("Refer to the figure -5.28 shown")
4 Vbe=0.7;
5 Rb=100e3;
6 Rc=600;
7 Vcc=12; //supply voltage
8 T1=25; //temperature in degree celsius
9 T2=75; //temperature in degree celsius
10 disp("at T1=25 degree celsius , applying KVL to the
      base circuit we get")
11 disp("Vcc-Ib*Rb-Vbe=0")
12 Beta=100; //voltage gain at T1=25 degree celsius
13 Ib=(Vcc-Vbe)/Rb; //since Vcc-Ib*Rb-Vbe=0
14 Ic=Beta*Ib;
15 printf("\n Therefore Ic=%f mA \n",Ic*1e3)
16 disp("Apply KVL to the collector side Vcc-Ic*Rc-Vce
      =0")
17 Vce=Vcc-Ic*Rc; //since Vcc-Ic*Rc-Vce=0
18 printf("\n Therefore Vce=%f V \n",Vce)
19 Beta=125; //voltage gain at T1=25 degree celsius
20 Ic1=Beta*Ib;
21 Vce1=Vcc-Ic1*Rc; //since Vcc-Ic*Rc-Vce=0
22 printf("\n At 75 degree celsius Vce=%f \n",Vce1)
23 Ic_change=(Ic1-Ic)*100/Ic; //percentage in Ic
24 printf("\n change in Ic=%f %% (an increase) \n",
      Ic_change)
25 Vce_change=(Vce1-Vce)*100/Vce; //percentage in Vce
26 printf("\n change in Vce=%f %% (a decrease) \n",
      Vce_change)

```

Chapter 6

Power control Devices

Scilab code Exa 6.1 Finding of various ratings of SCR

```
1 //EX6_1 PG-6.15
2 clc
3 Es=20; //rms value of the supply voltage
4 Ep=sqrt(2)*Es; //peak value
5 printf("\n Therefore peak value of the input voltage
       is %.4f V \n",Ep)
6 printf("\n Therefore forward and reverse blocking
       voltge of SCR=% .4f V \n",Ep)
7 Rl=30; //load resistance
8 Ih=5e-3; //holding current
9 Vtm=1.7; //state voltage drop
10 Vl_peak=Ep-Vtm;
11 printf("\n Vl_peak=% .4f V \n",Vl_peak)
12 Il_peak=Vl_peak/Rl;
13 printf("\n Il_peak=% .4f A \n",Il_peak)
14 Il_rms=Il_peak/2;
15 printf("\n rms value of current flowing through the
       SCR is % .3f A \n",Il_rms)
16 //SCR current rating should be greater than Il_rms
17 Es_off=Vtm+Ih*Rl; //voltage which cause SCR to switch
       off
```

```
18 printf("\n voltage which cause SCR to switch off is  
%.2f V \n",Es_off)
```

Scilab code Exa 6.2 Designing values of R1 R2 and R3

```
1 //EX6_2 PG-6.18  
2 clc  
3 disp("Refer to the figure -6.19 shown")  
4 Es=25; //rms value of the supply voltage  
5 Vd1=0.7; //diode drop  
6 Vg=0.75; //SCR triggering voltage  
7 alpha1=10; //minimum phase angle  
8 alpha2=90; //maximum phase angle  
9 Ep=sqrt(2)*Es; //peak value  
10 Es1=Ep*sind(alpha1)  
11 Es2=Ep*sind(alpha2)  
12 Vt=Vd1+Vg; //voltage across R3  
13 printf("\n Position of R2 at top to trigger at 10  
degree ")  
14 Vr1=Es1-Vt; //since Vt=Vr2+Vr3  
15 //I1_min>>Ig ie 200 microA  
16 I1_min=1e-3;  
17 R1=Vr1/I1_min;  
18 printf("\n Therefore R1=%f kohm \n",R1*1e-3)  
19 printf(" We use R1=4.7 kohm standard value \n\n")  
20 R1=4.7e3; //standard value R1  
21 x=Vt/I1_min; //x=R2+R3  
22 printf(" Position of R2 at bottom to trigger at 90  
degree ")  
23 Vr3=Vt;  
24 I1=Es2/(R1+x);  
25 R3=Vr3/I1;  
26 printf("\n Therefore R3=%f ohm \n",R3)  
27 printf(" We use R3=270 ohm standard value \n")  
28 R3=270; //standard value R3
```

```
29 R2=x-R3; // since x=R2+R3
30 printf("\n Therefore R2=%f kohm \n",R2*1e-3)
31 printf(" We use the pot=1.5 kohm standard value for
precise judgement")
```

Scilab code Exa 6.3 Frequency of oscillations

```
1 //EX6_3 PG-6.33
2 clc
3 Rt=5; //resistance in kohm
4 Ct=0.1; //capacitance in micro farad
5 n=0.58; //standoff ratio
6 T=Rt*Ct*log(1/(1-n)); //time period in seconds
7 fo=1/T; //frequency of oscillations
8 fo=fo;
9 printf("\n Therefore frequency of oscillation is %.3
f kHz \n",fo)
```

Scilab code Exa 6.4 Frequency of oscillations

```
1 //EX6_4 PG-6.34
2 clc
3 Vbb=20;
4 Ct=0.1e-6; //capacitance
5 Rt=10e3; //resistance
6 Vv=1.5; //valley potential
7 Vd=0.7; //cut in voltage of diode
8 n=0.6; //stand off ratio
9 Vp=n*Vbb+Vd;
10 disp("We know that Vp=Vbb(1-exp(-T/(Rt*Ct)))")
11 x=(Vp-Vv)/Vbb; //x=(1-exp(-T/(Rt*Ct)))
12 y=1-x; //y=exp(-T/(Rt*Ct))
13 z=Rt*Ct;
```

```
14 T=-log(y)*z; //time period
15 fo=1/T; //frequency of oscillations
16 fo=fo*1e-3;
17 printf("\n Therefore frequency of oscillation is %.3
f kHz \n", fo)
```

Scilab code Exa 6.5 Range of Rt

```
1 //EX6_5 PG-6.34
2 clc
3 Vbb=30;
4 Vv=0.8; //valley potential
5 Iv=15e-3
6 Vd=0.7; //cut in voltage of diode
7 n=0.33; //stand off ratio
8 Vp=18;
9 Ip=35e-6;
10 printf(" For turn ON")
11 printf("\n Rt<(Vbb-Vp)/Ip")
12 Rt=(Vbb-Vp)/Ip;
13 printf("\n therefore Rt<%0.0f 0hm \n",Rt)
14 printf("\n For turn OFF")
15 printf("\n Rt>(Vbb-Vv)/Iv")
16 Rt1=(Vbb-Vv)/Iv
17 printf("\n therefore Rt>%0.0f 0hm \n",Rt1)
18 printf("\n So range of Rt is %.3f kohm< Rt <%0.2f
kohm \n",Rt1*1e-3,Rt*1e-3)
```

Chapter 7

Junction field effect transistors

Scilab code Exa 7.1 Drain current

```
1 //Ex7_1 PG-7.13
2 clc
3 Idss=10e-3;
4 Vgs_off=-4;
5 printf("For Vgs =0 V")
6 Vgs=0;
7 Id=Idss;
8 printf("\n Idss=%.0f mA \n",Id*1e3)
9 printf("\n For Vgs =-1 V")
10 Vgs=-1;
11 Id=Idss*(1-Vgs/Vgs_off)^2;
12 printf("\n Idss=%.3f mA \n",Id*1e3)
13 printf("\n For Vgs =-4 V")
14 Vgs=-4;
15 Id=Idss*(1-Vgs/Vgs_off)^2;
16 printf("\n Idss=%.0f A \n",Id)
17 //In the book this example is mention as Example-4_3
18 //but it is the first example in this chapter so I've taken this as Example-7_1
```

Scilab code Exa 7.2 1maximum and minimum od output voltage 2voltage gain

```
1 //Ex7_2 PG-7.17
2 clc
3 Vi=50e-3//input supply
4 Rd=5e3;
5 Yfs_max=4000e-6;
6 Yfs_min=1000e-6;
7 disp(" For Yfs_max=4000e-6")
8 Id_delta=Yfs_max*Vi;
9 printf("\n Change in Id is +/- %.1f mA \n",Id_delta
    *1e3)
10 Vo=Id_delta*Rd;//output voltage
11 Av=Vo/Vi;//voltge gain
12 printf("\n Voltage gain is %.0f \n",Av)
13 disp(" For Yfs_min=1000e-6")
14 Id_delta=Yfs_min*Vi;
15 printf("\n Change in Id is +/- %.2f mA \n",Id_delta
    *1e3)
16 Vo=Id_delta*Rd;//output voltage
17 Av=Vo/Vi;//voltge gain
18 printf("\n Voltage gain is %.0f \n",Av)
19 //In the book this example is mention as Example-7_1
20 //but it is the second example in this chapter so I
    've taken this as Example-7_2
```

Chapter 8

Amplifiers

Scilab code Exa 8.1 Gain in dB scale

```
1 //Ex8_1 PG-8.3
2 clc
3 Av=100; //voltage gain
4 G=20*log10(Av); //gain in decibel
5 printf("\n Therefore gain in decibel=%f dB \n",G)
```

Scilab code Exa 8.2 Maximum voltage gain

```
1 //Ex8_2 PG-8.5
2 clc
3 Av=200; //gain at cut-off frequencies
4 Avm=Av*sqrt(2); //maximum voltage gain
5 printf("\n Therefore maximum voltage gain=%f \n",Avm)
```

Scilab code Exa 8.3 Gain of an amplifier

```
1 //Ex8_3 PG-8.6
2 clc
3 Amid=100; //mid-band gain
4 f1=1e3; //lower cut-off frequency
5 f=20; //frequency at which the gain of the amplifier
       should be found
6 A=Amid/sqrt(1+(f1/f)^2)
7 printf("\n Therefore the gain of the amplifier at f
       = 20Hz is %.0f \n",A)
```

Scilab code Exa 8.4 Gain of an amplifier

```
1 //Ex8_4 PG-8.7
2 clc
3 G=200; //3dB gain
4 f2=20e3; //higher cut-off frequency
5 Amid=G*sqrt(2); //mid-band gain
6 f=100e3; //frequency at which the gain of the
       amplifier should be found
7 A=Amid/sqrt(1+(f/f2)^2)
8 printf("\n Therefore the gain of the amplifier at f
       =100kHz is %.2f \n",A)
9 //in the book the answer for the gain is 115.47
       which is wrong
10 //the correct answer is 55.47
```

Chapter 9

Oscillators

Scilab code Exa 9.1 Frequency of oscillations

```
1 //EX9_1 PG-9.13
2 clc
3 R=4.7e3;//each resistance of the RC phase shift
    oscillator
4 C=0.47e-6;//each capacitance of the RC phase shift
    oscillator
5 f=1/(2*pi*sqrt(6)*R*C);
6 printf("\n Therefore frequency of oscillation is %.3
    f Hz \n",f)
```

Scilab code Exa 9.2 Design of an RC phase shift oscillator

```
1 //EX9_2 PG-9.13
2 clc
3 f=900e3;//frequency of oscillation
4 C=1e-12;//each capacitance of the RC phase shift
    oscillator
5 R=1/(2*pi*sqrt(6)*f*C);
```

```
6 printf("\n each resistance of the RC phase shift
 oscillator is %.3f kohm \n",R*1e-3)
7 G=29; //opamp gain Rf/R1=29
8 R1=1e3;
9 printf("\n R1=%.0f kohm \n",R1*1e-3)
10 Rf=G*R1;
11 printf("\n Rf=%.0f kohm \n",Rf*1e-3)
12 disp("the design circuit is shown ")
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 9.3 estimation of R and C

```
1 //EX9_3 PG-9.14
2 clc
3 f=1e3; //frequency of oscillation
4 C=0.1e-6; //We choose the value of each capacitance
            of the RC phase shift oscillator
5 R=1/(2*pi*sqrt(6)*f*C);
6 printf("\n each resistance of the RC phase shift
 oscillator is %.3f ohm \n",R)
7 disp(" The standard value of R=680 ohm")
```

Scilab code Exa 9.4 Frequency of oscillations

```
1 //EX9_4 PG-9.14
2 clc
3 R=5e3; //each resistance of the RC phase shift
          oscillator
4 C=0.1e-6; //each capacitance of the RC phase shift
          oscillator
5 f=1/(2*pi*sqrt(6)*R*C);
```

```
6 printf("\n Therefore frequency of oscillation is %.3
f Hz \n",f)
```

Scilab code Exa 9.5 Value of capacitor C

```
1 //EX9_5 PG-9.20
2 clc
3 L=100e-6;
4 f=500e3;
5 disp("We know that for a colpitts oscillator f=1/(2*
%pi*sqrt(L*Ceq))")
6 Ceq=1/(f^2*4*pi^2*L)
7 Ceq1=Ceq*1e9;
8 printf("\n Ceq = %.5f nF \n",Ceq1)
9 //C1=C2=C
10 C=Ceq1*2; //Ceq=(C1*C2)/(C1+C2)
11 printf("\n Therefore C = %.5f nF \n",C)
```

Scilab code Exa 9.6 Frequency of oscillation

```
1 //EX9_6 PG-9.20
2 clc
3 L=50e-6;
4 C1=150e-12;
5 C2=1.5e-9;
6 Ceq=(C1*C2)/(C1+C2);
7 f=1/(2*pi*sqrt(L*Ceq));
8 f=f*1e-6;
9 printf("\n Therefore frequency of oscillation is %.3
f MHz \n",f)
```

Scilab code Exa 9.7 value of inductance L

```
1 //EX9_7 PG-9.21
2 clc
3 C=1000e-12;
4 C1=C;
5 C2=C;
6 f=500e3;
7 Ceq=(C1*C2)/(C1+C2);
8 L=1/(4*pi^2*f^2*Ceq); // since f=1/(2*pi*sqrt(L*Ceq))
9 L=L*1e6;
10 printf("\n Therefore L=%f micro H \n",L)
```

Scilab code Exa 9.8 designing the value of inductor L

```
1 //EX9_8 PG-9.21
2 clc
3 C1=100e-12;
4 C2=50e-12;
5 f=10e6;
6 Ceq=(C1*C2)/(C1+C2);
7 L=1/(4*pi^2*f^2*Ceq); // f=1/(2*pi*sqrt(L*Ceq));
8 L=L*1e6;
9 printf("\n Therefore inductor L = %f microH \n",L)
```

Scilab code Exa 9.9 Frequency of oscillation

```
1 //EX9_9 PG-9.24
2 clc
3 L1=0.5e-3;
4 L2=1e-3;
5 C=0.2e-6;
```

```

6 Leq=L1+L2; //total inductance for Hartley oscillator
7 f=1/(2*pi*sqrt(Leq*C));
8 printf("\n Therefore frequency of oscillation is %.f
      Hz \n",f)
9 //there is a slight difference between the answer
   given in the book
10 //and the and output in the book they have taken the
    approximate value

```

Scilab code Exa 9.10 Range for the capacitor C

```

1 //EX9_10 PG-9.24
2 clc
3 L1=2e-3;
4 L2=20e-6;
5 Leq=L1+L2; //total inductance for Hartley oscillator
6 fmax=2050e3; //maximum frequency
7 fmin=950e3; //minimum frequency
8 printf("For f=fmax=2050kHz")
9 f=fmax;
10 C=1/(4*pi^2*f^2*Leq); //since f=1/(2*pi*sqrt(Leq*C)
    );
11 C=C*1e12
12 printf("\n C=%.2f pF \n",C)
13 printf("\n For f=fmin=950kHz")
14 f=fmin;
15 C1=1/(4*pi^2*f^2*Leq); //since f=1/(2*pi*sqrt(Leq*C
    );
16 C1=C1*1e12
17 printf("\n C=%.2f pF \n",C1)
18 printf("\n Hence C must be varied between %.2f pF
      and %.2f pF \n",C,C1)

```

Scilab code Exa 9.11 Range of capacitor C

```
1 //EX9_11 PG-9.25
2 clc
3 L1=20e-6;
4 L2=2e-3
5 Leq=L1+L2; //total inductance for Hartley oscillator
6 fmax=2.5e6; //maximum frequency
7 fmin=1e6; //minimum frequency
8 printf("For f=fmax=2.5MHz")
9 f=fmax;
10 C=1/(4*pi^2*f^2*Leq); //since f=1/(2*pi*sqrt(Leq*C))
11 );
12 C=C*1e12
13 printf("\n C=%f pF \n",C)
14 printf("\n For f=fmin=1MHz")
15 f=fmin;
16 C1=1/(4*pi^2*f^2*Leq); //since f=1/(2*pi*sqrt(Leq*C))
17 );
18 C1=C1*1e12
19 printf("\n C=%f pF \n",C1)
20 printf("\n Hence C must be varied between %f pF
and %f pF \n",C,C1)
```

Scilab code Exa 9.12 1series resonant frequency 2parallel resonant frequency 3perc

```
1 //EX9_12 PG-9.32
2 clc
3 L=0.4;
4 C=0.085e-12;
5 R=5e3;
6 Cm=1e-12;
7 f=1/(2*pi*sqrt(L*C)); //series resonant frequency
for crystal oscillator
8 printf("\n series resonant frequency for crystal
```

```

    oscillator fs=% .3f MHz \n" ,f*1e-6)
9 Ceq=C*Cm/(C+Cm);
10 fp=1/(2*pi*sqrt(L*Ceq)); // parallel resonant
    frequency for crystal oscillator
11 printf("\n parallel resonant frequency for crystal
    oscillator=% .3f MHz \n" ,fp*1e-6)
12 %increase=(fp-f)/f*100;
13 printf("\n increase in parallel frequency fp=% .3f %% \n" ,%increase)
14 w=2*pi*f;
15 Q=w*R; //Q factor
16 printf("\n Therefore Q factor=% .3f \n" ,Q)
17 //in the book fs=0.856MHz is wrong, correct answer is
    fs=.863MHz
18 //in the book %increase=5.023% is wrong the correct
    answer is %increase=4.163%
19 //in the Q=430.272 which is wrong the correct
    answer is Q=433.861

```

Scilab code Exa 9.13 Series and parallel resonant frequency

```

1 //EX9_13 PG-9.32
2 clc
3 C=0.01e-12;
4 Cm=2e-12;
5 L=2;
6 R=2e3;
7 fs=1/(2*pi*sqrt(L*C)); // series resonant frequency
    for crystal oscillator
8 printf("\n series resonant frequency for crystal
    oscillator fs=% .3f MHz \n" ,fs*1e-6)
9 Ceq=C*Cm/(C+Cm);
10 fp=1/(2*pi*sqrt(L*Ceq)); // parallel resonant
    frequency for crystal oscillator
11 printf("\n parallel resonant frequency for crystal

```

oscillator =%.3f MHz \n" ,fp*1e-6)

Chapter 10

Introduction to Operational Amplifiers

Scilab code Exa 10.1 Output voltage

```
1 //EX10_1 PG-10.7
2 clc
3 disp(" Refer to the figure -10.5 shown")
4 V1=300e-6;
5 V2=240e-6;
6 Vd=V1-V2// differential mode voltage
7 Vc=(V1+V2)/2; //common mode voltage
8 Ad=5000; // differential gain
9 printf("\n when CMRR=100")
10 CMRR=100; //common mode rejection ratio
11 Ac=Ad/CMRR;
12 printf("\n common mode gain Ac=%f \n",Ac)
13 Vo=Ad*Vd+Ac*Vc; //output voltage
14 printf(" output voltage is Vo=%f mV \n",Vo*1e3)
15 printf("\n when CMRR=100000")
16 CMRR=1e5; //common mode rejection ratio
17 Ac=Ad/CMRR;
18 printf("\n common mode gain Ac=%f \n",Ac)
19 Vo=Ad*Vd+Ac*Vc; //output voltage
```

```
20 printf(" output voltage is Vo=%f mV \n",Vo*1e3)
```

Scilab code Exa 10.2 Input bias current and input offset current

```
1 //EX10_2 PG-10.17
2 clc
3 Ib1=18; //in microA
4 Ib2=22; //in microA
5 Ib=(Ib1+Ib2)/2; //input bias current
6 Ib=Ib
7 printf("\n input bias current= %.0f microA \n",Ib)
8 Iios=(Ib1-Ib2); //input offset current
9 Iios=abs(Iios);
10 Iios=Iios
11 printf("\n input offset current= %.0f microA \n",
    Iios)
```

Scilab code Exa 10.3 Values of two input bias current

```
1 //EX10_3 PG-10.17
2 clc
3 Iios=20;//Input offset current in nA
4 Ib=60;//Input bias current in nA
5 //Iios=Ib1-Ib2=20
6 //Ib=(Ib1+Ib2)/2=60
7 //ie Ib=(Ib1+Ib2)=120
8 disp(" Iios=Ib1-Ib2=20")
9 disp(" ie Ib=(Ib1+Ib2)/2=60 ie Ib=(Ib1+Ib2)=120")
10 a=[1 -1;1 1]; //coefficient of Ib1 and Ib2 for Iios
    and Ib
11 b=[20 ;120]; //value of Iios and Ib
12 x=inv(a)*b
13 disp(" values of Ib1 and Ib2 are")
```

```
14 printf(" %.0f nA ",x)
```

Scilab code Exa 10.4 Voltage gain

```
1 //EX10_4 PG-10.35
2 clc
3 disp("Refer to the figure -10.32 shown")
4 //the circuit is an inverting amplifier
5 R1=10e3;
6 Rf=47e3;//feedback resistance
7 A=-Rf/R1;//gain of an inverting amplifier
8 printf("\n the gain is %.1f (inverting amplifier) \n",A)
```

Scilab code Exa 10.5 Output voltage and waveforms

```
1 //EX10_5 PG-10.35
2 clc
3 R1=10e3;
4 Rf=50e3;//feedback resistance
5 Vcc=12;//supply voltage in volts
6 A=-Rf/R1;//gain of an inverting amplifier
7 A=abs(A);//magnitude of the gain
8 printf("If Vm=0.5V then")
9Vm=0.5;//peak value of the input voltage
10 Vo=A*Vm;//output voltage
11 printf("\n peak value of the output voltage Vo=%.1f
V \n",Vo)
12 printf("\n if Vm=5V then")
13Vm=5;//peak value of the input voltage
14 Vo1=A*Vm;//output voltage
15 printf("\n peak value of the output voltage Vo=%.0f
V \n",Vo1)
```

```

16 disp("but the opamp output saturates at +/- 12V
      hence portion above +12V and")
17 printf(" below -12V will be clipped off. So 25V \n
      peak output is not practically possible it will
      show upto +/- 12V")
18 clf()
19
20 subplot(2,1,1)           //input voltage Vin=0.5V peak
21 x=0:%pi/100:9
22 y=0.5*sin(x)
23 plot(x,y)
24 xtitle("(Vin)m=0.5V" , "time" , "Input voltage Vin= 0.5
      V peak")
25 xgrid(color("grey"));
26
27 subplot(2,1,2)           //output voltage Vo=2.5V peak
28 x=0:%pi/100:9
29 y=-Vo*sin(x)           //output is inverted
30 plot(x,y)
31 xtitle("(Vin)m=0.5V" , "time" , "Output voltage (
      inverted) Vo=2.5V peak")
32 xgrid(color("grey"));
33
34 xset('window',1)
35 clf()
36
37 subplot(2,1,1)           //input voltage Vin=5V peak
38 x=0:%pi/100:9
39 y=5*sin(x)
40 plot(x,y)
41 xtitle("(Vin)m=5V" , "time" , "Input voltage Vin=5V
      peak")
42 xgrid(color("grey"));
43
44 subplot(2,1,2)           //output voltage Vo=25V peak
      but clipped at + or -12V
45 x=0:%pi/100:9
46 y=-Vo1*sin(x)           //output is inverted

```

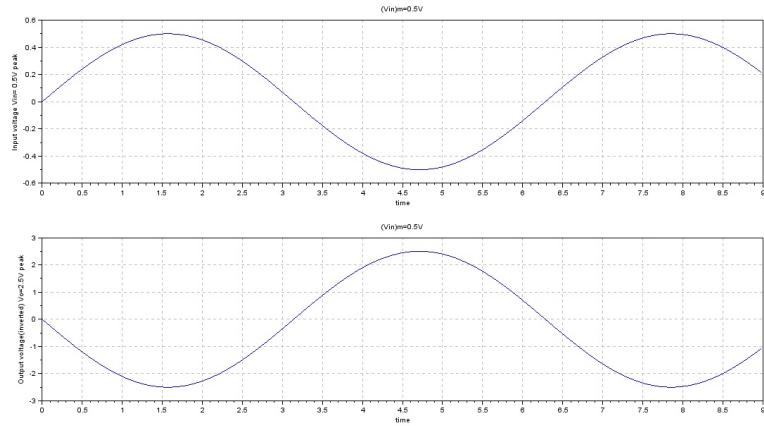


Figure 10.1: Output voltage and waveforms

```

47 y(find(y > 12)) = 12;
48 y(find(y < -12))= -12;
49 plot(x,y,style=3)
50 xtitle("(Vin)m=5V" , "time" , "Output voltage (inverted)
Vo=12V clipped")
51 xgrid(color("grey"));

```

Scilab code Exa 10.6 Reading of output voltage on the voltmeter

```

1 //EX10_6 PG-10.36
2 clc
3 R1=10e3;
4 Rf=47e3;//feedback resistance
5 Vcc=12;//supply voltage
6 A=-Rf/R1;//gain of an inverting amplifier
7 A=abs(A);//magnitude of the gain of an inverting
amplifier

```

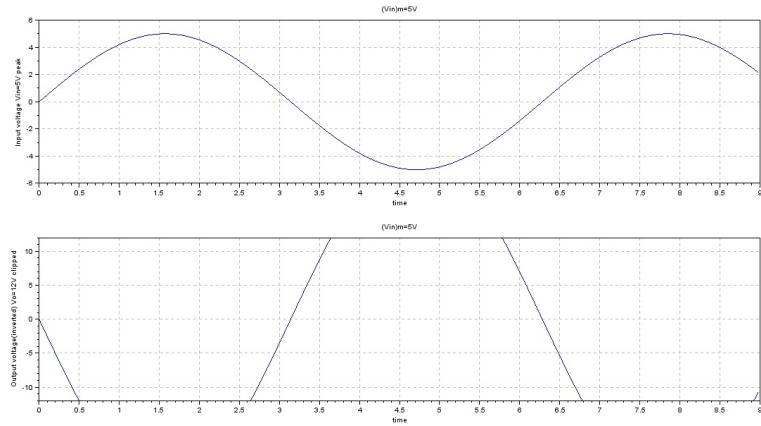


Figure 10.2: Output voltage and waveforms

```

8 Vin=2; //peak to peak input voltage
9 Voo=Vin*A; //peak to peak output voltage
10 //the AC voltmeter measures the rms value
11 Vo=Voo/2; //peak output voltage
12 Vrms=Vo/sqrt(2); //rms value of the output voltage
13 printf("\n Reading on the AC voltmeter is %.4f V \n"
      ,Vrms)

```

Scilab code Exa 10.7 Voltage gain and output waveforms

```

1 //EX10_7 PG-10.37
2 clc
3 R1=1e3;
4 Rf=10e3; //feedback resistance
5 Vin=100e-3; //input voltage peak to peak
6 A=-Rf/R1; //gain of an inverting amplifier
7 Vo=A*Vin;
8 printf("\n peak to peak value of the output voltage
      Vo = %.0f V \n",Vo)
9 printf("\n voltage gain of the inverting amplifier
      Af = %.0f \n ",A)

```

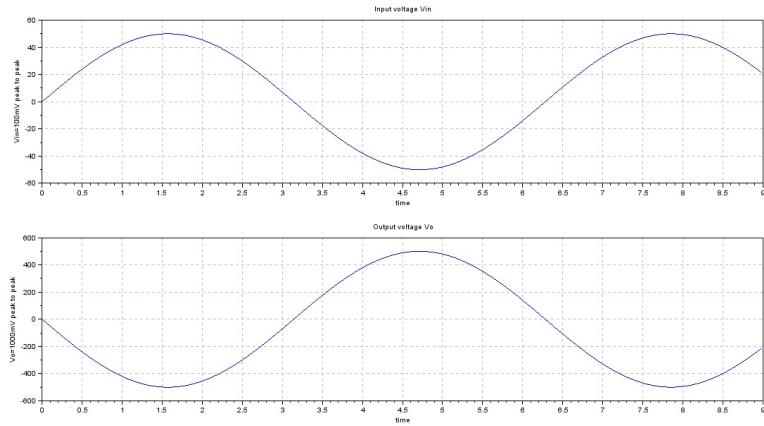


Figure 10.3: Voltage gain and output waveforms

```

10 // plotting of the waveforms
11 clf()
12
13 subplot(2,1,1)      //input voltage Vin=0.5V peak
14 x=0:%pi/100:9
15 y=50*sin(x)
16 plot(x,y)
17 xtitle("Input voltage Vin" , "time" , "Vin=100mV peak
          to peak")
18 xgrid(color("grey"));
19 subplot(2,1,2)      //output voltage Vo=2.5V peak
20 x=0:%pi/100:9
21 y=-500*sin(x)
22 plot(x,y)
23 xtitle("Output voltage Vo" , "time" , "Vo=1000mV peak
          to peak")
24 xgrid(color("grey"));

```

Scilab code Exa 10.8 Feedback resistor Rf

```

1 //EX10_8 PG-10.40
2 clc
3 A=61; //gain required for the non inverting amplifier
4 R1=1e3;
5 printf("Refer to the figure -10.36 shown\n")
6 printf("\n The gain of the non inverting amplifier
    is A=1+Rf/R1")
7 //the gain of the non inverting amplifier is A=1+Rf/
    R1
8 x=A-1; //x=Rf/R1
9 Rf=x*R1;
10 printf("\n\n Therefore feedback resistance Rf=%f of
    kohm \n",Rf*1e-3)

```

Scilab code Exa 10.9 Gain and output voltage

```

1 //EX10_9 PG-10.40
2 clc
3 R1=1e3;
4 Rf=10e3;//feedback resistance
5 A=1+Rf/R1;//gain of a non-inverting amplifier
6 printf("Gain is %f\n",A)
7 disp("For Vin =0.5V ")
8 Vin=0.5;//input voltage
9 Vo=A*Vin;
10 printf(" Output voltage Vo=%f V \n",Vo)
11 disp("For Vin =-3V ")
12 Vin=-3;//input voltage
13 Vo=A*Vin;
14 printf(" Output voltage Vo=%f V \n",Vo)
15 printf("\n but Vo=-33V is not possible. Output will
    saturate at -12V \n")
16 printf(" And the remaining portion will be clipped
    from output .")

```

Scilab code Exa 10.10 Closed loop gain and feedback resistance

```
1 //EX10_10 PG-10.48
2 clc
3 printf("Refer to the figure -10.43 shown\n ")
4 //A is grounded so B is virtual ground
5 //Vb=Va=0
6 Vb=0;
7 R1=1e3;
8 R2=5e3;
9 R3=5e3;
10 R4=100;
11 printf("\n Vb=Va=0 ..... (1) ")
12 printf("\n Vb=0 \n I1=(Vin-Vb)/R1=Vin/R1 \n I1=(Vb-
    Vx)/R2=-Vx/R2 \n \n Vin/Rf=-Vx/R2")
13 printf("\n =>Vx=-R2/R1*Vin ..... (2) \n \n now Vx=
    I2*R4 and (I1-I2)=(Vx-Vo)/R3 \n")
14 printf(" =>I2=Vx/R4 and I1-Vx/R4=(Vx-Vo)/R3 \n
    Therefore \n Vin/R1-Vx/R4=(Vx-Vo)/R3 ....")
15 printf(" ..... using I1=Vin/R1 \n Vin/R1-Vx(1/R4+1/
    R3)=-Vo/R3 \n \n ")
16 printf(" Vin/R1-(-R2/R1)*Vin*(1/R4+1/R3)=-Vo/R3
    ..... using (2) \n")
17 printf(" Vin*(1/R1+R2/R1*(1/R4+1/R3))=-Vo/R3 \n \n ")
18 printf(" Vin=-(R1*R4/(R3*R4+R2*R3+R2*R4))*Vo \n \n")
19 printf(" Acl=Vo/Vin=-(R3*R4+R2*R3+R2*R4)/(R1*R4) \n"
    )
20 Acl=-(R3*R4+R2*R3+R2*R4)/(R1*R4);
21 printf("\n closed loop gain Acl=%.0f \n",Acl)
22 Acl=abs(Acl);
23 Rf=R1*Acl;//equivalent feedback resistance
24 printf("\n equivalent feedback resistance Rf= %.0f
    kohm ",Rf*1e-3)
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 10.11 Output voltage Vo

```
1 //EX10_11 PG-10.50
2 clc
3 disp("Refer to the figure -10.45 and figure -10.45(a)
      shown")
4 //the circuit is a non inverting amplifier
5 Vin=10; //input voltage
6 //opamp input current is zero...
7 R1=10e3;//resistance connected to the -ve terminal
           of the amplifier
8 R2=1e3;//resistance connected to the +ve terminal of
           the amplifier to the input voltage
9 R3=1e3;///resistance connected to the +ve terminal
           of the amplifier to the ground
10 Rf=50e3;//feedback resistance
11 I=Vin/(R2+R3);
12 Vb=I*R3;
13 V0=(1+Rf/R1)*Vb; //output voltage
14 printf("\n output voltage Vo=%f V \n",V0)
```

Scilab code Exa 10.12 Output voltage Vo

```
1 //EX10_12 PG-10.51
2 clc
3 disp("Refer to the figure -10.46 and figure -10.46(a)
      shown")
4 disp("We split the circuit of the figure -10.46 as
      shown in figure -10.46(a) " )
```

```

5 disp("For first stage the circuit is a non-inverting
       amplifier")
6 Rf=10e3;//feedback resistance for the first stage of
       the circuit
7 R1=100e3;//value of R1 for the first stage of the
       circuit
8 V1=poly(0, 'V1');//V1=Vin
9 Vo1=(1+Rf/R1)*V1;
10 disp(Vo1,"Therefore Vo1 =")
11
12 printf("\n For the second stage we use superposition
       principle.\n We use each input at one time\n")
13 disp("First we assume Vo1 is active and V2 is
       grounded as shown in figure10.46(b)")
14 Rf1=100e3;//feedback resistance for figure -10.46(b)
15 R11=10e3;//value of R1 for figure1 -10.46(a)
16 Vo_=-Rf1/R11*Vo1;//when V2=0V as shown in figure
       -10.46(b)
17 disp(Vo_,"Therefore Vo_ =")
18
19 disp("then we assume V2 is active and Vo1 is
       grounded as shown in figure10.46(c)")
20 V2=poly(0, 'V2')
21 Vo__=(1+Rf1/R11)*V2;//when Vo1=0V as shown in figure
       -10.46(c), it is a non inverting amplifier
22 disp(Vo__,"Therefore Vo__ =")
23 printf("\n Therefore output voltage Vo = Vo_ +
       Vo__= 11V2-11V1 ")
24 disp(" =>Vo=11(V2-V1)" )

```

This code can be downloaded from the website www.scilab.in This code

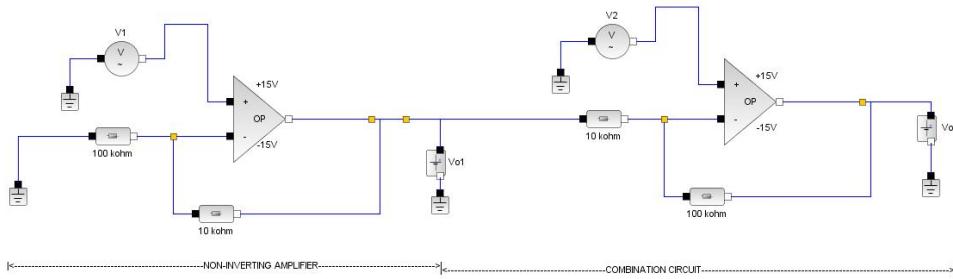


Figure 10.4: Output voltage V_o

can be downloaded from the website www.scilab.in

Scilab code Exa 10.13 Output voltage V_o

```

1 //EX10_13 PG-10.62
2 clc
3 disp("Refer to the figure -10.55 and shown")
4 R1=1e3;
5 Rf=1e3; //feedback resistance
6 Vin1=2;
7 Vin2=1;
8 Vin3=4;
9 Vout=-(Vin1+Vin2+Vin3)*Rf/R1
10 printf("\n output voltage Vout=%f V \n",Vout)

```

Scilab code Exa 10.14 Design of Scaling adder

```

1 //EX10_14 PG-10.62
2 clc
3 printf("\n Vo = -(3V1 + 4V2 + 5V3)\n\n")
4 Rf=120; //we assume feedback resistance to be equal
        to 120kohm
5 R1=Rf/3; //Rf/R1=3 given

```

```

6 R2=Rf/4; //Rf/R2=4 given
7 R3=Rf/5; //Rf/R3=5 given
8 printf("    R1= %.0 fkohm   R2= %.0 fkohm   R3 = %.0 fkohm \
n",R1,R2,R3)
9 printf("\n      The circuit design is shown")

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 10.15 Relation between Rf and R

```

1 //EX10_15 PG-10.63
2 clc
3 printf("\n      Refer to the figure -10.57 shown")
4 printf("\n      Output in terms of Va is Vo = (1+Rf/R
) *Va.....(1)")
5 printf("\n\n      (V1-Va)/R +(V2-Va)/R +(V3-Va)/R = 0"
)
6 printf("\n\n      Rearranging for Va we get Va = (V1+
V2+V3)/R*(R/3)")
7 printf("\n      Putting the value of Va in (1) we get
")
8 printf("\n\n      Vo = (1+Rf/R)*(V1+V2+V3)/3")
9 printf("\n      But from the figure Vo = V1+V2+V3 \n\
n      Therefore")
10 printf("      (V1+V2+V3) = (1+Rf/R)*(V1+V2+V3)/3")
11 printf("\n\n      Therefore (1+Rf/R) = 3")
12 printf("\n      => Rf=2R")

```

Scilab code Exa 10.16 Output voltage

```

1 //EX10_16 PG-10.64
2 clc

```

```

3 disp("Refer to the figure -10.58 and figure -10.58(a)
      shown")
4 R1=1e3;
5 R2=R1;
6 Rf=5e3; //feedback resistance
7 R=1e3; //resistance connected to the inverting
      terminal
8 V1=1; //first input voltage at the non inverting
      terminal
9 V2=3; //second input voltage at the non inverting
      terminal
10 Vb=(V1*R2+V2*R1)/(R1+R2); //voltage at the non
      inverting terminal
11 Vo=(1+Rf/R)*Vb; //output voltage
12 printf("\n Therefore output voltage is Vo=%f V \n",
      ,Vo)
13 //alternatively we can find the output voltage by
      the following equation
14 Vo1=(R2*(R+Rf))/(R*(R1+R2))*V1+(R1*(R+Rf))/(R*(R1+R2
      ))*V2
15 printf("\n Vo=%f \n",Vo1)

```

Scilab code Exa 10.17 Output voltage

```

1 //EX10_17 PG-10.65
2 clc
3 disp("Refer to the figure -10.59 shown")
4 Rf=10e3; //feedback resistance
5 R1=10e3;
6 R2=20e3;
7 R3=30e3;
8 R4=40e3;
9 V1=-1; //first input voltage at the inverting
      terminal
10 V2=2; //second input voltage at the inverting

```

```

    terminal
11 V3=3; //third input voltage at the inverting terminal
12 V4=-2; //fourth input voltage at the inverting
    terminal
13 Vo=-(Rf/R1*V1+Rf/R2*V2+Rf/R3*V3+Rf/R4*V4); //output
    voltage
14 printf("\n Therefore output voltage is Vo=%f V \n"
    ,Vo)

```

Scilab code Exa 10.18 Output voltage

```

1 //EX10_18 PG-10.66
2 clc
3 Rf=1e6; //feedback resistance
4 R1=200e3;
5 R2=250e3;
6 R3=500e3;
7 V1=-2; //first input voltage at the inverting
    terminal
8 V2=2; //second input voltage at the inverting
    terminal
9 V3=11; //third input voltage at the inverting
    terminal
10 Vo=-(Rf/R1*V1+Rf/R2*V2+Rf/R3*V3); //output voltage
11 printf("\n Therefore output voltage is Vo=%f V \n"
    ,Vo)
12 //in the book the output Vo=-20V if the value of V3
    =11V
13 //but in the question the value of V3=1V so
14 //I have taken V3=11V so that the Vo=-20V

```

Scilab code Exa 10.19 Output voltage

```

1 //EX10_19 PG-10.66
2 clc
3 Rf=60e3; //feedback resistance
4 R1=10e3;
5 R2=20e3;
6 R3=30e3;
7 V1=-1; //first input voltage at the inverting
    terminal
8 V2=-2; //second input voltage at the inverting
    terminal
9 V3=3; //third input voltage at the inverting terminal
10 Vo=-(Rf/R1*V1+Rf/R2*V2+Rf/R3*V3); //output voltage
11 printf("\n Therefore output voltage is Vo= %.0 f V \n"
    ,Vo)

```

Scilab code Exa 10.20 Design of adder circuit

```

1 //EX10_20 PG-10.67
2 clc
3 printf("\n      Vo = -(0.1V1 + 0.5V2 + 20V3)\n\n")
4 Rf=10; //we assume feedback resistance to be equal to
    10kohm
5 R1=Rf/0.1; //Rf/R1=0.1 given
6 R2=Rf/0.5; //Rf/R2=0.5 given
7 R3=Rf/20; //Rf/R3=20 given
8 printf("      R1= %.0 f kohm  R2= %.0 f kohm R3 = %.0 f
    ohm\n",R1,R2,R3*1e3)
9 printf("\n      The circuit design is shown")

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 10.21 Design of an Opamp circuit

```

1 //EX10_21 PG-10.70
2 clc
3 printf("\n      Vo = (2V1 - 3V2 + 4V3 - 5V4)\n\n")
4 printf("      The positive terms and negative terms can
           be added separately\n\n")
5 printf("\n      Vo1 = (2V1 + 4V3 )\n")
6 Rf1=100; //we assume feedback resistance to be equal
           to 100kohm
7 R1=Rf1/2; //Rf/R1=2 given
8 R3=Rf1/4; //Rf/R3=4 given
9 printf("      Therefore R1= %.0 fkohm      R3 = %.0 fkohm\n"
           ,R1 ,R3)
10
11 printf("\n      Vo2 = -(3V2 + 5V4)\n")
12 Rf2=120; //we assume feedback resistance to be equal
           to 120kohm
13 R2=Rf2/3; //Rf/R2=3 given
14 R4=Rf2/5; //Rf/R4=5 given
15 printf("      Therefore R2= %.0 fkohm      R4 = %.0 fkohm\n"
           ,R2 ,R4)
16 printf("\n      The output voltage is Vo = Vo2-Vo1 = (2
           V1 - 3V2 + 4V3 - 5V4)")
17 printf("\n      The circuit design is shown")
18 printf("\n      For the subtractor we use R = 100kohm
           ")

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 10.22 Output voltage

```

1 //EX10_22 PG-10.76
2 clc
3 R1=100e3;
4 Cf=1e-6;

```

```
5 Vm=6e-3; //peak value of the input voltage
6 fr=2e3; //frequency supplied at the input
7 w=2*pi*fr; //angular frequency in rad/s
8 a=-Vm/(R1*Cf) //constant
9 printf("\n We integrate Vin ie Vo = %.2f*integrate
        (sin(4*pi*t))\n\n",a)
10 function y=f(x),y=sin(w*x),endfunction
11 t=input(' Enter the value of t (between 0 and 1) :
           ');
12 //the limit is from 0 to t
13 I=intg(0,t,f); //we should enter the value of t
14 x=I*a;
15 disp(x);
```

Chapter 11

Cathode Ray Oscilloscope CRO

Scilab code Exa 11.1 Amplitude and rms value of sinusoidal voltage

```
1 //EX11_1 PG-11.16
2 clc
3 disp("Refer to the figure -11.11 showwn")
4 disp("from the figure we can see that the screen is
      divided such")
5 disp("that one part of the half wave is sub-divided
      into 5 units")
6 disp("1subdivision=(1/5) units=0.2 units")
7 disp("amplitude of the positive peak signal=2
      division+3subdivision ")
8 disp("ie amplitude of the positive peak signal
      =2+3*0.2=2.6")
9 Vp=2+3*0.2; //amplitude of the peak voltage in terms
               of division
10 Vpp=2*Vp; //peak to peak voltage in terms of division
11 VA=2; //Vertical attenuation in (mV/div)
12 V=Vpp*VA; //required peak to peak output voltage in
               volts
13Vm=V/2; //amplitude of the output voltage in volts
14 printf("\n Therefore amplitude of the output voltage
      in volts=%f mV \n",Vm)
```

```
15 Vrms=Vm/sqrt(2); //rms value of the output voltage
16 printf("\n Therefore rms value of the output voltage
in volts=%f mV \n",Vrms)
```

Scilab code Exa 11.2 Rms voltage and frequency

```
1 //EX11_2 PG-11.19
2 clc
3 Vd=2; //voltage per division in (V/div)
4 Td=2e-3; //time base division in (s/div)
5 Vdiv=3; //vertical occupancy in division as shown in
the screen
6 Vpp=Vd*Vdiv; //peak to peak voltage
7 Vm=Vpp/2; //peak voltage
8 Vrms=Vm/sqrt(2); //rms value of the output voltage
9 printf("\n Therefore rms value of the output voltage
in volts=%f V \n",Vrms)
10 Hdiv=2; //horizontal occupancy in division as shown
in the screen
11 T=Hdiv*Td; //time period of the waveform
12 f=1/T; //frequency
13 printf("\n Therefore frequency f=%f Hz \n ",f)
```

Chapter 12

Communication Systems

Scilab code Exa 12.1 Modulation index and percentage modulation

```
1 //EX12_1 Pg-12.14
2 clc
3 Vm=40; //peak value of the modulating signal
4 Vc=50; //peak value of the carrier signal
5 m=Vm/Vc; //modulation index
6 %m=m*100;
7 printf("modulation index m=%.1f \n
    %%m=%.0f%% \n",m,%m)
```

Scilab code Exa 12.2 Lower and upper side band frequency

```
1 //EX12_2 Pg-12.14
2 clc
3 clear
4 L=40e-6;
5 C=12e-9;
6 x=2*pi*sqrt(L*C);
7 fc=1/x; //carrier frequency
```

```

8 f=5e3; //given audio frequency
9 fusb=fc+f; //upper side band frequency
10 flsb=fc-f; //lower side band frequency
11 BW=fusb-flsb; //required bandwidth
12 printf("Therefore upper side band frequency fusb=%.
          f Hz \n",fusb)
13 printf(" Therefore lower side band frequency flsb=%
          .0f Hz \n",flsb)
14 printf("\n required bandwidth BW=%0.0fHz",BW)
15 //in the book fc is approximated to 230Khz but the
      exact answer is 229.72kHz

```

Scilab code Exa 12.3 AM modulated waveform

```

1 //EX12_3 Pg-12.17
2 clc
3 clear
4 fm=5e3; //assume modulation frequency f=5kHz
5 fc=1080e3; //assume carrier frequency f=1080kHz
6 time=0:2.3148e-7:8e-4;
7 //Waveform of modulated signal for m=0.75
8 m1=0.75; //modulation index
9 VmbyVc=m1
10 Vm=1; //we assume modulation voltage=1V
11 Vc=Vm/m1; //carrier voltage
12 k=VmbyVc; //modulation index = Vm/Vc
13 printf("\n for modulation index m=0.75 Vc=%0.2f V",Vc
          )
14
15 xset('window',1)
16 mt=k*pi*(fm*time);
17 sam=Vc*(1+mt).*sin(2*pi*fc*time);
18 plot(time(1:1500),sam(1:1500));
19 title(' Waveform of modulated signal m=0.75 ');
20 xlabel('Time ( sec )');

```

```

21 ylabel('Amplitude (Vc=1.33V)');
22 xgrid(color("gray"));
23
24 //Waveform of modulated signal for m=1
25 m1=1;
26 VmbyVc=m1
27 Vm=1; //we assume modulation voltage=1V
28 Vc=Vm/m1; //carrier voltage
29 k=VmbyVc;//modulation index = Vm/Vc
30 printf("\n for modulation index m=1 Vc=%f V",Vc
)
31
32 xset('window',2)
33 mt=k*sin(2*pi*fm*time);
34 sam=Vc*(1+mt).*sin(2*pi*fc*time);
35 plot(time(1:1500),sam(1:1500));
36 title(' Waveform of modulated signal m=1');
37 xlabel('Time (sec)');
38 ylabel('Amplitude (Vc=1V)');
39 xgrid(color("gray"));
40
41 //Waveform for modulated signal for m=1.25
42 m1=1.25;
43 VmbyVc=m1
44 Vm=1; //we assume modulation voltage=1V
45 Vc=Vm/m1; //carrier voltage
46 k=VmbyVc;//modulation index = Vm/Vc
47 printf("\n for modulation index m=1.25 Vc=%f V",Vc
)
48
49 xset('window',3)
50 mt=k*sin(2*pi*fm*time);
51 sam=Vc*(1+mt).*sin(2*pi*fc*time);
52 plot(time(1:1500),sam(1:1500));
53 title(' Waveform of modulated signal m=1.25');
54 xlabel('Time (sec)');
55 ylabel('Amplitude (Vc=0.8V)');
56 xgrid(color("gray"));

```

Scilab code Exa 12.4 1Modulation index 2sideband frequencies and amplitude 3bandwidth

```
1 //EX12_4 Pg-12.22
2 clc
3 clear
4 //modulation index
5 Vm=10; //peak value of the audio frequency signal
6 Vc=50; //peak value of the carrier signal
7 m=Vm/Vc;//modulation index
8 %m=m*100;
9 printf("modulation index m=%1f \n      ie
10 %%m=%0.f %% \n",m,%m)
11 //sideband frequencies
12 wm=2*%pi*500;
13 fm=wm/(2*%pi);
14 wc=2*%pi*1e5;
15 fc=wc/(2*%pi);
16 fusb=fc+fm; //upper side band frequency
17 flsb=fc-fm; //lower side band frequency
18 printf("\n Therefore upper side band frequency fusb=
19 %.1f kHz \n",fusb*1e-3)
20 printf(" Therefore lower side band frequency fusb=%
21 .1f kHz \n",flsb*1e-3)
22 //amplitude of each sinusoidal frequency
23 A=m*Vc/2;
24 printf("\n amplitude of upper and lower side bands=%
25 .f V \n",A)
26 //bandwidth required
27 BW=fusb-flsb;//required bandwidth
28 printf("\n required bandwidth BW=%0.0fHz \n",BW)
29 //power delivered to the load
30 R=600;//load resistance
31 P=Vc^2/(2*R)*(1+m^2/2)
32 printf("\n power delivered to the load %.3f W \n ",P)
```

```
    )
29 //transmission efficiency
30 n=m^2/(2+m^2)*100;
31 mprintf("\n transmission efficiency n=%f %% \n",n)
```

Scilab code Exa 12.5 Total power

```
1 //EX12_5 Pg-12.23
2 clc
3 clear
4 Pc=400; //power of the carrier signal
5 m=0.8; //modulation index
6 P=Pc*(1+m^2/2)
7 printf(" Therefore total power in the modulated
       wave is %.0f W",P)
```

Scilab code Exa 12.6 Power of each sidebands

```
1 //EX12_6 Pg-12.23
2 clc
3 clear
4 m=0.75; //modulation index
5 P=20; //total power in kW
6 Pc=P/(1+m^2/2) //since P=Pc*(1+m^2/2)
7 printf(" therefore carrier power in the modulated
       wave is %.1f kW",Pc)
8 Psb=Pc*m^2/4; //side band power
9 Pusb=Ps;
10 Plsb=Ps;
11 printf("\n Pusb=%.1f kW \n Plsb=%.1f kW",Pusb,Plsb)
```

Scilab code Exa 12.7 Antenna current

```
1 //EX12_7 Pg-12.25
2 clc
3 clear
4 m=0.6; //modulation index
5 Itotal=5; //total antenna current
6 //Ic=total antenna current when only the carrier is sent
7 Ic=Itotal/sqrt(1+m^2/2) //since Itotal=Ic*sqrt(1+m^2/2)
8 printf("Therefore total antenna current when only the carrier is sent Ic=%f A",Ic)
```

Scilab code Exa 12.8 modulation index

```
1 //EX12_8 Pg-12.26.
2 clc
3 clear
4 Ic=poly(0,'Ic'); //unmodulated carrier signal
5 Itotal=1.15*Ic; //total rms current when the signal is modulated
6 x=Itotal/Ic;
7 x=horner(x,1)
8 y=2*((x)^2-1)
9 m=sqrt(y)
10 printf("modulation index m=%f ",m)
```

Scilab code Exa 12.9 modulation index

```
1 //EX12_9 Pg-12.28
2 clc
3 clear
```

```
4 m1=0.6; //first modulation index
5 m2=0.3; //second modulation index
6 m3=0.4; //third modulation index
7 mt=sqrt(m1^2+m2^2+m3^2);
8 printf(" total modulation index m=%f ",mt)
```

Scilab code Exa 12.10 modulation index and total radiated power

```
1 //EX12_10 Pg-12.28
2 clc
3 clear
4 Ptotal=11.8; //radiated power in kW when the carrier
   is modulated
5 Pc=10; //radiated power in kW when the carrier is
   unmodulated
6 m=sqrt(2*((Ptotal/Pc)-1))
7 //when another sine wave of 30% of the
8 //initial modulation is transmitted simultaneously
   then
9 m1=0.3; //added sine wave signal is 30%
10 mt=sqrt(m1^2+m^2);
11 P=Pc*(1+mt^2/2); //total radiated power
12 printf(" total radiated power P=%f kW ",P)
```

Scilab code Exa 12.11 Carrier power

```
1 //EX12_11 Pg-12.30
2 clc
3 clear
4 Ptotal=10; //radiated power in kW when the carrier is
   modulated
5 m=0.75; //modulation index
6 Pc=Ptotal/(1+m^2/2) //since Ptotal=Pc*sqrt(1+m^2/2)
```

```
7 printf("\n carrier power Pc=%.1f kW \n",Pc)
```

Scilab code Exa 12.12 Frequencies

```
1 //EX12_12 Pg-12.30
2 clc
3 clear
4 fc=1000e3; //carrier frequency
5 fm1=300; //first audio frequency
6 fm2=800; //second audio frequency
7 fm3=1e3; //third audio frequency
8 fusb1=fc+fm1; //upper side band frequency
9 flsb1=fc-fm1; //lower side band frequency
10 fusb2=fc+fm2; //upper side band frequency
11 flsb2=fc-fm2; //lower side band frequency
12 fusb3=fc+fm3; //upper side band frequency
13 flsb3=fc-fm3; //lower side band frequency
14 printf("fusb1=% .1f kHz \n flsb1=% .1f kHz\n\n fusb2=% .1f kHz\n",fusb1*1e-3,flsb1*1e-3,fusb2*1e-3)
15 printf(" flsb2=% .1f kHz \n\n fusb3=% .1f kHz \n flsb3=% .1f kHz \n",flsb2*1e-3,fusb3*1e-3,flsb3*1e-3)
```

Scilab code Exa 12.13 Total sideband power radiated

```
1 //EX12_13 Pg-12.30
2 clc
3 clear
4 m1=0.55; //first modulation index
5 m2=0.65; //second modulation index
6 mt=sqrt(m1^2+m2^2);
7 Pc=360; //power radiated by the carrier signal
8 Psb=Pc*mt^2/2 //total sideband power radiated
```

```
9 printf("Therefore total sideband power radiated Psb= %.3f W",Psb)
10 //in the question Pc is taken as 360W but in the answer it is taken as
11 //300W I have taken Pc=300W so that Psb=150.5W
```

Scilab code Exa 12.14 Current I

```
1 //EX12_14 Pg-12.30
2 clc
3 clear
4 m=0.5; // modulation index
5 It=12; //antenna current when AM transmitter is 50% modulated
6 Ic=It/sqrt(1+m^2/2); //carrier current
7 m=0.9; //when modulation depth is increase to 0.9
8 It=Ic*sqrt(1+m^2/2)
9 printf("Therefore total antenna current It=%f A", It)
```

Scilab code Exa 12.15 Current and percentage power swing

```
1 //EX12_15 Pg-12.31
2 clc
3 clear
4 m1=0.6; // modulation index
5 It=1.5; //antenna current when AM transmitter is 50% modulated
6 Ic=It/sqrt(1+m1^2/2); //carrier current
7 m2=0.7 //when another modulated signal is added
8 m=sqrt(m1^2+m2^2); //total modulation index
9 It=Ic*sqrt(1+m^2/2)
10
```

```

11 printf("\n Therefore total antenna current It=%f A
12 \n",It)
13 disp(" Ptotal=Pc+Pc*m^2/4+Pc*m^2/4 => Total power
14 radiated")
15 Pc=poly(0,'Pc');
16 Ptotal=Pc+Pc*m^2/4+Pc*m^2/4 ;
17 P=Pc+Pc*m^2/4 //Total power if one of the side band
18 is suppressed
19 %P=P/Ptotal;//percentage power saving
20 %P=horner(%P,1)*100
21 mprintf("\n Therefore percentage power saving %%P=%
22 .0 f %%",%P)

```

Scilab code Exa 12.16 1Carrier frequency 2modulating frequency 3carrier power 4tot

```

1 //EX12_16 Pg-12.32
2 clc
3 clear
4 disp(" Output voltage of the transmitter Vam
5 =400(1+0.4 sin6280t)sin3.14*10^7 t")
6 Vc=400;//amplitude of carrier voltage
7 m=0.4;//modulation index
8 R=600;//load resistance
9 wm=6280;
10 wc=3.14e7;
11 fc=wc/(2*pi);
12 fm=wm/(2*pi);
13 Pc=Vc^2/(2*R);
14 Ptotal=Pc*(1+m^2/2);
15 printf("\n carrier frequency Fc=%f MHz \n
16 modulating frequency =%f Hz \n ",fc*1e-6,fm)
17 printf("\n carrier power Pc=%f W \n Total power
18 output Ptotal=%f W \n ",Pc,Ptotal)
19 //peak power output results when modulating signal
20 //is at the peak of the +ve half cycle

```

```

18 Vm=m*Vc ;
19 V=Vc+Vm; //peak output voltage
20 P=V^2/(2*R); //peak power output
21 printf("\n Peak output voltage P=%f W ",P)
22 //The exact value of fc is 4997465 Hz but in the
   book the
23 //value is taken as 5 MHz same is the case for fm

```

Scilab code Exa 12.17 Equation of the wave and output wave form

```

1 //EX12_17 Pg-12.33
2 clc
3 clear
4 disp(" equation of the Am sine wave =Vc(1+m*sinwm*t)
      *sinwc*t")
5 Vc=12; //amplitude of carrier voltage
6 m=0.5; //modulation index
7 fc=10e6; //carrier frequency
8 fm=1e3; //modulated frequency
9 wc=2*pi*fc;
10 wm=2*pi*fm;
11 t=0:2.3148e-7:8e-4;
12 Vam=Vc*(1+m*sin(wm*t).*sin(wc*t))
13 fusb=fc+fm; //upper side band frequency
14 flsb=fc-fm; //lower side band frequency
15 A=m*Vc/2; //amplitude of side bands
16
17 //plotting of the graph
18 clf();
19 x=[ flsb flsb ]; //x-coordinate
20 y=[ 0 A ]; //y-coordinate
21
22 plot2d(x,y,style=2)
23 x1=[10e6 10e6]; //x-coordinate
24 y1=[ 0 12]; //y-coordinate

```

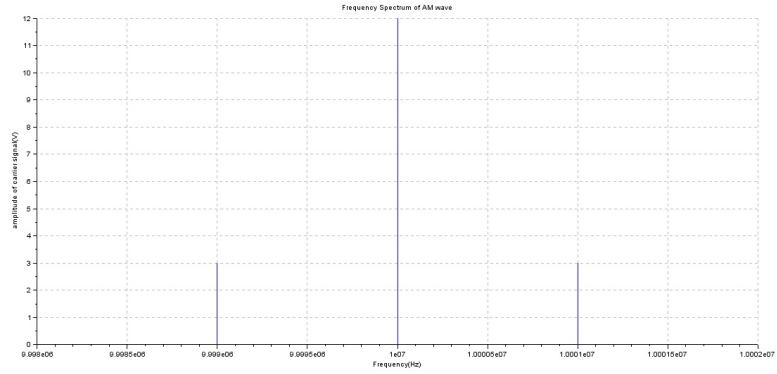


Figure 12.1: Equation of the wave and output wave form

```

25 plot2d(x1,y1,style=2)
26 x2=[fusb fusb]; //x-coordinate
27 y2=[ 0 A]; //y-coordinate
28 plot(x2,y2)
29 x5=[flsb-1e3 flsb-1e3]; //x-coordinate
30 y5=[ 0 4 ]; //y-coordinate
31 plot(x5,y5)
32 x6=[fusb+1e3 fusb+1e3]; //x-coordinate
33 y6=[ 0 4 ]; //y-coordinate
34 plot2d(x6,y6)
35
36 xlabel('Frequency (Hz)');
37 ylabel('amplitude of carrier signal(V)');
38 title("Frequency Spectrum of AM wave")
39 xgrid(color("grey"));

```

Scilab code Exa 12.18 Percentage power saving

```
1 //Ex12_18 PG-12.18
```

```

2 clc
3 clear
4 printf(" When modulation index m=100%% ")
5 m=1;
6 disp(" Now Pdsbfc=1.5*Pc or Pdsbfc/Pc=1.5")
7 Pc=poly(0, 'Pc')
8 Pdsbfc=Pc*(1+m^2/2); //power required for double
    sideband with full carrier transmission
9 Pssb=Pc*m^2/4;
10 %P=(Pdsbfc-Pssb)/Pdsbfc*100
11 x=horner(%P ,1)
12 printf(" %%Power saving %%P :%f %%\n\n",x)
13
14 disp(" When modulation index m=50%% ")
15 m=0.5;
16 Pdsbfc=Pc*(1+m^2/2); //power required for double
    sideband with full carrier transmission
17 printf(" Now Pdsbfc=Pc*(1+m^2/2) \n Pdsbfc=1.125*
    Pc or Pdsbfc/Pc=1.125\n")
18 Pssb=Pc*m^2/4;
19 %P=(Pdsbfc-Pssb)/Pdsbfc*100
20 x=horner(%P ,1)
21 printf(" %%Power saving %%P :%f %%",x)

```

Scilab code Exa 12.19 frequency deviation and modulation index

```

1 //EX12_19 Pg-40
2 clc
3 clear
4 R=2; //frequency deviation constant in KHz/V
5 V=20; //amplitude of the modulation signal
6 fd=R*V; // frequency deviation
7 f=4; //frequency applied in kHz
8 printf("\n Therefore frequency deviation f=%0.0f kHz
    \n",fd)

```

```
9 m=fd/f; // modulation index
10 printf(" modulation index m=%f ",m)
```

Scilab code Exa 12.20 Frequency deviation and modulation index

```
1 //EX12_20 Pg-40
2 clc
3 clear
4 disp("when modulating voltage V=2.5 V")
5 V=2.5; //modulating voltage
6 fd1=5; // frequency deviation in kHz
7 R=fd1/V; //frequency deviation constant in KHz/V
8 printf("\n frequency deviation constant R=%f KHz/V
      \n",R)
9 disp("when modulating voltage V=7.5 V")
10 V=7.5; //new value amplitude of the modulating
           voltage
11 fd2=R*V//new frequency deviation in kHz
12 printf("\n Therefore frequency deviation f=%f kHz
      \n",fd2)
13 disp("when modulating voltage V=10 V")
14 V=10; //new value amplitude of the modulating voltage
15 fd3=R*V//new frequency deviation in kHz
16 printf("\n Therefore frequency deviation f=%f kHz
      \n",fd3)
17 fm=0.5; //modulation frequency in kHz ie 0.5kHz=500Hz
18 mf1=fd1/fm;
19 mf2=fd2/fm;
20 fm1=.25 //new modulation frequency in kHz ie 0.25kHz
           =250Hz
21 mf3=fd3/fm1;
22 printf("\n modulation index \n mf1=%f \n mf2=%f
      \n mf3=%f \n",mf1,mf2,mf3)
```

Scilab code Exa 12.21 Maximum deviation and modulation index

```
1 //EX12_21 Pg-41
2 clc
3 clear
4 mf=60; //modulation index
5 fm=0.4; //modulation frequency in kHz ie 0.4 kHz=400Hz
6 //fd_max=maximum frequency deviation
7 fd_max=mf*fm; //since mf=fd_max/fm
8 printf("maximum deviation fd_max=%f kHz \n", fd_max
)
9 V=2.4; //modulating voltage
10 R=fd_max/V; //frequency deviation constant in KHz/V
11 disp("when modulating voltage V=3.2 V")
12 V=3.2;
13 fd=R*V; //frequency deviation
14 fm=0.25 //modulation frequency in kHz ie 0.25 kHz=250
    Hz
15 mf=fd/fm;
16 printf("\n modulation index mf=%f", mf)
17 //in the book the final answer for modulation mf=80
18 //is wrong the correct answer is mf=128
```

Scilab code Exa 12.22 Peak frequency deviation modulation index

```
1 //EX12_22 Pg-41
2 clc
3 clear
4 R=5; //frequency deviation constant in KHz/V
5 fm=10; //modulation frequency in kHz
6 V=15; //amplitude of the modulating signal
7 fd=R*V; //frequency deviation
```

```

8 printf("\n maximum frequency deviation fd=%f KHz/
      V \n",fd)
9 mf=fd/fm;
10 printf(" \n modulation index mf=%f",mf)

```

Scilab code Exa 12.23 1carrier and modulating frequency 2modulation index and maxi

```

1 //EX12_23 Pg-41.43
2 clc
3 clear
4 disp(" equation of a frequency modulated v=A*sin(wc*t
      +mf*sin(wm*t))")
5 disp(" or v=A*sin(wc*t-fd/fm*cos(wm*t)) where fd=
      frequency deviation")
6 disp("Now v=50*sin(5e8*t-10*cos(1000*t))")
7 A=50; //peak value of the modulating signal
8 wc=5e8;
9 mf=10;
10 wm=1000;
11 fc=wc/(2*pi); //carrier frequency
12 printf("\n carrier frequency fc=%f MHz \n",fc*1e
      -6)
13 fm=wm/(2*pi); //modulating frequency
14 printf(" modulating frequency fc=%f Hz \n",fm)
15 //fd_max=maximum frequency deviation
16 fd_max=mf*fm; //since mf=fd_max/fm
17 printf(" \n modulation index mf=%f",mf)
18 printf(" \n maximum deviation fd_max=%f Hz \n",
      fd_max)
19 Vrms=A/sqrt(2); //rms value of the modulating signal
20 R=75; //wave resistance
21 P=Vrms^2/R;
22 printf("\n Power dissipated by the wave in
      resistance P=%f W",P)

```

Scilab code Exa 12.24 sketching the spectrum of the modulated FM wave

```
1 //EX12_24 Pg-41.47
2 clc
3 clear
4 V=5; //amplitude of modulating voltage
5 R=1; //frequency deviation constant in KHz/V
6 fd=V*R; // frequency deviation in kHz
7 fm=15; //modulating frequency in kHz
8 mf=fd/fm; //modulation index
9 printf("\n modulation index mf=%f",mf);
10 disp("Now we refer from the table -12.2 of Bessel
      function ")
11 printf("\n For modulation index mf=%f we take the
      value of J0,J1, and J2 ",mf);
12 J0=0.96; //for carrier frequency
13 J1=0.18; //first side frequency
14 J2=0.02; //second side frequency
15 A=5 //amplitude of the carrier frequency
16 J0=J0*A; //for carrier frequency
17 J1=J1*A; //first side frequency
18 J2=J2*A; //second side frequency
19 printf("\n J0=%f\n J1=%f\n J2=%f",J0,J1,J2)
20 disp("Now we plot the frequency spectrum")
21 clf()
22 x=[ 89.97    89.97]; //x-coordinate
23 y=[ 0        0.1]; //y-coordinate
24 plot2d(x,y,style=2)
25 x1=[89.985   89.985]; //x-coordinate
26 y1=[ 0        0.9]; //y-coordinate
27 plot2d(x1,y1,style=2)
28 x2=[90       90]; //x-coordinate
29 y2=[ 0      4.8]; //y-coordinate
```

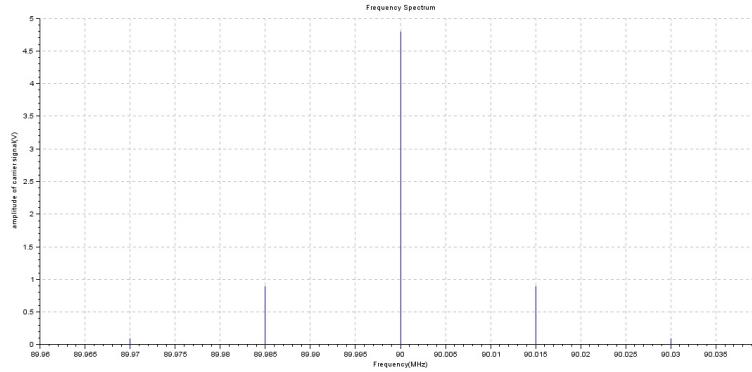


Figure 12.2: sketching the spectrum of the modulated FM wave

```

30 plot(x2,y2)
31 x3=[90.015 90.015]; //x-coordinate
32 y3=[ 0      0.9]; //y-coordinate
33 plot(x3,y3)
34 x4=[90.03 90.03]; //x-coordinate
35 y4=[ 0      0.1]; //y-coordinate
36 plot(x4,y4)
37 x5=[90.04 90.04]; //x-coordinate
38 y5=[ 0      5]; //y-coordinate
39 plot(x5,y5)
40 x6=[ 89.96 89.96]; //x-coordinate
41 y6=[ 0      5]; //y-coordinate
42 plot2d(x6,y6)
43 xlabel('Frequency (MHz)');
44 ylabel('amplitude of carrier signal(V)');
45 title("Frequency Spectrum")
46 xgrid(color("grey"));

```

Scilab code Exa 12.25 Percent modulation

```

1 //EX12_25 Pg-41.48
2 clc
3 clear
4 fd=15; //frequency deviation in kHz
5 f=75; //maximum frequency deviation in kHz for FM
        broadcast
6 %M=fd/f*100;
7 printf("\n For FM broadcast percent modulation is
        %%M=%.0f%%\n",%M)
8 f=25; //maximum frequency deviation in kHz for TV
        broadcast
9 %M=fd/f*100;
10 printf("\n For TV broadcast percent modulation is
        %%M=%.0f%% \n",%M)

```

Scilab code Exa 12.26 Frequency deviation and carrier swing

```

1 //EX12_26 Pg-41.48
2 clc
3 clear
4 %M=80; // percent modulation in %
5 f=75; //maximum frequency deviation in kHz for FM
        broadcast
6 fd=f*%M/100; //frequency deviation in kHz since %M=fd
        /f*100;
7 printf("\n Therefore frequency deviation for FM
        broadcast fd=%.0f Khz \n",fd)
8 cs=2*fd;//carrier swing
9 printf(" carrier swing=%.0f kHz\n",cs)
10 f=25; //maximum frequency deviation in kHz for TV
        broadcast
11 fd=f*%M/100; //frequency deviation in kHz since %M=fd
        /f*100;
12 printf("\n Therefore frequency deviation for TV
        broadcast fd=%.0f Khz \n",fd)

```

```
13 cs=2*fd;//carrier swing
14 printf(" carrier swing=%0.0 f kHz\n",cs)
```

Scilab code Exa 12.27 1Carrier swing 2highest and lowest frequencies 3modulation index

```
1 //EX12_27 Pg-41.51
2 clc
3 clear
4 fd=40; //frequency deviation in kHz
5 cs=2*fd;//carrier swing
6 printf("\n carrier swing=%0.0 f kHz\n",cs)
7 fc=93.2e3;//carrier frequency in kHz
8 fh=fc+fd;//highest frequency reached
9 fl=fc-fd;//lowest frequency reached
10 printf("\n Therefore highest frequency reached fh=%
.2 f MHz\n ",fh*1e-3)
11 printf("Lowest frequency reached fl=%0.2 f MHz",fl*1e
-3)
12 fm=5;//modulating frequency in kHz
13 m=fd/fm;//frequency modulation
14 printf("\n\n modulation index m=%0.0 f ",m)
```

Scilab code Exa 12.28 1Frequency deviation 2carrier swing 3lowest frequency reached

```
1 //EX12_28 Pg-41.51
2 clc
3 clear
4 fc=50.4e3;//carrier frequency in kHz
5 fh=50.405e3//highest frequency reached in kHz
6 fd=fh-fc;//frequency deviation in kHz
7 printf("\n Therefore frequency deviation produced fd
=%0.0 f Khz \n",fd)
8 cs=2*fd;//carrier swing
```

```
9 printf("\n carrier swing=%f kHz\n",cs)
10 fl=fc-fd; //lowest frequency reached
11 printf("\n Therefore lowest frequency reached fl=%f
12 f MHz",fl*1e-3)
```

Scilab code Exa 12.29 modulation index

```
1 //EX12_29 Pg-41.52
2 clc
3 clear
4 cs=70; //carrier swing in kHz
5 //since cs=2*fd
6 fd=cs/2; //frequency deviation in kHz
7 fm=7 //modulating frequency in kHz
8 m=fd/fm;
9 printf("\n Modulation index m=%f ",m)
```

Scilab code Exa 12.30 1Carrier swing 2frequency deviation 3carrier frequency 4modu

```
1 //EX12_30 Pg-41.52
2 clc
3 clear
4 fh=99.047e3; //highest frequency reached in kHz
5 fl=99.023e3; //lowest frequency reached in kHz
6 fm=7 //modulating frequency in kHz
7 cs=fh-fl; //carrier swing
8 printf("Carrier swing=%f kHz\n",cs)
9 fd=cs/2; //frequency deviation in kHz
10 printf("\n Therefore frequency deviation fd=%f Khz
11 \n",fd)
12 fc=fh-fd; //carrier frequency in kHz
13 printf("\n Therefore carrier frequency fc=%f Mhz \
14 n",fc*1e-3)
```

```
13 m=fd/fm;  
14 printf("\n Modulation index m=%f ",m)
```

Chapter 13

Number Systems

Scilab code Exa 13.1 Represesntation of a number 98point72 in powers of 10

```
1 //EX13_1 PG-13.2
2 clc
3 clear
4 disp(" representation of the number 98.72 in power of
      10")
5 disp("N=(9*10^1)+(8*10^0)+(7*10^(-1))+(2*10^(-2))
      =98.72")
6 disp("The digit 9 has a weight of 10, the digit 8 has
      a weight of 1, the digit 7")
7 disp("has a weight of (1/10) and the digit 2 has a
      weight of (1/100)")
```

Scilab code Exa 13.2 1101point101 in power of 2 and its decimal equivalent

```
1 //EX13_2 PG-13.3
2 clc
3 clear
4 disp(" Representation of the binary number 1101.101
      in power of 2")
```

```
5 disp("N=(1*2^3)+(1*2^2)+(0*2^1)+(1*2^0)+(1*2^(-1))  
+ (0*2^(-2))+(1*2^(-3))=13.625")  
6 N=(1*2^3)+(1*2^2)+(0*2^1)+(1*2^0)+(1*2^(-1))  
+ (0*2^(-2))+(1*2^(-3))  
7 printf("\n The decimal equivalent of binary no  
1101.101 is: %.3f",N)
```

Scilab code Exa 13.3 567 in power of 8 and its decimal equivalent

```
1 //EX13_3 PG-13.3  
2 clc  
3 clear  
4 disp(" representation of the number 567 in power of 8  
")  
5 disp("N=(5*8^2)+(6*8^1)+(7*8^0)=375")  
6 printf(" Therefore decimal equivalent of 567 is: ")  
7 N=(5*8^2)+(6*8^1)+(7*8^0)  
8 printf("%0.0f",N)
```

Scilab code Exa 13.4 3FD in power of 16 and its decimal equivalent

```
1 //EX13_4 PG-13.4  
2 clc  
3 clear  
4 disp(" Representation of the hexadecimal number 3FD in  
power of 16")  
5 disp("N=(3*16^2)+(F*16^1)+(D*16^0)=1021")  
6 printf(' The Decimal equivalent of the Binary number  
3FD is: ');  
7 N=(3*16^2)+(15*16^1)+(13*16^0)  
8 printf("%0.0f",N)
```

Scilab code Exa 13.5 decimal equivalent of 231point23 with base 4

```
1 //EX13_5 PG-13.5
2 clc
3 clear
4 printf('The Decimal equivalent of the number 231.23
      with base 4 is: ');
5 x=(2*4^2)+(3*4^1)+(1*4^0)+(2*4^(-1))+(3*4^(-2))
6 printf("%.4 f",x)
```

Scilab code Exa 13.6 counting from 0 to 9 in radix 5

```
1 //EX13_6 PG-13.5
2 clc
3 clear
4 disp("decimal from 0 to 9 in radix 5 ")
5 for i=0:1:9;
6   a=i/5;
7   b=modulo(i,5);
8   printf("%d=%d%d\n",i,a,b); //conversion from
      decimal to radix 5
9 end
```

Scilab code Exa 13.7 111101100 with base 2 to octal equivalent

```
1 //EX13_7 PG-13.7
2 clc
3 clear
4 printf("Conversion of binary no 111101100 to octal
      equivalent is :")
```

```
5 a=[ '111101100 '];
6 x=bin2dec(a);
7 y=dec2oct(x);
8 printf("%s",y)
```

Scilab code Exa 13.8 634 with base 8 to binary equivalent

```
1 //EX13_8 PG-13.7
2 clc
3 clear
4 printf("conversion of octal no 634 to binary
equivalent is :")
5 a=[ '634 ']
6 x=oct2dec(a)//first we convert to decimal
7 y=dec2bin(x)
8 printf("%s",y)
```

Scilab code Exa 13.9 725point63 with base 8 to binary equivalent

```
1 //EX13_9 PG-13.7
2 clc
3 clear
4 disp("conversion of octal no 725.63 to binary
equivalent")
5 a=725.63;
6 // first we convert the number 725.63(octal)to
decimal
7 x=(7*8^2)+(2*8^1)+(5*8^0)+(6*8^(-1))+(3*8^(-2));
8 //then we convert the decimal to binary
9 z=modulo(x,1)
10 x=floor(x); //separating the decimal from the integer
part
11 b=0;
```

```

12 c=0;
13 d=0;
14 while(x>0) //taking integer part into a matrix and
    convert to equivalent binary
15 y=modulo(x,2);
16 b=b+(10^c)*y;
17 x=x/2;
18 x=floor(x);
19 c=c+1;
20 end
21 for i=1:10; //converting the values after the decimal
    point into binary
22     z=z*2;
23     q=floor(z);
24     d=d+q/(10^i);
25     if z>=1 then
26         z=z-1;
27     end
28 end
29 s=b+d;
30 printf("\n The binary equivalent of the given octal
    number 725.63 is =%.6f",s);

```

Scilab code Exa 13.10 1101100010011011 with base 2 to hexadecimal equivalent

```

1 //EX13_10 PG-13.7
2 clc
3 clear
4 printf("hexadecimal equivalent of 1101100010011011
    binary is : ")
5 a=['1101100010011011'];
6 x=bin2dec(a);
7 y=dec2hex(x);
8 printf("%s",y)

```

Scilab code Exa 13.11 3FD with base 16 to binary equivalent

```
1 //EX13_11 PG-13.8
2 clc
3 clear
4 printf("Binary equivalent of 3FD hexadecimal is :")
5 a=[ '3FD ']
6 x=hex2dec(a)
7 y=dec2bin(x)
8 printf("00%b",y)
```

Scilab code Exa 13.12 5A9pointB4 with base 16 to binary equivalent

```
1 //EX13_12 PG-13.8
2 clc
3 clear
4 printf("Conversion of hexadecimal no 5A9.B4 to
      binary equivalent\n ")
5 a=[ '5A9.B4 '];
6 // first we convert the number 5A9.B4(hexadecimal)
      to decimal
7 x=(5*16^2)+(10*16^1)+(9*16^0)+(11*16^(-1))
      +(4*16^(-2));
8 //then we convert the decimal to binary
9 z=modulo(x,1)
10 x=floor(x); //separating the decimal from the integer
      part
11 b=0;
12 c=0;
13 d=0;
14 while(x>0) //taking integer part into a matrix and
      convert to equivalent binary
```

```

15 y=modulo(x,2);
16 b=b+(10^c)*y;
17 x=x/2;
18 x=floor(x);
19 c=c+1;
20 end
21 for i=1:10; //converting the values after the decimal
   point into binary
22 z=z*2;
23 q=floor(z);
24 d=d+q/(10^i);
25 if z>=1 then
26     z=z-1;
27 end
28 end
29 s=b+d;
30 printf("The binary equivalent of the given\n
   hexadecimal number 5A9.B4 is = %0.6f",s);

```

Scilab code Exa 13.13 615 with base 8 to hexadecimal equivalent

```

1 //EX13_13 PG-13.9
2 clc
3 clear
4 printf("conversion of octal no 615 to its
   hexadecimal equivalent :")
5 a=['615'];
6 x=oct2dec(a)
7 y=dec2hex(x)
8 printf("%s",y)

```

Scilab code Exa 13.14 25B with base 16 to octal equivalent

```
1 //EX13_14 PG-13.9
2 clc
3 clear
4 printf("conversion of hexadecimal no 25B to its
      octal equivalent : ")
5 a=['25B'];
6 x=hex2dec(a)
7 y=dec2oct(x)
8 printf("%s",y)
```

Scilab code Exa 13.15 1101point1 with base 2 to decimal equivalent

```
1 //EX13_15 PG-13.10
2 clc
3 clear
4 printf("conversion of binary no 1101.1 to its
      decimal equivalent =")
5 N=(1*2^3)+(1*2^2)+(0*2^1)+(1*2^0)+(1*2^(-1));
6 printf("%.1f",N)
```

Scilab code Exa 13.16 475point25 with base 8 to decimal equivalent

```
1 //EX13_16 PG-13.10
2 clc
3 clear
4 printf("conversion of octal no 475.25 to its decimal
      equivalent =")
5 N=(4*8^2)+(7*8^1)+(5*8^0)+(2*8^(-1))+(5*8^(-2));
6 printf("%.5f",N)
```

Scilab code Exa 13.17 9B2point1A with base 16 to decimal equivalent

```
1 //EX13_17 PG-13.10
2 clc
3 clear
4 printf("conversion of hexadecimal no 9B2.1A to its
      decimal equivalent =")
5 N=(9*16^2)+(11*16^1)+(2*16^0)+(1*16^(-1))
     +(10*16^(-2));
6 printf("%.1f",N)
```

Scilab code Exa 13.18 3102point12 with base 4 to decimal equivalent

```
1 //EX13_18 PG-13.10
2 clc
3 clear
4 printf("Conversion of the number 3102.12 \n with
      base 4 to its decimal equivalent =")
5 N=(3*4^3)+(1*4^2)+(0*4^1)+(2*4^0)+(1*4^(-1))
     +(2*4^(-2));
6 printf("%.3f",N)
```

Scilab code Exa 13.19 614point15 with base 7 to decimal equivalent

```
1 //EX13_18 PG-13.10
2 clc
3 clear
4 printf("Conversion of the number 614.15 with base 7
      to its decimal equivalent =")
5 N=(6*7^2)+(1*7^1)+(4*7^0)+(1*7^(-1))+(5*7^(-2));
6 printf("%.4f",N)
```

Scilab code Exa 13.20 37 with base 10 to binary equivalent

```
1 //Ex13_20 PG-13.11
2 clc
3 clear
4 printf(" Conversion of decimal number 37 to its
      binary equivalent =")
5 a=[37];
6 x=dec2bin(a);
7 printf("%s",x)
```

Scilab code Exa 13.21 214 with base 10 to octal equivalent

```
1 //Ex13_21 PG-13.12
2 clc
3 clear
4 printf("conversion of decimal number 214 to its
      octal equivalent =")
5 a=[214];
6 x=dec2oct(a)
7 printf("%s",x)
```

Scilab code Exa 13.22 3509 with base 10 to hexadecimal equivalent

```
1 //Ex13_22 PG-13.12
2 clc
3 clear
4 printf("conversion of decimal number 3509 to its
      hexadecimal equivalent =")
```

```
5 a=[3509];
6 x=dec2hex(a)
7 printf("%s",x)
```

Scilab code Exa 13.23 54 with base 10 to radix 4

```
1 //Ex13_23 PG-13.13
2 clc
3 clear
4 printf("conversion of decimal number 54 base to a
      number with base 4 =")
5 a=[54]
6 x=dec2base(a,4);
7 printf("%s",x)
```

Scilab code Exa 13.24 point8125 with base 10 to binary equivalent

```
1 //Ex13_24 PG-13.13
2 clc
3 clear
4 disp("Conversion of decimal number 0.8125 base to
      its binary equivalent ")
5 a=[0.8125];
6 z=modulo(a,1);
7 d=0;
8 for i=1:10; //converting the values after the decimal
      point into binary
9   z=z*2;
10  q=floor(z);
11  d=d+q/(10^i);
12  if z>=1 then
13    z=z-1;
14 end
```

```
15 end
16 s=d;
17 printf("\n The binary equivalent of the given
           decimal number 0.8125 is = %.4f",s);
```

Scilab code Exa 13.25 point95 with base 10 to binary equivalent

```
1 //Ex13_25 PG-13.14
2 clc
3 clear
4 disp("Conversion of decimal number 0.95 base to its
      binary equivalent ")
5 a=[0.95];
6 z=modulo(a,1);
7 d=0;
8 for i=1:10; //converting the values after the decimal
      point into binary
9     z=z*2;
10    q=floor(z);
11    d=d+q/(10^i);
12    if z>=1 then
13        z=z-1;
14    end
15 end
16 s=d;
17 printf("\n The binary equivalent of the given
           decimal number 0.95 is = %.7f",s);
```

Scilab code Exa 13.26 point640625 with base 10 to octal equivalent

```
1 //Ex13_26 PG-13.14
2 clc
3 clear
```

```

4 disp("Conversion of decimal number 0.640625 base to
      its octal equivalent =")
5 a=[0.640625];
6 z=modulo(a,1);
7 d=0;
8 for i=1:10; //converting the values after the decimal
      point into octal
9     z=z*8;
10    q=floor(z);
11    d=d+q/(10^i);
12    if z>=1 then
13        z=z-q;
14    end
15 end
16 s=d;
17 printf("\n The octal equivalent of the given decimal
      number 0.640625 is = %.2f",s);

```

Scilab code Exa 13.27 point1289062 with base 10 to hexadecimal equivalent

```

1 //Ex13_27 PG-13.14
2 clc
3 clear
4 disp("Conversion of decimal number 0.1289062 base
      to its hexadecimal equivalent ")
5 a=[0.1289062];
6 z=modulo(a,1);
7 d=0;
8 for i=1:10; //converting the values after the decimal
      point into octal
9     z=z*16;
10    q=floor(z);
11    d=d+q/(10^i);
12    if z>=1 then
13        z=z-q;

```

```

14     end
15 end
16 s=d;
17 printf("\n The hexadecimal equivalent of the given
           decimal number 0.640625 is = %.3f",s);

```

Scilab code Exa 13.28 24point6 with base 10 to binary equivalent

```

1 //Ex13_28 PG-13.14
2 clc
3 clear
4 disp("Conversion of decimal number 24.6 base to its
      binary equivalent ")
5 a=24.6;
6 z=modulo(a,1)
7 x=floor(a); //separating the decimal from the integer
      part
8 b=0;
9 c=0;
10 d=0;
11 while(x>0) //taking integer part into a matrix and
      convert to equivalent binary
12 y=modulo(x,2);
13 b=b+(10^c)*y;
14 x=x/2;
15 x=floor(x);
16 c=c+1;
17 end
18 for i=1:10; //converting the values after the decimal
      point into binary
19     z=z*2;
20     q=floor(z);
21     d=d+q/(10^i);
22
23     if z>=1 then

```

```

24         z=z-1;
25     end
26 end
27 s=b+d;
28 printf("\n The binary equivalent of the given
decimal number 24.6 is =%.5f",s);

```

Scilab code Exa 13.29 35point45 with base 10 to octal equivalent

```

1 //Ex13_29 PG-13.15
2 clc
3 clear
4 disp("Conversion of decimal number 35.45 to its
      octal equivalent ")
5 a=35.45;
6 z=modulo(a,1)
7 x=floor(a); //separating the decimal from the integer
      part
8 b=0;
9 c=0;
10 d=0;
11 while(x>0) //taking integer part into a matrix and
      convert to equivalent octal
12 y=modulo(x,8);
13 b=b+(10^c)*y;
14 x=x/8;
15 x=floor(x);
16 c=c+1;
17 end
18 for i=1:10; //converting the values after the decimal
      point into octal
19     z=z*8;
20     q=floor(z);
21     d=d+q/(10^i);
22     if z>=1 then

```

```

23         z=z-q;
24     end
25 end
26 s=b+d;
27 printf("\n The octal equivalent of the given decimal
        number 35.45 is =%.5f",s);

```

Scilab code Exa 13.30 22point46 with base 10 to hexadecimal equivalent

```

1 //Ex13_30 PG-13.16
2 clc
3 clear
4 printf("\n Conversion of decimal number 22.64 to its
        hexadecimal equivalent \n ")
5 a=22.64;
6 z=modulo(a,1)
7 x=floor(a); //separating the decimal from the integer
        part
8 b=dec2hex(x)
9
10 //converting the decimal part of the number into
        hexadecimal
11 z=z*16;
12 q=floor(z);
13 if (q==10)
14     a1=['A']
15 else if (q==11)
16     a1=['B']
17 else if (q==12)
18     a1=['C']
19 else if (q==13)
20     a1=['D']
21 else if (q==14)
22     a1=['E']
23 else if (q==15)

```

```

24           a1=[ 'F ']
25           else a1=q
26   end
27   end
28   end
29   end
30   end
31   end
32 if z>=1 then
33           z=z-q;
34 end
35
36   z=z*16;
37   q=floor(z);
38   if (q==10)
39       a2=[ 'A ']
40   else if (q==11)
41       a2=[ 'B ']
42   else if (q==12)
43       a2=[ 'C ']
44   else if (q==13)
45       a2=[ 'D ']
46   else if (q==14)
47       a2=[ 'E ']
48   else if (q==15)
49       a2=[ 'F ']
50   else a2=q
51 end
52 end
53 end
54 end
55 end
56 end
57 if z>=1 then
58           z=z-q;
59 end
60
61   z=z*16;

```

```

62     q=floor(z);
63         if (q==10)
64             a3=[ 'A']
65     else    if (q==11)
66         a3=[ 'B']
67     else    if (q==12)
68         a3=[ 'C']
69     else    if (q==13)
70         a3=[ 'D']
71     else    if (q==14)
72         a3=[ 'E']
73     else    if (q==15)
74         a3=[ 'F']
75     else a3=q
76 end
77 end
78 end
79 end
80 end
81 end
82 if z>=1 then
83     z=z-q;
84 end
85
86 z=z*16;
87 q=floor(z);
88 if (q==10)
89     a4=[ 'A']
90 else    if (q==11)
91     a4=[ 'B']
92 else    if (q==12)
93     a4=[ 'C']
94 else    if (q==13)
95     a4=[ 'D']
96 else    if (q==14)
97     a4=[ 'E']
98 else    if (q==15)
99     a4=[ 'F']

```

```

100      else a4=q
101 end
102 end
103 end
104 end
105 end
106 end
107 if z>=1 then
108     z=z-q;
109 end
110 printf("The hexadecimal equivalent of the given
           decimal number 22.64 is :")
111 printf( "%s.%s%.0f%s%.0f" ,b,a1,a2,a3,a4);

```

Scilab code Exa 13.31 convert the given binary nos to dec hex and oct

```

1 //Ex13_31 PG-13.17
2 clc
3 clear
4 printf("\n i)\n Conversion of binary number
          101101.1101 to\n\n")
5
6 //conversion into decimal form
7 N=(1*2^5)+(0*2^4)+(1*2^3)+(1*2^2)+(0*2^1)+(1*2^0)
     +(1*2^(-1))+(1*2^(-2))+(0*2^(-3))+(1*2^(-4));
8 printf(" Decimal form = %.4f\n" ,N)
9
10 //Conversion into hexadecimal form
11 x=floor(N); //separating the integer part from the
               decimal part
12 b=dec2hex(x);
13 z=modulo(N,1);
14 d=0;
15 //converting the values after the decimal point into
       hexadecimal

```

```

16 // first we convert into decimal form and then into
17 // hexadecimal form
17 for i=2:5; //converting the values after the decimal
18 // point into hexadecimal
18     z=z*16;
19     q=floor(z);
20     d=d+q/(10^i);
21     if z>=1 then
22         z=z-q;
23     end
24 end
25 if (d==.10)
26     a=[ 'A']
27     end
28 if (d==.11)
29     a=[ 'B']
30     end
31 if (d==.12)
32     a=[ 'C']
33     end
34 if (d==.13)
35     a=[ 'D']
36     end
37 if (d==.14)
38     a=[ 'E']
39     end
40 if (d==.15)
41     a=[ 'F']
42     end
43 printf(" Hexadecimal form = %s.%s\n",b,a)
44
45 //conversion into octal form
46 z=modulo(N,1)
47 x=floor(N); //separating the decimal from the integer
48 // part
48 b=0;
49 c=0;
50 d=0;

```

```

51 while(x>0) //taking integer part into a matrix and
               convert to equivalent binary
52 y=modulo(x,8);
53 b=b+(10^c)*y;
54 x=x/8;
55 x=floor(x);
56 c=c+1;
57 end
58 for i=1:10; //converting the values after the decimal
               point into octal
59 z=z*8;
60 q=floor(z);
61 d=d+q/(10^i);
62 if z>=1 then
63     z=z-q;
64 end
65 end
66 s=b+d;
67 printf(" octal form = %.2f\n\n",s);
68 printf("\n ii)\n Conversion of binary number
           11011011.100101 to\n\n")
69
70 //conversion into decimal form
71 N=(1*2^7)+(1*2^6)+(0*2^5)+(1*2^4)+(1*2^3)+(0*2^2)
      +(1*2^1)+(1*2^0)+(1*2^(-1))+(0*2^(-2))+(0*2^(-3))
      +(1*2^(-4))+(0*2^(-5))+(1*2^(-6));
72 printf(" Decimal form =%.6f\n\n",N)
73
74 //Conversion into hexadecimal form
75 x=floor(N); //separating the integer part from the
               decimal part
76 b=dec2hex(x);
77 z=modulo(N,1); //first we convert into decimal form
                  and then into hexadecimal form
78 d=0;
79 //converting the values after the decimal point into
               hexadecimal
80 for i=1:10; //converting the values after the decimal

```

```

        point into hexadecimal
81      z=z*16;
82      q=floor(z);
83      d=d+q/(10^i);
84      if z>=1 then
85          z=z-q;
86      end
87  end
88 printf(" Hexadecimal form\n      integer part 11011011
     = %s \n      ",b)
89 printf("decimal part 100101      =%.2 f\n\n" ,d)
90
91 //conversion into octal form
92 z=modulo(N,1)
93 x=floor(N); //separating the decimal from the integer
    part
94 b=0;
95 c=0;
96 d=0;
97 while(x>0) //taking integer part into a matrix and
    convert to equivalent binary
98 y=modulo(x,8);
99 b=b+(10^c)*y;
100 x=x/8;
101 x=floor(x);
102 c=c+1;
103 end
104 for i=1:10;//converting the values after the decimal
    point into octal
105 z=z*8;
106 q=floor(z);
107 d=d+q/(10^i);
108 if z>=1 then
109     z=z-q;
110     end
111 end
112 s=b+d;
113 printf(" octal      form =%.2 f" ,s);

```

Scilab code Exa 13.32 2AC5pointD with base 16 to dec oct and bin

```
1 //EX13_32 Pg-18
2 clc
3 clear
4 printf("\n\n    Conversion of hexadecimal number 2AC5
      .D to \n\n")
5
6 //conversion into decimal form
7 N=(2*16^3)+(10*16^2)+(12*16^1)+(5*16^0)+(13*16^(-1))
8 printf("    Decimal form = %.4f\n\n",N)
9
10 //conversion into octal form
11 //we take the value of the decimal form and convert
     it to octal form
12 z=modulo(N,1)
13 x=floor(N); //separating the decimal from the integer
     part
14 b=0;
15 c=0;
16 d=0;
17 while(x>0) //taking integer part into a matrix and
     convert to equivalent binary
18 y=modulo(x,8);
19 b=b+(10^c)*y;
20 x=x/8;
21 x=floor(x);
22 c=c+1;
23 end
24 for i=1:10; //converting the values after the decimal
     point into octal
25     z=z*8;
26     q=floor(z);
27     d=d+q/(10^i);
```

```

28     if z>=1 then
29         z=z-q;
30     end
31 end
32 s=b+d;
33 printf("    Octal form = %.2f\n",s);
34
35 //conversion into binary form
36 //we take the value of the decimal form and convert
   it to octal form
37 z=modulo(N,1)
38 x=floor(N); //separating the decimal from the integer
   part
39 b=0;
40 c=0;
41 d=0;
42 while(x>0) //taking integer part into a matrix and
   convert to equivalent binary
43 y=modulo(x,2);
44 b=b+(10^c)*y;
45 x=x/2;
46 x=floor(x);
47 c=c+1;
48 end
49 for i=1:10; //converting the values after the decimal
   point into binary
50     z=z*2;
51     q=floor(z);
52     d=d+q/(10^i);
53
54     if z>=1 then
55         z=z-1;
56     end
57 end
58 s=b+d;
59 printf("    Binary form : ")
60 printf("\n          Integer part 2AC5 = 00%.0f",b)
61 printf("\n          Decimal part 0.D = %.4f00",d)

```

Scilab code Exa 13.33 determination of the value of base x

```
1 //EX13_33 Pg-18
2 clc
3 clear
4 printf("\n      i )\n      Detemination of value of base
      x \n")
5 printf("      (193)_x = (623)_8\n\n")
6 printf("      First we convert (623)_8 octal into
      decimal\n\n")
7 N=(6*8^2)+(2*8^1)+(3*8^0)
8 printf("      (623)_8 = (%.0 f)_10\n\n",N)
9 printf("      Therefore (193)_x = (%.0 f)_10\n\n",N)
10 printf("      (1*x^2)+(9*x^1)+(3*x^0) = %.0 f\n\n",N)
11 printf("      x^2 + 9x + 3 = %.0 f\n\n",N)
12 printf("      x^2 + 9x %.0 f = 0\n\n",3-N)
13 a=1;
14 b=9;
15 c=-400
16 x1=(-b+sqrt(b^2-4*a*c))/(2*a);
17 x2=(-b-sqrt(b^2-4*a*c))/(2*a);
18 printf("Therefore x1 = %.0 f\n          x2 = %.0 f",x1
      ,x2)
19 printf("\n      Negative is not applicable. Therefore x
      = %.0 f",x1)
20 printf("\n      Hence (193).%.0 f = (623)_8\n\n",x1)
21
22 printf("\n      i i )\n      Detemination of value of base
      x \n")
23 printf("      (225)_x = (341)_8\n\n")
24 printf("      First we convert (341)_8 octal into
      decimal\n\n")
25 N=(3*8^2)+(4*8^1)+(1*8^0)
26 printf("      (341)_8 = (%.0 f)_10\n\n",N)
```

```

27 printf("Therefore (225)_x = (%.0f)_10\n\n",N)
28 printf(" (2*x^2)+(2*x^1)+(2*x^0) = %.0f\n\n",N)
29 printf(" 2x^2 + 2x +5 = %.0f\n\n",N)
30 printf(" 2x^2 + 2x %.0f= 0\n\n",5-N)
31 a=2;
32 b=2;
33 c=-200
34 x1=(-b+sqrt(b^2-4*a*c))/(2*a);
35 x2=(-b-sqrt(b^2-4*a*c))/(2*a);
36 printf("Therefore x1 = %.0f\n           x2 = %.0f",x1
           ,x2)
37 printf("\n      Negative is not applicable. Therefore x
           = %.0f",x1)
38 printf("\n      Hence (225)%0f = (341)_8\n\n",x1)
39
40 printf("\n      i i i )\n      Detemination of value of
           base x \n")
41 printf(" (211)_x = (152)_8\n\n")
42 printf(" First we convert (152)_8 octal into
           decimal\n\n")
43 N=(1*8^2)+(5*8^1)+(2*8^0)
44 printf(" (152)_8 = (%.0f)_10\n\n",N)
45 printf("Therefore (211)_x = (%.0f)_10\n\n",N)
46 printf(" (2*x^2)+(1*x^1)+(1*x^0) = %.0f\n\n",N)
47 printf(" 2x^2 + 1x +1 = %.0f\n\n",N)
48 printf(" 2x^2 + 1x %.0f = 0\n\n",1-N)
49 a=2;
50 b=1;
51 c=-105
52 x1=(-b+sqrt(b^2-4*a*c))/(2*a);
53 x2=(-b-sqrt(b^2-4*a*c))/(2*a);
54 printf("Therefore x1 = %.0f\n           x2 = %.0f",x1
           ,x2)
55 printf("\n      Negative is not applicable. Therefore x
           = %.0f",x1)
56 printf("\n      Hence (211)%0f = (152)_8\n\n",x1)

```

Scilab code Exa 13.34 1s complement of 1101

```
1 //EX13_34 Pg-20
2 clc
3 clear
4 printf(" 1 's complement of 1101 = ")
5 x=['1101'];
6 y=bin2dec(x)
7 z=dec2bin(bitcmp(y,4))
8 printf("00%0s",z)
```

Scilab code Exa 13.35 1s complement of 10111001

```
1 //EX13_34 Pg-20
2 clc
3 clear
4 printf(" 1 's complement of 10111001 = ")
5 x=['10111001'];
6 y=bin2dec(x)
7 z=dec2bin(bitcmp(y,8))
8 printf("0%0s",z)
```

Scilab code Exa 13.36 2s complement of 1001

```
1 //EX13_36 Pg-21
2 clc
3 clear
4 printf(" 2 's complement 1001 is :")
5 x=['1001'];
```

```
6 y=bin2dec(x); //binary to decimal conversion//  
7 z=bitcmp(y,4); //one's complement of the number//  
8 z=z+1;  
9 z2=dec2bin(z); //2's complement of the number//  
10 printf(" 0%8s",z2)
```

Scilab code Exa 13.37 2s complement of 10100011

```
1 //EX13_37 Pg-21  
2 clc  
3 clear  
4 printf(" 2's complement 10100011 is : ")  
5 x=['10100011'];  
6 y=bin2dec(x); //binary to decimal conversion//  
7 z=bitcmp(y,8); //one's complement of the number//  
8 z=z+1;  
9 z2=dec2bin(z); //2's complement of the number//  
10 printf("0%8s",z2)
```

Scilab code Exa 13.38 7s complement of 612

```
1 //EX13_38 Pg-22  
2 clc  
3 clear  
4 printf(" 7's complement of (612)_8 is : ")  
5 x=['612'];  
6 y=oct2dec(x)  
7 z=dec2oct(bitcmp(y,8))  
8 printf("%s",z)
```

Scilab code Exa 13.39 8s complement of 346

```
1 //EX13_39 Pg-21
2 clc
3 clear
4 printf("8's complement (346)_8 is : ")
5 x=[ '346 '];
6 y=oct2dec(x); //octal to decimal conversion //
7 z=bitcmp(y,9); //one's complement of the number //
8 z=z+1;
9 z2=dec2oct(z) //8's complement of the number //
10 printf("%s",z2)
```

Scilab code Exa 13.40 15s complement of A9B

```
1 //EX13_40 Pg-22
2 clc
3 clear
4 printf("15's complement (A9B)_16 is :")
5 x=[ 'A9B '];
6 y=hex2dec(x); //hexadecimal to decimal conversion //
7 z=dec2hex(bitcmp(y,11)); //15's complement of the
     number //
8 printf("%s",z)
```

Scilab code Exa 13.41 16s complement of A8C

```
1 //EX13_41 Pg-23
2 clc
3 clear
4 printf("16's complement (A8C)_16 is : ")
5 x=[ 'A8C '];
6 y=hex2dec(x); //hexadecimal to decimal conversion //
```

```
7 z=bitcmp(y,12); //one's complement of the number//  
8 z=z+1;  
9 z2=dec2hex(z) //16's complement of the number//  
10 printf("%s",z2)
```

Scilab code Exa 13.42 binary addition

```
1 //EX13_42 Pg-23  
2 clc  
3 clear  
4 x=[ '1010 '];  
5 y=[ '0011 '];  
6 //binary to decimal conversion//  
7 x=bin2dec(x)  
8 y=bin2dec(y)  
9 z=x+y;  
10 a=dec2bin(z) //decimal to binary conversion//  
11 printf('the addition of given numbers is: ')  
12 printf("%s",a)
```

Scilab code Exa 13.43 addition of 28 and 15 in binary

```
1 //EX13_43 Pg-23  
2 clc  
3 clear  
4 x=28;  
5 y=15;  
6 // decimal to binary conversion//  
7 z=x+y;  
8 a=dec2bin(z)  
9 printf('the addition of given numbers in binary is:  
' )  
10 printf("%s",a)
```

```
11 printf ('\n the addition of given numbers in decimal  
           is : ')  
12 printf ("% .0 f" ,z)
```

Scilab code Exa 13.44 subtraction of 0101 from 1011

```
1 //EX13_44 Pg-24  
2 clc  
3 clear  
4 x=[ '1011 '];  
5 y=[ '0101 '];  
6 //binary to decimal conversion//  
7 x=bin2dec(x)  
8 y=bin2dec(y)  
9 z=x-y;  
10 a=dec2bin(z)//decimal to binary conversion//  
11 printf ('the subtraction of given numbers is : ')  
12 printf ("0% s" ,a)
```

Scilab code Exa 13.45 subtraction of 101011 from 111001 using 1's complement

```
1 //EX13_45 Pg-25  
2 clc  
3 clear  
4 printf ("subtraction of 101011 from 111001 using 1 's  
           complement method")  
5 printf ("\n\n we know that 111001>101011\n\n")  
6 printf (" Therefore 111001-101011 =")  
7 x=[ '111001 '];  
8 y=[ '101011 '];  
9 //we should note that in the question the first  
   binary number is 101011 and not 1001011
```

10

```

11 //binary to decimal conversion//
12 x=bin2dec(x)
13 y=bin2dec(y)
14 y1=bitcmp(y,6)//one's complement of the smaller
   number
15 z=x+y1;//addition of x with the one's complement of y
16 //subtraction of smaller number from larger number
17 w=bitset(z,7,0)//the end round carry should be
   remove and add to z
18 a=w+1;
19 a1=dec2bin(a)//final result
20 printf(" 00%0s",a1)

```

Scilab code Exa 13.46 subtraction of 111001 from 101011 using 1's complement

```

1 //EX13_46 Pg-25
2 clc
3 clear
4 printf("subtraction of 111001 from 101011 using 1's
   complement method")
5 printf("\n\n we know that 101011<111001\n\n")
6 printf(" Therefore 101011-111001 = ")
7 x=['101011'];
8 y=['111001'];
9 //binary to decimal conversion//
10 x=bin2dec(x)
11 y=bin2dec(y)
12 y1=bitcmp(y,6)//one's complement of the larger
   number
13 z=x+y1;//addition of x with the one's complement of
   y
14 //subtraction of larger number from smaller number
15 z=bitcmp(z,6); //one's complement of the result
16 a=dec2bin(z)//decimal to binary conversion
17 printf(" -00%0s",a)//final answer is -ve

```

Scilab code Exa 13.47 subtraction of 101011 from 111001 using 2s complement

```
1 //EX13_47 Pg-26
2 clc
3 clear
4 printf("subtraction of 101011 from 111001 using 2's
      complement method")
5 printf("\n\n we know that 111001>101011\n\n")
6 printf(" Therefore 111001-101011 = ")
7 x=['111001'];
8 y=['101011'];
9 //binary to decimal conversion//
10 x=bin2dec(x)
11 y=bin2dec(y)
12 y1=bitcmp(y,6)//one's complement of the smaller
      number
13 y2=y1+1;//2's complement of the smaller number
14 //subtraction of smaller number from larger number
15 a=x+y2;
16 w=bitset(a,7,0)//we discard the carry
17 s=dec2bin(w)
18 printf("00%s",s)
```

Scilab code Exa 13.48 subtraction of 111001 from 101011 using 2s complement

```
1 //EX13_48 Pg-26
2 clc
3 clear
4 printf("subtraction of 111001 from 101011 using 2's
      complement method")
5 printf("\n\n we know that 101011<111001\n\n")
```

```

6 printf(" Therefore 101011-111001 =")
7 x=['101011'];
8 y=['111001'];
9 //binary to decimal conversion/
10 x=bin2dec(x)
11 y=bin2dec(y)
12 y1=bitcmp(y,6)//one's complement of the larger
   number
13 y2=y1+1;//2's complement of the larger number
14 //subtraction of larger number from smaller number
15 a=x+y2;//result is in two complement
16 a1=bitcmp(a,6)//one's complement of the result
17 a2=a1+1;//final answer
18 s=dec2bin(a2)
19 printf(" -00%0s",s)//final answer is -ve

```

Scilab code Exa 13.49 expression of the given decimal nos in 1s and 2s complement

```

1 //EX13_49 Pg-26
2 clc
3 clear
4 printf('for decimal number = -56 the binary
   equivalent is ')
5 x=56;
6 y=dec2bin(x)
7 printf("%0s",y)
8 z=bitcmp(x,7)//1's complement=-56
9 printf('\n the 1's complement is ')
10 z1=dec2bin(z)
11 printf("%s",z1)
12 z=z+1;//2's complement
13 printf('\n the 2's complement ')
14 z2=dec2bin(z)
15 printf("%s",z2)
16 printf('\n\n for decimal number = -107 the binary

```

```

equivalent is ')
17 x=107;
18 y=dec2bin(x)
19 printf("0%8s",y)
20 z=bitcmp(x,8) // 1's complement=-56
21 printf('\n the 1's complement is ')
22 z1=dec2bin(z)
23 printf("%8s",z1)
24 z=z+1; // 2's complement
25 printf('\n the 2's complement ')
26 z2=dec2bin(z)
27 printf("%8s",z2)

```

Scilab code Exa 13.50 decimal nos subtraction using 2s complement

```

1 //EX13_50 Pg-27
2 clc
3 clear
4 //subtraction of decimal numbers using 2's
   complement
5 //given decimal numbers
6 x=42;
7 y=68;
8 //conversion from
9 x1=dec2bin(x)
10 y1=dec2bin(y)
11 printf("The binary equivalent of 42 is :")
12 printf(" 00%8s\n",x1)
13 printf(" The binary equivalent of 68 is :")
14 printf(" 0%8s\n",y1)
15 //finding 2's complement of 68
16 y2=bitcmp(y,7);
17 y2=y2+1;
18 z=x+y2;
19 //since we have subtracted a larger number from a

```

```

20 // smaller we should take 2's complement of the
   result
21 z1=bitcmp(z,7)
22 z2=z1+1;
23 a=dec2bin(z2)
24 printf(" Therefore  $(42)_{10} - (68)_{10}$  in binary is =")
25 //final answer
26 printf(" 00%b = ",a)//the final result is negative
27 printf('-%d',z2)

```

Scilab code Exa 13.51 binary nos subtraction using 1s and 2s complement

```

1 //EX13_51 Pg-29
2 clc
3 clear
4 //subtraction of 10000 from 11010 using 1's
   complement method
5 printf(" i)\n subtraction of 10000 from 11010
   using 1's complement method ")
6 printf("\n Therefore  $11010 - 10000 =$ ")
7 x=['11010'];
8 y=['10000'];
9 //binary to decimal conversion//
10 x=bin2dec(x)
11 y=bin2dec(y)
12 y1=bitcmp(y,5)//one's complement of the larger
   number
13 z=x+y1;//addition of x with the one's complement of
   y
14 //subtraction of smaller number from larger number
15 w=bitset(z,6,0)//the end round carry should be
   remove and add to z
16 a=w+1;
17 a1=dec2bin(a)//final result
18 printf(" %b",a1)

```

```

19 x=['1000100'];
20 y=['1010100'];
21 //subtraction of 1000100 from 1010100 using 1's
   complement method
22 printf("\n\n Subtraction of 1010100 from 1000100
   using 1's complement method ")
23 printf("\n Therefore 1000100-1010100 =")
24 //binary to decimal conversion//
25 x=bin2dec(x)
26 y=bin2dec(y)
27 y1=bitcmp(y,6)//one's complement of the larger
   number
28 z=x+y1;//addition of x with the one's complement of
   y
29 //subtraction of larger number from smaller number
30 z=bitcmp(z,6);//one's complement of the result
31 a=dec2bin(z)//decimal to binary conversion
32 printf(" -%s\n",a)//the final result is negative
33
34 //subtraction of 10000 from 11010 using 2's
   complement method
35 printf("\n\n ii)\n Subtraction of 10000 from 11010
   using 2's complement method")
36 printf("\n Therefore 11010-10000 =")
37 x=['11010'];
38 y=['10000'];
39 //binary to decimal conversion//
40 x=bin2dec(x)
41 y=bin2dec(y)
42 y1=bitcmp(y,6)//one's complement of the smaller
   number
43 y2=y1+1;//2's complement of the smaller number
44 //subtraction of smaller number from larger number
45 a=x+y2;
46 w=bitset(a,7,0)//we discard the carry
47 s=dec2bin(w)
48 printf(" %s",s)
49 //subtraction of 1000100 from 1010100 using 2's

```

```

        complement method
50 printf("\n\n Subtraction of 1010100 from 1000100
           using 2's complement method ")
51 printf("\n Therefore 1000100-1010100 =")
52 x=['1000100'];
53 y=['1010100'];
54 //binary to decimal conversion//
55 x=bin2dec(x)
56 y=bin2dec(y)
57 y1=bitcmp(y,6)//one's complement of the larger
   number
58 y2=y1+1;//2's complement of the larger number
59 //subtraction of larger number from smaller number
60 a=x+y2;//result is in two complement
61 a1=bitcmp(a,6)//one's complement of the result
62 a2=a1+1;//final answer
63 s=dec2bin(a2)
64 printf(" -%s",s)//the final result is negative

```

Scilab code Exa 13.52 addition of octal nos

```

1 //EX13_52 Pg-30
2 clc
3 clear
4 printf("Addition of two numbers with octal base")
5 printf("\n\n      4_8+2_8 = ")
6 x=['4'];
7 y=['2'];
8 //octal to decimal conversion
9 x1=oct2dec(x)
10 y1=oct2dec(y)
11 z=x1+y1;//addition
12 a=dec2oct(z)//final result
13 printf("%s\n",a)
14 printf("\n\n      6_8+7_8 = ")

```

```

15 x=[ '6' ];
16 y=[ '7' ];
17 //octal to decimal conversion
18 x1=oct2dec(x)
19 y1=oct2dec(y)
20 z=x1+y1;//addition
21 //we should note that the decimal sum is greater
   than 8
22 //hence we should subtract the decimal sum by 8 to
   obtain the octal result
23 a=z-8;
24 a=dec2oct(a)
25 printf("%s\n",a)
26 printf("\n\n      1_8+7_8 = ")
27 x=[ '1' ];
28 y=[ '7' ];
29 //octal to decimal conversion
30 x1=oct2dec(x)
31 y1=oct2dec(y)
32 z=x1+y1;//addition
33 //we should note that the decimal sum is greater
   than 8
34 //hence we should subtract the decimal sum by 8 to
   obtain the octal result
35 a=z-8;
36 a=dec2oct(a)
37 printf("%s\n",a)

```

Scilab code Exa 13.53 octal nos addition

```

1 //EX13_53 Pg-31
2 clc
3 clear
4 printf("Addition of two octal numbers ")
5 printf("\n\n      167_8+325_8 = ")

```

```
6 x=[ '167 '];
7 y=[ '325 '];
8 //octal to decimal conversion
9 x1=oct2dec(x)
10 y1=oct2dec(y)
11 z=x1+y1;//addition
12 a=dec2oct(z)//final result
13 printf("%s\n",a)
```

Scilab code Exa 13.54 octal nos addition

```
1 //EX13_54 Pg-31
2 clc
3 clear
4 printf("Addition of four octal numbers ")
5 printf("\n\n      (341)_8 + (125)_8 + (472)_8 + (577)_8 = ")
6 x=[ '341 '];
7 y=[ '125 '];
8 u=[ '472 ']
9 v=[ '577 ']
10 //octal to decimal conversion
11 x1=oct2dec(x)
12 y1=oct2dec(y)
13 u1=oct2dec(u)
14 v1=oct2dec(v)
15 z=x1+y1+u1+v1;//addition
16 a=dec2oct(z)//final result
17 printf("%s\n",a)
```

Scilab code Exa 13.55 7s complement of 612

```
1 //EX13_55 Pg-31
2 clc
```

```
3 clear
4 printf("7's complement of (612)-8 = ")
5 x=['612']
6 y=oct2dec(x)
7 z=bitcmp(y,8)
8 a=dec2oct(z)
9 printf("%s\n",a)
```

Scilab code Exa 13.56 subtract 157 from 176 using 7s complement

```
1 //EX13_56 Pg-32
2 clc
3 clear
4 printf("subtraction of two octal numbers using 7's
complement")
5 printf("\n (176)-8-(157)-8")
6 printf("\n\n Therefore (176)-8-(157)-8 = ")
7 x=['176']
8 y=['157']
9 //octal to decimal conversion //
10 x=oct2dec(x)
11 y=oct2dec(y)
12 y1=bitcmp(y,9)//7's complement of the smaller
number
13 z=x+y1;//subtraction of smaller number from larger
number
14 //if there's any carry we should discard the carry
15 //and add the carry to the result
16 z=bitset(z,10,0)
17 z1=z+1;
18 a=dec2oct(z1)
19 printf("0%s\n",a)
```

Scilab code Exa 13.57 subtract 243 from 153 using 7s complement

```
1 //EX13_57 Pg-32
2 clc
3 clear
4 printf("subtraction of two octal numbers using 7's
complement")
5 printf("\n (153)_8-(243)_8")
6 printf("\n\n Therefore (153)_8 - (243)_8 =")
7 x=['153']
8 y=['243']
9 //octal to decimal conversion//
10 x=oct2dec(x)
11 y=oct2dec(y)
12 y1=bitcmp(y,9)//7's complement of the larger number
13 z=x+y1;
14 //in the subtraction of larger number from smaller
number
15 //no carry is present so we should take 7's
complement of the result
16 z1=bitcmp(z,8)
17 a=dec2oct(z1)
18 printf(" -%s",a)//the final result is negative
```

Scilab code Exa 13.58 8s complement of 346

```
1 //EX13_58 Pg-33
2 clc
3 clear
4 printf("8's complement (346)_8 is : ")
5 x=['346'];
6 y=oct2dec(x); //octal to decimal conversion//
7 z=bitcmp(y,9); //one's complement of the number//
8 z=z+1;
9 z2=dec2oct(z) //8's complement of the number//
```

```
10 printf("%s\n",z2)
```

Scilab code Exa 13.59 subtract 413 from 516 using 8s complement

```
1 //EX13_59 Pg-33
2 clc
3 clear
4 printf("subtraction of two octal numbers using 8's
complement")
5 printf("\n (516)_8 > (413)_8")
6 printf("\n\n (516)_8 - (413)_8 =")
7 x=[ '516 ']
8 y=[ '413 ']
9 //octal to decimal conversion //
10 x=oct2dec(x)
11 y=oct2dec(y)
12 y1=bitcmp(y,8)//7's complement of the smaller
number
13 y2=y1+1;//8's complement of the smaller number
14 //subtraction of smaller number from larger number
15 a=x+y2;
16 w=bitset(a,10,0)//we discard the carry
17 s=dec2oct(w)
18 printf(" %s\n",s)
```

Scilab code Exa 13.60 subtract 451 from 316 using 8s complement

```
1 //EX13_60 Pg-34
2 clc
3 clear
4 printf("subtraction of two octal numbers using 8's
complement")
5 printf("\n (316)_8 < (451)_8")
```

```

6 printf("\n\n (316)_8 - (451)_8 =")
7 x=['316']
8 y=['451']
9 //octal to decimal conversion //
10 x=oct2dec(x)
11 y=oct2dec(y)
12 y1=bitcmp(y,8)//7's complement of the larger number
13 y2=y1+1;//8's complement of the larger number
14 //subtraction of larger number from smaller number
15 a=x+y2;//the result obtained will have no carry
    since
16 //the second number is larger than the first number
17 //hence we should take 8's complement of the result
18 a1=bitcmp(a,8)//8's complement of the result
19 a2=a1+1;//final answer
20 s=dec2oct(a2)
21 printf(" -%s",s)//the final result is negative

```

Scilab code Exa 13.61 hexadecimal addition

```

1 //EX13_61 Pg-34
2 clc
3 clear
4 printf("Addition of two numbers with hexadecimal
    base")
5 printf("\n\n      3_16 + 9_16 =")
6 x=['3'];
7 y=['9'];
8 //octal to decimal conversion
9 x1=hex2dec(x)
10 y1=hex2dec(y)
11 z=x1+y1;//addition
12 a=dec2hex(z)//final result
13 printf(" %s\n",a)
14 printf("\n      9_16 + 7_16 =")

```

```

15 x=[ '9' ];
16 y=[ '7' ];
17 //octal to decimal conversion
18 x1=hex2dec(x)
19 y1=hex2dec(y)
20 z=x1+y1;//addition
21 //we should note that the decimal sum is greater
   than 16
22 //hence we should subtract the decimal sum by 16 to
   obtain the hexadecimal result
23 a=z-16;
24 a=dec2hex(a)
25 printf(" %s ",a)
26 printf('with carry of 1')
27 printf("\n\n      A_16+8_16 =")
28 x=[ 'A' ];
29 y=[ '8' ];
30 //octal to decimal conversion
31 x1=hex2dec(x)
32 y1=hex2dec(y)
33 z=x1+y1;//addition
34 //we should note that the decimal sum is greater
   than 16
35 //hence we should subtract the decimal sum by 16 to
   obtain the hexadecimal result
36 a=z-16;
37 a=dec2hex(a)
38 printf(" %s ",a)
39 printf('with carry of 1')

```

Scilab code Exa 13.62 hexadecimal addition

```

1 //EX13_62 Pg-35
2 clc
3 clear

```

```
4 printf("Addition of two hexadecimal numbers ")
5 printf("\n\n      (3F8)16+(5B3)16 =")
6 x=[ '3F8 '];
7 y=[ '5B3 '];
8 //octal to decimal conversion
9 x1=hex2dec(x)
10 y1=hex2dec(y)
11 z=x1+y1; //addition
12 a=dec2hex(z) //final result
13 printf(" %s\n",a)
```

Scilab code Exa 13.63 hexadecimal addition

```
1 //EX13_63 Pg-35
2 clc
3 clear
4 printf("    Addition of four hexadecimal numbers")
5 printf("\n    Therefore (4FB)16+(75D)16+(A12)16+
       C39)16 = ")
6 x=[ '4FB ']
7 y=[ '75D ']
8 u=[ 'A12 ']
9 v=[ 'C39 ']
10 x1=hex2dec(x)
11 y1=hex2dec(y)
12 u1=hex2dec(u)
13 v1=hex2dec(v)
14 z=x1+y1+u1+v1
15 a=dec2hex(z)
16 printf("%s",a)
```

Scilab code Exa 13.64 15s complement of A9B

```
1 //EX13_64 Pg-35
2 clc
3 clear
4 printf(" 15 's complement of (A9B)16 =")
5 x=[ 'A9B ']
6 y=hex2dec(x)
7 z=bitcmp(y,11)
8 a=dec2hex(z)
9 printf(" %s\n",a)
```

Scilab code Exa 13.65 subtraction of 98F from B02 using 15s complement

```
1 //EX13_65 Pg-36
2 clc
3 clear
4 printf("subtraction of two hexadecimal numbers using
      15 's complement")
5 printf("\n      (B02)16 > (98F)16")
6 printf("\n\n      (B02)16 - (98F)16 =")
7 x=[ 'B02 ']
8 y=[ '98F ']
9 //hexadecimal to decimal conversion
10 x=hex2dec(x)
11 y=hex2dec(y)
12 y1=bitcmp(y,12) //15's complement of the smaller
      number
13 z=x+y1; //subtraction of smaller number from larger
      number
14 //if there's any carry we should discard the carry
15 //and add the carry to the result
16 z=bitset(z,13,0)
17 z1=z+1;
18 a=dec2hex(z1)
19 printf(" %s\n",a)
```

Scilab code Exa 13.66 subtraction of C14 from 69B using 15s complement

```
1 //EX13_66 Pg-36
2 clc
3 clear
4 printf("subtraction of two hexadecimal numbers using
      15's complement")
5 printf("\n      (69B)16<(C14)16")
6 printf("\n\n      (69B)16-(C14)16 =")
7 x=['69B']
8 y=['C14']
9 //hexadecimal to decimal conversion
10 x=hex2dec(x)
11 y=hex2dec(y)
12 y1=bitcmp(y,10)//15's complement of the larger
      number
13 z=x+y1;
14 // in subtraction of larger number from smaller
      number
15 //no carry is present so we should take 15's
      complement of the result
16 z1=bitcmp(z,12)
17 a=dec2hex(z1)
18 printf(" -%s",a)//the final result is negative
```

Scilab code Exa 13.67 16s complement of A8C

```
1 //EX13_67 Pg-37
2 clc
3 clear
4 printf(" 16's complement of (A8C)16 =")
5 x=['A8C']
```

```
6 y=hex2dec(x)
7 z=bitcmp(y,11)
8 z1=z+1
9 a=dec2hex(z1)
10 printf("%s\n",a)
```

Scilab code Exa 13.68 subtraction of 972 from CB2 using 16s complement

```
1 //EX13_68 Pg-37
2 clc
3 clear
4 printf(" Subtraction of two hexadecimal numbers
      using 16's complement")
5 printf("\n (CB2)_16 > (972)_16")
6 printf("\n Therefore (CB2)_16 - (972)_16 =")
7 x=['CB2']
8 y=['972']
9 //hexadecimal to decimal conversion
10 x=hex2dec(x)
11 y=hex2dec(y)
12 y1=bitcmp(y,12)//15's complement of the smaller
      number
13 y2=y1+1;//16's complement of the smaller number
14 //subtraction of smaller number from larger number
15 a=x+y2;
16 w=bitset(a,13,0)//we discard the carry
17 s=dec2hex(w)
18 printf("%s\n",s)
```

Scilab code Exa 13.69 subtraction of 854 from 3B7 using 16s complement

```
1 //EX13_68 Pg-37
2 clc
```

```

3 clear
4 printf(" Subtraction of two hexadecimal numbers
      using 16's complement")
5 printf("\n (3B7)<16-(854)_16")
6 printf("\n Therefore (3B7)_16 - (854)_16 =")
7 x=['3B7']
8 y=['854']
9 //hexadecimal to decimal conversion
10 x=hex2dec(x)
11 y=hex2dec(y)
12 y1=bitcmp(y,12)//15's complement of the larger
      number
13 y2=y1+1;//16's complement of the larger number
14 //subtraction of larger number from smaller number
15 a=x+y2;//the result obtained will have no carry
      since
16 //the second number is larger than the first number
17 //hence we should take 16's complement of the result
18 a1=bitcmp(a,12)//16's complement of the result
19 a2=a1+1;//final answer
20 s=dec2hex(a2)
21 printf(" -%s",s)

```

Scilab code Exa 13.70 decimal addition in 8421BCD

```

1 //EX13_70 Pg-13.41
2 clc
3 clear
4 printf("Decimal addition in 8-4-2-1 BCD ")
5 printf("\n\n 24+18 = 42 =")
6 //given decimal number
7 x=24;
8 y=18;
9 //we separate each of the digit in the decimal
      number

```

```

10 x1=2;      x2=4;
11 y1=1;      y2=8;
12 //then we add each of the digit together
13 //ie x1+y1 and x2+y2
14 z1=x1+y1;    z2=x2+y2;
15
16 a=9;           //since 9_(decimal)=1001_(binary)
17 if (z1>a)
18   z1=z1+6;        //since 6_(decimal)=0110_(binary)
19 )
20 end
21 if (z2>a) then
22   z2=z2+6;
23 //if any carry is present in z2
24 //we should add the carry with z1
25 m=bitget(z2,5)
26 if (m==1) then
27   z1=z1+m
28 z2=bitset(z2,5,0)
29 end
30 end
31 z1=dec2bin(z1)
32 z2=dec2bin(z2)
33 printf(" 0%s 00%s",z1,z2)
34
35 printf("\n\n 48+58 = 106 =")
36 // given decimal number
37 x=48;
38 y=58;
39 //we separate each of the digit in the decimal
39 //number
40 x1=4;      x2=8;
41 y1=5;      y2=8;
42 //then we add each of the digit together
43 //ie x1+y1 and x2+y2
44 z3=0;      z1=x1+y1;    z2=x2+y2;
45

```

```

46 // if there is any carry is present in z2
47 // during addition then it is added to z1
48 m=bitget(z2,5)
49 if (m==1) then
50 z1=z1+m;
51 //if z2 is greater than 9(=1001 in binary )
52 //then we should add 6(=0110 in binary )
53 if (z2>9) then
54 z2=bitset(z2,5,0)
55 z2=z2+6;
56 end
57 end
58
59 //again if z1 is greater than 9(=1001 in binary )
       then 6(=0110 in binary ) is added
60 if (z1>9) then
61 z1=z1+6;
62 // if any carry is present is present in z1 then we
       should add the carry with z3
63 m=bitget(z1,5)
64 if (m==1) then
65 z3=z3+m
66 z1=bitset(z1,5,0)
67 end
68 end
69 //conversion into binary
70 z4=dec2bin(z3)
71 z5=dec2bin(z1)
72 z6=dec2bin(z2)
73 printf(" 000%s 000%s 0%s",z4,z5,z6)
74
75 printf("\n\n    175+326 = 501 =")
76 //given decimal number
77 x=175;
78 y=326;
79 //we separate each of the digit in the decimal
       number
80 x1=1;      x2=7;      x3=5;

```

```

81 y1=3;      y2=2;      y3=6
82 //then we add each of the digit together
83 //ie x1+y1 and x2+y2  x3+y3
84 z1=x1+y1;      z2=x2+y2;      z3=x3+y3;
85 // if z1 ,z2 ,z3>9(=1001 in binary ) then 6(=0110
     inbinary) is added
86 if (z1>9) then
87 z1=z1+6;
88 end
89 if (z2>9) then
90 z2=z2+6;
91 end
92 if (z3>9) then
93 z3=z3+6;
94 end
95 //if there is any carry is present in z3 during
     addition then it is added
96 //to z2 and in turn is there is any carry in z2 it
     is added to z1
97 m=bitget(z3,5)
98 if (m==1) then
99 z2=z2+m
100 if (z3>9) then
101 z3=bitset(z3,5,0)
102 end
103 end
104 //if z2  is greater than 9 then we add 6 to z2
105 if (z2>9) then
106 z2=z2+6;
107 end
108 //if there is any carry present in z2 during
     addition then it is added to z1
109 m=bitget(z2,5)
110 if (m==1) then
111 z1=z1+m
112 if (z2>9) then
113 z2=bitset(z2,5,0)
114 end

```

```

115 end
116 //conversion into binary
117 z4=dec2bin(z1)
118 z5=dec2bin(z2)
119 z6=dec2bin(z3)
120 printf(" 0%0s 000%0s 000%0s" ,z4 ,z5 ,z6)
121
122 printf("\n\n      589+199 = 788 =")
123 //given decimal number
124 x=589;
125 y=199;
126 //we separate each of the digit in the decimal
   number
127 x1=5;    x2=8;    x3=9;
128 y1=1;    y2=9;    y3=9;
129 //then we add each of the digit together
130 //ie x1+y1 and x2+y2  x3+y3
131 z1=x1+y1;    z2=x2+y2;    z3=x3+y3;
132
133 //if there is any carry is present in z3 during
   addition then it is added
134 //to z2 and in turn is there is any carry in z2 it
   is added to z1
135 //for z2
136 m=bitget(z2,5)
137 if (m==1) then
138 z1=z1+m
139 //if z2 is greater than 9(=1001 in binary )
140 //then we should add 6(=0110 in binary )
141 if (z2>9) then
142 z2=bitset(z2,5,0)
143 z2=z2+6;
144 end
145 end
146
147 //for z3
148 m=bitget(z3,5)
149 if (m==1) then

```

```

150 z2=z2+m
151 // if z3 is greater than 9(=1001 in binary )
152 //then we should add 6(=0110 in binary )
153 if (z3>9) then
154 z3=bitset(z3,5,0)
155 z3=z3+6;
156 end
157 end
158
159 //conversion into binary
160 z4=dec2bin(z1)
161 z5=dec2bin(z2)
162 z6=dec2bin(z3)
163 printf(" %s %s %s",z4,z5,z6)

```

Scilab code Exa 13.71 decimal subtraction in 8421BCD using 9s complement method

```

1 //EX13_71 Pg-13.43
2 clc
3 clear
4 printf(" Decimal subtraction in 8-4-2-1 BCD using
      9's complement method")
5 printf("\n\n    79-26 = 53 =")
6 //given decimal number
7 x=79;
8 y=26;
9 //we separate each of the digit in the decimal
   number
10 x1=7;    x2=9;
11 y1=2;    y2=6;
12 //first we take 9's complement of the second number
13 // ie 2 and 6
14 y1=9-y1        //9's complement of y1
15 y2=9-y2        //9's complement of y2
16

```

```

17 //then we add each of the digit of the number
    together
18 //ie x1+y1 and x2+y2
19 z1=x1+y1;      z2=x2+y2;
20 //if z2>9(=1001 in binary) then we should add
21 //6(=0110 in binary) to z2 and add the carry to z1
22 if (z2>9) then
23     z2=z2+6;
24     m=bitget(z2,5)
25 if (m==1) then
26     z1=z1+m
27     z2=bitset(z2,5,0)
28 end
29 end
30
31 //again if z1>9(=1001 in binary) then we should add
    the
32 //6(=0110 in binary) to z1 and add the carry to z2
33
34 if (z1>9) then
35     z1=z1+6;
36     m=bitget(z1,5)
37 if (m==1) then
38     z2=z2+m
39     z1=bitset(z1,5,0)
40 end
41 end
42 //decimal to binary conversion
43 z3=dec2bin(z1)
44 z4=dec2bin(z2)
45
46 printf(" 0%s 00%s ",z3,z4)
47
48 printf("\n\n    89-54 = 35 =")
49 //given decimal number
50 x=89;
51 y=54;
52 //we separate each of the digit in the decimal

```

```

        number
53 x1=8;      x2=9;
54 y1=5;      y2=4;
55 // first we take 9's complement of the second number
56 // ie 2 and 6
57 y1=9-y1          // 9's complement of y1
58 y2=9-y2          // 9's complement of y2
59
60 // then we add each of the digit of the number
   together
61 // ie x1+y1 and x2+y2
62 z1=x1+y1;      z2=x2+y2;
63 // if z2>9(=1001 in binary) then we should add
64 // 6(=0110 in binary) to z2 and add the carry to z1
65 if (z2>9) then
66     z2=z2+6;
67     m=bitget(z2,5)
68 if (m==1) then
69     z1=z1+m
70     z2=bitset(z2,5,0)
71 end
72 end
73
74 // again if z1>9(=1001 in binary) then we should add
   the
75 // 6(=0110 in binary) to z1 and add the carry to z2
76
77 if (z1>9) then
78     z1=z1+6;
79     m=bitget(z1,5)
80 if (m==1) then
81     z2=z2+m
82     z1=bitset(z1,5,0)
83 end
84 end
85 // decimal to binary conversion
86 z3=dec2bin(z1)
87 z4=dec2bin(z2)

```

88

89 **printf**(” 00%s 0%s ” ,z3 ,z4)

Chapter 14

Digital Logic

Scilab code Exa 14.1 Representation of the given boolean expression

```
1 //EX14_1 Pg-14.25
2 clc
3 clear
4 printf("    (((A+B)C) '')D")
5 printf("\n      Given inputs are A,B,C and D")
6 printf("\n\n      (A+B)C then we take the complement "
)
7 printf("\n      ((A+B)C) ''")
8 printf("\n      Then we AND together with D")
9 printf("\n      Therefore Y = (((A+B)C) '')D")
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 14.2 Implementation of EXNOR gate using NAND gate

```
1 //example 14.2 PG-14.27//
2 clc
```

```
3 clear
4 printf(" Implementation of EX-OR gate using NAND
      gate")
5 printf("\n      Refer to the figure -14.45(a) shown"
      )
6 printf("\n      The Boolean expression for EX-OR gate
      is Y=AB' +A'B")
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 14.3 Implementation of EXNOR gate using NOR gate

```
1 //example 14.3 PG-14.27//
2 clc
3 clear
4 printf(" Implementation of EX-NOR gate using NOR
      gate")
5 printf("\n      Refer to the figure -14.46(a) shown"
      )
6 printf("\n      The Boolean expression for EX-NOR
      gate is Y=AB+A'B' ")
7 printf("\n      Y=(AB'+A'B)' \n      Y= (AB')'.(A
      ,B)' ")
8 printf("\n      Y=(A'+B).( A+B' )")
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 14.4 Boolean Solutions

```
1 //example 14.4 PG-14.38
2 clc
```

```
3 clear
4 printf(" given=> A.A' 'C = 0.C..... Since A.A''=0\
n\n")
5 printf(" A.A' 'C = 0 ..... Since A.0=0")
```

Scilab code Exa 14.5 Boolean Solutions

```
1 //example 14.5 PG-14.38
2 clc
3 clear
4 printf(" Given=> ABCD+ABD = ABD(C+1) .....
Distributive property\n\n")
5 printf(" ABCD+ABD = ABD.1 ..... Since A
+1=1\n\n")
6 printf(" ABCD+ABD = ABD ..... Since A
.1=A")
```

Scilab code Exa 14.6 Boolean Solutions

```
1 //example 14.6 PG-14.38
2 clc
3 clear
4 printf(" Given=> ABCD+AB' 'CD = ACD(B+B' ') .....
Distributive property\n\n")
5 printf(" ABCD+AB' 'CD = ACD.1 ..... ...
Since A+A''=1\n\n")
6 printf(" ABCD+AB' 'CD = ACD ..... ...
Since A.1=A")
```

Scilab code Exa 14.7 Boolean Solutions

```

1 //example 14.7 PG-14.38
2 clc
3 clear
4 printf(" Given=> A(A+B) = AA+AB . . . .
          Distributive property\n\n")
5 printf("           A(A+B) = A+AB . . . . . Since A.A=
          A\n\n")
6 printf("           A(A+B) = A(1+B) . . . .
          Distributive property\n\n")
7 printf("           A(A+B) = A . . . . . . . Since A
          +1=1\n\n")

```

Scilab code Exa 14.8 Boolean Solutions

```

1 //example 14.8 PG-14.38
2 clc
3 clear
4 printf(" Given=> AB+ABC+AB(D+E) = AB(1+C+D+E)
          . . . . Distributive property\n\n")
5 printf("           AB+ABC+AB(D+E) = AB
          . . . . . Since A+1=1\n\n")

```

Scilab code Exa 14.9 Boolean Solutions

```

1 //example 14.9 PG-14.38
2 clc
3 clear
4 printf(" Given=> XY+XYZ+XYZ''+X''YZ = XY(1+Z)+XYZ''+X
          ''YZ . . . . Distributive property\n\n")
5 printf("           XY+XYZ+XYZ''+X''YZ = XY+XYZ'' + X
          ''YZ . . . . . Since A+1=1\n\n")
6 printf("           XY+XYZ+XYZ''+X''YZ = XY(1+Z'') + X
          ''YZ \n\n")

```

```

7 printf("          XY+XYZ+XYZ' +X' YZ = XY + X' YZ
           ..... Since A+1=1\n\n")
8 printf("          XY+XYZ+XYZ' +X' YZ = Y(X+X' Z)      \
           n\n")
9 printf("          XY+XYZ+XYZ' +X' YZ = Y(X+Z)
           ..... Since A+A' B=A+B" )

```

Scilab code Exa 14.10 Boolean Solutions

```

1 //example 14.10 PG-14.39
2 clc
3 clear
4 printf("Given=> A' B' C' +A' BC' +A' BC = A' C' (B
         ''+B)+A' BC ..... Distributive property")
5 printf("\n\n          A' B' C' +A' BC' +A' BC = A' C
         ''+ A' BC ..... Since A+A'=1\n\n")
6 printf("          A' B' C' +A' BC' +A' BC = A' (C' +
         BC) ..... Distributive property")
7 printf("\n\n          A' B' C' +A' BC' +A' BC = A' (C
         ''+B) ..... Since A+A' B=A+B" )

```

Scilab code Exa 14.11 Boolean Solutions

```

1 //example 14.11 PG-14.39
2 clc
3 clear
4 printf("      Given=> LHS = ABC+AB' C+ABC' \n\n")
5 printf("                  = AC(B+B' ) + ABC' ,
         ..... Distributive property\n\n")
6 printf("                  = AC.1 + ABC' ,
         ..... Since A+A'=1\n\n")
7 printf("                  = AC + ABC' ,
         ..... Since A.1=1\n\n")

```

```

8 printf(" = A(C+BC' ')
..... Distributive property\n\n")
9 printf(" = A(C+B)
..... Since A+A' B=A+B\n\n")
10 printf("Therefore \n")
11 printf(" ABC+AB' C+ABC' = A(C+B)" )

```

Scilab code Exa 14.12 Boolean Solutions

```

1 //example 14.12 PG-14.39
2 clc
3 clear
4 printf(" Given=> \n")
5 printf(" A' BCD' + BCD' + BC' D' + BC' D\n\
n")
6 printf(" = BCD' (A' +1)+ BC' D' + BC' '
D ..... Distributive property\n\n")
7 printf(" = BCD' + BC' D' + BC' D
..... Since A+1=1\n\n")
8 printf(" = BD' (C+C') + BC' D
..... Distributive property\n\n")
9 printf(" = BD' + BC' D
..... Since A+A'=1\n\n")
10 printf(" = B(D' +C' D)
..... Distributive property\n\n")
11 printf(" = B(D' +C')
..... Since A+A' B=A+B\n\n")
12 printf("Therefore \n")
13 printf(" A' BCD' + BCD' + BC' D' + BC' D =
B(D' +C' )")

```

Scilab code Exa 14.13 Boolean Solutions

```

1 //example 14.13 PG-14.39
2 clc
3 clear
4 printf(" Given=> \n")
5 printf(" AC+C(A+A' )B = ")
6 printf("AC+AC+A' BC ..... Distributive property
    \n\n")
7 printf(" = AC + A' BC
    ..... Since A+A=A\n\n")
8 printf(" = C(A+A' )B
    ..... Distributive property\n\n")
9 printf(" = C(A+B)
    ..... Since A+A' B=A+B\n\n")
10 printf(" Therefore \n")
11 printf(" AC+C(A+A' )B = C(A+B) ")

```

Scilab code Exa 14.14 Boolean Solutions

```

1 //example 14.14 PG-14.39
2 clc
3 clear
4 printf("\n\n Given=> \n\n")
5 printf(" A' BC' D + A' BCD + ABD = ")
6 printf("A' BD(C'+C)+ ABD ..... Distributive
    property\n\n")
7 printf(" = A' BD + ABD
    ..... Since A+A=A\n\n")
8 printf(" = BD(A' +A)
    ..... Distributive property\n\n")
9 printf(" = BD
    ..... Since A+A'=1\n\n")
10 printf(" Therefore \n\n")
11 printf(" A' BC' D + A' BCD + ABD = BD" )

```

Scilab code Exa 14.15 Boolean Solutions

```
1 //example 14.15 PG-14.39
2 clc
3 clear
4 printf("\n\n Given=> \n")
5 printf("      LHS = A + A' B + AB' \n\n")
6 printf("      = (A + A' B) + AB' \n\n")
7 printf("      = A + B + AB' ..... Since A+
     A' B=A+B\n\n")
8 printf("      = A + A + B ..... Since A+A
     'B=A+B\n\n")
9 printf("      = A + B ..... Since A+A
     =A\n\n")
10 printf(" Therefore \n\n")
11 printf("      A + A' B + AB' = A + B")
```

Scilab code Exa 14.16 Boolean Solutions

```
1 //example 14.16 PG-14.40
2 clc
3 clear
4 printf("\n\n Given=> \n\n")
5 printf("      ((AB) ''+A''+AB) '' = ")
6 printf(" (A''+ B''+ A''+ AB) '' ..... Since (AB) ''=
     A''+B''\n\n")
7 printf("      = (A''+ B''+ A''+ B)
     '' ..... Since A+A' B=A+B\n\n")
8 printf("      = (A''+ B''+ B) ''
     ..... Since A+A=A\n\n")
9 printf("      = (A''+ 1) ''
     ..... Since A+A'=1\n\n")
```

```

10 printf(" = 1 ,  

..... Since A+1=1\n\n")
11 printf(" = 0 \n\n")
12 printf(" Therefore \n\n")
13 printf(" (A' B' +A' +AB) , = 0")

```

Scilab code Exa 14.17 Boolean Solutions

```

1 //example 14.17 PG-14.40
2 clc
3 clear
4 printf("\n\n Given=> \n\n")
5 printf(" AB+(AC) ''+AB' 'C(AB+C) = ")
6 printf("AB+ (AC) ''+AAB' 'BC+AB' 'CC .....
      Distributive property\n\n")
7 printf(" = AB+ (AC) ''+ AB' 'CC
..... Since A.A''=0\n\n")
8 printf(" = AB+ (AC) ''+ AB' 'C
..... Since A.A=A\n\n")
9 printf(" = AB+ A''+ C''+ AB' 'C
..... Since (AB) ''=A''+B' '\n\n")
10 printf(" = A''+ B+C''+ AB' 'C
..... Since A+A' 'B=A+B\n\n")
11 printf(" = A''+ AB' 'C + B+C' ,
..... Commutative property")
12 printf("\n\n = A''+ B' 'C + B+C
, ..... Since A+A' 'B=A+B")
13 printf("\n
      Where B=B' 'C\n\n")
14 printf(" = A''+ B+C''+ B' 'C
..... Commutative property")
15 printf("\n\n = A''+ B+C' 'B' ,
..... Since A+A' 'B=A+B")
16 printf("\n\n = A''+C' '+1

```

```

    ..... Since  $A+A' = 1$ \n")
17 printf(" = 1
    ..... Since  $A+1=1$ \n")
18 printf(" Therefore \n")
19 printf("  $AB+(AC)' + AB'C(AB+C) = 1$ ")

```

Scilab code Exa 14.18 Boolean Solutions

```

1 //example 14.18 PG-14.40
2 clc
3 clear
4 printf(" Refer to the Figure -14.50 shown\n\n")
5 printf(" The Boolean expression for the output Y
       is :\n\n")
6 printf("  $Y = (A' + B')' . BC$ \n\n")
7 printf("  $Y = ((AB)')$ ' . BC .... Since  $A' + B'$ 
       ' =  $(AB)'$  and  $(A')$ ' =  $A$ \n")
8 printf(" DeMorgan 's
       Therem\n\n")
9 printf("  $Y = A . B . B . C$  .... Since  $A . A = A$ \n")
10 printf("  $Y = ABC$ \n\n")
11 printf(" Truth Table\n")
12 printf(" A      B      C      Y")
13 a=zeros(1,4)
14 b=[0 0 1 0;0 1 0 0;0 1 1 0;1 0 0 0;1 0 1 0;1 1 0 0]
15 c=ones(1,4)
16 d=[a;b;c]
17 disp(d)

```

Scilab code Exa 14.19 construction of the given logic circuit using AND OR and INV

```

1 //example 14.19 PG-41

```

```

2 clc
3 clear
4 printf("a) Given =>\n")
5 printf("Y = (AB(C+D)) ,'\n\n")
6 printf("b) Given =>\n")
7 printf("Z = (W+PQ' ) ,'"')

```

This code can be downloaded from the website www.scilab.in This code
can be downloaded from the website www.scilab.in

Scilab code Exa 14.20 truth table of the given logic expression

```

1 //example 14.20 PG-14.41
2 clc
3 clear
4 printf("Refer to the Figure -14.52 shown\n\n")
5 printf("From the Figure we can see that\n\n")
6 printf("Y = ((A+B) ' .(B+C' ) ') ,'\n\n")
7 printf("Y = (A+B) ' ' '+ (B+C' ) ' ' ,'\n\n' .... Since
(A.B) ' ' = A' ' + B' '\n\n")
8 printf("DeMorgan ' ' s
Therem \n")
9 printf("where A=A+B
and B=B+C' ,\n\n")
10 printf("Y = A+B+B+C' ,\n\n' .... Since (A
') ' ' = A\n\n")
11 printf("Y = A+B+C' ,\n\n' .... Since A+A=
A\n\n")
12 printf("Truth Table\n")
13 printf("A B C Y\n")
14 a=[0 0 0 1;0 0 1 0;0 1 0 1;0 1 1 1;1 0 0 1;1 0 1 1;1
1 0 1]

```

```

15 b=ones(1,4)
16 c=[a;b]
17 disp(c)
```

Scilab code Exa 14.21 simplification of the given logic expression

```

1 //example 14.21 PG-14.42
2 clc
3 clear
4 printf("\n\n Given=> \n\n")
5 printf("      Y = (A+B)(A' +C)(B' +C' ) \n\n")
6 printf("      Y = (AA' + AC +A' B + BC)(B' +C' ) \n\n")
7 printf("      Y = (AC +A' B + BC)(B' +C' ) .....
           Since A.A' = 0\n\n")
8 printf("      Y = AB' C + ACC' + A' BB' + A' BC' + BB
           'C+ BC'\n\n")
9 printf("      Y = AB' C + A' BC' ,      Since A.A' = 0"
           )
```

Scilab code Exa 14.22 simplification of the given logic expression using Demorgans

```

1 //example 14.22 PG-14.41
2 clc
3 clear
4 printf("\n    a) Given=> \n\n")
5 printf("      ((A+B') .(A' +B))' = (A+B')' +(A' +B)'
           .... Since (AB)' = A' +B' \n")
6 printf("      DeMorgan ' s Therem\n\n")
7 printf("          = A' .B' +A' .B'
           .... Since A' +B' =(AB)' \n")
```

```

8 printf("DeMorgan ' s Therem\n\n")
9 printf("= A' '.B + A.B' ,
       .... Since (A' ') ''=A\nn")
10 printf("Therefore \n")
11 printf("((A+B'').(A' '+B))'' = A' '.B + A.B' ")
12
13 printf("\n\n b) Given=> \n\n")
14 printf("(((A.B) '')C) ''D) '' = ((AB) '')C) '''+D' ,
       .... Since (AB) ''= A' '+B' '\n")
15 printf("DeMorgan ' s Therem\n\n")
16 printf("= (AB) '''.C + D' ,
       .... Since (A' '') ''=A\nn")
17 printf("= (A' '+B' ')C + D' ,
       .... Since (AB) ''=A' '+ B' '\n")
18 printf("DeMorgan ' s Therem\n\n")
19 printf("Therefore \n")
20 printf("(((A.B) '')C) ''D) '' = (A' '+B' ')C + D' , ")

```
