

Scilab Textbook Companion for  
Electronic Devices and Circuits  
by I. J. Nagrath<sup>1</sup>

Created by  
Ashutosh Kumar  
B.Tech.  
Computer Engineering  
Dr. A.P.J. Abdul Kalam Technical University  
College Teacher  
None  
Cross-Checked by  
Chaitanya

July 30, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Electronic Devices and Circuits

**Author:** I. J. Nagrath

**Publisher:** Prentice-hall Of India Pvt.ltd

**Edition:** 1

**Year:** 2007

**ISBN:** 9788120331952

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 SEMICONDUCTORS DIODE AND DIODE CIRCUITS	5
2 TRANSISTORS AND OTHER DEVICES	32
3 SMALL SIGNAL MODELS AMPLIFICATION AND BI-ASING	42
4 SMALL SIGNAL AMPLIFIERS FREQUENCY RESPONSE	71
5 Large Signals Amplifiers	97
6 Feedback Amplifiers And Oscillators	110
7 Operational Amplifiers	119
8 Multivibrators And Switching Regulators	130
9 Integrated Circuit Fabrication	139
10 Circuit Theory	142
11 Cathode Ray Oscilloscope	149

# List of Scilab Codes

Exa 1.1	Example . . . . .	5
Exa 1.2	Example . . . . .	6
Exa 1.3	Example . . . . .	6
Exa 1.4	Example . . . . .	7
Exa 1.5	Example . . . . .	8
Exa 1.6	Example . . . . .	8
Exa 1.7	Example . . . . .	9
Exa 1.9	Example . . . . .	10
Exa 1.11	Example . . . . .	11
Exa 1.12	Example . . . . .	11
Exa 1.13	Example . . . . .	12
Exa 1.14	Example . . . . .	13
Exa 1.15	Example . . . . .	14
Exa 1.16	Example . . . . .	15
Exa 1.17	Example . . . . .	17
Exa 1.18	Example . . . . .	17
Exa 1.19	Example . . . . .	18
Exa 1.20	Example . . . . .	19
Exa 1.24	Example . . . . .	20
Exa 1.25	Example . . . . .	20
Exa 1.26	Example . . . . .	22
Exa 1.27	Example . . . . .	23
Exa 1.28	Example . . . . .	23
Exa 1.29	Example . . . . .	25
Exa 1.30	Example . . . . .	27
Exa 1.32	Example . . . . .	27
Exa 1.33	Example . . . . .	28
Exa 1.34	Example . . . . .	29

Exa 1.35	Example . . . . .	30
Exa 1.36	Example . . . . .	31
Exa 2.1	Example . . . . .	32
Exa 2.2	Example . . . . .	33
Exa 2.3	Example . . . . .	34
Exa 2.4	Example . . . . .	34
Exa 2.5	Example . . . . .	35
Exa 2.7	Example . . . . .	36
Exa 2.8	Example . . . . .	36
Exa 2.10	Example . . . . .	37
Exa 2.13	Example . . . . .	38
Exa 2.14	Example . . . . .	38
Exa 2.15	Example . . . . .	39
Exa 2.16	Example . . . . .	40
Exa 3.1	Example . . . . .	42
Exa 3.2	Example . . . . .	43
Exa 3.3	Example . . . . .	43
Exa 3.4	Example . . . . .	44
Exa 3.5	Example . . . . .	45
Exa 3.6	Example . . . . .	45
Exa 3.7	Example . . . . .	46
Exa 3.8	Example . . . . .	47
Exa 3.9	Example . . . . .	48
Exa 3.10	Example . . . . .	49
Exa 3.11	Example . . . . .	51
Exa 3.12	Example . . . . .	51
Exa 3.13	Example . . . . .	52
Exa 3.14	Example . . . . .	53
Exa 3.15	Example . . . . .	55
Exa 3.16	Example . . . . .	55
Exa 3.17	Example . . . . .	56
Exa 3.18	Example . . . . .	58
Exa 3.19	Example . . . . .	59
Exa 3.20	Example . . . . .	60
Exa 3.21	Example . . . . .	61
Exa 3.22	Example . . . . .	62
Exa 3.23	Example . . . . .	64
Exa 3.24	Example . . . . .	64

Exa 3.25	Example . . . . .	65
Exa 3.26	Example . . . . .	66
Exa 3.28	Example . . . . .	67
Exa 3.29	Example . . . . .	68
Exa 3.30	Example . . . . .	69
Exa 3.31	Example . . . . .	70
Exa 4.1	Example . . . . .	71
Exa 4.2	Example . . . . .	72
Exa 4.3	Example . . . . .	72
Exa 4.4	Example . . . . .	73
Exa 4.5	Example . . . . .	74
Exa 4.6	Example . . . . .	75
Exa 4.7	Example . . . . .	76
Exa 4.8	Example . . . . .	77
Exa 4.9	Example . . . . .	78
Exa 4.10	Example . . . . .	80
Exa 4.11	Example . . . . .	82
Exa 4.12	Example . . . . .	83
Exa 4.13	Example . . . . .	83
Exa 4.14	Example . . . . .	84
Exa 4.15	Example . . . . .	85
Exa 4.16	Example . . . . .	87
Exa 4.17	Example . . . . .	88
Exa 4.18	Example . . . . .	89
Exa 4.19	Example . . . . .	91
Exa 4.21	Example . . . . .	93
Exa 4.23	Example . . . . .	95
Exa 5.1	Example . . . . .	97
Exa 5.2	Example . . . . .	98
Exa 5.3	Example . . . . .	99
Exa 5.4	Example . . . . .	100
Exa 5.5	Example . . . . .	101
Exa 5.6	Example . . . . .	102
Exa 5.7	Example . . . . .	104
Exa 5.8	Example . . . . .	105
Exa 5.9	Example . . . . .	106
Exa 5.10	Example . . . . .	107
Exa 5.12	Example . . . . .	108

Exa 5.13	Example . . . . .	109
Exa 6.1	Example . . . . .	110
Exa 6.2	Example . . . . .	111
Exa 6.3	Example . . . . .	111
Exa 6.4	Example . . . . .	112
Exa 6.5	Example . . . . .	112
Exa 6.7	Example . . . . .	113
Exa 6.8	Example . . . . .	114
Exa 6.9	Example . . . . .	115
Exa 6.10	Example . . . . .	116
Exa 6.11	Example . . . . .	117
Exa 6.12	Example . . . . .	117
Exa 6.13	Example . . . . .	118
Exa 7.1	Example . . . . .	119
Exa 7.2	Example . . . . .	120
Exa 7.3	Example . . . . .	120
Exa 7.4	Example . . . . .	121
Exa 7.6	Example . . . . .	121
Exa 7.7	Example . . . . .	122
Exa 7.8	Example . . . . .	123
Exa 7.9	Example . . . . .	124
Exa 7.10	Example . . . . .	124
Exa 7.11	Example . . . . .	125
Exa 7.14	Example . . . . .	126
Exa 7.21	Example . . . . .	127
Exa 7.22	Example . . . . .	127
Exa 7.23	Example . . . . .	128
Exa 8.1	Example . . . . .	130
Exa 8.2	Example . . . . .	131
Exa 8.3	Example . . . . .	132
Exa 8.4	Example . . . . .	133
Exa 8.5	Example . . . . .	134
Exa 8.6	Example . . . . .	135
Exa 8.7	Example . . . . .	136
Exa 8.8	Example . . . . .	137
Exa 9.2	Example . . . . .	139
Exa 9.3	Example . . . . .	140
Exa 9.4	Example . . . . .	140

Exa 9.5	Example . . . . .	141
Exa 10.1	Example . . . . .	142
Exa 10.2	Example . . . . .	142
Exa 10.3	Example . . . . .	143
Exa 10.4	Example . . . . .	144
Exa 10.5	Example . . . . .	144
Exa 10.6	Example . . . . .	145
Exa 10.7	Example . . . . .	145
Exa 10.9	Example . . . . .	146
Exa 10.10	Example . . . . .	147
Exa 10.11	Example . . . . .	148
Exa 11.2	Example . . . . .	149
Exa 11.3	Example . . . . .	150
Exa 11.4	Example . . . . .	151

# Chapter 1

## SEMICONDUCTORS DIODE AND DIODE CIRCUITS

Scilab code Exa 1.1 Example

```
1 //Variable declaration
2 A=6.022*10**23 //avagadro's number(/m^3)
3 d=2.7*10**6 //density of aluminium conductor(
  g/m^3)
4 a=26.98 // atomic weight aluminium
  conductor(g/g-atom)
5 D=10**4. //current density(A/m^2)
6 e=1.6*10**-19 //electronic charge(C)
7
8 //Calculations
9 //Part a
10 n=A*d/a //number of atoms(n/m^3)
11
12 //Part b
13 u=D/(n*e) //drift velocity (m/s)
14
15 //Results
16 printf ("number of atoms per cubic meter is %.3f *
  10**28/m^3",n/10**28)
```

```
17 printf ( " drift velocity is %.2e m/s",u)
```

---

### Scilab code Exa 1.2 Example

```
1 //Variable declaration
2 n=10**23 //number of electrons(n/m^3)
3 e=1.6*10**-19 //electronic charge(C)
4 u=0.4 //mobility(m^2/Vs)
5 a=10**-7 //cross sectional area(m^2)
6 l=15*10**-2 //conductor length(m)
7
8 //Calculations
9 //Part a
10 G=n*e*u //conductivity(S/m)
11
12 //Part b
13 R=1/(a*G) //resistance(ohm)
14
15 //Results
16 printf ("conductivity of the conductor is %.1e S/m",
17 G)
17 printf ("resistance of the conductor is %.1f ohm",R)
```

---

### Scilab code Exa 1.3 Example

```
1 //Variable declaration
2 A=6.022*10**23 //avagadro's number
3 d=5.32*10**6 //density of Ge at 300k(g/m^3)
4 a=72.60 //atomic weight of Ge(g/g-atom)
5 e=1.6*10**-19 //electronic charge(C)
6 ni=2.4*10**19 //intrinsic concentration(electron-
7 hole pairs/m^3)
7 un=0.39 //electron mobility(m^2/V.s)
```

```

8 up=0.19          //hole mobility(m^2/V.s)
9
10 //Calculations
11 //Part a
12 nA=A*d/a        //number of atoms(nA/m^3) using
    avagadro's law
13 x=nA/ni         //Germanium atoms/electron hole
    pair
14
15 //Part b
16 g=(un+up)*e*ni  //intrinsic conductivity(S/m)
17 r=1/g           //intrinsic resistivity(ohm.m)
18
19 //Results
20 printf("the relative concentration of Ge and
    electron hole pairs is %.2e atoms/electron-hole
    pair",x)
21 printf("the intrinsic resistivity of Ge is %.3f ohm
    .m",r)

```

---

#### Scilab code Exa 1.4 Example

```

1 //Variable declaration
2 ni=1.5*10**16    //intrinsic concentration(electron-
    hole pairs/m^3)
3 n=4.99*10**28   //number of Si atoms(atoms/m^3)
4 un=0.13         //electron mobility(m^2/V.s)
5 up=0.05         //hole mobility(m^2/V.s)
6 e=1.6*10**-19  //electronic charge(c)
7
8 //Calculation
9 //Part a
10 g=e*ni*(un+up) //intrinsic conductivity(S/m)
11 r=1/g           //intrinsic resistivity(ohm.m)
12 Nd=n/10**8     //doped silicon(atoms/m^3)=nn,

```

```

    majority carriers
13 pn=ni**2/Nd      //minority carrier density(holes/m
    ^3)
14
15 //Part b
16 k=e*un*Nd      //conductivity(S/m)
17                //using Nd in place of nn as Nd=nn
18 rho=1/k        //resistivity(ohm.m)
19
20 //Results
21 printf("the minority carrier density of Si is %.2e
    holes/m^3 ",pn)
22 printf("the resistivity of Si is %.2e ohm.m",rho)

```

---

#### Scilab code Exa 1.5 Example

```

1
2
3 //Variable declaration
4 Vo=0.7          //contact potential(V)
5 Vf=0.4          //forward biasing voltage(V)
6
7 //Calculation
8 x=exp(-20*(Vo-Vf))/exp(-20*Vo) //increase in
    probability of majority carriers
9
10 //Result
11 printf("increase in probability of majority
    carriers is %.f times",x)

```

---

#### Scilab code Exa 1.6 Example

```

1

```

```

2
3 //Variable declaration
4 I=10 //Ge diode carries current (mA)
5 V=0.2 //forward bias voltage (V)
6
7 //Calculation
8 //Part a
9 Is=I/(exp(40*V)-1) //reverse current (mA)
10
11 //part b
12 I1=1*10**3
13 V1=(log(1/3.355*10**3 + 1))/40 //voltage (V)
14 I2=100*10**-3 //current (mA)
15 V2=(log(100/3.355*10**3+1))/40 //voltage (V)
16
17 //Part c
18 Is1=4*Is //reverse saturation
//current doubles for every 10 degree celcius temp
//rise ,so for 20 degree rise it will be 4 timese/
19 x=37.44 //let x=e/kT
20 I3=Is1*(exp(x*V)) //current when temp doubles (mA)
21
22 //Results
23 printf ("the reverse current is %.3f mA",Is/1e-3)
//incorrect units given in the textbook
24 printf ("bias voltages are %.3f V and %.3f V resp",
V1,V2)
25 printf ("Is at 20 degree is %.2f uA and diode
current at 0.2 V is %.2f mA",Is1/1e-3,I3)

```

---

### Scilab code Exa 1.7 Example

```

1 //Variable declaration
2 V=3. //Voltage (V)
3 Req=300. //total resistance as per circuit(

```

```

    ohm)
4 Rfa=20           //forward resistance(ohm)
5 Vt=0.7          //Thevinine's voltage(V)
6 Rfb=0           //forward resistance(ohm)
7
8 //Calculations
9 //Part a
10 I=V/Req        //current(A)
11
12 //Part b
13 Id=(V-Vt)/Req  //diode current(mA)
14
15 //Part c
16 Rf=20          //forward resistance(ohms)
17 Id1=(V-Vt)/(Req+Rfa) //diode current(mA)
18
19 //Results
20 printf("current in this case is %.2f A",I)
21 printf("diode current is %.2f mA",(Id/1E-3))
22 printf("diode current is %.2f mA" ,(Id1/1E-3))

```

---

#### Scilab code Exa 1.9 Example

```

1 //Variable declaration
2 Vx=1.4          //voltage at point X(V)
3 Vt=0.7          //diode voltage(V)
4 Vcc=5           //cathode voltage(V)
5 R=1             //circuit resistance(ohm)
6 Vs=Vx-Vt       //supply voltage(V)
7
8 //Calculations
9 I1=(Vcc-Vt-Vs)/R //current through D1(mA) for 0<
    Vs<0.7
10 I2=0           //current through D2 and D3
11 I1=(Vcc-Vt-Vs)/R //for Vs>0.7 as D2 and D3

```

```

    conducts
12
13 //Results
14 printf (" I1 for 0<Vs<0.7 is %.1f mA" ,I1)
15 printf (" I2 for 0<Vs<0.7 is %.1f mA" ,I2)
16 printf (" I1 and I2 for Vs>0.7 is %.1f mA" ,I1)

```

---

### Scilab code Exa 1.11 Example

```

1 //Variable declaration
2 Vz=100           //zener voltage(V)
3 Rz=25           //diode resistance(ohm)
4 I1=0.05         //load current(A)
5 Iz=0.01         //zener diode current(A)
6 Rs=250          //supply resistance(ohm)
7
8 //Calculations
9 V1=Vz+(Iz*Rz)   //load voltage(V)
10 Vs=V1+(I1+Iz)*Rs //supply voltage(V)
11 VL=V1*1.01     //increase in V1(V)
12 IZ=(VL-Vz)/Rz  //increase in zener current
13 VS=V1+(I1+IZ)*Rs //increase in supply voltage(V)
14 Vss=(VS-Vs)/Vs //%increase in supply voltage(V)
15 P=I1*VL        //power consumed(W)
16
17 //Results
18 printf ("load voltage is %.2f V" ,V1)
19 printf ("supply voltage is %.2f V" ,Vs)
20 printf ("increase in supply voltage is %.3f V" ,VS)
21 printf ("power consumed is %.2f W" ,P)

```

---

### Scilab code Exa 1.12 Example

```

1 //Variable declaration
2 Vbb=5           //bias voltage(V)
3 Rl=1           //resistance(ohm)
4 Id=4.4         //from the figure(mA)
5
6 //Part a
7 i=Vbb/Rl       //load line intercepts the Id axis
   at i(mA)
8 Vl=Id*Rl       //load voltage(V)
9
10 //Part b
11 Vd=Vbb-Vl     //diode voltage(V)
12 P=Vd*Id       //power absorbed in diode(mW)
13
14 //Part c
15 Ida=1.42      //diode current(mA) for 2V
16 Idb=7.35      //diode current(mA) for 8V
17
18 //Part d
19 Idc=8.7       //diode current(mA) for Rl=0.5k ohm
20 Idl=2.2       //diode current(mA) for Rl=2k ohm
21
22 //Results
23 printf ("diode current is %.1f mA and voltage across
   the load is %.1f V", Id,Vl)
24 printf ("power absorbed in diode is %.2f mW",P)
25 printf ("diode current for Vbb=2V is %.2f mA and for
   Vbb=8V is %.2f mA",Ida,Idb)
26 printf ("diode current for Rl=0.5 kohm is %.1f mA
   and for Rl=2 kohm is %.1f mA",Idc,Idl)

```

---

### Scilab code Exa 1.13 Example

```

1 //Variable declaration
2 T=300           //temperature(k)

```

```

3 Ig=100*10**-3      // current (mA)
4 Is=1*10**-9       // current (nA)
5 x=0.0259          // x=kT/e
6
7 // Calculations
8 Voc=x*log(Ig/Is+1) // as Voc=kT/e*ln((Ig/Is)+1)
   where ln((Ig/Is)+1)=18.42 after solving
9 Isc=Ig
10
11 // Result
12 printf ("for a solar cell Voc is %.3f V and Isc is %
   . f mA",Voc ,Isc/1E-3)

```

---

#### Scilab code Exa 1.14 Example

```

1
2
3 //Variable declaration
4 Idc=0.1           //dc current(A)
5 Rf=0.5            //forward resistance(ohms)
6 Rl=20             //load resistance(ohm)
7 Rs=1              //secondary resistance of
   transformer(ohm)
8
9 //Calculations
10 //Part a
11 Vdc=Idc*Rl        //dc voltage(V)
12 Vm=(%pi/2)*(Vdc+Idc*(Rs+Rf)) //mean voltage(V)
13 Vrms=Vm/sqrt(2)   //rms value of voltage(V)
   )
14
15 //Part b
16 Pdc=Idc**2*Rl    //dc power supplied
   to the load
17

```

```

18 //Part c
19 PIV=2*Vm //PIV rating for each
    diode(V)
20
21 //Part d
22 Im=(%pi/2)*Idc //peak value of current(mA
    )
23 Irms=Im/sqrt(2) //rms value of current(A)
24 Pac=Irms**2*(Rs+Rf+Rl) //ac power input(W)
25
26 //Part e
27 eta=(Pdc/Pac)*100 //conversion
    efficiency
28
29 //Part f
30 Vr=((Rs+Rf)/Rl)*100 //voltage regulation(V
    )
31
32 //results
33 printf ("rms value of voltage is %.2f V",Vrms)
34 printf ("dc power supplied to load is %.1f W",Pdc)
35 printf ("PIV rating for each diode %.2f V",PIV)
36 printf ("ac input power is %.3f W",Pac)
37 printf ("conversion efficiency %.1f %%",eta)
38 printf ("voltage regulation %.1f %%",Vr)

```

---

### Scilab code Exa 1.15 Example

```

1
2 //Variable declaration
3 Vt=1
4 V1=12
5 Vm=63.63 //peak voltage(V) as
    Vm=sqr root of 2*45
6 Idc=8. //charging current(A)

```

```

7
8 // Calculations
9 // Part a
10 theta1= asind((Vt+Vl)/Vm)
11 theta2=180-theta1
12 //Rl=((2*Vm*cos(theta1))-(2*(%pi-2*theta1)*(Vt+Vl)))/
    /(Idc*%pi)
13 Rl=(2*sqrt(2)*45*cosd(11.8) - (2*(%pi-2*0.206)*(Vt+
    Vl)))/(Idc*%pi)
14
15 function ans = ft(wt)
16     ans =((((sqrt(2)*45*sin(wt))-(Vt+Vl))/Rl)*wt)
    **2)
17 endfunction
18 // Part b
19 integ = intg(theta1,theta2,ft)
20 disp ( integ)
21 Irms = (integ/%pi)**0.5
22 Pl=Irms**2*Rl //power loss in
    resistance (W)
23
24 // Part c
25 P=Vl*Idc //power supplied to
    battery (W)
26
27 // results
28 printf (" Resistance to be added is %.2 f Ohms" ,R1)
29 printf (" power supplied to battery is %.f W" ,P)

```

---

#### Scilab code Exa 1.16 Example

```

1
2
3 // Variable declaration
4 Rf=5 //forward resistance (ohms)

```

```

5 Vo=20 //output voltage(V)
6 Rs=10 //secondary resistance of
   transformer(ohm)
7
8 //Calculations
9 //Part a
10 Idc=0.1 //dc current(A)
11 Vm=Vo*(sqrt(2)) //mean voltage(V)
12 Vdc=(2*Vm/(%pi))-Idc*(Rs+2*Rf) //dc voltage(V)
13
14 //Part b
15 Idc1=0.2 //full load dc current(A)
16 Vdc2=((2*(sqrt(2))*Vo)/(%pi))-Idc1*(Rs+2*Rf) //full
   load dc voltage(V)
17 Rl=Vdc2/Idc1 //load resistance(ohm)
18 x=((2*Rf+Rs)/Rl)*100 //% regulation
19
20 //Part c
21 Idc=0.2 //dc current(A)
22 Im=(%pi)*Idc/2 //peak current(mA)
23 Ilrms=Im/sqrt(2) //rms current(mA)
24 Vlrms=Ilrms*Rl //load rms voltage(V)
25
26 //Part d
27 Vldc=14 //load dc
   voltage(V)
28 Vlacrms=sqrt(Vlrms**2-Vldc**2) //rms value of ac
   component(V)
29
30 //Results
31 printf("dc voltage %.f V",Vdc)
32 printf("regulation is %.2f %%",x)
33 printf("rms value of output voltage at dc load
   current is %.2f V",Vlrms)
34 printf("rms value of ac component of voltage %.2f V
   ",Vlacrms)

```

---

### Scilab code Exa 1.17 Example

```
1 //Variable declaration
2 Vh=60.           //higher output voltage(V)
3 Vl=45.           //lower output voltage(V)
4 fz=50.           //frequency(Hz)
5 Vr=15.           //peak to peak ripple voltage(V)
6 Rl=600.          //resistance(ohms)
7
8 //Calculations
9 Vldc=(Vh+Vl)/2   //avg load dc voltage(V) as voltage
                   drops from 60 to 45
10 Idc=Vldc/Rl     //dc current(A)
11 T=1/fz           //discharging time(ms)
12 C=(Idc*T)/Vr    //linear discharge rate(uF)
13 C1=C*2          //new capacitance(uF)
14
15 Vr1 = (20*120*1000)/(1200*254)
16 Idc1=(Vh-(Vr1/2))/Rl           //dc load current
                                   (mA)
17
18 //Results
19 printf ("value of capacitance is %.f uF",C/1E-6)
20 printf ("Vr1 is %d V" ,Vr1)
21 printf ("dc load current Idc is %.f mA",Idc1/1E-3)
22 printf("Note : Answer may be vary because of
         rounding off error.")
```

---

### Scilab code Exa 1.18 Example

```
1
2
```

```

3 //Variable declaration
4 Vdc=30 //dc voltage(V)
5 V1=220 //source voltage(V)
6 f=50 //frequency(Hz)
7 R1=1000 //load resistance(k
    ohms)
8 Vr = 15
9
10 //Calculations
11 C=100/f*R1 //as Vdc/Vr=100
12 Vm=Vdc+0.01*(30/2) //peak voltage(
    V)
13 V2=Vm/(sqrt(2)) //secondary voltage(V)
14 r=V1/V2 //transformer turn
    ratio
15
16 //Results
17 printf ("capacitor filter is %.f uF",C)
18 printf ("transformer turn ratio is %.2f",r)

```

---

### Scilab code Exa 1.19 Example

```

1
2
3 //Variable declaration
4 Idc=60*10**-3 //dc current(A)
5 Vm=60 //peak volage(V)
6 f=50 //frequency(Hz)
7 C=120*10**-6 //capacitance(F)
8
9 //Calculations
10 //Part a
11 Vrms=Idc/(4*(sqrt(3))*f*C*Vm) //rms voltage(V)
12 Vr=2*(sqrt(3))*Vrms //ripple factor(V)
13

```

```

14 //Part b
15 Vdc=Vm-(Vr/2) //by simplifying
16 Vdc = 57.6 // V
17 //Part c
18 r=(Vrms/Vdc)*100 //ripple factor
19
20 //Results
21 printf ("ripple factor is %.3f Vdc",Vr)
22 printf ("dc voltage is %.1f V",Vdc)
23 printf ("ripple factor %.3f %%",r)

```

---

#### Scilab code Exa 1.20 Example

```

1
2
3 // Calculations
4 //Part a
5 //      200*1.141      4
6 //v1(t)=-----(1- cos628t)
7 //      3.14      3
8 //      200*1.141      800*1.141
9 //v2(t)=----- - ----- cos(628t+<(V2/V1
10 //      3.14      3*3.14
11 //
12 //V2/V1|w=0 =0.8;V2/V1|w=628 =6.43*10^-4 <V2/V1|w
13 //      =628 =180
14 //v2(t)=72.02+0.0538 cos628t
15
16 //Part b
17 vrms=0.0538
18 vdc=sqrt(2)*72.02
19 r=vrms/vdc
20

```

```
21 //Results
22 printf ("ripple factor is %.2e",r)
```

---

#### Scilab code Exa 1.24 Example

```
1
2
3 //Variable declaration
4 Vz=2 //zener voltage(V)
5 r1=10 //resistance after reducing
   circuit by thevinin(ohms)
6 r2=20 //resistance after reducing
   circuit by thevinin(ohms)
7 V1=7.5 //voltage after circuit
   reduction(V)
8 V2=15 //voltage after circuit
   reduction(V)
9 Rz=100/3 //zener resistance(ohms)
10
11 //Calculations
12 Vab=V2-(((V2-V1)/(r1+r2))*r2) //thevinin
   voltage at ab(V)
13 Rth=(Vab*r2)/(Vab+r2) //thevinin
   resistance at ab(ohms)
14 Vd=Vab-Vz //diode
   voltage(V)
15 Id=Vd/(Rth+Rz) //diode
   current(A)
16
17 //Results
18 printf ("diode current is %.2 f A",Id)
```

---

#### Scilab code Exa 1.25 Example

```

1 //Variable declaration
2 Vd=0.7 //diode voltage(V)
3 Ro=18 //output resistance(k
   ohms)
4 R1=2 //diode1 resistance(k
   ohms)
5 R2=2 //diode2 resistance(k
   ohms)
6
7 //Calculations
8 //Part a
9 V1=10 //voltage to D1(V)
10 V2=0 //voltage to D2(V)
11 Io=(V1-Vd)/(R1+Ro) //output current(mA)
12 Vo=Io*Ro //output voltage(V)
13
14 //Part b
15 V1=5 //voltage to D1(V)
16 V2=0 //voltage to D2(V)
17 Io=(V1-Vd)/(R1+Ro) //output current(mA)
18 Vo1=Io*Ro //output voltage(V)
19
20 //Part c
21 V1=10 //voltage to D1(V)
22 V2=5 //voltage to D2(V)
23 Vo=8.37 //as D1 only conducts,so,
   Vo is same as in part a
24 Vd1=V2-Vo //assume D1 conducts
25 Vo2=8.37 //D2 does not conduct as
   as Vd1 is negative
26
27 //Part d
28 V1=5 ; V2=5 //voltage to D1 and D2(
   V)
29 Id1=(V1-Vd-Vo)/2 //diode1 current(mA)
30 Io=Vo/Ro //output current(mA)
31 Vo3=(Ro*(V1-Vd))/(Ro+1) //output voltage(V)
32

```

```

33 printf ("a)output voltage is %.2f V",Vo)
34 printf ("b)output voltage is %.2f V",Vo1)
35 printf ("c)output voltage is %.2f V",Vo2)
36 printf ("d)output voltage is %.2f V",Vo3)

```

---

### Scilab code Exa 1.26 Example

```

1 //Variable declaration
2 Vs=10. //supply voltage(V)
3 Rs=1 //supply resistane(ohm)
4 Vl=10. //load voltage(V)
5 Vi=50. //nput voltage(V)
6 Iz=32 //zener diode current(
    mA)
7 Is=40 //supply current(mA)
8
9 //Calculations
10 //Part a (Rl is min when Iz=0)
11 Is=(Vi-Vs)/Rs //source current(mA)
12 Rlmin=Vl/(Vi-Vs) //load resistance
    minimum(ohm)
13
14 //Part b(Rl is maximum when Iz=32 mA)
15 Il=(Is-Iz)*10**-3 //load current(A)
16 Rlmax=Vl/Il //maximum load resistance
    (k ohms)
17 P=Vl*Iz //max diode wattage
    consumed(mW)
18
19 //Results
20 printf ("Range of Rl is %.2f ohm to %.2f k ohm" ,(
    Rlmin/1E-3),(Rlmax/1E+3))
21 printf (" Il = %.e A",Il)
22 printf ("max power consumed is %.f mW",P)

```

---

### Scilab code Exa 1.27 Example

```
1 //Variable declaration
2 Vz=20 //zener voltage(V)
3 Izmax=50 //maximum zener current(mA)
4 Rz=0 //zener resistance(ohms)
5 Rl=2. //load resistance(ohm)
6 Vl=20. //as Vz=Vl(V)
7 Rs=0.25 //source resistance(k ohms)
8
9 //Calculations
10 //Part a
11 I1=Vl/Rl //load current(mA)
12 Vsmin=(Rs+Rl)*I1 //as Iz is floating so Iz=0
13
14 //Part b
15 Is=Izmax+I1 //source current(mA)
16 Vsmax=Vz+(Is*Rs) //maximum source voltage(V)
17
18 //Results
19 printf ("Vsmin %.1f V",Vsmin)
20 printf ("Range of input voltage is %.1f to %.1f V",
    Vsmin, Vsmax)
```

---

### Scilab code Exa 1.28 Example

```
1 //Variable declaration
2 Ilmax=100 //load maximum current(mA)
3 Ilmin=0 //load minimum current(mA)
4 Rz=0.05 //zener diode resistance(
    ohms)
```

```

5  Rs=10.                //source resistance(k ohms
   )
6  Vl=16.015            //load voltage(V)
7  Vl1=16.              //nominal load voltage(V)
8  Vs=20                //source voltage(V)
9  Vz=16                //zener diode voltage(V)
10
11 // Calculations
12 //Case 1 (i)
13 Iz=(Vl-Vl1)/Rz       //zener current(mA)
14 Is=Iz+Iymax          //supply current(A)
15
16 //Case 1 (ii)
17 Is1=(Vs-Vz)/(Rs+Rz)  //supply current(mA)
18 Vl2=Vl1+(Is1*Rz)     //voltage(V)
19 Vr=((Vl2-Vl)/Vl1)*100 //voltage regulation
20
21 //Case 2 (i)
22 Vs=18                //supply voltage(V)
23 Iymax=0.1            //load current max(A)
24 Vl=16.005            //load voltage(V)
25 Iz=(Vl-Vl1)/Rz       //zener current(mA)
26 Is2=Iymax+Iz        //supply current(A)
27
28 //Case 2 (ii)
29 Ixmin=0
30 Iz1=(Vs-Vl1)/(Rs+Rz) //minimum diode current(
   mA)
31 Vl=Vl1+(Iz*Rz)      //load voltage at Ixmin(
   V)
32
33 //Part a
34 //Variable declaration
35 Is=0.4                //supply current(A)
36 Vs=20                //supply voltage(V)
37 Vl=16.015            //load voltage(V)
38 Iz=0.3                //zener current(mA)
39

```

```

40 // Calculations
41 P=Is**2*Rs //power dissipated by Rs(W)
42
43 //Part b
44 Pd=Vl*Iz //power dissipated (W)
45 Po=(Vs**2)/Rs //output power(W)
46
47 printf ("maximum power dissipated by Rs is %.1f W",P
)
48 printf ("maximum power dissipated by diode is %.3f W
",Pd)
49 printf ("minimum diode current is %.3f A",Iz1)
50 printf ("voltage regulation is %.2f %%",Vr)
51 printf ("output shorted will be %.1f W",Po)

```

---

#### Scilab code Exa 1.29 Example

```

1
2
3 //Variable declaration
4 Vrms=20 //secondary voltage(V)
5 Rs=10 //Winding resistance(ohm)
6 Rf=5 //diode has forward
resistance(ohms)
7 Idc=2*10**-3 //load current(mA)
8
9 //Calculations
10 //Part a
11 Vdc=(Vrms*(sqrt(2)))/(%pi) //no load Vdc
12
13 //Part b
14 Vldc=Vdc-(Idc*(Rs+Rf)) //dc
output voltage when load is 20mA
15
16 //Part c

```

```

17 Rl=Vldc/Idc //load
    resistance(ohms)
18 r=((Rs+Rf)/Rl)*100 //
    percentage regulation(%)
19
20 //Part d
21 Im=Idc*(%pi) //peak
    current(mA)
22 Ilrms=Im/2 //rms
    load current(mA)
23 Vlrms=Ilrms*Rl //rms
    load voltage(V)
24 Vlrmsac=sqrt((Vlrms**2)-(Vldc**2)) //Ripple
    voltage rms(V)
25 f=50*2 //rippLe
    frequency(Hz)
26
27 //Part e
28 eta=((2*(%pi)**2)/(1+((Rs+Rf)/Rl)))*100 //
    efficiency
29
30 //Part f
31 PIV=Vrms*(sqrt(2)) //peak
    inverse voltage(V)
32 Vm= PIV
33 //Results
34 printf("no load dc voltage is %.f V",Vdc)
35 printf("dc output voltage when the load is drawing
    20 mA is %.2f V",Vldc)
36 printf("percentage regulation at this load is %.2f
    %%", (r/1E-1))
37 printf("ripple voltage rms is %.2f V and ripple
    frequency is %.f Hz",Vlrmsac,f)
38 printf("power conversion efficiency is %.1f %%", (
    eta/1E+2))
39 printf("PIV is %.f V",PIV)

```

---

### Scilab code Exa 1.30 Example

```
1
2
3 //Variable declaration
4 V1=24 //battery voltage(V)
5 Vm=60*(sqrt(2)) //peak voltage(V)
6 Ip=2.5 //peak current(A)
7 c=20 //charge(Ah)
8
9 //Calculations
10 //Part a
11 theta=asin(V1/Vm) //angle at which conduction
    begins
12 Rs=(Vm-V1)/Ip //source resistance(ohms)
13
14 //Part b
15 Idc=(Vm/(%pi)*Rs)*(cos(theta))-(((%pi)-(2*theta))/2*
    %pi)*(V1/Rs) //load current(A)
16 T=c/Idc
    //time to deliver 20Ah(h)
17
18 //Results
19 printf ("resistance connected in series is %.1f ohm"
    ,Rs)
20 printf ("time required to deliver a charge of 20 Ah
    is %.1f h", (T/1E-3))
21 printf ("Idc %.2f A", (Idc/1E+3))
```

---

### Scilab code Exa 1.32 Example

```

1
2
3 //Variable declaration
4 R=25. //external resistance(ohms)
5 Vm=200. //peak value of voltage(V) as
    vs=200 sinwt
6 Rf=50. //forward resistance(ohms)
7
8 //Calculations
9 //Part a
10 Id=Vm/(2*Rf+R) //diode current(peak)
11
12 //Part b
13 Idc=(2*Id)/%pi //dc current(A)
14
15 //Part c
16 PIV=Vm/2 //peak value of voltage
    across D1
17 PIVac=100/%pi //average value of voltage across
    D1
18
19 //Part d
20 Im=Id //peak value of current(A)
21 Irms=Im/(sqrt(2)) //rms value of current(A)
22
23 //Results
24 printf ("peak value of current is %.1f A",Id)
25 printf ("dc current is %.2f A",Idc)
26 printf ("across D1 are peak voltage is %.1f V and
    average voltage is %.1f V",PIV,PIVac)
27 printf ("Irms is %.2f A",Irms)

```

---

Scilab code Exa 1.33 Example

1

```

2
3 //Variable declaration
4 f=50. //frequency (Hz)
5 dv=7. //difference between maximum and
    minimum(25-18) voltages across the load (V)
6 Ic=100. //load current (mA)
7
8 //Calculations
9 dt=1/(2*f) //time of discharge (seconds)
10 C=Ic/(dv/dt) //capacitance (uF)
11
12 //Results
13 printf ("value of capacitor is %.2 f uF" ,(C/1E-3))

```

---

#### Scilab code Exa 1.34 Example

```

1
2
3 //Variable declaration
4 Vr=10. //peak to peak
    ripple voltage (V)
5 Vm=50. //peak output
    voltage (V)
6 C=300. //Capacitance (uF)
7 Rl=470. //load resistance (
    ohms)
8 f=50. //frequency (Hz)
9
10 //Calculations
11 //Part a
12 Vdc=Vm-(Vr/2) //dc voltage (V)
13 C=Vdc/(f*Vr*Rl) //capacitance (mF)
14
15 //Part b
16 C1=300*10**-6 //capacitance is

```

```

    increased (uF)
17 Vr=2*Vm/((2*f*C1*R1)+1)
18 Vdc=Vm-Vr/2 //load voltage
    ripple (V)
19 Idc=Vdc/R1 //average load
    current (mA)
20
21 //Results
22 printf ("value of capacitor is %.1f mF", (C/1E-6))
23 printf ("load voltage ripple is %.2f V and average
    load current is %.1f mA", Vdc, (Idc/1E-4))

```

---

#### Scilab code Exa 1.35 Example

```

1
2
3 //Variable declaration
4 vo=7.5 //instantaneous voltage (V)
5 R1=15 //resistance (k ohms)
6 Von=0.5 //voltage of diode when on (V
    )
7
8 //Calculations
9 Rth=(R1*vo)/(R1+vo) //equivalent
    resistance (V)
10 T=2*(%pi)/10**4 //time period (ms)
11 t1=(asin(Von/2.5))/10**4 //timings when D1
    conducts (ms)
12 t2=(T/2)-t1
13
14 //Results
15 printf ("time period is %.3f ms", (T/1E-3))
16 printf ("t1 is %.3e ms", t1)
17 printf ("t2 is %.3f ms", (t2/1E-3))

```

---

### Scilab code Exa 1.36 Example

```
1
2
3 //Variable declarations
4 v=12 //output voltage(V)
5 vm=20. //peak voltage(V)
6 v1=8 //output voltage(V) for
    negative half cycle
7 vm1=20. //peak voltage(V) for
    negative half cycle
8
9 //Calculations
10 t1=(asin(v/vm))/10**4 //for positive half
    cycle when D1 conducts
11 t2=(0.1*%pi)-t1/1e-3
12 t3=(asin(v1/vm1))/10**4 //for negative half
    cycle when D2 conducts
13 t4=(0.1*(%pi))+t3/1e-3
14 t5=(0.2*(%pi))-t3/1e-3
15
16 //Results
17 printf ("t1 is %.3 f ms",t1/1e-3)
18 printf ("t2 is %.2 f ms",t2)
19 printf ("t3 is %.3 f ms",t3/1e-3)
20 printf ("t4 is %.3 f ms",t4)
21 printf ("t5 is %.3 f ms",t5)
22 printf ("vo is -5.33+6.66*sin(10**4*.15)")
```

---

## Chapter 2

# TRANSISTORS AND OTHER DEVICES

Scilab code Exa 2.1 Example

```
1 //Variable declaration
2 Rb=200 //base resistance(ohm)
3 Vbe=0.7 //base emitter voltage drop(
    V) in active region
4 Vbb=5 //base voltage of bipolar
    transistor(V)
5 beeta=100 //current gain
6 Rc=3 //collector resistance(k
    ohms)
7 Vcc=10 //voltage given to the
    collector(V)
8
9 //Calculations
10 Ib=(Vbb-Vbe)/Rb //base current(mA)
11 Ic=beeta*Ib //collector current(mA)
12 Vcb=-Vbe-(Rc*Ic)+Vcc //collector base voltage
    drop(V)
13
14 //Results
```

```

15 printf ("Base current Ib = %.4f mA",Ib)
16 printf ("Collector current Ic = %.2f mA",Ic)
17 printf ("Reverse bias collector junction Vcb = %.2f
    V",Vcb)

```

---

### Scilab code Exa 2.2 Example

```

1 //Variable declaration
2 Vbb=5 //base voltage of bipolar
    transistor (V)
3 Vbe=0.7 //base emitter voltage drop (V)
    in active region
4 Rb=150 //base resistance (ohm)
5 beeta=125 //curret gain
6 Rc=3 //collector resistance (k ohms)
7 Vcc=10 //supply voltage (V)
8 Vce=0.2 //collector to emitter voltage (V)
    )
9
10 //Calculations
11 //Part a
12 Ib=(Vbb-Vbe)/Rb //base current (mA)
13 Ic=beeta*Ib //collector current (mA)
14 Vcb=-Vbe-(Rc*Ic)+Vcc //collector base voltage drop (
    V)
15
16 //Part b -for npn transistor
17 Vbe=0.8 //base emitter voltage drop (V)
    in saturation
18 Ic=(Vcc-Vce)/Rc //collector current (mA)
19 Ib=(Vbb-Vbe)/Rb //base current (mA)
20 Ibmin=Ic/beeta //minimum base current (mA) to go
    into saturation (mA)
21
22 //Results

```

```

23 printf ("In active region , base current is %.1e mA
    and collector current is %.2f mA" ,Ib,Ic)
24 printf ("base current and collector current in npn
    are %.2e mA and %.2f mA resp." ,Ib,Ic)
25 printf ("base current minimum is %.3f mA" ,Ibmin)

```

---

### Scilab code Exa 2.3 Example

```

1 //Variable declaration
2 Vbb=5 //base voltage of bipolar
    transistor (V)
3 Vbe=0.7 //base emitter voltage drop (V)
    in active region
4 Rb=50 //base resistance (ohm)
5 beeta=50 //current gain
6 Re=1.8 //emitter resistance (k ohms)
7 Vcc=10 //supply voltage (V)
8 Vce=0.2 //collector to emitter voltage
    (V)
9
10 // Calculations
11 Ib=(Vbb-Vbe)/(Rb+Re*(beeta+1)) //base current (
    mA)
12 Ic=beeta*Ib //collector
    current (mA)
13 Ie=Ib+Ic //emitter
    current (mA)
14
15 // Results
16 printf ("values are Ib: %.2f mA, Ic: %.2f mA and Ie
    : %.2f mA" ,Ib,Ic,Ie)

```

---

### Scilab code Exa 2.4 Example

```

1 //Variable declaration
2 Vbe=0.7 //base to emitter
   voltage (V)
3 Rb=250 //base resistance(k
   ohms)
4 Vcc=10 //supply voltage(V)
5 Rl=0.5 //load resistance(k
   ohms)
6
7 // Calculations
8 Ic=Vcc/Rl //collector current(mA)
9 IbQ=(Vcc-Vbe)/Rb //Ib at operating point
   (uA)
10 IcQ=8 //Ic at operating point
   (mA)
11 VceQ=6 //Vce at operating
   point (V)
12
13 //Results
14 printf (" values are IbQ : %.4f uA,IcQ: %.f mA and
   Vcc : %.f V",IbQ,IcQ,Vcc)
15 printf (" collector current Ic is %d mA and output
   voltage ,vL=6-2 sinwt V",Ic)

```

---

### Scilab code Exa 2.5 Example

```

1 //Variable declaration
2 Vgs=12 //gate to source voltage(V)
3 Vt=4 //threshold voltage(V)
4 Id=12.8 //drain current(mA)
5 K=0.0002 //device parameter
6 Vdd=24 //drain voltage(V)
7 Vds=8 //drain to source voltage(V)
8 Vgs=8
9

```

```

10 // Calculations
11 Id=K*((Vds-Vt)^2) //drain current at Vds=8V
12 Rd=(Vdd-Vds)/Id //drain resistance(k ohms)
13
14 //Result
15 printf ("diode resistance is %.f ohms",Rd)

```

---

#### Scilab code Exa 2.7 Example

```

1 //Variable declaration
2 Vds=7.5 //drain to source voltage(V)
3 Id=5 //drain current(mA)
4
5 //Calculations
6 Vgs=-1.5 //gate to source voltage(V)
7 Vgg=-Vgs //gate voltage=gate to source
    voltage(V)
8
9 //Result
10 printf ("gate voltage is %.1f V",Vgg)

```

---

#### Scilab code Exa 2.8 Example

```

1 //Variable declaration
2 Vds=7.5 //drain to source voltage(V)
    )
3 Idss=8. //drain current for Vgs(V)
4 Vgs=2. //gate to source voltage(V)
5 Vp=4. //peak voltage(V)
6
7 //Calculations
8 Id=Idss*((Vp-Vgs)/Vp)**2 //drain current(mA)
9

```

```

10 //Result
11 printf ("diode current is %.1f mA",Id)

```

---

### Scilab code Exa 2.10 Example

```

1 //Variable declaration
2 beeta=160 //current gain
3 Vee=10 //emitter voltage(V)
4 Rb=400 //base resistance(k ohms)
5 Veb=0.8 //emitter to base voltage(V)
6 Re=2.5 //emitter resistance(k ohms)
7 Rc=1.5 //collector resistance(k
    ohms)
8
9 //Calculations
10 //Part a
11 Ib=(Vee-Veb)/((Re*(1+beeta))+Rb) //base current(
    uA)
12 Ic=beeta*Ib //collector
    current(mA)
13 Ie=(beeta+1)*Ib //emitter
    current(mA)
14 Vce=Vee-(Re*Ie)-(Rc*Ic) //emitter to
    collector voltage(V)
15 Vce=-Vce //collector to
    emitter voltage(V)
16
17 //Part b
18 beeta=80 //current gain
19 Ib1=(Vee-Veb)/((Re*(1+beeta))+Rb) //base current(
    uA)
20 Ic1=beeta*Ib1 //collector
    current(mA)
21 Ie1=(beeta+1)*Ib1 //emitter
    current(mA)

```

```

22 Vce1=-(Vee-(Ie1*Re)-(Rc*Ic1))           //collector to
    emitter voltage(V)
23
24 //Result
25 printf (" collector current and Vce for beeta=160 are
    %.2f mA and %.2f" ,Ic,Vce)
26 printf (" Ic and Vce for beeta=80 are %.2f mA and %.2
    f" ,Ic,Vce1)

```

---

### Scilab code Exa 2.13 Example

```

1
2 //Variable declaration
3 K=2                               //device parameter
4 Rd=2.5*10**3                       //drain resistance(k ohms)
5 Rs= Rd
6 R1=100*10**3                       //resistance(ohms)
7 R2=200*10**3                       //resistance(ohms)
8 Vdd=12                             //drain voltage(V)
9 Vt=4                               //threshold voltage(V)
10
11 //Calculations
12 Vgg=(R2*Vdd)/(R1+R2)
13 syms Id
14 expr=solve([Id**2-3.28*Id+2.56],[Id])
15 disp(expr)
16 Id=1.28
17 Vds=Vdd-5*Id
18
19 //Result
20 printf (" Id is %.2f mA and Vds is %.1f V" ,Id,Vds)

```

---

### Scilab code Exa 2.14 Example

```

1 //Variable declaration
2 k=2. //device parameter
3 Vt=-1. //threshold voltage(V)
4 Vdd=-12. //drain voltage(V)
5 R1=300. //resistance (kohms)
6 R2=100. //resistance (kohms)
7
8 //Calculations
9 //Part a
10 Vgs=-2 //gate to source voltage(V)
11 Vgg=(R2*Vdd)/(R1+R2) //gate voltage(V)
12 Id=k*((Vgs-Vt)**2) //drain current(mA)
13 Rs=(Vgs-Vgg)/Id //source resistance(k ohms)
    as Id=Is ,Kvl in GS loop
14 Is=Id
15
16 //Part b
17 Vds=-4 //drain to source voltage(
    V)
18 Rd=(-Vdd+Vds-(Is*Rs))/Id //applying kvl in DS loop
19
20 //Part c
21 Vt=-1.5 //threshold voltage(V)
22 Vgg=-1.5 //gate voltage using Id
    formula
23 R2new=(Vgg*R1)/(Vdd-Vgg) //new resistance(k ohms
    )
24
25 //Results
26 printf ("a)source resistance is %.1f kohm",Rs)
27 printf ("b)drain resistance is %.1f kohm",Rd)
28 printf ("c)R2new is %.2f kohm",R2new)

```

---

Scilab code Exa 2.15 Example

```

1
2
3 //Variable declaration
4 Vp=-4 //peak voltage(V)
5 Idss=10 //drain current for Vgs(V)
6 Vdd=18 //drain voltage(V)
7 Rs=2 //source resistance(ohms)
8 Rd=2 //drain resistance(ohms)
9 R1=450*10**3 //resistance(ohms)
10 R2=90*10**3 //resistance(ohms)
11
12 //Calculations
13 Vgg=(R2*Vdd)/(R1+R2)
14 syms Id
15 expr=solve([20*Id**2-148*Id+245],[Id])
16 disp(expr)
17 Id1=2.5
18 Vds=Vdd-((Rs+Rd)*Id1)
19
20 //Result
21 printf("Id is %.1f mA and Vds is %.1f V",Id1,Vds)

```

---

### Scilab code Exa 2.16 Example

```

1
2
3 //Variable declaration
4 Vp=4 //peak voltage(V)
5 Idss=12. //drain current for Vgs(V)
6 Vdd=12 //drain voltage(V)
7 Id=4. //drain current(mA)
8 Vds=6 //drain to source voltage(V)
9
10 //Calculations
11 Rs=(Vp/4)*(1-(sqrt(Id/Idss))) //by Id=Idss(1-(

```

```
    Vgs/Vp))^2 and putting Vgs=4Rs in it and solving
12 Rd=((Vdd+Vds)/Id)-Rs //solving
    equation -Vdd-Vds+(Id*(Rd+Rs))=0
13
14 //Result
15 printf ("source resistance is %.2f kohm",Rs)
16 printf ("drain resistance %.2f kohms",Rd)
```

---

## Chapter 3

# SMALL SIGNAL MODELS AMPLIFICATION AND BIASING

Scilab code Exa 3.1 Example

```
1 //Variable declaration
2 beeta=100           //current gain
3 Ic=2.5             //collector current (mA)
4 Io=-0.5            //output current (mA)
5 Rl=2.5             //load resistance (kohm)
6
7 //Calculations
8 rpi=beeta*(25/Ic)  //dynamic resistance (ohms)
9 Ib=Io/(-beeta)    //as Io=-beeta*Ib
10 Vs=rpi*Ib         //signal voltage (V)
11 Vo=Rl*Io          //output voltage (V)
12 Av=Vo/Vs          //voltage gain
13 Ai=Io/Ib          //current gain
14
15 //Results
16 printf ("signal voltage is %.1f mV",Vs)
17 printf ("current gain is %.1f",Ai)
```

```
18 printf ("voltage gain is %.f",Av/1E-3)
```

---

### Scilab code Exa 3.2 Example

```
1
2
3 //Variable declaration
4 Id=1.6 //drain current(mA)
5 Vgs=-3 //gate to source voltage(V)
6 Id1=.4 //drain current(mA)
7 Vgs1=-4 //gate to source voltage(V)
8 Vp=-5 //peak voltage(V) by solving
    equations 1.6=Idss(1+3/Vp)^2 and .4=Idss(1+4/Vp)
    ^2
9 Idss=10 //small signal drain current(mA
    ) by solving equations 1.6=Idss(1+3/Vp)^2 and .4=
    Idss(1+4/Vp)^2
10
11 //Calculations
12 gmo=-(2*Idss)/Vp //transconductance(
    mS)
13 gm=gmo*(sqrt(Id/Idss)) //transconductance(uS)
14 gm1=gmo*(sqrt(Id1/Idss)) //transconductance(uS)
15
16 //Results
17 printf ("Idss and Vp are %.f mA and %.f V",Idss,Vp)
18 printf ("gmo is %.f mS",gmo)
19 printf ("gm at Id is %.f gm at Id1 is %.f uS",gm/1E
    -3,gm1/1E-3)
```

---

### Scilab code Exa 3.3 Example

```
1 //Variable declaration
```

```

2 gm=1600          //gm(us)
3 rd=50           //resistance(kohms)
4 Rl=5            //load resistance(kohms)
5
6 //Calculations
7 Av=-gm*Rl       //Vgs=Vs from circuit model
8                //Vo=-(gm*Vgs)*Rl
9                //as Av=Vo/Vs=-gm*Rl
10
11 //Result
12 printf("voltage gain of the circuit is %.f",Av/1E
        +3)

```

---

#### Scilab code Exa 3.4 Example

```

1 //Variable declaration
2 beta=100.       //current gain
3 rpi=2*10**3     //dynamic resistance(ohms)
4 rx=500          //resistance(ohms)
5 ro=250*10**3   //output resistance(ohms)
6 R1=50*10**3    //resistance(k ohms)
7 R2=10*10**3    //resistance(k ohms)
8 Rc=5*10**3     //collector current(k ohms)
9 Rl=5*10**3     //load current(k ohms)
10 Rs=1*10**3    //source resistance(k ohms)
11
12 //Calculations
13 Rb=(R1*R2)/(R1+R2) //equivalent
    resistance of R1 and R2(kohms)
14 r=rpi+rx       //series resistance
    of rpi and rx(k ohms)
15 gm=beta/rpi    //transconductance(
    mS)
16 Vo=-gm*((Rc*Rl)/(Rc+Rl))*0.526 //output voltage(V)
    as

```

```

17 Av=Vo //voltage gain
18 Ai=Av*((Rs+((Rb*r)/(Rb+r)))/Rl) //current gain
19
20 //Results
21 printf ("source to load voltage gain is %.2f",Av)
22 printf ("source to load current gain is %f",Ai)
23 disp ("Note : Solution given in the textbook is
        incorrect")

```

---

### Scilab code Exa 3.5 Example

```

1 //Variable declaration
2 beta=100. //current gain
3 rd=50*10**3 //internal dynamic resistance(ohms)
4 gm=5*10**-3 //transconductance(mS)
5 R1=50*10**3 //resistance(ohms)
6 R2=10*10**3 //resistance(ohms)
7 Rs=10*10**3 //source current(ohms)
8 Rg=1*10**6. //gate resistance(ohms)
9 Rd=10*10**3 //drain resistance(ohms)
10
11 //Calculations
12 Vgs=(Rg/(Rs+Rg)) //gate to source
    voltage (V) as Vgs=Vs((Rg/(Rs+Rg))
13 Av=-Vgs*gm*((rd*Rd)/(rd+Rd)) //voltage gain ,Av=
    Vo/Vs and Vo=-gmVgs(rd||Rd)
14 Ai=Av*((Rs+Rg)/Rd) //current gain
15
16 //Results
17 printf ("source to load voltage gain is %.f",Av)
18 printf ("source to load current gain is %.f",Ai)

```

---

### Scilab code Exa 3.6 Example

```

1 //Variable declaration
2 Rs=500 //collector current(k ohms)
3 Io=-1*10**-3 //output current(mA)
4 Rc=5*10**3. //collector resistance(ohms)
5 hie=2*10**3
6 hoe=10*10**-6.
7 hfe=100.
8 hre=5*10**-4
9 Rb=50*10**3. //base resistance(ohms)
10
11 //Calculations
12 Io1=-1/(1+Rc*hoe)*hfe //as Io=-1/(1+Rc*hoe)*hfe*Ib
13 Ib=-1/Io1 //base current(uA)
14 Vo=Io*Rc //output voltage(V)
15 Vi=hie*Ib+Vo*hre //input voltage(V)
16 Is=Ib+Vi/Rb //source current(ohms)
17 Ai=Io/Is //current gain
18 Vs=(Is*Rs)+Vi //source voltage(V)
19 Av=Vo/Vs //voltage gain
20
21 //Results
22 printf ("source to load voltage gain is %.f",Av/1E
-3)
23 printf ("source to load current gain is %.f",Ai/1E
-3)

```

---

### Scilab code Exa 3.7 Example

```

1 //Variable declaration
2 beeta=100. //current gain
3 Ic=4. //collector current(mA)
4 Vbe=0.7 //base to emitter voltage(V)
5 Re=2. //emitter resistance(ohms)
6 Vcc=32. //supply voltage(V)
7 abeeta=40. //actual current gain

```

```

8
9 // Calculations
10 Ib=Ic/beeta //base current (mA
   )
11 Rb=(Vcc-Vbe-((Ib+Ic)*Re))/Ib // as Vcc=(Ib*Rb)+
   Vbe+(Ib+Ic)*Re
12 Ib=(Vcc-Vbe-8)/(Rb+Re) // as Vcc=Rb*Ib+
   Vbe+(Ib+Ic)*Re
13 Ic1=abeeta*Ib // collector
   current (mA)
14 deltaIc=Ic-Ic1 //change in
   collector current (mA)
15
16 // Result
17 printf ("change in Ic when beeta=40 is %.1f mA",
   deltaIc)

```

---

### Scilab code Exa 3.8 Example

```

1 // Variable declaration
2 Rb1=36 //base resistance 1(kohms)
3 Rb2=12 //base resistance 2(kohms)
4 Rc=4 //emitter resistance (kohms)
   )
5 Re=1.8 //emitter resistance (kohms)
6 Vcc=12 //supply voltage (V)
7 Vbe=0.7 //base to emitter voltage (V)
   )
8
9 // Calculations
10 Rb=(Rb1*Rb2)/(Rb1+Rb2) //base resistance (ohms)
11 Vbb=Vcc*(Rb2/(Rb1+Rb2)) //voltage supply to base (V)
12 // (10.8*Ib)+(1.8*Ic)=2.3
   equation 1... solving
   -Vbb+RbIb+Vbe+(Ib+IC)Re

```

```

13                                     //(1.8*Ib)+(5.8*Ic)+Vce=12
                                     equation 2 solving -
                                     Vcc+RcIc+Vce+(Ob+Ic)Re
14 //Part a
15 beeta=50                            //current gain
16 Ib=2.3/100.8                        //(10.8*Ib)+(90*Ib)=2.3 , using
    -Vbb+Rb*Ib+Vbe+(Ib+Ic)*Re
17                                     //as Ic=50Ib and putting this
                                     in equation 1
18 Icq=Ib*beeta
19 Vceq=Vcc-(1.8*Ib)-(5.8*Icq) //from equation 2
20
21 //Part b
22 beeta=150                            //current gain
23 Ib=2.3/280.8                        //(10.8*Ib)+(270*Ib)=2.3, using
    -Vcc+Rc*Ic+Vce+(Ib+Ic)*Re
24                                     //as Ic=150Ib and putting this
                                     in equation 1
25 Icq1=Ib*beeta
26 Vceq1=Vcc-(1.8*Ib)-(5.8*Icq1)      //from
    equation 2
27
28 //Results
29 printf ("when beeta increases by 300%%,Icq increases
    by %.1f %%", (Icq1-Icq)/Icq1*100)
30 printf ("when beeta increases by 300%%, Vceq
    increases by %.f %%", (Vceq-Vceq1)/Vceq*100)

```

---

### Scilab code Exa 3.9 Example

```

1 //Variable declaration
2 Ic=4                                //collector current (mA)
3 Vce=8                                //collector emitter
    voltage (V)
4 beeta=100                            //current gain

```

```

5 Rb2=24 //base resistance(kohms)
6 Vbe=0.7 //base to emitter voltage(
  V)
7 Rc=4 //collector current(kohm)
8 Re=2 //emitter resistance(kohms)
9 Ib=0.04 //base current(mA)
10
11 // Calculations
12 //Part a
13 Vcc=(Ic*Rc)+Vce+Ic*Re //from formula Vcc=
  IcRc+Vce+(Ic+Ib)Re.. eq 1
14
15 //Part b
16 Rb1=Rb2*(Vcc-(Vbe+Ic*Re))/((Vbe+Ic*Re)+Ib) //from
  eq 1 and also from Vbb= Vcc(Rb2/(Rb1+Rb2))
17 Rb=(Rb1*Rb2)/(Rb1+Rb2) //base
  resistance(ohms)
18 Vbb=(Vcc*Rb2)/(Rb1+Rb2) //supply
  to base(V)
19
20 //Part c
21 abeeta=40 //actual
  current gain
22 Ib1=((Vbe+Re*Ic)-Vbe)/((1+abeeta)*2+Rb) //from
  equation Vbb=IbRb+Vbe+(Ic+Ib)Re
23 Ic1=abeeta*Ib1 //
  collector gain
24
25 //Results
26 printf ("a)Vcc is %.1f V",Vcc)
27 printf ("b) values are Rb1: %.2f KOhms,Rb : %.2f kohm
  and Vbb : %.2f V" ,Rb1,Rb,Vbb)
28 printf ("c) actual value of Ic1 : %.2f mA",Ic1)

```

---

Scilab code Exa 3.10 Example

```

1 //Variable declaration
2 Vcc=10 //supply voltage(V)
3 Rc=4.7 //collector current(kohms)
4 Rb=250 //base resistance(kohms)
5 Re=1.2 //emitter resistance(kohms)
6 beeta=100 //current gain
7 Vbe=0.7 //base to emitter voltage(V)
8
9 //Calculations
10 //Part a
11 Ib=(Vcc-Vbe)/(Rb+(beeta*(Rc+Re))) //base current(
    uA)
12 Ic=beeta*Ib //collector
    current(mA)
13 Vce=Vcc-Ic*(Rc+Re) //collector to
    emitter voltage(V)
14 //Part b
15 beeta1=150 //current gain
16 Ib1=(Vcc-Vbe)/(Rb+(beeta1*(Rc+Re))) //base current(
    mA)
17 Ic1=beeta1*Ib1 //collector
    current(mA)
18 Vce1=Vcc-Ic1*(Rc+Re) //collector to
    emitter voltage(V)
19 deltaIc=((Ic1-Ic)/Ic)*100 //small change
    in Ic(mA)
20 deltaVce=((Vce-Vce1)/Vce)*100 //small change
    in Vce(V)
21
22 //Results
23 printf ("values of Ic is %.2f mA and Vce : %.2f V",
    Ic,Vce)
24 printf ("values of Ic1 is %.2f mA and Vce1 is %.2f V
    ",Ic1,Vce1)
25 printf ("%%% change in Ic is %.2f %% and in Vce is %
    .2f %% ",deltaIc,deltaVce)

```

---

### Scilab code Exa 3.11 Example

```
1 //Variable declaration
2 Id=3 //drain current (mA)
3 Vds=12 //drain source voltage (V)
4 Vgs=-3 //gate source voltage (V)
5 Vdd=36 //drain voltage (V)
6 Vgg=12 //gate voltage (V)
7 Rg=12 //gate resistance (Mohms)
8
9 //Calculations
10 R1=(Rg*Vdd)/Vgg //resistance (Mohms)
11 R2=(Rg*R1)/(R1-Rg) //resistance (kohms)
12 Rs=(Vgg-Vgs)/Id //resistance (kohms)
13 Rd=(Vdd-Vds-Id*Rs)/Id //as Vdd-IdRd-Vds-IdRs
14 Vgs=-3.6 //consider Vgs increases
    by 20%
15 Idnew=(Vgg-Vgs)/Rs //new drain current (mA)
16
17 //Results
18 printf ("value of R1 : %.f MOhm , R2: %.f Mohms, Rs
    : %.f KOhm and Rd: %.f kohms",R1,R2,Rs,Rd)
19 printf ("new Id is %.2f mA",Idnew)
```

---

### Scilab code Exa 3.12 Example

```
1
2 //Variable declaration
3 k=0.0002 //device parameter
4 Vt=4 //thevinin voltage (V)
5 Vdd=24 //drain voltage (V)
6 Id0=3 //drain current (mA)
```

```

7
8 // Calculations
9 Vgs=(sqrt(Id0/k))+4 // as Id=k(Vgs-Vt)^2
10 Rd=-(Vgs-Vdd)/Id0 // as Vds=Vdd-IdRd and Vgs=
    Vds=7.87
11 k=0.0003 //device parameter
12
13 syms Id
14 expr = solve([Id**2-7.5*Id+13.7],[Id])
15 printf ("equation has 2 solutions")
16 disp(expr) //
    putting value of k=0.0003 in eq of Id,
17 Id1=3.15 // we
    get Vgs=Vds=24-5.4Id and putting Vgs again in Id
    we get,
18 // Id^2-7.5Id
    +13.7=0
19
20 Idchange=((Id1-Id0)/Id0)*100
    //changed Id(mA)
21
22 //Result
23 printf ("change in Id is %.1f %% increase",Idchange)

```

---

### Scilab code Exa 3.13 Example

```

1 //Variable declaration
2 Vt=2 //threshold voltage(V)
3 Id=8 //drain current(mA)
4 Vgs=6. //gate to source
    voltage(V)
5 k=0.5 //device parameter
6 Vdd=24 //drain voltage(V)
7 Vds=10 //drain to source

```

```

        voltage(V)
8
9 // Calculations
10 // Part a
11 Vgs1=4 //
    gate to source voltage(V)
12 Id1=k*(Vgs1-Vt)**2
    //drain current(mA)
13
14 // Part b
15 Vgg=3*Vgs1
    //gate voltage(V)
16 R2=(Vdd/Vgg)-1 //
    resistance(Mohms)
17 Rs=(Vgg-Vgs1)/2
    //source resistance(k ohms)
18 Rd=(Vdd-Vds-Id1*Rs)/2
19
20 // part c
21 K=1.5*k //increased by 50%
22 Vgs2=3.67 //solving 12=Vgs+4Id and
    Id=0.75(Vgs-2)^2
23 Id2=2.08 //drain current when k is
    increased(mA)
24 Vds1=Vdd-Id2*(Rd+Rs) //drain to source voltage(
    V)
25
26 // Results
27 printf ("drain current defined by Vgs=4 and Vds=10
    is %.1f mA", Id1)
28 printf ("value of Rs,Rd,R2 are %.1f k ohms %.1f k
    ohms %.1f Mohms resp.", Rs, Rd, R2)
29 printf ("actual value of Id and Vds are %.2f mA %.2f
    mA and %.2f V resp.", Id2, Vds1, Vds)

```

---

### Scilab code Exa 3.14 Example

```
1 //Variable declaration
2 Ic=10 //collector current (mA)
3 beeta=100 //current gain
4 Vbe=0.7 //base to emitter
   voltage (V)
5 Vcc=10 //supply voltage (V)
6
7 //Calculations
8 //Part a
9 R=(beeta*(Vcc-Vbe))/((beeta+2)*Ic) //
   resistance (k ohms)
10 beeta1=200 //
   current gain
11 Ic1=(beeta1/(beeta1+2))*((Vcc-Vbe)/R) //
   collector current (mA)
12 Icchange=((Ic-Ic1)/Ic) //
   change in collector current (mA)
13
14 //Part b
15 Ic2=0.1 //
   collector current (mA)
16 R1=(beeta*(Vcc-Vbe))/((beeta+2)*Ic) //
   resistance (k ohms)
17 Ic3=(beeta1/(beeta1+2))*((Vcc-Vbe)/R1) //
   collector current (mA)
18 Icchange1=((Ic2-Ic3)/Ic2) //
   change in collector current (mA)
19
20 //Results
21 printf ("%%" change in Ic is %.1f %% increase",
   Icchange)
22 printf ("%%" change in Ic is %.1f %% increase",
   Icchange1)
```

---

### Scilab code Exa 3.15 Example

```
1 //Variable declaration
2 Vcc=6 //supply voltage(V)
3 R=1.2 //resistance(k ohms)
4 Vbe=0.7 //base to emitter voltage
   (V)
5 beeta=100. //current gain
6
7 //Calculations
8 //Part a
9 Ir=(Vcc-Vbe)/R //current (mA)
10 I=(beeta/(beeta+3))*Ir //current (mA) as
   transistors are identical ,I=Ie
11
12 //Result
13 printf ("load current I is %.2f mA ",I)
```

---

### Scilab code Exa 3.16 Example

```
1
2
3 //Variable declaration
4 Idss=10 //drain current for zero bias(
   mA)
5 Vp=-4 //peak voltage(V)
6 Idq=2.5 //quiescent drain current (mA)
7 Id=Idq
8 Vdd=24 //voltage drain drain(V)
9 Vgg=4 //gate voltage(V)
10 R1=22 //resistance (Mohms)
11
```

```

12 // Calculations
13 // Part a
14 Vgs=Vp*(1-(sqrt(Id/Idss))) // solving Id=Idss
    (1-Vgs/Vp)^2
15 Rs=(Vgg-Vgs)/Id // as Vgg-Vgs
    -IdRs=0 ,Id=Is
16 Rd=2.5*Rs // given
17 R2=(Vgg*R1)/(R1-Vgg) // from Vgg=(
    R1*R2)/(R1+R2)
18
19 // Part b
20 gmo=-(2*Idss)/Vp //
    transconductance (mS)
21 gm=gmo*(sqrt(Id/Idss)) // transconductance
    (mS)
22
23 // Part c
24 Av=-gm*Rd // voltage
    gain
25
26 // Results
27 printf (" values of Rs : %.1f Kohms, Rd : %.1f k ohms
    and R2 is %.1f M ohms",Rs,Rd,R2)
28 printf (" value of gm is %.1f mS and gmo is %.1f mS",
    gm,gmo)
29 printf (" voltage amplification is %.1f",Av)

```

---

### Scilab code Exa 3.17 Example

```

1
2
3 // Variable declaration
4 beeta=98. // current gain
5 rpi=1.275 // dynamic
    resistance(k ohms)

```

```

6 Rb=220. //base resistance
   (k ohms)
7 Re=3.3 //emitter
   resistance(k ohms)
8 Vcc=12. //supply voltage(
   V)
9 Vbe=0.7 //base to emitter
   voltage(V)
10
11 //Calculations
12 //Part a
13 x=rpi/(1+beeta)
14 Av=Re/(Re+x) //voltage gain
15
16 //Part b
17 Zb=rpi+(1+beeta)*Re //impedance(k ohms)
18 Zi=(Zb*Rb)/(Zb+Rb) //input impedance(k
   ohms)
19 Zo=(Re*x)/(Re+x) //output impedance(k
   ohms)
20
21 //Part c
22 Ib=(Vcc-Vbe)/(Rb+(Re*(1+beeta))) //as Ie=(1+
   beeta)*Ib
23 Ic=beeta*Ib //collector
   current(mA)
24 rpi=beeta*(25/Ic) //dynamic
   resistance(k ohms)
25
26 //Results
27 printf ("voltage gain is %.3f",Av)
28 printf ("input impedance is %.1f KOhm and output
   impedance is %.1f ohms",Zi,Zo/1E-3)
29 printf ("value of Ic is %.3f mA",Ic)
30 printf ("value of rpi is %.3f k ohms",rpi/1E+3)

```

---

### Scilab code Exa 3.18 Example

```
1
2
3 //Variable declaration
4 Idss=16 //drain current
   bias to zero (mA)
5 Vp=-4 //pinch off
   voltage (V)
6 Rg=1 //gate resistance(
   ohms)
7 Rs=2.2 //source
   resistance (ohm)
8 Vdd=9 //drain drain
   voltage (V)
9
10 //Calculations
11 //Part a
12 //Id=Idss*(1-(Vgs/Vp))**2
13 // putting value of Vgs=2.2*Id inequation of Id ,we
   get
14 //Id**2-3.84Id+3.31
15
16 syms Id
17 expr=solve([Id**2-3.84*Id+3.31],[Id])
18 disp(expr)
19 Id1=1.3
20 Vgs=-Id1*Rs
   //gate to source voltage (V)
21 gm0=-(2*Idss)/Vp
   //transconductance (mS)
22 gm=gm0*(1-(Vgs/Vp))
   //transconductance (mS)
23 rm=1/gm
```

```

    //transresistance(k ohms)
24 Av=(Rs*gm)/(1+(Rs*gm))
    //voltage gain
25
26 //Part b
27 Zi=Rg
    //input impedance(Mohms)
28 Zo=(Rs*rm)/(Rs+rm)
    //output impedance(ohms)
29
30 //Results
31 printf ("voltage gain is %.3f",Av)
32 printf ("input and output impedences are %.f Mohms
    and %.1f ohms",Zi,Zo/1E-3)

```

---

### Scilab code Exa 3.19 Example

```

1
2
3 //Variable declaration
4 Re=0.56 //emitter
    resistance(k ohms)
5 beta=1600 //current gain
6 R1=110 //resistance(k ohms)
    )
7 R2=330 //resistance(k ohms)
    )
8
9 //Calculations
10 //Part a
11 Av1=Re*(beta+1) //voltage gain
12
13 //part b
14 Rb=(R1*R2)/(R1+R2) //base resistance(k
    ohms)

```

```

15 Vs=(1.56/(Re*(beta+1)))+1           //source voltage(V)
16 Avs=1/Vs
17
18 //part c
19 R=1+(1+beta)*Re
    //resistance presented to Ib
20 I=Rb/(Rb+R)
    //I=Ib/Ii
21 Ai=(1+beta)*I
    //current gain
22
23 //part d
24 Rl=10*10**3                          //load
    resistance(ohm)
25 Re1=(Re*Rl)/(Re+Rl)                  //emitter
    resistance(k ohms)
26 R1=1+(1+beta)*Re1                    //resistance
    presented to Ib(k ohms)
27 I1=Rb/(Rb+R1)                        //I1=Ib/Ii
28 Ai1=(beta+1)*I1                       //current
    gain
29 Av2=Re1*(1+beta)                      //voltage
    gain
30
31 //Results
32 printf ("a)voltage gain is %.2f",Av1)
33 printf ("b)Avs is %.2f",Avs)
34 printf ("c)Ai is %.2f ",Ai)
35 printf ("when output Vo1 feeds a load of 10 k ohms
    Ai is %d and Av2 is %.f",Ai1,Av2)

```

---

### Scilab code Exa 3.20 Example

```

1 //Variable declaration
2 beeta1=120.                               //current gain

```

```

3  beeta2=160.                //current gain
4  Vcc=18                    //supply voltage(V)
5  Rc=0.1                    //collector
    resistance(ohms)
6  Rb=2*10**3.              //base resistance(
    ohms)
7  Vbe=0.7                  //base to emitter
    voltage(V)
8
9  // Calculations
10 Ib1=(Vcc-Vbe)/(Rb+(beeta1*beeta2*Rc)) //base current(
    uA)
11 Ib2=beeta1*Ib1           //base current(
    mA)
12 Ie1=(beeta1+1)*Ib1      //emitter
    current(mA)
13 Ic=Ie1+(beeta2*Ib2)     //collector
    current(mA)
14 Vo=Vcc-(Ic*Rc)          //output voltage
    (V)
15 Vi=Vo-Vbe               //input voltage(
    V)
16
17 // Results
18 printf ("dc biased current is %.1f mA",Ic)
19 printf ("output voltage %.2f V",Vo)
20 printf ("input voltage %.2f V",Vi)

```

---

### Scilab code Exa 3.21 Example

```

1
2
3 //Variable declaration
4 deltaId=2.                //change in Id(mA
    )

```

```

5  deltaVgs=1.                                //change in Vgs(V
   )
6  deltaVds=5.                                //change in Vds(V
   )
7  Idss=10.                                    //drain current
   biased to zero(mA)
8  Id=5.                                       //drain current(
   mA)
9  Vp=-6.                                      //pinch off
   voltage(V)
10
11 // Calculations
12 //Part a
13 gm=(deltaId)/(deltaVgs)                    //
   transconductance (mS)
14 rds=(deltaVds)/(deltaId)                   //resistance (k
   ohms)
15 gm0=-(2*Idss)/Vp                           //
   transconductance (mS)
16 gm=gm0*(sqrt(Id/Idss))                     //transconductance (mS)
17
18 //Part b
19 R1=4.5                                       //resistance (k
   ohms)
20 R2=2                                         //resistance (k
   ohms)
21 Av=gm*((R1*R2)/(R1+R2))                    //voltage gain
22
23 // Results
24 printf ("drain current biased to zero is %.1f mA and
   pinch off voltage is %.1f V",Idss,Vp)
25 printf ("value of gm and rds are %.2f mS and %.2f k
   ohms",gm,rds)
26 printf ("small signal amplifier gain is %.2f ",Av)

```

---

### Scilab code Exa 3.22 Example

```

1
2
3 //Variable declaration
4 Idson=0.2
5 Vgs=5 //gate to source voltage(
   V)
6 Vdd=12 //drain voltage(V)
7 Vt=2 //thevinine voltage(V)
8 R1=100. //resistance(k ohms)
9 R2=100. //resistance(k ohms)
10 Rd=30 //drain resistance(K ohms
   )
11 Rs=6 //source resistance(k
   ohms)
12 deltaVdd=0.3 //change in Vdd(V)
13 rds=50 //internal drain to
   source resistance()
14
15 //Calculations
16 //Part a
17 k=Idson/((Vgs-Vt)**2) //device
   parameter
18 Vgg=Vdd*(R1/(R1+R2)) //gate voltage(V)
19 Vgs=4.89 //gate to source
   voltage(V)
20 Id=k*(Vgs-Vt)**2 //drain current(
   mA)
21 Vds=Vdd-((Rd+Rs)*Id) //drain to source
   voltage(V)
22 gm=2*(sqrt(k*Id)) //transconductance(mS)
23 deltaVgg=deltaVdd*(R2/(R1+R2)) //change in Vgg(V
   )
24
25 vgs=0.105 //as vgs=0.15-6id
   where id=u*vgs/(rds+Rs+Rd)=0.74vgs after solving
26 id= 0.074*vgs*10**3

```

```

27
28 //Results
29 printf ("id is %.2f uA",id)

```

---

### Scilab code Exa 3.23 Example

```

1
2
3 //Variable declaration
4 deltaId=1 //change in Id(mA)
5 deltaVgs=0.75 //change in Vgs(V)
6 rd=100 //internal drain
   resistance(k ohms)
7 Rd=100 //drain resistance
   (k ohms)
8 Vgs=2 //as Vgs= 2sinwt
9
10 //Calculations
11 gm=(deltaId)/(deltaVgs) //transconductance
   (m)
12 Vo=-gm*Vgs*((rd*Rd)/(rd+Rd)) // as Vi=2sin(w*t)
13
14 //Results
15 printf ("value of Vo is %.f *sinwt mV",Vo)

```

---

### Scilab code Exa 3.24 Example

```

1 //Finding resistance
2
3 //Variable declaration
4 Rd=4 //drain resistance(ohms)
5 Rs=2.5 //ource resistance(ohms)
6 R1=200*10**3 //resistance(ohms)

```

```

7 R2=100*10**3           //resistance (ohms)
8 gm=2.5                 //transconductance (mS)
9 rd=60                  //internal drain resistance (
    ohms)
10
11 //Calculations
12 //Part b
13 Ro=Rs/(1+(((1+gm*rd)*Rs)/(rd+Rd))) //output
    resistance (ohms)
14
15 //Part c
16 Rd1=0                 //drain
    resistance
17 Ro1=Rs/(1+(((1+gm*rd)*Rs)/rd)) //output
    resistance (ohms)
18
19 //Results
20 printf ("value of Ro is %.f ohms",Ro/1E-3)
21 printf ("value of Ro1 is %.f ohms",Ro1/1E-3)

```

---

### Scilab code Exa 3.25 Example

```

1 //Variable declaration
2 beeta=100              //current gain factor
3 Vbe=0.7               //base to emitter
    voltage (V)
4 Rb=250                //base resistance (k
    ohms)
5 Vee=10                //emitter voltage (V)
6 Re=1                  //emitter resistance (
    k ohms)
7
8 //Calculations
9 Ib=(Vee-Vbe)/(Rb+1+beeta) // solving Rb*Ib+Vbe
    +(Ic+Ib)=Vee and putting Ic+Ib=(1+beeta)Ib

```

```

10 Ic=beeta*Ib           //collector current(
    mA)
11 rpi=beeta*(25/Ic)     //dynamic resistance
    (ohms)
12 Vi=(rpi*Ib)+(1+beeta)*Re*Ib //input voltage(V)
13 Ri=Vi/Ib             //input resistance(k
    ohms)
14
15 //Results
16 printf ("value of Ri is %.1f K ohms",Ri/1E+1)

```

---

#### Scilab code Exa 3.26 Example

```

1 //Variable declaration
2 beeta=125           //current gain
3 gm=35              //transconductance(
    mS)
4 Re=4               //emitter resistance
    (k ohms)
5 Rb=1.5             //base resistance(k
    ohms)
6
7 //Calculations
8 //Part a
9 rpi=beeta/gm       //dynamic resistance(
    k ohms)
10 Ri=rpi+((1+beeta)*Re) //input resistance(k
    ohms)
11 Ro=((Rb+rpi)*Re)/((Rb+rpi)+((1+beeta)*Re)) //output
    resistance(ohms) as Ro=Vo/Isc
12
13 //Part b
14 f=((1+beeta)*Re)/(Rb+rpi+((1+beeta)*Re)) //transfer
    function
15

```

```

16 //Results
17 printf ("value of Ri is %.1f K ohms and Ro is %.4f k
    ",Ri ,Ro)
18 printf ("transfer function is %.2f",f)

```

---

### Scilab code Exa 3.28 Example

```

1 //Variable declaration
2 Vcc=16 //supply voltage(V)
3 Vc=12 //collector voltage(V)
4 Ic=8 //collector current(mA)
5 Ic1=12
6 deltaIc=2000 //collector current(uA)
7 deltaVce=4 //collector emitter voltage(
    Vce)
8 deltaIb=20 //base current(mA)
9 Rl=2. //load reistance(k ohms)
10
11 //Calculations
12 hfe=(deltaIc)/(deltaIb)
13 hoe=(deltaIc)/(deltaVce)
14 Rdc=Vcc/Ic //dc resistance(k
    ohms)
15 Rac=Vc/Ic1 //ac resistance(k
    ohms)
16 Re=Rdc-Rac //emitter
    resistance(k ohms)
17 Rac1=(Rac*Rl)/(Rac+Rl) //for load of 2
    kohms, Rc=Rac
18 Icq=Vcc/(Rac1+Rdc) //Ic at
    operatingpoint(mA)
19 Vceq=Vcc-(Icq*Rdc) //Vc at operating
    point(V)
20
21 //Results

```

```

22 printf ("value of hfe and hoe are %d uS and %d uS",
    hfe, hoe)
23 printf ("value Rc and Re are %d k ohms and %d k ohms
    resp.", Rac, Re)
24 printf ("value of Icq and Vce %d mA and %.1f V resp.
    ", Icq, Vceq)

```

---

### Scilab code Exa 3.29 Example

```

1 //Variable declaration
2 hfe=120 //current gain
3 r1=1.5 //resistance(k ohms)
4 Vi=1 //input voltage(V)
5 hoe=50*10**-3 //output conductance with input
    open circuited
6 Rs=2 //source resistance(k ohms)
7 Vbe=0.7 //base to emitter voltage(V)
8 Vcc=10 //supply voltage(V)
9 r3=0.33 //resistance(k ohms)
10 r4=5.8 //rsistance(k ohms)
11 r5=27 //rsistance(k ohms)
12 hoe=50*10**-3 //output conductance with input
    open circuited
13
14 //Calculations
15 //Part a
16 Vbb=Vcc*(r4/(r4+r5)) //voltage to bae(V)
17 Rb=(r5*r4)/(r5+r4) // as Vbb-Vbe=RbIb+(
    hfe+1)Ib*R, here hfe=beeta
18 ib=(Vbb-Vbe)/(Rb+(hfe+1)*r3) //instantaneous base
    current (mA)
19 hie=(0.02/ib)*10**3
20 Ib=Vi/hie //base current (mA)
21 h=hfe*Ib
22 Avo=-h*r1 //voltage gain

```

```

23
24 //Part b
25 r=1/hoe //resistance(k ohms)
26 R1=(r*r1)/(r+r1) //resistance(k ohms)
27 R=(R1*Rs)/(R1+Rs) //resistance(k ohms)
28 Ib1=1/(Rs+R) //base current(mA)
29 h1=hfe*Ib1
30 Avl=-h1*R //voltage gain
31
32 //Results
33 printf ("hie and Avo are %.f and %.1f",hie,Avo/1E-3)
34 printf ("Avl is %.2f",Avl)

```

---

### Scilab code Exa 3.30 Example

```

1 //Variable declaration
2 Rl=20 //load resistance(ohms)
3 Vcc=30 //supply voltage(V)
4 beeta=150 //current gain
5 Re=2200 //emitter resistance(ohms)
6 Rb=350 //base resistance(k ohms)
7 Vbe=0.7 //base to emitter voltage(V)
8 Is=10**-3 //source current(A)
9 r1=2000 //resistance(ohms)
10
11 //Calculations
12 Ib=(Vcc-Vbe)/(Rb+(1+beeta)*Re) //base current(uA)
13 Ic=beeta*Ib //collector current(mA)
14 rpi=beeta*(25/Ic) //dynamic resistance(
ohms)
15 R=(Re*Rl)/(Re+Rl) //resistance(ohms)
16 Ib1=17.95 //round the base
emitter(as Rb>>2 kohms,it is ignored)
17 Vl=(beeta+1)*Ib1*R //load voltage(V)

```

```

18 Av1=V1 //Voltage gain
19 I1=V1/R1 //load current(A
   )
20 Ail=I1/Is //current gain
21
22 //Results
23 printf ("overall voltage gain is %.2f",Av1/1E+3)
24 printf ("overall current gain is %.f",Ail/1E+3)

```

---

### Scilab code Exa 3.31 Example

```

1 //Variable declaration
2 Vcc=15 //supply voltage(V)
3 beeta=30 //current gain
4 R=.47 //emitter resistance(ohms)
5 Vbe=0.7 //base to emitter voltage(V)
6 Vo=5 //output voltage(V)
7
8 //Calculations
9 Vbb=Vcc/2 //base
   voltage(V)
10 Ib=Vo/(R*930) //from equation(i)
11 R1=((6.1-4.98)/0.0114)*2 //
   resistance(k ohms)
12
13 //Results
14 printf ("value of R1 is %.f K ohms",R1)

```

---

## Chapter 4

# SMALL SIGNAL AMPLIFIERS FREQUENCY RESPONSE

Scilab code Exa 4.1 Example

```
1
2
3 //Variable declaration
4 Vs = 1. //source voltage(V)
5 C = 100*10^-6 //value of capacitance(uF)
6 r1 = 1 //resistance 1(k ohms)
7 r2 = 4 //resistance 2(k ohms)
8 R = 5 //total resistance ,R = r1+r2
9
10 //Calculations
11 Imax = Vs/(r1+r2)*10^3 //maximum current(uA)
12 fc = 1/(2*(%pi)*C*R) //critical frequency(Hz)
13 //As  $\omega C R = 1$  and  $\omega = 2 * \pi * f$ 
14 f = 10*fc //lowest frequency(Hz)
15 )
```

```

16 //Results
17 printf ("maximum current %.1f uA",Imax)
18 printf ("critical frequency %.3f Hz",fc/1E+3)
19 printf ("lowest frequency %.2f Hz",f/1E+3)

```

---

#### Scilab code Exa 4.2 Example

```

1
2
3 //Variable declaration
4 C = 100*10^-6 //capacitance(uF)
5 Rg = 1. //galvanometer resistance(k oms)
6 Rl = 4. //load resistance(k ohms)
7
8 //Calculations
9 Rth = (Rg*Rl)/(Rg+Rl) //thevinine's equivalent
    resistance
10 fc = 1/(2*(%pi)*C*Rth) //critical frequency(Hz)
11 f = fc*C //lowest frequency(Hz)
12
13 //Results
14 printf ("lowest frequency at which the point A gets
    grounded is %.1f Hz",f/1E-2)

```

---

#### Scilab code Exa 4.3 Example

```

1
2
3 //Variable declaration
4 rpi = 600 //dynamic junction
    resistance(ohms)
5 beta = 100 //common emitter current
    gain

```

```

6 Vs = 5.                //source voltage(V)
7 Rs = 400              //source resistance(ohms)
8 R = 10                //resistance(k ohms)
9
10 //Calculations
11 Ib = Vs/(Rs+rpi)     //base current(uA)
12 Vo = R*beta*Ib      //output voltage(V)
13 Rin = rpi           //input resistance(ohms)
14 Rout = R            //output resistance(k ohms)
15
16 //Results
17 printf ("output voltage is %.1f V",Vo)
18 printf ("input resistance %.1f ohms",Rin)
19 printf ("output resistance %.1f k ohms",Rout)

```

---

#### Scilab code Exa 4.4 Example

```

1 //Variable declaration
2 gm = 1.                //transconductance(mS)
3 rd = 40                //dynamic drain
   resistance(k ohms)
4 Rd1 = 40              //JFET 1 drain resistance
   (k ohms)
5 Rd2 = 10              //JFET 2 drain resistance
   (k ohms)
6
7 //Calculations
8 Avo = (-gm*((rd*Rd1)/(rd+Rd1)))*(-gm*((rd*Rd2)/(rd+
   Rd2)))                //voltage gain
9
10 //Results
11 printf ("Avo is %.1f ",Avo)

```

---

### Scilab code Exa 4.5 Example

```
1 //Variable declaration
2 beta = 125 //common emitter current gain
3 rpi = 2.5 //dynamic junction resistance(k
  ohms)
4 rd = 40 //dynamic drain resistance(k
  ohms)
5 gm = 2 //transconductance(mS)
6 Vs = 1 //assume, source voltage(V)
7 Rs = 10 //source resistance(k ohms)
8 Rc = 1 //collector resistance(k ohms)
9 rb = 2 //resistance(k ohms)
10 Vgs = 1 //gate to source voltage(V)
11
12 //Calculations
13 //Part a
14 R = (rd*Rs)/(rd+Rs) //equivalent resistance(k
  ohms)
15 Ib = gm*Vgs*(R/(rpi+R)) //base current(mA)
16 Vo = beta*Ib*Rc //output voltage(V)
17 Av0 = Vo //voltage gain
18
19 //Part b
20 Ib1 = Vs/(rb+rpi) //base current(mA) after
  interchanging stages of JFET and BJT
21 Vgs1 = beta*Ib1*Rc //gate to source voltage(V)
  after interchanging stages of JFET and BJT
22 Vo1 = gm*Vgs1*R //output voltage(V) after
  interchanging stages of JFET and BJT
23 Av01 = Vo1 //voltage gain after
  interchanging stages of JFET and BJT
24
25 //Results
26 printf ("Av0 is %.1f ",Av0)
27 printf ("Av01 when BJT and FET stages are reversed
  is %.f",Av01)
```

---

### Scilab code Exa 4.6 Example

```
1
2
3 //Variable declaration
4 Cc1 = 1*10^-6 //coupling capacitor
   1(uF)
5 Cc2 = 1*10^-6 //coupling capacitor 2
   (uF)
6 Rs = 10^3 //source resistance(k
   ohms)
7 rpi = 2*10^3 //dynamic junction
   resistance(k ohms)
8 Rc = 4500 //collector
   resistance(ohms)
9 Rl = 9*10^3 //load resistance(k
   ohms)
10 w = 100 //corner frequency(
   rad/s)
11
12 //Calculations
13 w11 = 1/(Cc1*(Rs+rpi)) //corner
   frequency input circuit (rad/s)
14 w12 = 1/(Cc2*(Rc+Rl)) //corner
   frequency output circuit(rad/s)
15 f = w11/(2*(%pi)) //lower cutoff
   frequency(Hz)
16 Zin = complex((Rs+rpi),-(1/(w*Cc1))) //input
   impedance(k ohms)
17 Zout = complex(Rc,-(1/(w*Cc2))) //output
   impedance(k ohms)
18
19 //Results
20 printf ("lower cut-off freq is %.f Hz",f)
```

```

21 disp ("ohms", Zin , " Zin")
22 disp ("ohms" ,Zout , " Zout")

```

---

#### Scilab code Exa 4.7 Example

```

1
2
3 //Variable declaration
4 Re = 1.5*10^3 //collector resistance(
    ohms)
5 Rc = Re
6 Rs = 600 //source resistance(
    ohms)
7 Rl = 2*10^3 //load resistance(ohms
    )
8 beta = 100 //common emitter
    current gain
9 rpi = 1*10^3 //dynamic junction
    resistance(ohms)
10 f = 50 //frequency (Hz)
11
12 //Calculations
13 w = 2*f*(%pi) //corner frequency(rad/s)
14 CE = 1/(w*(Rs+rpi)) //capacitance(uF)
15 Ce = CE*(beta+1) //capacitance(uF)
16 w11 = w/10 //corner frequency
    input circuit (rad/s)
17 w12 = w11/20 //corner frequency
    output circuit(rad/s)
18 Cc1 = 1/(w11*(Rs+rpi)) //coupling capacitor
    1(uF)
19 Cc2 = 1/(w12*(Rc+Rl)) //coupling capacitor
    2 (uF)
20
21 //Results

```

```

22 printf ("Ce is %.f uF", Ce/1E-6)
23 printf ("Cc1 is %.1f uF", Cc1/1e-6)
24 printf ("Cc2 is %.2f uF", Cc2/1E-5)

```

---

#### Scilab code Exa 4.8 Example

```

1
2
3 //Variable declaration
4 gm = 2.5*10^-3 //transconductance (mS)
5 Rd = 6*10^3 //drain resistance (ohms)
6 rd = 200*10^3 //dynamic drain resistance
   (ohms)
7 Cc1 = 0.12*10^-6 //coupling capacitors (uF)
8 Cc2 = Cc1
9 Rs = 1*10^3 //source resistance (ohms)
10 Rg = 0.1*10^6 //R1 || R2
11 Cgs = 12*10^-9 //gate to source capacitor
   (pF)
12 Cgd = 2*10^-9 //gate to drain capacitor (
   pF)
13 Co1 = 10 // as Co1 = C1+Cw = 10
14
15 //Calculations
16 //Part a
17 Ro = (rd*Rd)/(rd+Rd) //equivalent
   resistance of rd and Rd (ohms)
18 Vo = -gm*((rd*Rd)/(rd+Rd)) //as Vgs = Vs
19 Avo = Vo //Avo = Vo/Vs
   = (-gm*Vs*((rd*Rd)/(rd+Rd)))/Vs = Vo
20
21 //Part b
22 f11 = 1/(2*(%pi)*Cc1*(Rs+Rg))
23
24 //Part c

```

```

25 Ceq = Cgs+(Cgd*(1+gm*Ro)) //on
    application of miller theorem
26 Co = Co1+Cgd*(1+(1/(gm*Ro))) //
    output capacitance(pF)
27 f21 = 1/(2*(%pi)*Ceq*((Rs*Rg)/(Rs+Rg))) //input
    circuit cutoff frequency(MHz)
28 f22 = 1/(2*(%pi)*Co*Ro)*10^3 //output
    circuit cutoff frequency(MHz)
29 fH = f22 //
    cutoff frequency of high frequency band(MHz)
30
31 //Results
32 printf ("a)mid freq gain is %.1f",Avo)
33 printf ("b)input circuit cut-off is %.1f Hz",f11)
34 printf ("c)high freq input cutoff is %.2f and output
    cutoff is %.2f MHz",f21/1E+3,f22/1E-3)
35 printf ("high freq cut-off is %.2f MHz",fH/1E-3)

```

---

#### Scilab code Exa 4.9 Example

```

1
2
3 //Variable declaration
4 beta = 50. //common emitter current
    gain
5 R1 = 11.5 //resistance(k ohms)
6 R2 = 41.4 //resistance(k ohms)
7 Vcc = 10. //supply voltage to
    collector(V)
8 Rc = 5. //collector resistance(k
    ohms)
9 Re = 1. //emitter resistance(k ohms)
10 Rs = 1. //source resistance(k ohms)
11 Vbe = 0.7 //base emitter voltage(V)
12 Rl = 10. //load resistance(k ohms)

```

```

13 Cc1 = 20*10^-6.      //coupling capacitors(uF)
14 Cc2 = Cc1
15 Ce = 150*10^-6.      //emitter capacitor(uF)
16 Cpi = 100
17 Cu = 5.
18
19 // Calculations
20 //Part a
21 Rb = (R1*R2)/(R1+R2)      //R1||R2(k ohms
    )
22 Vbb = Vcc*(R1/(R1+R2))    //suply voltage
    to base(V)
23 Ib = (Vbb-Vbe)/(Rb+(Rs*(1+beta))) //base current(
    mA)
24 Ic = beta*Ib              //collector
    current(mA)
25 Vce = Vcc-(Ic*Rc)-(Ic+Ib)*Re //collector to
    emitter voltage(V)
26 rpi = (25*beta)*10^-3/Ic   //dynamic
    junction resistance(K ohms)
27
28 //Part b
29 rpi = 1                    //dynamic
    junction resistance(K ohms)
30 R = (rpi*Rb)/(rpi+Rb)     //equivalent
    resistance(rpi||Rb)
31 Vbe = (R*Rs)/(R+Rs)       //base to
    emitter voltage(V)
32 Ib1 = Vbe/rpi            //base current(
    mA)
33 Ro = (Rc*Rl)/(Rc+Rl)     //Rc||Rl(k ohms
    )
34 Vo = -(beta*Ib1*Ro)       //output voltage
    (V)
35 Avo = Vo                  //voltage gain
36
37 //Part c
38 r1 = (Rs*Rb)/(Rs+Rb)     //Rs||Rb(k ohms)

```

```

39 w11 = 1/(Cc1*(Rs+R))           //low freq
    cutoff(rad/s)
40 w12 = 1/(Cc2*(Rc+Rl))         //high freq
    cutoff(rad/s)
41 w1p = 1/((Ce/(beta+1))*(r1+rpi)) //low cutoff freq
    (rad/s)
42
43 //Part d
44 Co1 = 5                       //as Co1 = Cw+Cl
45 gm = beta/rpi                 //transconductance(
    mS)
46 Ceq = Cpi+(Cu*(1+(gm*Ro)))    //equivalent
    capacitance(pF)
47 Rs1 = (Rb*Rs)/(Rb+Rs)         //Rb||Rs(k ohms)
48 r2 = (Rs1*rpi)/(Rs1+rpi)      //Rs1||rpi(k ohms)
49 w21 = 10^12/(Ceq*r2*10^3)     //low freq
    cutoff(MHz)
50
51 //Results
52 printf ("a)dc bias values are Vbb : %.2f V, Ib : %.4
    f mA, Ic : %.2f mA, Vce : %.3f V, rpi : %.f k
    ohms",Vbb,Ib,Ic,Vce,rpi)
53 printf ("mid freq gain is %.2f ",Avo)
54 printf ("low freq cut-off is %.f rad/s",w1p/1E+3)
55 printf ("high cut-off freq is %.2e rad/s",w21)

```

---

#### Scilab code Exa 4.10 Example

```

1
2
3 //Variable declaration
4 Qcoil = 75.                   //coil inductance
5 f = 200.                       //frequency(Hz)
6 BW = 4.                         //bandwidth(kHz)
7 C = 470*10^-9.                 //capacitance(pF)

```

```

8
9 // Calculations
10 // Part a
11 Qcircuit = f/BW // circuit
    inductance
12 L = 1/(((2*(%pi)*f)^2)*C) // inductance (mH)
13
14 // Part b
15 R = Qcircuit*2*(%pi)*f*L // resistance (k ohms)
16
17 // Part c
18 r = (2*(%pi)*f*L)/Qcoil // internal
    resistance (ohms)
19 req = (Qcoil^2)*r // equivalent
    resistance (k ohms)
20 ro = (R*req)/(req-R) // output
    resistance (k ohms)
21
22 // Part d
23 BW = 5 // bandwidth (kHz
    )
24 Qcircuit = f/BW // circuit
    inductance
25 Req = Qcircuit*2*(%pi)*f*L // equivalent
    resistance (k ohms)
26 Rl = (Req*R)/(R-Req) // load
    resistance (k ohms)
27
28 // Results
29 printf ("a) coil inductance is %.2f mH",L)
30 printf ("b) circuit output impedance at resonant freq
    is %.2f K ohms",R/1E+3)
31 printf ("c) internal resistance ro is %.2f k ohms",ro
    /1E+3)
32 printf ("d) value of load resistance is %.2f k ohms",
    Rl/1E+3)

```

---

### Scilab code Exa 4.11 Example

```
1
2
3 //Variable declaration
4 fo = 50 //output frequency
   (KHz)
5 L = 10^-3 //inductance(H)
6 ro = 100 //output
   resistance(k ohms)
7 Q = 80 //coil inductance
8 Ri = 10 //input resistance
   (k ohms)
9 beta = 125 //common emitter
   current gain
10
11 //Calculations
12 //Part a
13 C = 1/(((2*(%pi)*fo)^2)*L) //tunning capacitance(
   nF)
14 r = (2*(%pi)*fo*L)/Q //internal resistance
   (k ohms)
15 req = (Q^2)*r //equivalent
   resistance(k ohms)
16 R = (ro*req)/(ro+req) //ro || req(k ohms)
17 Avo = -(beta*R)/Ri //voltage gain
18
19 //Part b
20 Qcircuit = R/(2*(%pi)*fo*L) //circuit inductance
21 BW = fo/Qcircuit //bandwidth
22
23 //Results
24 printf ("a) value of capacitance is %.f nF",C/1E-3)
25 printf (" gain is %.1f",Avo)
```

```
26 printf ("b)bandwidth is %.f Hz",BW/1E-3)
27 printf ("Note : value used for beta in textbook is
    wrong in the solution")
```

---

#### Scilab code Exa 4.12 Example

```
1 //Variable declaration
2
3 f = 1*10^6 //radio frequency(Hz)
4 beta = 50 //common emitter
    current gain
5 fT = 5*10^6 //short circuit current
    gain bandwidth product(Hz)
6
7 //Calculations
8 betaf = fT/f //measurement of short
    circuit current gain
9 fbeta = fT/beta //frequency at beta(Hz)
10
11 //Results
12 printf ("frequency is %.f Hz",fbeta)
13 if fbeta<1*10^6 then
14     printf ("transistor is not suitable for 1Mhz
        amplifier as fbeta is less than 1Mhz")
15 else
16     printf ("transistor is suitable for 1Mhz
        amplifier")
17 end
```

---

#### Scilab code Exa 4.13 Example

```
1
2
```

```

3 //Variable declaration
4 rpi = 2 //dynamic junction
   resistance(K ohms)
5 beta = 50. //common emitter
   current gain
6 f = 1 //frequency(MHz)
7 beta1 = 2.5 //common emitter
   current gain
8 f1 = 20*10^6 //frequency(Hz)
9
10 //Calculations
11 fT = beta1*f1 //short circuit
   current gain bandwidth product(Hz)
12 fbeta = fT/beta //frequency at beta(
   Hz)
13 Cpi = 1/(2*(%pi)*fbeta*rpi) //dynamic capacitance(
   pF)
14
15 //Results
16 printf ("fT is %.f MHz",fT/1e+6)
17 printf ("fB is %.f MHz",fbeta/1e+6)
18 printf ("Cpi is %.f pF",Cpi/1e-9)

```

---

#### Scilab code Exa 4.14 Example

```

1
2
3 //Variable declaration
4 R1 = 60 //resistance(k ohms)
5 R2 = 140 //resistance(k ohms)
6 Rs = 4 //source resistance(k ohms)
7 Re = 3 //emitter resistance(k ohms)
8 Rc = 4 //collector resistance(k
   ohms)
9 Vcc = 10 //supply voltage to

```

```

    collector(V)
10 Vbe = 0.7 //base to emitter voltage(V)
11 beta = 100 //common emitter current
    gain
12 Av0 = -30 //voltage gain
13
14 //Calculations
15 //Part a
16 Rb = (R1*R2)/(R1+R2) //R1||R2(k
    ohms)
17 Vth = (Vcc*R1)/(R1+R2) //thevinine's
    voltage(V)
18 Ib = (Vth-Vbe)/(Rb+(beta+1)*Re) //base current
    (uA)
19 Ic = Ib*beta //collector
    current(mA)
20 Vce = Vcc-(Rc*Ic)-((beta+1)*Ib*Re) //collector to
    emitter voltage(V)
21
22 //Part b
23 rpi = ((25*beta)/Ic)*10^-3 //dynamic
    junction resistance(k ohms)
24 r = (Rb*rpi)/(Rb+rpi) //resistance
    across Vs
25 Ib1 = r/((Rs+r)*rpi) //base current(
    mA)
26 Rl = (-Rc*Av0)/(Av0+(beta*Ib1*Rc)) //load
    resistance(k ohms)
27
28 //Results
29 printf ("value of Ic and Vce are %.3f mA and %.2f V"
    ,Ic,Vce)
30 printf ("Rl is %.2f k ohms",Rl)

```

---

Scilab code Exa 4.15 Example

```

1
2
3 //Variable declaration
4 R1 = 25. //resistances(k ohms)
5 R2 = 100. //resistances(k ohms)
6 Re = 2. //emitter resistance(k
    ohms)
7 Vcc = 10. //supply voltage to
    collector
8 Vbe = 0.7 //base to emitter
    voltage(V)
9 beta = 100. //common emitter
    current gain
10 Av0 = 160 //voltage gain
11 Rs = 1 //source resistance(k
    ohms)
12 Vs = 1 //source voltage(V)
13 Rl = 12.5 //load resistance(k
    ohms)
14 Rc1 = 20. //collector resistance
    (k ohms)
15
16 //Calculations
17 //Part a
18 Rb = (R1*R2)/(R1+R2) //R1||R2
19 Vth = (Vcc*R1)/(R1+R2) //thevinines
    voltage(V)
20 Ib = (Vth-Vbe)/(Rb+(beta+1)*Re) //base current(uA)
21 Ic = Ib*beta //collector
    current(mA)
22 rpi = (25*beta)*10^-3/Ic //dynamic
    junction resistance(k ohms)
23
24 //Part b
25 Ib1 = 1/rpi //small signal
    analysis
26 Rc = -Av0/(-beta*Ib1) //collector
    resistance()

```

```

27
28 //Part c
29 r = (Rc1*rpi)/(Rc1+rpi)           //Rc1 || rpi1 (k
    ohms)
30 Ib2 = (Vs*r)/((1+r)*rpi)         //base curret
    (mA)
31 Rc2 = 6.84                       //collector
    resistance(k ohms)
32 Av0 = -(beta*Ib2)*((R1*Rc2)/(R1+Rc2)) //voltage
    gain
33
34 //Results
35 printf ("value of Ic %.3f mA and rpi is %.2f k ohms"
    ,Ic,rpi)
36 printf ("Rc is %.2f k ohms",Rc)
37 printf ("Av0 is %.1f",Av0)

```

---

#### Scilab code Exa 4.16 Example

```

1 //Variable declaration
2 R1 = 12.           //resistance(k ohms)
3 R2 = 100.         //resistance(k ohms)
4 Rc = 2            //collector resistance(k
    ohms)
5 Ic = 1.2          //collector current(mA)
6 beta = 60         //common emitter current
    gain
7 Ib1 = 1           //(say)
8 Rs = 1            //source resistance(k ohms)
9 Vs = 1            //source vcoltage(say)
10
11 //Calculations
12 //Part a
13 rpi = ((25*beta)/Ic)*10^-3       //dynamic junction
    resistance(k ohms)

```

```

14 Rb = (R1*R2)/(R1+R2)           //R1||R2(k ohms)
15 r = (Rb*rpi)/(Rb+rpi)        //Rb||rpi(k ohms)
16 Ro1 = (Rc*rpi)/(Rc+rpi)      //Rc||rpi(k ohms)
17 Vo1 = -(beta*Ib1*Ro1)        //base to emitter
    voltage(V)
18 Vbe2 = Vo1
19 Ib2 = Vo1/rpi                 //base current(mA)
20 Ai = Ib2/Ib1                 //current gain
21
22 //Part b
23 Ib11 = (Rs*r)/((Rs+r)*rpi)   //base currents(
    mA)
24 Ib21 = Ib11*Ai               //base current(mA)
25 Avo1 = Ib21*rpi              //voltage gain
26 Vo1 = Avo1
27
28 //Results
29 printf ("current gain is %.2f",Ai)
30 printf ("overall voltage gain is %.2f",Avo1)
31 printf ("Note : solution in the textbook is
    incorrect")

```

---

#### Scilab code Exa 4.17 Example

```

1 //Variable declaration
2 beta = 50.                    //common emitter current
    gain
3 R1 = 25.                      //resistance(k ohms)
4 R2 = 75.                      //resistance(k ohms)
5 Ic = 1.25                     //collector current(mA)
6 Vcc = 10                      //supply voltage to
    collector(V)
7 s = 10*10^-3                 //signal strength(V)
8 Rs = 0.5                      //output impedance(k ohms)
9 Vo = 1                       //output voltage(V)

```

```

10 Vs = 1.                //source voltage(V)
11 V1 = 12                //load at output terminal(
    V1)
12 Vbe = 0.7             //base to emitter voltage(
    V)
13 R1 = 12
14
15 //Calculations
16 rpi = ((25*beta)/Ic)   //dynamic junction
    resistance(k ohms)
17 Rb = (R1*R2)/(R1+R2)   //R1||R2(k ohms)
18 r = (Rb*rpi*10^-3)/(Rb+rpi*10^-3) //Rb
    || rpi(k ohms)
19 Avo = ((Vo*rpi)/Vcc)   //voltage
    gain
20 Ib = (r*Vs)/(Rs+r)*Vs //base
    current(mA)
21 Rc = (R1*Avo)/(beta*Ib*R1-Avo) //collector
    resistance(k ohms)
22 Vth = (Vcc*R1)/(R1+R2) //thevinine
    's voltage(V)
23 Ib1 = Ic/beta         //base
    current(mA)
24 Re = (Vth-Vbe-(Rb*Ib1))/((beta+1)*Ib1) //emitter
    resistance(k ohms)
25
26 //Results
27 printf ("value of Rc is %.2f and Re is %.2f k ohms",
    Rc,Re)
28 printf (" Vth value is wrong substituted in the book
    ")

```

---

Scilab code Exa 4.18 Example

1

```

2
3 //Variable declaration
4 Cpi = 20*10^-9 //opening capacitor(F)
5 Cu = 5*10^-9
6 C = 50*10^-9 //here C = C1+Cw
7 rpi = 3.75*10^3 //dynamic drain resistance(
    ohms)
8 r1 = 4*10^3 //resistance(ohms)
9 r2 = 42*10^3 //resistance(ohms)
10 r3 = 303*10^3 //resistance(ohms)
11 f = 20 //frequency(Hz)
12 beta = 100 //common emitter current
    gain
13 Rl = 10*10^3 //load resistance(ohms)
14
15 //Calculations
16 //Part a
17 Req = (((r1*r2)/(r1+r2)+rpi)*r3)/(((r1*r2)/(r1+r2)+
    rpi)+r3) //equivalent resistance(ohms)
18 Ce = (beta+1)/(2*(%pi)*f*Req) //emitter capacitance
    (uF)
19
20 //Part b
21 gm = beta/rpi //transconductance
22 Ro = (Rl*r1)/(r1+Rl) //output resistance
    (k ohms)
23 Ceq = Cpi+(Cu*(1+gm*Ro)) //equivalent
    capacitance(pF)
24 Co = C+(Cu*(1+(1/(gm*Ro)))) //output
    capacitance(pF)
25 r = (rpi*r1)/(rpi+r1) //rpi || r1
26 w21 = 1/(Ceq*r) //lower cutoff
    frequency(MHz)
27 w22 = 1/(Co*Ro) //higher cutoff
    frequenct(MHz)
28
29 //Part c

```

```

30 gm = 79.2
31 Ro = 0.75
32 Ceqnew = 20+(5*(1+((gm*Ro))))           //as gain is
    reduced to 75% of original value
33 wHnew = (10^12)/(Ceqnew*r)/10**6
    //corner value of high frequency(Mrad/s)
34 fHnew = wHnew/(2*(%pi))                 //new
    value of higher frequency cutoff(KHz)
35
36 //Results
37 printf ("a)value of bypass capacitor Ce is %.f uF",
    Ce/1E-6)
38 if w21>w22 then
39     printf ("higher frequency is w21")
40 else
41     printf ("higher frequency is w22")
42 end
43
44 printf ("b)high frequency cut-off is %.2f Mrad/s",
    w22/1E+3)
45 printf ("c)high frequency cut-off is %.3f MHz",fHnew
    )

```

---

#### Scilab code Exa 4.19 Example

```

1
2
3 //Variable declaration
4 Vcc = 3.           //supply voltage to
    collector(V)
5 Vee = -3.         //supply voltage to
    emitter(V)
6 r1 = 40.          //resistance(ohms)
7 r2 = 25.          //resistance(ohms)
8 r3 = 1.56         //resistance(ohms)

```

```

9 Vs = 3. //source voltage(V)
10 beta = 200 //common emitter current
    gain
11 r4 = 0.6 //resistance(ohms)
12 r5 = 0.15 //resistance(ohms)
13 Vbe = 0.7 //base to emitter
    voltage
14 r = 0.5 //resistance(k ohms)
15 fL = 20 //frequency(Hz)
16 Req1 = 24.24 //solving r || (Rth+rpi+R
    ) || Re
17 f = 2 //non dominant cutoff
    freq is fL/10 i.e 20/10
18
19 //Calculations
20 //Part a
21 Vth = Vs-(((Vcc-Vee)/(r1+r2))*r1) //
    thevinine 's voltage(V)
22 Rth = (r1*r2)/(r1+r2) //
    thevinine 's voltage(V)
23 Ib = (Vth-Vbe+Vcc)/(Rth+((r4+r5)*(beta+1))) //base
    current(mA)
24 Ic = Ib*beta //
    Collector current(mA)
25 Vo = Vcc-(r3*Ic) //
    output voltage(V)
26
27 //Part b
28 rpi = (25*beta)/Ic //
    dynamic drain resistance(ohms)
29 R = r4*(beta+1) //
    resistance(k ohms)
30 ro = (rpi*R)/(rpi+R) //rpi ||
    R(k ohms)
31 Req = r+((Rth*ro)/(Rth+ro)) //
    equivalent resistance(k ohms)
32 Cc1 = 1/(Req*2*(%pi)*fL) //coupling
    capacitor(uF)

```

```

33
34 //Part c
35 Ce = 1/(2*(%pi)*fL*Req1) //emitter
    capacitance(uF)
36 CE = beta*Ce //emitter
    capacitance(uF) after current gain
37
38 //Part d
39 Ce1 = 1/(2*(%pi)*f*Req1) //emitter
    capacitance(uF)
40 CE1 = beta*Ce1 //emitter
    capacitance(uF) after current gain
41 Csum = Cc1+CE1 //total
    capacitance(uF)
42
43 //Results
44 printf ("a)Ic and Vo are %.2f mA and %.f V",Ic,Vo)
45 printf ("b)Cc1 is %.3f uF",Cc1/1E-3)
46 printf ("c)Ce is %.1f uF",CE/1E-3)
47 printf ("d)Csum is %.3f uF",Csum/1E-2)

```

---

#### Scilab code Exa 4.21 Example

```

1
2
3 //Variable declaration
4 gm = 2 //transconductance
5 rd = 200*10^3 //dynamic drain resistance(
    ohms)
6 Cgs = 10 //gate to source
    capacitance(pF)
7 Cgd = 0 //gate to drain capacitance
    (pF)
8 Rs = 1*10^3 //source resistance(ohms)
9 Rg = 1*10^6 //Rg = R1||R2

```

```

10 Rd = 5*10^3           //drain resistance(ohms)
11 Rs1 = 2              //resistance(k ohms)
12 Cc1 = 0.1*10^-6     //coupling capacitors(F)
13 Cc2 = Cc1
14 Co = 10*10^-12      //output capacitance(F)
15 Vgs = 1              //gate to source voltage(V)
16
17 // Calculations
18 //Part a
19 R = (Rd*rd)/(Rd+rd) //Rd||rd(k ohms)
20 Avo = -Vgs*gm*R      //voltage gain
21 Vo = Avo
22
23 //Part b
24 w11 = 1/(Cc1*(Rs*Rg)) //corner freq(rad/s)
25 wL = w11             //input circuit
    corner freq(rad/s)
26
27 //Part c
28 w22 = 10^12/((Cgs*R)*10^3) //output circuit
    corner frequency(rad/s)
29 wH = w22/(2*%pi)
30
31 //Part d
32 G = -Avo*wH          //gain bandwidth
    product
33
34 //Part e
35 Rd = 4*10^3          //drain resistance
    reduced(ohms)
36 Rnew = (Rd*rd)/(Rd+rd) //new resistance(
    ohms)
37 Avo1 = -Vgs*gm*Rnew //new voltage gain
38 BWnew = (10^8/Rnew)/(2*%pi) //new
    bandwidth(Mrad/s)
39 Gnew = -Avo1*BWnew //gain bandwidth
    product new
40

```

```

41 //Results
42 printf ("a)Avo is %.2 f" ,Avo/1E+3)
43 printf ("b)wL is %.2 f rad/s" ,wL/1E-3)
44 printf ("c)wH is %.1 f MHz" ,wH/1E+3)
45 printf ("d)G is %.2 f MHz" ,G/1E+6)
46 printf ("e)Gnew is %.1 f MHz" ,Gnew/1E+6)

```

---

### Scilab code Exa 4.23 Example

```

1
2
3 //Variable declaration
4 gm = 1 //transconductance
5 rd = 40 //dynamic drain resistance
   (k ohms)
6 Cgs = 5 //gate to source
   capacitance(pF)
7 Cgd = 1 //gate to drain
   capacitance(pF)
8 Cds = 1 //drain to source
   capacitance(pF)
9 Avo1 = 20. //voltage gain of JFET 1
10 Avo2 = 8. //voltage gain of JFET 2
11 R1 = 5 //resistance(k ohms)
12 R2 = 20 //resistance(k ohms)
13 R3 = 8 //resistance(k ohms)
14
15 //Calculations
16 //Part a
17 Avo = Avo1*Avo2 //voltage gain
18 Ceq1 = Cgs+Cgd*(1+Avo1) //input circuit for
   first JFET
19 Co1 = Cds+(Cgd*(1+(1/Avo1))) //output circuit for
   first JFET
20 Ceq2 = Cgs+Cgd*(1+Avo2) //input circuit for

```

```

    second JFET
21 Co2 = Cds+(Cgd*(1+(1/Avo2))) //output circuit for
    second JFET
22
23 //Part b
24 w21 = 1/(R1*Ceq1) //input circuit
    frequency
25 w2 = 10^12/(R2*10^3*(Co1+Ceq2)) //common
    circuit frequency
26 w22 = 1/(R3*Co2) //output circuit
    frequency
27
28
29 //Results
30 printf ("a)Avo is %.1f",Avo)
31 printf ("b)w21,w2,w22 are %.2f Mrad/sec , %.2f Mrad/
    sec and %.2f Mrad/sec",w21/1E-3,w2/1E+6,w22/1E-3)
32 printf ("nondominant corner freq is %.2f Mrad/sec",
    w2/1E+6)

```

---

# Chapter 5

## Large Signals Amplifiers

Scilab code Exa 5.1 Example

```
1
2
3 //Variable declaration
4 Rb=1*10**3 //base resistance (ohms
   )
5 Vcc=20 //supply voltage(V)
6 Rc=20 //collector resistance
   (ohms)
7 beeta=25 //current gain
8 Vbe=0.7 //base to emitter
   voltage(V)
9 ib=10*10**-3 //base current (ohms)
10
11 //Calculations
12 Ibq=(Vcc-Vbe)/Rb //current (A)
13 Icq=beeta*Ibq //current (A)
14 Vceq=Vcc-(Icq*Rc) //collector voltage(V
   )
15 ic=beeta*ib //collector current(A
   )
16 Po=((ic/(sqrt(2)))**2)*Rc //output voltage(V)
```

```

17 Pi=Vcc*Icq //input power(W)
18 eta=(Po/Pi)*100 //efficiency
19 Pd=Pi-((Icq**2)*Rc)-Po //power dissipated(W)
20
21 //Results
22 printf ("input power is Pi %.1f W",Pi)
23 printf ("output power is Po %.1f W",Po)
24 printf ("power dissipated is %.1f W",Pd)

```

---

### Scilab code Exa 5.2 Example

```

1
2
3 //Variable declaration
4 Rl=500 //load resistance(
   ohms)
5 Vceq=50 //queinscent
   collector voltage(V)
6 beetamin=30 //current gain
   minimum(at Q)
7 Icq=0.4 //queinscent
   collector current(A)
8 Ibq=8 //queinscent base
   current(mA)
9
10 //Calculations
11 Rac=Vceq/Icq //ac resistance(
   ohms)
12 beeta=(Icq*10**-3)/Ibq //current gain
13 Re=5/Icq //emitter
   resistance(ohms)
14 Rc=(512.5*Rac)/(512.5-Rac) //as Re+Rl
   =500+12.5=512.5
15 Vcc=5+Vceq+(Icq*Rc) //supply voltage(
   V)

```

```

16 Rb=(betamin*Re)/10 //base resistance
    (ohms)
17 R1=39.5 //solving 125=Rc
    |(R1+Re) and Vbb=Vcc*(R1/(R1+R2))
18 R2=750
19 Pi=120*Icq //Vcc chosen as
    120
20 r=(Rc*R1)/(Rc+R1)
21 Poac=(100/(2*sqrt(2)))**2/r //output power(W)
22 etamax=Poac/Pi //efficiency
23 Poac1=(100/(2*sqrt(2)))**2/R1 //ac power absorbed by
    load (W)
24 eta=Poac1/Pi
25 Pc=(Icq**2)*Rc //power lost in Rc(W
    )
26 Pe=(Icq**2)*Re //power lost in Re(W
    )
27 Pd=Pi-Pc-Pe-Poac //power consumed(W
    )
28
29 //Results
30 printf("input power is Pi %.1f W",Pi)
31 printf("output power is Po %.2f W",Poac)
32 printf("dissipated power is %.2f W",Pd)
33 printf("values of R1,R2,Re and Rc are %.1f ohms, %
    .1f ohms, %.1f ohms and %.f ohms resp.",R1,R2,Re,
    Rc)
34 printf("Note : Calculated value of Rc is wrong in
    the book")

```

---

### Scilab code Exa 5.3 Example

```

1
2
3 //Variable declaration

```

```

4 Pmax=10 //power maximum(W)
5 Ic=1 //collector current(
  A)
6 Vcemax=100 //max collector to
  emitter current(V)
7 Vcemin=2 //min collector to
  emitter current(V)
8
9 //Calculations
10 //Part a
11 Vceq=46 //Vce at Q point
12 Icq=0.21 //Ic at Q point
13 Vcc=92 //supply voltage(V)
14 ic=0.42 //collector current(A)
15
16 //Part b
17 Rl=Vceq/Icq //load resistance(
  ohms)
18
19 //Part c
20 Pi=Vcc*Icq //input power(W)
21 Po=((ic/(2*sqrt(2)))**2)*Rl //output power(W)
22 eta=(Po/Pi)*100 //efficiency
23
24 //Results
25 printf ("Rl for maximum power input is %.f ohms",Rl)
26 printf ("input power is is %.1f W",Pi)
27 printf ("Po is %.1f",Po)
28 printf ("eta is %.1f %%",eta)

```

---

#### Scilab code Exa 5.4 Example

```

1
2
3 //Variable declaration

```

```

4 Vcc=15 //supply voltage(V)
5 beeta=40. //current gain
6 Icq=5. //Ic at Q(mA)
7 Vceq=7.5 //Vce at Q(V)
8 icswing=10 //swing in ic(mA)
9
10 // Calculations
11 //Part a
12 Rl=Vceq/Icq*10**-3 //load resistance(ohms)
13
14 //Part b
15 Ibq=Icq/beeta //base current at Q(uA)
16
17 //Part c
18 ibswing=icswing/beeta //swing in
    ib(mA)
19 Pac=Rl*(icswing/(2*sqrt(2)))**2 //ac power(W)
20 Pdc=Vcc*(Icq*10**-3) //dc power(W)
    )
21 eta=(Pac/Pdc)*100 //efficiency
22
23 // Results
24 printf ("a) value of Rl is %.f ohms",Rl/1E-6)
25 printf ("b) Ibq is %.f uA",Ibq/1E-3)
26 printf ("c) ac power output is %.2f mW",Pac/1E-3)
27 printf ("efficiency is %.1f %%",eta)
28 printf ("corresponding swing in ib is %.2f mA",
    ibswing)

```

---

### Scilab code Exa 5.5 Example

```

1
2
3 //Variable declaration
4 Vcc=10 //supply voltage(V)

```

```

5 Vce=10
6 Icq=140*10**-3           //Ic at Q point(A)
7 Rl=8                     //load resistance(ohms)
8 vce=16                   //instantaneous
    collector to emitter voltage(V)
9 ic=235*10**-3           //instantaneous
    collector current(A)
10
11 //Calculations
12 RL=Vcc/Icq
13 r=sqrt(RL/Rl)           //load
    resistance for max ac swing(ohms)
14 Po=(vce*ic)/(2*sqrt(2)*2*sqrt(2)) //output power(
    W)
15 Pi=Vcc*Icq             //
    input power(W)
16 eta=Po/Pi              //
    efficiency
17 Pd=Pi-Po              //
    dissipated power(W)
18
19 //Results
20 printf ("a)transformation ratio is %.f",r)
21 printf ("c)power output is %.2f W",Po)
22 printf ("efficiency is %.2f %%",eta*100)

```

---

### Scilab code Exa 5.6 Example

```

1
2
3 //Variable declaration
4 Rl=4.5                   //load resistance(ohms)
5 Vceq=50                 //Vc at point Q(V)
6 Icq=400*10**-3         //Ic at Q(A)
7 Re=12.5                 //emitter resistance(ohms)

```

```

8 Vcemax=90 //from figure
9 Vcemin=10 //from figure
10 Icmax=730 //max Ic (mA)
11 Icmin=30 //min Ic (mA)
12
13 // Calculations
14 //Part a
15 Rac=Vceq/Icq //ac resistance (ohms)
16 n=sqrt(Rac/Rl) //as n=N1/N2 and Rac=(N1/N2)
    ^2*Rl
17
18 //Part b
19 Vcc=Vceq+(Icq*Re) //supply voltage (V)
20
21 //Part c
22 vce=Vcemax-Vcemin
    //
    instantaneous collector to emitter voltage (V)
23 ic=Icmax-Icmin
    //
    instantaneous collector current (mA)
24 Po=(vce*ic)/((2*sqrt(2))*(2*sqrt(2))) //output
    voltage (V)
25 Pi=Vcc*Icq //input
    voltage (V)
26 eta=(Po/Pi)*100 //efficiency
27 Pd=Pi-(Icq**2*Re)-Po*10**-3 //dissipated power (W)
28
29 // Results
30 printf ("a)transformation ratio is %.2f",n)
31 printf ("b)Vcc is %.1f V",Vcc)
32 printf ("c)power efficiency for the load is %.1f %%"
    ,eta/1E+3)
33 printf ("power dissipated is %.1f W",Pd)

```

---

### Scilab code Exa 5.7 Example

```
1
2 //Variable declaration
3 Vcc=30 //supply voltage(V)
4 Rl=16 //load resistance(ohms
   )
5 n=2 //transformation ratio
6 Im=1 //peak value of
   current(A)
7 etamax=78.54 //max efficiency(%)
8
9 //Calculations
10 //Part a
11 Rl1=Rl*(n/2)**2 //load resistance(
   ohms)
12 Pi=(2*Vcc*Im)/%pi //input power(W)
13 Pimax=(2*Vcc**2)/((%pi)*Rl1) //input power max(W)
14
15 //Part b
16 Po=((Im**2)*Rl1)/2 //output power(W)
17 Pomax=(Vcc**2)/(2*Rl1) //output power max(
   W)
18
19 //Part c
20 eta=Po/Pi //efficiency
21
22
23 //Part d
24 P=((2*Vcc*Im)/%pi)-((Im**2*Rl1)/2) //Power
   dissipated by transistors(W)
25 Pd=P/2 //power
   dissipated by each transistors
26 Pmax=(2*Vcc**2)/((%pi)**2*Rl1) //max power
```

```

    dissipated by transistors
27 Pdmax=Pmax/2 //max power
    dissipated by each transistor
28
29 //Results
30 printf ("a)input power is %.1f W and max input
    power is %.2f W",Pi,Pimax)
31 printf ("b)output power %.1f W and max output power
    is %.2f W",Po,Pomax)
32 printf ("c)power efficiency for the load is %.2f %%
    and its max value is %.2f %%",eta/1E-2,etamax)
33 printf ("power dissipated by each transiator is %.1f
    W and max value is %.1f W",Pd,Pdmax)

```

---

#### Scilab code Exa 5.8 Example

```

1
2 //Variable declaration
3 Pd=10
4
5 //Calculations
6 //Part a
7 Poacmax=10. //as Pd=Po(ac)max by
    class A
8
9 //Part b
10 Pd=2*Poacmax //power dissipated (W)
11 Poacmax1=146/2 //max output power by
    class B
12 f=Poacmax1/Poacmax //factor by which power
    of class B is greater than class A
13
14 //Results
15 printf ("maximum signal output powerclass A produce
    is %.1f W",Poacmax)

```

```

16 printf ("maximum signal output powerclass produce
    is %.1f W",Poacmax1)
17 printf ("factor by which power in class b is larger
    than power in class A transformer is %.1f",f)

```

---

### Scilab code Exa 5.9 Example

```

1
2
3 //Variable declaration
4 Vcc=30. //supply voltage(V)
5 Im=1 //peak value of
    current(A)
6 Rl=10. //load resistance(
    ohms)
7
8 //Calculations
9 //Part a
10 Pi=(Vcc*Im)/%pi //input power(W)
11 Pimax=(Vcc**2)/(%pi*2*Rl) //max input power(W)
12
13 //Part b
14 Po=((Im**2)*Rl)/2 //output power(W)
15 Pomax=(Vcc**2)/(8*Rl) //output power max(W)
    )
16
17 //Part c
18 eta=Po/Pi //efficiency
19 etamax=Pomax/Pimax //efficiency max
20
21 //Part d
22 Pd=Pi-Po //Power
    dissipated by transistors(W)
23 Pmax=(Vcc**2)/(2*(%pi)**2*Rl) //max power
    dissipated by transistors

```

```

24
25 // Results
26 printf ("a)input power is %.2f W and max input power
        is %.2f W",Pi,Pimax)
27 printf ("b)output power is %.1f W and max output
        power is %.2f W",Po,Pomax)
28 printf ("c)power efficiency for the load is %.2f %%
        and its max value is %.2f %%",eta/1E-2,etamax/1E
        -2)
29 printf ("power dissipated and its max value are %.2f
        W and %.2f W",Pd,Pmax)

```

---

#### Scilab code Exa 5.10 Example

```

1
2
3 // Variable declaration
4 P1=2 //transistor power(W)
5 R1=5*10**3. //load resistance ()
6 Ic=35 //collector current(mA
    )
7
8 // Calculations
9 Bo=40-Ic
10 B1=sqrt((2*P1)/R1)
11 B2=Bo
12 D2=(B2/B1)*100 //second harmonic
    distortion (%)
13
14 // Results
15 printf ("second harmonic distortion is %.2f %%", (D2
    /1E+3))

```

---

### Scilab code Exa 5.12 Example

```
1
2
3 //Variable declaration
4 Vcc=15. //supply voltage(
   V)
5 Rl=10. //load resistance
   (ohms)
6
7 //Calculations
8 //Part a
9 Immax=Vcc/Rl //max peak current
   (A)
10 Irmsmax=Immax/(sqrt(2)) //max rms current(A)
11 Pomax=Irmsmax**2*Rl //max output power
   (W)
12 Pi=(2*Vcc*Immax)/%pi //max input power(W)
13 eta=Pomax/Pi //efficiency
14
15 //Part b
16 Im=(2*Vcc)/(%pi*Rl) //peak
   current(A)
17 Pdmmax=((2*Vcc*Im)/(%pi))-((Im**2*Rl)/2) //max
   power dissipated(W)
18 eta1=((Im**2)*Rl*%pi)/(2*2*Vcc*Im) //
   efficiency
19
20 //Results
21 printf ("a)max signal output power, collector
   dissipation are %.2f W , %.2f W and efficiency
   is %.2f %%", Pomax, Pi, eta/1E-2)
22 printf ("b)max dissipation of each transistor and
   corresponding efficiency is %.2f W and %.1f resp.
   ", Pdmmax, eta1)
```

---

### Scilab code Exa 5.13 Example

```
1 // Calculations
2 eta=0.5 //As  $Po(ac)=Vcc^2/2*\pi^2*Rl$  and
    $Pi(dc)=Vcc^2/\pi^2*Rl$ 
3 //put these in  $eta=Po(ac)/Pi(dc)$ 
   which is  $1/2=0.5$ 
4
5 // Results
6 printf ("push pull amplifier efficiency is %.f %%",
   eta/1E-2)
```

---

# Chapter 6

## Feedback Amplifiers And Oscillators

Scilab code Exa 6.1 Example

```
1 //Variable declaration
2 Vo=12.           //output voltage (V)
3 f=1.5*10**3     //frequency (Hz)
4 h=0.25          //second harmonic content (%)
5 ho=2.5          //reduced harmonic content of
   output (%)
6 A=100           //power amplifier gain
7
8 //Calculations
9 Vd=Vo*h         //second harmonic content in
   output (V)
10 Vd1=Vo*ho      //reduced value of second
   harmonic content (V)
11 beta=((Vd1/Vd)-1)/A //feedback gain from formula
   Vd1=Vd/(1+beta*A)
12 Vs=Vo*(1+beta*A)/A //signal voltage (V) from
   formula (A/(1+Beta*A))*Vs
13 V=Vo/A         //signal input needed without
   feedback
```

```

14 s=Vs/V //additional signal
    amplification needed before feedback amplifier
15
16 //Results
17 printf ("feedback gain is %.2f",beta)
18 printf ("signal input to the overall system is %.1f"
    ,s)

```

---

### Scilab code Exa 6.2 Example

```

1 //Variable declaration
2 w2=10**4. //corner frequency(rad/s)
3 w2new=10**5. //new corner frequency(rad/s)
4 Ao=1000. //high frequency response
5
6 //Calculations
7 beta=((w2new/w2)-1)/Ao //feedback factor
8 Anew=Ao/(1+beta*Ao) //overall gain of amplifier
    from formula w2new=w2(1+beta*Ao)
9 p=w2*Ao //gain bandwidth product
    without feedback from formula Anew=Ao/1+beta*Ao
10 pnew=Anew*w2new //gain bandwidth product with
    feedback
11
12 //Results
13 printf ("beta is %.3f",beta)
14 printf ("overall gain is %.1f",Anew)
15 printf ("gain-bandwidth products with and without
    feedback are %.1f and %.1f resp.",p,pnew)

```

---

### Scilab code Exa 6.3 Example

```

1 //Variable declaration

```

```

2 A=100. //high frquency
   response
3 Af=100 //gain
4 A1=A**2 //forward gain
5 A1new=50 //gain reduces
   to 50%
6
7 //Calculations
8 beta=((A1/Af)-1)/A1 //feedback
   factor
9 Afnew=A1new**2/(1+beta*A1new**2) //new value of
   A
10 g=Af-Afnew //reduction in
   overall gain
11
12 //Results
13 printf ("%%" change in gain of feedback unit is %.2f
   ",g)

```

---

#### Scilab code Exa 6.4 Example

```

1 //Variable declaration
2 beta=0.008 //positive gain
3
4 //Calculations
5 Ao=-(8/beta)**(1/3) //A=Ao/2,so beta(A^3)
   =-1
6
7 //Results
8 printf ("%%" change in gain of feedback unit is %.f",
   Ao/1E-1)

```

---

#### Scilab code Exa 6.5 Example

```

1
2 //Variable declarations
3 A = complex(0,60)           // amplifier
4 B = complex(0,30)         // amplifier
5 AB = A*B
6 C = (1+A)/AB              //condition for
    oscillation
7 phi = phasemag(C)         //phase
8
9 //Result
10 printf ( "C = %.4f with phase = %.2f ",abs(C),phi)

```

---

#### Scilab code Exa 6.7 Example

```

1 //Variable declaration
2 Rbb=8*10**3                //base resistance(k
    ohms)
3 eta=0.7                   //efficiency
4 R1=0.2                    //R1(k ohms)
5 Rt=40*10**3              //Rt(ohms)
6 Ct=0.12*10**-6          //capacitance(F)
7 Vv=2                      //capacitor is charged
    to voltage(V)
8 Iv=10*10**-3             //current to capacitor(A
    )
9 Ip=10*10**-3             //peak current(A)
10 Vd=0.7                  //diode voltage(V)
11 V=12.                   //voltage(V)
12
13 //Calculations
14 //Part a
15 Rb1=eta*Rbb              //base resistance(ohms)
16 Rb2=Rbb-Rb1             //base resistance(ohms)
17
18 //Part b

```

```

19 Vp=Vd+((Rb1+R1)*V/(Rbb+R1)) //peak voltage (V)
20
21 //Part c
22 Rtmin=(V-Vv)/Iv //Rt minimum(k ohms)
23 Rtmax=(V-Vp)/Ip //Rt minimum(k ohms)
24
25 //Part d
26 Rb11=.12 //resistance during
    discharge(ohms)
27 t1=Rt*Ct*1.27 //charging time(mS)
28 t2=(Rb11+R1)*Ct*1.52 //discharging time(uS)
29 T=t1+t2 //cycle time
30 foscE=1/T //oscillations frequency(Hz)
31 foscA=1/(Rt*Ct*1.2) //oscillations frequency(Hz)
32
33 //Part e
34 vR1=(R1*V)/(R1+Rbb) //vR1 at discharging
    period
35 vR1d=(R1*(Vp-Vd))/(R1+Rb11) //vR1 at
    discharging period
36
37 //Results
38 printf ("Rb1 and Rb2 are %.1f k ohms and %.1f k ohms
    resp.",Rb1/1E+3,Rb2/1E+3)
39 printf ("Vp is %.1f V",Vp)
40 printf ("Rtmin is %.f k ohms and Rtmax is %.f k ohms
    ,hence Rt is in the range",Rtmin/1E+3,Rtmax/1E+1)
41 printf ("foscE is %.f Hz and foscA is %.f Hz",foscE,
    foscA)
42 printf ("vR1 is %.3f and vRd1 is %.2f V ",vR1/1E-3,
    vR1d)
43 printf("(range of Rt is wrong in the book)")

```

---

Scilab code Exa 6.8 Example

```

1 //Variable declaration
2 A=1500 //voltage gain
3 beta=1/25. //current gain
4
5 //Calculations
6 //Part a
7 Af=A/(1+A*beta) //voltage gain with
  feedback
8
9 //Part b
10 g=0.1 //amplifier gain
  changes by 10%=0.1
11 gf=g/(1+A*beta) //% by which its gain
  in feedback mode changes dAf/Af
12
13 //Results
14 printf (" Amplifier gain with feedback is %.1f ",Af)
15 printf ("%%" by which gain in feedback changes is %.3
  f %%",gf/1E-2)

```

---

### Scilab code Exa 6.9 Example

```

1 //Variable declaration
2 A=500 //voltage gain
3 beta=1/20. //current gain
4 Ro=50*10**3 //output resistance(ohms)
5 Ri=1.5*10**3 //input resistance(ohms)
6
7 //Calculations
8 //Part a
9 Af=A/(1+A*beta) //voltage gain with
  feedback
10
11 //Part b
12 Rif=Ri*(1+(A*beta)) //input resistance(k

```

```

    ohms)
13 Rof=Ro/(1+A*beta)           //output resistance (k
    ohms)
14
15 //Results
16 printf ("Amplifier gain is %.2f",Af)
17 printf ("input resistance is %.f K ohms and output
    resistance is %.2f kW",Rif/1E+3,Rof/1E+3)

```

---

### Scilab code Exa 6.10 Example

```

1 //Variable declaration
2 Ro=50*10**3                 //output resistance (ohms
    )
3 Rd=10*10**3                //drain resistance (ohms)
4 R1=800*10**3               //resistance (ohms)
5 R2=200*10**3               //resistance (ohms)
6 gm=5500*10**-6             //transconductance (us)
7
8 //Calculations
9 r=(Rd*Ro)/(Rd+Ro)          //Rd||Ro
10 R=R1+R2                    //combined resistance
    of R1 and R2
11 Rl=(R*r)/(R+r)             //load resistance (ohms)
12 A=-gm*Rl                   //voltage gain without
    feedback
13 beta=R2/(R1+R2)            //current gain
14 Af=A/(1+A*beta)            //voltage gain with
    feedback
15
16 //Results
17 printf ("Amplifier gain with feedback is %.1f and
    without feedback is %.1f",Af/1E+1,A)

```

---

### Scilab code Exa 6.11 Example

```
1 //Variable declaration
2 Re=1.25*10**3           //emitter resistance (ohms
   )
3 Rc=4.8*10**3           //collector resistance (
   ohms)
4 Rb=800*10**3           //base resistance (ohms)
5 rpi=900                 //dynamic resistance (ohms
   )
6 Vcc=16                  //supply voltage (V)
7 beta=100.               //current gain
8
9 //Calculations
10 A=-(beta/rpi)          //amplifier voltage gain
11 B=-Re
12 V=(A*Rc)/(1+B*A)      //V=Vo/Vs
13
14 //Results
15 printf ("Amplifier voltage gain is %.1f",V)
```

---

### Scilab code Exa 6.12 Example

```
1
2
3 //Variable declaration
4 C1=800*10**-9           //capacitance (F)
5 C2=2400*10**-9         //capacitance (F)
6 L=50*10**-6            //inductance (H)
7
8 //Calculations
```

```

9 Ceq=(C1*C2)/(C1+C2) //equivalent
   capacitance (F)
10 fo=1/(2*%pi*sqrt(L*Ceq)) //output frequency (Hz)
11
12 //Results
13 printf ("the oscillation frequency is %.2f KHz",fo/1
   E+3)

```

---

### Scilab code Exa 6.13 Example

```

1
2
3 //Variable declaration
4 C=200*10**-9 //capacitance (F)
5 Lrcf=0.5*10**-3 //shunt across L2
6 L1=800*10**-6 //inductance (H)
7 L2=800*10**-6 //inductance (H)
8 M=200*10**-6
9
10 //Calculations
11 L21=(L2*Lrcf)/(L2+Lrcf) //effective
   value of L2(uH)
12 Leq=L1+L21+2*M //
   equivalent inductance (H)
13 fo=1/(2*%pi*sqrt(Leq*C)) //output frequency (
   Hz)
14
15 //Results
16 printf ("the oscillation frequency is %.2f KHz",fo/1
   E+3)

```

---

# Chapter 7

## Operational Amplifiers

Scilab code Exa 7.1 Example

```
1 //Variable declaration
2 V1=120 //negative terminal Vn(uV)
3 V2=80 //positive terminal Vp(uV)
4 Ad=10**3 //difference mode gain
5
6
7 //Calculations
8 Vd=V1-V2 //difference mode signal(uV)
9 Vc=(V1+V2)/2 //common mode signal(uV)
10
11 //Part a
12 CMRR=100. //common mode rejection
    ratio
13 Vo=Ad*Vd*(1+(Vc/(CMRR*Vd))) //output voltage(mV)
14
15 //Part b
16 CMRR=10**5. //common mode
    rejection ratio
17 Vo1=Ad*Vd*(1+(1/CMRR)*(Vc/Vd)) //output voltage(mV)
18
19 //Results
```

```
20 printf ("output voltage is %.f mV",Vo/1E+3)
21 printf ("output voltage is %.f mV",Vo1/1E+3)
```

---

### Scilab code Exa 7.2 Example

```
1 //Variable declaration
2 deltavi=0.5 //change in vi(V)
3 deltat=10 //change in time(us)
4 s=1 //slew rate(V/us)
5
6 //Calculations
7 Kvf=(s*deltat)/deltavi //closed loop gain of
   amplifier
8
9 //Results
10 printf ("closed loop gain of amplifier is %.1f",Kvf)
```

---

### Scilab code Exa 7.3 Example

```
1
2
3 //Variable declaration
4 f=50*10**3. //OPAMP frequency(Hz)
5 Vm=0.02 //maximum value of
   signal voltage(V)
6 S=.5*10**6 //slew rate(V/s)
7
8 //Calculations
9 Kvf=S/(2*(%pi)*f*Vm) //closed loop gain of
   amplifier
10
11 //Results
12 printf ("closed loop gain of amplifier is %.f",Kvf)
```

---

### Scilab code Exa 7.4 Example

```
1 //Variable declaration
2 Ic=100 //current at quinscent point(uA)
3 beta=2000. //current gain
4 Ad=250 //difference mode gain
5 CMRR=5000 //as 74 dB=5000,common mode
   rejection ratio(dB)
6
7 //Calculations
8 rpi=(25*beta)/Ic //dynamic internal resistance(k
   ohms)
9 gm=beta/rpi //transconductance(mS)
10 Re=CMRR/gm //emitter resistance(k ohms)
11 Rc=(Ad*2)/gm //collector resistance(k ohms)
   from formula Ad=gmRc/2
12 Rin=2*rpi //input resistance(k ohms)
13
14 //Results
15 printf ("Re is %.1f k ohms",Re)
16 printf ("Rc is %.1f k ohms",Rc)
17 printf ("input resistance is %.1f k ohms",Rin)
```

---

### Scilab code Exa 7.6 Example

```
1 //Variable declaration
2 Icq=.428 //current at quinscent point(uA)
3 beta=200. //current gain
4 //as 74 dB=5000,common mode
   rejection ratio(dB)
5 Rc=10. //collector resistance(k ohms)
```

```

6 Re=16.           //emitter resistance(k ohms)
7 Vcc=15.         //supply voltage(V)
8
9 //Calculations
10 //Part b
11 Ibq=Icq/beta    //Ib at Q(uA)
12 rpi=(25*beta)/Icq //dynamic resistance(k ohms)
13 gm=beta/rpi     //transconductance
14
15 //Part b
16 vo1=Vcc-(Icq*Rc) //terminal 1 voltage(V)
17 vo2=vo1         //terminal 2 voltage(V)
18
19 //Part c
20 Ad=(gm*Rc)/2    //differential mode gain
21 Ac=Rc/(2*Re)   //common mode gain
22 CMRR=Ad/Ac     //common mode rejection ratio
23
24 //Part d
25 Rid=2*rpi       //differential input
    resistance(k ohms)
26 rpi=11.7        //dynamic resistance(k
    ohms)
27 Ric=rpi+(2*(beta+1)*Re) //common mode input
    resistance(k ohms)
28
29 //Results
30 printf ("Icq is %.3f mA, and Ibq is %.2f uA",Icq,Ibq
    /1E-3)
31 printf ("vo1 and vo2 have same value as %.1f V",vo1)
32 printf ("Ad : %.f , Ac : %.3f and CMRR is %.f",Ad/1E
    -3,Ac,CMRR/1E-3)
33 printf ("Rid is %.1f K ohms and Ric is %.2f Mohms",
    Rid/1E+3,Ric/1E+3)

```

---

### Scilab code Exa 7.7 Example

```
1 //Variable declaration
2 R1=10. //series resistance(K ohms)
3 Rf=10**3. //feedback resistance(k
    ohms)
4 vo=-5. //output voltage(V)
5 Ri=1000 //input resistance(k ohms)
6 Av=2.5*10**5 //gain
7
8 //Calculations
9 v1=-vo*(R1/Rf) //input signal voltage(V)
10 vi=-vo/Av //inverting voltage(V)
11 i1=((v1*10**-3)-vi)/R1 //current through R1(uA)
12 ii=vi/Ri //inverting current(uA)
13 iF=-ii //forward current(uA)
14
15 //Results
16 printf ("value of vi is %.e mV",vi)
17 printf ("value of ii: %.e uA i1: %.e uA and iF is %.
    e uA",ii,i1,iF)
```

---

### Scilab code Exa 7.8 Example

```
1 //Variable declaration
2 Vs=4 //source voltage(V)
3 R1=10. //resistance(k ohms)
4 Vb=2 //voltage at point A and point
    B
5 Va=2
6 Rf=30 //forward resistance(k ohms)
7
8 //Calculations
9 I=(Vs-Vb)/R1 //current(mA)
10 Vo=(-I*Rf)+Vb //output voltage(V)
```

```

11
12 //Result
13 printf ("output voltage %.1f V",Vo)

```

---

#### Scilab code Exa 7.9 Example

```

1 //Variable declaration
2 Rf=2 //as vs=2sinwt and vo=(1+Rf/Rs)*vb
   and vB=vA=vs
3 Rs=1
4
5
6 //Calculations
7 vo=(1+(Rf/Rs))*2 //output voltage(V)
8
9 //Result
10 printf ("output voltage %.1f sinwt",vo)

```

---

#### Scilab code Exa 7.10 Example

```

1 //Variable declaration
2 Ro=100. //output resistance(ohms)
3 vo=10. //output voltage(V)
4 A=10**5. //gain
5 Ri=100*10**3 //input resistance(ohms)
6 Rs=1*10**3. //resistance(ohms)
7 Rl=10*10**3 //load resistance(ohms)
8
9 //Calculations
10 //Part i
11 iL=vo/Rl //load current(mA)
12 Avi=vo+(iL*Ro) //voltage gain without
   feedback

```

```

13 vi=Avi/A // voltage (V)
14 ii=vi/Ri // current (A)
15 vs=vo+ii*(Rs+Ri) // source voltage (V)
16
17 //Part ii
18 Avf=vo/vs //voltage gain with
    feedback
19
20
21 //Part iii
22 Rif=vs/ii //input resistance (ohms)
23 Rof=Ro/A //output resistance (ohms)
24
25 //Results
26 printf ("vs is %.4f v",vs)
27 printf ("vo/vs that is Avf is %.f",Avf)
28 printf ("input and output resistances are %.2f , %.3
    f ohms",Rif,Rof)

```

---

### Scilab code Exa 7.11 Example

```

1 //Variable declaration
2 Vb=3 //voltage at A and B
3 Va=Vb
4 R1=40*10**3. //input resistance (ohms)
5 t=50*10**-3 //time after switch is
    open (mS)
6 V1=5 //input voltage (V)
7
8 //Calculations
9 //Part a
10 vo=-3 //as Va=Vb=3
11
12 //Part b
13 i1=(V1-Vb)/R1 //input current (A)

```

```

14 vo1=(-250*50*10**-3)- Vb           //vo at 50 mS
15
16 //Result
17 printf ("output voltage %1f V",vo1)
18
19 // Note : Answer in book is wrong.

```

---

### Scilab code Exa 7.14 Example

```

1
2
3 //Variable declaration
4 BW=30*10**3           //specified bandwidth(k Hz
   )
5 fc=18*10**3          //centered frequency(Hz)
6 R1=20                //resistance(k ohms)
7 R2=180               //resistance(k ohms)
8 C=1.2*10**-9         //capacitance(F)
9 G=40                 //pass band gain(dB)
10 g=20                //pass region gain(dB)
11
12 //Calculationsv
13 fc1=fc-(BW/2)        //high pass section
   frequency(Hz)
14 fc2=fc+(BW/2)        //low pass section
   frequency(Hz)
15 Rfc1=1/(2*%pi*fc1*C) //high pass section resistance
   (k ohms)
16 Rfc2=1/(2*%pi*fc2*C) //low pass section resistance(
   k ohms)
17 Gfc1=G-g            //gain at frequency 0.3KHz
   (dB)
18 Gfc2=G-2*6          //gain at frequency 132KHz
   (dB)
19

```

```

20 // Results
21 printf ("R1 and R2 are %.1f K ohms and %.1f K ohms",
    R1,R2)
22 printf ("Rfc1 is %.f k ohms and Rfc2 is %.f k ohms",
    Rfc1/1E+3,Rfc2/1E+3)
23 printf ("filter gain at frequencies 0.3 KHz is %.1f
    dB and 132 k Hz are %.1f dB",Gfc1,Gfc2)

```

---

### Scilab code Exa 7.21 Example

```

1 // Variable declaration
2 R=250 //resistance(k ohms)
3
4 // Calculations
5 //part a
6 R1=-R/(-5) // as vo=-5va+3vb(given),so when vb=0,
    vo/voa=-250/R1=-5
7
8 //part b
9 R2=R1/(2-1) // as va=0
10 // vx=(R1/R1+R)*vob=(1/6)*vb
11 // vy=(R2/R1+R2)*vb
12 // vx=vy
13 // (1/6)*vob=(R2/R1+R2)*vb
14 // vob=3vb
15 // (1/6)*3=R2/(50+R2)
16
17 // Result
18 printf ("R1 and R2 are %.1f K ohms and %.1f K ohms",
    R1,R2)

```

---

### Scilab code Exa 7.22 Example

```

1 //Variable declaration
2 R1=10*10**3 //resistance(k
   ohms)
3 C1=10**-6 //capacitance(uF)
4 C=0.1*10**-6 //capacitance(uF)
5 R=100*10**3 //resistance(k
   ohms)
6
7 //Calculations
8 //part b
9 wc1=1/C1*R1 //angular frequency(
   rad/s)
10 wc2=1/C*R //angular frequency(
   rad/s)
11 wc=wc2 //angular frequency(rad/
   s)
12 wc1=wc2
13
14 //Results
15 printf ("wc1 is %.2f rad/s",wc1/1E+10)
16 printf ("wc2 is %.2f rad/s",wc2/1e+10)

```

---

### Scilab code Exa 7.23 Example

```

1 //Variable declaration
2 vo1=5 //say (V)
3 K=25 //proportionality constant
4 Q=250 //volume of fluid passed
   across metering point(cm^3)
5 R1=2.5 //output resistance(k ohms)
6
7 //Calculations
8 C1=(K*Q)/(R1*vo1) //capacitor(nF)
9
10 //Results

```

```
11 printf ("C1 is %.f uF", C1/1E+1)
12 printf ("vo1 is -5 V when Q=250 cm^3")
```

---

# Chapter 8

## Multivibrators And Switching Regulators

Scilab code Exa 8.1 Example

```
1 //Variable declaration
2 C=0.1 //capacitance(uF)
3 R1=10 //resistance(k ohms)
4 R2=2.3 //resistance(k ohms)
5 Vcc=12. //supply voltage(V)
6 R1=10**3. //resistance(k ohms)
7
8 //Calculations
9 //Part a
10 f=1/(0.693*C*(R2+R1/2)) //frequency(Hz)
11
12 //Part b
13 D=(1+(R2/R1))/(1+2*(R2/R1))*100 //duty
    cycle
14
15 //Part c
16 //(i)
17 T1=0.693*C*(R1+R2) //time
    period through R1(ms)
```

```

18 T2=0.693*R2*C //time
    period through R2(ms)
19 Pavg=(Vcc/R1)**2*(T1/(T1+T2)) //average
    power dissipated during current sourcing(mW)
20
21 //Part d
22 Pavg1=(T2/(T1+T2))*(Vcc/R1)**2 //average
    power dissipated during current sinking(mW)
23
24 //Results
25 printf (" %.2f kHz",f)
26 printf ("duty cycle is %.2f %%",D)
27 printf ("average power dissipated in current
    sourcing is %.3f mW",Pavg/1E-3)
28 printf ("average power dissipated in current sinking
    is %.3f mW",Pavg1/1e-3)

```

---

### Scilab code Exa 8.2 Example

```

1
2
3 //Variable declaration
4 t=1 //time constant
5 e=1.8 //e=R1/R2 min=1.8
6 e1=9. //e1=R1/R2 max=9
7
8 //Calculations
9 Betamin=1/(1+e) //current gain
    minimum
10 Betamax=1/(1+e1) //current gain
    maximum
11 Tmax=2*t*log((1+Betamin)/(1-Betamin))
12 Tmin=2*t*log((1+Betamax)/(1-Betamax))
13 fmin=1/Tmax //minimum freq (Hz)
14 fmax=1/Tmin //maximum freq (k Hz)

```

```

15
16 // Results
17 printf ("fmin is %.f Hz and fmax is %.1f KHz",fmin/1
    E-3,fmax)

```

---

### Scilab code Exa 8.3 Example

```

1
2
3 // Variable declaration
4 C=0.01 // capacitance (uF)
5 R2=15 // resistance (k ohms)
6 Va2=4 // voltage (V)
7 Vcc=15. // supply voltage (V)
8 R1=33 // resistance (k ohms)
9
10 // Calculations
11 Va1=0.67*Vcc // voltage (V)
12 Vamax=Va1+Va2 // Va maximum (V)
13 Vamin=Va1-Va2 // Va minimum (V)
14 T1max=C*(R1+R2)*(log((1-(Vamax/(2*Vcc)))/(1-(Vamax/
    Vcc)))) //time period (ms)
15 T1min=C*(R1+R2)*(log((1-(Vamin/(2*Vcc)))/(1-(Vamin/
    Vcc)))) //time period (ms)
16 T2=0.693*R2*C
17 fmax=1/(T1min+T2) //maximum
    frequency (K Hz)
18 fmin=1/(T1max+T2) //miniimum
    frequency (K Hz)
19
20 // Results
21 printf ("minimum freq is %.2f",fmin)
22 printf ("maximum freq is %.2f",fmax)
23 printf (" (solution given in the textbook is
    incorrect)");

```

---

### Scilab code Exa 8.4 Example

```
1 //Variable declaration
2 Vi=25 //input voltage(V)
3 Vsmax=30 //supply voltage max(V
   )
4 Vomn=12 //output minimum voltage
   or load voltage(V)
5 V1=12
6 R1=20 //load voltage (V)
7 Io=15. //output current(mA)
8 Iq=3. //quinscent current of
   regulator (mA)
9 Vo=20. //output voltage(V)
10
11 //Calculations
12 //Part a
13 //(i)
14 Vimax=Vsmax //maximum
   permissible voltage(V)
15 Ro=0 //for Vomn=beta=0
16 //(ii)
17 Vomax=Vi-2
18 betaVomax=Vomax-Vomn //output
   voltage(V)
19 R2max=(R1*betaVomax)/(Vomax-betaVomax) //R2max(k
   ohms)
20 //(iii)
21 R3=betaVomax/Io //R3(k ohms)
22
23 //Part b
24 Vt=(Iq*betaVomax)/Io //common
   terminal fall(V)
25 Vomn1=V1+Vt //voltage
```

```

        output minimum(V)
26
27 //Part c
28 betaVo=Vo-V1 //output
        voltage(V)
29 beta=betaVo/Vo //current gain
30 R2=(R1*betaVo)/(Vo-betaVo) //R2(ohms)
31
32 //Results
33 printf ("a) i) max permissible supply voltage is %.1f
        V", Vimax)
34 printf ("ii) output voltage range for Vi=25V is %.1f
        V to %.1f V and R2max is %.f k ohms", Vomax,
        R2max)
35 printf ("iii) R3 is %.2f kohms", R3)
36 printf ("b) Vomax is %.1f V", Vomax)
37 printf ("c) R2 is %.2f ohms and R3 is %.3f ohms", R2,
        R3)

```

---

### Scilab code Exa 8.5 Example

```

1 //Variable declaration
2 A=.0025 //voltage gain
3 Vi=8 //input voltage(V)
4 R2=1.5 //resistance 2(k ohms)
5 R1=1 //resistance 1(k ohms)
6 V1=5 //load voltage(V)
7
8 //Calculations
9 beta=R2/(R1+R2) //current gain
10 Vo=V1/(1-beta) //output voltage(V)
11 Vo1=(A*Vi)/(1+(A*beta)-beta) //output voltage
        ripple if Vi=8Vp-p
12
13 //Results

```

```

14 printf ("Vo is %.1f V",Vo)
15 printf ("expression of output voltage ripple %.2f Vp
    -p",Vo1)

```

---

### Scilab code Exa 8.6 Example

```

1 //Variable declaration
2 Ro=7.5 //output
    resistance(ohms)
3 hfe=50
4 Ve=20 //voltage given
    to emitter(V)
5 Vbe=0.8 //base to
    emitter voltage(V)
6 Vc=15 //collector
    voltage(V)
7 P=12 //maximum power
    dissipation(W)
8 Ib1=5 //for minimum
    load current I1=0,Ib=5
9
10 //Calculations
11 Io=(Vc/Ro)*10**3 //output
    current(A)
12 I1=76 //load current
    (mA)
13 Is=I1+5 //supply
    current(mA)
14 Ic=Io-Is //collector
    current(A)
15 Ib=Ic/hfe //base current
    (mA)
16 Ie=Ic-Ib //emitter
    current(mA)
17 Pt=(Ve*Ie)-(Vc*Ic) //power

```

```

    dissipated in transistor (W)
18 P1=(Ve-Vbe)*Is-Vc*I1           //power
    dissipated in LR
19 Vimax=(P+Vc*(Ic*10**-3))/(Ie*10**-3) //input
    voltage maximum
20 Iomin=hfe*Ib1                 //output
    current minimum (mA)
21
22 //Results
23 printf ("power dissipated in the transistor is %.2f
    W and in LR is %.3f W",Pt/1E+3,P1/1E+3)
24 printf ("maximum permissible input voltage is %.2f V
    ",Vimax)
25 printf ("minimum load current for load voltage to
    remain stabalized is %.1f mA",Iomin)

```

---

#### Scilab code Exa 8.7 Example

```

1 //Variable declaration
2 VL=12           //load voltage (V)
3 I=2.           //current at 12 V
4 V=240          //dc source (V)
5 d=17/50.       //duty cycle
6 d1=0.6         //duty cycle
7 eta1=0.8       //efficiency
8 Vdc = 12
9 //Calculations
10 P=VL*I        //average load power (W
    )
11 Isav=(1*d)/2  //average supply
    current (A)
12 Pav=V*Isav    //average supply power
    (W)
13 eta=(P/Pav)*100 //regulator efficiency
14 Isav1=(1*d1)/2 //average supply

```

```

    current(A)
15 I1=(eta1*V*Isav1)/Vdc           //load current(A)
16 Po=I1*Vdc                       //power output(W)
17
18 //Results
19 printf ("regulator efficiency is %.1f %%",eta)
20 printf ("average supply current is %.1f A",I1)
21 printf ("power output is %.1f W",Po)

```

---

### Scilab code Exa 8.8 Example

```

1 //Variable declaration
2 Vs=200                          //dc source voltage(V)
3 I1=5                             //current to load voltage(A)
4 V1=15                             //load voltage(V)
5 eta=.85                          //efficiency
6 f=20                             //oscillator frequency(Hz)
7 iSmax=2.6                       //peak value of supply current
    (A)
8 P=100                            //full load power supply(W)
9 pdf=0.4                          //pulse duty factor
10
11 //Calculations
12 Isav=(V1*I1)/(Vs*eta)           //average peak supply
    current(A)
13 iS=(2*Isav)/pdf                 //supply current(A)
14 T=1000/f                       //oscillation time period(uS
    )
15 tp=pdf*T                        //transistor time(us)
16 d=iS/tp                         //change in iS with respect
    to time(A/us)
17 tp1=iSmax/d                    //transistor time(us)
18 pdf1=tp1/T                     //pulse duty factor
19 Isav1=(iSmax*pdf1)/2           //average peak supply
    current(A)

```

```
20 eta1=(P*100)/(Vs*Isav1) //efficiency
21
22 //Results
23 printf ("peak value of supply current is %.3f A",
        Isav)
24 printf ("pdf is %.3f ",pdf)
25 printf ("overall efficienc is %.1f %%",eta1)
```

---

# Chapter 9

## Integrated Circuit Fabrication

Scilab code Exa 9.2 Example

```
1 //Variable declaration
2 t=1 //thickness(mil)
3 e=1.6*10**-19 //charge on electron(C)
4 Pp=10**17 //concentration of phosphorous
   (atoms/cm^3)
5 Bn=5*10**16 //boron concentration(atoms/cm
   ^3)
6 un=.135 //mobility(m^2/Vs)
7
8 //Calculations
9 n=(Pp-Bn)*10**6 //net concentration(atoms/cm
   ^3)
10 g=e*un*n //conductivity()
11 rho=10**6/(g*25) //resistivity(ohm mil)
12 Rs=rho/t //sheet resistance(ohm mil^2)
13
14 //Results
15 printf ("Sheet resistance is %.f ohm(mil**2)",Rs)
```

---

### Scilab code Exa 9.3 Example

```
1 //Variable declaration
2 R=20*10**3 //resistance of resistor(
   ohms)
3 w=25 //width(um)
4 Rs=200 //sheet resistance(ohm/
   square)
5 R1=5*10**3 //resistance(ohms)
6
7 //Calculations
8 //Part a
9 l=(R*w)/Rs //length required to
   fabricate 20 kohms(um)
10
11 //Part b
12 L=25 //length of resistor of 5 k ohms(um
   )
13 w1=(Rs*L)/R1 //width required to fabricate 5
   kohms(um)
14
15 //Results
16 printf ("length required to fabricate 20 kohms
   resistor is %.1f um",l)
17 printf ("width required to fabricate 5 kohms
   resistor is %.1f um",w1)
```

---

### Scilab code Exa 9.4 Example

```
1 //Variable declaration
2 C=0.4*10**-12 //capacitance(pF/um^2)
3 A=10**-12 //area of film(m^2)
4 d=400*10**-10 //thickness of SiO2(
   amstrong)
5 Eo=8.849*10**-12 //absolute electrical
```

```

        permittivity of free space
6
7 // Calculations
8 Er=(C*d)/(Eo*A)           //relative dielectric
        constant
9
10 // Results
11 printf ("relative dielectric constant of SiO2 is %.f
        ",Er)
12 printf(" Note : Solution given in the textbook is
        incorrect")

```

---

#### Scilab code Exa 9.5 Example

```

1 //Variable declaration
2 C=250*10**-12           //capacitance(pF)
3 d=500*10**-10         //thickness of SiO2
        layer(amstrong)
4 Eo=8.849*10**-12       //absolute electrical
        permittivity of free space
5 Er=3.5                 //relative dielectric
        constant
6
7 // Calculations
8 A=(C*d)/(Eo*Er)       //chip area(um^2)
9
10 // Results
11 printf ("chip area needed for a 250 pF MOS
        capacitor %.2f um^2",A/1e-7)
12 printf("Note: Solution given in the textbook is
        incorrect")

```

---

# Chapter 10

## Circuit Theory

Scilab code Exa 10.1 Example

```
1 //Variable declaration
2 i1=4.           //current through r1(A)
3 v3=3           //voltage(V)
4 v4=8           //voltage(V)
5 r3=3           //resistance(ohms)
6 r2=2           //resistance(ohms)
7 r4=4           //resistance(ohms)
8
9 //Calculations
10 i3=v3/r3       //current through r3(A)
11 i4=v4/r4       //current through r4(A)
12 i2=-(i3+i4-i1)/2 //current through r2(A)
13 v2=i2*r2       //voltage through r2(V)
14
15 //Result
16 printf ("v2 is %.1f V",v2)
```

---

Scilab code Exa 10.2 Example

```

1 //Variable declaration
2 v1=6 //current through r1(A)
3 i2=2 //voltage through r3(V)
4 i3=4 //voltage through r4(V)
5 r3=2 //resistance(ohms)
6 v3=3 //voltage through r3(ohms)
7 r2=2 //resistance(ohms)
8 r4=3 //resistance(ohms)
9
10 //Calculations
11 v2=i2*r2 //voltage through r2(ohms)
12 v3=i3*r3 //voltage through r3(ohms)
13 v4=4*i2+v3-v2-v1 //voltage through r4(ohms)
14 i4=v4/r4 //current through r4(A)
15
16 //Result
17 printf (" i4 is %.f A",i4)

```

---

### Scilab code Exa 10.3 Example

```

1
2 //Calculations
3 a = [7 -3 -4 ; -3 6 -2 ; -4 -2 11] //solving three
    linear mesh equations
4 b = [-11;3;25]
5 x = a\b
6
7 v=x(3) - x(2) //
    voltage across 2mho conductance(V)
8
9 //Results
10 printf ("v is %.1f V",v)

```

---

### Scilab code Exa 10.4 Example

```
1
2 //Variable declaration
3 R=20 //resistance across
      which voltage is to be calculated(ohms)
4
5 //Calculations
6 a = [35 -20 ; -20 50] //solving two linear mesh
      equations
7 b = [50;-100]
8 x = a\b
9 i=x(1)-x(2) //current through 20 ohms
      resistor(ohms)
10 V=20*i //voltage across 20 ohms(V)
11
12 //Results
13 printf ("i is %.2f",i)
14 printf ("voltage across 20 ohms is %.1f V",V)
```

---

### Scilab code Exa 10.5 Example

```
1 //Variable declaration
2 Vs=16. //source voltage(V)
3
4 //Calculations
5 //Part b
6 I=0 //current through 10 V
7 Is=-4*(I-(Vs/32)) //current of current source(A)
8
9 //Part c
10 Is1=16 //current of current source(A)
11 I=0 //current through 10 V
12 Vs1=(I+(Is1/4))*32 //source voltage(V)
13
```

```

14 //Results
15 printf (" Is is %.f A",Is)
16 printf (" Vs1 is %.f V",Vs1)

```

---

#### Scilab code Exa 10.6 Example

```

1 //Variable declaration
2 V=9 //voltmeter of voltage(V)
3 i=9 //ammeter current of 9V
4 r1=1 //resistance(ohms)
5 r2=3 //resistance(ohms)
6 r=5 //resistance parallel to
    ammeter(ohms)
7
8 //Calculations
9 Isc=((i*r)-V)/(r1+r) //short circuiting a and
    b and converting current source to a voltage
    source(A)
10 Ro=((r+r1)*r2)/((r+r1)+r2) //output resistance(ohms)
11
12 //Results
13 printf (" Isc is %.f A",Isc)
14 printf (" Ro is %.f ohms",Ro)

```

---

#### Scilab code Exa 10.7 Example

```

1
2 //Variable declaration
3 syms t //symbol defined
4 et1 = complex(50,86.6) //defining complex number
5
6 //calculations

```

```

7 et = (real(et1)*sqrt(2)*cos(314*t))+imag(et1)*sqrt
      (2)*cos(314*t+90) //expression
8
9 //Result
10 disp ( et)

```

---

### Scilab code Exa 10.9 Example

```

1
2 //Variable declarations
3 syms V1 V2
4
5
6 //Calculations
7 V = 0.3*V1
                                     //
      voltage(V)
8 I1 = 0.007*V1
                                     //
      current
9 y11 = I1/V1
                                     //y
      parameter
10
11 I2 = -V/40
                                     //
      current
12 y21 = I2/V1
                                     //y
      parameter
13
14 I2 = V2/(((40+100)*200.)/((40+100)+200.))
                                     //y parameter
15 y22 = I2/V2 //incorrect answer in textbook
      //y parameter

```

```

16
17 I1 = (-I2*200)/300
18 y12 = I1/V2 //current //incorrect answer in textbook
           //y parameter
19
20 //Results
21 disp ("mho" , y11+y12 ,"y11+y12 is")
22 disp ("mho" , y22+y12 ,"y22+y12 is")
23 disp ("mho" , y21-y12 ,"y21-y12 is")
24 disp ( "\n(The difference in answers is due to the
           y12 and y21 values calculated wrongly in the
           textbook)")

```

---

#### Scilab code Exa 10.10 Example

```

1 //Variable declaration
2
3 //port 2 open circuited ,port 1 excited
4 z11= complex(1075,1075) //as z11=
           V1/I1=(1.52<45)/(10**3<0)=1075+1075j
5 z21 = complex(2022,-1075) //as z21
           =V2/I1=(2.29<-28)/(10**3<0)=2022+1075j
6
7 //port 1 open circuited and port 2 excited
8 z12= complex(0,-1075) //as z12
           =V1/I2=(1.075<-90)/(10**3<0)=-1075j
9 z22= complex(751,-1073) //as z22=
           V2/I2=(1.31<-55)/(10**3<0)=751-j1073
10
11 //Calculations
12 z=z11-z12 //parameters with
           reference to circuit
13 z1=z22-z12
14 z2=z21-z12

```

```
15
16 //Results
17 printf ("z11-z12(z) is ")
18 disp(z)
19 printf ("z22-z12(z1) is")
20 disp(z1)
21 printf ("z21-z12(z2) is")
22 disp(z2)
```

---

#### Scilab code Exa 10.11 Example

```
1 //Variable declaration
2 V2=6/7. //voltage source(V)
3
4 //Calculations
5 Rth=V2 //thevinin resistance(
   ohms)
6 Z1=Rth //load resistance(ohms)
7
8 //Result
9 printf ("load resistance is %.3f ohms",Z1)
```

---

# Chapter 11

## Cathode Ray Oscilloscope

Scilab code Exa 11.2 Example

```
1 //Variable declaration
2 E=120 //electric field (V/m)
3 B=5*10**-5 //magnetic field (T)
4 q=1.6*10**-19 //charge on electron (C)
5 u=10**6 //velocity of electron (m/s)
6 m=9.1*10**-31 //mass of electron (Kg)
7 a=9.81 //acceleration of gravitation
   (m/s^2)
8
9 //Calculations
10 //Part a
11 fe=q*E //force on electron due to
   electric field (N)
12
13 //Part
14 fm=B*q*u //force on electron due to
   magnetic field (N)
15
16 //Part c
17 fg=m*a //force on electron due to
   gravitational field (N)
```

```

18
19 //Results
20 printf ("force on electron due to electric field is
    %.2e N",fe)
21 printf ("force on electron due to magnetic field is
    %.e N",fm)
22 printf ("force on electron due to gravitational
    field is %.4e N",fg)

```

---

### Scilab code Exa 11.3 Example

```

1
2
3 //Variable declaration
4 T1=1200. //temperature(k)
5 T2=1000. //temperature(k)
6 Ww=1.2*10**5 //work function(eV)
7 k=8.62
8 Ie1=200 //emission current
    density
9 T3=1500. //temperature(k)
10
11 //Calculations
12 Ie2=Ie1*(T2/T1)**2*exp(-(Ww/k)*((1/T2)-(1/T1)))
    //current density(mA/cm^2) at 1000k
13 Ie3=Ie1*(T3/T1)**2*exp(-(Ww/k)*((1/T3)-(1/T1)))
    //current density(mA/cm^2) at 1000k
14
15 //Results
16 printf ("current density at 1000 k is %.2f mA/cm^2",
    Ie2)
17 printf ("current density at 1500 k is %.2f mA/cm^2",
    Ie3)

```

---

### Scilab code Exa 11.4 Example

```
1
2
3 //Variable declaration
4 Ls=40 //distance from screen(m)
5 d=1.5 //distance between plates(
   cm)
6 Va=1200 //accelerating potential(V
   )
7 L=3 //length of CRT(m)
8 e=1.6*10**-19 //charge on electron(C)
9 m=9.1*10**-31 //mass of electron(Kg)
10 Y=4*10**-2 //vertical deflection(V)
11
12 //Calculations
13 //Part a
14 U=sqrt((2*e*Va)/m) //velocity of electron upon
   striking screen(m/s)
15
16 //Part
17 Vd=(2*d*Va*Y)/(L*Ls) //deflecting voltage(V)
18
19 //Part c
20 Vdmax=(m*d**2*U**2)/(e*L**2) //maximum allowable
   deflection(V)
21
22 //Results
23 printf ("velocity of electron upon stricking the
   screen is %.3e m/s",U)
24 printf ("deflecting voltage is %.f V",Vd/1E-2)
25 printf ("maximum allowable deflection is %.f V",
   Vdmax)
```

---