

Scilab Textbook Companion for
Principles of Electronics
by V. K. Mehta and R. Mehta¹

Created by
Kavan Patel
B.Tech
Instrumentation Engineering
Dharmsinh Desai University
College Teacher
None
Cross-Checked by
Chaitanya

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Principles of Electronics

Author: V. K. Mehta and R. Mehta

Publisher: S.Chand, New Delhi

Edition: 9

Year: 2005

ISBN: 81-219-2450-2

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Introduction	5
2 Electron emission	15
3 Vacuum tubes	17
4 Vacuum tube rectifiers	22
5 Vacuum tube amplifiers	27
9 Semiconductor diode	31
10 Special purpose diodes	53
11 Transistors	57
12 Transistor biasing	70
13 Single stage transistor amplifiers	93
14 Multistage transistor amplifiers	108
15 Transistor audio power amplifiers	122

16 Amplifiers with negative feedback	131
17 Sinusoidal oscillations	144
18 Transistor tuned amplifiers	149
19 Modulation and demodulation	154
20 Regulated dc power supply	163
21 Solid state switching circuits	172
22 Field Effect Transistors	181
23 Silicon controlled rectifiers	188
24 Power electronics	194
25 Electronic instruments	196
26 Integrated circuits	203
27 Hybrid parameters	204
28 Digital electronics	211

List of Scilab Codes

Exa 1.1	terminal voltage	5
Exa 17.1	Example 1	5
Exa 1.2	Exmaple 2	6
Exa 1.3	Exmaple 3	7
Exa 1.4	Exmaple 4	7
Exa 1.5	Exmaple 5	8
Exa 1.6	Exmaple 6	9
Exa 1.7	Exmaple 7	9
Exa 1.8	Exmaple 8	10
Exa 1.9	Exmaple 9	11
Exa 1.10	Exmaple 10	12
Exa 1.11	Exmaple 11	13
Exa 1.12	Exmaple 12	14
Exa 2.1	Example 1	15
Exa 2.2	Example 2	15
Exa 3.1	Example 1	17
Exa 3.2	Example 2	17
Exa 3.3	Example 3	18
Exa 3.4	Example 4	19
Exa 3.5	Example 5	20
Exa 4.1	Example 1	22
Exa 4.2	Example 2	23
Exa 4.3	Example 3	23
Exa 17.4	Example 4	24
Exa 4.4	Example 4	25
Exa 4.5	Example 5	25
Exa 5.1	Example 1	27
Exa 5.2	Example 2	27

Exa 5.3	Example 3	28
Exa 5.4	Example 4	29
Exa 5.5	Example 5	30
Exa 9.1	Example 1	31
Exa 9.2	Example 2	32
Exa 9.3	Example 3	33
Exa 9.4	Example 4	33
Exa 9.5	Example 5	34
Exa 9.6	Example 6	34
Exa 9.7	Example 7	35
Exa 9.8	Example 8	36
Exa 9.9	Example 9	36
Exa 9.10	Example 10	37
Exa 9.11	Example 11	38
Exa 9.12	Example 12	38
Exa 9.13	Example 13	39
Exa 19.14	power	39
Exa 9.14	Example 14	40
Exa 9.15	Example 15	41
Exa 9.16	Example 16	42
Exa 9.17	Example 17	44
Exa 9.18	Example 18	44
Exa 9.19	Example 19	45
Exa 9.20	Example 20	46
Exa 9.21	Example 21	47
Exa 9.22	Example 22	48
Exa 9.23	Example 23	48
Exa 9.24	Example 24	49
Exa 9.25	Example 25	50
Exa 9.26	Example 26	50
Exa 9.27	Example 27	51
Exa 9.28	Example 28	52
Exa 10.1	required series resistor	53
Exa 10.2	current through LED	53
Exa 10.3	dark resistance	54
Exa 10.4	reverse current	54
Exa 10.5	resonant frequency	55
Exa 10.11	base current	55

Exa 11.1	voltage amplification	57
Exa 11.2	base current	57
Exa 11.3	base current	58
Exa 11.4	amplification factor	58
Exa 11.5	collector current	59
Exa 11.6	base current	59
Exa 11.7	collector current	60
Exa 11.8	Example 8	61
Exa 11.9	Example 9	61
Exa 11.10	collector current	62
Exa 11.11	base current	62
Exa 11.12	collector emitter voltage	63
Exa 11.13	base current	63
Exa 11.14	dc load line	64
Exa 11.15	Q point	64
Exa 11.16	collector load	65
Exa 11.17	input resistance	66
Exa 11.18	output resistance	66
Exa 11.19	voltage gain	67
Exa 11.20	saturation collector current	67
Exa 11.21	maximum allowable collector current	68
Exa 12.1	circuit diagram	70
Exa 12.2	maximum input signal voltage	71
Exa 12.3	Example 3	72
Exa 12.4	Example 4	73
Exa 12.5	Example 5	74
Exa 12.6	Example 6	74
Exa 12.7	Example 7	75
Exa 12.8	Example 8	76
Exa 12.9	Example 9	77
Exa 12.10	base resistance	78
Exa 12.11	voltage across	78
Exa 12.12	thevenin	79
Exa 12.13	Example 12	80
Exa 12.14	collector current	81
Exa 12.15	collector emitter	82
Exa 12.16	Kirchoff voltage law	83
	collector resistance	84

Exa 12.17	thevenin	84
Exa 12.18	kilo ohm	85
Exa 12.19	transistor	86
Exa 12.20	circuit is not mid-point biased	87
Exa 12.21	circuit is not mid-point biased	88
Exa 12.22	base current	88
Exa 12.23	collector cutoff current	89
Exa 12.24	base current	90
Exa 12.25	since base voltage is zero	91
Exa 12.26	voltage at base	91
Exa 1.1	collector current	93
Exa 1.2	Thevenin circuit	94
Exa 13.3	the operating point	95
Exa 13.4	maximum collector	96
Exa 13.5	plot	98
Exa 13.6	voltage gain	99
Exa 13.7	output voltage	100
Exa 13.8	input impedance	100
Exa 13.9	output voltage	101
Exa 13.10	circuit	102
Exa 13.11	ac emitter resistance	102
Exa 13.12	voltage gain	103
Exa 13.13	voltage gain	103
Exa 13.14	input impedance of amplifier circuit	104
Exa 13.15	Class A	105
Exa 13.16	required input signal voltag	105
Exa 13.17	magnitude of output voltage	106
Exa 13.18	required signal voltage	107
Exa 14.1	gain	108
Exa 14.2	gain	108
Exa 14.3	total voltage gain	109
Exa 14.4	Example 4	109
Exa 14.5	Example 5	110
Exa 14.6	output voltage	110
Exa 14.7	minimum value of load resistance	111
Exa 14.8	output voltage	112
Exa 14.9	frequency	112
Exa 14.10	gain	113

Exa 14.11	gain	114
Exa 14.12	voltage gain	115
Exa 14.13	biasing potential	115
Exa 14.14	voltage gain	116
Exa 14.15	transformer	118
Exa 14.16	voltage across external load	119
Exa 14.17	turn ratio for maximum power transfer . . .	119
Exa 14.18	inductance	120
Exa 14.19	inductance	120
Exa 15.1	maximum collector current	122
Exa 15.2	maximum collector current	122
Exa 15.3	ac output	123
Exa 15.4	collector efficiency	123
Exa 15.5	collector efficiency	124
Exa 15.6	maximum ac power output	125
Exa 15.7	power dissipation	125
Exa 15.8	loudspeaker	126
Exa 15.9	current	127
Exa 15.10	maximum ambient temperature at which transistor can be operated	128
Exa 15.11	maximum power dissipation	128
Exa 15.12	allowed collector current	129
Exa 16.1	voltge gain with negative feedback	131
Exa 16.2	fraction of output fed back to input	131
Exa 16.3	overall gain	132
Exa 16.4	fraction of output fed back to input	132
Exa 16.5	percentage reduction in gain	133
Exa 16.6	percentage change in gain	134
Exa 16.7	voltage gain with negative feedback	134
Exa 16.8	voltage gain with negative feedback	135
Exa 16.9	Example 9	136
Exa 16.10	distortion of amplifier with negative feedback	136
Exa 16.11	cutoff frequency with negative feedback	137
Exa 16.12	effective current gain of amplifier	138
Exa 16.13	input impedance with negative feedback	138
Exa 16.14	output impedance with negative feedback	139
Exa 16.15	Bandwidth with negative feedback	139
Exa 16.16	voltage across	140

Exa 16.17	voltage gain	140
Exa 16.18	voltage gain	141
Exa 16.19	input impedance	141
Exa 16.20	output impedance	142
Exa 17.1	frequency of oscillations	144
Exa 17.2	operating frequency	144
Exa 17.3	feedback function	145
Exa 17.4	frequency of oscillations	146
Exa 17.5	frequency of oscillations	146
Exa 17.6	thickness of crystal	147
Exa 17.7	resonant frequency	147
Exa 18.1	impedance of circuit at resonance	149
Exa 18.2	circuit	149
Exa 18.3	frequency	150
Exa 18.4	frequency	151
Exa 18.5	co-efficient of coupling	151
Exa 18.6	ac load	152
Exa 18.7	load	153
Exa 19.1	V _{max} &V _{min}	154
Exa 19.2	modulation factor	154
Exa 19.3	modulation factor	155
Exa 19.4	Bandwidth for RF amplifier	155
Exa 19.5	amplitudes of components	156
Exa 19.6	amplitude of each sideband term	157
Exa 19.7	power of modulated wave	158
Exa 19.8	sideband power	158
Exa 19.9	modulating signal	159
Exa 19.10	frequencie & bandwith	159
Exa 19.11	antenna current	160
Exa 19.12	modulation factor	160
Exa 19.13	modulation factor	161
Exa 19.14	AM wave	161
Exa 20.1	regulation	163
Exa 20.2	full load voltage	163
Exa 20.3	regulation for power	164
Exa 20.4	minimum load resistance	165
Exa 20.5	maximum zener current	165
Exa 20.6	required series resistance	166

Exa 20.7	load voltage & current	167
Exa 20.8	Zener diode	167
Exa 20.9	Zener diode	168
Exa 20.10	regulated output voltage	169
Exa 20.11	closed loop voltage gain	170
Exa 20.12	collector current	170
Exa 21.1	voltage required to saturate transistor . . .	172
Exa 21.2	square wave	172
Exa 21.3	differentiating circuit	173
Exa 21.4	output voltage	173
Exa 21.5	plotting input and output waveforms	174
Exa 21.6	plotting input and output waveforms	175
Exa 21.7	plotting input and output waveforms	176
Exa 21.8	plotting input and output waveforms	176
Exa 21.9	empty	178
Exa 21.10	plot input and output waveforms	178
Exa 21.11	plot input and output waveforms	179
Exa 22.1	I_d	181
Exa 22.2	drain current	181
Exa 22.3	pinch off voltage	182
Exa 22.4	gate source resistance	182
Exa 22.5	transconductance	183
Exa 22.6	amplification factor	183
Exa 22.7	Kirchoff's law	184
Exa 22.8	required value of R_s	185
Exa 22.9	voltage amplification of the circuit	186
Exa 22.10	V_{ds}	186
Exa 22.11	dc voltage of drain	187
Exa 23.1	Breakover voltage	188
Exa 23.2	rating	189
Exa 23.3	maximum allowable duration of surge . . .	189
Exa 23.4	average current	190
Exa 23.5	power output	191
Exa 23.6	forward breakdown voltage	191
Exa 23.7	voltage	192
Exa 24.1	$(RB_1+RB_2) = RB_1/R_{bb}$	194
Exa 24.2	voltage	194
Exa 25.1	sensitivity	196

Exa 25.2	equivalent resistance of meter	196
Exa 25.3	voltage read by multimeter	197
Exa 25.4	voltage read by multimeter	198
Exa 25.5	resistance of voltmeter	198
Exa 25.6	spot shift	200
Exa 25.7	applied voltage	200
Exa 25.8	unknown voltage	201
Exa 25.9	ratio of fv to fh	201
Exa 26.1	regulated dc output voltage	203
Exa 27.1	ratio	204
Exa 27.2	impedance	205
Exa 27.3	voltage gain of circuit	206
Exa 27.4	approximate current gain	207
Exa 27.5	input impedance	208
Exa 27.6	voltage gain	208
Exa 27.7	micro mho	209
Exa 28.1	binary equivalent of decimal number 37 . . .	211
Exa 28.2	binary equivalent of decimal number 23 . . .	211
Exa 28.3	equivalent decimal of binary 110001	212
Exa 28.4	page598	212
Exa 28.5	page598	213
Exa 28.6	factorize	213
Exa 28.7	Apply cummulative law and theorem	214
Exa 28.8	Based on theorem 16 & 3	215
Exa 28.9	Using De Morgan theory	216
Exa 28.10	De Morgan theorem	216
Exa 28.11	De Morgan theorem	217
Exa 28.12	theorem	218
Exa 28.13	theorem	218

Chapter 1

Introduction

Scilab code Exa 1.1 terminal voltage

```
1 //chapter 1
2 //example 1.1
3 //page8
4
5 Eg=24 // V
6 Ri=.01 // ohm
7 P=100 // W
8
9 I=P/Eg // we know that P=Eg*I since for ideal source
      , V is equivalent to Eg
10 Vi=I*Ri
11 V=Eg-(I*Ri)
12
13 printf("voltage drop in internal resistance = %.3f V
      \n",Vi)
14 printf("terminal voltage = %.3f V",V)
```

Scilab code Exa 17.1 Example 1

```

1 //chapter17
2 //example17.1
3 //page375
4
5 L1=58.6d-6 // H
6 C1=300d-12 // F
7
8 f=1/(2*pi*(L1*C1)^0.5)
9 printf("frequency of oscillations = %.3f Hz or %.3f
kHz",f,f/1000)
10
11 // in book the answer is 1199 kHz but the accurate
answer is 1200.358 kHz

```

Scilab code Exa 1.2 Example 2

```

1 //chapter1
2 //example1.2
3 //page10
4
5 Eg=500 // V
6 Ri=1000 // ohm
7
8 // for Rl=10 ohm
9 Rl1=10 // ohm
10 I1=Eg/(Rl1+Ri)
11 printf("load current for Rl=10ohm is %.3f A \n",I1)
12
13 // for Rl=10 ohm
14 Rl2=50 // ohm
15 I2=Eg/(Rl2+Ri)
16 printf("load current for Rl=50ohm is %.3f A \n",I2)
17
18 // for Rl=10 ohm
19 Rl3=100 // ohm

```

```
20 I3=Eg/(Rl3+Ri)
21 printf("load current for Rl=100ohm is %.3f A",I3)
```

Scilab code Exa 1.3 Example 3

```
1 //chapter1
2 //example1.3
3 //page11
4
5 V=10 // V
6 R=10 // ohm
7
8 I=V/R // calculate short-circuit current by shorting
      AB
9 printf("equivalent current source has magnitude = %
      .3f A",I)
10
11 // no load is connected across AB and 10V source has
      negligible resistance
12 // so resistance across AB is 10 ohm
13
14 // the constant voltage source when converted to
      constant current source will thus have a source
      of 1A in parallel with resistor of 10 ohm
```

Scilab code Exa 1.4 Example 4

```
1 //chapter1
2 //example1.4
3 //page12
4
5 I=6 // mA
6 R=2 // kilo ohm
```

```

7
8 V=I*R // by ohm law
9 printf("voltage of voltage source = %.3f V",V)
10
11 // this voltage source when connected in series with
   2000 ohm gives equivalent voltage source for the
   given constant current source

```

Scilab code Exa 1.5 Example 5

```

1 //chapter1
2 //example1.5
3 //page13
4
5 E=200 // V
6 Ri=100 // ohm
7
8 Rl=100 // for load=100ohm
9 I=E/(Ri+Rl)
10 P1=I^2*Rl
11 Pt=I^2*(Rl+Ri)
12 efficiency=(P1/Pt)*100
13 printf("for load=100 ohm, power delivered to load=%
.3f W and efficiency=% .3f percentage \n \n",P1,
   efficiency)
14
15 Rl=300 //for load=300ohm
16 I=E/(Ri+Rl)
17 P1=I^2*Rl
18 Pt=I^2*(Rl+Ri)
19 efficiency=(P1/Pt)*100
20 printf("for load=300 ohm, power delivered to load=%
.3f W and efficiency=% .3f percentage \n \n",P1,
   efficiency)
21

```

```
22 printf("comment: \n ")
23 printf("if load resistance is equal to internal
      resistance ,maximum power is \n transferred but
      efficiency is low \n ")
24 printf("if load resistance is more than internal
      resistance , power transferred \n is less but
      efficiency is high")
```

Scilab code Exa 1.6 Exmaple 6

```
1 //chapter1
2 //example1.6
3 //page14
4
5 //for maximum power transfer , resistance of load and
   amplifier should match
6 //so we take load=15 ohm
7
8 Rl=15 // ohm
9 Ri=15 // ohm
10 V=12 // V
11
12 Rt=Rl+Ri
13 I=V/Rt
14 P=I^2*Rl
15
16 printf("for maximum power transfer load must equal
      amplifier resistance \n so required load = %d ohm\
      n \n",Rl)
17 printf("power delivered to load = %.3f W",P)
```

Scilab code Exa 1.7 Exmaple 7

```

1 //chapter1
2 //example1.7
3 //page14
4
5 V=50 // V
6 Rl=100 // ohm
7 Zi=100+50*i
8 //for maximum power transfer load impedance should
   be conjugate of internal resistance so
9 Zl=100-50*i
10
11 Zt=Zi+Zl
12 I=V/Zt
13 P=I^2*Rl
14
15 printf("load for maximum power (in ohms) =")
16 disp(Zl)
17
18 printf("maximum power transferred to load = %.3f W",P)

```

Scilab code Exa 1.8 Exmaple 8

```

1 //chapter1
2 //example1.8
3 //page21
4
5 R=8 // ohm
6 R1=10 // ohm
7 R2=20 // ohm
8 R3=12 // ohm
9 //removing 100 ohm resistance , we form linear
   equations by assuming currents I1 through loop1
   and I2 through loop2
10
11 //100=10*I1+20*(I1-I2)

```

```

12 //0=(12+8)*I2+20*(I2-I1)
13
14 //thus we get the following linear equations
15
16 //30*I1-20*I2=100
17 //-20*I1+40*I2=0
18 //solving these equations
19
20 a=[30 -20;-20 40]
21 b=[100;0]
22 x=inv(a)*b // matrix of I1 and I2
23
24 I2=x(2,1) // current through 8 ohm resistor
25
26 E0=I2*R
27 printf("voltage across AB with 100 ohm resistance
           not connected = %.3f V \n",E0)
28
29 R_equi=(R1*R2/(R1+R2))+R3
30 R0=R_equi*R/(R_equi+R)
31 printf("resistance between AB with 100 ohm removed
           and voltage source shorted = %.3f ohm \n",R0)
32
33 I=E0/(R0+R1)
34 printf("current through 100 ohm resistor = %.3f A" ,I
      )

```

Scilab code Exa 1.9 Exmaple 9

```

1 //chapter1
2 //exzmple1.8
3 //page16
4
5 R1=1 // kilo ohm
6 R2=1 // kilo ohm

```

```

7 R3=1 // kilo ohm
8 V=20 // V
9
10 E0=(R3/(R1+R2))*V // thevenin voltage = voltage
    across R3 since A and B are open circuited which
    means no drop across R2
11 R0=R2+(R1*R3/(R1+R3)) // thevenin resistance =
    resistance between A and B with no load and
    voltage source shorted
12
13 printf("thevenin voltage = %.2f V \nthevenin
    resistance = %.2f kilo ohm",E0,R0)

```

Scilab code Exa 1.10 Example 10

```

1 //chapter1
2 //example1.10
3 //page18
4
5 V=120 // V
6 R1=40 // ohm
7 R2=20 // ohm
8 R3=60 // ohm
9
10 //removing load , voltage across AB is
11 E0=R2*V/(R1+R2)
12
13 //replacing voltage source by short and removing
    load , resistance across AB is
14 R0=R3+(R1*R2/(R1+R2))
15
16 //for maximum power transfer , load must be equal to
    resistance across AB so
17 Rl=R0
18

```

```
19 P=E0^2/(4*R1)
20 printf("load resistance for maximum power transfer =
    %.3f ohm \n",R1)
21 printf("maximum power to load = %.3f W",P)
```

Scilab code Exa 1.11 Exmaple 11

```
1 //chapter1
2 //example1.11
3 //page20
4
5 R1=4 // ohm
6 R2=6 // ohm
7 R3=5 // ohm
8 R4=8 // ohm
9 V=40 // V
10
11 // load is removed and A and B are shorted
12 load_source=R1+(R2*R3/(R2+R3))
13 source_current=V/load_source
14
15 norton_current=source_current*(R2/(R2+R3)) // short
    circuit current in AB
16
17 printf("shortcircuit current in AB = %.3f A \n",
    norton_current)
18
19 // load is removed and battery is replaced by a
    short
20 norton_resistance=R3+(R1*R2/(R1+R2))
21 printf("norton resistance= %.3f ohm \n",
    norton_resistance)
22
23 // equivalent circuit is norton current source in
    parallel with norton resistance
```

```
24 I=norton_current*(norton_resistance/(
    norton_resistance+R4)) // current through 8 ohm
    resistance
25 printf("current through 8ohm resistor = %.3f A",I)
```

Scilab code Exa 1.12 Example 12

```
1 // chapter 1
2 // example 1.12
3 // page 21
4
5 printf("To find Norton equivalent circuit we need to
        find \nNorton current I_N and Norton resistance
        R_N \n \n")
6 printf("If Thevenin resistnce = Ro and Thevenin
        voltage = Eo then \n \n")
7 printf("To convert Thevenin circuit to Norton
        circuit , \n")
8 printf("I_N=Eo/Ro and R_N=Ro \n \n")
9 printf("To convert Norton circuit to Thevenin
        circuit , \n")
10 printf("Eo=I_N*R_N and Ro=R_N \n")
```

Chapter 2

Electron emission

Scilab code Exa 2.1 Example 1

```
1 //chapter 2
2 //example 2.1
3 //page 29
4
5 A=60.2d4 // ampere per square m per square kelvin
6 T=2500 // kelvin
7 phi=4.517 // eV
8 d=0.01d-2 // m
9 l=5d-2 // m
10
11 b=11600*phi
12 Js=A*T^2*exp(-b/T)
13 a=%pi*d*l
14
15 emission_current=Js*a
16
17 printf("emission current=%f A",emission_current)
```

Scilab code Exa 2.2 Example 2

```

1 // Chapter 2
2 // example 2.2
3 // page 29
4 Js=0.1 // ampere per square cm
5 A=60.2 // ampere per square cm per square kelvin
6 T=1900 // kelvin
7
8 // Js=A*T^2*exp(-b/T) so b=-T*log( Js/(A*T^2) )
9
10 b=-T*log( Js/(A*T^2) )
11
12 // b=11600*phi so making phi as subject
13
14 phi=b/11600
15
16 printf("work function=%f eV \n",phi)
17 // the accurate answer is 3.521466
18 // but in the book it is mistakenly written as 3.56
19
20 if(2.63<phi & phi<4.52)
21     printf("thoriated tungsten has work function
22           between 2.63eV to 4.52eV.\nSo sample is
23           likely to be thoriated tungsten")
24 elseif(phi<=2.63 | phi>4.52)
25     printf("tungsten is contaminated") // for
26           pure tungsten, phi must be 4.52 exactly
27
28 else
29     printf("tungsten is pure") // phi=4.52 implies
           tungsten is pure
30 end
31
32 // please note that there is error in the answer of
33 // work function phi in the book
34 // The correct answer is 3.521466 eV and not 3.56 eV

```

Chapter 3

Vacuum tubes

Scilab code Exa 3.1 Example 1

```
1 //chapter3
2 //example3.1
3 //page41
4
5 Ib1=10 // mA
6 Eb1=100 // V
7 Ib2=20 // mA
8
9 // Ib is proportional to Eb^(3/2)
10 // so we can say Ib1/Ib2 = Eb1^1.5/Eb2^1.5
11 //thus we can write
12
13 log_Eb2=(2/3)*log(Eb1^1.5*Ib2/Ib1)
14 Eb2=exp(log_Eb2)
15 printf(" required plate voltage = %.3f V" ,Eb2)
```

Scilab code Exa 3.2 Example 2

```

1 //chapter3
2 //example3.2
3 //page49
4
5 mu=20
6 rp=8000 // ohm
7
8 gm=mu/rp // since mu=rp*gm
9 gm_micro=gm*10^6 //micro mho
10 printf("mutual conductance of triode = %f mho or %.3
          f micro mho",gm,gm_micro)

```

Scilab code Exa 3.3 Example 3

```

1 //chapter3
2 //example3.3
3 //page49
4
5 // for constant Ec=-1.5
6 Eb1=100 // V
7 Eb2=150 // V
8 Ib1=7.5d-3 // A
9 Ib2=12d-3 // A
10
11 Eb_diff=Eb2-Eb1
12 Ib_diff=Ib2-Ib1
13
14 rp=Eb_diff/Ib_diff
15 rp_kilo_ohm=rp/10^3 //kilo ohm
16
17 printf(" plate resistance = %.3f ohm or %.3f kilo ohm
          \n",rp,rp_kilo_ohm)
18
19 // for constant Eb=150
20 Ib1=5d-3 // A

```

```

21 Ib2=12d-3 // A
22 Ec1=-3 // V
23 Ec2=-1.5 // v
24
25 Ib_diff=Ib2-Ib1
26 Ec_diff=Ec2-Ec1
27
28 gm=Ib_diff/Ec_diff
29 gm_micro_mho=gm*10^6 // micro mho
30 printf("mutual conductance=%f mho or %.3f micro
           mho \n",gm,gm_micro_mho)
31
32 mu=rp*gm
33 printf("amplification factor = %.3f",mu)
34
35 //in book the answer of amplification factor i.e.
      51.852 is rounded off to 52

```

Scilab code Exa 3.4 Example 4

```

1 //chapter3
2 //example3.4
3 //page50
4
5 Eb=250 // V
6 Ec=-3 // V
7
8 // given that Ib=0.003*(Eb+30*Ec)^1.5 mA
9 // differentiating w.r.t Ec with Eb=constant , we get
10 gm=0.003*1.5*(Eb+30*Ec)^0.5*30*10^-3
11 mutual_inductance_micro=gm*10^6
12
13 printf("mutual conductance = %f mho or %.3f micro
           mho \n",gm,mutual_inductance_micro)
14

```

```

15 // differentiating given equation w.r.t Ec with Ib=
   constant , we get
16 // 0=0.003*10^-3*1.5*(Eb+Ec)^1.5*(mu+30) where mu is
   equal to ratio of changes in Eb and Ec i.e.
   amplification factor
17 // thus mu+30=0 hence we get
18 mu=-30
19     printf("here negative sign of amplification
           factor indicates that Eb and Ec are in
           opposite direction. \n \n")
20 // here we need not worry as to if mu may be
   positive because the equation given in problem
   statement will always give mu+30=0 i.e. mu=-30
21
22 printf("amplification factor = %.3f \n",mu)
23
24 rp=mu/gm
25 if rp<0      // rp can not be negative
26     rp=-rp
27 end
28
29 printf("plate resistance = %.3f ohm \n",rp)
30
31 //in book, the answers are less accurate. The
   accurate answers are
32 // gm=1707.630 micro mho
33 // plate resistance=17568.209 ohm

```

Scilab code Exa 3.5 Example 5

```

1 //chapter3
2 //example3.5
3 //page58
4
5 // use of Rsg = to obtain desired potential on

```

```

        screen grid since it is connected between power
        supply and screen grid
6 // use of Csg = to provide ac grounding for the
    screen
7
8 Ebb=300 // V
9 Ib=10d-3 // A
10 Rl=4.7d3 // ohm
11 Rk=68 // ohm
12 Isg=3d-3 // A
13 Vsg=150 // V
14
15 cathode_voltage=Ebb-(Ib*Rl)
16 grid_cathode_bias=-Rk*(Ib+Isg) // since current
    through cathode resistance is Ib+Isg
17 Rsg=(Ebb-Vsg)/Isg // since plate supply voltage =
    grid voltage + drop across Rsg
18 Rsg_kilo_ohm=Rsg/10^3 // in kilo ohm
19
20 printf("zero signal plate cathode voltage = %.3f V \
n",cathode_voltage)
21 printf("grid cathode bias = %.3f V \n",
    grid_cathode_bias)
22 printf("Resistor Rsg = %.3f ohm or %.3f kilo ohm \n"
    ,Rsg,Rsg_kilo_ohm)

```

Chapter 4

Vacuum tube rectifiers

Scilab code Exa 4.1 Example 1

```
1 //chapter4
2 //example4.1
3 //page68
4
5 rp=300 // ohm
6 Rl=1200 // ohm
7
8 Vm=200*2^0.5 //V
9 Im=Vm/(rp+Rl)
10 Idc=Im/%pi // in ampere
11 Idc_mA=Idc*1000 // in mA
12 Irms=Im/2
13 Irms_mA=Irms*1000
14 Pdc=Idc^2*Rl
15 Pac=Irms^2*(rp+Rl)
16 efficiency=(Pdc/Pac)*100
17
18 printf("dc current = %.3f A or %.3f mA \n",Idc ,
    Idc_mA)
19 printf("rms current = %.3f A or %.3f mA \n",Irms ,
    Irms_mA)
```

```
20 printf("rectification efficiency = %.2f percentage" ,  
         efficiency)  
21  
22 // accurate answer of rms current is 94.281 mA but  
   in book it is given as 94.5 mA
```

Scilab code Exa 4.2 Example 2

```
1 //chapter4  
2 //example4.2  
3 //page68  
4  
5 rp=200 // ohm  
6 Rl=800 // ohm  
7 Edc=100 // V  
8  
9 // if maximum ac voltage required=Vm then  
10 // Edc=Idc*Rl i.e. Edc=Vm*Rl/(%pi*(rp+Rl))  
11 // thus  
12  
13 Vm=Edc*%pi*(rp+Rl)/Rl  
14 efficiency=(0.406/(1+(rp/Rl)))*100  
15  
16 printf("required ac voltage = %.3f V \n" ,Vm)  
17 printf("rectification efficiency = %.3f percentage" ,  
         efficiency)
```

Scilab code Exa 4.3 Example 3

```
1 //chapter4  
2 //example4.3  
3 //page69  
4
```

```

5 Vm=1000 // V
6 rp=500 // ohm
7 Rl=4500 // ohm
8
9 Im=Vm/(rp+Rl) // in A
10 Idc=Im/%pi // in A
11 Idc_mA=Idc*1000 // in mA
12 Irms=Im/2 // since ac current is equal to rms
   current
13 Irms_mA=Irms*1000 // in mA
14 W=Irms^2*(rp+Rl) // in watts
15
16 printf("dc ammeter reading = %.3f A or %.3f mA \n" ,
   Idc , Idc_mA)
17 printf("reading of ac ammeter = %.3f A or %.3f mA \n"
   " , Irms , Irms_mA)
18 printf("reading of wattmeter = %.3f W" , W)

```

Scilab code Exa 17.4 Example 4

```

1 //chapter17
2 //example17.4
3 //page381
4
5 R=1d6 // ohm
6 C=68d-12 // F
7
8 fo=1/(2*%pi*R*C*(6)^0.5)
9 printf("frequency of oscillations = %.3f Hz" , fo)
10
11 // in book the answer given is 954 Hz but the
   accurate answer is 955.511 Hz

```

Scilab code Exa 4.4 Example 4

```
1 //chapter4
2 //example4.4
3 //page74
4
5 Vs=300 // V
6 rp=500 // ohm
7 Rl=2000 // ohm
8Vm=Vs*2^0.5 // in V
9 Im=Vm/(rp+Rl) // A
10 Idc=2*Im/%pi // A
11 Pdc=Idc^2*Rl // W
12 Irms=Im/2^0.5 //A
13 Pac=Irms^2*(rp+Rl) // W
14 efficiency=(Pdc/Pac)*100
15
16 printf("dc power output = %.3f W \n",Pdc)
17 printf("ac power input = %.3f W \n",Pac)
18 printf("efficiency = %.2f percentage",efficiency)
```

Scilab code Exa 4.5 Example 5

```
1 //chapter4
2 //example4.5
3 //page74
4
5Vm=1000 // V
6 rp=500 // ohm
7 Rl=4500 // ohm
8
9 Im=Vm/(rp+Rl) // in ampere
10 Idc=2*Im/%pi // in ampere
11 Idc_mA=Idc*1000 // in mA
12 Iac=Im/2^0.5 // in ampere
```

```
13 Iac_mA=Iac*1000 // in mA
14
15 printf("dc ammeter reading = %.3f A or %.3f mA \n",
16 Idc,Idc_mA)
17 printf("ac ammeter reading = %.3f A or %.3f mA",Iac,
Iac_mA)
```

Chapter 5

Vacuum tube amplifiers

Scilab code Exa 5.1 Example 1

```
1 //chspter5
2 //example5.1
3 //page85
4
5 mu=20
6 rp=10 // kilo ohm
7 Rl=15 // kilo ohm
8
9 Av=mu*Rl/(rp+Rl)
10
11 printf(" voltage gain = %.3f",Av)
```

Scilab code Exa 5.2 Example 2

```
1 //chspter5
2 //example5.2
3 //page85
4
```

```

5 mu=20
6 rp=10 // kilo ohm
7 Rl=15 // kilo ohm
8 Eg=3 // V
9
10 // the diagram in book is for understanding only.
    Also we do not have a block of "triode" in scilab
    xcos. The figure is not required to solve the
    problem.

11
12 Av=mu*Rl/(rp+Rl)
13 Ip=(mu*Eg/2^0.5)/(rp+Rl)
14 V_out=Ip*Rl
15
16 printf("voltage gain = %.3f \n",Av)
17 printf("load current = %.3f mA \n",Ip)
18 printf("output voltage = %.3f V" ,V_out)
19
20 // the accurate answer for output voltage is 25.456V
    but in book it is given as 25.35V

```

Scilab code Exa 5.3 Example 3

```

1 //chapter5
2 //example5.3
3 //page85
4
5 // for Rl=50, Av=30
6 // for Rl=85, Av=34
7
8 // Av=mu*Rl/(rp+Rl)
9 // thus
10 // Av*rp-mu*Rl==Av*rl
11 // substituting for Rl=50 and Rl=85 we get the
    following linear equations

```

```

12
13 // 30*rp -50*mu=-1500 and
14 // 34*rp -85*mu=-2890
15 // solving by matrix
16
17 a=[30 34 ; -50 -85]
18 b=[-1500 -2890]
19 solution=b/a
20 mu=solution(1,2)
21 rp=solution(1,1) // in kilo ohms since RL was in
    kilo ohm in the equations
22
23 gm_kilo_mho=mu/rp
24 gm=gm_kilo_mho/1000
25 printf("mu = %.3f \n",mu)
26 printf("rp = %.3f kilo ohm \n",rp)
27 printf("gm = %.4f mho \n",gm)

```

Scilab code Exa 5.4 Example 4

```

1 //chapter5
2 //example5.4
3 //page86
4
5 mu=6
6 Eg=9 // V
7 rp=2400 // ohm
8 Rl=3000 // ohm
9
10 Ip=mu*Eg/(rp+Rl) // A
11 power=Ip^2*Rl // W
12
13 printf("ac power in load = %.3f W",power)

```

Scilab code Exa 5.5 Example 5

```
1 //chapter5
2 //example5.5
3 //page95
4
5 rp=1000 // ohm
6 Rl=10 // ohm
7 Eg=8 // V
8 mu=20
9
10 // the diagram in book is for understanding only.
    Also we do not have a block of "triode" in scilab
    xcos. The figure is not required to solve the
    problem.
11 // however, the equivalent circuit has been drawn in
    xcos for reference.
12
13 // since rp=n^2*Rl for maximum power transfer so
14 n=(rp/Rl)^0.5
15
16 // P_max=Ip ^2*RE where Ip=mu*Eg/( rp+RE) and RE=rp
17 // thus
18 P_max=((mu*Eg)^2)/(4*rp)
19
20 printf("transformation ratio n= %.2f \n",n)
21 printf("power supplied to speaker when signal is 8V
    rms is = %.3f W",P_max)
```

Chapter 9

Semiconductor diode

Scilab code Exa 9.1 Example 1

```
1 //chapter9
2 //example9.1
3 //page142
4
5 printf("in fig. (i), the conventional current coming
       out of battery flows in the \nbranch circuits .
       In diode D1, the conventional current flows in the
       \ndirection of arrowhead and hence this diode is
       forward biased. \nHowever in diode D2, the
       conventional current flows opposite \nto
       arrowhead and hence this diode is reverse biased
       .\n \n")
6 printf("in fig. (ii), During the positive half cycle
       of input ac voltage , the \nconventional current
       flows in the direction of arrowhead and hence
       diode \nis forward biased. However , during the
       negative half cycle \nof input ac voltage , the
       diode is reverse biased.\n \n")
7 printf("in fig. (iii), During the positive half
       cycle of input ac voltage , the \nconventional
       current flows in the direction of arrowhead in D1
```

but it flows \n opposite to arrowhead in D2. So during positive half cycle , \ndiode D1 is forward biased and diode D2 is reverse biased. \nHowever in the negative half cycle of the input ac voltage , diode D2 \nis forward biased and diode D1 is reverse biased.\n \n")

8 **printf**("in fig . (iv) , During the positive half cycle of input ac voltage , \nboth diodes are reverse biased. However in the negative half cycle of the \ninput ac voltage , both diodes are forward biased.\n \n")

Scilab code Exa 9.2 Example 2

```
1 //chapter9
2 //example9.2
3 //page145
4
5 Vi_p=20 // V
6 rf=10 // ohm
7 Rl=500 // ohm
8 Vo=0.7 // V
9 Vin=20 // V
10
11 // peak current through diode will occur when Vin=Vf
   so
12 Vf=Vin
13 // since Vf=Vo+If_peak ( rf+Rl) making If_peak as
   subject we get
14 If_peak1=(Vf-Vo)/(rf+Rl) // in ampere
15 Vout_peak1=If_peak1*Rl
16
17 // for ideal diode , Vo=0 and rf=0 so
18 // Vf=If_peak*Rl so we get
19 If_peak2=Vf/Rl // in ampere
```

```
20 Vout_peak2=If_peak2*R1
21
22 printf(" peak current through given diode = %.3f mA
23 and peak output voltage = %.3f V \n",If_peak1
24 *1000,Vout_peak1)
25 printf("peak current through ideal diode = %.3f mA
26 and peak output voltage = %.3f V \n",If_peak2
27 *1000,Vout_peak2)
```

Scilab code Exa 9.3 Example 3

```
1 //chapter9
2 //example9.3
3 //page146
4
5 R1=50 // ohm
6 R2=5 // ohm
7 V=10 // V
8
9 Eo=V*R2/(R1+R2) // thevenin voltage
10 Ro=R1*R2/(R1+R2) // thevenin resistance
11 I_D=Eo/Ro // current through diode in ampere
12
13 printf("current through diode = %.3f mA \n",I_D
14 *1000)
```

Scilab code Exa 9.4 Example 4

```
1 //chapter9
2 //example9.4
3 //page146
4
5 V=10 // V
```

```

6 V_D1=0.7 // V
7 V_D2=0.7 // V
8 R=48 // ohm
9 R_D1=1 // ohm
10 R_D2=1 // ohm
11
12 // D1 and D3 are forward biased while D2 and D4 are
   reverse biased thus
13 V_net=V-V_D1-V_D2
14 R_t=R_D1+R+R_D2
15 I=V_net/R_t
16
17 printf("circuit current = %.3f mA \n",I*1000)

```

Scilab code Exa 9.5 Example 5

```

1 //chapter9
2 //example9.5
3 //page147
4
5 E1=24 // V
6 E2=4 // V
7 Vo=0.7 // V
8 R=2 // kilo ohm
9
10 // diode D1 is forward biased and diode D2 is
    reverse biased so
11 I=(E1-E2-Vo)/R
12
13 printf("current in the circuit = %.3f mA \n",I)

```

Scilab code Exa 9.6 Example 6

```

1 //chapter9
2 //example9.6
3 //page147
4
5 V=20 // V
6 V_D_Ge=0.3 // V
7
8 // when voltage is applied , Ge diode turns on first
   and 0.3 V is maintained across circuit so Si
   diode never turns on. So
9 V_A=V-V_D_Ge
10
11 printf(" voltage V_A at point A = %.3f V \n",V_A)

```

Scilab code Exa 9.7 Example 7

```

1 //chapter9
2 //example9.7
3 //page148
4
5 V=10 // V
6 V_D=0.7 // V
7 R_BC=2 // kilo ohm
8 R=2 // kilo ohm
9
10 // by Kirchoff voltage law we get
11 // -V_D-I_D*R_BC-2*I_D*R+V=0 thus making I_D as
   subject we get
12 I_D=(V-V_D)/(R_BC+2*R)
13 V_Q=2*I_D*R
14
15 printf("I_D = %.3f mA \n",I_D)
16 printf("V_Q = %.3f V \n",V_Q)

```

Scilab code Exa 9.8 Example 8

```
1 //chapter9
2 //example9.8
3 //page148
4
5 V=15 // V
6 R=0.5 // kilo ohm
7 V_D=0.7 // V
8
9 // both diodes are forward biased
10
11 I1=(V-V_D)/R
12 I_D1=I1/2
13 I_D2=I_D1
14
15 printf("current through diode D1 = %.3f mA and diode
D2 = %.3f mA \n", I_D1, I_D2)
```

Scilab code Exa 9.9 Example 9

```
1 //chapter9
2 //example9.9
3 //page151
4
5 P_dc=40 // W
6 P_ac=100 // W
7
8 efficiency=100*P_dc/P_ac
9
10 printf("rectification efficiency = %.3f percent \n \
n", efficiency)
```

```
11 printf("remaining 60 watts are not lost. Crystal  
diode consumes only a \nlittle power due to its  
small internal resistance. \nActualy 100 W ac  
power is contained as 50 W in positive half \n  
cycle and 50 W in negative half cycle.\nThe 50 W  
of negative half cycle are not supplied at all.  
\nThe 50 W of positive half cycle are converted  
to 40 W \n")
```

Scilab code Exa 9.10 Example 10

```
1 //chapter9  
2 //example9.10  
3 //page152  
4  
5 n=10  
6 Vp=230 // V  
7  
8 Vpm=2^0.5*Vp  
9 Vsm=Vpm/n // since n=Vpm/Vsm=N1/N2  
10  
11 // Idc=Im/%pi and Vdc=Idc*Rl so  
12 // Vdc=(Im/%pi)*Rl . Also Im*Rl=Vsm so  
13 Vdc=Vsm/%pi  
14  
15 // in negative half cycle diode is reverse biased so  
// maximum secondary voltage appears across diode.  
16 PIV=Vsm  
17  
18 printf("output dc voltage = %.2f V \n",Vdc)  
19 printf("peak inverse voltage = %.2f V \n",PIV)  
20  
21 // accurate answer for output dc voltage is 10.35 V  
not 10.36 V
```

Scilab code Exa 9.11 Example 11

```
1 //chapter9
2 //example9.11
3 //page152
4
5 rf=20 // ohm
6 Rl=800 // ohm
7 Vm=50 // V
8
9 Im=Vm/(rf+Rl) // in ampere
10 Idc=Im/%pi // in ampere
11 Irms=Im/2 // in ampere
12 Pac=Irms^2*(rf+Rl)
13 Pdc=Idc^2*Rl
14 Vout=Idc*Rl
15 efficiency=100*Pdc/Pac
16
17 printf("Im = %.1f mA \n",Im*1000)
18 printf("Idc = %.1f mA \n",Idc*1000)
19 printf("Irms = %.1f mA \n \n",Irms*1000)
20 printf("ac power input = %.3f W \n",Pac)
21 printf("dc power output = %.3f W \n \n",Pdc)
22 printf("dc output voltage = %.3f V \n \n",Vout)
23 printf("efficiency = %.3f percent \n",efficiency)
```

Scilab code Exa 9.12 Example 12

```
1 //chapter9
2 //example9.12
3 //page153
4
```

```

5 Vdc=50 // V
6 rf=25 // ohm
7 Rl=800 // ohm
8
9 // Vdc=Idc*Rl and Idc=Im/%pi so
10 // Vdc=Im*Rl/%pi
11 // but Im=Vm/(rf+Rl) so
12 // Vdc=Vm*Rl/(%pi*(rf+Rl))
13 // making Vm as subject we get
14
15 Vm=Vdc*%pi*(rf+Rl)/Rl
16
17 printf("ac voltage required = %.1f V \n",Vm)

```

Scilab code Exa 9.13 Example 13

```

1 //chapter9
2 //example9.13
3 //page157
4
5 rf=20 // ohm
6 Rl=980 // ohm
7 Vs=50 // V
8
9 Vm=Vs*2^0.5
10 Im=Vm/(rf+Rl)
11 Idc=2*Im/%pi // in ampere
12 Irms=Im/2^0.5 // in ampere
13
14 printf("mean load current = %.3f mA \n",Idc*1000)
15 printf("rms load current = %.3f mA \n",Irms*1000)

```

Scilab code Exa 19.14 power

```

1 //chapter19
2 //example19.14
3 //page424
4
5 Vc=5 // V
6 V_lower=2.5 // V
7 V_upper=2.5 // V
8 R=2 // kilo ohm
9
10 // figure given in book is just for understanding
   purpose. It is not a part of solution.
11 // however, the figure has been made in xcos and
   screenshot has been attached for reference
12
13 // since power=(rms voltage)^2/R we get
14
15 Pc=(0.707*Vc)^2/R
16 P_lower=(0.707*V_lower)^2/R
17 P_upper=(0.707*V_upper)^2/R
18 Pt=Pc+P_lower+P_upper
19
20 printf("power delivered by carrier = %.3f mW \n",Pc)
21 printf("power delivered by lower sideband = %.3f mW
   \n",P_lower)
22 printf("power delivered by upper sideband = %.3f mW
   \n",P_upper)
23 printf("total power delivered by AM wave = %.3f mW \
   \n",Pt)

```

Scilab code Exa 9.14 Example 14

```

1 //chapter9
2 //example9.14
3 //page157
4

```

```

5 rf=0
6 n=5
7 Vp=230 // V rms
8 Rl=100 //ohm
9
10 Vs=Vp/n // V rms
11 Vsm=Vs*2^0.5 // maximum voltage across secondary
12Vm=Vsm/2 // maximum voltage across half secondary
   winding
13
14 Idc=2*Vm/(%pi*Rl)
15 Vdc=Idc*Rl
16 PIV=Vsm
17 efficiency=100*0.812/(1+rf/Rl)
18
19 printf("dc output voltage = %.3f V \n",Vdc)
20 printf("PIV = %.3f V \n",PIV)
21 printf("efficiency = %.3f percent \n",efficiency)

```

Scilab code Exa 9.15 Example 15

```

1 //chapter9
2 //example9.15
3 //page158
4
5 n=4
6 Rl=200 // ohm
7 fin=50 // Hz
8 Vp=230 // V rms
9
10 Vs=Vp/n // V rms
11 Vsm=Vs*2^0.5 // maximum voltage across secondary
12
13 Idc=2*Vsm/(%pi*Rl)
14 Vdc=Idc*Rl

```

```

15 PIV=Vs_m
16
17 // in full wave rectifier , output frequency is twice
   input frequency since there are two ouput pulses
   for each cycle of input
18 f_out=2*f_in
19
20 printf("dc output voltage = %.3f V \n",Vdc)
21 printf("peak inverse voltage = %.3f V \n",PIV)
22 printf("output frequency = %.3f Hz",f_out)
23
24 // the accurate answer for dc output voltage is
   51.768 V but in book it is given as 52 V

```

Scilab code Exa 9.16 Example 16

```

1 //chapter9
2 //example9.16
3 //page158
4
5 // for dc output
6   // for centre-tap circuit
7   n=5
8   Vp=230 // V rms
9   Rl=100 //ohm
10  Vs=Vp/n // V rms
11  Vs_m=Vs*2^0.5 // maximum voltage across
      secondary
12  Vm=Vs_m/2 // maximum voltage across half
      secondary winding
13  Vdc=2*Vm/%pi // since Vdc=Idc*Rl and Idc=2*
      Vm/(%pi*Rl)
14
15 // for bridge circuit
16 n_dash=5

```

```

17     Vp_dash=230 // V rms
18     Rl_dash=100 //ohm
19     Vs_dash=Vp_dash/n_dash// V rms
20     Vsm_dash=Vs*2^0.5 // maximum voltage across
        secondary
21    Vm_dash=Vsm_dash
22     Vdc_dash=2*Vm_dash/%pi // since Vdc=Idc*Rl
        and Idc=2*Vm/(%pi*Rl)
23
24
25 // for same dc output Vm must be same for both
circuits i.e. n=5 for centre-tap and n=10 for
bridge
26 // for centre-tap circuit
27 n1=5
28 Vs1=Vp/n1 // V rms
29 Vsm1=Vs1*2^0.5 // maximum voltage across
secondary
30 Vm1=Vsm1/2
31 PIV1=2*Vm1
32
33 // for bridge circuit
34 n2=5
35 Vs2=Vp/n2 // V rms
36 Vsm2=Vs2*2^0.5 // maximum voltage across
secondary
37 Vm2=Vsm2/2
38 PIV2=Vm2
39
40 printf("dc output voltage for centre-tap circuit = %
.3f V \n",Vdc)
41 printf("dc output voltage for bridge circuit = %.3f
V \n \n",Vdc_dash)
42
43 printf("for same output , PIV for centre-tap circuit
= %.3f V and bridge circuit = %.3f V \n",PIV1,
PIV2)
44

```

```
45 // the figure of transformer is for reference only.  
// Also it cannot be plotted in scilab since scilab  
// does not have centre-tap transformer
```

Scilab code Exa 9.17 Example 17

```
1 //chapter9  
2 //example9.17  
3 //page160  
4  
5 Vin=240 // V rms  
6 Rl=480 // ohm  
7 rf=1 // ohm  
8  
9 Vm=Vin*2^0.5  
10 // for bridge rectifier we know that  
11 Im=Vm/(2*rf+Rl)  
12 Idc=2*Im/%pi  
13 Irms=Im/2  
14 P=Irms^2*rf  
15  
16 printf("mean load current = %.3f A \n",Idc)  
17 printf("power dissipated in each diode = %.3f W \n",  
P)  
18  
19 // the accurate answers are mean load current =  
// 0.448 A and power dissipated in each diode =  
// 0.124 W
```

Scilab code Exa 9.18 Example 18

```
1 //chapter9  
2 //example9.18
```

```

3 //page162
4
5 Vrms_A=0.5 // V
6 Vdc_A=10 // V
7 Vrms_B=1 // V
8 Vdc_B=25 // V
9
10 ripple_A=Vrms_A/Vdc_A
11 ripple_B=Vrms_B/Vdc_B
12
13 if ripple_A>ripple_B
14     printf("power supply B is better \n")
15 elseif ripple_B>ripple_A
16     printf("power supply A is better \n")
17 else
18     printf("both are equal \n")
19 end

```

Scilab code Exa 9.19 Example 19

```

1 //chapter9
2 //example9.19
3 //page165
4
5 // the waveform given in book is for understanding
   only. It is not required to solve the problem.
   Also it cannot be plotted in scilab unless Vm and
   Vdc are given.
6
7 R=25 // ohm
8 Rl=750 // ohm
9 Vm=25.7 // V
10
11 Vdc_dash=2*Vm/%pi
12 Vdc=Vdc_dash*Rl/(R+Rl)

```

```
13
14 printf("voltage across load is %.3f V plus a small
15      ripple \n",Vdc)
16 // the accurate answer is 15.833 V but in book it is
17      given as 15.9 V
```

Scilab code Exa 9.20 Example 20

```
1 //chapter9
2 //example9.20
3 //page170
4
5 R=5 // kilo ohm
6 Rl=10 // kilo ohm
7 Ei=120 // V
8 Vz=50 // V
9
10 V=Ei*Rl/(R+Rl) // voltage across open circuit if
11      zener diode is removed
12 Vo=Vz // output voltage
13 V_R=Ei-Vz // drop across R
14 I1=Vz/Rl // load current
15 I=V_R/R // current through R
16 // by Kirchoff first law I=Iz+I1
17 Iz=I-I1
18
19 printf("output voltage = %.3f V \n",Vo)
20 printf("voltage drop across series resistance = %.3f
21      V \n",V_R)
22 printf("current through Zener diode = %.3f mA \n",Iz
)
```

Scilab code Exa 9.21 Example 21

```
1 //chapter9
2 //example9.21
3 //page171
4
5 Vmax=120 // V
6 Vmin=80 // V
7 Vz=50 // V
8 R_L=10 // kilo ohm
9 R1=5 // kilo ohm
10
11 // zener diode is on for Vmax and Vmin both since
   they are > Vz
12
13 // for max Iz
14     V_R1=Vmax-Vz
15     I=V_R1/R1 // current through R1
16     I_L=Vz/R_L // current through load
17     // by Kirchoff first law I=I_L+Iz so applying it
       we get
18     Iz_max=I-I_L
19
20 // for min Iz
21     V_R1_dash=Vmin-Vz
22     I_dash=V_R1_dash/R1 // current through R1
23     I_L_dash=Vz/R_L // current through load
24     // by Kirchoff first law I=I_L+Iz so we get
25     Iz_min=I_dash-I_L_dash
26
27 printf("maximum zener current = %.3f mA \n",Iz_max)
28 printf("minimum zener current = %.3f mA \n",Iz_min)
```

Scilab code Exa 9.22 Example 22

```
1 //chapter9
2 //example9.22
3 //page172
4
5 Ei=12 // V
6 Vz=7.2 // V
7 Eo=Vz
8 Iz_min=10d-3 // A
9 Il_max=100d-3 // A
10
11 // we see that R=(Ei-Eo)/(Iz-Il) and minimum Iz
   occurs when Il is maximum so
12 R=(Ei-Eo)/(Iz_min+Il_max)
13
14 printf("required series resistance = %.3f ohm \n",R)
15
16 // on inserting this series resistance the output
   voltage will remain constant at 7.2 V
17
18 // the accurate answer is 43.636 ohm but in book it
   is given as 43.5 ohm
```

Scilab code Exa 9.23 Example 23

```
1 //chapter9
2 //example9.23
3 //page172
4
5 Ei=22 // V
6 Vz=18 // V
```

```

7 Rl=18 // ohm
8 Eo=Vz
9 Iz_min=200d-3 // A
10
11 // Zener current will be min when input voltage is
min
12
13 // load current is
14 Il_max=Vz/Rl
15
16 // we see that  $R = (E_i - E_o) / (I_z - I_l)$  and minimum  $I_z$ 
occurs when  $I_l$  is maximum so
17 R=(Ei-Eo)/(Iz_min+Il_max)
18
19 printf("required series resistance = %.3f ohm \n",R)
20
21 // on inserting this series resistance the output
voltage will remain constant at 18 V

```

Scilab code Exa 9.24 Example 24

```

1 //chapter9
2 //example9.24
3 //page172
4
5 Ei=13 // V
6 Vz=10 // V
7 Eo=Vz
8 Iz_min=15d-3 // A
9 Il_max=85d-3 // A
10
11 // Zener current will be min when input voltage is
min
12
13 // we see that  $R = (E_i - E_o) / (I_z - I_l)$  and minimum  $I_z$ 

```

```
    occurs when Il is maximum so
14 R=(Ei-Eo)/(Iz_min+Il_max)
15
16 printf(" required series resistance = %.3f ohm \n",R)
```

Scilab code Exa 9.25 Example 25

```
1 //chapter9
2 //example9.25
3 //page173
4
5 Ei=45 // V
6 Vz1=15 // V
7 Vz2=15 // V
8 Iz=200d-3 // current rating for each zener in ampere
9
10 Eo=Vz1+Vz2
11
12 R=(Ei-Eo)/Iz
13
14 printf(" regulated output voltage = %.3f V \n",Eo)
15 printf(" required series resistance = %.3f ohm \n",R)
```

Scilab code Exa 9.26 Example 26

```
1 //chapter9
2 //example9.26
3 //page173
4
5 Ei=45 // V
6 Vz1=10 // V
7 Vz2=10 // V
8 Vz3=10 // V
```

```

9 Iz=1000d-3 // current rating for each zener in
   ampere
10
11 Eo=Vz1+Vz2+Vz3
12
13 R=(Ei-Eo)/Iz
14
15 printf(" required series resistance = %.3f ohm \n",R)
16
17 // since zener diode is not available in xcos ,
   simple diodes are used to represent zener diode
   in the circuit made in xcos

```

Scilab code Exa 9.27 Example 27

```

1 //chapter9
2 //example9.27
3 //page174
4
5 R=200 // ohm
6 Rl=2000 // ohm
7 Eo=30 // V
8
9 // for minimum input voltage i.e. Iz=0
10 Il=Eo/Rl
11 I=Il // since Iz=0
12 Vin_min=Eo+I*R
13
14 // for maximum input voltage i.e. Iz=25 mA
15 Iz=25d-3 // A
16 Il_dash=Eo/Rl
17 I_dash=Il_dash+Iz
18 Vin_max=Eo+I_dash*R
19
20 printf(" minimum input voltage = %.3f V \n",Vin_min)

```

```
21 printf("maximum input voltage = %.3f V \n",Vin_max)
22 printf("thus range of input = %.3f to %.3f V \n",
    Vin_min,Vin_max)
```

Scilab code Exa 9.28 Example 28

```
1 //chapter9
2 //example9.28
3 //page174
4
5 Ei=16 // V
6 Vz=12 // V      since we want to regulate at 12 V
7 Eo=Vz
8 Iz_min=0 // A
9 Il_max=200d-3 // A
10
11 // Zener current will be min when input voltage is
   min
12
13 // we see that R=(Ei-Eo)/(Iz-Il) and minimum Iz
   occurs when Il is maximum so
14 R=(Ei-Eo)/(Iz_min+Il_max)
15
16 Izm=Il_max
17 Pzm=Vz*Izm
18
19 printf("Zener voltage = %.3f V \n",Vz)
20 printf("required series resistance = %.3f ohm \n",R)
21 printf("maximum power rating of zener diode = %.3f W
   \n",Pzm)
```

Chapter 10

Special purpose diodes

Scilab code Exa 10.1 required series resistor

```
1 //chapter10
2 //example10.1
3 //page182
4
5 Vs=10 // V
6 Vd=1.6 // V
7 If=20d-3 // A
8
9 Rs=(Vs-Vd)/If
10
11 printf(" required series resistor = %.3f ohm" ,Rs)
```

Scilab code Exa 10.2 current through LED

```
1 //chapter10
2 //example10.2
3 //page183
4
```

```
5 Vs=15 // V
6 Vd=2 // V
7 Rs=2.2d3 // ohm
8
9 If=(Vs-Vd)/Rs
10
11 printf("current through LED = %.3f A or %.3f mA",If,
    If*1000)
```

Scilab code Exa 10.3 dark resistance

```
1 //chapter10
2 //example10.3
3 //page187
4
5 //from graph , we see that for zero illumination , the
      reverse current i.e. dark current is 50 micro
      ampere
6
7 Ir=50d-6 // A
8 Vr=10 // V
9
10 Rr=Vr/Ir
11
12 printf("dark resistance = %.3f ohm or %.3f kilo ohm"
    ,Rr,Rr/1000)
```

Scilab code Exa 10.4 reverse current

```
1 //chapter10
2 //example10.4
3 //page188
4
```

```
5 m=37.4 // microA/mW/cm^2
6 E=2.5 // mW/cm^2
7
8 //since reverse current = sensitivity*illumination
   we can write
9 Ir=m*E
10
11 printf("reverse current = %.3f micro ampere",Ir)
```

Scilab code Exa 10.5 resonant frequency

```
1 //chapter10
2 //example10.5
3 //page192
4
5 L=1d-3 // H
6 C=100d-12 // F
7
8 fr=1/(2*%pi*(L*C)^0.5)
9
10 printf("resonant frequency = %.3f Hz or %.3f kHz",fr
      ,fr/1000)
```

Scilab code Exa 10.11 base current

```
1 //chapter11
2 //example11.11
3 //page210
4
5 V_Rc=1
6 gain_beta=45
7 Rc=1 // kilo ohm
8
```

```
9 Ic=V_Rc/Rc
10 //since gain_beta=Ic/Ib
11 Ib=Ic/gain_beta
12
13 printf("base current = %.3f mA", Ib)
```

Chapter 11

Transistors

Scilab code Exa 11.1 voltage amplification

```
1 //chapter11
2 //example11.1
3 //page202
4
5 Rin=20 //ohm
6 Rout=100d3 //ohm
7 Rc=1d3 //ohm
8 signal=500d-3 //V
9
10 Ie=signal/Rin // A
11 Ic=Ie
12 Vout=Ic*Rc
13 Av=Vout/signal
14
15 printf(" voltage amplification = %.2f \n",Av)
```

Scilab code Exa 11.2 base current

```
1 //chapter11
2 //example11.2
3 //page205
4
5 Ie=1 //mA
6 Ic=0.95 //mA
7
8 // since Ie=Ib+Ic we get
9 Ib=Ie-Ic
10
11 printf("base current = %.3f mA \n", Ib)
```

Scilab code Exa 11.3 base current

```
1 //chapter11
2 //example11.3
3 //page205
4
5 alpha=0.9
6 Ie=1 //mA
7
8 // since alpha=Ic/Ie we get
9
10 Ic=alpha*Ie
11
12 // since Ie=Ic+Ib we get
13
14 Ib=Ie-Ic
15
16 printf("base current = %.3f mA \n", Ib)
```

Scilab code Exa 11.4 amplification factor

```
1 //chapter11
2 //example11.4
3 //page205
4
5 Ic=0.95
6 Ib=0.05
7
8 Ie=Ib+Ic
9 alpha=Ic/Ie
10
11 printf("amplification factor = %.3f \n",alpha)
```

Scilab code Exa 11.5 collector current

```
1 //chapter11
2 //example11.5
3 //page205
4
5 Ie=1 //mA
6 alpha=0.92
7 Icbo=50d-3 //mA
8
9 Ic=alpha*Ie+Icbo
10
11 printf("collector current = %.3f mA \n",Ic)
```

Scilab code Exa 11.6 base current

```
1 //chapter11
2 //example11.6
3 //page205
4
5 alpha=0.95
```

```

6 V_Rc=2 // V
7 Rc=2 // kilo ohm
8
9 Ic=V_Rc/Rc // mA
10
11 // since alpha=Ic/Ie
12 Ie=Ic/alpha
13
14 // since Ie=Ib+Ic
15 Ib=Ie-Ic
16
17 printf("base current = %.3f mA \n", Ib)

```

Scilab code Exa 11.7 collector current

```

1 //chapter11
2 //example11.7
3 //page206
4
5 Vbe=0.7 // V
6 Vcc=18 // V
7 Vee=8 // V
8 Rc=1.2 // kilo ohm
9 Re=1.5 // kilo ohm
10
11 // by Kirchoff's voltage law to emitter side loop ,
   we get Vee=Ie*Re+Vbe so
12 Ie=(Vee-Vbe)/Re
13 Ic=Ie // nearly
14
15 // by Kirchoff's voltage law to collector side loop ,
   we get Vcc=Ic*Rc=Vcb so
16 Vcb=Vcc-Ic*Rc
17
18 printf("collector current = %.3f mA \n", Ic)

```

```
19 printf(" collector base voltage = %3f V \n",Vcb)
```

Scilab code Exa 11.8 Example 8

```
1 //chapter11
2 //example11.8
3 //page209
4
5 alpha1=0.9
6 alpha2=0.98
7 alpha3=0.99
8
9 beta1=alpha1/(1-alpha1)
10 beta2=alpha2/(1-alpha2)
11 beta3=alpha3/(1-alpha3)
12
13 printf(" for alpha=0.9, beta=%.1f \n",beta1)
14 printf(" for alpha=0.98, beta=% .1f \n",beta2)
15 printf(" for alpha=0.99, beta=% .1f \n",beta3)
```

Scilab code Exa 11.9 Example 9

```
1 //chapter11
2 //example11.9
3 //page210
4
5 gain_beta=50
6 Ib=20d-3 // mA
7
8 // since gain_beta = Ic/Ib we get
9 Ic=gain_beta*Ib
10 Ie=Ic+Ib
11
```

```
12 printf("emitter current = %.3f mA \n", Ie)
```

Scilab code Exa 11.10 collector current

```
1 //chapter11
2 //example11.10
3 //page210
4
5 gain_beta=49
6 Ib=240d-3 // mA
7 Ie=12 // mA
8
9 alpha=gain_beta/(1+gain_beta)
10 Ic=alpha*Ie // or Ic=gain_beta*Ib
11
12 printf("collector current = %.3f mA \n", Ic)
```

Scilab code Exa 11.11 base current

```
1 //chapter11
2 //example11.11
3 //page210
4
5 V_Rc=1
6 gain_beta=45
7 Rc=1 // kilo ohm
8
9 Ic=V_Rc/Rc
10 //since gain_beta=Ic/Ib
11 Ib=Ic/gain_beta
12
13 printf("base current = %.3f mA", Ib)
```

Scilab code Exa 11.12 collector emitter voltage

```
1 //chapter11
2 //example11.12
3 //page210
4
5 Rc=800d-3 // kilo ohm
6 V_Rc=0.5 // V
7 Vcc=8 // V
8 alpha=0.96
9
10 Vce=Vcc-V_Rc
11 Ic=V_Rc/Rc // mA
12 gain_beta=alpha/(1-alpha)
13 Ib=Ic/gain_beta
14
15 printf(" collector emitter voltage = %.3f V \n" ,Vce)
16 printf(" base current = %.3f mA \n" ,Ib)
```

Scilab code Exa 11.13 base current

```
1 //chapter11
2 //example11.13
3 //page211
4
5 Ic=1000 // micro ampere
6 // when emitter circuit is open, leakage current =
   Icbo so
7 Icbo=0.2 // micro ampere
8
9 // when base is open, leakage current = Icbo so
10 Icbo=20 // micro ampere
```

```

11
12 // since  $I_{ceo} = I_{cbo}/(1 - \alpha)$  we get
13  $\alpha = 1 - (I_{cbo}/I_{ceo})$ 
14
15 // since  $I_c = \alpha * I_e + I_{cbo}$  we get
16  $I_e = (I_c - I_{cbo})/\alpha$ 
17  $I_b = I_e - I_c$ 
18
19 printf("alpha = %.3f \n", alpha)
20 printf("emitter current = %.3f micro ampere \n", Ie)
21 printf("base current = %.3f micro ampere \n", Ib)

```

Scilab code Exa 11.14 dc load line

```

1 //chapter11
2 //example11.14
3 //page218
4
5 Vcc=12.5 // V
6 Rc=2.5 // kilo ohm
7
8 // we know that  $V_{ce} = V_{cc} - I_c * R_c$ 
9 // when  $I_c = 0$ ,  $V_{ce} = V_{cc}$  i.e. 12.5V
10 // when  $V_{ce} = 0$ ,  $I_c = V_{cc}/R_c$  i.e. 5mA
11
12 // so equation of load line becomes  $I_c = -0.4 * V_{ce} + 5$ 
13 x=linspace(0,12.5,5)
14 y=-0.4*x+5
15 clf()
16 xtitle("dc load line","Vce(volts)","Ic(mA)")
17 plot2d(x,y,style=3,rect=[0,0,13,6])

```

Scilab code Exa 11.15 Q point

```

1 //chapter11
2 //example11.15
3 //page219
4
5 Vcc=12 // V
6 Rc=6 // kilo ohm
7
8 // we know that Vce=Vcc-Ic*Rc
9 // when Ic=0, Vce=Vcc i.e. 12V
10 // when Vce=0, Ic=Vcc/Rc i.e.2mA
11
12 // so equation of load line becomes Ic=-(1/6)*Vce+2
13 x=linspace(0,12,5)
14 y=-(1/6)*x+2
15 clf()
16 xtitle("dc load line","Vce(volts)","Ic(mA)")
17 plot2d(x,y,style=3,rect=[0,0,13,6])
18
19
20 // for Q point
21 Ib=20d-3 // mA
22 gain_beta=50
23
24 Ic=gain_beta*Ib
25 Vce=Vcc-Ic*Rc
26
27 printf("Q point = %.3f V and %.3f mA i.e. (%.3f ,%.3f
) \n",Vce,Ic,Vce,Ic)

```

Scilab code Exa 11.16 collector load

```

1 //chapter11
2 //example11.16
3 //page219
4

```

```
5 Vcc=10
6 Ic=1 // mA
7 Rc1=4 // kilo ohm
8 Rc2=5 // kilo ohm
9
10 Vce1=Vcc-Ic*Rc1
11 Vce2=Vcc-Ic*Rc2
12
13 printf("for collector load = 4 kilo ohm, operating
           point is %.3f V,%.3f mA \n",Vce1,Ic)
14 printf("for collector load = 5 kilo ohm, operating
           point is %.3f V,%.3f mA \n",Vce2,Ic)
```

Scilab code Exa 11.17 input resistance

```
1 //chapter11
2 //example11.17
3 //page222
4
5 del_Vbe=200 //mV
6 del_Ib=100 // micro ampere
7
8 Ri=del_Vbe/del_Ib
9
10 printf("input resistance = %.3f kilo ohm \n",Ri)
```

Scilab code Exa 11.18 output resistance

```
1 //chapter11
2 //example11.18
3 //page222
4
5 Vce2=10 // V
```

```

6 Vce1=2 // V
7 Ic1=2 // mA
8 Ic2=3 // mA
9
10 del_Vce=Vce2-Vce1 // V
11 del_Ic=Ic2-Ic1 // mA
12
13 Ro=del_Vce/del_Ic
14
15 printf("output resistance = %.3f kilo ohm \n",Ro)

```

Scilab code Exa 11.19 voltage gain

```

1 //chapter11
2 //example11.19
3 //page223
4
5 Rc=2 // kilo ohm
6 Ri=1 // kilo ohm
7 gain_beta=50
8
9 // for single stage, R_AC=Rc so voltage gain becomes
10 Av=gain_beta*Rc/Ri
11
12 printf("voltage gain = %.3f \n",Av)

```

Scilab code Exa 11.20 saturation collector current

```

1 //chapter11
2 //example11.20
3 //page224
4
5 Vcc=20 // V

```

```

6 Rc=1 // kilo ohm
7
8 // for saturation collector current , knee voltage
   becomes 0V so we get
9 Ic_sat=Vcc/Rc
10
11 // it can be seen from the circuit that cut-off
    voltage (i.e. when Ib=0) equals Vcc itself
12 Vce_cutoff=Vcc
13
14 // the equation of load line becomes Ic=-Vce+20
15
16 clf()
17 x=linspace(0,20,5)
18 y=-x+20
19 plot2d(x,y,style=3,rect=[0,0,21,21])
20 xtitle("dc load line","Vce(volts)","Ic(mA)")
21
22 printf("saturation collector current = %.3f mA \n",
         Ic_sat)
23 printf("cut-off collector emitter voltage = %.3f V \
         \n",Vce_cutoff)

```

Scilab code Exa 11.21 maximum allowable collector current

```

1 //chapter11
2 //example11.21
3 //page225
4
5 Vce=20 // V
6 Pd=100 // mW
7
8 // since Pd=Vce*Ic we get
9 Ic=Pd/Vce
10

```

```
11 printf("maximum allowable collector current = %.3f  
mA \n ", Ic)
```

Chapter 12

Transistor biasing

Scilab code Exa 12.1 circuit diagram

```
1 // chapter 12
2 // example 12.1
3 // page 235
4
5 V_CC=6 // V
6 R_C=2.5 // kilo ohm
7
8 // for faithful amplification V_CE should not be
   less than V_CC for Si transistor so
9 V_max=V_CC-1
10 I_max=V_max/R_C
11
12 // As negative and positive half cycles of input are
   equal, change in collector current will be equal
   and opposite so
13 I_min=I_max/2
14
15 printf("Maximum allowable collector current = %.3f
          mA \n", I_max)
16 printf("Minimum zero signal collector current = %.3f
          mA \n", I_min)
```

```

17
18 // the circuit diagram is constructed on xcos and
   its screenshot has been taken.
19 // the waveform given can not be obtained in xcos
   unless we assume necessary values as data is
   insufficient for plotting graph in scilab .
20 // so waveform is constructed as below
21
22 clf()
23 x=linspace(1,5*pi,100)
24 [t]=sin(x)+1
25 plot(x,[t])
26 xtitle("max and min allowable collector currents","t"
         ,"i_c (mA)")

```

Scilab code Exa 12.2 maximum input signal voltage

```

1 //chapter12
2 //example12.2
3 //page236
4
5 Vcc=13 // V
6 V_knee=1 // V
7 Rc=4 // kilo ohm
8 gain_beta=100
9
10 V_Rc=Vcc-V_knee
11 Ic=V_Rc/Rc
12 Ib=Ic/gain_beta
13 Vs=Ic/5 // since Ic/Vs = 5 mA/V given
14
15 printf("maximum input signal voltage = %.3f V or %.3
         f mV \n",Vs,Vs*1000)

```

Scilab code Exa 12.3 Example 3

```
1 //chapter12
2 //example12.3
3 //page240
4
5 Vbb=2 // V
6 Vcc=9 // V
7 Rc=2 // kilo ohm
8 Rb=100 // kilo ohm
9 gain_beta=50
10
11 // by Kirchoff voltage law on base side , we get Ib*
Rb+Vbe=Vbb so
12 Ib=Vbb/Rb // Vbe is negligible
13 Ic=gain_beta*Ib
14
15 // by Kirchoff voltage law on collector side , we get
Ic*Rc+Vce=Vcc so
16 Vce=Vcc-Ic*Rc
17
18 // now for Rb=50 kilo ohm
19 Rb2=50 // kilo ohm
20
21 // since Rb is halved , Ib is doubled so
22 Ib2=2*Ib
23 Ic2=Ib2*gain_beta
24 Vce2=Vcc-Ic2*Rc
25
26 printf("for Rb = 100 kilo ohm, collector current = %f mA \nand collector emitter voltage = %f V \n",Ic,Vce)
27 printf("for Rb = 50 kilo ohm, collector current = %f mA \nand collector emitter voltage = %f V \n",Ic2,Vce2)
```

n" , Ic2 , Vce2)

Scilab code Exa 12.4 Example 4

```
1 //chapter12
2 //example12.4
3 //page241
4
5 Vcc=6 // V
6 Rb=530 // kilo ohm
7 Rc=2 // kilo ohm
8 gain_beta=100
9 Vbe=0.7 // V
10
11 // when Ic=0, Vce=Vcc i.e. Vce=6 and when Vce=0, Ic=
12 // Vcc/Rc i.e. Ic=6/2
13 // so equation of load line becomes Ic=-0.5*Vce+3
14
15 x=linspace(0,6,5)
16 y=-0.5*x+3
17 plot2d(x,y,style=3,rect=[0,0,7,4])
18 xtitle("dc load line","Vce(volts)","Ic(mA)")
19
20 // since Vcc=Ib*Rb+Vbe we get
21 Ib=(Vcc-Vbe)/Rb
22 Ic=Ib*gain_beta
23 Vce=Vcc-Ic*Rc
24
25 printf("the operating point is %.3f V and %.3f mA \n
26 ",Vce,Ic)
27 stability_factor=gain_beta+1
28 printf("stability factor=% .1f \n",stability_factor)
```

Scilab code Exa 12.5 Example 5

```
1 //chapter12
2 //example12.5
3 //page242
4
5 Vcc=12 // V
6 gain_beta=100
7 Vbe=0.3 // V
8 Ic=1 // mA
9
10 // since gain_beta=Ic/Ib
11 Ib=Ic/gain_beta
12
13 // since Vcc=Ib*Rb+Vbe we get
14 Rb=(Vcc-Vbe)/Ib
15
16 gain_beta2=50
17
18 // since Vcc=Ib*Rb+Vbe we get
19 Ib2=(Vcc-Vbe)/Rb
20 Ic2=Ib2*gain_beta2
21
22 printf("for beta = 100, base resistor = %.3f kilo
          ohm \n",Rb)
23 printf("for beta = 50, zero signal collector current
          for same Rb is = %.3f mA \n",Ic2)
```

Scilab code Exa 12.6 Example 6

```
1 //chapter12
2 //example12.6
```

```

3 // page242
4
5 Vcc=10 // V
6 R_B=1d3 // kilo ohm
7 R_E=1 // kilo ohm
8 Vbe=0 // since it is negligible
9 gain_beta=100
10
11 // by Kirchoff voltage law to base side we get Vcc=
12 // I_B*R_B+Vbe+I_E*R_E
13 // but I_E=I_B+I_C and I_C=gain_beta*I_B
14 // so we get Vcc=I_B*R_B+Vbe+R_E*I_B*(1+gain_beta)
15 // making I_B as subject we get
16 I_B=(Vcc-Vbe)/(R_B+R_E*(1+gain_beta)) // in ampere
17 I_C=gain_beta*I_B // in ampere
18 I_E=I_C+I_B // in ampere
19
20 printf("base current = %.4f mA \n", I_B)
21 printf("collector current = %.4f mA \n", I_C)
22 printf("emitter current = %.4f mA \n", I_E)

```

Scilab code Exa 12.7 Example 7

```

1 //chapter12
2 //example12.7
3 //page243
4
5 V_CC=15 // V
6 gain_beta=100
7 V_BE=0.6 // V
8 V_CE=8 // V
9 I_C=2 // mA
10
11 // here V_CC=V_CE+I_C*R_C so we get

```

```

12 R_C=(V_CC-V_CE)/I_C
13
14 I_B=I_C/gain_beta
15
16 // also V_CC=I_B*R_B+V_BE so we get
17 R_B=(V_CC-V_BE)/I_B
18
19 printf("collector resistance = %.3f kilo ohm \n",R_C
      )
20 printf("base resistance = %.3f kilo ohm \n",R_B)

```

Scilab code Exa 12.8 Example 8

```

1 //chapter12
2 //example12.8
3 //page245
4
5 V_CC=20 // V
6 R_B=100 // kilo ohm
7 R_C=1 // kilo ohm
8 V_BE=0.7 // V
9 gain_beta=100
10
11 // we know that R_B=(V_CC-V_BE-gain_beta*R_C*I_B) /
    I_B so we get
12 I_B=(V_CC-V_BE)/(R_B+gain_beta*R_C)
13
14 I_C=gain_beta*I_B
15
16 V_CE=V_CC-I_C*R_C
17
18 printf("operating point is %.3f V, %.3f mA \n",V_CE,
      I_C)
19
20 // the accurate answer is 10.35V,9.65mA but in book

```

it is given as 10.4V, 9.6mA

Scilab code Exa 12.9 Example 9

```
1 //chapter12
2 //example12.9
3 //page245
4
5 V_CC=12 // V
6 gain_beta1=100
7 gain_beta2=50
8 V_BE=0.3 // V
9 V_CE=8 // V
10 I_C=1 // mA
11
12 // here V_CC=V_CE+I_C*R_C so we get
13 R_C=(V_CC-V_CE)/I_C
14
15 I_B=I_C/gain_beta1
16
17 // we know that R_B=(V_CC-V_BE-gain_beta1*R_C*I_B)/
18 I_B so
18 R_B=(V_CC-V_BE-gain_beta1*R_C*I_B)/I_B
19
20
21 // for gain_beta=50 i.e. gain_beta2
22
23 // we know that R_B=(V_CC-V_BE-gain_beta2*R_C*I_B)/
24 I_B so we get
24 I_B2=(V_CC-V_BE)/(R_B+gain_beta2*R_C)
25
26 I_C2=gain_beta2*I_B2
27
28 V_CE2=V_CC-I_C2*R_C
29
```

```
30 printf("for beta=100, required base resistance = %.3f  
kilo ohm \n",R_B)  
31 printf("for beta=50,new operating point is %.3f V, %  
.3 f mA \n",V_CE2,I_C2)
```

Scilab code Exa 12.10 base resistance

```
1 //chapter12  
2 //example12.10  
3 //page246  
4  
5 V_BE=0.7 // V  
6 gain_beta=100  
7 I_C=1 // mA  
8 V_CE=2 // V  
9  
10 I_B=I_C/gain_beta  
11  
12 // since V_CE=V_BE+V_CB we get  
13 V_CB=V_CE-V_BE  
14  
15 R_B=V_CB/I_B  
16  
17 printf("base resistance=%f kilo ohm \n",R_B)
```

Scilab code Exa 12.11 voltage across

```
1 //chapter12  
2 //example12.11  
3 //page248  
4  
5 Vcc=15 // V  
6 Re=2 // kilo ohm
```

```

7  Rc=1 // kilo ohm
8  gain_beta=100
9  Vbe=0.7 // V
10 R1=10 // kilo ohm
11 R2=5 // kilo ohm
12
13 // when Ic=0, Vce=Vcc i.e. Vce=6 and when Vce=0, Ic=
   Vcc/(Rc+Re) i.e. Ic=15/(1+2)
14 // so equation of load line becomes Ic=-(1/3)*Vce+5
15
16 clf()
17 x=linspace(0,15,5)
18 y=-(1/3)*x+5
19 plot2d(x,y,style=3,rect=[0,0,16,6])
20 xtitle("dc load line","Vce(volts)","Ic(mA)")
21
22 V2=Vcc*R2/(R1+R2) // voltage across R2 i.e. 5 kilo
   ohm
23 Ie=(V2-Vbe)/Re
24 Ic=Ie
25 Vce=Vcc-Ic*(Rc+Re)
26
27 printf("the operating point is %.3f V and %.3f mA \n
   ",Vce,Ic)

```

Scilab code Exa 12.12 thevenin

```

1 //chapter12
2 //example12.12
3 //page249
4
5 Vcc=15 // V
6 Re=2 // kilo ohm
7 Rc=1 // kilo ohm
8 gain_beta=100

```

```

9 Vbe=0.7 // V
10 R1=10 // kilo ohm
11 R2=5 // kilo ohm
12
13 Eo=Vcc*R2/(R1+R2)
14 Ro=R1*R2/(R1+R2)
15
16 printf("thevenin voltage = %.3f V \n",Eo)
17 printf("thevenin resistance = %.3f kilo ohm \n",Ro)
18
19 // here Eo=Ib*Ro+Vbe+Ie*Re
20 // now considering Ie=gain_beta*Ib , and making Ib as
   subject we get
21 // Ib=(Eo-Vbe)/(Ro+gain_beta*Re)
22 // Ic=gain_beta*Ib=gain_beta*(Eo-Vbe)/(Ro+gain_beta*
   Re)
23 // dividing numerator and denominator by gain_beta
   we get
24 // Ic=(Eo-Vbe)/(Re+Ro/gain_beta)
25 // Ro/gain_beta is negligible compared to Re so
26 Ic=(Eo-Vbe)/Re
27 Vce=Vcc-Ic*(Rc+Re)
28
29 printf("the operating point is %.3f V and %.3f mA \n
   ",Vce,Ic)

```

Scilab code Exa 19.12 Example 12

```

1 //chapter19
2 //example19.12
3 //page424
4
5 It=8.93 // A
6 Ic=8 // A
7

```

```

8 // we know that  $(I_t/I_c)^2 = 1 + m^2/2$  so making m as
  subject we get
9 m=(2*((It/Ic)^2-1))^0.5
10
11 printf(" modulation factor = %.3f or %.3f percent \n"
      ,m,m*100)

```

Scilab code Exa 12.13 collector current

```

1 //chapter12
2 //example12.13
3 //page250
4
5 R1=50 // kilo ohm
6 R2=10 // kilo ohm
7 Re=1 // kilo ohm
8 Vcc=12 // V
9 Vbe1=0.1 // V
10 Vbe2=0.3 // V
11
12 V2=Vcc*R2/(R1+R2) // voltage across R2
13
14 // for Vbe=0.1 V
15 Ic1=(V2-Vbe1)/Re
16
17 // for Vbe=0.3 V
18 Ic2=(V2-Vbe2)/Re
19
20 printf("for V_BE=0.1 V, collector current = %.3f mA
      \n",Ic1)
21 printf("for V_BE=0.3 V, collector current = %.3f mA
      \n \n",Ic2)
22
23 Vbe_change=100*(Vbe2-Vbe1)/Vbe1
24 Ic_change=-100*(Ic2-Ic1) // negative sign since

```

```

Ic decreases
25 printf("comment : if V_BE changes by %.5f percent , \
    collector current changes by %.3f percent \n",
    Vbe_change,Ic_change)
26 printf("so collector current is independent of
    transistor parameter variations \n")
27
28 // the change in V_BE is 200 percent not 300 percent
    .It is mistake in textbook

```

Scilab code Exa 12.14 collector emitter

```

1 //chapter12
2 //example12.14
3 //page251
4
5 Vcc=20 // V
6 Re=5 // kilo ohm
7 Rc=1 // kilo ohm
8 Vbe=0 // considering it as negligible
9 R1=10 // kilo ohm
10 R2=10 // kilo ohm
11
12 V2=Vcc*R2/(R1+R2)
13
14 // since V2=Vbe+Ie*Re so
15 Ie=(V2-Vbe)/Re
16 Ic=Ie
17
18 Vce=Vcc-Ic*(Rc+Re)
19 Vc=Vcc-Ic*Rc
20
21 printf("emitter current = %.3f mA \n",Ie)
22 printf("collector emitter voltage = %.3f V \n",Vce)
23 printf("collector potential = %.3f V \n",Vc)

```

Scilab code Exa 12.15 Kirchoff voltage law

```
1 //chapter12
2 //example12.15
3 //page252
4
5 R_C=2.2 // kilo ohm
6 V_CC=9 // V
7 gain_beta=50
8 V_BE=0.3 // V
9 I_C=2 // mA
10 V_CE=3 // V
11
12 I_B=I_C/gain_beta
13 I1=10*I_B
14
15 // I1=V_CC/(R1+R2) so let Rt=R1+R2 thus we get
16 Rt=V_CC/I1
17
18 // by Kirchoff voltage law to collector side we get
19 // V_CC=I_C*R_C+V_CE+I_E*R_E and also we have I_C=
    I_E so
20 // V_CC=I_C*R_C+V_CE+I_C*R_E so making R_E as
    subject we get
21 R_E=((V_CC-V_CE)/I_C)-R_C // in kilo ohm
22
23 V2=V_BE+I_C*R_E // since V_E=I_C*R_E
24 R2=V2/I1
25 R1=Rt-R2
26
27 printf("emitter resistance = %.3f ohm \n",R_E*1000)
28 printf("R1 = %3f kilo ohm \n",R1)
29 printf("R2 = %3f kilo ohm \n",R2)
```

Scilab code Exa 12.16 collector resistance

```
1 //chapter12
2 //example12.16
3 //page252
4
5 alpha=0.985
6 V_BE=0.3 // V
7 V_CC=16 // V
8 V_CE=6 // V
9 I_C=2 // mA
10 R_E=2 // kilo ohm
11 R2=20 // kilo ohm
12
13 gain_beta=alpha/(1-alpha)
14 I_B=I_C/gain_beta
15
16 V_E=I_C*R_E
17 V2=V_BE+V_E
18 V1=V_CC-V2
19
20 I1=V2/R2
21 R1=V1/I1
22
23 V_RC=V_CC-V_CE-V_E
24 R_C=V_RC/I_C
25
26 printf("R1 = %.3f kilo ohm \n",R1)
27 printf("collector resistance = %.3f kilo ohm \n",R_C
)
```

Scilab code Exa 12.17 thevenin

```

1 //chapter12
2 //example12.17
3 //page253
4
5 Vcc=15 // V
6 Re=2 // kilo ohm
7 Rc=1 // kilo ohm
8 gain_beta=100
9 Vbe=0.7 // V
10 R1=10 // kilo ohm
11 R2=5 // kilo ohm
12
13 Eo=Vcc*R2/(R1+R2)
14 Ro=R1*R2/(R1+R2)
15
16 printf("thevenin voltage = %.3f V \n",Eo)
17 printf("thevenin resistance = %.3f kilo ohm \n",Ro)
18
19 // here Eo=Ib*Ro+Vbe+Ie*Re
20 // now considering Ie=gain_beta*Ib , we can replace
21 // Ib=Ie/gain_beta
22 // making Ie as subject we get
23 Ie=(Eo-Vbe)/(Re+Ro/gain_beta)
24
25 printf("emitter current = %.3f mA \n",Ie)

```

Scilab code Exa 12.18 kilo ohm

```

1 //chapter12
2 //example12.18
3 //page254
4
5 V_CC=10 // V
6 V_BE=0.2 // V

```

```

7 I_E=2 // mA
8 I_B=50d-3 // mA
9 R_E=1 // kilo ohm
10 R2=10 // kilo ohm
11
12 V2=V_BE+I_E*R_E
13 I2=V2/R2
14
15 I1=I2+I_B
16 V1=V_CC-V2
17 R1=V1/I1
18
19 printf("R1 = %.3f kilo ohm \n",R1)

```

Scilab code Exa 12.19 transistor

```

1 //chapter12
2 //example12.19
3 //page255
4
5 printf(" i) if R2 is shorted , base will be grounded .
        It will be \n      left without forward bias and
        transistor \n      will be cutoff so output is zero
        .\n \n")
6 printf(" ii) if R2 is open , forward bias will be very
        high. The \n      collector current will be very
        high and collector \n      emitter voltage will be
        very low. \n \n")
7 printf(" iii) if R1 is shorted , transistor will be
        in saturation \n      due to excessive forward bias
        . The base will be at \n      Vcc and emitter will
        be slightly below Vcc.\n \n")
8 printf(" iv) if R1 is open , transistor will be
        without forward bias.\n      Hence transistor will
        be cutoff i.e. output will be zero. \n")

```

Scilab code Exa 12.20 circuit is not mid-point biased

```
1 //chapter12
2 //example12.20
3 //page256
4
5 Vcc=8 // V
6 Rb=360 // kilo ohm
7 Rc=2 // kilo ohm
8 gain_beta=100
9 Vbe=0.7 // V
10
11 // when Ic=0, Vce=Vcc i.e. Vce=8 and when Vce=0, Ic=
12 // Vcc/Rc i.e. Ic=8/2
13 // so equation of load line becomes Ic=-0.5*Vce+4
14 clf()
15 x=linspace(0,8,5)
16 y=-0.5*x+4
17 plot2d(x,y,style=3,rect=[0,0,9,5])
18 xtitle("dc load line","Vce(volts)","Ic(mA)")
19
20 // since Vcc=Ib*Rb+Vbe we get
21 Ib=(Vcc-Vbe)/Rb
22 Ic=Ib*gain_beta
23 Vce=Vcc-Ic*Rc
24
25 printf("the operating point is %.3f V and %.3f mA \n
26 " ,Vce,Ic)
27 if Vce<Vcc/2+0.1 | Vce>Vcc/2-0.1 // check if V_CE is
28 // nearly half of V_CC
29     printf("circuit is mid-point biased \n")
30 else
31     printf("circuit is not mid-point biased. \n")
```

30 **end**

Scilab code Exa 12.21 circuit is not mid-point biased

```
1 //chapter12
2 //example12.21
3 //page257
4
5 V_CC=10 // V
6 R1=12 // kilo ohm
7 R2=2.7 // kilo ohm
8 V_BE=0.7 // V
9 R_E=180d-3 // kilo ohm
10 R_C=620d-3 // kilo ohm
11
12 V2=V_CC*R2/(R1+R2)
13 I_E=(V2-V_BE)/R_E
14 I_C=I_E
15 V_CE=V_CC-I_C*(R_C+R_E)
16
17 printf("the operating point is %.3f V and %.3f mA \n
      ",V_CE,I_C)
18 if V_CE<V_CC/2+0.1 | V_CE>V_CC/2-0.1 // check if
      V_CE is nearly half of V_CC
19     printf("circuit is mid-point biased \n")
20 else
21     printf("circuit is not mid-point biased. \n")
22 end
23
24 // the accurate answer for collector current is
      6.315 mA but in book it is given as 6.33 mA
```

Scilab code Exa 12.22 base current

```

1 //chapter12
2 //example12.22
3 //page257
4
5 V_CC=10 // V
6 R1=1.5 // kilo ohm
7 R2=0.68 // kilo ohm
8 R_E=0.24 // kilo ohm
9 V_BE=0.7 // V
10 beta_min=100
11 beta_max=400
12
13 V2=V_CC*R2/(R1+R2)
14 I_E=(V2-V_BE)/R_E
15 I_C=I_E
16
17 beta_avg=(beta_min*beta_max)^0.5
18 I_B=I_E/(beta_avg+1)
19
20 printf("base current = %f micro ampere \n", I_B*1000)
21
22 // the accurate answer for base current is 50.151
    micro ampere but in book it is given as 49.75
    micro ampere

```

Scilab code Exa 12.23 collector cutoff current

```

1 //chapter12
2 //example12.23
3 //page258
4
5 gain_beta=40
6 I_C1=2 // mA
7 t1=25 // degrees
8 t2=55 // degrees

```

```

9 I_CB01=5d-3 // mA
10
11 // for I_CBO=5 micro ampere at 25 degrees
12 I_CE01=(1+gain_beta)*I_CB01
13
14 I_CB02=I_CB01*2^((t2-t1)/10) // since it doubles
   every 10 degrees. So for t2-t1, it becomes 2^((t2
   -t1)/10) times.
15 I_CE02=(1+gain_beta)*I_CB02
16 I_C2=I_CE02+I_C1
17 I_C_change=100*(I_C2-I_C1)/I_C1
18
19 // for I_CBO=0.1 micro ampere at 25 degrees
20 t1_dash=25 // degrees
21 t2_dash=55 // degrees
22 I_CB01_dash=0.1d-3 // mA
23 I_C1_dash=2 // mA
24
25 I_CB02_dash=I_CB01_dash*2^((t2-t1)/10) // since it
   doubles every 10 degrees. So for t2-t1, it
   becomes 2^((t2-t1)/10) times.
26 I_CE02_dash=(1+gain_beta)*I_CB02_dash
27 I_C2_dash=I_CE02_dash+I_C1_dash
28 I_C_change_dash=100*(I_C2_dash-I_C1_dash)/I_C1_dash
29
30 printf("collector cutoff current = %.3f mA \n \n",
         I_CE01)
31 printf("percent change in zero signal current given
         that \nI_CBO=5 micro ampere at 25 degree is = %.3
         f percent \n \n", I_C_change)
32 printf("percent change in zero signal current given
         that \nI_CBO=0.01 micro ampere at 25 degree is =
         %.3f percent \n", I_C_change_dash)

```

Scilab code Exa 12.24 base current

```

1 //chapter12
2 //example12.24
3 //page259
4
5 alpha=0.99
6 I_E=1 // mA
7 t1=27 // degrees
8 t2=57 // degrees
9 I_CB01=0.02d-3 // mA
10
11 I_CB02=I_CB01*2^((t2-t1)/6) // since it doubles
   every 6 degrees. So for t2-t1, it becomes 2^((t2-
   t1)/6) times.
12
13 I_C=alpha*I_E+I_CB02
14 I_B=I_E-I_C
15
16 printf("base current = %.1f micro ampere",I_B*1000)

```

Scilab code Exa 12.25 since base voltage is zero

```

1 //chapter12
2 //example12.25
3 //page261
4
5 printf("since base voltage is zero, it means that
   there is no path \nfor current in the base
   circuit. So the transistor will be off i.e. I_C
   =0,I_E=0. \nSo V_C=10V and V_E=0.\nSo obvious
   fault is R1 is open.\n")

```

Scilab code Exa 12.26 voltage at base

```
1 //chapter12
2 //example12.26
3 //page261
4
5 R1=18 // kilo ohm
6 R2=4.7 // kilo ohm
7 Re=1 // kilo ohm
8 Vcc=10 // V
9
10 V_B=Vcc*R2/(R1+R2)
11
12 printf(" voltage at base = %.3f V \n",V_B)
13 printf("The fact that V_C=10V and V_E is nearly
equal to V_B reveals \nthat I_C=0 and I_E=0. So
I_B drops to zero .So obvious fault is R_E is open
. \n")
```

Chapter 13

Single stage transistor amplifiers

Scilab code Exa 1.1 collector current

```
1 // chapter 13
2 // example 13.1
3 // page 272
4
5 Rc=4 // kilo ohm
6 Vcc=10 // V
7 Ib_zero=10d-3 // mA
8 Ib_max=15d-3 // mA
9 Ib_min=5d-3 // mA
10 gain_beta=100
11
12 Ic_zero=Ib_zero*gain_beta
13 Ic_max=Ib_max*gain_beta
14 Ic_min=Ib_min*gain_beta
15
16 Vc_zero=Vcc-Ic_zero*Rc
17 Vc_max=Vcc-Ic_max*Rc
18 Vc_min=Vcc-Ic_min*Rc
19
```

```

20 printf("As collector current increases from %.3f mA
          to %.3f mA \noutput voltage decreases from %.3f V
          to %.3f V \n",Ic_zero,Ic_max,Vc_zero,Vc_max)
21 printf("As collector current decreases from %.3f mA
          to %.3f mA \noutput voltage increases from %.3f V
          to %.3f V \n",Ic_max,Ic_min,Vc_max,Vc_min)
22 printf("Thus output voltage is 180 degrees out of
          phase from input voltage \n")
23
24 printf("Note : \ni) input voltage and input current
          are in phase \nii) input voltage and output
          current are in phase \nniii) output voltage is 180
          degrees out of phase with input voltage\n")
25
26
27 // plotting base current and collector current and
   output voltage in same graph using following code
   instead of xcos
28 clf()
29 x=linspace(0,2*pi,100)
30 ib=5*sin(x)+10
31 ic=0.5*sin(x)+1
32 vc=-4*sin(x)+6
33 plot2d(x,ib,style=1,rect=[0,0,20,20])
34 xtitle("base current (micro ampere) - Black
          collector current (mA) -
          Blue           output voltage (V) - Green
          " , "t" )
35 plot2d(x,ic,style=2,rect=[0,0,20,20])
36 plot2d(x,vc,style=3,rect=[0,0,20,20])

```

Scilab code Exa 1.2 Thevenin circuit

```

1 // chapter 13
2 // example 13.2

```

```

3 // page 274
4
5 printf("i) Referring to the Thevenin circuit , we see
       that voltage source \nis short and resistances
       except  $R_c$  and  $R_e$  are bypassed.\nThus dc load =  $R_c$ 
       +  $R_e$ \n")
6 printf(" ii) Referring to ac equivalent circuit ,  $R_c$  is
       parallel with  $R_l$ .\\nThus ac load =  $R_c * R_l / (R_c + R_l)$  \
       n \n \n")
7 printf(" iii) Since  $V_{cc} = V_{ce} + I_c * (R_c + R_e)$  we get \n max
        $V_{ce} = V_{cc}$  and max  $I_c = V_{cc} / (R_c + R_e)$  \n \n \n")
8 printf(" iii) On applying ac signal , collector current
       and collector emitter \nvoltage change about Q
       point.\nMaximum collector current =  $I_c$ .\nMaximum
       positive swing of ac collector emitter voltage =
        $I_c * R_{AC}$  \n So total maximum collector emitter
       voltage =  $V_{ce} + I_c * R_{AC}$  \n\nMaximum positive swing
       of ac collector current =  $V_{ce} / R_{AC}$  so \nTotal
       maximum collector current =  $I_c + V_{ce} / R_{AC}$  \n")

```

Scilab code Exa 13.3 the operating point

```

1 // chapter 13
2 // example 13.3
3 // page 278
4
5 Vcc=15 // V
6 Re=2 // kilo ohm
7 Rc=1 // kilo ohm
8 Rl=1 // kilo ohm
9 Vbe=0.7 // V
10
11 // dc load line
12
13 // when  $I_c = 0$ ,  $V_{ce} = V_{cc}$  i.e.  $V_{ce} = 15$  and when  $V_{ce}$ 

```

```

14      =0, Ic=Vcc/(Rc+Re) i.e. Ic=15/3
14      // so equation of load line becomes Ic=-(1/3)*
14      Vce+15
15
16      clf()
17      x=linspace(0,15,5)
18      y=-(1/3)*x+5
19      plot2d(x,y,style=3,rect=[0,0,16,6])
20      xtitle("dc load line-green ac load line-
20      blue","collector emitter voltage(volts)",""
20      collector current(mA)")
21
22      V2=5 // V
23      // since voltage across R2 is V2=5 V and V2=Vbe+
23      Ie*Re we get
24      Ie=(V2-Vbe)/Re
25      Ic=Ie
26      Vce=Vcc-Ic*(Rc+Re)
27
28      printf("the operating point is %.3f V and %.3f
28      mA \n",Vce,Ic)
29
30
31 // ac load line
32
33      R_AC=Rc*Rl/(Rc+Rl) // ac load
34      V_ce=Vce+Ic*R_AC // maximum collector emitter
34      voltage
35      I_c=Ic+Vce/R_AC // maximum collector current
36      // the equation of ac load line in terms of V_ce
36      and I_c becomes
37      y=-(I_c/V_ce)*x+I_c
38      plot2d(x,y,style=2,rect=[0,0,10,20])

```

Scilab code Exa 13.4 maximum collector

```

1 // chapter 13
2 // example 13.4
3 // page 279
4
5 Vcc=20 // V
6 Re=0 // kilo ohm, since given as negligible
7 Rc=10 // kilo ohm
8 Rl=30 // kilo ohm
9 Vbe=0.7 // V
10
11 Vce=10 // mV
12 Ic=1 // mA
13
14 // dc load line
15
16 // when Ic=0, Vce=Vcc i.e. Vce=15 and when Vce
   =0, Ic=Vcc/(Rc+Re) i.e. Ic=20/10 mA
17 // so equation of load line becomes Ic=-(1/10)*
   Vce+2
18
19 clf()
20 x=linspace(0,20,5)
21 y=-(1/10)*x+2
22 plot2d(x,y,style=3,rect=[0,0,21,6])
23 xtitle("dc load line-green ac load line-
   blue","collector emitter voltage(volts)",""
   collector current(mA)")
24
25 // ac load line
26
27 R_AC=Rc*Rl/(Rc+Rl) // ac load
28 V_ce=Vce+Ic*R_AC // maximum collector emitter
   voltage
29 I_c=Ic+Vce/R_AC // maximum collector current
30 // the equation of ac load line in terms of V_ce
   and I_c becomes
31 x=linspace(0,V_ce,10)
32 y=-(I_c/V_ce)*x+I_c

```

```
33      plot2d(x,y,style=2,rect=[0,0,21,6])
```

Scilab code Exa 13.5 plot

```
1 // chapter 13
2 // example 13.5
3 // page 280
4
5 printf("operating point is (8V,1mA). During positive
       half cycle of \nac signal collector current
       swings from 1 mA to 1.5 mA \nand collector
       emitter voltage swings from 8 V to 7 V.\nThis is
       at A. During negative half cycle of \nac signal
       collector current swings from 1 mA to 0.5 mA \
       nand collector emitter voltage swings from 8 V to
       9 V.\nThis is at B. \n \n")
6
7 printf("Note : When ac signal is applied , ac signal
       collector current and \ncollector emitter voltage
       variations take place about Q point. \nAlso ,
       operating point moves along load line.\n")
8
9 clf()
10 x=linspace(-3*pi,-pi,10)
11 plot(x,-0.5*sin(x)+1)
12
13 x=linspace(7,9,10)
14 plot(x,5-0.5*x)
15
16 x=linspace(-3*pi,-pi,10)
17 plot(-sin(x)+8,x)
18 plot(x,xgrid())
19 xtitle("collector current and collector emitter
       voltage swings","collector emitter voltage (volts
       )","collector current (mA)")
```

```

20 a=gca(); // Handle on axes entity
21 a.x_location = "origin";
22 a.y_location = "origin";
23
24 // Some operations on entities created by plot ...
25 a=gca();
26 a.isoview='on';
27 a.children // list the children of the axes : here
    it is an Compound child composed of 2 entities
28 poly1= a.children.children(2); //store polyline
    handle into poly1
29 poly1.foreground = 4; // another way to change the
    style...
30 poly1.thickness = 3; // ...and the tickness of a
    curve.
31 poly1.clip_state='off' // clipping control
32 a.isoview='off';

```

Scilab code Exa 13.6 voltage gain

```

1 //chapter13
2 //example13.6
3 //page282
4
5 Rc=2 // kilo ohm
6 Rl=0.5 // kilo ohm
7 Rin=1 // kilo ohm
8 gain_beta=60
9
10 R_AC=Rc*Rl/(Rc+Rl)
11 Av=gain_beta*R_AC/Rin
12
13 printf("voltage gain = %.3f \n",Av)

```

Scilab code Exa 13.7 output voltage

```
1 //chapter13
2 //example13.7
3 //page282
4
5 Rc=10 // kilo ohm
6 Rl=10 // kilo ohm
7 Rin=2.5 // kilo ohm
8 gain_beta=100
9 Vin=1 // mV
10
11 R_AC=Rc*Rl/(Rc+Rl)
12 Av=gain_beta*R_AC/Rin
13
14 // since Av=Vout/Vin we get
15 Vout=Av*Vin
16
17 printf("output voltage = %.3f mV \n",Vout)
```

Scilab code Exa 13.8 input impedance

```
1 //chapter13
2 //example13.8
3 //page282
4
5 del_Ib=10d-3 // mA
6 del_Ic=1 // mA
7 del_Vbe=0.02 // V
8 Rc=5 // kilo ohm
9 Rl=10 // kilo ohm
10 gain_beta=60.0;
```

```

11
12 Ai=del_Ic/del_Ib
13 Rin=del_Vbe/del_Ib
14 R_AC=Rc*Rl/(Rc+Rl)
15 Av=gain_beta*R_AC/Rin
16 Ap=Av*Ai
17
18 printf(" current gain = %.3f \n",Ai)
19 printf(" input impedance = %.3f kilo ohm \n",Rin)
20 printf(" ac load = %.3f kilo ohm \n",R_AC)
21 printf(" voltage gain = %.3f \n",Av)
22 printf(" power gain = %.3f \n",Ap)
23
24 // the accurate answer for voltage gain = 166.667
   and for power gain = 16666.667 but in book they
   are given as 165 and 16500 respectively.

```

Scilab code Exa 13.9 output voltage

```

1 //chapter13
2 //example13.9
3 //page283
4
5 Rc=3 // kilo ohm
6 Rl=6 // kilo ohm
7 Rin=0.5 // kilo ohm
8 Vin=1 // mV
9 gain_beta=50
10
11 R_AC=Rc*Rl/(Rc+Rl)
12 Av=gain_beta*R_AC/Rin
13
14 // since Av=Vout/Vin we get
15 Vout=Av*Vin
16

```

```
17 printf("output voltage = %.3f mV \n", Vout)
```

Scilab code Exa 13.10 circuit

```
1 //chapter13
2 //example13.10
3 //page283
4
5 R1=1 // kilo ohm
6 R2=2 // kilo ohm
7 Vt=6 // V
8
9 Vb=Vt*R1/(R1+R2)
10
11 if Vb==4
12     printf("circuit is operating properly \n")
13 else
14     printf("circuit is not operating properly
           because voltage at B should be %.1f V instead
           of 4 V \n", Vb)
15 end
```

Scilab code Exa 13.11 ac emitter resistance

```
1 //chapter13
2 //example13.11
3 //page284
4
5 R1=40 // kilo ohm
6 R2=10 // kilo ohm
7 Re=2 // kilo ohm
8 Vcc=10 // V
9 Vbe=0.7 // V
```

```
10
11 V2=Vcc*R2/(R1+R2) // voltage across R2
12 Ve=V2-Vbe // voltage across Re
13 Ie=Ve/Re
14 re_dash=25/Ie
15
16 printf("ac emitter resistance = %.3f ohm \n",re_dash
    )
```

Scilab code Exa 13.12 voltage gain

```
1 //chapter13
2 //example13.12
3 //page286
4
5 R1=150 // kilo ohm
6 R2=20 // kilo ohm
7 Re=2.2 // kilo ohm
8 Rc=12 // kilo ohm
9 Vcc=20 // V
10 Vbe=0.7 // V
11
12 V2=Vcc*R2/(R1+R2) // voltage across R2
13 Ve=V2-Vbe // voltage across Re
14 Ie=Ve/Re
15 re_dash=1d-3*25/Ie // in kilo ohm
16 Av=Rc/re_dash
17
18 printf("voltage gain = %.3f \n",Av)
19
20 // the accurate answer is 360.642
```

Scilab code Exa 13.13 voltage gain

```

1 //chapter13
2 //example13.13
3 //page287
4
5 Rc=12 // kilo ohm
6 Rl=6 // kilo ohm
7 re_dash=33.3d-3 // kilo ohm
8
9 RAC=Rc*Rl/(Rc+Rl)
10 Av=RAC/re_dash
11
12 printf(" voltage gain = %.3f \n",Av)
13
14 // the accurate answer is 120.120

```

Scilab code Exa 13.14 input impedance of amplifier circuit

```

1 //chapter13
2 //example13.14
3 //page288
4
5 R1=45 // kilo ohm
6 R2=15 // kilo ohm
7 Re=7.5 // kilo ohm
8 Vcc=30 // V
9 Vbe=0.7 // V
10 gain_beta=200
11
12 V2=Vcc*R2/(R1+R2) // voltage across R2
13 Ve=V2-Vbe // voltage across Re
14 Ie=Ve/Re
15 re_dash=1d-3*25/Ie // in kilo ohm
16 Zin_base=gain_beta*re_dash
17 Zin=Zin_base*(R1*R2/(R1+R2))/(Zin_base+R1*R2/(R1+R2)
)
```

```
18
19 printf("input impedance of amplifier circuit = %.3f
      kilo ohm \n",Zin)
20
21 // the accurate answer for input impedance is 3.701
      kilo ohm but in book it is given as 3.45 kilo ohm
```

Scilab code Exa 13.15 Class A

```
1 //chapter13
2 //example13.15
3 //page289
4
5 printf("i) Class A amplifier means that it raises
      voltage level of signal and its \nmode of
      operation is such that collector current flows
      for whole input signal. \n \n")
6 printf("ii) Audio voltage amplifier means it raises
      voltage level of audio signal \nand its mode of
      operation is class A. \n \n")
7 printf("iii) Class B power amplifier means that it
      raises power level of signal and its \nmode of
      operation is such that collector current flows
      for half cycle of input signal only. \n \n")
8 printf("iv) Class A transformer coupled power
      amplifier means that power amplification \nis
      being done , coupling is by tranformer and mode of
      operation is class A. \n")
```

Scilab code Exa 13.16 required input signal voltag

```
1 //chapter13
2 //example13.16
```

```

3 // page290
4
5 Ao=1000
6 Rout=1 // ohm
7 Rl=4 // ohm
8 Rin=2d3 // ohm
9 I2=0.5 // A
10
11 // here I2/I1=Ao*Rin/(Rout+Rl) so
12 I1=I2*(Rout+Rl)/(Ao*Rin)
13 V1=I1*Rin // in V
14
15 printf(" required input signal voltage = %.3f mV \n" ,
V1*1d3)

```

Scilab code Exa 13.17 magnitude of output voltage

```

1 //chapter13
2 //example13.17
3 //page291
4
5 Ao=1000
6 Es=10d-3 // V
7 Rs=3d3 // ohm
8 Rin=7d3 // ohm
9 Rout=15 // ohm
10 Rl=35 // ohm
11
12 I1=Es/(Rs+Rin)
13 V1=I1*Rin
14 Av=Ao*Rl/(Rout+Rl)
15 // since V2/V1=Av, we get
16 V2=V1*Av
17
18 P2=V2^2/Rl

```

```
19 P1=V1^2/Rin
20 Ap=P2/P1
21
22 printf(" magnitude of output voltage = %.2f V \n",V2)
23 printf(" power gain = %.2f \n",Ap)
```

Scilab code Exa 13.18 required signal voltage

```
1 //chapter13
2 //example13.18
3 //page292
4
5 Av=80
6 Ai=120
7 V2=1 // V
8 Rout=1 // ohm
9 Rl=2 // ohm
10
11 V1=V2/Av // in V
12
13 // Av=Ao*Rl/(Rout+Rl) and Ai=Ao*Rin/(Rout+Rl) so
14 // Av/Ai=Rl/Rin hence
15 Rin=Rl*Ai/Av
16
17 I1=V1/Rin // in mA
18 Ap=Av*Ai
19
20 printf(" required signal voltage = %.2f mV and
           current = %.2f micro ampere \n",V1*1d3,I1*1d3)
21 printf(" power gain = %.3f \n",Ap)
```

Chapter 14

Multistage transistor amplifiers

Scilab code Exa 14.1 gain

```
1 //chapter 14
2 //example 14.1
3 //page 301
4
5 Av=20*log10(30)
6
7 Pv=10*log10(100)
8
9 printf(" voltage gain = %.3f db \n",Av)
10 printf(" power gain = %.3f db \n",Pv)
```

Scilab code Exa 14.2 gain

```
1 //chapter 14
2 //example 14.2
3 //page 301
4
5 Ap1=40 // db
```

```

6 Ap2=43 // db
7
8 // since Ap = 10*log10(power_gain), we get
9 power_gain1=10^(Ap1/10)
10 power_gain2=10^(Ap2/10)
11
12 printf("power gain of 40 db = %.3f \n",power_gain1)
13 printf("power gain of 43 db = %.3f \n",power_gain2)
14
15 // the accurate answer for power gain of 43 db is
    19952 but in book it is given as 20000 db

```

Scilab code Exa 14.3 total voltage gain

```

1 //chapter 14
2 //example 14.3
3 //page 301
4
5 Av1=20*log10(100) // db
6 Av2=20*log10(200) // db
7 Av3=20*log10(400) // db
8
9 Av_total=Av1+Av2+Av3
10
11 printf("total voltage gain = %.3f db \n",Av_total)

```

Scilab code Exa 14.4 Example 4

```

1 //chapter 14
2 //example 14.4
3 //page 302
4
5 gain_abs=30

```

```
6 n=5
7
8 Ap1=10*log10(gain_abs) // db
9 Ap_tot=Ap1*n
10 Ap_f=Ap_tot-10 // db
11
12 printf("total power gain = %.3f db \n",Ap_tot)
13 printf("power gain with negative feedback = %.3f db
\n",Ap_f)
```

Scilab code Exa 14.5 Example 5

```
1 //chapter 14
2 //example 14.5
3 //page 302
4
5 P1=1.5 // W
6 P2=0.3 // W
7 Pi=10d-3 // W
8
9 // power gain at 2 kHz
10 Ap1=10*log10(P1/Pi)
11
12 // power gain at 20 Hz
13 Ap2=10*log10(P2/Pi)
14
15 Ap_diff=Ap1-Ap2
16 printf("fall in gain from 2 kHz to 20 Hz = %.3f db \
n",Ap_diff)
```

Scilab code Exa 14.6 output voltage

```
1 // chapter 14
```

```

2 //example 14.6
3 //page 302
4
5 Av=15 // db
6 V1=0.8 // V
7
8 // since db voltage gain  $Av=20*\log_{10}(V2/V1)$  making
   V2 as subject we get
9
10 V2=V1*10^(Av/20)
11
12 printf("output voltage = %.2f V \n",V2)

```

Scilab code Exa 14.7 minimum value of load resistance

```

1 //chapter 14
2 //example 14.7
3 //page 302
4
5 Ao_db=70 // db
6 Av_db=67 // db
7 Rout=1.5 // kilo ohm
8
9 // since  $20*\log(Ao) - 20*\log(Av) = Ao_db - Av_db$  we get
10 //  $20*\log(Ao/Av) = Ao_db - Av_db$  so
11 //  $Ao/Av = 10^{(Ao_db - Av_db)/20}$ 
12 // and also  $Ao/Av = 1 + Rout/Rl$  since  $Av/Ao = Rl/(Rl + Rout)$ 
13
14 // so making Rl as subject we get
15 Rl=Rout/(10^((Ao_db-Av_db)/20)-1)
16
17 printf("minimum value of load resistance = %.3f kilo
          ohm \n",Rl)
18
19 // the accurate answer is 3.636 kilo ohm

```

Scilab code Exa 14.8 output voltage

```
1 //chapter 14
2 //example 14.8
3 //page 303
4
5 gain_db=40 // db
6 Vin=10d-3 // mV
7 Rl=1 // kilo ohm
8
9 // we know that Vout/Vin=10^(gain_db/20) so making
   Vout as subject we get
10 Vout=Vin*10^(gain_db/20)
11 P_load=Vout^2/Rl
12
13 printf("output voltage = %.3f V \n",Vout)
14 printf("load power = %.3f mW \n",P_load)
```

Scilab code Exa 14.9 frequency

```
1 // chapter14
2 // example14.9
3 // page 303
4
5 // figure given in book is for reference only. It is
   not required to solve the example since the
   required details are very clearly specified in
   the problem statement.
6 // moreover more data is needed to plot the graph
   given in book.
7
```

```

8 Av_max1=2000 // for 2 kHz
9 Av_sqrt_2=1414 // for 10 kHz and 50 Hz
10
11 percent_Av_max1=70.7*Av_max1/100
12 printf("70.7 percent of maximum gain 2000 is =%.3f
13 \n",percent_Av_max1)
14 if Av_sqrt_2==percent_Av_max1
15 printf("we observe that 70.7 percent of max gain
16 2000 is 1414 \n")
17 printf("this gain 1414 is at 50 Hz and 10 kHz \n")
18 printf("so bandwidth = 50 Hz to 10 kHz \n \n")
19 printf("since frequency on lower side at which gain
falls to \n70.7 percent is 50 Hz.So lower cutoff
frequency = 50 Hz \n \n")
20 printf("since frequency on upper side at which gain
falls to \n70.7 percent is 10 kHz.So upper cutoff
frequency = 10 kHz \n \n")
21 else printf("data is insufficient for finding
bandwidth and cutoff frequencies \n")
22 end

```

Scilab code Exa 14.10 gain

```

1 // chapter14
2 // example14.10
3 // page 305
4
5 Rc=500 // ohm
6 Rin=1d3 // ohm
7
8 // gain of second stage is 60 since it has no
loading effect of any stage so
9 Av2=60

```

```

10 load1=Rc*Rin/(Rc+Rin)
11 Av1=Av2*load1/Rc
12 Av=Av1*Av2
13
14 printf(" total gain = %.3f \n",Av)
15 printf("comment : gain of one stage=60.So total gain
           should be 60*60=%d but here it is %.3f.\nThis is
           because of loading effect of input impedance of
           second stage on first stage. \n",60*60,Av)
16 printf("So gain of first stage decreases.\nHowever,
           second stage has no loading effect of any next
           stage.So its gain does not decrease. \n")
17
18 // the accurate answer for total gain is 2400 but in
   book it is given as 2397

```

Scilab code Exa 14.11 gain

```

1 // chapter14
2 // example14.11
3 // page 306
4
5 Rin=1 // kilo ohm
6 Rc= 2 // kilo ohm
7 gain_beta=100
8
9 // since first stage has loading effect of input
   impedance of second stage , we get effective load
   of first stage as
10 R_AC=Rc*Rin/(Rc+Rin)
11 Av1=gain_beta*R_AC/Rin
12
13 // second stage has no loading effect so its gain
14 Av2=gain_beta*Rc/Rin
15 Av=Av1*Av2

```

```
16
17 printf(" voltage gain of first stage = %.3f \n",Av1)
18 printf(" voltage gain of second stage = %.3f \n",Av2)
19 printf(" total voltage gain = %.3f \n",Av)
20
21 // the accurate answer for gain of first stage is
   66.667 and total gain is 13333.33 but in book
   they are given as 66 and 13200 respectively
```

Scilab code Exa 14.12 voltage gain

```
1 // chapter14
2 // example14.12
3 // page 307
4
5 Rin=1d3 // ohm
6 Rc= 10d3 // ohm
7 Rl=100 // ohm
8 gain_beta=100
9
10 // effective collector load is
11 R_AC=Rc*Rl/(Rc+Rl)
12 Av=gain_beta*R_AC/Rin
13
14 printf(" voltage gain = %.3f \n",Av)
15 printf("comment : load is only 100 ohm so efective
   load of amplifier is too much reduced.\nThus
   voltage gain is very small.\n")
16 printf("In such cases we can use a step down
   transformer to serve the purpose. \n")
```

Scilab code Exa 14.13 biasing potential

```

1 // chapter14
2 // example14.13
3 // page 307
4
5 Vcc=20 // V
6 R3=10 // kilo ohm
7 R4=2.2 // kilo ohm
8 Rc=3.6 // kilo ohm
9
10 V_B=Vcc*R4/(R3+R4)
11
12 // replacing Cc by wire
13 Req=R3*Rc/(R3+Rc)
14 V_B2=Vcc*R4/(Req+R4)
15
16 printf("biasing potential before replacing Cc = %.3f
          V \n",V_B)
17 printf("biasing potential after replacing Cc = %.3f
          V \n \n",V_B2)
18 printf("thus biasing potential of second stage
          changes.\nThis could cause the transistor to
          saturate and it would not work as amplifier.\n")
19 printf("Also, we see the use of coupling capacitor
          to maintain \n independent biasing potential for
          each stage.\nThis allows ac output from one stage
          to pass to next stage.\n")

```

Scilab code Exa 14.14 voltage gain

```

1 // chapter14
2 // example14.14
3 // page 308
4
5 Vcc=15 // V
6 R1=22 // kilo ohm

```

```

7 R2=3.3 // kilo ohm
8 R3=5 // kilo ohm
9 R4=1 // kilo ohm
10 R5=15 // kilo ohm
11 R6=2.5 // kilo ohm
12 R8=1 // kilo ohm
13 R3=5 // kilo ohm
14 R7=5 // kilo ohm
15 Rl=10 // kilo ohm
16 gain_beta=200
17 Vbe=0.7 // V
18
19 // for second stage
20 V_R6=Vcc*R6/(R6+R5)
21 V_R8=V_R6-Vbe
22 I_E2=V_R8/R8 // emitter current in R8
23 re_dash2=25d-3/I_E2
24 Zin_base=gain_beta*re_dash2
25 Zin=R5*(R6*Zin_base/(R6+Zin_base))/(R5+(R6*Zin_base
    /(R6+Zin_base)))
26 R_AC2=R7*Rl/(R7+Rl)
27 Av2=R_AC2/re_dash2
28
29 // for first stage
30 V_R2=Vcc*R2/(R2+R1)
31 V_R4=V_R2-Vbe
32 I_E1=V_R4/R4 // emitter current in R4
33 re_dash1=25d-3/I_E1
34 R_AC1=R3*Zin/(R3+Zin)
35 Av1=R_AC1/re_dash1
36
37 Av=Av1*Av2
38
39 printf("voltage gain of first stage = %.3f \n",Av1)
40 printf("voltage gain of second stage = %.3f \n",Av2)
41 printf("overall voltage gain= %.3f \n",Av)
42
43 // the accurate answers are voltage gain of first

```

stage = 52.616, voltage gain of second stage =
192.381, overall voltage gain= 10122.329. In book
the answers are 53,191.4 and 10144
44 // respectively

Scilab code Exa 14.15 transformer

```
1 // chapter14
2 // example14.15
3 // page 311
4
5 // for maximum power transfer , primary impedance =
   transistor output impedance and secondary
   impedance = load impedance
6 Rp=1d3 // ohm
7 Rs=10 // ohm
8
9 // since Rp=(Np/Ns)^2*Rs , making Np/Ns i.e. n as
   subject we get
10 n=(Rp/Rs)^(0.5)
11
12 printf(" required turn ratio = %d \n",n)
13
14 if n>1
15     printf("transformer required is step down
           tranformer \n")
16 elseif n<1
17     printf("transformer required is step up
           tranformer \n")
18 else // n=1
19     printf("transformer is not required \n")
20 end
```

Scilab code Exa 14.16 voltage across external load

```
1 // chapter14
2 // example14.16
3 // page 312
4
5 Vp=10 // V
6 // for maximum power transfer , primary impedance =
   output impedance of aource
7 Rp=10d3 // ohm
8 Rs=16 // ohm
9
10 // since  $R_p = (N_p/N_s)^2 * R_s$  , making  $N_p/N_s$  i.e. n as
    subject we get
11 n=(Rp/Rs)^(0.5)
12
13 // since  $V_s/V_p = N_s/N_p$  , making Vs as subject we get
14 Vs=(1/n)*Vp
15 printf(" required turn ratio = %d \n",n)
16 printf(" voltage across external load = %.3f V \n",Vs
      )
```

Scilab code Exa 14.17 turn ratio for maximum power transfer

```
1 // chapter14
2 // example14.17
3 // page 312
4
5 Rp=300 //ohm
6 Rs=3 // ohm
7 Ro=3d3 // ohm
8
9 // since output resistance of transistor  $R_o = R_p + n^2 * R_s$ 
   for maximum power transfer , making n as
   subject we get
```

```
10 n=((Ro-Rp)/Rs)^0.5
11
12 printf("turn ratio for maximum power transfer = %d \
n",n)
```

Scilab code Exa 14.18 inductance

```
1 // chapter14
2 // example14.18
3 // page 313
4
5 f=200 // Hz
6 Ro=10d3 // ohm, transistor output impedance
7 Zi2=2.5d3 // ohm, input impedance of next stage
8
9 // since Ro=2*pi*f*Lp, making Lp as subject we get
10 Lp=Ro/(2*pi*f)
11
12 // since Zi2=2*pi*f*Ls, making Ls as subject we get
13 Ls=Zi2/(2*pi*f)
14
15 printf("primary inductance = %.1f H \n",Lp)
16 printf("secondary inductance = %.1f H \n",Ls)
```

Scilab code Exa 14.19 inductance

```
1 // chapter14
2 // example14.19
3 // page 313
4
5 L=10d-6 // H
6 N=1 // turn
7 Lp=8 // H
```

```
8 Ls=2 // H
9
10 // since L is proportional to N^2, L=K*N^2 so making
    K as subject we get
11 K=L/N^2
12
13 // Lp=K*Np^2 so
14 Np=(Lp/K)^0.5
15
16 // Ls=K*Ns^2 so
17 Ns=(Ls/K)^0.5
18
19 printf("primary turns = %d \n",Np)
20 printf("secondary turns = %d \n",Ns)
```

Chapter 15

Transistor audio power amplifiers

Scilab code Exa 15.1 maximum collector current

```
1 //chapter15
2 //example15.1
3 //page321
4
5 V=12 // V
6 P=2 // W
7
8 // since P=V*Ic we get
9 Ic_max=P/V // in ampere
10
11 printf("maximum collector current = %.3f mA \n",
Ic_max*1000)
```

Scilab code Exa 15.2 maximum collector current

```
1 //chapter15
```

```
2 //example15.2
3 //page321
4
5 V=12 // V
6 R=4 // kilo ohm
7
8 //since maximum collector current will flow when
  whole battery voltage is dropped across Rc, we
  get
9 Ic_max=V/R
10
11 printf("maximum collector current = %.3f mA \n",
         Ic_max)
```

Scilab code Exa 15.3 ac output

```
1 //chapter15
2 //example15.3
3 //page321
4
5 P=50 // W
6 R=8 // ohm
7
8 // since p=V^2/R we get
9 V=(P*R)^0.5
10 I=V/R
11
12 printf("ac output voltage = %.3f V \n",V)
13 printf("ac output current = %.3f A \n",I)
```

Scilab code Exa 15.4 collector efficiency

```
1 //chapter15
```

```

2 //example15.4
3 //page325
4
5 Vcc=20 // V
6 Vbe=0.7 // V
7 Rb=1d3 // ohm
8 Rc=20 // ohm
9 gain=25
10
11 Ib=(Vcc-Vbe)/Rb
12 Ic=Ib*gain
13 Vce=Vcc-Ic*Rc
14
15 ib_peak=10d-3
16 ic_peak=gain*ib_peak
17 Po_ac=ic_peak^2*Rc/2
18 P_dc=Vcc*Ic
19 eta=(Po_ac/P_dc)*100
20
21 printf("operating point = %.3f V and %.3f mA \n",Vce
   ,Ic*1000)
22 printf("output power = %.3f W \n",Po_ac)
23 printf("input power = %.3f W \n",P_dc)
24 printf("collector efficiency = %.3f percent \n",eta)

```

Scilab code Exa 15.5 collector efficiency

```

1 //chapter15
2 //example15.5
3 //page328
4
5 Pdc=10 // W
6 Po=4 // W
7
8 eta=(Po/Pdc)*100

```

```
9
10 // maximum power dissipation in a transistor occurs
   under zero signal conditions so
11 P=Pdc
12
13 printf(" collector efficiency = %.3f percent \n",eta)
14 printf(" power rating of transistor = %.3f W \n",P)
```

Scilab code Exa 15.6 maximum ac power output

```
1 //chapter15
2 //example15.6
3 //page328
4
5 Rl=100 // ohm
6 n=10
7 Ic=100d-3 // ampere
8
9 Rl_1=n^2*Rl
10 Pmax=0.5*Ic^2*Rl_1
11
12 printf("maximum ac power output = %.3f W \n",Pmax)
```

Scilab code Exa 15.7 power dissipation

```
1 //chapter15
2 //example15.7
3 //page329
4
5 Vcc=5 // V
6 Ic=50d-3 // ampere
7
8 Pac_max=Vcc*Ic/2
```

```

9 Pdc=Vcc*Ic
10 Pdis=Pac_max*2
11 eta=(Pac_max/Pdc)*100
12
13 printf("maximum power output= %.3f mW \n", Pac_max
14 *1000)
14 printf("power dissipation = %.3f mW \n", Pdis*1000)
15 printf("maximum collector efficiency = %.3f percent
16 \n", eta)

```

Scilab code Exa 15.8 loudspeaker

```

1 //chapter15
2 //example15.8
3 //page329
4
5 del_Ic=100d-3 // ampere
6 del_Vce=12 // V
7 Rl=5 // ohm
8
9 //case 1 : loudspeaker directly connected
10 V=del_Ic*Rl
11 P=V*del_Ic
12
13 //case2 : loudspeaker transformer coupled
14 R_primary=del_Vce/del_Ic // for maximum power
15 transfer the primary resistance should be equal
16 to R
17 n=(R_primary/Rl)^0.5
18 V_secondary=del_Vce/n
19 I1=V_secondary/Rl
20 P_1=I1^2*Rl
21
22 printf("case1 : loudspeaker connected directly \n
23 power transferred to loudspeaker = %.3f mW \

```

```
n" ,P*1000)  
21 printf("case2 : loudspeaker is transformer coupled \  
n      power transferred to loudspeaker = %.3f mW  
\n" ,P_1*1000)
```

Scilab code Exa 15.9 current

```
1 //chapter15  
2 //example15.9  
3 //page331  
4  
5 Vcc=17.5 // V  
6 ic_max=35d-3 // ampere  
7 ic_min=1d-3 // ampere  
8 IC=18 // ampere  
9 gain=100  
10 vce_max=30 // V  
11 vce_min=5 // V  
12 Rl=81.6 // ohm  
13  
14 IC=ic_min+((ic_max-ic_min)/2)  
15 IB=IC/gain  
16 VCE=vce_min+((vce_max-vce_min)/2)  
17  
18 Pdc=Vcc*IC  
19 Vce=(vce_max-vce_min)/(2*2^0.5)  
20 Ic=(ic_max-ic_min)/(2*2^0.5)  
21 Pac=Vce*Ic  
22  
23 eta=(Pac/Pdc)*100  
24  
25 slope=(ic_max-ic_min)/(vce_min-vce_max)  
26 Rl_dash=-1/slope  
27 n=(Rl_dash/Rl)^0.5  
28
```

```
29 printf("zero signal collector current = %.3f mA \n" ,  
    IC*1000)  
30 printf("zero signal base current = %.3f mA \n" ,IB  
    *1000)  
31 printf("dc power = %.3f mW and ac power = %.3f mW \n  
    " ,Pdc*1000 ,Pac*1000)  
32 printf("collector efficiency = %.3f percent \n" ,eta)  
33 printf("transformer turn ratio = %.1f \n" ,n)
```

Scilab code Exa 15.10 maximum ambient temperature at which transistor can be operated

```
1 //chapter15  
2 //example15.10  
3 //page333  
4  
5 P_total=4 // W  
6 T_Jmax=90 // degree celcius  
7 theta=10 // degree celcius per watt  
8  
9 // P_total=(T_Jmax-Tamb)/theta so making Tamb as  
// subject we get  
10 Tamb=T_Jmax-P_total*theta  
11  
12 printf("maximum ambient temperature at which  
    transistor can be operated = %.3f degree C \n" ,  
    Tamb)
```

Scilab code Exa 15.11 maximum power dissipation

```
1 //chapter15  
2 //example15.11  
3 //page333  
4
```

```

5 T_Jmax=90 // degree celcius
6 T_amb=30 // degree celcius
7
8 //case 1 : without heat sink
9 theta1=300 // degree celcius per watt
10 P_total1=(T_Jmax-T_amb)/theta1
11
12 //case 2 : with heat sink
13 theta2=60 // degree celcius per watt
14 P_total2=(T_Jmax-T_amb)/theta2
15
16 printf("case 1 : without heat sink \n maximum
           power dissipation = %.3f mW \n",P_total1*1000)
17 printf("case 2 : with heat sink \n maximum power
           dissipation = %.3f mW \n",P_total2*1000)

```

Scilab code Exa 15.12 allowed collector current

```

1 //chapter15
2 //example15.12
3 //page334
4
5 T_Jmax=200 // degree celcius
6 T_amb1=25 // degree celcius
7 T_amb2=75 // degree celcius
8 theta=20 // degree celcius per watt
9 Vcc=4 // V
10
11 P_total1=(T_Jmax-T_amb1)/theta
12 Ic1=P_total1/Vcc
13
14 P_total2=(T_Jmax-T_amb2)/theta
15 Ic2=P_total2/Vcc
16
17 printf("for ambient = 25 degree C, allowed collector

```

```
    current = %.3f A \n",Ic1)  
18 printf("for ambient = 75 degree C, allowed collector  
    current = %.3f A \n",Ic2)
```

Chapter 16

Amplifiers with negative feedback

Scilab code Exa 16.1 voltge gain with negative feedback

```
1 //chapter16
2 //example16.1
3 //page345
4
5 Av=3000
6 mv=0.01
7
8 Avf=Av/(1+Av*mv)
9 printf("voltge gain with negative feedback = %.3f \n
      ",Avf)
10
11 // accurate answer is 96.774 but in book it is given
     as 97
```

Scilab code Exa 12.2 fraction of output fed back to input

```
1 //chapter16
2 //example16.2
3 //page346
4
5 Av=140
6 Avf=17.5
7
8 // since Avf=Av/(1+Av*mv) , making mv as subject we
   get
9 mv=(Av/Avf-1)/Av
10 printf("fraction of output fed back to input = %.3f
          \n",mv)
```

Scilab code Exa 16.3 overall gain

```
1 //chapter16
2 //example16.3
3 //page346
4
5 Av1=100
6 Avf1=50
7 Avf2=75
8
9 // since Avf=Av/(1+Av*mv) , we get
10 mv=(Av1/Avf1-1)/Av1
11 Av2=Avf2/(1-mv*Avf2)
12
13 printf("fraction of output fed back to input = %.3f
          \n",mv)
14 printf("for overall gain = 75 and same fraction ,
          required gain = %.3f \n",Av2)
```

Scilab code Exa 16.4 fraction of output fed back to input

```

1 // chapter16
2 // example16.4
3 // page346
4
5 Vo=10
6 Vi=0.25
7 Vif=0.5
8
9 Av=Vo/Vi
10 Avf=Vo/Vif
11
12 // since Avf=Av/(1+Av*mv) , we get
13 mv=(Av/Avf-1)/Av
14
15 printf("fraction of output fed back to input = %.3f
          \n",mv)

```

Scilab code Exa 16.5 percentage reduction in gain

```

1 // chapter16
2 // example16.5
3 // page347
4
5 Av=50
6 Avf=25
7
8 // since Avf=Av/(1+Av*mv) , we get
9 mv=(Av/Avf-1)/Av
10
11 // without feedback , gain falls from 50 to 40
12 Av1=50
13 Av2=40
14 reduction1=100*(Av1-Av2)/Av1
15
16 // with feedback

```

```
17 Av3=25
18 Av4=Av2/(1+mv*Av2)
19 reduction2=100*(Av3-Av4)/Av3
20
21 printf(" percentage reduction in gain : \n with
    feedback = %.3f percent \n ",reduction1)
22 printf("without feedback = %.3f percent",reduction2)
```

Scilab code Exa 16.6 percentage change in gain

```
1 //chapter16
2 //example16.6
3 //page347
4
5 Av=100
6 mv=0.1
7
8 Avf=Av/(1+Av*mv)
9 mv=(Av/Avf-1)/Av
10
11 // fall in gain is 6dB so 20 log (Av/Av1)=6
12 // making Av1 as subject we get
13 Av1=Av/exp(6*log(10)/20)
14 Avf_new=Av1/(1+Av1*mv)
15 change=100*(Avf-Avf_new)/Avf
16
17 printf("percentage change in gain = %.3f percent \n"
    ,change)
18
19 // the accurate answer is 8.297 percent but in book
    it is given as 8.36 percent
```

Scilab code Exa 16.7 voltage gain with negative feedback

```

1 //chapter16
2 //example16.7
3 //page348
4
5 A0=1000
6 Rout=100 // ohm
7 Rl=900
8 mv=1/50
9
10 Av=A0*Rl/(Rout+Rl)
11 Avf=Av/(1+Av*mv)
12 printf("voltage gain with negative feedback = %.3f \
n",Avf)
13
14 // the accurate answer is 47.368 but in book it is
given as 47.4

```

Scilab code Exa 16.8 voltage gain with negative feedback

```

1 //chapter16
2 //example16.8
3 //page351
4
5 Av=10000
6 R1=2 // kilo ohm
7 R2=18 // kilo ohm
8 Vi=1 // mV
9
10 mv=R1/(R1+R2)
11 Avf=Av/(1+Av*mv)
12 Vout=Avf*Vi
13
14 printf("feedback fraction = %.1f \n",mv)
15
16 printf("voltage gain with negative feedback = %.1f \

```

```
    n" ,Avf)  
17  
18 printf("output voltage = %.1f mV \n",Vout)
```

Scilab code Exa 16.9 Example 9

```
1 //chapter16  
2 //example16.9  
3 //page351  
4  
5 Av=10000  
6 R1=10 // kilo ohm  
7 R2=90 // kilo ohm  
8 Zin=10 // kilo ohm  
9 Zout=100d-3 // kilo ohm  
10  
11 mv=R1/(R1+R2)  
12 Avf=Av/(1+Av*mv)  
13 Zin_dash=(1+Av*mv)*Zin  
14 Zout_dash=Zout/(1+Av*mv)  
15  
16 printf("feedbackfraction = %.1f \n",mv)  
17  
18 printf("voltage gain with negative feedback = %.1f \n",Avf)  
19  
20 printf("input impedance with feedback = %.3f kilo  
        ohm or %.3f mega ohm \n",Zin_dash,Zin_dash/1000)  
21  
22 printf("output impedance with feedback = %f kilo ohm  
        or %.3f ohm \n",Zout_dash,Zout_dash*1000)
```

Scilab code Exa 16.10 distortion of amplifier with negative feedback

```

1 //chapter16
2 //example16.10
3 //page352
4
5 Av=150
6 D=5/100
7 mv=10/100
8
9 Dvf=100*D/(1+Av*mv) // in percent
10
11 printf("distortion of amplifier with negative
    feedback = %.3f percent",Dvf)

```

Scilab code Exa 16.11 cutoff frequency with negative feedback

```

1 //chapter16
2 //example16.11
3 //page352
4
5 Av=1000
6 mv=0.01
7 f1=1.5 // kHz
8 f2=501.5 // kHz
9
10 f_1f=f1/(1+Av*mv)
11 f_2f=f2*(1+mv*Av)
12
13 printf("new lower cutoff frequency with negative
    feedback = %.3f kHz or %.3f Hz \n",f_1f,f_1f
    *1000)
14 printf("new upper cutoff frequency with negative
    feedback = %.3f kHz or %.3f MHz \n",f_2f,f_2f
    /1000)
15
16 // the accurate answers are 136.364 Hz and 5.516 MHz

```

but in book they are given as 136.4 Hz and 5.52 MHz respectively

Scilab code Exa 16.12 effective current gain of amplifier

```
1 //chapter16
2 //example16.12
3 //page353
4
5 Ai=200
6 mi=0.012
7
8 Aif=Ai/(1+mi*Ai)
9
10 printf("effective current gain of amplifier = %.3f \
n",Aif)
```

Scilab code Exa 16.13 input impedance with negative feedback

```
1 //chapter16
2 //example16.13
3 //page354
4
5 Zin=15 // kilo ohm
6 Ai=240
7 mi=0.015
8
9 Zin_dash=Zin/(1+mi*Ai)
10
11 printf("input impedance with negative feedback = %.3
f kilo ohm \n",Zin_dash)
```

Scilab code Exa 16.14 output impedance with negative feedback

```
1 //chapter16
2 //example16.14
3 //page355
4
5 Zout=3 // kilo ohm
6 Ai=200
7 mi=0.01
8
9 Zout_dash=Zout*(1+mi*Ai)
10
11 printf("output impedance with negative feedback = %.
.3f kilo ohm \n",Zout_dash)
```

Scilab code Exa 16.15 Bandwidth with negative feedback

```
1 //chapter16
2 //example16.15
3 //page355
4
5 BW=400 // kHz
6 Ai=250
7 mi=0.01
8
9 BW_dash=BW*(1+mi*Ai)
10
11 printf("Bandwidth with negative feedback = %.3f kHz
\n",BW_dash)
```

Scilab code Exa 16.16 voltage across

```
1 //chapter16
2 //example16.16
3 //page356
4
5 Vcc=18 // V
6 R1=16 // kilo ohm
7 R2=22 // kilo ohm
8 Vbe=0.7 // V
9 Re=910d-3 // kilo ohm
10
11 V2=Vcc*R2/(R1+R2)
12 Ve=V2-Vbe
13 Ie=Ve/Re
14
15 printf("voltage across Re = %.3f V \n",Ve)
16 printf("emitter current = %.3f mA \n",Ie)
17
18 clf()
19 x=linspace(0,18,100)
20 y=-(19.78/18)*x+19.78
21 xtitle("dc load line","Vce(volts)","Ic(mA)")
22 plot2d(x,y,style=3,rect=[0,0,19,20])
```

Scilab code Exa 16.17 voltage gain

```
1 //chapter16
2 //example16.17
3 //page357
4
5 Vcc=10 // V
6 R1= 10 // kilo ohm
7 R2=10 // kilo ohm
8 Vbe=0.7 // V
```

```
9 Re=5000 // ohm
10
11 V2=Vcc*R2/(R1+R2)
12 Ve=V2-Vbe
13 Ie=Ve/(Re/1000) // in mA
14 re_dash=25/Ie
15 Av=Re/(re_dash+Re)
16
17 printf(" voltage gain = %.3f \n",Av)
```

Scilab code Exa 16.18 voltage gain

```
1 //chapter16
2 //example16.18
3 //page358
4
5 Re=5d3 // ohm
6 Rl=5d3 // ohm
7 re_dash=29.1 // in ohm, from example 16_17
8
9 Re_dash=Re*Rl/(Re+Rl)
10 Av=Re_dash/(re_dash+Re_dash)
11
12 printf(" voltage gain = %.3f \n",Av)
```

Scilab code Exa 16.19 input impedance

```
1 //chapter16
2 //example16.19
3 //page359
4
5 Vcc=10 // V
6 R1= 10 // kilo ohm
```

```

7 R2=10 // kilo ohm
8 Vbe=0.7 // V
9 Re=4.3 // kilo ohm
10 gain_beta=200
11
12 V2=Vcc*R2/(R1+R2)
13 Ve=V2-Vbe
14 Ie=Ve/Re
15 re_dash=25/Ie
16 Re_dash=Re*R1/(Re+R1)
17 Zin_base=gain_beta*(re_dash+Re_dash)
18 Zin=Zin_base*(R1*R2/(R1+R2))/(Zin_base+R1*R2/(R1+R2))
    )
19
20 printf("input impedance = %.3f kilo ohm \n",Zin)
21
22 // the accurate answer is 4.996 kilo ohm but in book
    it is given as 4.96 kilo ohm

```

Scilab code Exa 16.20 output impedance

```

1 //chapter16
2 //example16.20
3 //page361
4
5 R1=3d3 // ohm
6 R2=4.7d3 // ohm
7 Rs=600 // ohm
8 re_dash=20 // ohm
9 gain_beta=200
10
11 Rin_dash=R1*(R2*Rs/(R2+Rs))/(R1+(R2*Rs/(R2+Rs)))
12
13 Zout=re_dash+Rin_dash/gain_beta
14

```

```
15 printf("output impedance = %.1f ohm \n", Zout)
```

Chapter 17

Sinusoidal oscillations

Scilab code Exa 17.1 frequency of oscillations

```
1 //chapter17
2 //example17.1
3 //page375
4
5 L1=58.6d-6 // H
6 C1=300d-12 // F
7
8 f=1/(2*%pi*(L1*C1)^0.5)
9 printf("frequency of oscillations = %.3f Hz or %.3f
kHz",f,f/1000)
10
11 // in book the answer is 1199 kHz but the accurate
answer is 1200.358 kHz
```

Scilab code Exa 17.2 operating frequency

```
1 //chapter17
2 //example17.2
```

```

3 // page377
4
5 C1=0.001d-6 // F
6 C2=0.01d-6 // F
7 L=15d-6 // H
8
9 Ct=C1*C2/(C1+C2) // since both are in series
10
11 f=1/(2*pi*(L*Ct)^0.5)
12 mv=C1/C2
13
14 printf("operating frequency = %.3f Hz or %.3f kHz \n
           ", f, f/1000)
15 printf("feedback function = %.3f", mv)
16
17 //in book the answer given is 1361 kHz but accurate
   answer is 1362.922 kHz

```

Scilab code Exa 17.3 feedback function

```

1 //chapter17
2 //example17.3
3 //page379
4
5 L1=1000d-6 // H
6 L2=100d-6 // H
7 M=20d-6 // H
8 C=20d-12 // F
9
10 Lt=L1+L2+2*M
11
12 f=1/(2*pi*(Lt*C)^0.5)
13 mv=L2/L1
14
15 printf("operating frequency = %.3f Hz or %.3f kHz \n
           ", f, f/1000)

```

```
    " ,f ,f/1000)
16 printf(" feedback function = %.3f" ,mv)
17
18 // in book the answer is 1052 kHz but the accurate
   answer is 1054.029 kHz
```

Scilab code Exa 17.4 frequency of oscillations

```
1 //chapter17
2 //example17.4
3 //page381
4
5 R=1d6 // ohm
6 C=68d-12 // F
7
8 fo=1/(2*pi*R*C*(6) ^0.5)
9 printf(" frequency of oscillations = %.3f Hz" ,fo)
10
11 // in book the answer given is 954 Hz but the
   accurate answer is 955.511 Hz
```

Scilab code Exa 17.5 frequency of oscillations

```
1 //chapter17
2 //example17.5
3 //page382
4
5 R=220d3 // ohm
6 C=250d-12 // F
7
8 f=1/(2*pi*R*C)
9 printf(" frequency of oscillations = %.3f Hz" ,f)
10
```

```
11 //in book the answer given is 2892 Hz but the  
    accurate answer is 2893.726 Hz
```

Scilab code Exa 17.6 thickness of crystal

```
1 //chapter17  
2 //example17.6  
3 //page387  
4  
5 // frequency is inversely proportional to thickness  
6 // so if thickness is reduced by 1%, frequency  
    increases by 1%  
7  
8 printf("If thickness of crystal is reduced by 1  
    percent , then \nfrequency is increased by 1  
    percent \nbecause frequency is inversely  
    proportional to thickness \n")
```

Scilab code Exa 17.7 resonant frequency

```
1 //chapter17  
2 //example17.7  
3 //page387  
4  
5 L=1 // H  
6 C=0.01d-12 // F  
7 Cm=20d-12 // F  
8  
9 fs=1/(2*%pi*(L*C)^0.5)  
10 Ct=C*Cm/(C+Cm)  
11 fp=1/(2*%pi*(L*Ct)^0.5)  
12
```

```
13 printf("series resonant frequency = %.3f Hz or %.3f  
kHz\n", fs, fs/1000)  
14 printf("parallel resonant frequency = %.3f Hz or %.3  
f kHz\n", fp, fp/1000)  
15  
16 // in book the answer given is 1589 kHz for series  
resonant frequency but the accurate answer is  
1591.549 kHz  
17 // in book the answer given is 1590 kHz for parallel  
resonant frequency but the accurate answer is  
1591.947 kHz
```

Chapter 18

Transistor tuned amplifiers

Scilab code Exa 18.1 impedance of circuit at resonance

```
1 //chapter18
2 //example18.1
3 //page396
4 L=1.25d-3 // H
5 C=250d-12 // F
6 R=10 // ohm
7
8 fr(((1/(L*C))-(R^2/L^2))^0.5)/(2*pi)
9 Zr=L/(C*R)
10 Q=2*pi*fr*L/R
11
12 printf("resonant frequency of circuit = %.3f Hz or %.
.3f kHz \n",fr,fr/1000)
13 printf("impedance of circuit at resonance = %.3f ohm
or %.3f kilo ohm \n",Zr,Zr/1000)
14 printf("quality factor of the circuit = %.3f",Q)
```

Scilab code Exa 18.2 circuit

```

1 //chapter18
2 //example18.2
3 //page396
4
5 L=100d-6 // H
6 C=100d-12 // F
7 R=10 // ohm
8 V=10 // V
9
10 fr(((1/(L*C))-(R^2/L^2))^0.5)/(2*pi)
11 Zr=L/(C*R)
12 I=V/Zr
13
14 printf("resonant frequency of circuit = %.3f Hz or %.
.3f kHz \n",fr,fr/1000)
15 printf("impedance of circuit at resonance = %.3f ohm
or %.3f kilo ohm or %.3f mega ohm\n",Zr,Zr/1000,
Zr/1d6)
16 printf("line current = %.4f ampere or %.3f micro
ampere",I,I*1d6)
17
18 // the accurate answer for resonant frequency is
1591.470 kHz

```

Scilab code Exa 18.3 frequency

```

1 //chapter18
2 //example17.3
3 //page398
4
5 fr=1200 // kHz
6 Q=60
7
8 BW=fr/Q
9 f1=fr-(BW/2)

```

```
10 f2=fr+(BW/2)
11
12 printf("bandwidth = %.3f kHz \n",BW)
13 printf("lower cut-off frequency = %.3f kHz \n",f1)
14 printf("upper cut-off frequency = %.3f kHz \n",f2)
```

Scilab code Exa 18.4 frequency

```
1 //chapter18
2 //example18.4
3 //page401
4
5 L=33d-3 // H
6 C=0.1d-6 // F
7 R=25 // ohm
8
9 fr=1/(2*pi*(L*C)^0.5)
10 Xl=2*pi*fr*L
11 Q=Xl/R
12 BW=fr/Q
13
14 printf("resonant frequency = %.3f Hz or %.3f kHz \n"
,fr,fr/1000)
15 printf("quality factor = %.3f \n",Q)
16 printf("bandwidth = %.3f Hz \n",BW)
17
18 // the accurate answer for bandwidth is 120.572 Hz
// but in book it is given as 120 Hz
19 // the accurate answer for quality factor is 22.978
// but in book it is given as 23
```

Scilab code Exa 18.5 co-efficient of coupling

```

1 //chapter18
2 //example18.5
3 //page402
4
5 BW=200 // kHz
6 fr=10d3 // kHz
7
8 k=BW/fr
9
10 printf("co-efficient of coupling = %.3f \n",k)

```

Scilab code Exa 18.6 ac load

```

1 //chapter18
2 //example18.6
3 //page405
4
5 L=50.7d-6 // H
6 C=500d-12 // F
7 R=10 // ohm
8 Rl=1d6 // ohm
9
10 fr=1/(2*pi*(L*C)^0.5)
11 R_dc=R
12 Xl=2*pi*fr*L
13 Q=Xl/R
14 Rp=Q*Xl
15 R_ac=Rp*Rl/(Rp+Rl)
16
17 printf("resonant frequency = %.3f Hz or %.3f kHz \n"
18 ,fr,fr/1000) // answer in book is incorrect
19 printf("dc load = %.3f ohm \n",R_dc)
20 printf("ac load = %.3f ohm or %.3f kilo ohm \n",R_ac
21 ,R_ac/1000)
20

```

```
21 // in book the answer for resonant frequency is 106
22 // Hz which is incorrect
23 // the correct answer is 999.611 kHz
24 // the accurate answer for ac load is 10.038 kilo
ohm
```

Scilab code Exa 18.7 load

```
1 //chapter18
2 //example18.7
3 //page406
4
5 Vcc=50 // V
6 Np=5
7 Ns=1
8 R=50 // ohm
9 R_ac=(Np/Ns)^2*R
10 Po=Vcc^2/R_ac
11
12 printf("ac load = %.3f ohm \n",R_ac)
13 printf("maximum load power = %.3f W \n",Po)
```

Chapter 19

Modulation and demodulation

Scilab code Exa 19.1 Vmax\&Vmin

```
1 //chapter19
2 //example19.1
3 //page416
4
5 // the figure in book is for reference only as
   equations for Ec and Es are already explained in
   the theory in the book.
6
7 printf("Ec=(Vmax+Vmin)/2 \n")
8 printf("Es=(Vmax-Vmin)/2 \n")
9 printf("But, Es=m*Ec \n")
10 printf("So (Vmax-Vmin)/2 = m*(Vmax+Vmin)/2 \n")
11 printf("thus, m = (Vmax-Vmin)/(Vmax+Vmin) \n")
```

Scilab code Exa 19.2 modulation factor

```
1 //chapter19
2 //example19.2
```

```
3 // page416
4
5 // figure is given in book for understanding purpose
   only. It is not required for solving the example
   as maximum and minimum peak voltages are given in
   the problem statement itself.
6
7 Vmax_pp=16 // mV
8 Vmin_pp=4 // mV
9
10 Vmax=Vmax_pp/2
11 Vmin=Vmin_pp/2
12
13 m=(Vmax-Vmin)/(Vmax+Vmin)
14
15 printf(" modulation factor = %.3f \n",m)
```

Scilab code Exa 19.3 modulation factor

```
1 // chapter19
2 // example19.3
3 // page417
4
5 Es=50 // V
6 Ec=100 // V
7
8 m=Es/Ec
9
10 printf(" modulation factor = %.3f \n",m)
```

Scilab code Exa 19.4 Bandwidth for RF amplifier

```
1 // chapter19
```

```

2 //example19.4
3 //page419
4
5 fc=2500 // kHz
6 fs_min=0.05 // kHz
7 fs_max=15 // kHz
8
9 upper_sideband_min=fc+fs_min
10 upper_sideband_max=fc+fs_max
11
12 lower_sideband_min=fc-fs_min
13 lower_sideband_max=fc-fs_max
14
15 BW=upper_sideband_max-lower_sideband_max
16
17 printf("lower sideband is from %.3f to %.3f kHz \n",
18     lower_sideband_min,lower_sideband_max)
19 printf("upper sideband is from %.3f to %.3f kHz \n",
20     upper_sideband_min,upper_sideband_max)
21 printf("Bandwidth for RF amplifier = %.3f kHz \n",BW
22 )

```

Scilab code Exa 19.5 amplitudes of components

```

1 //chapter19
2 //example19.5
3 //page420
4
5 // v=5*(1+0.6*cos(6280*t))*sin(211d4*t) V
6 // compare with v=Ec*(1+m*cos(ws*t))*sin(wc*t) we
7 // get
8 Ec=5 // V
9 m=0.6
10 fs=6280/(2*pi) // Hz
11 fc=211d4/(2*pi) // Hz

```

```

11
12 Vmin=Ec-m*Ec
13 Vmax=Ec+m*Ec
14
15 f1=(fc-fs)/1000 // in kHz
16 f2=fc/1000 // in kHz
17 f3=(fc+fs)/1000 // in kHz
18
19 V1=m*Ec/2
20 V2=Ec
21 V3=m*Ec/2
22
23 printf("minimum amplitude = %.3f V and maximum
           amplitude = %.3f V \n",Vmin,Vmax)
24 printf("frequency components = %.1f kHz, %.1f Hz, %
           .1fkHz \n",f1,f2,f3)
25 printf("amplitudes of components = %.3f V, %.3f V, %
           .3 f V \n",V1,V2,V3)
26
27 // in book there is error of 0.2 kHz in every
   frequency component. The accurate answers are
   334.8,335.8,336.8 kHz

```

Scilab code Exa 19.6 amplitude of each sideband term

```

1 //chapter19
2 //example19.6
3 //page420
4
5 fc=1000 // kHz
6 fs=5 // kHz
7 m=0.5
8 Ec=100 // V
9
10 lower_sideband=fc-fs

```

```
11 upper_sideband=fc+fs
12 amplitude=m*Ec/2
13
14 printf("lower and upper sideband frequencies = %.3f
    kHz and %.3f kHz \n",lower_sideband,
    upper_sideband)
15 printf("amplitude of each sideband term = %.3f V \n"
    ,amplitude)
```

Scilab code Exa 19.7 power of modulated wave

```
1 //chapter19
2 //example19.7
3 //page422
4
5 Pc=500 // W
6 m=1
7
8 Ps=0.5*m^2*Pc
9 Pt=Pc+Ps
10
11 printf("sideband power = %.3f W \n",Ps)
12 printf("power of modulated wave = %.3f W \n",Pt)
```

Scilab code Exa 19.8 sideband power

```
1 //chapter19
2 //example19.8
3 //page422
4
5 m1=0.8
6 m2=0.1
7 Pc=50 // kW
```

```
8
9 Ps1=0.5*m1^2*Pc
10 Ps2=0.5*m2^2*Pc
11
12 printf("for m=0.8, sideband power = %.3f kW \n",Ps1)
13 printf("for m=0.1, sideband power = %.3f kW \n",Ps2)
```

Scilab code Exa 19.9 modulating signal

```
1 //chapter19
2 //example19.9
3 //page422
4
5 // block diagram is for understanding purpose only.
      It is not required to solve the example
6 m=1
7 eta=0.72
8 // carrier is not affected by modulating signal so
      its power level remains unchanged before and
      after modulation
9 Pc=40 // kW
10 Ps=0.5*m^2*Pc
11 P_audio=Ps/eta
12
13 printf("carrier power after modulation = %.3f kW \n"
      ,Pc)
14 printf("required audio power = %.3f kW \n",P_audio)
```

Scilab code Exa 19.10 frequencie & bandwith

```
1 //chapter19
2 //example19.10
3 //page423
```

```

4
5 fc=500 // kHz
6 fs=1 // kHz
7
8 lower_sideband=fc-fs
9 upper_sideband=fc+fs
10 BW=upper_sideband-lower_sideband
11
12 printf("sideband frequencies = %.3f kHz and %.3f kHz
13 printf("bandwidth required = %.3f kHz \n",BW)

```

Scilab code Exa 19.11 antenna current

```

1 //chapter19
2 //example19.11
3 //page423
4
5 m=0.4
6 Ic=8 // A
7 // Pt=Pc+Ps and Ps=0.5*m^2*Pc so Pt=Pc*(1+m^2/2)
8 // so Pt/Pc=1+m^2/2 but P is proportional to I^2 so
9 // (It/Ic)^2=1+m^2/2 and thus we get
10
11 It=Ic*(1+m^2/2)^0.5
12
13 printf("antenna current for m=0.4 is = %.3f A \n",It
)

```

Scilab code Exa 19.12 modulation factor

```

1 //chapter19
2 //example19.12

```

```

3 // page424
4
5 It=8.93 // A
6 Ic=8 // A
7
8 // we know that (It/Ic)^2=1+m^2/2 so making m as
   subject we get
9 m=(2*((It/Ic)^2-1))^0.5
10
11 printf("modulation factor = %.3f or %.3f percent \n"
      ,m,m*100)

```

Scilab code Exa 19.13 modulation factor

```

1 //chapter19
2 //example19.13
3 //page424
4
5 Vt=110 // V
6 Vc=100 // V
7
8 // since Pt/Pc=1+m^2/2 and P is proportional to V^2
   we get (Vt/Vc)^2=1+m^2/2
9 // making m as subject we get
10
11 m=(2*((Vt/Vc)^2-1))^0.5
12
13 printf("modulation factor = %.3f or %.3f percent \n"
      ,m,m*100)

```

Scilab code Exa 19.14 AM wave

```
1 //chapter19
```

```

2 //example19.14
3 //page424
4
5 Vc=5 // V
6 V_lower=2.5 // V
7 V_upper=2.5 // V
8 R=2 // kilo ohm
9
10 // figure given in book is just for understanding
   purpose. It is not a part of solution.
11 // however, the figure has been made in xcos and
   screenshot has been attached for reference
12
13 // since power=(rms voltage)^2/R we get
14
15 Pc=(0.707*Vc)2/R
16 Plower=(0.707*Vlower)2/R
17 Pupper=(0.707*Vupper)2/R
18 Pt=Pc+Plower+Pupper
19
20 printf("power delivered by carrier = %.3f mW \n",Pc)
21 printf("power delivered by lower sideband = %.3f mW
   \n",Plower)
22 printf("power delivered by upper sideband = %.3f mW
   \n",Pupper)
23 printf("total power delivered by AM wave = %.3f mW \
   \n",Pt)

```

Chapter 20

Regulated dc power supply

Scilab code Exa 20.1 regulation

```
1 //chapter20
2 //example20.1
3 //page437
4
5 V_NL=400 // V
6 V_FL=300 // V
7
8 regulation=((V_NL-V_FL)/V_FL)*100
9
10 printf(" percent voltage regulation = %.3f percent \n
" ,regulation)
```

Scilab code Exa 20.2 full load voltage

```
1 //chapter20
2 //example20.2
3 //page437
4
```

```

5 V_NL=30 // V
6 regulation=1
7
8 // since regulation=((V_NL-V_FL)/V_FL)*100, we get
   V_FL as
9
10 V_FL=100*V_NL/(100+regulation)
11 printf(" full load voltage = %.3f V \n",V_FL)

```

Scilab code Exa 20.3 regulation for power

```

1 //chapter20
2 //example20.3
3 //page437
4
5 // for power supply A
6 V_NL1=30 // V
7 V_FL1=25 // V
8
9 regulation1=((V_NL1-V_FL1)/V_FL1)*100
10
11 //for power supply B
12 V_NL2=30 // V
13 V_FL2=29 // V
14
15 regulation2=((V_NL2-V_FL2)/V_FL2)*100
16
17 printf(" regulation for power supply A =%.3f percent
      \n",regulation1)
18 printf(" regulation for power supply B =%.3f percent
      \n",regulation2)
19
20 if regulation1>regulation2 then
21     printf("thus, power supply B is better \n")
22 elseif regulation2>regulation1 then

```

```
23         printf("thus , power supply A is better \n")
24     else      printf("both are equally good \n")
25 end
```

Scilab code Exa 20.4 minimum load resistance

```
1 //chapter20
2 //example20.4
3 //page438
4
5 V_NL=500 // V
6 V_FL=300 // V
7 I_FL=120 // mA
8
9 regulation=((V_NL-V_FL)/V_FL)*100
10
11 Rl_min=V_FL/I_FL
12
13 printf("voltage regulation = %.3f percent \n",
14 regulation)
14 printf("minimum load resistance = %.3f kilo ohm \n",
15 Rl_min)
```

Scilab code Exa 20.5 maximum zener current

```
1 //chapter20
2 //example20.5
3 //page441
4
5 Vin=24 // V
6 Vout=12 // V
7 Rs=160 // ohm
8 Rl_min=200 // ohm
```

```

9
10 Is=(Vin-Vout)/Rs // in ampere
11
12 // minimum load occurs when Rl tends to infinity so
13 Il_min=0
14
15 // maximum load occurs when Rl=200 ohm
16 Il_max=Vout/Rl_min // in ampere
17
18 Iz_min=Is-Il_max // in ampere
19 Iz_max=Is-Il_min // in ampere
20
21 printf("current through series resistance = %.3f mA \
n \n",Is*1000)
22 printf("minimum load current = %.3f mA \n",Il_min
*1000)
23 printf("maximum load current = %.3f mA \n",Il_max
*1000)
24 printf("minimum zener current = %.3f mA \n",Iz_min
*1000)
25 printf("maximum zener current = %.3f mA \n \n",
Iz_max*1000)
26
27 printf("comment : current Is through Rs is constant
.\nAs load current increases from 0 to 60 mA,
zener current decreases from 75 to 15 mA,
\nmaintaining Is constant.\nThis is the normal
operation of zener regulator \ni.e. Is and Vout
remain constant inspite of changes in load or
source voltage .")

```

Scilab code Exa 20.6 required series resistance

```

1 //chapter20
2 //example20.6

```

```

3 //page441
4
5 Vin_min=22 // V
6 Vout=15 // V
7 Il_max=0.1 // A
8
9 // for maximum series resistance , we consider the
   case when input voltage is minimum and load
   current is maximum because then zener current
   drops to minimum.Thus ,
10 Rs_max=(Vin_min-Vout)/Il_max
11
12 printf(" required series resistance = %.3f ohm \n",
      Rs_max)

```

Scilab code Exa 20.7 load voltage & current

```

1 //chapter20
2 //example20.7
3 //page442
4
5 Vz=10 // V
6 Vbe=0.5 // V
7 Rl=1000 // ohm
8
9 Vout=Vz-Vbe
10 Il=Vout/Rl
11
12 printf("load voltage = %.3f V \n",Vout)
13 printf("load current = %.3f mA \n",Il*1000)

```

Scilab code Exa 20.8 Zener diode

```

1 //chapter20
2 //example20.8
3 //page441
4
5 Ic=1 // A
6 gain=50
7 Vout=6 // V
8 Vbe=0.5 // V
9 Vin=10 // V
10 Iz=10d-3 // A
11
12 Ib=Ic/gain
13 Vz=Vbe+Vout // Vout=Vz-Vbe
14
15 V_Rs=Vin-Vz
16 Rs=V_Rs/(Ib+Iz)
17
18 printf("required breakdown voltage for zener diode =
    %.3f V \n",Vz)
19 printf("required value of Rs = %.3f ohm \n",Rs)
20
21 // in book Rs=117 ohm but accurate answer is 116.667
    ohm
22
23 // note : in xcos , there is no Zener diode so in the
    result (circuit) file a simple diode is used to
    represent a zener diode

```

Scilab code Exa 20.9 Zener diode

```

1 //chapter20
2 //example20.9
3 //page443
4
5 Vz=12 // V

```

```

6 Vbe=0.7 // V
7 Vin=20 // V
8 Rs=220 // ohm
9 Rl=1d3 // ohm
10 gain=50
11
12 Vout=Vz-Vbe
13 V_Rs=Vin-Vz
14 I_Rs=V_Rs/Rs
15 I1=Vout/Rl
16 Ic=I1
17 Ib=Ic/gain
18 Iz=I_Rs-Ib
19
20 printf("output voltage = %.3f V \n",Vout)
21 printf("zener current = %.3f mA \n",Iz*1000)

```

Scilab code Exa 20.10 regulated output voltage

```

1 //chapter20
2 //example20.10
3 //page445
4
5 R2=1 // kilo ohm
6 R1=2 // kilo ohm
7 Vz=6 // V
8 Vbe=0.7 // V
9
10 m=R2/(R1+R2)
11 A_CL=1/m
12 Vout=A_CL*(Vz+Vbe)
13
14 printf("regulated output voltage = %.3f V \n",Vout)

```

Scilab code Exa 20.11 closed loop voltage gain

```
1 //chapter20
2 //example20.11
3 //page445
4
5 R2=10 // kilo ohm
6 R1=30 // kilo ohm
7
8 m=R2/(R1+R2)
9 A_CL=1/m
10
11 printf("closed loop voltage gain = %.3f \n",A_CL)
```

Scilab code Exa 20.12 collector current

```
1 //chapter20
2 //example20.12
3 //page446
4
5 Vz=8.3 // V
6 Vbe=0.7 // V
7 Rl=100 // ohm
8 Rs=130 // ohm
9 Vin=22 // V
10
11 Vout=Vz+Vbe
12 Il=Vout/Rl
13 Is=(Vin-Vout)/Rs
14 Ic=Is-Il
15
16 printf("regulated output voltage = %.3f V \n",Vout)
```

```
17 printf("load current = %.3f mA \n", I1*1000)
18 printf("current through Rs = %.3f mA \n", Is*1000)
19 printf("collector current = %.3f mA \n", Ic*1000)
```

Chapter 21

Solid state switching circuits

Scilab code Exa 21.1 voltage required to saturate transistor

```
1 //chapter21
2 //example21.1
3 //page456
4
5 Vcc=10 // V
6 Vbe=0.7 // V
7 Rb=47d3 // ohm
8 Rc=1d3 // ohm
9 gain=100
10
11 Ic_sat=Vcc/Rc
12 Ib=Ic_sat/gain
13 V_plus=Ib*Rb+Vbe
14
15 printf("voltage required to saturate transistor = +%
.3f V \n",V_plus)
```

Scilab code Exa 21.2 square wave

```

1 //chapter21
2 //example21.2
3 //page463
4
5 R=10d3 // ohm
6 C=0.01d-6 // F
7
8 T=1.4*R*C
9 f=1/T
10
11 printf("time period of square wave = %.3f ms \n",T
    *1000)
12 printf("frequency of square wave = %.3f kHz \n",f
    /1000)
13
14 // the accurate answer for frequency is 7.143 kHz
    but in book it is given 7 kHz

```

Scilab code Exa 21.3 differentiating circuit

```

1 // chapter 21
2 // example 21.3
3 // page 468
4
5 printf("In RC differentiating circuit , the output
    votage is taken across \nR and waveform of output
    depends on time constant of \ncircuit. For
    proper functioning , product RC should be many \
    ntimes smaller than time period of input wave. \n
    ")

```

Scilab code Exa 21.4 output voltage

```

1 //chapter21
2 //example21.4
3 //page468
4
5 R=10d3 // ohm
6 C=2.2d-6 // F
7 V1=0 // V
8 V2=10 // V
9 t1=0 // sec
10 t2=0.4 // sec
11
12 Eo=R*C*(V2-V1)/(t2-t1)
13
14 printf("output voltage = %.3f V \n",Eo)

```

Scilab code Exa 21.5 plotting input and output waveforms

```

1 //chapter21
2 //example21.5
3 //page472
4
5 Vin_peak=12 // V
6
7 // for positive half cycle diode conducts so
8 Vout_peak=Vin_peak-0.7 // V
9
10 // for negative half cycle diode does not conduct so
11 Vout_min=0 // V
12
13 printf("peak output voltage = %.3f V in positive
           half cycle and \n                               %.3f V in
           negative half cycle",Vout_peak,Vout_min)
14
15 // plotting input and output waveforms in same graph
   using following code instead of using xcos

```

```

16 clf()
17 t=linspace(0,2*pi,100)
18 Vin=12*sin(t)
19 Vout=Vout_peak*sin(t)+Vout_min
20 plot2d(t,Vin,style=2,rect=[0,0,10,20])
21 xtitle("input - blue      output - green","t","volts")
22 plot2d(t,Vout,style=3,rect=[0,0,10,20])

```

Scilab code Exa 21.6 plotting input and output waveforms

```

1 //chapter21
2 //example21.6
3 //page472
4
5 Rl=4 // kilo ohm
6 R=1 // kilo ohm
7 Vin_peak=10 // V
8
9 Vout_peak=Vin_peak*Rl/(Rl+R)
10 Vout_min=0 // because of diode
11 printf("peak output voltage = %.3f V \n",Vout_peak)
12
13 // plotting input and output waveforms in same graph
14 // using following code instead of using xcos
14 clf()
15 t=linspace(0,2*pi,100)
16 Vin=Vin_peak*sin(t)
17 Vout=Vout_peak*sin(t)+Vout_min
18 plot2d(t,Vin,style=2,rect=[0,0,10,20])
19 xtitle("input - blue      output - green","t","volts")
20 plot2d(t,Vout,style=3,rect=[0,0,10,20])

```

Scilab code Exa 21.7 plotting input and output waveforms

```
1 //chapter21
2 //example21.7
3 //page473
4
5 V=-10 // V
6 Vout=-0.7 // V
7
8 Vr=V-Vout
9
10 printf("output voltage = %.3f V \n",Vout)
11 printf("voltage across R = %.3f V \n",Vr)
12
13 // plotting input and output waveforms in same graph
   using following code instead of using xcos
14 clf()
15 t=linspace(0,%pi,100)
16 Vin=V*sin(t)
17 Vout=Vr*sin(t)
18 subplot(1,2,2)
19 plot2d(t,Vout,style=3,rect=[0,-0.7,10,11])
20 xtitle("Vout","t","volts")
21
22 subplot(1,2,1)
23 plot2d(t,Vin,style=2,rect=[0,-11,10,1])
24 xtitle("Vin","t","volts")
```

Scilab code Exa 21.8 plotting input and output waveforms

```
1 //chapter21
2 //example21.8
```

```

3 // page473
4
5 Rl=1d3 // ohm
6 R=200 // ohm
7
8 // for positive half cycle , diode is forward biased
   and since load is in parallel with diode we get
9 V_out_p=0.7 // V
10
11 // for negative half cycle , diode is reverse biased
    so it is open. Hence
12 V_in=-10 // V
13 V_out_n=V_in*Rl/(Rl+R)
14
15 printf("output voltage for positive cycle = %.3f V \
      and for negative cycle = %.3f V",V_out_p,V_out_n)
16
17 // plotting input and output waveforms in same graph
   using following code instead of using xcos
18 clf()
19 t=linspace(0,%pi,100)
20 Vin=V_in*sin(t)
21 Vout=-V_out_n*sin(t)
22 subplot(2,2,1)
23 plot2d(t,-Vin,style=3,rect=[0,0,10,11])
24 xtitle("Vin +ve","t","volts")
25 subplot(2,2,2)
26 plot2d(t,Vout,style=2,rect=[0,-5,10,0.7])
27 xtitle("Vout","t","volts")
28 t=linspace(%pi,2*pi,100)
29 Vin=V_in*sin(t)
30 subplot(2,2,3)
31 plot2d(t,-Vin,style=3,rect=[0,-11,10,0])
32 xtitle("Vin -ve","t","volts")
33 subplot(2,2,4)
34 plot2d(t,-Vout,style=2,rect=[0,-11,10,0])
35 xtitle("Vout","t","volts")

```

Scilab code Exa 21.9 empty

```
1 //chapter21
2 //example21.9
3 //page474
4
5 printf("The purpose of using series resistance R is
       : \n 1) if R is not present , diode will short
       voltage source in positive half cycle \n 2) so
       large current will flow which may damage voltage
       source or diode. \n To prevent this i.e. to
       protect diode and voltage source , R is used .")
```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 21.10 plot input and output waveforms

```
1 // chapter 21
2 // example 21.10
3 // page 478
4
5 V=2 // V
6 Vin=5 // V
7
8 // during positive half cycle
9 Vc_p=Vin-V // since Vin-Vc-V=0
10 // thus capacitor charges to Vc_p
11
12 // during negative half cycle
13 Vout=-Vin-Vc_p // since Vin-Vc_p-Vout=0
```

```

14
15 // we plot input and output waveforms using the
   following code instead of using xcos
16
17 clf()
18 t=0:0.1:5*pi
19 plot(t,5*squarewave(t,50))
20 plot2d(t,-Vc_p+(-Vout+V)*squarewave(t,50)/2,style=3)
21 xtitle("input - blue           output -"
         "green", "t", "volts")

```

Scilab code Exa 21.11 plot input and output waveforms

```

1 // chapter 21
2 // example 21.11
3 // page 479
4
5 V=-2 // V
6 Vin=5 // V
7
8 // during positive half cycle
9 Vc_p=Vin-V // since Vin-Vc-V=0
10 // thus capacitor charges to Vc_p
11
12 // during negative half cycle
13 Vout=-Vin-Vc_p // since Vin-Vc_p-Vout=0
14
15 // we plot input and output waveforms using the
   following code instead of using xcos
16
17 clf()
18 t=0:0.1:5*pi
19 plot(t,5*squarewave(t,50))
20 plot2d(t,-Vc_p+(-Vout+V)*squarewave(t,50)/2,style=3)
21 xtitle("input - blue           output -"
         "green", "t", "volts")

```

green," t," volts")

Chapter 22

Field Effect Transistors

Scilab code Exa 22.1 Id

```
1 // chpater22
2 //example22.1
3 //page491
4
5 I_DSS=12 // mA
6 V_GS_off=-5 // V
7
8 printf("I_D=%d*(1+V_GS/%d)^2 mA \n", I_DSS, -V_GS_off)
```

Scilab code Exa 22.2 drain current

```
1 //chapter22
2 //example22.2
3 //page491
4
5 I_DSS=32 // mA
6 V_GS=-4.5 // V
7 V_GS_off=-8 // V
```

```

8
9 I_D=I_DSS*(1-V_GS/V_GS_off)^2
10
11 printf("drain current = %.3f mA \n", I_D)

```

Scilab code Exa 22.3 pinch off voltage

```

1 //chapter22
2 //example22.3
3 //page491
4
5 I_D=5 // mA
6 I_DSS=10 // mA
7 V_GS_off=-6 // V
8
9 // we know that I_D=I_DSS*(1-V_GS/V_GS_off)^2 so
   making V_GS as subject we get
10
11 V_GS=V_GS_off*(1-(I_D/I_DSS)^0.5)
12 V_P=-V_GS_off
13
14 printf("gate source voltage = %.3f V \n", V_GS)
15 printf("pinch off voltage = %.3f V \n", V_P)

```

Scilab code Exa 22.4 gate source resistance

```

1 //chapter22
2 //example22.4
3 //page493
4
5 V_GS=15 // V
6 I_G=1d-9 // A
7

```

```
8 R_GS=V_GS/I_G
9
10 printf("gate source resistance = %.3f ohm or %.3f
      mega ohm \n",R_GS,R_GS/1d6)
```

Scilab code Exa 22.5 transconductance

```
1 //chapter22
2 //example22.5
3 //page493
4
5 Vgs1=-3.1 // V
6 Vgs2=-3 // V
7 Id1=1d-3 // A
8 Id2=1.3d-3 // A
9
10 g_fs=(Id2-Id1)/(Vgs2-Vgs1)
11
12 printf("transconductance = %.3f mho or %.3f micro
      mho \n",g_fs,g_fs*1d6)
```

Scilab code Exa 22.6 amplification factor

```
1 //chapter22
2 //example22.6
3 //page493
4
5 // for V_GS = 0V constant
6 V_DS1=7 // V
7 V_DS2=15 // V
8 I_D1=10 // mA
9 I_D2=10.25 // mA
10
```

```

11 rd=(V_DS2-V_DS1)/(I_D2-I_D1)
12
13 // for V_DS = 15V constant
14 V_GS1=0
15 V_GS2=0.2
16 I_D1=9.65
17 I_D2=10.25
18
19 g_fs=(I_D2-I_D1)/(V_GS2-V_GS1)
20
21 mu=rd*g_fs
22
23 printf("ac drain resistance = %.3f ohm or %.3f kilo
          ohm \n",rd/1000,rd)
24 printf("transconductance = %.3f mho or %.3f micro
          mho \n",g_fs,g_fs*1000)
25 printf("amplification factor = %.3f \n",mu)

```

Scilab code Exa 22.7 Kirchoff's law

```

1 //chapter22
2 //example22.7
3 //page496
4
5 I_DSS=5d-3 // A
6 V_DD=20 // V
7 V_DS=10 // V
8 V_P=-2 // V
9 V_G=0 // V
10 I_D=1.5d-3 // A
11
12 V_GS=V_P*(1-((I_D/I_DSS)^0.5)) // I_D=I_DSS*(1-V_GS/
          V_P)^2
13 V_S=V_G-V_GS
14 R_S=V_S/I_D

```

```

15
16 // by Kirchoff's law we get V_DD=I_D*R_D+V_DS+I_D*
17 R_S so making R_D as subject we get
18 R_D=(V_DD-V_DS-I_D*R_S)/I_D
19 printf("Rs = %.3f kilo ohm and Rd = %.3f kilo ohm \n"
    ,R_S/1000,R_D/1000)

```

Scilab code Exa 22.8 required value of Rs

```

1 //chapter22
2 //example22.8
3 //page496
4
5 V_P=-5 // V
6 V_DD=30 // V
7 I_DSS=10 // mA
8 I_D=2.5 // mA
9 R1=1000 // kilo ohm
10 R2=500 // kilo ohm
11
12 // since I_D=I_DSS*(1-(V_GS/V_P))^2, making V_GS as
13 // subject we get
14 V_GS=V_P*(1-(I_D/I_DSS)^0.5)
15
16 V2=V_DD*R2/(R1+R2)
17
18 // since V2 = V_GS + I_D*Rs, making Rs as subject we
19 // get
20 Rs=(V2-V_GS)/I_D
21
22 printf("required value of Rs = %.3f kilo ohm \n",Rs)

```

Scilab code Exa 22.9 voltage amplification of the circuit

```
1 //chapter22
2 //example22.9
3 //page497
4
5 R_L=10d3 // ohm
6 g_fs=3000d-6 // mho
7
8 // since rd >> R_L, we can write
9
10 Av=g_fs*R_L
11
12 printf("voltage amplification of the circuit = %.3f
    \n",Av)
```

Scilab code Exa 22.10 Vds

```
1 //chapter22
2 //example22.10
3 //page498
4
5 V_DD=30 // V
6 I_D=2.5d-3 // A
7 R_D=5d3 // ohm
8 R_S=200 // ohm
9
10 V_DS=V_DD-I_D*(R_D+R_S)
11 V_GS=-I_D*R_S
12
13 printf("V_DS = %.3f V \n",V_DS)
14 printf("V_GS = %.3f V \n",V_GS)
```

Scilab code Exa 22.11 dc voltage of drain

```
1 //chapter22
2 //example22.11
3 //page498
4
5 V_DD=30 // V
6 I_D1=2.15d-3 // A
7 I_D2=9.15d-3 // A
8 R_D1=8.2d3 // ohm
9 R_D2=2d3 // ohm
10 R_S1=680 // ohm
11 R_S2=220 // ohm
12
13 V_RD1=I_D1*R_D1
14 V_D1=V_DD-V_RD1
15 V_S1=I_D1*R_S1
16
17 V_RD2=I_D2*R_D2
18 V_D2=V_DD-V_RD2
19 V_S2=I_D2*R_S2
20
21 printf("For stage 1 : dc voltage of drain = %.3f V
        and source = %.3f V \n",V_D1,V_S1)
22 printf("For stage 2 : dc voltage of drain = %.3f V
        and source = %.3f V \n",V_D2,V_S2)
```

Chapter 23

Silicon controlled rectifiers

Scilab code Exa 23.1 Breakover voltage

```
1 //chapter23
2 //example23.1
3 //page509
4
5 printf("1) Breakover voltage of 400V : It means that
       if gate is open and the \n")
6 printf("   supply voltage is 400V, then SCR will
       start conducting heavily. \n")
7 printf("   However, as long as the supply voltage <
       400V, SCR stays open. \n \n")
8
9 printf("2) Trigger current of 10mA : It means that
       if the supply voltage is \n")
10 printf("   less than breakover voltage and a minimum
        gate current of 10 mA \n")
11 printf("   is passed , SCR conducts. It wont conduct
        if gate current is less \n")
12 printf("   than 10mA. \n \n")
13
14 printf("3) Holding current of 10mA : When SCR is
        conducting , it will not open \n")
```

```
15 printf(" even if triggering current is removed.  
        However, if supply voltage \n")  
16 printf(" is reduced, anode current also decreases.  
        When anode current drops \n")  
17 printf(" to 10mA, the holding current , SCR turns  
        off. \n \n")  
18  
19 printf(" 4) If gate current is increased to 15mA, the  
        SCR will be turned on \n")  
20 printf(" lower supply voltage. \n")
```

Scilab code Exa 23.2 rating

```
1 //chapter23  
2 //example23.2  
3 //page510  
4  
5 t=12d-3 // sec  
6 I=50 // A  
7 fuse_rating=I^2*t  
8  
9 if fuse_rating < 90  
10     printf(" rating = %.3f ampere square second  
              which is less than maximum \nrating so  
              device will not be destroyed \n",fuse_rating  
          )  
11 else printf(" rating = %.3f ampere square second  
              which is more than maximum \nrating so device may  
              get damaged \n",fuse_rating)  
12  
13 end
```

Scilab code Exa 23.3 maximum allowable duration of surge

```

1 //chapter23
2 //example23.3
3 //page510
4
5 rating=50 // ampere square second
6 Is=100 // A
7
8 t_max=rating/Is^2
9
10 printf("maximum allowable duration of surge = %.3f s
         or %.3f ms\n",t_max,t_max*1000)

```

Scilab code Exa 23.4 average current

```

1 //chapter23
2 //example23.4
3 //page514
4
5 v=100 // V
6 Vm=200 // V
7 R_L=100 // ohm
8
9 // since v=Vm*sin(theta), we get
10
11 theta=asin(v/Vm)*180/%pi // in terms of degrees
12
13 phi=180-theta
14
15 V_avg=Vm*(1+cos(theta*%pi/180))/(2*%pi)
16
17 I_avg=V_avg/R_L
18
19 printf("firing angle = %.2f degrees \n",theta)
20 printf("conduction angle = %.2f degrees \n",phi)
21 printf("average current = %.4f A \n",I_avg)

```

```
22
23 // the accurate answer for average current is 0.594
   A but in book it is given as 0.5925 A
```

Scilab code Exa 23.5 power output

```
1 //chapter23
2 //example23.5
3 //page515
4
5 Vm=400 // V
6 v=150 // V
7 R_L=200 // ohm
8
9 // since v=Vm*sin(theta), we get
10
11 theta=asin(v/Vm)*180/%pi // in terms of degrees
12
13 V_av=Vm*(1+cos(theta*%pi/180))/(2*%pi)
14 I_av=V_av/R_L
15 P=V_av*I_av
16
17 printf("firing angle = %.2f degrees \n",theta)
18 printf("average output voltage = %.3f V \n",V_av)
19 printf("average current for load of 200 ohm = %.3f A
          \n",I_av)
20 printf("power output = %.3f W \n",P)
21
22 // the accurate answer for power output is 75.250 W
   but in book it is given as 75.15 W
```

Scilab code Exa 23.6 forward breakdown voltage

```

1 //chapter23
2 //example23.6
3 //page515
4
5 Vm=240 // V
6 v=180 // V
7
8 // figure given is for understanding purpose only.
   It is not required to solve the example
9
10 // SCR remains off till it reaches 180 V i.e.
    forward breakdown voltage
11
12 // since v=Vm*sin(theta), we get
13
14 theta=asin(v/Vm) // firing angle in terms of degrees
15
16 // since theta=314*t, we get
17
18 t=theta/314 // seconds
19
20 printf("off duration of SCR = %.3f ms \n",t*1000) //
   multiply t by 1000 to display time in
   milliseconds

```

Scilab code Exa 23.7 voltage

```

1 //chapter23
2 //example23.7
3 //page517
4
5 alpha=60 // degrees
6 Vm=200 // V
7 R_L=100 // ohm
8

```

```
9 V_av=Vm*(1+cos(alpha*pi/180))/pi
10
11 I_av=V_av/R_L
12
13 printf("dc output voltage = %.3f V \n",V_av)
14 printf("load current for firing angle of 60 degrees
           = %.3f A \n",I_av)
```

Chapter 24

Power electronics

Scilab code Exa 24.1 $(RB1+RB2) = RB1/Rbb$

```
1 // chapter24
2 // example24.1
3 // page533
4
5 RBB=10 // kilo ohm
6 eta=0.6
7
8 // eta=RB1/(RB1+RB2) = RB1/Rbb so
9 RB1=eta*RBB
10 RB2=RBB-RB1
11 printf("RB1 = %.3f kilo ohm \n",RB1)
12 printf("RB2 = %.3f kilo ohm",RB2)
```

Scilab code Exa 24.2 voltage

```
1 // chapter24
2 // example24.2
3 // page533
```

```
4
5 VBB=10 // V
6 eta=0.65
7 VD=0.7 // V
8
9 stand_off_voltage=eta*VBB
10 peak_point_voltage=VD+eta*VBB
11
12 printf("stand off voltage = %.3f V \n",
13     stand_off_voltage)
14 printf("peak point voltage = %.3f V \n",
15     peak_point_voltage)
```

Chapter 25

Electronic instruments

Scilab code Exa 25.1 sensitivity

```
1 //chapter25
2 //example25.1
3 //page543
4
5 Ig=1d-3 // A
6
7 S=1/Ig
8
9 printf("sensitivity = %.3f ohm per volt \n",S)
```

Scilab code Exa 25.2 equivalent resistance of meter

```
1 //chapter25
2 //example25.2
3 //page543
4
5 S=1000 // ohm per volt
6 V=50 // V
```

```

7 R=50d3 // ohm
8
9 R_meter=S*V
10
11 R_equi=R*R_meter/(R+R_meter) //equivalent resistance
      of meter and given resistance across which meter
      is connected
12
13 printf("ratio of circuit resistance before and after
      connecting multimeter = %.3f \n",R/R_equi)
14 printf("Thus equivalent resistance is reduced to
      half. So current drawn is double \n")
15 printf("Thus multimeter will give highly incorrect
      reading \n \n")
16 printf("As a rule, multimeter resistance should be
      100 times the resistance across \nwhich voltage
      is to be measured \n")

```

Scilab code Exa 25.3 voltage read by multimeter

```

1 //chapter25
2 //example25.3
3 //page544
4
5 S=4 // kilo ohm per volt
6 V_range=10 // V
7 V=20 // V
8 R=10 // kilo ohm
9
10 R_meter=S*V_range
11 R_equi=R+R*R_meter/(R+R_meter)
12 I=V/R_equi
13 V_reading=I*R*R_meter/(R+R_meter)
14
15 printf("voltage read by multimeter = %.3f V \n",

```

V_reading)

Scilab code Exa 25.4 voltage read by multimeter

```
1 //chapter25
2 //example25.4
3 //page544
4
5 S=20 // kilo ohm per volt
6 V_range=10 // V
7 V=20 // V
8 R=10 // kilo ohm
9
10 R_meter=S*V_range
11 R_equi=R+R*R_meter/(R+R_meter)
12 I=V/R_equi
13 V_reading=I*R*R_meter/(R+R_meter)
14
15 printf("voltage read by multimeter = %.3f V \n",
   V_reading)
16
17 // answer in book is 9.88V but accurate answer is
   9.756V
```

Scilab code Exa 25.5 resistance of voltmeter

```
1 //chapter25
2 //example25.5
3 //page545
4
5 R1=20d3 // ohm
6 R2=20d3 // ohm
7 R3=30d3 // ohm
```

```

8 R4=30d3 // ohm
9 V=100 // V
10 Rm=60d3 // ohm
11
12 // case 1 : meter is not connected
13 R=R1+R2+R3+R4
14 I=V/R
15 V_A=V
16 V_B=V-I*R2
17 V_C=V-I*(R1+R2)
18 V_D=V-I*(R1+R2+R3)
19
20 // case2 : meter is connected
21 // At A
22 V_A1=V
23
24 // At B
25 R_total_B=R1+(Rm*(R2+R3+R4)/(Rm+R2+R3+R4))
26 I1=V/R_total_B
27 V_B1=I1*(Rm*(R2+R3+R4)/(Rm+R2+R3+R4))
28
29 // At C
30 R_total_C=R1+R2+(Rm*(R3+R4)/(Rm+R3+R4))
31 I2=V/R_total_C
32 V_C1=V*(Rm*(R3+R4)/(Rm+R3+R4))/R_total_C
33
34 // At D
35 R_total_D=R1+R2+R3+(Rm*R4/(Rm+R4))
36 I2=V/R_total_D
37 V_D1=V*(Rm*R4/(Rm+R4))/R_total_D
38
39 printf("CASE 1 : meter is not connected \n
          Voltage at A = %.3f V \n      Volatge at B = %.3f
          V \n      Volatge at C = %.3f V \n      Volatge at
          D = %.3f V \n",V_A,V_B,V_C,V_D)
40 printf("CASE 2 : meter is connected \n      At A
          then voltage at A = %.3f V",V_A1)
41 printf("\n      At B then voltage at B = %.3f V",

```

```
V_B1)
42 printf("\n      At C then voltage at C = %.3f V" ,
        V_C1)
43 printf("\n      At D then voltage at D = %.3f V \n \
        n",V_D1)
44
45 printf("resistance of voltmeter should be 100 times
the resistance across \nwhich voltage is to be
measured. Since this condition is not \nsatisfied
here , readings are wrong. \n")
```

Scilab code Exa 25.6 spot shift

```
1 //chapter25
2 //example25.6
3 //page552
4
5 S=0.01 //mm per volt
6 V=400 // V
7
8 spot_shift=S*V
9
10 printf("spot shift = %.3f mm \n",spot_shift)
```

Scilab code Exa 25.7 applied voltage

```
1 //chapter25
2 //example25.7
3 //page552
4
5 S=0.03 // mm per volt
6 spot_shift=3 // mm
7
```

```
8 V=spot_shift/S // since spot shift = deflection  
    sensitivity * applied voltage  
9  
10 printf(" applied voltage = %.3f V \n",V)
```

Scilab code Exa 25.8 unknown voltage

```
1 //chapter25  
2 //example25.8  
3 //page555  
4  
5 V1=200 // V  
6 d1=2 // cm  
7 d2=3 // cm  
8  
9 // since sensitivity = voltage / deflcetion we get  
10 S=V1/d1  
11 V2=S*d2  
12  
13 printf("unknown voltage = %.3f V",V2)
```

Scilab code Exa 25.9 ratio of fv to fh

```
1 //chapter25  
2 //example25.9  
3 //page556  
4  
5 fh=1000 // Hz  
6  
7 // case (i) :- ratio of fv to fh = 1:1  
8 fv1=1*fh  
9  
10 // case (ii) :- ratio = 2:1
```

```
11 fv2=2*fh
12
13 // case (iii) :- ratio = 6:1
14 fv3=6*fh
15
16 printf("for case1 i.e. fv/fh = 1/1, fv = %.3f Hz \n"
17     ,fv1)
17 printf("for case2 i.e. fv/fh = 2/1, fv = %.3f Hz \n"
18     ,fv2)
18 printf("for case3 i.e. fv/fh = 6/1, fv = %.3f Hz \n"
19     ,fv3)
```

Chapter 26

Integrated circuits

Scilab code Exa 26.1 regulated dc output voltage

```
1 //chapter26
2 //example26.1
3 //page570
4
5 R2=2.4d3 // ohm
6 R1=240 // ohm
7
8 V_out=1.25*(1+R2/R1)
9
10 printf("regulated dc output voltage = %.3f V \n",
V_out)
```

Chapter 27

Hybrid parameters

Scilab code Exa 27.1 ratio

```
1 //chapter27
2 //example27.1
3 //page574
4
5 R1=10 // ohm
6 R2=5 // ohm
7
8 // for h11 and h21, imagine that output terminals
   are shorted hence it is clear that input
   impedance is equal to R1.
9    // this is h11 by definition so
10   h11=R1
11
12  // now current will flow of same magnitude but
   in opposite directions through input and
   output terminals so output_current/
   input_current = -1
13  // but this ratio is h21 by definition. Thus
14  h21=-1
15
16 // for h12 and h22 imagine a voltage source on
```

```

    output terminals
17     // this voltage will be available on input
        terminals also since current through 10 ohm
        resistor = 0,
18     // hence input_voltage/output_voltage = 1
19     // but this ratio is h12 by definition. Thus
20     h12=1
21
22     // here output impedance looking into output
        terminals with input terminals open is 5 ohm.
23     // its reciprocal is h22 by definition. Thus
24     h22=1/5
25
26 printf("h11 = %.3 f ohm \n",h11)
27 printf("h21 = %.3 f \n",h21)
28 printf("h12 = %.3 f \n",h12)
29 printf("h22 = %.3 f ohm \n",h22)

```

Scilab code Exa 27.2 impedance

```

1 //chapter27
2 //example27.2
3 //page575
4
5 R1=4 // ohm
6 R2=4 // ohm
7 R3=4 // ohm
8
9 // for h11 and h21, imagine that output terminals
    are shorted hence it is clear that input
    impedance is equal to  $R1+R2*R3/(R2+R3)$ 
10    // this is h11 by definition so
11    h11=R1+R2*R3/(R2+R3)
12
13    // now current will divide equally at junction

```

```

          of 4 ohm resistors so output_current/
          input_current = -0.5
14      // but this ratio is h21 by definition. Thus
15      h21=-0.5
16
17 // for h12 and h22 imagine a voltage source on
   output terminals
18      // this voltage will be divided by a factor 2
19      // hence input_voltage/output_voltage = 0.5
20      // but this ratio is h12 by definition. Thus
21      h12=0.5
22
23      // here output impedance looking into output
         terminals with input terminals open is 8 ohm.
24      // its reciprocal is h22 by definition. Thus
25      h22=1/8
26
27 printf("h11 = %.3f ohm \n",h11)
28 printf("h21 = %.3f \n",h21)
29 printf("h12 = %.3f \n",h12)
30 printf("h22 = %.3f ohm \n",h22)

```

Scilab code Exa 27.3 voltage gain of circuit

```

1 //chapter27
2 //example27.3
3 //page578
4
5 h11=10
6 h12=1
7 h21=-1
8 h22=0.2
9 rL=5 // ohm
10
11 Zin=h11-(h12*h21/(h22+1/rL))

```

```

12 Av=-h21/(Zin*(h22+1/rL))
13
14 printf("input impedance = %.3f ohm \n",Zin)
15 printf("voltage gain of circuit = %.3f \n",Av)

```

Scilab code Exa 27.4 approximate current gain

```

1 //chapter27
2 //example27.4
3 //page581
4
5 hie=2000 // ohm
6 hoe=1d-4 // mho
7 hre=1d-3
8 hfe=50
9 rL=600 // ohm
10
11 Zin=hie-hre*hfe/(hoe+1/rL)
12 // here second term can be neglected compared to hie
   so
13 Zin_approx=hie
14
15 Ai=hfe/(1+hoe*rL)
16 // if hoe*rL << 1 then
17 Ai_approx=hfe
18
19 Av=-hfe/(Zin*(hoe+1/rL))
20 // negative sign indicates phase shift between input
   and output
21
22 printf("input impedance = %.3f ohm \n",Zin)
23 printf("current gain = %.3f \n",Ai)
24 printf("voltage gain = %.3f. Here negative sign
   indicates phase shift between input and output.\n
   \n",Av)

```

```
25
26 printf(" approximate input impedance = %.3f ohm \n" ,
27      Zin_approx)
27 printf(" approximate current gain = %.3f \n" ,
28      Ai_approx)
```

Scilab code Exa 27.5 input impedance

```
1 //chapter27
2 //example27.5
3 //page582
4
5 hie=1700 // ohm
6 hre=1.3d-4
7 hoe=6d-6 // mho
8 hfe=38
9 rL=2000 // ohm
10
11 Zin=hie-hre*hfe/(hoe+1/rL)
12
13 Ai=hfe/(1+hoe*rL)
14
15 Av=-hfe/(Zin*(hoe+1/rL))
16
17 printf("input impedance = %.3f ohm \n",Zin)
18 printf("current gain = %.3f \n",Ai)
19 printf("voltage gain = %.3f \n",-Av) // considering
   magnitude of Av,we neglect its negative sign and
   so we display -Av instead of Av
```

Scilab code Exa 27.6 voltage gain

```
1 //chapter27
```

```

2 //example27.6
3 //page582
4
5 hie=1500 // ohm
6 hre=4d-4
7 hoe=5d-5 // mho
8 hfe=50
9 Rc=10d3 // ohm
10 R_L=30d3 // ohm
11 R1=80d3 // ohm
12 R2=40d3 // ohm
13
14 rL=Rc*R_L/(Rc+R_L)
15 Zin=hie-hre*hfe/(hoe+1/rL)
16 Zin_stage=Zin*(R1*R2/(R1+R2))/(Zin+(R1*R2/(R1+R2)))
17
18 Av=-hfe/(Zin*(hoe+1/rL))
19
20 printf("input impedance = %.3f ohm \n",Zin_stage)
21 printf("voltage gain = %.3f \n",Av)
22
23 // the accurate answers are input impedance =
    1321.957 ohm and voltage gain = -196.078 but in
    book they are given as 1320 ohm and -196
    respectively

```

Scilab code Exa 27.7 micro mho

```

1 //chapter27
2 //example27.7
3 //page584
4
5 Vbe=10d-3 // V
6 Vbe2=0.65d-3 // V
7 Vce=1 // V

```

```
8 Ib=10d-6 // A
9 Ic=1d-3 // A
10 Ic2=60d-6 // A
11
12 hie=Vbe/Ib // in ohm
13 hfe=Ic/Ib // in ohm
14 hre=Vbe2/Vce
15 hoe=Ic2/Vce // in mho
16
17 printf("hie = %.3f ohm \n",hie)
18 printf("hfe = %.3f ohm \n",hfe)
19 printf("hre = %.5f \n",hre)
20 printf("hoe = %.3f micro mho \n",hoe*1d6)
```

Chapter 28

Digital electronics

Scilab code Exa 28.1 binary equivalent of decimal number 37

```
1 //chapter28
2 //example28.1
3 //page590
4
5 a= dec2bin (37)
6 disp(a, 'binary equivalent of decimal number 37 = ')
```

Scilab code Exa 28.2 binary equivalent of decimal number 23

```
1 //chapter28
2 //example28.2
3 //page590
4
5 a= dec2bin (23)
6 disp(a, 'binary equivalent of decimal number 23 = ')
```

Scilab code Exa 28.3 equivalent decimal of binary 110001

```
1 //chapter28
2 //example28.3
3 //page591
4
5 a= bin2dec ( ' 110001 ' )
6 printf("equivalent decimal of binary 110001 is %d \n"
    ,a)
```

Scilab code Exa 28.4 page598

```
1 //chapter28
2 //example28.4
3 //page598
4
5 disp(" A      B      Y_dash = A + B      Y = Y_dash.A
      ")
6 disp(" 0      0      0      0      ")
7 disp(" 1      0      1      1      ")
8 disp(" 0      1      1      0      ")
9 disp(" 1      1      1      1      ")
10
11 printf("\nexplanation: \n")
12 printf("A=0 and B=0 give A'=1 and B'=1 so Y_dash = A
      + B is 0 and Y = Y_dash.A is 0 \n")
13
14 printf("A=1 and B=0 give A'=0 and B'=1 so Y_dash = A
      + B is 1 and Y = Y_dash.A is 1 \n")
15
16 printf("A=0 and B=1 give A'=1 and B'=0 so Y_dash = A
      + B is 1 and Y = Y_dash.A is 0 \n")
17
18 printf("A=1 and B=1 give A'=0 and B'=0 so Y_dash = A
      + B is 1 and Y = Y_dash.A is 1 \n")
```

Scilab code Exa 28.5 page598

```
1 //chapter28
2 //example28.5
3 //page598
4
5 disp(" A      B      A'      Y_dash = A'. B      B'
       Y = Y_dash + B' ")
6 disp(" 0      0      1      0
           1 ")
7 disp(" 1      0      0      0
           1 ")
8 disp(" 0      1      1      1
           1 ")
9 disp(" 1      1      0      0
           0 ")
10
11 printf("\nexplanation: \n")
12 printf("A=0 and B=0 give A'=1 and B'=1 so Y_dash = A
           '.B is 0 and Y = Y_dash + B' is 1 \n")
13
14 printf("A=1 and B=0 give A'=0 and B'=1 so Y_dash = A
           '.B is 0 and Y = Y_dash + B' is 1 \n")
15
16 printf("A=0 and B=1 give A'=1 and B'=0 so Y_dash = A
           '.B is 1 and Y = Y_dash + B' is 1 \n")
17
18 printf("A=1 and B=1 give A'=0 and B'=0 so Y_dash = A
           '.B is 0 and Y = Y_dash + B' is 0 \n")
```

Scilab code Exa 28.6 factorize

```

1 // chapter28
2 // example28.6
3 //page606
4
5 printf("Y = A . B . C' . D' + A' . B . C' . D' + A'
       . B . C . D' + A . B . C . D' \n")
6 printf("taking out the common factors \n")
7 printf("Y = B . C' . D' . ( A + A' ) + B . C . D' .
       ( A + A' ) \n")
8 printf("By theorem 3 \n")
9 printf("Y = B . C' . D' + B . C . D' \n")
10 printf("again factorize \n")
11 printf("Y = B . D' ( C + C' ) \n")
12 printf("By theorem 3 \n")
13 printf("Y = B . D' . 1 \n")
14 printf("thus \n")
15 printf("Y = B . D' \n")

```

Scilab code Exa 28.7 Apply cummulative law and theorem

```

1 // chapter28
2 // example28.7
3 //page606
4
5 printf("Y = A . B + A . ( B + C ) + B . ( B + C ) \n
       ")
6 printf("By thoerem 14 \n")
7 printf("Y = A . B + A . B + A . C + B . B + B .C \n"
       )
8 printf("By theorem 6 \n")
9 printf("Y= A . B + A . B + A . C + B + B .C \n")
10 printf("By theorem 5 \n")
11 printf("Y = A . B + A . C + B + B . C \n")
12 printf("Factor B out of last 2 terms \n")
13 printf("Y = A . B + A . C + B . ( 1 + C ) \n")

```

```

14 printf("Apply cummulative law and theorem 7 \n")
15 printf("Y = A . B + A . C + B . 1 \n")
16 printf("Apply theorem 2 \n")
17 printf("Y = A . B + A . C + B \n")
18 printf("Factor B out of first and third terms \n")
19 printf("Y = B . ( A + 1 ) + A . C \n")
20 printf("Apply theorem 7 \n")
21 printf("Y = B . 1 + A . C \n")
22 printf("Apply theorem 2 \n")
23 printf("Y = B + A . C \n")

```

Scilab code Exa 28.8 Based on theorem 16 & 3

```

1 //chapter28
2 //example28.8
3 //page607
4
5 printf(" i ) Y = A + A' . B \n")
6 printf(" By theorem 16 \n")
7 printf(" Y = A + A . B + A' . B \n")
8 printf(" = A + B ( A + A' ) \n")
9 printf(" By theorem 3 \n")
10 printf(" Y = A + B \n \n")
11
12 printf(" ii ) Y = A . B + A' . C + B . C \n")
13 printf(" = A . B + A' . C + B . C ( A + A' ) \n")
14 printf(" = A . B + A' . C + A . B . C + A' . B
15 printf(" . C \n")
16 printf(" = A . B ( 1 + C ) + A' . C( 1 + B ) \n")
17 printf(" = A . B + A' . C \n")

```

Scilab code Exa 28.9 Using De Morgan theorem

```
1 //chapter28
2 //example28.9
3 //page607
4
5 printf("Y = ( ( A + B ) ' . C . D' ) ' \n")
6 printf("Using De Morgan theorem \n")
7 printf("Y = ( A + B ) + C' + D \n")
8 printf("Y = A + B + C' + D \n")
```

Scilab code Exa 28.10 De Morgan theorem

```
1 //chapter28
2 //example28.10
3 //page607
4
5 printf(" 1) Y = A . B . C' + A . ( B . C ) ' \n")
6 printf("      Y' = ( A . B . C' + A . ( B . C ) ' ) ' \n")
7 printf("      By De Morgan theorem \n")
8 printf("      Y' = ( A . B . C') ' . ( A . ( B . C) ' ) ' \n")
9 printf("      By De Morgan theorem \n")
10 printf("     Y' = ( A' + B' + C ) . ( A' + B + C ) \n")
11 printf("     Y = A' . ( B . C' + B' . C ) \n")
12 printf("     Y' = ( A' . ( B . C' + B' . C ) ) ' \n")
13 printf("     By De Morgan theorem \n")
14 printf("     Y' = A + ( B . C' + B' . C ) ' \n")
15 printf("     By De Morgan theorem \n")
16 printf("     Y' = A + ( B . C') ' . ( B' . C ) ' \n")
17 printf("     By De Morgan theorem \n")
18 printf("     Y' = A + ( B' + C ) . ( B + C' ) \n")
19 printf("     Y' = A + ( B . C ) ' + ( B . C ) \n")
```

Scilab code Exa 28.11 De Morgan theorem

```
1 //chapter28
2 //example28.11
3 //page608
4
5 printf("1) Y = ( A + B + C ) . ( A + B ) \n")
6 printf("      Y = A . A + A . B + B . A + B . B + C . A
+ C . B \n")
7 printf("      Using A . A = A we get \n")
8 printf("      Y = A + A . B + A . B + B + A . C + B . C
\n")
9 printf("      Using A . B + A . B = A . B we get \n")
10 printf("      Y = A + A . B + B + A . C + B . C \n")
11 printf("      Using A + A . B = A we get \n")
12 printf("      Y = A + B + A . C + B . C \n")
13 printf("      = A . ( 1 + C ) + B . ( 1 + C ) \n")
14 printf("      Using 1 + C = 1 we get \n")
15 printf("      Y = A . 1 + B . 1 \n")
16 printf("      Y = A + B \n")
17
18 printf("2) Y = A . B + A . B . C + A . B . C' \n")
19 printf("      = A . B + A . B ( C + C' ) \n")
20 printf("      Since C + C' = 1 we get \n")
21 printf("      Y = A . B + A . B \n")
22 printf("      = A . B \n")
23
24
25 printf("3) Y = 1 + A . ( B . C' + B . C + B' . C' ) +
A . B' . C + A . C \n")
26 printf("      Using 1 + A = 1 and 1 + A . ( B . C' + B
. C + ( B . C )' ) = 1 we get \n")
27 printf("      Y = 1 + A . B' . C + A . C \n")
28 printf("      Y = 1 + A . C \n")
```

```

29 printf(" Y = 1 \n \n")
30
31 printf(" 4) Y = ( ( A + B' + C ) + ( B + C' ) )' \n")
32 printf(" By De Morgan theorem \n")
33 printf(" Y = ( A + B' + C )' . ( B + C' )' \n")
34 printf(" By De Morgan theorem \n")
35 printf(" Y = ( A' . B . C' ) . ( B' . C ) \n")
36 printf(" Since B . B' = 0 and C . C' = 0 we get \n
         ")
37 printf(" Y = 0 \n")

```

Scilab code Exa 28.12 theorem

```

1 //chapter28
2 //example28.12
3 //page609
4
5 printf(" Y = A . B' . D + A . B' . D' \n")
6 printf(" Factor out A . B' by theorem 14 \n")
7 printf(" Y = A . B' ( D + D' ) \n")
8 printf(" But by theorem 3 D + D' = 1 \n")
9 printf(" Y = A . B' . 1 \n")
10 printf(" By theorem 2 \n")
11 printf(" Y = A . B' \n")

```

Scilab code Exa 28.13 theorem

```

1 //chapter28
2 //example28.13
3 //page609
4
5 printf(" Y = ( A' + B ) . ( A + B ) \n")
6 printf(" By theorem 15 \n")

```

```
7 printf(" Y = A' . A + A' . B + B . A + B . B \n")
8 printf(" By theorem 4 and 6 \n")
9 printf(" Y = 0 + A' . B + B . A + B \n")
10 printf(" Y = A' . B + B . A + B \n")
11
12 printf(" By theorem 14 \n")
13 printf(" Y = B . ( A' + A + 1 ) \n")
14 printf(" By theorem 7 \n")
15 printf(" Y = B . ( A' + 1 ) \n")
16 printf(" By theorem 7 \n")
17 printf(" Y = B . 1 ) \n")
18 printf(" By theorem 2 \n")
19 printf(" Y = B \n")
```
