

Scilab Textbook Companion for
Introductory Electronic Devices and Circuits –
Conventional Flow Version
by R. T. Paynter¹

Created by
Nihal Bisen
B.Tech
Electronics Engineering
NIT Meghalaya
College Teacher
None
Cross-Checked by
None

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Introductory Electronic Devices and Circuits – Conventional Flow
Version

Author: R. T. Paynter

Publisher: Prentice Hall

Edition: 7

Year: 2005

ISBN: 978-0131716414

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
2 Diodes	5
3 Common Diode Applications Basic Power supply	12
4 Common Diode Applications clippers clampers Voltage multiplier and Display	24
6 Bipolar Junction Transistors	27
7 DC Biasing Circuits	30
8 Introduction to Amplifiers	39
9 Common Emitter Amplifiers	44
10 Other BJT Amplifiers	52
11 Power Amplifier	59
12 Field Effect Transistor	66
13 MOSFETs	76

14 Amplifier Frequency Responce	78
15 Operational Amplifiers	89
16 Additional Op Amp Applications	96
17 Tuned Amplifiers	99
18 Oscillators	106
19 Solid State Switching Circuits	107
20 Thyristors and Optoelectronics Devices	113
21 Discrete and Integrated voltage Regulators	116

List of Scilab Codes

Exa 2.1	current voltage	5
Exa 2.2	circuit current and voltage	5
Exa 2.3	voltmeter reading	6
Exa 2.4	total current	6
Exa 2.5	circuite current	7
Exa 2.6	Value of I_t	7
Exa 2.7	percentage of error by using ideal diode	7
Exa 2.9	average forward current	8
Exa 2.10	min forward power dissipation rating	8
Exa 2.11	forward power dissipation	9
Exa 2.12	voltage across diode	9
Exa 2.13	Current I_{zm}	10
Exa 2.14	derating factor and P_d rating	10
Exa 2.16	diode application	10
Exa 2.17	current limiting resistor	11
Exa 3.1	secondary current	12
Exa 3.2	peak load voltage	12
Exa 3.3	peak load voltage for the circuit	13
Exa 3.4	peak load current	13
Exa 3.5	average voltage	14
Exa 3.6	average current	15
Exa 3.7	dc load current	15
Exa 3.8	dc output voltage	15
Exa 3.9	dc load voltage	16
Exa 3.10	I_{lpk} and I_{ave}	16
Exa 3.11	dc load voltage and current	17
Exa 3.12	dc load voltage	17
Exa 3.13	averagen voltage	18

Exa 3.14	surge current	19
Exa 3.15	ripple output	19
Exa 3.16	average voltage	20
Exa 3.17	circuit current	20
Exa 3.18	load current	20
Exa 3.19	load current and zener current	21
Exa 3.20	minimum allowable value of RL	21
Exa 3.21	ripple at the load	22
Exa 3.22	dc voltage V_{rout} and I_L	22
Exa 4.1	peak load voltage	24
Exa 4.2	voltage at register	24
Exa 4.3	voltage at load	25
Exa 4.4	peak load voltage	25
Exa 4.5	capacitor charge and discharge	25
Exa 6.1	collector current	27
Exa 6.2	collector current emitter current	27
Exa 6.3	collector and base current	28
Exa 6.4	base and collector current	28
Exa 6.5	collector current	28
Exa 6.6	max base current	29
Exa 7.1	dc load line	30
Exa 7.2	dc load line	30
Exa 7.3	Q point values	32
Exa 7.4	midpoint biased	33
Exa 7.5	Q Point	34
Exa 7.6	effect of temprature	34
Exa 7.7	Q point vales	35
Exa 7.8	base current	35
Exa 7.9	Q point	36
Exa 7.10	I_{cq} and V_{ceq}	37
Exa 7.11	I_{csat} and V_{ceoff}	37
Exa 7.12	Q points	37
Exa 7.13	Q points	38
Exa 8.1	voltage gain	39
Exa 8.2	output voltage	39
Exa 8.3	input voltage	40
Exa 8.4	output voltage	40
Exa 8.5	load voltage	40

Exa 8.6	efficiency	41
Exa 8.7	gain in dB	41
Exa 8.8	power gain	41
Exa 8.9	amplifier output gain	41
Exa 8.10	input power	42
Exa 8.12	Output power	42
Exa 8.13	voltage gain	42
Exa 8.14	voltage gain	43
Exa 8.15	Voltage gain	43
Exa 9.1	emitter resistance	44
Exa 9.3	voltage gain	44
Exa 9.4	voltage gain	45
Exa 9.5	Voltage gain	45
Exa 9.6	ac output voltage	46
Exa 9.7	output power	46
Exa 9.8	voltage gain	46
Exa 9.9	input impedance	47
Exa 9.10	current gain	47
Exa 9.11	voltage gain	48
Exa 9.12	Voltage gain for the two stage amplifier . . .	48
Exa 9.13	Voltage gain	49
Exa 9.14	change in gain	49
Exa 9.15	base impedance	49
Exa 9.16	Input ipedance	50
Exa 9.17	voltage gain	50
Exa 9.18	Input impedance and Voltage gain	51
Exa 10.1	voltage and current	52
Exa 10.2	dc load line	53
Exa 10.3	Voltage gain	53
Exa 10.4	power gain	54
Exa 10.5	Input and base impedance	54
Exa 10.6	output impedance	55
Exa 10.7	Input impedance	55
Exa 10.8	Input resistance	56
Exa 10.9	circuit gain and impedance	56
Exa 10.10	gain and impedance	57
Exa 11.1	Output compliance	59
Exa 11.2	total dc power	59

Exa 11.3	Ac load power	60
Exa 11.4	Ac load power	60
Exa 11.5	Ac load power	60
Exa 11.6	Maximum efficiency	61
Exa 11.7	Maximum efficiency	61
Exa 11.8	End point values for its ac load line	62
Exa 11.9	Maximum load power	62
Exa 11.10	Total power demand	62
Exa 11.11	Maximum load power	63
Exa 11.12	Efficiency of Amplifier	63
Exa 11.13	Efficiency of Amplifier	64
Exa 11.14	Pd value	64
Exa 11.15	Pd value	64
Exa 12.1	Drain current	66
Exa 12.2	Transconductance curve	66
Exa 12.3	Two transconduction plot	67
Exa 12.4	Vgs Id and Vds determine	68
Exa 12.7	Dc characteristics of the amplifier	69
Exa 12.8	Plot dc bias line	69
Exa 12.9	Minimum And maximum Q point value	70
Exa 12.10	Minimum and maximum value of Vdsq	71
Exa 12.11	Value of Gm	71
Exa 12.12	Max and min value of voltage gain	72
Exa 12.13	Max and min gain voltage gain	72
Exa 12.14	Input Impedance	73
Exa 12.15	Voltage gain	73
Exa 12.16	Minimum and maximum value of Voltage gain Output voltage	74
Exa 12.17	Min and Approximated value of Zout	75
Exa 13.1	Transconductance curve	76
Exa 13.2	Drain current	76
Exa 13.3	Id and Vds	77
Exa 14.1	Bandwidth of the circuit	78
Exa 14.2	Geometric center frequency	78
Exa 14.3	ratio of f0 and fc1 fc2 and f0	79
Exa 14.4	Fc1 and bandwidth	79
Exa 14.5	fc2 and bandwidth	79
Exa 14.6	dB power gain of the amplifier	80

Exa 14.7	Value of f_{b1}	80
Exa 14.8	F_{1b}	81
Exa 14.9	Value of F_{c1}	82
Exa 14.10	f_{1E}	82
Exa 14.11	Gain of the amplifier	82
Exa 14.12	Value of C_{be}	83
Exa 14.13	Miller input and output capacitance	83
Exa 14.14	Value of f_{2B}	84
Exa 14.15	Value of f_{2C}	84
Exa 14.16	Lower input circuit cutoff frequency	84
Exa 14.17	Value f_{1G}	85
Exa 14.18	Overall value of f_{c1}	85
Exa 14.19	Input miller capacitance	86
Exa 14.20	f_{2G} and f_{2D}	86
Exa 14.21	C_{ds} C_{gd} and C_{gs}	87
Exa 14.22	f_{c2} for the two stage amplifier	87
Exa 14.23	f_{c1} for the two stage amplifier	88
Exa 15.1	Output voltage polarity	89
Exa 15.2	Peak to peak output voltage	89
Exa 15.3	Maximum Allowable value of v_{in}	90
Exa 15.4	Maximum input and output voltage	90
Exa 15.5	Maximum operating frequency	91
Exa 15.6	Maximumn operating frequency	91
Exa 15.7	Complete analysis	91
Exa 15.8	Analysis of non inverting amplifier	92
Exa 15.9	Analysis of voltage follower	93
Exa 15.10	Bandwidth and A_{cL}	93
Exa 15.12	Value of A_{cL}	94
Exa 15.13	Value of feedback	94
Exa 15.14	Amplifier input impedence	94
Exa 15.15	Amplifier Output	95
Exa 16.1	Output voltage	96
Exa 16.2	Refrence voltage for comparator	97
Exa 16.4	Output voltage of summing amplifier	97
Exa 16.5	output voltage	97
Exa 16.6	Output voltage	98
Exa 17.1	Q of a tuned amplifier	99
Exa 17.2	Bandwidth	99

Exa 17.3	f0 fave and Q determine	99
Exa 17.4	Bandwidth of low pass filter	100
Exa 17.5	Bandwidth of filter	100
Exa 17.6	Complete frequency analysis	101
Exa 17.7	f0 value	101
Exa 17.8	Q and bandwidth	102
Exa 17.9	Percentage of error	102
Exa 17.10	Percentage of error and approximated values	103
Exa 17.11	close loop voltage gain	103
Exa 17.12	f0 for tuned amplifier	103
Exa 17.13	Q for the tank	104
Exa 17.14	loaded Q	104
Exa 17.15	Bandwidth of the amplifier	105
Exa 18.1	av value	106
Exa 19.1	Minimum high input voltage	107
Exa 19.2	high and low output voltage	107
Exa 19.3	Output voltage	108
Exa 19.4	PW And T	108
Exa 19.5	duty cycle	109
Exa 19.6	fc and practical limit on frequency	109
Exa 19.7	UTP and LTP for the circuit	109
Exa 19.8	UTP and LTP for non inverting schmit	110
Exa 19.9	UTP and LTP	110
Exa 19.10	pulse width	111
Exa 19.11	values of VT	111
Exa 19.12	value f0 and duty cycle	111
Exa 20.1	Current surge	113
Exa 20.2	duration of surge	113
Exa 20.3	highest surge current	114
Exa 20.4	noise amplitude for false triggering	114
Exa 20.5	Maximum peak voltage	114
Exa 20.6	wavelength	115
Exa 21.1	line regulation	116
Exa 21.2	load regulation	116
Exa 21.3	allowable input voltage	117
Exa 21.4	regulated dc output	117
Exa 21.5	dc average of the load voltage	117

Chapter 2

Diodes

Scilab code Exa 2.1 current voltage

```
1 clc;
2 //ex2.1
3 R1=1000; //kohm;
4 VS=5; //Volt//voltage across voltage source
5 IT=0; //Ampere; because diode in reverse bias and
   does not allow conduction through diode
6 VD1=VS-(IT*R1); //apply kvl in the circuit
7 VR1=VD1-VS; //apply kvl in the circuit
8 disp( 'Volt ',VD1*1,"VD1=");
9 disp( 'Ampere ',IT*1,"IT=");
10 disp( 'Volt ',VR1*1,"VR1=");
```

Scilab code Exa 2.2 circuit current and voltage

```
1 clc;
2 //ex2.2
3 VD1=0; //Volt//diode is forward bias for ideal diode
   total Rideal=0 so VD1=IT*Rideal=0V
```

```

4 R1=1000; //kilo ohm;
5 VS=5; //Volt //voltage across voltage source
6 IT=(VS/R1)-(VD1/R1); //Ampere; apply kvl in the
   circuit
7 VR1=IT*R1; //Volt//apply ohms law voltage across
   resistance
8 disp( 'Volt ',VD1*1,"VD1=");
9 disp( 'mAmpere ',IT*1000,"IT=");
10 disp( 'Volt ',VR1*1,"VR1=");

```

Scilab code Exa 2.3 voltmeter reading

```

1 clc
2 //ex2.3
3 Vd=0.7; //volt
4 Vs=6; //volt
5 Vr1=Vs-Vd; //volt //Voltmeter's reading
6 disp( 'Volt ',Vr1*1,"Vr1=");

```

Scilab code Exa 2.4 total current

```

1 clc;
2 //ex2.4
3 Vs=6; //volt
4 Vd=0.7; //volt
5 R1=10000; //ohm
6 It=(Vs-Vd)/R1; //Total circuit current using
   kirchoff's volatage law
7 disp( 'Ampere ',It,"It=")

```

Scilab code Exa 2.5 circuite current

```
1 clc;
2 //ex2.5
3 Vs=5; // volt
4 Vd=0.7; // volt
5 R1=1200; //ohm
6 R2=2200; //ohm
7 It=(Vs-Vd)/(R1+R2); //Ampere//Apply KVL to circuit
8 disp(' Ampere ',It*1, " It=")
```

Scilab code Exa 2.6 Value of It

```
1 clc;
2 //ex2.6
3 Vs=4; // volt
4 Vd=0.7; // volt
5 R1=5100; //ohm
6 IT=(Vs-2*Vd)/R1; //Ampere//KVL int the circuit
7 disp(' Ampere ',IT*1, " IT=")
```

Scilab code Exa 2.7 percentage of error by using ideal diode

```
1 clc;
2 //ex2.7
3 //assume diode is ideal(Vf=0V)
4 Vs=10; //Volt
5 Rt=3030; //Ohm
6 IT=Vs/Rt; //Ampere
7 //assume diode is practical(Vf=0.7V)
8 Vf=1.4; //Volt
9 Vs1=Vs-Vf; //Volt
10 IT1=Vs1/Rt; //Ampere
```

```

11 e=(-100*(IT1-IT))/IT1; //Percentage of error between
    two circuit current
12 disp( 'Ampere',IT*1,"IT=");
13 disp( 'Ampere',IT1*1,"IT1=");
14 disp( '%',e*1,"Percentage Error="); //The answers
    vary due to round off error

```

Scilab code Exa 2.9 average forward current

```

1 clc;
2 //ex2.9
3 Vs=50; //Volt
4 Vd=0.7; //volt
5 RL=200; //ohm
6 If=(Vs-Vd)/RL; //Ampere//forward current in the
    circuit
7 Io=(20/100)*If+If; //Ampere//Average forward current
    rating 20% greater than calculated value of If
8 disp( 'mAmp',If*1000,"If="); //The answers vary due
    to round off error
9 disp( 'mAmp',Io*1000,"Io=") //The answers vary due to
    round off error

```

Scilab code Exa 2.10 min forward power dissipation rating

```

1 clc;
2 //ex2.10
3 Vss=10; //voltage
4 Vf=0.7; //voltage
5 R=100; //ohm
6 //total current through the circuit by using
    kirchhoff's voltage law
7 If=(Vss-Vf)/R; //Ampere

```

```

8 //power dissipation form diode for Vf and If
9 Pf=Vf*If; //Watt
10 PDmax=(20/100)*Pf+Pf; //Watt//forward power
    dissipation that is 20% greater than value of Pf
11 disp( 'mA',If*1000," If=");
12 disp( 'mW',Pf*1000," Pf=");
13 disp( 'mW',PDmax*1000," PDmax=");

```

Scilab code Exa 2.11 forward power dissipation

```

1 clc;
2 //ex2.11
3 Pdmax=500; //miliwatt
4 Vf=0.7; //volt
5 Io=Pdmax/Vf; //Ampere//using P=V*I
6 Ifmax=(80/100)*Io; //Ampere//maximum forward current
    80% of IO
7 disp( 'mA',Io," Io="); //The answers vary due to
    round off error
8 disp( 'mA',Ifmax," Ifmax="); //The answers vary due to
    round off error

```

Scilab code Exa 2.12 voltage across diode

```

1 clc;
2 //ex2.12
3 Vb=0.7; //volt
4 If=[0.001 0.005]; //Ampere
5 Rb=5; //ohm
6 Vf1=Vb+If(1,1)*Rb; //Volt//VF=VB+If*Rb;
7 Vf2=Vb+If(1,2)*Rb; //Volt//VF=VB+If*Rb;
8 disp( 'mV',Vf1," Vf1=");
9 disp( 'mV',Vf2," Vf2=");

```

Scilab code Exa 2.13 Current Izm

```
1 clc;
2 Pdmax=0.5; //watt
3 Vz=6.8; //volt
4 Izm=Pdmax/Vz; //Ampere//Power(P)=V*I
5 disp('mA',Izm*1000,"Izm="); //The answers vary due
   to round off error
```

Scilab code Exa 2.14 derating factor and Pd rating

```
1 clc;
2 //ex2.14;
3 T=100; //degree celcius
4 Pdissi=4 //miliwatt
5 D=Pdissi*(T-75); //D IS Derating value in miliwatt
6 Pd=(500-D); //W
7 disp('mW',Pd,"Pd=");
```

Scilab code Exa 2.16 diode application

```
1 clc;
2 //ex2.16
3 Vz=20; //volt
4 Izm=0.15; //Ampere
5 Pdmax=Vz*Izm; //Watt//p=v*i
6 disp('W',Pdmax,"Pdmax=");
```

Scilab code Exa 2.17 current limiting resistor

```
1 clc ;  
2 Voutpk=8; // volt  
3 Vf=1.8; // volt  
4 If=0.02; //Ampere  
5 Rs=(Voutpk-Vf)/If; //Ohm//v=r*i  
6 disp( 'Ohm' ,Rs , "Rs=" );
```

Chapter 3

Common Diode Applications Basic Power supply

Scilab code Exa 3.1 secondary current

```
1 clc;
2 //ex3.1
3 Np=1;
4 Ns=4;
5 Ip=1; //Ampere
6 Is=(Np/Ns)*Ip; //Ampere
7 disp('mA',Is*1000,' Is="'); //The answers vary due to
   round off error
```

Scilab code Exa 3.2 peak load voltage

```
1 clc;
2 //ex3.2
3 Vprms=120; //volt
4 Vppk=Vprms/0.707; //volt
5 Np=5;
```

```

6 Ns=1;
7 Vspk=(Ns/Np)*Vppk; //voltage
8 Vf=0.7; //voltage
9 VLpk=Vspk-Vf //voltage
10 disp('V',Vppk,"Vppk="); //The answers vary due to
    round off error
11 disp('V',Vspk,"Vspk="); //The answers vary due to
    round off error
12 disp('V',VLpk,"VLpk="); //The answers vary due to
    round off error

```

Scilab code Exa 3.3 peak load voltage for the circuit

```

1 clc;
2 //ex3.3
3 Vsrms=25; //voltage
4 Vspk=Vsrms/0.707; //voltage
5 Vf=0.7; //voltage
6 VLpk=Vspk-Vf; //voltage
7 disp('V',Vspk,"Vspk="); //The answers vary due to
    round off error
8 disp('V',VLpk,"VLpk="); //The answers vary due to
    round off error

```

Scilab code Exa 3.4 peak load current

```

1 clc;
2 //ex3.4
3 Vprms=120; //voltage
4 Vppk=Vprms/0.707; //voltage
5 Ns=1;
6 Np=3;
7 Vspk=(Ns/Np)*Vppk; //voltage

```

```

8 Vf=0.7; //voltage
9 VLpk=Vspk-Vf; //voltage
10 RL=10000; //ohm
11 ILpk=VLpk/RL; //Ampere
12 disp('V',Vppk,"Vppk="); //The answers vary due to
    round off error
13 disp('V',Vspk,"Vspk="); //The answers vary due to
    round off error
14 disp('V',VLpk,"VLpk="); //The answers vary due to
    round off error
15 disp('mA',ILpk*1000,"ILpk="); //The answers vary due
    to round off error

```

Scilab code Exa 3.5 average voltage

```

1 clc;
2 //ex=3.5
3 Vprms=120; //voltage
4 Vppk=Vprms/0.707; //voltage
5 Ns=1;
6 Np=2;
7 Vspk=(Ns/Np)*Vppk; //voltage
8 Vf=0.7; //voltage
9 Vlpk=Vspk-Vf; //voltage
10 Vave=Vlpk/3.14; //voltage
11 disp('V',Vppk,"Vppk="); //The answers vary due to
    round off error.
12 disp('V',Vspk,"Vspk="); //The answers vary due to
    round off error.
13 disp('V',Vlpk,"Vlpk="); //The answers vary due to
    round off error.
14 disp('V',Vave,"Vave="); //The answers vary due to
    round off error

```

Scilab code Exa 3.6 average current

```
1 clc;
2 //ex3.6
3 Vave=26.8; //Volt
4 RL=20000; //Ohm
5 Iave=Vave/RL; //Ampere//from  $v=r*i$ 
6 disp('mA',Iave*1000,"Iave=");
```

Scilab code Exa 3.7 dc load current

```
1 clc;
2 //ex3.7;
3 Vac=24; //volt
4 Vspk=Vac/0.707; //volt
5 Vlpk=Vspk-0.7; //volt
6 RL=20000; //Ohm
7 Ilpk=Vlpk/RL; //Ampere
8 Iave=Ilpk/3.14; //Ampere
9 disp('V',Vspk,"Vspk="); //The answers vary due to
   round off error
10 disp('V',Vlpk,"Vlpk="); //The answers vary due to
   round off error
11 disp('mili Amperes',Ilpk*1000,"Ilpk="); //The
   answers vary due to round off error
12 disp('Micro Amperes',Iave*1000000,"Ilpk="); //The
   answers vary due to round off error
```

Scilab code Exa 3.8 dc output voltage

```

1  clc;
2  //ex3.8
3  Vac=48; //volt
4  Vspk=Vac/0.707; //volt
5  Vf=0.7; //volt
6  Vlpk=Vspk-Vf; //volt
7  Vave=Vlpk/%pi; //volt
8  disp('V',-Vspk,"Vspk="); //The answers vary due to
   round off error
9  disp('V',-Vlpk,"Vlpk="); //The answers vary due to
   round off error
10 disp('V',-Vave,"Vave="); //The answers vary due to
   round off error

```

Scilab code Exa 3.9 dc load voltage

```

1  clc;
2  //ex3.8
3  Vac=30; //volt
4  Vspk=Vac/0.707; //volt
5  Vf=0.7; //volt
6  Vlpk=(Vspk/2)-Vf; //volt
7  Vave=(2*Vlpk)/%pi; //volt
8  disp('V',Vspk,"Vspk="); //The answers vary due to
   round off error
9  disp('V',Vlpk,"Vlpk="); //The answers vary due to
   round off error
10 disp('V',Vave,"Vave="); //The answers vary due to
   round off error

```

Scilab code Exa 3.10 I_{lpk} and I_{ave}

```

1  clc;

```

```

2 //ex3.10
3 V1pk=20.5; //volt
4 RL=5100; //ohm
5 I1pk=V1pk/RL; //Ampere// from v=r*i
6 Vave=13.1; //volt//from v=r*i
7 Iave=Vave/RL; //Ampere
8 disp('mA',I1pk*1000,"I1pk="); //The answers vary due
   to round off error
9 disp('mA',Iave*1000,"Iave="); //The answers vary due
   to round off error

```

Scilab code Exa 3.11 dc load voltage and current

```

1 clc;
2 //ex3.11
3 Vac=12; //volt
4 Vspk=Vac/0.707; //volt
5 Vf=0.7; //volt
6 V1pk=Vspk-2*Vf; //volt
7 Vave=(2*V1pk)/%pi; //volt
8 RL=120; //ohm
9 Iave=Vave/RL; //Ampere
10 disp('V',Vspk,"Vspk="); //The answers vary due to
   round off error
11 disp('V',V1pk,"V1pk="); //The answers vary due to
   round off error
12 disp('V',Vave,"Vave="); //The answers vary due to
   round off error
13 disp('mA',Iave*1000,"Iave="); //The answers vary due
   to round off error

```

Scilab code Exa 3.12 dc load voltage


```

1  clc;
2  //ex3.12
3  Vac=12; //volt
4  Vspk=Vac/0.707; //volt
5  Vf=0.7; //volt
6  Vlpk=(Vspk/2)-Vf; //volt
7  Vave=(2*Vlpk)/%pi; //volt
8  RL=120; //ohm
9  Iave=Vave/RL; //Ampere
10 disp('V',Vspk,"Vspk="); //The answers vary due to
    round off error
11 disp('V',Vlpk,"Vlpk="); //The answers vary due to
    round off error
12 disp('V',Vave,"Vave="); //The answers vary due to
    round off error
13 disp('mA',Iave*1000,"Iave="); //The answers vary due
    to round off error

```

Scilab code Exa 3.13 averagen voltage

```

1  clc;
2  //ex3.13
3  Vac=36; //Volt
4  Vspk=Vac/0.707; //Volt
5  Vf=0.7; //Volt
6  Vlpk=Vspk-2*Vf; //Volt
7  Vave=(2*Vlpk)/%pi; //Volt
8  disp('V',Vspk,"Vspk="); //The answers vary due to
    round off error
9  disp('V',Vlpk,"Vlpk="); //The answers vary due to
    round off error
10 disp('V',Vave,"Vave="); //The answers vary due to
    round off error

```

Scilab code Exa 3.14 surge current

```
1  clc;
2  //ex3.14
3  Vppk=170; //volt
4  Ns=1;
5  Np=2;
6  Vspk=(Ns/Np)*Vppk; //Volt //(N1/N2=Vp/Vs)
7  Rw=0.8; //ohm
8  Rb=5; //ohm
9  Isurge=Vspk/(Rw+Rb); //Ampere
10 disp('V',Vspk,"Vspk="); //The answers vary due to
    round off error
11 disp('A',Isurge,"Isurge="); //The answers vary due
    to round off error
```

Scilab code Exa 3.15 ripple output

```
1  clc;
2  //ex3.15
3  IL=0.02; //Ampere
4  t=[0.0167 0.00833]; //seceond
5  c=0.0005; // Farad
6  Vr1=(IL*t(1,1))/c; //peakvolt
7  Vr2=(IL*t(1,2))/c; //peakvolt
8  disp('mVpp',Vr1*1000,"Vr1=");
9  disp('mVpp',Vr2*1000,"Vr2="); //The answers vary
    due to round off error
```

Scilab code Exa 3.16 average voltage

```
1 clc;
2 //ex3.16
3 Vac=24; //voltage
4 Vspk=Vac/0.707; //voltage
5 Vf=0.7; //voltage
6 Vlpk=(Vspk/2)-Vf; //voltage
7 Vdc=Vlpk; //voltage
8 RL=1200; //ohm
9 IL=Vdc/RL; //Amperes //v=r*i
10 t=0.00833 //second
11 C=0.00047 //farad
12 Vr=(IL*t)/C; //voltage
13 Vdc=Vlpk-(Vr/2); //voltage
14 disp('V',Vdc,"Vdc="); //The answers vary due to
    round off error
```

Scilab code Exa 3.17 circuit current

```
1 clc;
2 //ex3.17
3 Vin=20; //voltage
4 Vz=9.1; //voltage
5 Rs=2200; //ohm
6 I=(Vin-Vz)/Rs; //Ampere
7 disp('mA',I*1000,"I="); //The answers vary due to
    round off error
```

Scilab code Exa 3.18 load current

```
1 clc;
2 //Ex3.18
```

```

3 Vz=9.1; //voltage
4 RL=10000; //ohm
5 IL=Vz/RL; //Ampere from V=R*I
6 disp('micro Amperes',IL*1000000,'IL='); //The
    answers vary due to round off error

```

Scilab code Exa 3.19 load current and zener current

```

1 clc;
2 //Ex3.19
3 IT=0.00495; //Ampere
4 Vz=9.1; //voltage
5 RL=10000; //ohm
6 IL=Vz/RL; //Ampere//from V=R*I
7 Iz=IT-IL; //Ampere/Iz=IT-IL;
8 disp('mA',Iz*1000,'Iz='); //The answers vary due to
    round off error

```

Scilab code Exa 3.20 minimum allowable value of RL

```

1 clc;
2 //ex3.20
3 Vin=20; //voltage
4 Vz=3.3; //voltage
5 Rs=1000; //ohm
6 I=(Vin-Vz)/Rs; //Ampere
7 IZK=0.003 //Ampere
8 Ilmax=I-IZK; //Ampere
9 RLmin=Vz/Ilmax; //ohm
10 disp('ohm',RLmin,'RLmin='); //The answers vary due
    to round off error

```

Scilab code Exa 3.21 ripple at the load

```
1 clc;
2 //Ex3.21
3 Vr=1.5; //Volt
4 Zl=5; //Ohm
5 RL=120; //Ohm
6 Rs=51; //Ohm
7 R1=(Zl*RL)/(Zl+RL); //Ohm
8 VROUT=(R1/(R1+Rs))*Vr; //Volt
9 disp('mVpp',VROUT*1000,"VROUT="); //The answers vary
    due to round off error
```

Scilab code Exa 3.22 dc voltage VROUT and IL

```
1 clc;
2 //ex3.22
3 Vac=36; //Volt
4 VSPK=Vac/0.707; //Volt
5 Vf=0.7; //Volt
6 VPK=VSPK-2*Vf; //Volt
7 VIN=VPK; //Volt
8 Rs=75; //Ohm
9 Vz=30; //Volt
10 Ir=(VIN-Vz)/Rs; //Amperes
11 t=0.00833 //second
12 C=0.0022 //Farad
13 Vr=(Ir*t)/C; //Volt
14 Vdc=30; //Volt
15 RL=300; //Ohm
16 ZZ=60 //Ohm
17 RL=300 //Ohm
```

```
18 Rs=75 //Ohm
19 Znet=(ZZ*RL)/(ZZ+RL); //Ohm
20 I1=Vz/RL; //Ampere
21 Vrout=(Znet/((Znet)+Rs))*Vr; //Volt
22 disp('V',Vdc,"Vdc="); //The answers vary due to
    round off error
23 disp('mVpp',Vrout*1000,"Vrout="); //The answers vary
    due to round off error
24 disp('mA',I1*1000,"I1="); //The answers vary due to
    round off error
```

Chapter 4

Common Diode Applications clippers clampers Voltage multiplier and Display

Scilab code Exa 4.1 peak load voltage

```
1 clc;  
2 Vin=12; //volt  
3 RL=5100; //ohm  
4 Rs=1000; //ohm  
5 VL=(RL/(RL+Rs))*Vin ; //volt //voltage divide rule  
6 disp('Vpk',VL,"VL="); //The answers vary due to round  
   off error
```

Scilab code Exa 4.2 voltage at register

```
1 clc;  
2 VL=-0.7; //volt  
3 Vin=-12; //volt  
4 VRS=Vin-VL; //volt
```

```
5 disp('Vpk',VRS,"VRS="); //The answers vary due to  
   round off error
```

Scilab code Exa 4.3 voltage at load

```
1 clc;  
2 Vf=0.7; //volt  
3 Vin=10; //volt  
4 VRs=Vin-Vf; //volt  
5 RL=1200; //ohm  
6 Rs=220; //ohm  
7 VL=-Vin*(RL/(RL+Rs)); //volt  
8 disp('Vpk',VL,"VL="); //The answers vary due to round  
   off error
```

Scilab code Exa 4.4 peak load voltage

```
1 clc;  
2 Vin=8; //volt  
3 RL=6200; //ohm  
4 Rs=100; //ohm  
5 VL=Vin*(RL/(RL+Rs)); //volt  
6 disp('Vpk',VL,"VL="); //The answers vary due to round  
   off error
```

Scilab code Exa 4.5 capacitor charge and discharge

```
1 clc;  
2 Rd=10; //Ohm  
3 C1=0.000001; //Farad
```



```
4 RL=10000; //Ohm
5 Tc=5*(Rd*C1);
6 Td=5*(RL*C1);
7 disp('seconds ',Tc,"Tc="); //The answers vary due to
  round off error
8 disp('seconds ',Td,"Td="); //The answers vary due to
  round off error
```

Chapter 6

Bipolar Junction Transistors

Scilab code Exa 6.1 collector current

```
1 clc;
2 B=300;
3 Ib=[0.00002 0.00005]; //Ampere
4 Ic1=B*Ib(1,1); //Ampere
5 Ic2=B*Ib(1,2); //Ampere
6 disp('mA',Ic1*1000,"Ic1=");
7 disp('mA',Ic2*1000,"Ic2=");
```

Scilab code Exa 6.2 collector current emitter current

```
1 clc;
2 B=200;
3 Ib=0.000125; //Ampere
4 Ic=B*Ib; //Ampere
5 Ie=Ib+Ic; //Ampere
6 disp('mA',Ic*1000,"Ic=");
7 disp('mA',Ie*1000,"Ie=");
```

Scilab code Exa 6.3 collector and base current

```
1 clc ;
2 B=200;
3 Ie=0.015; //Ampere
4 Ib=Ie/(B+1); //Ampere
5 Ic=B*Ib; //Ampere
6 disp('micro Amperes ',Ib*1000000," Ic="); //The answers
    vary due to round off error
7 disp('mA',Ic*1000," Ie="); //The answers vary due to
    round off error
```

Scilab code Exa 6.4 base and collector current

```
1 clc ;
2 B=400;
3 Ic=0.05; //Amperes
4 Ib=Ic/B; //Amperes
5 Ie=Ic+Ib; //Amperes
6 disp('Amperes ',Ib," Ib="); //The answers vary due to
    round off error
7 disp('Amperes ',Ie," Ie="); //The answers vary due to
    round off error
```

Scilab code Exa 6.5 collector current

```
1 clc ;
2 B=300;
3 Ie=0.03; //Ampere
```

```
4 Ib=0.0001; //Ampere
5 A=B/(B+1);
6 Ic1=A*Ie; //Ampere
7 Ic2=B*Ib //Ampere
8 disp('Amperes ',Ic1," Ic1="); //The answers vary due to
    round off error
9 disp('Amperes ',Ic2," Ic2="); //The answers vary due to
    round off error
```

Scilab code Exa 6.6 max base current

```
1 clc;
2 Icmax=0.5; //Ampere
3 Bmax=300;
4 Ibmax=Icmax/Bmax; //Ampere
5 disp('mA',Ibmax*1000," Ibmax="); //The answers vary
    due to round off error
```

Chapter 7

DC Biasing Circuits

Scilab code Exa 7.1 dc load line

```
1  clc;
2  Vcc=12; // volt
3  Vceoff=12; // volt
4  Rc=2000; //ohm
5  Icsat=Vceoff/Rc; //Ampere//v=r*i
6  disp('mA',Icsat*1000,"Icsat="); //The answers vary
   due to round off error
7  T1=0:2:12; // T1 axes is for voltage axes
8  T2=6:-1:0 // T2 axes is for Ic mA And T2(max)=Icsat
   =6 mA
9  plot(T1,T2)
10 xlabel('Vce(V)')
11 ylabel('Ic(mA)')
```

Scilab code Exa 7.2 dc load line

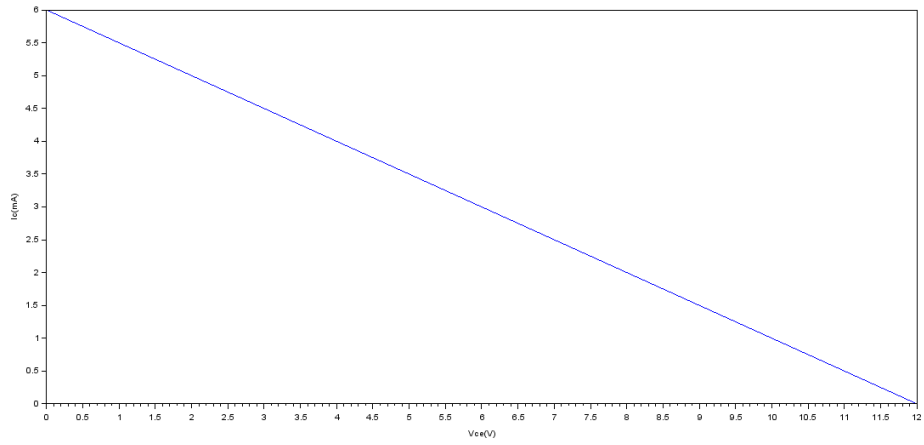


Figure 7.1: dc load line

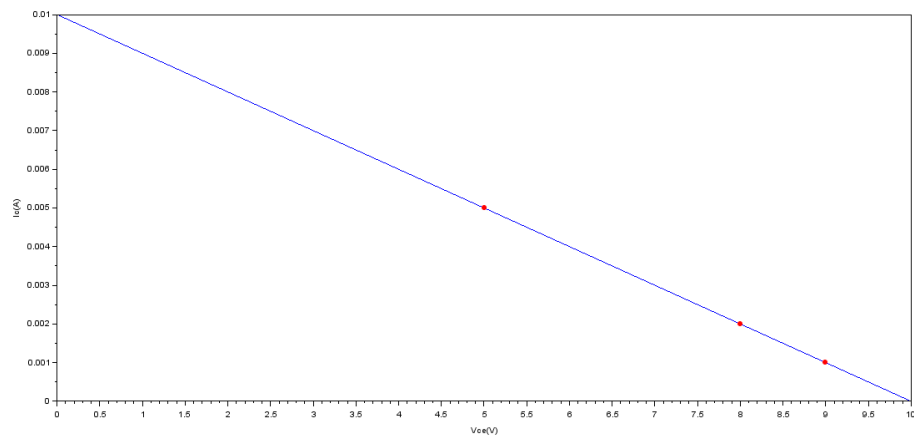


Figure 7.2: dc load line

```

1  clc;
2  Vcc=10; // volt
3  Rc=1000; //ohm
4  Icsat=Vcc/Rc; //Ampere
5  Vceoff=10; // Volt
6  Ic=[0.001 0.002 0.005] //Ampere
7  Vce=zeros(1,3); // Volt
8  for i=1:3
9      Vce(1,i)=Vcc-Ic(1,i)*Rc; // volt
10 end
11 disp('V',Vce(1,1),'Vce1='); //The answers vary due to
    round off error
12 disp('V',Vce(1,2),'Vce2='); //The answers vary due to
    round off error
13 disp('V',Vce(1,3),'Vce3='); //The answers vary due to
    round off error
14
15 T1=0:1:10; // T1 axes is for voltage axes
16 T2=10:-1:0 // T2 axes is for Ic mA
17 plot(T1,T2)
18 plot((Vce(1,1),Ic(1,1)))
19 xlabel('Vce(V)')
20 ylabel('Ic(mA)')

```

Scilab code Exa 7.3 Q point values

```

1  clc;
2  Vcc=8; // volt
3  Vbe=0.7; // volt
4  Rb=360000; //ohm
5  Ib=(Vcc-Vbe)/Rb; //Ampere
6  Hfe=100;
7  Ic=Hfe*Ib; //Ampere
8  Rc=2000; //ohm
9  Vce=Vcc-Ic*Rc; // volt

```

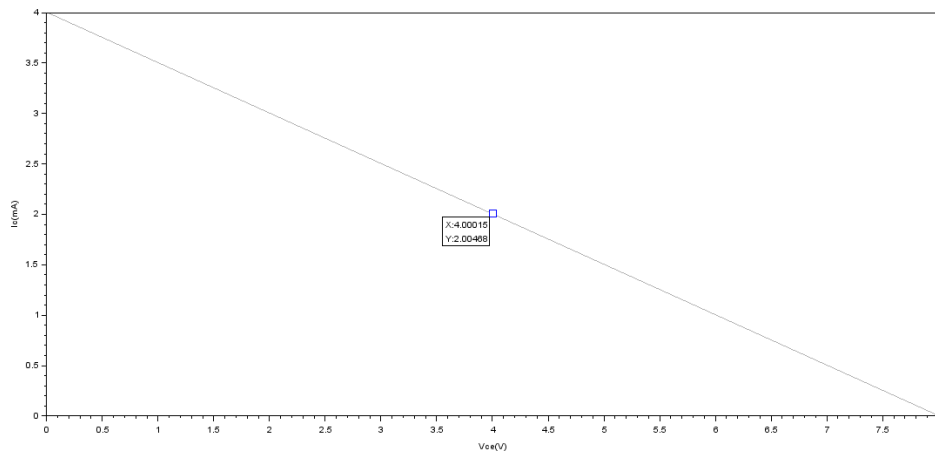


Figure 7.3: midpoint biased

```

10 disp('mA', Ic*1000, " Ic="); //The answers vary due to
    round off error
11 disp('V', Vce, " Vce="); //The answers vary due to round
    off error

```

Scilab code Exa 7.4 midpoint biased

```

1  clc;
2  Vcc=8; // volt
3  Rc=2000; //ohm
4  Icsat=Vcc/Rc; //Ampere
5  Vceoff=Vcc; // volt
6  Vcc=8; // volt
7  Vbe=0.7; // volt
8  Rb=360000; //ohm
9  Ib=(Vcc-Vbe)/Rb; //Ampere
10 Hfe=100;
11 Ic=Hfe*Ib; //Ampere

```



```

12 Rc=2000; //ohm
13 Vce=Vcc-Ic*Rc; //volt
14
15 T1=0:2:8; // T1 axes is for voltage axes
16 T2=4:-1:0; //T2 axes is for Ic mA
17
18 plot(T1,T2)
19 xlabel('Vce(V)')
20 ylabel('Ic(mA)')

```

Scilab code Exa 7.5 Q Point

```

1 clc;
2 //A circuit is midpoint bised when the Q-point value
   of Vce is one half of Vcc.
3 //from example and 7.3
4 Vcc=8; //volt
5 Vbe=0.7; //volt
6 Rb=360000; //ohm
7 Ib=(Vcc-Vbe)/Rb; //Ampere
8 Hfe=100;
9 Ic=Hfe*Ib; //Ampere
10 Rc=2000; //ohm
11 Vce=Vcc-Ic*Rc; //volt
12 disp('V',Vce,'Vce='); //The answers vary due to round
   off error
13 //Here we get Vce = (Vcc/2)
14 //We can conclude that the circuit is midpoint

```

Scilab code Exa 7.6 effect of temprature

```

1 clc;
2 //for T=25' and Hfe=100

```

```

3 Ib=0.0000203; //Ampere
4 Ic=0.00203; //Ampere
5 Vce=3.94; //Volt
6 //for T=100' andHfe=150
7 Hfe=150;
8 Vcc=8; //volt
9 Rc=2000; //ohm
10 Ic=Hfe*Ib; //Ampere
11 Vce=Vcc-Ic*Rc; //volt
12 disp('mA',Ic*1000,"Ic="); //The answers vary due to
    round off error
13 disp('V',Vce,"Vce="); //The answers vary due to round
    off error

```

Scilab code Exa 7.7 Q point vales

```

1 clc;
2 Vcc=10; //volt
3 R1=18000; //ohm
4 R2=4700; //Ohm
5 Vb=(R2/(R1+R2))*Vcc; //volt //voltage divider rule
6 Ve=Vb-0.7; //volt
7 Re=1100; //ohm
8 Icq=Ve/Re; //Ampere//assumption Icq=Ie
9 Rc=3000; //Ohm
10 Re=1100; //Ohm
11 Vceq=Vcc-Icq*(Rc+Re); //Volt
12 disp('A',Icq,"Icq="); //The answers vary due to round
    off error
13 disp('V',Vceq,"Vceq="); //The answers vary due to
    round off error

```

Scilab code Exa 7.8 base current

```

1  clc;
2  Vcc=20; // volt
3  R2=1000; //ohm
4  R1=6800; //ohm
5  Vb=(R2/(R1+R2))*Vcc; //volt//voltage divider rule
6  Ve=Vb-0.7; // volt
7  Re=1000; //ohm
8  Ie=Ve/Re; //Ampere
9  Hfe=50;
10 Ib=Ie/(Hfe+1); //Ampere
11 disp('Amperes',Ib,"Ib="); //The answers vary due to
    round off error

```

Scilab code Exa 7.9 Q point

```

1  clc;
2  Vcc=20; // volt
3  R2=10000; //Ohm
4  R1=68000; //ohm
5  Vth=(R2/(R1+R2))*Vcc; //volt//by voltage divider
    rule Thevenin
6  Rth=(R1*R2)/(R1+R2); //ohm
7  Vbe=0.7; //Volt
8  Hfe=50;
9  Re=1100; //Ohm
10 Rc=6200; //Ohm
11 Icq=(Vth-Vbe)/((Rth/Hfe)+Re); //Ampere
12 Vceq=Vcc-Icq*(Rc+Re); //Volt
13 disp('mA',Icq*1000,"Icq="); //The answers vary due to
    round off error
14 disp('V',Vceq,"Vceq="); //The answers vary due to
    round off error

```

Scilab code Exa 7.10 I_{cq} and V_{ceq}

```
1 clc;
2 Vee=-12; //volt
3 Re=1500; //ohm
4 Icq=-(Vee+0.7)/Re; //Ampere
5 Vcc=12; //volt
6 Rc=750; //ohm
7 Vceq=Vcc-Icq*Rc+0.7; //volt
8 disp('mA',Icq*1000,"Icq="); //The answers vary due to
   round off error
9 disp('V',Vceq,"Vceq="); //The answers vary due to
   round off error
```

Scilab code Exa 7.11 I_{csat} and V_{ceoff}

```
1 clc;
2 Vcc=12; //volt
3 Rc=750; //ohm
4 Re=1500; //ohm
5 Icsat=(2*Vcc)/(Rc+Re); //Ampere
6 Vceoff=2*Vcc; //volt
7 disp('mA',Icsat*1000,"Icsat="); //The answers vary
   due to round off error
8 disp('V',Vceoff,"Vceoff="); //The answers vary due to
   round off error
```

Scilab code Exa 7.12 Q points

```
1 clc;
2 Vcc=10; //volt
3 Vbe=0.7; //volt
4 Rb=180000; //ohm
```

```

5 Hfe=100;
6 Rc=1500; //Ohm
7 Ib=(Vcc-Vbe)/(Rb+(Hfe*Rc)); //Ampere
8 Icq=Hfe*Ib; //Ampere
9 Vceq=Vcc-Icq*Rc; //volt
10 disp('mA',Icq*1000,"Icq="); //The answers vary due to
    round off error
11 disp('V',Vceq,"Vceq="); //The answers vary due to
    round off error

```

Scilab code Exa 7.13 Q points

```

1 clc;
2 Vcc=16; //Volt
3 Vbe=0.7; //Volt
4 Rb=680000; //Ohm
5 Hfe=50;
6 Rc=6200; //Ohm
7 Re=1600; //Ohm
8 Ib=(Vcc-Vbe)/(Rb+((Hfe+1)*Re)); //Ampere
9 Icq=Hfe*Ib; //Ampere
10 Vceq=Vcc-Icq*(Rc+Re); //Volt
11 disp('mA',Icq*1000,"Icq="); //The answers vary due to
    round off error
12 disp('V',Vceq,"Vceq="); //The answers vary due to
    round off error

```

Chapter 8

Introduction to Amplifiers

Scilab code Exa 8.1 voltage gain

```
1 clc;  
2 Vout=0.25; //voltage  
3 Vin=0.0004; //voltage  
4 Av=Vout/Vin; //Voltagegain  
5 disp(' ',Av,"Av="); //The answers vary due to round  
   off error
```

Scilab code Exa 8.2 output voltage

```
1 clc;  
2 Vin=0.00024; //voltage  
3 Av=625; //Voltagegain  
4 Vout=Av*Vin; //voltage  
5 disp('mV',Vout*1000,"Vout="); //The answers vary due  
   to round off error
```

Scilab code Exa 8.3 input voltage

```
1 clc;
2 Zin=1500; //ohm
3 Rs=100; //Ohm
4 Vs=0.002; //Volt
5 Vin=Vs*(Zin/(Zin+Rs)); //Volt
6 disp('mV',Vin*1000,"Vin="); //The answers vary due to
   round off error
```

Scilab code Exa 8.4 output voltage

```
1 clc;
2 Vin=[0.002 0.00188]; //Volt
3 Av=500;
4 Vout1=Av*Vin(1,1); //Volt
5 Vout2=Av*Vin(1,2); //Volt
6 disp('V',Vout1,"Vout1="); //The answers vary due to
   round off error
7 disp('mV',Vout2*1000,"Vout2="); //The answers vary
   due to round off error
```

Scilab code Exa 8.5 load voltage

```
1 clc;
2 Vout=0.3; //volt
3 RL=1200; //Ohm
4 Zout=300; //ohm
5 VL=Vout*(RL/(RL+Zout)); //voltage divider rule
6 disp('mV',VL*1000,"Vl="); //The answers vary due to
   round off error
```

Scilab code Exa 8.6 efficiency

```
1 clc;  
2 PL=0.24; //watt  
3 Pdc=1.2; //watt  
4 efficiency=(PL/Pdc)*100;  
5 disp('%',efficiency," efficiency="); //The answers  
    vary due to round off error
```

Scilab code Exa 8.7 gain in dB

```
1 clc;  
2 Pout=2; //watt  
3 Pin=0.0001; //watt  
4 ApdB=10*log10(Pout/Pin);  
5 disp('dB',ApdB," ApdB="); //The answers vary due to  
    round off error
```

Scilab code Exa 8.8 power gain

```
1 clc;  
2 ApdB=3;  
3 Ap=10^(ApdB/10);  
4 disp(' ',Ap," Ap=");
```

Scilab code Exa 8.9 amplifier output gain


```
1 clc;  
2 ApdB=3;  
3 Ap=10^(ApdB/10);  
4 Pout=Ap*0.05; //Watt  
5 disp('mW',Pout*1000,"Pout="); //The answers vary due  
   to round off error
```

Scilab code Exa 8.10 input power

```
1 clc;  
2 ApdB=-3;  
3 Ap=10^(ApdB/10);  
4 Pout=0.05; //watt  
5 Pin=Pout/Ap; //watt  
6 disp('mW',Pin*1000,"Pin=");
```

Scilab code Exa 8.12 Output power

```
1 clc;  
2 ApdB=50;  
3 Ap=10^(ApdB/10);  
4 Pin=0.001; //watt  
5 Pout=Pin*Ap; //watt  
6 disp('W',Pout,"Pout=");
```

Scilab code Exa 8.13 voltage gain

```
1 clc;  
2 Vout=2; //volt  
3 Vin=0.025; //volt
```

```
4 AvdB=20*log10(Vout/Vin);
5 disp('dB',AvdB,"AvdB="); //The answers vary due to
    round off error
```

Scilab code Exa 8.14 voltage gain

```
1 clc;
2 AvdB=6;
3 Av=10^(AvdB/20);
4 disp(' ',Av,"Av="); //The answers vary due to round
    off error
```

Scilab code Exa 8.15 Voltage gain

```
1 clc;
2 AvdB=-6;
3 Av=10^(AvdB/20);
4 disp(' ',Av,"Av="); //The answers vary due to round
    off error
```

Chapter 9

Common Emitter Amplifiers

Scilab code Exa 9.1 emitter resistance

```
1  clc;
2  R2=2200; //ohm
3  R1=10000; //ohm
4  Vcc=10; //volt
5  Vb=Vcc*(R2/(R1+R2)); //volt
6  Ve=Vb-0.7; //volt
7  Re=1000; //ohm
8  Ie=Ve/Re; //Ampere
9  re=0.025/Ie; //Ohm
10 disp('ohm',re,'re='); //The answers vary due to round
    off error
```

Scilab code Exa 9.3 voltage gain

```
1  clc;
2  Vout=12; //Volt
3  Vin=0.06; //Volt
4  Av=Vout/Vin;
```

```
5 disp(' ',Av,"Av="); //The answers vary due to round  
   off error
```

Scilab code Exa 9.4 voltage gain

```
1 clc;  
2 //step1  
3 Vcc=20; //volt  
4 R2=20000; //ohm  
5 R1=150000; //ohm  
6 Vb=20*(R2/(R2+R1)); //Volt  
7 Ve=Vb-0.7; //volt  
8 Re=2200; //ohm  
9 Ie=Ve/Re; //Ampere  
10 re=0.025/Ie; //ohm  
11 Rc=12000; //ohm  
12 RL=50000; //ohm  
13 rc=(Rc*RL)/(Rc+RL); //ohm  
14 Av=rc/re;  
15 disp(' ',Av,"Av="); //The answers vary due to round  
   off error
```

Scilab code Exa 9.5 Voltage gain

```
1 clc;  
2 R2=4700; //Ohm  
3 R1=18000; //ohm  
4 Vcc=10; //volt  
5 Vth=Vcc*(R2/(R1+R2)); //volt  
6 Rth=(R1*R2)/(R1+R2); //ohm  
7 Vbe=0.7; //volt  
8 Hfe=30;  
9 Re=1200; //ohm
```

```

10 Icq=(Vth-Vbe)/((Rth/Hfe)+Re); //Ampere
11 Ie=Icq; //Ampere
12 re=0.025/Ie; //Ohm
13 Rc=1500; //Ohm
14 RL=5100; //Ohm
15 rc=(Rc*RL)/(Rc+RL); //Ohm
16 Av=rc/re;
17 disp(' ',Av,"Av="); //The answers vary due to round
    off error

```

Scilab code Exa 9.6 ac output voltage

```

1 clc;
2 Vin=0.08; //Volt
3 Av=48.3;
4 Vout=Av*Vin; //Volt
5 disp('V',Vout,"Vout=");

```

Scilab code Exa 9.7 output power

```

1 clc;
2 Ai=20;
3 Av=48.3;
4 Ap=Ai*Av;
5 Pin=0.00008; //Watt
6 Pout=Ap*Pin; //Watt
7 disp('mW',Pout*1000,"Pout="); //The answers vary due
    to round off error

```

Scilab code Exa 9.8 voltage gain

```

1  clc;
2  Rc=3000; //Ohm
3  re=25 //Ohm
4  Av=Rc/re;
5  disp(' ',Av,"Av="); //The answers vary due to round
    off error

```

Scilab code Exa 9.9 input impedance

```

1  clc;
2  re=22.3; //Ohm
3  Hfe=200;
4  Zbase=Hfe*re; //Ohm
5  R1=18000; //Ohm
6  R2=4700; //Ohm
7  Req=(R1*R2)/(R1+R2); //Ohm
8  Zin=(Req*Zbase)/(Req+Zbase); //Ohm
9  disp('kohm ',Zin/1000,"Zin="); //The answers vary due
    to round off error

```

Scilab code Exa 9.10 current gain

```

1  clc;
2  re=22.3; //Ohm
3  Hfe=200;
4  Zbase=Hfe*re; //Ohm
5  R1=18000; //Ohm
6  R2=4700; //Ohm
7  Req=(R1*R2)/(R1+R2); //Ohm
8  Zin=(Req*Zbase)/(Req+Zbase); //Ohm
9  rc=1150; //Ohm
10 RL=5000; //Ohm
11 Ai=Hfe*((Zin*rc)/(Zbase*RL));

```

```
12 disp(' ',Ai,"Ai="); //The answers vary due to round
    off error
```

Scilab code Exa 9.11 voltage gain

```
1 clc;
2 re=19.8; //Ohm
3 Hfe=200;
4 Zbase=Hfe*re; //Ohm
5 R5=15000; //Ohm
6 R6=2500; //Ohm
7 Req=(R5*R6)/(R5+R6); //Ohm
8 Zin=(Req*Zbase)/(Req+Zbase); //Ohm
9 R3=5000; //Ohm
10 rc=(R3*Zin)/(R3+Zin); //Ohm
11 Av=rc/re;
12 disp(' ',Av,"Av="); //The answers vary due to round
    off error
```

Scilab code Exa 9.12 Voltage gain for the two stage amplifier

```
1 clc;
2 R7=5000; //Ohm
3 RL=10000; //Ohm
4 rc=(R7*RL)/(R7+RL); //Ohm
5 re=17.4; //Ohm
6 Av2=rc/re;
7 Av1=53;
8 AvT=Av1*Av2;
9 disp(' ',AvT,"AvT="); //The answers vary due to round
    off error
```

Scilab code Exa 9.13 Voltage gain

```
1 clc;  
2 Ve=1.37; //Volt  
3 Re=910; //Ohm  
4 re=300; //Ohm  
5 Ie=Ve/(Re+re); //Ampere  
6 re1=0.025/Ie; //Ohm  
7 Rc=1500; //Ohm  
8 RL=10000; //Ohm  
9 rc=(Rc*RL)/(Rc+RL); //Ohm  
10 Av=rc/(re1+re);  
11 disp(' ',Av,"Av="); //The answers vary due to round  
    off error
```

Scilab code Exa 9.14 change in gain

```
1 clc;  
2 rc=1300; //Ohm  
3 re=2*22.1; //Ohm  
4 rE=300; //Ohm  
5 Av1=rc/(re+rE);  
6 Av2=4.04;  
7 DelAv=Av2-Av1;  
8 disp(' ',DelAv,"DelAv="); //The answers vary due to  
    round off error
```

Scilab code Exa 9.15 base impedance


```

1  clc;
2  re=25; //Ohm
3  Hfe=200;
4  Zbase=Hfe*re; //Ohm
5  rE=200; //Ohm
6  Zbase=Hfe*(re+rE); //Ohm
7  disp('kohm',Zbase/1000,"Zbase="); //The answers vary
   due to round off error

```

Scilab code Exa 9.16 Input ipedance

```

1  clc;
2  R1=10000; //Ohm
3  R2=2200; //Ohm
4  Zbase1=5000; //Ohm
5  Req=(R1*R2)/(R1+R2); //Ohm
6  Zin1=(Req*Zbase1)/(Req+Zbase1); //Ohm
7  Zbase2=45000; //ohm
8  Zin2=(Req*Zbase2)/(Req+Zbase2); //Ohm
9  disp('kohm',Zin1/1000,"Zin="); //The answers vary due
   to round off error
10 disp('kohm',Zin2/1000,"Zin="); //The answers vary due
    to round off error

```

Scilab code Exa 9.17 voltage gain

```

1  clc;
2  Rc=8000; //Ohm
3  Zin1=1330; //Ohm
4  rc1=(Rc*Zin1)/(Rc+Zin1); //Ohm
5  re=25; //Ohm
6  Zin2=1730; //Ohm
7  rc2=(Rc*Zin2)/(Rc+Zin2); //Ohm

```

```
8 re=25; //Ohm
9 Av1=rc1/re;
10 Av2=rc2/re;
11 disp(' ',Av1,"Av1="); //The answers vary due to round
    off error
12 disp(' ',Av2,"Av2="); //The answers vary due to round
    off error
```

Scilab code Exa 9.18 Input impedance and Voltage gain

```
1 clc;
2 Hfemin1=110;
3 Hfemax1=140;
4 Hfe=(Hfemin1*Hfemax1)^0.5;
5 Hiemin2=600; //Ohm
6 Hiemax2=800; //Ohm
7 Hie=(Hiemin2*Hiemax2)^0.5; //Ohm
8 rc=460; //Ohm
9 Av=(Hfe*rc)/Hie;
10 disp(' ',Av,"Av="); //The answers vary due to round
    off error
```

Chapter 10

Other BJT Amplifiers

Scilab code Exa 10.1 voltage and current

```
1  clc;
2  R1=20000; //Ohm
3  R2=20000; //Ohm
4  Vcc=10; //Volt
5  Vb=Vcc*(R2/(R1+R2)); //Volt
6  Ve=Vb-0.7; //Volt
7  Re=5000; //Ohm
8  Ie=Ve/Re; //Ampere
9  Vceq=Vcc-Ve; //Volt
10 disp('V',Vb,"Vb="); //The answers vary due to round
    off error
11 disp('V',Ve,"Ve="); //The answers vary due to round
    off error
12 disp('A',Ie,"Ie="); //The answers vary due to round
    off error
13 disp('V',Vceq,"Vceq="); //The answers vary due to
    round off error
```

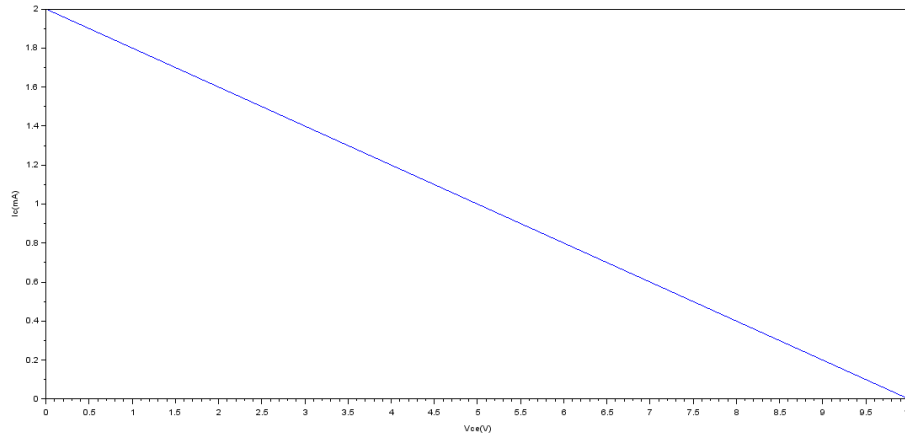


Figure 10.1: dc load line

Scilab code Exa 10.2 dc load line

```

1  clc;
2  Vcc=0.002; // Volt
3  Re=5000; //Ohm
4  Icsat=Vcc/Re; //Ampere
5  Vceoff=Vcc; //Volt
6  disp(' Amperes ',Icsat," Icsat=");
7  disp(' Volt ',Vceoff," Vceoff=");
8  T1=0:2:10 //Here on X-axis T1=Vce=10V
9  T2=2:-0.4:0; //Here on the Y-Axis T2=Ic=2miliAmpere
10 plot(T1,T2)
11 xlabel(' Vce(V) ')
12 ylabel(' Ic (mA) ')

```

Scilab code Exa 10.3 Voltage gain

```

1  clc;
2  Re=2000; //Ohm
3  RL=5000; //Ohm
4  rE=(Re*RL)/(Re+RL); //Ohm
5  Ie=0.031; //Ampere
6  re=0.025/Ie; //Ohm
7  Av=rE/(rE+re);
8  disp(' ',Av,"Av="); //The answers vary due to round
    off error

```

Scilab code Exa 10.4 power gain

```

1  clc;
2  //power gain of circuit
3  Ai=2.7;
4  Av=0.994;
5  Ap=Ai*Av;
6  disp(' ',Ap,"Ap=");

```

Scilab code Exa 10.5 Input and base impedance

```

1  clc;
2  re=8.1; //Ohm
3  rE=1430; //ohm
4  hfc=220;
5  Zbase=hfc*(re+rE); //Ohm
6  R1=25000; //Ohm
7  R2=33000; //Ohm
8  Req=(R1*R2)/(R1+R2); //Ohm
9  Zin=(Zbase*Req)/(Zbase+Req); //Ohm
10 disp('kohm',Zin/1000,"Zin="); //The answers vary due
    to round off error

```

Scilab code Exa 10.6 output impedance

```
1  clc;
2  hic=4000;
3  hfc=200;
4  re=hic/hfc; //Ohm
5  R1=3000; //Ohm
6  R2=4700; //Ohm
7  Req=(R1*R2)/(R1+R2); //Ohm
8  Rs=600; //Ohm
9  Rth=(Req*Rs)/(Req+Rs); //Ohm
10 Re=390; //Ohm
11 R=(re+(Rth/hfc)); //Ohm
12 Zout=(Re*R)/(Re+R); //Ohm
13 disp('Ohm',Zout,'Zout='); //The answers vary due to
    round off error
```

Scilab code Exa 10.7 Input impedance

```
1  clc;
2  hic=650; //Ohm
3  hfc=150;
4  re=hic/hfc; //Ohm
5  Re=2000; //Ohm
6  RL=8000; //Ohm
7  rE=(Re*RL)/(Re+RL); //Ohm
8  Zbase=hfc*(re+rE); //Ohm
9  R1=190000; //ohm
10 Zin1=(R1*Zbase)/(R1+Zbase); //Ohm//for emitter
    feedback
11 R1=30000; //Ohm
12 R2=39000; //Ohm
```

```

13 Req=(R1*R2)/(R1+R2); //Ohm
14 Zin2=(Zbase*Req)/(Zbase+Req); //Ohm //for voltage
    divider biased
15 disp('kOhm',Zin1/1000,"Zin1=");
16 disp('kOhm',Zin2/1000,"Zin2=");

```

Scilab code Exa 10.8 Input resistance

```

1 clc;
2 R2=120; //Ohm
3 R1=120; //Ohm
4 Vcc=10; //Volt
5 Vb=Vcc*(R2/(R1+R2)); //Volt
6 Re=3300; //Ohm
7 Vbe=0.7; //Volt
8 Ie=(Vb-2*Vbe)/Re; //Amperes
9 hfc1=70;
10 hfc2=70;
11 RE=3300; //Ohm
12 Rin1=hfc1*hfc2*RE; //Ohm//hfe=70 for current (Icq)
13 disp('MegaOhm',Rin1/1000000,"Rin1="); //The answers
    vary due to round off error

```

Scilab code Exa 10.9 circuit gain and impedance

```

1 clc;
2 Re=3300; //Ohm
3 RL=1000; //Ohm
4 rE=(Re*RL)/(Re+RL); //Ohm
5 hic1=40000; //Ohm
6 hfc1=120;
7 hic2=3000; //Ohm
8 hfc2=150;

```

```

 9 Zbase=hic1+hfc1*(hic2+(hfc2*rE)); //Ohm
10 R1=120000; //Ohm
11 R2=120000; //Ohm
12 Req=(R1*R2)/(R1+R2); //Ohm
13 Zin=(Zbase*Req)/(Zbase+Req); //Ohm//input impedance
14 re1=hic1/hfc1; //Ohm
15 re2=hic2/hfc2; //Ohm
16 R1=120000; //Ohm
17 R2=120000; //Ohm
18 Req=(R1*R2)/(R1+R2); //Ohm
19 Rs=3300; //Ohm
20 Rth=(Req*Rs)/(Req+Rs); //Ohm
21 Zout=re2+(re1+(Rth/hfc1))/hfc2; //Ohm//output
    impedance
22 Ai=(hfc1*hfc2)*((Zin*rE)/(Zbase*RL)); //current gain
23 disp(' ',Ai,"Ai="); Answer variation due to round of
    error

```

Scilab code Exa 10.10 gain and impedance

```

1  clc;
2  Vee=5; //Volt
3  Vbe=0.7; //Volt
4  Re=13000; //Ohm
5  Ie=0.000331 //Ampere
6  re=0.025/Ie; //Ohm
7  Zin=re; //Ohm
8  Rc=10000; //Ohm
9  Zout=Rc; //Ohm
10 RL=5100; //Ohm
11 rc=(RL*Rc)/(RL+Rc); //Ohm
12 Av=rc/re;
13 Ai=rc/RL;
14 disp(' ',Av,"Av=");
15 disp(' ',Ai,"Ai=");

```



```
16 disp('Ohm',Zin," Zin="); //The answers vary due to
    round off error
17
18 disp('Ohm',Zout," Zout="); //The answers vary due to
    round off error
```

Chapter 11

Power Amplifier

Scilab code Exa 11.1 Output compliance

```
1 clc;
2 Vceq=5.72; //Volt
3 PP1=2*Vceq; //Vpp(peak to peak voltage)
4 Icq=0.103; //Ampere
5 rc=25.7; //Ohm
6 PP2=2*Icq*rc; //Volt
7 disp('Vpp',PP1,"PP1="); //The answers vary due to
   round off error
8 disp('Vpp',PP2,"PP2="); //The answers vary due to
   round off error
```

Scilab code Exa 11.2 total dc power

```
1 clc;
2 Vcc=12; //Volt
3 R1=300; //Ohm
4 R2=100; //ohm
5 I1=Vcc/(R1+R2); //Ampere
```

```
6 Icq=0.103; //Ampere
7 Icc=Icq+I1; //Ampere
8 Ps=Vcc*Icc; //Watt
9 disp('W',Ps,'Ps='); //The answers vary due to round
  off error
```

Scilab code Exa 11.3 Ac load power

```
1 clc;
2 VL=10.6; //volt
3 RL=20; //Ohm
4 PL=VL^2/RL; //Watt
5 disp('W',PL,'PL='); //The answers vary due to round
  off error
```

Scilab code Exa 11.4 Ac load power

```
1 clc;
2 Vpk=20; //Volt
3 RL=75; //Ohm
4 PL=Vpk^2/(2*RL); //Watt
5 disp('W',PL,'PL='); //The answers vary due to round
  off error
```

Scilab code Exa 11.5 Ac load power

```
1 clc;
2 PP=36; //Vpp
3 RL=75; //Ohm
4 PLmax=PP^2/(8*RL); //Watt
```

```
5 disp('W',PLmax,"PLmax="); //The answers vary due to  
   round off error
```

Scilab code Exa 11.6 Maximum efficiency

```
1 clc;  
2 PP=5.29; //Vpp(Volt peak to peak))  
3 RL=75; //Ohm  
4 PL=PP^2/(8*RL); //Watt  
5 Ps=1.6; //Watt  
6 N=(PL/Ps)*100;  
7 disp('%',N,"N="); //The answers vary due to round off  
   error
```

Scilab code Exa 11.7 Maximum efficiency

```
1 Vcc=10; //Volt  
2 R1=470; //Ohm  
3 R2=110; //Ohm  
4 I1=Vcc/(R1+R2); //Ampere  
5 Icq=0.0976; //Ampere  
6 Icc=Icq+I1; //Ampere  
7 Ps=Vcc*Icc; //Watt  
8 Vceq=8.63; //Volt  
9 PP1=2*Vceq; //Volt  
10 rc=80; //Ohm  
11 PP2=2*Icq*rc; //Volt  
12 Ns=1;  
13 Np=4;  
14 Vpp=(Ns/Np)*PP2; //Volt  
15 RL=5;  
16 PLmax=Vpp^2/(8*RL); //Watt//maximum load power  
17 Ps=1.15 //Watt
```

```
18 H=(PLmax/Ps)*100;
19 disp( '%',H,"H="); //The answers vary due to round off
    error
```

Scilab code Exa 11.8 End point values for its ac load line

```
1 clc;
2 Vcc=10; //voltage
3 RL=10; //ohm
4 Icsat=Vcc/(2*RL); //Ampere
5 Vceoff=Vcc/2; //Volt
6 disp( 'mA',Icsat*1000," Icsat="); //The answers vary
    due to round off error
7
8 disp( 'V',Vceoff," Vceoff="); //The answers vary due to
    round off error
```

Scilab code Exa 11.9 Maximum load power

```
1 clc;
2 Vcc=12; //voltage
3 PP=Vcc; //voltage
4 RL=8; //ohm
5 PLmax=PP^2/(8*RL); //watt
6 disp( 'W',PLmax," PLmax="); //The answers vary due to
    round off error
```

Scilab code Exa 11.10 Total power demand

```
1 clc;
```

```

2 Vcc=15; //Volt
3 R1=1000; //Ohm
4 R2=170; //Ohm
5 R3=1000; //Ohm
6 I1=Vcc/(R1+R2+R3); //Ampere
7 RL=10; //Ohm
8 Icave=Vcc/(2*3.14*RL); //Ampere
9 Icc=Icave+I1; //Ampere
10 Ps=Vcc*Icc; //Watt
11 disp('W',Ps,'Ps='); //The answers vary due to round
    off error

```

Scilab code Exa 11.11 Maximum load power

```

1 clc;
2 PP=15; //Vpp(peak to peak voltage Volt)
3 RL=10; //Ohm
4 PLmax=PP^2/(8*RL); //Watt
5 disp('W',PLmax,'PLmax='); //The answers vary due to
    round off error

```

Scilab code Exa 11.12 Efficiency of Amplifier

```

1 clc;
2 PL=2.81; //Watt
3 Ps=3.69; //Watt
4 N=(PL/Ps)*100;
5 disp('%',N,'N='); //The answers vary due to round off
    error

```

Scilab code Exa 11.13 Efficiency of Amplifier

```
1  clc;
2  Vppout=7.5; //Volt
3  RL=10; //Ohm
4  Iceq=0.119; //Ampere
5  Icave=Vppout/(2*3.14*RL); //Ampere
6  I1=0.00691; //Ampere
7  Icc=Icave+I1; //Ampere
8  Vcc=15; //Volt
9  Ps=Vcc*Icc; //Watt
10 PLmax=Vppout^2/(8*RL); //Watt
11 N=(PLmax/Ps)*100;
12 disp('%',N,'N=');//The answers vary due to round off
    error
```

Scilab code Exa 11.14 Pd value

```
1  clc;
2  Icq=0.001; //Ampere
3  Vceq=5.3; //Volt
4  Pd=Icq*Vceq; //Watt
5  disp('mW',Pd*1000,'Pd=');//The answers vary due to
    round off error
```

Scilab code Exa 11.15 Pd value

```
1  clc;
2  Vpp=12; //Volt
3  RL=8; //Ohm
4  Pd=Vpp^2/(40*RL); //Watt
5  disp('mW',Pd*1000,'Pd=');//The answers vary due to
    round off error
```


Chapter 12

Field Effect Transistor

Scilab code Exa 12.1 Drain current

```
1 clc;  
2 Idss=0.003;  
3 Vgs=-2;  
4 Vgsoff=-6;  
5 Id=Idss*(1-(Vgs/Vgsoff))^2;  
6 disp('mA',Id*1000," Id=");//The answers vary due to  
   round off error
```

Scilab code Exa 12.2 Transconductance curve

```
1 clc;  
2 Idss=0.003;  
3 Vgs=[0 -1 -3 -5];  
4 Vgsoff=-6;  
5 Id=zeros(1,5);  
6 Id(1,1)=Idss*(1-(Vgs(1,1)/Vgsoff))^2;  
7 Id(1,2)=Idss*(1-(Vgs(1,2)/Vgsoff))^2;
```

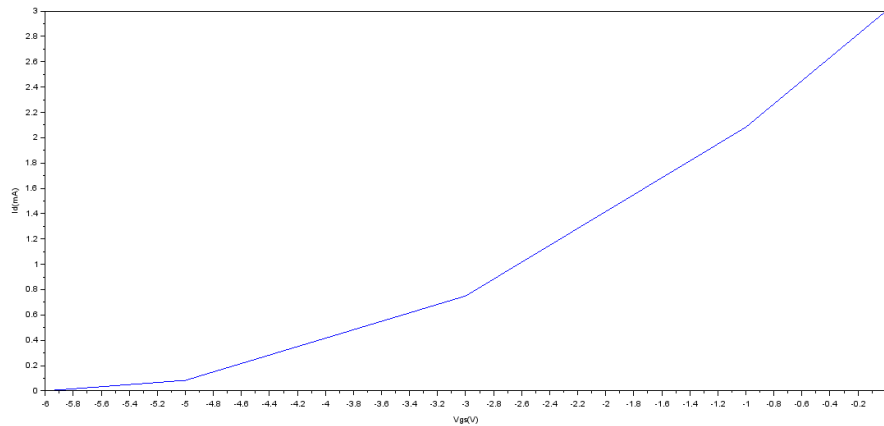


Figure 12.1: Transconductance curve

```

8 Id(1,3)=Idss*(1-(Vgs(1,3)/Vgs0ff))^2;
9 Id(1,4)=Idss*(1-(Vgs(1,4)/Vgs0ff))^2;
10 Vgs1=[0 -1 -3 -5 -6];
11 plot(Vgs1,Id*1000)
12 xlabel('Vgs(V)')
13 ylabel('Id(mA)')

```

Scilab code Exa 12.3 Two transduction plot

```

1 clc;
2 Vgs1=[-6 -4 -2 0];
3 Id1=[0 0.556 2.222 5];
4 Vgs2=[-0.5 -0.4 -0.2 0];
5 Id2=[0 0.04 0.36 1];
6 plot(Vgs1,Id1)
7 xgrid
8 set(gca(),"auto_clear","off")
9 plot2d(Vgs2,Id2)

```

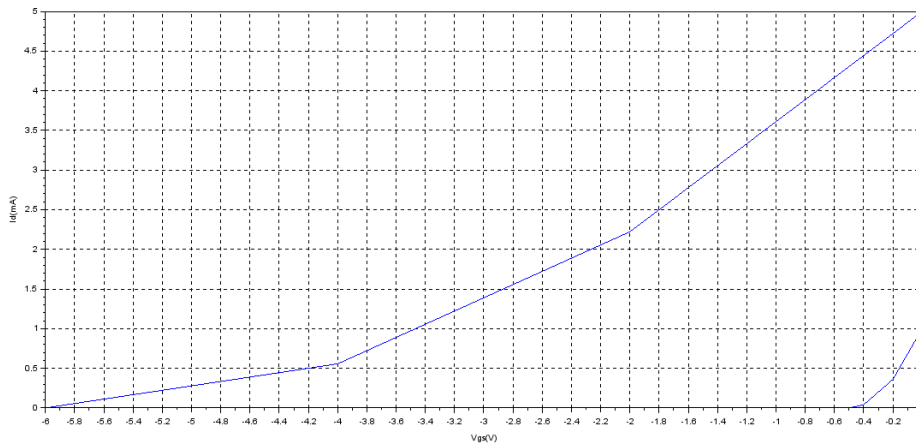


Figure 12.2: Two transconduction plot

```
10 xlabel('Vgs(V)')
11 ylabel('Id(mA)')
```

Scilab code Exa 12.4 Vgs Id and Vds determine

```
1  clc;
2  Vgs=-5;
3  Vgg=Vgs;
4  Idss=0.016;
5  Vgsoff=-8;
6  Id=Idss*(1-(Vgs/Vgsoff))^2;
7  Vdd=10;
8  Rd=2200;
9  VDS=Vdd-Id*Rd;
10 disp('V',Vgs,"Vgs=")
11 disp('mA',Id*1000,"Id=")
12 disp('V',VDS,"VDS=")
```

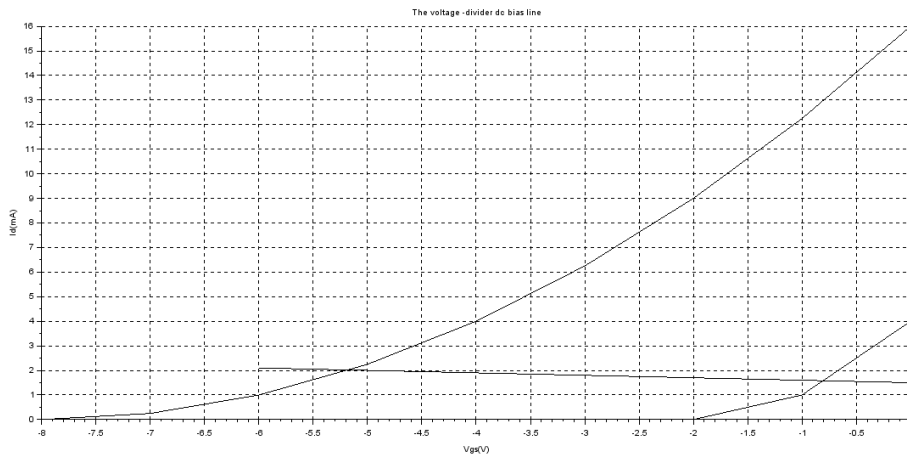


Figure 12.3: Plot dc bias line

Scilab code Exa 12.7 Dc characteristics of the amplifier

```

1  clc;
2  //from example 12.7 Idqmax and Idqmin
3  Idqmax=0.006;
4  Idqmin=0.0015;
5  Vdd=10;
6  Rs=500;
7  Rd=500;
8  Vdsqmax=Vdd-Idqmin*(Rs+Rd);
9  Vdsqmin=Vdd-Idqmax*(Rs+Rd);
10 disp('V',Vdsqmax,"Vdsqmax=")
11 disp('V',Vdsqmin,"Vdsqmin=")
12 disp('The value of Vdsq will fall between Vdsqmax
    and Vdsqmin')

```

Scilab code Exa 12.8 Plot dc bias line

```

1  clc;
2  R2=1500000;
3  R1=1500000;
4  Vdd=30;
5  Vg=Vdd*(R2/(R1+R2));
6  Rs=10000;
7  Id=Vg/Rs;
8  Vgsoff=-8;
9  Idss=0.016;
10 Vgs1=-8:1:0;
11 Id1=Idss*(1-(Vgs1/Vgsoff)).^2;
12 Vgsoff=-2;
13 Idss=0.004;
14 Vgs2=-2:1:0;
15 Id2=Idss*(1-(Vgs2/Vgsoff)).^2;
16 plot2d(Vgs1,Id1*1000)
17 xgrid
18 set(gca(),"auto_clear","off")
19 plot2d(Vgs2,Id2*1000)
20 set(gca(),"auto_clear","off")
21 Vgs3=-6:1:0;
22 Id3=((Vgs3.*-0.1)+1.5);
23 plot2d(Vgs3,Id3)
24 xlabel('Vgs(V)')
25 ylabel('Id(mA)')
26 xtitle('The voltage -divider dc bias line')

```

Scilab code Exa 12.9 Minimum And maximum Q point value

```

1  clc;
2  Idqmax=0.002;
3  Idqmin=0.0015;
4  Vgsmax=-5;
5  Vgsmin=-0.5;
6  Vdd=30;

```

```

7 R1=1500000;
8 R2=1500000;
9 Vg=Vdd*(R2/(R1+R2));
10 Vs=Vg-Vgsmax;
11 Rs=10000;
12 Idq1=Vs/Rs;
13 Idq2=(Vg-Vgsmin)/(Rs);
14 disp('mA', Idq1*1000, "Idq1=")
15 disp('mA', Idq2*1000, "Idq2=")
16 disp('Result Is verified ', , " ")

```

Scilab code Exa 12.10 Minimum and maximum value of Vdsq

```

1 clc;
2 Vdd=30;
3 Rd=1100;
4 Rs=10000;
5 Idq=[0.0015 0.002];
6 Vdsqmax=Vdd-Idq(1,1)*(Rd+Rs);
7 Vdsqmin=Vdd-Idq(1,2)*(Rd+Rs);
8 disp('V', Vdsqmax, "Vdsqmax=")
9 disp('V', Vdsqmin, "Vdsqmin=")

```

Scilab code Exa 12.11 Value of Gm

```

1 clc;
2 Vgs1=-3;
3 Vgs2=-5;
4 Gm0=0.006;
5 Vgsoff=-8;
6 Gm1=Gm0*(1-(Vgs1/Vgsoff));
7 Gm2=Gm0*(1-(Vgs2/Vgsoff));
8 disp('uS', Gm1*1000000, "Gm1=")

```

```
9 disp('uS', Gm2*1000000, 'Gm2=')
```

Scilab code Exa 12.12 Max and min value of voltage gain

```
1 Vgs1=-5;
2 Vgs2=-0.75;
3 Gm01=0.006;
4 Gm02=0.002;
5 Vgsoff1=-8;
6 Vgsoff2=-2;
7 Gm1=Gm01*(1-(Vgs1/Vgsoff1));
8 Gm2=Gm02*(1-(Vgs2/Vgsoff2));
9 RD=8200;
10 RL=100000;
11 rD=(RD*RL)/(RD+RL);
12 Avmax=rD*Gm1;
13 Avmin=rD*Gm2;
14 disp(' ', Avmax, 'Avmax=')//The answers vary due to
    round off error
15 disp(' ', Avmin, 'Avmin=')//The answers vary due to
    round off error
```

Scilab code Exa 12.13 Max and min gain voltage gain

```
1 clc;
2 rD=7580;
3 rS=2200;
4 Gm1=1/444;
5 Gm2=1/1000;
6 Avmax=rD/(rS+(1/Gm1));
7 Avmin=rD/(rS+(1/Gm2));
8 disp(' ', Avmax, 'Avmax=')//The answers vary due to
    round off error
```

```
9 disp(' ',Avmin,"Avmin=")//The answers vary due to  
round off error
```

Scilab code Exa 12.14 Input Impedance

```
1 clc;  
2 Hfe=200;  
3 re=22.7;  
4 R1=10000;  
5 R2=2200;  
6 Req=(R1*R2)/(R1+R2);  
7 X1=Hfe*re;  
8 ZinBJT=(Req*X1)/(Req+X1);  
9 ZinJFET=(R1*R2)/(R1+R2);  
10 disp('kOhm',ZinBJT/1000,"ZinBJT=")//The answers vary  
due to round off error  
11 disp('kOhm',ZinJFET/1000,"ZinJFET=")//The answers  
vary due to round off error
```

Scilab code Exa 12.15 Voltage gain

```
1 RD=8200;  
2 Zin=1290;  
3 rD1=(RD*Zin)/(RD+Zin);  
4 Gm=0.002;  
5 AvBJT=Gm*rD1;  
6 Zin=1800;  
7 rD2=(RD*Zin)/(RD+Zin);  
8 AvJFET=Gm*rD2;  
9 disp(' ',AvBJT,"AvBJT=")//The answers vary due to  
round off error  
10 disp(' ',AvJFET,"AvJFET=")//The answers vary due to  
round off error
```

Scilab code Exa 12.16 Minimum and maximum value of Voltage gain Output voltage

```
1  clc;
2  Vgs1=-0.5;
3  Vgs2=-5;
4  Gm01=0.002;
5  Gm02=0.006;
6  Vgsoff1=-2;
7  Vgsoff2=-8;
8  Gm1=Gm01*(1-(Vgs1/Vgsoff1));
9  Gm2=Gm02*(1-(Vgs2/Vgsoff2));
10 Rs=5100;
11 RL=20000;
12 rS=(Rs*RL)/(Rs+RL);
13 Avmin=rS/(rS+(1/Gm1));
14 Avmax=rS/(rS+(1/Gm2));
15 disp(' ',Avmax,"Avmax=")//The answers vary due to
    round off error
16 disp(' ',Avmin,"Avmin=")//The answers vary due to
    round off error
17 Gm11=1/667;
18 Gm22=1/444;
19 Zoutmax=(Rs/Gm11)/(Rs+(1/Gm11));
20 Zoutmin=(Rs/Gm22)/(Rs+(1/Gm22));
21 disp('Ohm',Zoutmax,"Zoutmax=")//The answers vary due
    to round off error
22 disp('Ohm',Zoutmin,"Zoutmin=")//The answers vary due
    to round off error
23 R1=1000000;
24 R2=1000000;
25 Zin=(R1*R2)/(R1+R2);
26 disp('KOhm',Zin/1000,"Zin=")//The answers vary due
    to round off error
```

Scilab code Exa 12.17 Min and Approximated value of Zout

```
1  clc;  
2  yos=0.00005;  
3  rd=1/yos; //minimum value  
4  Rd=1000;  
5  Zout=(Rd*rd)/(Rd+rd);  
6  disp('Ohm',Zout,"Zout=")//The answers vary due to  
   round off error
```

Chapter 13

MOSFETs

Scilab code Exa 13.1 Transconductance curve

```
1 clc ;
2 Vgs=-6:1:4;
3 Vgsoff=-6;
4 Idss=0.001;
5 Id=Idss*(1-(Vgs/Vgsoff)).^2;
6 plot(Vgs,Id*1000,'r')
7 xgrid
8 xlabel('Vgs(V)')
9 ylabel('Id(mA)')
```

Scilab code Exa 13.2 Drain current

```
1 Idon=0.01;
2 Vgson=10;
3 Vgsth=1.5;
4 k=Idon/(Vgson-Vgsth)^2;
5 Vdd=10;
```

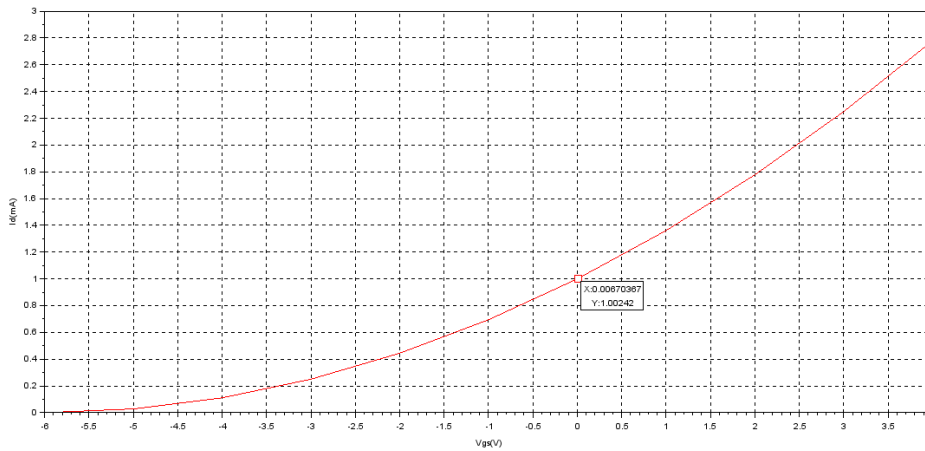


Figure 13.1: Transconductance curve

```

6 R2=1000000;
7 R1=1000000;
8 Vg=Vdd*(R2/(R1+R2));
9 Id=k*((Vg-Vgsth)^2);
10 disp('mA', Id*1000, " Id=") //The answers vary due to
    round off error

```

Scilab code Exa 13.3 Id and Vds

```

1 clc;
2 Vdd=20;
3 Id=0.01;
4 Rd=1000;
5 Vgs=Vdd-Id*Rd;
6 disp('V', Vgs, " Vgs=") //The answers vary due to round
    off error

```

Chapter 14

Amplifier Frequency Responce

Scilab code Exa 14.1 Bandwidth of the circuit

```
1 clc;
2 Fc1=30;
3 Fc2=275;
4 BW=Fc2-Fc1;
5 disp('kHz',BW,'BW=')//The answers vary due to round
  off error
```

Scilab code Exa 14.2 Geometric center frequency

```
1 clc;
2 fc1=30;
3 fc2=275;
4 f0=(fc1*fc2)^0.5; //geometric centre frequency
5 disp('kHz',f0,'f0=')//The answers vary due to round
  off error
```

Scilab code Exa 14.3 ratio of f0 and fc1 fc2 and f0

```
1 clc ;
2 fc1=30;
3 fc2=275;
4 f0=90.8;
5 ratio1=f0/fc1;
6 ratio2=fc2/f0;
7 disp('Ratio of f0/fc1 ',ratio1," ratio1=")//The
  answers vary due to round off error
8 disp('Ratio fof fc2/f0 ',ratio1," ratio1=")//The
  answers vary due to round off error
```

Scilab code Exa 14.4 Fc1 and bandwidth

```
1 clc ;
2 f0=60;
3 fc2=300;
4 fc1=(60)^2/(300);
5 BW=fc2-fc1;
6 disp('kHz ',BW,"BW=")//The answers vary due to round
  off error
7 disp('kHz ',fc1," fc1=")//The answers vary due to
  round off error
```

Scilab code Exa 14.5 fc2 and bandwidth

```
1 clc ;
2 f0=40;
3 fc1=8;
4 fc2=(f0)^2/(fc1);
5 BW=fc2-fc1;
```

```

ApT1dB=

    29.0309

dB

ApTdB=

    29.0309

dB

Proved total power gain ApT is equal to Ap1(dB)+Ap2(dB)+Ap3(dB).We have shown that
you can determine total multistage gain by adding the individual dB power gain
values

```

Figure 14.1: Value of fb1

```

6 disp('kHz',BW,"BW=")//The answers vary due to round
  off error
7 disp('kHz',fc2,"fc2=")//The answers vary due to
  round off error

```

Scilab code Exa 14.6 dB power gain of the amplifier

```

1 clc;
2 Pout=2;
3 Pin=0.0001;
4 ApdB=10*log10(Pout/Pin);
5 disp('dB',ApdB,"ApdB=")//The answers vary due to
  round off error

```

Scilab code Exa 14.7 Value of fb1

```

1 clc;

```

```

2 Ap1=100; //power gain at stage 1
3 Ap2=4; //power gain at stage 2
4 Ap3=2; //power gain at stage3
5 ApT=Ap1*Ap2*Ap3; //total power gain of a multistage
  amplifier
6 ApTdB=10*log10(ApT); //total power in dB
7 Ap1dB=10*log10(Ap1); //power gain at stage 1 in dB
8 Ap2dB=10*log10(Ap2); //power gain at stage 2 in dB
9 Ap3dB=10*log10(Ap3); //power gain at stage 3 in dB
10 ApT1dB=Ap1dB+Ap2dB+Ap3dB; ////total power in dB
11 disp('dB',ApT1dB,"ApT1dB=")//The answers vary due to
  round off error
12
13 disp('dB',ApTdB,"ApTdB=")//The answers vary due to
  round off error
14
15 if ApT1dB==ApTdB then
16     disp('Proved total power gain ApT is equal to
  Ap1(dB)+Ap2(dB)+Ap3(dB).We have shown that
  you can determine total multistage gain by
  adding the individual dB power gain values')
17 end

```

Scilab code Exa 14.8 F1b

```

1 clc;
2 R1=18000;
3 R2=4700;
4 Hie=4400;
5 Req=(R1*R2)/(R1+R2);
6 Rin=(Req*Hie)/(Req+Hie);
7 Rs=600;
8 C=0.000001;
9 fB1=1/(2*3.14*(Rs+Rin)*C);
10 disp('Hz',fB1,"fB1=")//The answers vary due to round

```


off error

Scilab code Exa 14.9 Value of Fc1

```
1 clc;
2 Rc=1500;
3 RL=5000;
4 C=0.00000022;
5 f1C=1/(2*3.14*(Rc+RL)*C);
6 disp('Hz',f1C,"f1C=")//The answers vary due to round
   off error
```

Scilab code Exa 14.10 f1E

```
1 clc;
2 R1=18000;
3 R2=4700;
4 Hie=600;
5 Req=(R1*R2)/(R1+R2);
6 Rth=(Req*Hie)/(Req+Hie);
7 hfc=201;
8 re=22;
9 Rout=re+(Rth/hfc);
10 Ce=0.00001;
11 f1E=1/(2*3.14*Rout*Ce);
12 disp('Hz',f1E,"f1E=")//The answers vary due to round
   off error
```

Scilab code Exa 14.11 Gain of the amplifier

```

1  clc;
2  Avmid=45;
3  fC1=2000;
4  f=500;
5  deltaAv=20*log10(1/(1+(fC1/f)^2)^0.5);
6  AvdB=Avmid+deltaAv;
7  disp('dB',AvdB,"AvdB=")//The answers vary due to
   round off error

```

Scilab code Exa 14.12 Value of Cbe

```

1  clc;
2  fT=300000000;
3  re=2.9;
4  //value of cbe
5  Cbe=1/(2*3.14*fT*re);
6  disp('Farad',Cbe,"Cbe=")//The answers vary due to
   round off error

```

Scilab code Exa 14.13 Miler input and output capacitance

```

1  clc;
2  Av=120;
3  Cbc=0.0000000000006;
4  CinM=Av*Cbc;
5  CoutM=Cbc;
6  disp('Farad',CinM,"CinM=")//The answers vary due to
   round off error
7  disp('pFarad',CoutM*1000000000000,"CoutM=")//The
   answers vary due to round off error

```

Scilab code Exa 14.14 Value of f2B

```
1 clc;
2 hfe=150;
3 rC=4000;
4 hie=3000;
5 Cbe=0.0000000000012;
6 Cbc=0.0000000000006;
7 Av=(hfe*rC)/hie;
8 CinM=Av*Cbc;
9 Rs=500;
10 Req=1000;
11 Rth=(Req*Rs)/(Req+Rs);
12 RX=(Rth*hie)/(Rth+hie);
13 f2B=1/(2*3.14*RX*(Cbe+CinM));
14 disp('kHz',f2B/1000,"f2B=")//The answers vary due to
    round off error
15 disp('The answers vary due to round off error', , " ")
    )
```

Scilab code Exa 14.15 Value of f2C

```
1 clc;
2 CoutM=0.0000000000006;
3 CL=0.0000000000720;
4 rC=4000;
5 f2C=1/(2*3.14*rC*(CoutM+CL));
6 disp('kHz',f2C/1000,"f2C=")//The answers vary due to
    round off error
```

Scilab code Exa 14.16 Lower input circuit cutoff frequency

```
1 clc;
```

```

2 //high input impedance of JFET
3 R1=18000;
4 R2=4700;
5 Rin=(R1*R2)/(R1+R2);
6 Rs=600;
7 Cc1=0.000001;
8 f1G=1/(2*3.14*(Rs+Rin)*Cc1);
9 disp('Hz',f1G,"f1G=")//The answers vary due to round
  off error

```

Scilab code Exa 14.17 Value f1G

```

1 clc;
2 //high input impedance of JFET
3 R1=18000000;
4 R2=4700000;
5 Rin=(R1*R2)/(R1+R2);
6 Rs=600;
7 Cc1=0.000001;
8 f1G=1/(2*3.14*(Rs+Rin)*Cc1);
9 disp('Hz',f1G,"f1G=")//The answers vary due to round
  off error

```

Scilab code Exa 14.18 Overall value of fc1

```

1 clc;
2 //high input impedance of JFET
3 R1=1500000;
4 R2=650000;
5 Rin=(R1*R2)/(R1+R2);
6 Rs=1000;
7 Cc1=0.00000001;
8 f1G=1/(2*3.14*(Rs+Rin)*Cc1);

```

```

9 Rd=5000;
10 RL=10000;
11 Cc2=0.00000001;
12 f1D=1/(2*3.14*(Rd+RL)*Cc2);
13 disp('Hz',f1G,"f1G=")//The answers vary due to round
    off error
14 disp('Hz',f1D,"f1D=")//The answers vary due to round
    off error

```

Scilab code Exa 14.19 Input miller capacitance

```

1 clc;
2 Cgd=0.00000000000004;
3 Gm=0.0025;
4 rD=5600;
5 CinM=Cgd*(Gm*rD+1);
6 disp('Farad',CinM,"CinM=")//The answers vary due to
    round off error

```

Scilab code Exa 14.20 f2G and f2D

```

1 clc;
2 Rin=454000;
3 Rs=1000;
4 Rth=(Rin*Rs)/(Rin+Rs);
5 Cgd=0.00000000000004;
6 Gm=0.004;
7 rD=3325;
8 CinM=Cgd*(Gm*rD+1);
9 Cgs=0.00000000000005;
10 Cg=Cgs+CinM;
11 Cg=0.00000000000622;
12 f2G=1/(2*3.14*Rth*Cg);

```

```

13 CoutM=0.0000000000004;
14 Cds=0.0000000000002;
15 CL=0.0000000000001;
16 Cd=CoutM+Cds+CL;
17 f2D=1/(2*3.14*rD*Cd);
18 disp('MHz',f2G/1000000,"f2G=")//The answers vary due
    to round off error
19 disp('MHz',f2D/1000000,"f2D=")//The answers vary due
    to round off error

```

Scilab code Exa 14.21 Cds Cgd and Cgs

```

1 clc;
2 Crss=0.0000000000001;
3 Cgd=Crss;
4 Ciss=0.0000000000005;
5 Cgs=Ciss-Crss;
6 Coss=0.0000000000002;
7 Cds=Coss-Crss;
8 disp('Farad',Cgd,"Cgd=");
9 disp('Farad',Cds,"Cds=");
10 disp('Farad',Cgs,"Cgs=");

```

Scilab code Exa 14.22 fc2 for the two stage amplifier

```

1 clc;
2 fC2=500000;
3 fC2T=fC2*(2^0.5-1)^0.5;
4 disp('kHz',fC2T/1000,"fC2T=");

```

Scilab code Exa 14.23 fc1 for the two stage amplifier

```
1 clc;  
2 fc1=5000;  
3 fc1T=fc1/(20.5-1)0.5;  
4 disp('kHz ',fc1T/1000,"fc1T=");
```

Chapter 15

Operational Amplifiers

Scilab code Exa 15.1 Output voltage polarity

```
1 clc;  
2 V1=2;  
3 V2=[4 0];  
4 Vdiff1=V2(1,1)-V1;  
5 Vdiff2=V2(1,2)-V2;  
6 disp('V',Vdiff1," Vdiff1=");  
7 disp('V',Vdiff2," Vdiff2=");
```

Scilab code Exa 15.2 Peak to peak output voltage

```
1 clc;  
2 Av=150;  
3 Vin=0.100;  
4 Vout=Av*Vin;  
5 V1=10;  
6 V2=-10;  
7 Vpk1=V1-1;  
8 Vpk2=V2+1;
```



```
9 disp('V+', Vpk1, " Vpk1=");
10 disp('V-', Vpk2, " Vpk1=");
```

Scilab code Exa 15.3 Maximum Allowable value of vin

```
1 clc;
2 Av=200;
3 Vout=8;
4 Vin=Vout/Av;
5 V1=6;
6 V2=-6;
7 Vpk1=V1-2;
8 Vpk2=V2+2;
9 disp('V+', Vpk1, " Vpk1=");
10 disp('V-', Vpk2, " Vpk1=");
11 disp('mVpp', Vin*1000, " Vin=");
```

Scilab code Exa 15.4 Maximum input and output voltage

```
1 clc;
2 Av=121;
3 Vout=4;
4 Vin=Vout/Av;
5 V1=4;
6 V2=-4;
7 Vpk1=V1-2;
8 Vpk2=V2+2;
9 disp('V+', Vpk1, " Vpk1=");
10 disp('V-', Vpk2, " Vpk1=");
11 disp('mVpp', Vin*1000, " Vin=");
```

Scilab code Exa 15.5 Maximum operating frequency

```
1 clc;
2 slewrate=500000;
3 Vpk=8;
4 fmax=slewrate/(2*3.14*Vpk);
5 disp('kHz',fmax/1000,"fmax=");
```

Scilab code Exa 15.6 Maximumn operating frequency

```
1 clc;
2 slewrate=500000;
3 Vpk=0.001;
4 fmax=slewrate/(2*3.14*Vpk);
5 disp('Hz',fmax,"fmax=");
6 //The provided in the textbook is wrong
```

Scilab code Exa 15.7 Complete analysis

```
1 clc;
2 Rf=100000;
3 Rin=10000;
4 AcL=Rf/Rin;
5 Zin=Rin;
6 AcM=0.001;
7 CMRR=AcL/AcM;
8 Vin=1;
9 Vout=AcL*Vin;
10 slewrate=500000;
11 Vpk=5;
12 fmax=slewrate/(2*3.14*Vpk);
13 disp(' ',AcL,"AcL="); //The answers vary due to round
    off error
```

```

14
15 disp(' ',CMRR,"CMRR="); //The answers vary due to
    round off error
16
17 disp('Vpp',Vout,"Vout="); //The answers vary due to
    round off error
18
19 disp('kHz',fmax/1000,"fmax="); //The answers vary due
    to round off error

```

Scilab code Exa 15.8 Analysis of non inverting amplifier

```

1 clc;
2 Rf=100000;
3 Rin=10000;
4 AcL=(Rf/Rin)+1;
5 Acm=0.001;
6 CMRR=AcL/Acm;
7 Vin=1;
8 Vout=AcL*Vin;
9 slewrate=500000;
10 Vpk=5.5;
11 fmax=slewrate/(2*3.14*Vpk);
12 disp(' ',AcL,"AcL="); //The answers vary due to round
    off error
13
14 disp(' ',CMRR,"CMRR="); //The answers vary due to
    round off error
15
16 disp('Vpp',Vout,"Vout="); //The answers vary due to
    round off error
17
18 disp('kHz',fmax/1000,"fmax="); //The answers vary due
    to round off error

```

Scilab code Exa 15.9 Analysis of voltage follower

```
1  clc;
2  AcL=1;
3  AcM=0.001;
4  CMRR=AcL/AcM;
5  slewrate=500000;
6  Vpk=3;
7  fmax=slewrate/(2*3.14*Vpk);
8  disp(' ',AcL,"AcL=");//The answers vary due to round
   off error
9  disp(' ',CMRR,"CMRR=");//The answers vary due to
   round off error
10 disp('kHz',fmax/1000,"fmax=");//The answers vary due
    to round off error
```

Scilab code Exa 15.10 Bandwidth and AcL

```
1  clc;
2  funity=15000000;
3  Ac1=500;
4  fc=funity/Ac1;
5  BW=fc;
6  fc1=200000;
7  AcL=funity/fc1;
8  disp('kHz',fc/1000,"fc=");//The answers vary due to
   round off error
9  disp(' ',AcL,"AcL=");//The answers vary due to round
   off error
```

Scilab code Exa 15.12 Value of AcL

```
1 clc;
2 AoL=150000;
3 av=0.005;
4 AcL=AoL/(1+(av*AoL));
5 disp(' ',AcL," AcL="); //The answers vary due to round
   off error
```

Scilab code Exa 15.13 Value of feedback

```
1 clc;
2 Rf=120000;
3 Rin=1500;
4 AcL=(Rf/Rin)+1;
5 av=1/AcL;
6 AoL=150000;
7 A=1+av*AoL;
8 disp('Feedback factor ',A,"A="); //The answers vary
   due to round off error
```

Scilab code Exa 15.14 Amplifier input impedance

```
1 clc;
2 AcL=151;
3 av=1/AcL;
4 AoL=180000;
5 A=1+av*AoL;
6 Zin=5000000;
7 Zinf=Zin*A;
8 disp('ohm ',Zinf," Zinf="); //The answers vary due to
   round off error
```

Scilab code Exa 15.15 Amplifier Output

```
1 clc;  
2 Zout=80;  
3 avAoL=1180;  
4 Zoutf=Zout/(1+avAoL);  
5 disp('mohm',Zoutf*1000 ,” Zoutf=”); //The answers vary  
    due to round off error
```

Chapter 16

Additional Op Amp Applications

Scilab code Exa 16.1 Output voltage

```
1  clc;  
2  Vin=4.999;  
3  Vref=5;  
4  Vdiff1=Vin-Vref;  
5  AoL=150000;  
6  Vout1=AoL*Vdiff1;  
7  V=10;  
8  VoutL1=-V+1;  
9  //assume RL>10000 ohm  
10 Vin=5.001;  
11 Vref=5;  
12 Vdiff2=Vin-Vref;  
13 Vout2=AoL*Vdiff2;  
14 VoutL2=9;  
15 //again assume RL.1000  
16 disp('Noninverting input at +4.999 ', , " ");  
17 disp('mV', Vdiff1*1000, " Vdif1=");  
18 disp('V', Vout1, " Vout1=");  
19 disp('V', VoutL1, " VoutL1=");
```

```
20 disp('Noninverting input at +5.001 ', , " ");
21 disp('V',Vout2," Vout2=");
22 disp('V',VoutL2," VoutL2=");
23 disp('mV',Vdiff2*1000," Vdif1=");
```

Scilab code Exa 16.2 Reference voltage for comparator

```
1 clc;
2 V=5;
3 R2=30000;
4 R1=120000;
5 Vref=V*(R2/(R1+R2));
6 disp('V',Vref," Vref=");
```

Scilab code Exa 16.4 Output voltage of summing amplifier

```
1 clc;
2 v1=3;
3 v2=6;
4 v3=4;
5 rf=10000;
6 r1=10000;
7 r2=10000;
8 r3=10000;
9 Vout=-rf*((v1/r1)+(v2/r2)+(v3/r3));
10 disp('V',Vout," Vout=");
```

Scilab code Exa 16.5 output voltage

```
1 clc;
```



```
2 v1=10;
3 v2=8;
4 v3=7;
5 rf=1000;
6 r1=10000;
7 r2=10000;
8 r3=10000;
9 Vout=-rf*((v1/r1)+(v2/r2)+(v3/r3));
10 disp('V',Vout," Vout=");
```

Scilab code Exa 16.6 Output voltage

```
1 clc;
2 rf=1000;
3 r1=1000;
4 r2=2000;
5 r3=4000;
6 v1=[10 0 10];
7 v2=[0 10 10];
8 v3=[10 0 10];
9 for i=1:3
10 Vout(1,i)=(rf/r1)*v1(1,i)+(rf/r2)*v2(1,i)+(rf/r3)*v3
    (1,i);
11 end
12 disp('V',Vout(1,1)," Vout(1,1)=");
13 disp('V',Vout(1,2)," Vout(1,2)=");
14 disp('V',Vout(1,3)," Vout(1,3)=");
```

Chapter 17

Tuned Amplifiers

Scilab code Exa 17.1 Q of a tuned amplifier

```
1 clc;  
2 f0=1000000;  
3 BW=40000;  
4 Q=f0/BW;  
5 disp('V',Q,"Q=");
```

Scilab code Exa 17.2 Bandwidth

```
1 clc;  
2 f0=1000000;  
3 BW=40000;  
4 Q=f0/BW;  
5 disp('V',Q,"Q=");
```

Scilab code Exa 17.3 f0 fave and Q determine

```

1 fc1=960000;
2 fc2=1440000;
3 BW=480000;
4 f0=ceil((fc1*fc2)^0.5);
5 fave=(fc1+fc2)/2;
6 Q=f0/BW;
7 disp('kHz',f0/1000,"f0=");
8 disp('kHz',fave/1000,"fave=");
9 disp(' ',Q,"Q="); //The answers vary due to round off
                    error in f0

```

Scilab code Exa 17.4 Bandwidth of low pass filter

```

1 clc;
2 r1=33000;
3 c1=0.00000001;
4 fc=1/(2*3.14*r1*c1);
5 rf1=4700;
6 rf2=9100;
7 AcL=(rf1/rf2)+1;
8 disp('Hz',fc,"fc=");
9 disp(' ',AcL,"AcL"); //The answers vary due to round
                        off error in f0

```

Scilab code Exa 17.5 Bandwidth of filter

```

1 clc;
2 r1=10000;
3 r2=10000;
4 c1=0.000000015;
5 c2=0.000000033;
6 fc=floor(1/(2*3.14*(r1*r2*c1*c2)^0.5));
7 disp('Hz',fc,"fc=");

```

Scilab code Exa 17.6 Complete frequency analysis

```
1  clc;
2  r1=10000;
3  r2=10000;
4  c1=0.00000001;
5  c2=0.00000002;
6  fc2=ceil(1/(2*3.14*(r1*r2*c1*c2)^0.5));
7  r3=15000;
8  r4=30000;
9  c3=0.00000001;
10 c4=0.00000001;
11 fc1=1/(2*3.14*(r3*r4*c3*c4)^0.5);
12 BW=(fc2-fc1);
13 f0=(fc2*fc1)^0.5;
14 Q=(f0/BW);
15 disp('Hz',fc2,"fc2="); //The answers vary due to
    round off error
16 disp('Hz',fc1,"fc1="); //The answers vary due to
    round off error
17 disp('Hz',BW,"BW="); //The answers vary due to round
    off error
18 disp(' ',Q,"Q="); //The answers vary due to round off
    error
```

Scilab code Exa 17.7 f0 value

```
1  clc;
2  r1=10000;
3  r2=10000;
4  rf=40000;
```

```

5 req=(r1*r2)/(r1+r2);
6 c1=0.0000001;
7 c2=0.000000068;
8 f0=ceil(1/(2*3.14*((req*c1*c2*rf)^0.5)));
9 disp('Hz',f0,"f0=");

```

Scilab code Exa 17.8 Q and bandwidth

```

1 clc;
2 c1=0.0000001;
3 c2=0.000000068;
4 c=(c1*c2)^0.5;
5 rf=40000;
6 f0=137;
7 Q=(3.14*f0*rf*c);
8 BW=f0/Q;
9 disp(' ',Q,"Q=");
10 disp('Hz',BW,"BW=");

```

Scilab code Exa 17.9 Percentage of error

```

1 clc;
2 f0=12000;
3 BW=6000;
4 Q=2;
5 fc1=f0-BW/2;
6 fc2=f0+BW/2;
7 fc11=ceil(f0*((1+(1/((2*Q)^2)))^0.5)-BW/2);
8 fc22=f0*(1+(1/(2*Q)^2))^0.5+BW/2;
9 Fc1=((fc11-fc1)/fc11)*100;
10 Fc2=((fc22-fc2)/fc22)*100;
11 disp('%',Fc1,"Fc1="); //The answers vary due to round
    off error

```

```
12 disp( '%',Fc2," Fc2="); //The answers vary due to round
    off error
```

Scilab code Exa 17.10 Percentage of error and approximated values

```
1 clc;
2 f0=100;
3 Q=1.02;
4 BW=floor(f0/Q);
5 fc1=ceil(f0-BW/2);
6 fc2=floor(f0+BW/2);
7 fc11=floor(f0*((1+(1/((2*Q)^2)))^0.5)-BW/2);
8 fc22=floor((f0*(1+(1/((2*Q)^2)))^0.5)+BW/2);
9 Fc1=((fc11-fc1)/fc11)*100;
10 Fc2=((fc22-fc2)/fc22)*100;
11 disp( '%',Fc1," Fc1="); //The answers vary due to round
    off error
12 disp( '%',Fc2," Fc2="); //The answers vary due to round
    off error
```

Scilab code Exa 17.11 close loop voltage gain

```
1 clc;
2 rf=40000;
3 r2=10000;
4 AcL=rf/(2*r2);
5 disp( '%',AcL," AcL="); //The answers vary due to round
    off error
```

Scilab code Exa 17.12 f0 for tuned amplifier

```
1 clc;
2 L=0.001;
3 C=0.00000000001;
4 f0=1/(2*3.14*(L*C)^0.5);
5 disp('Hz',floor(f0/1000),'f0=');//The answers vary
   due to round off error
```

Scilab code Exa 17.13 Q for the tank

```
1 clc;
2 XL=3160;
3 Rw=25;
4 Q=XL/Rw;
5 disp(' ',Q,'Q=');//The answers vary due to round off
   error
```

Scilab code Exa 17.14 loaded Q

```
1 clc;
2 Q=126;
3 Rw=25;
4 Rp=(Q^2)*Rw;
5 XL=3160;
6 rc=20000;
7 QL=rc/XL;
8 disp(' ',ceil(Rp/1000),'Rp=');//The answers vary due
   to round off error
9 disp(' ',QL,'QL=');//The answers vary due to round
   off error
```

Scilab code Exa 17.15 Bandwidth of the amplifier

```
1 clc;
2 f0=503000;
3 QL=6.33;
4 BW=f0/QL;
5 disp('khz ',BW,"BW="); //The answers vary due to round
    off error
```

Chapter 18

Oscillators

Scilab code Exa 18.1 av value

```
1  clc;
2  c1=0.0000000033;
3  c2=0.0000001;
4  L=0.000047;
5  cT=(c1*c2)/(c1+c2);
6  fr=1/(2*3.14*(L*cT)^0.5);
7  Xc1=117; //for fr value
8  Xc2=3.87;
9  av1=Xc2/Xc1;
10 av2=c1/c2;
11 disp('using equation 18.3 ',av1," av1="); //The answers
    vary due to round off error
12 disp('using equation 18.4 ',av2," av2="); //The answers
    vary due to round off error
```

Chapter 19

Solid State Switching Circuits

Scilab code Exa 19.1 Minimum high input voltage

```
1  clc;
2  vcc=12;
3  Rc=1200;
4  Icsat=vcc/Rc;
5  hfe=100;
6  Ib=Icsat/hfe;
7  Rb=47000;
8  vbe=0.7;
9  Vpk=(Ib*Rb)+vbe;
10 disp('V',Vpk,"Vpk="); //The answers vary due to round
    off error
```

Scilab code Exa 19.2 high and low output voltage

```
1  clc;
2  Vdd1=5;
3  Idss=0.005;
4  Rd1=1000;
```

```

5 Vout1=Vdd1-(Idss*Rd1);
6 Vdd=5;
7 Id=0;
8 Rd=1000;
9 Vout2=Vdd-(Id*Rd);
10 disp('V',Vout1,"Vout1="); //The answers vary due to
    round off error
11 disp('V',Vout2,"Vout2="); //The answers vary due to
    round off error

```

Scilab code Exa 19.3 Output voltage

```

1 clc;
2 Vdd=10;
3 Idss1=0.002;
4 Rd1=1000;
5 Rd2=100;
6 Vout1=Vdd-(Idss1*Rd1);
7 Vout2=Vdd-(Idss1*Rd2);
8 disp('V',Vout1,"Vout1="); //The answers vary due to
    round off error
9 disp('V',Vout2,"Vout2="); //The answers vary due to
    round off error

```

Scilab code Exa 19.4 PW And T

```

1 clc;
2 PW=2.5*0.000050;
3 T=6.5*0.000050;
4 disp('uS',PW*1000000,"PW="); //The provided in the
    textbook is wrong
5 disp('uS',T*1000000,"T="); //The provided in the
    textbook is wrong

```

Scilab code Exa 19.5 duty cycle

```
1 clc;
2 PW=0.000125;
3 T=0.000325;
4 dutycycle=(PW/T)*100;
5 disp('%',dutycycle," dutycycle="); //The provided in
   the textbook is wrong
```

Scilab code Exa 19.6 fc and practical limit on frequency

```
1 clc;
2 tr=0.000000040;
3 fc=0.35/tr;
4 tf=0.000000030;
5 fmax=0.35/(100*tr);
6 disp('MHz',fc/1000000," fc="); //The provided in the
   textbook is wrong
7 disp('kHz',fmax/1000," fmax="); //The provided in the
   textbook is wrong
```

Scilab code Exa 19.7 UTP and LTP for the circuit

```
1 clc;
2 Rin=20000;
3 rf=100000;
4 Vout1=-12;
5 Vout2=12;
6 Vin=2.4;
```

```

7 UTP=-(Rin/rf)*Vout1;
8 LTP=-(Rin/rf)*Vout2;
9 Vrin=(Vin-Vout1)*(Rin/(Rin+rf));
10 disp('V',UTP,"UTP="); //The answers vary due to round
    off error
11 disp('V',LTP,"LTP="); //The answers vary due to round
    off error
12 disp('V',Vrin,"Vrin="); //The answers vary due to
    round off error

```

Scilab code Exa 19.8 UTP and LTP for non inverting schmit

```

1 clc;
2 Rin=3300;
3 rf1=11000;
4 rf2=33000;
5 Vout1=-11;
6 Vout2=11;
7 UTP=-(Rin/rf1)*(Vout1+0.7);
8 LTP=-(Rin/rf2)*(Vout2-0.7);
9 disp('V',UTP,"UTP="); //The answers vary due to round
    off error
10 disp('V',LTP,"LTP="); //The answers vary due to round
    off error

```

Scilab code Exa 19.9 UTP and LTP

```

1 clc;
2 rf2=1000;
3 rf1=2000;
4 req=(rf2/(rf1+rf2));
5 UTP=req*9;
6 LTP=req*-9;

```

```
7 disp('V',UTP,"UTP="); //The answers vary due to round
  off error
8 disp('V',LTP,"LTP="); //The answers vary due to round
  off error
```

Scilab code Exa 19.10 pulse width

```
1 clc;
2 r=1200;
3 c=0.0000001;
4 PW=1.1*r*c;
5 disp('ms',PW*1000000,"PW="); //The answers vary due
  to round off error
```

Scilab code Exa 19.11 values of VT

```
1 clc;
2 Vcon=6;
3 Vcc=12;
4 VT1=(1/2)*Vcon;
5 VT2=(1/3)*Vcc;
6 disp('V',VT1,"VT1="); //The answers vary due to round
  off error
7 disp('V',VT2,"VT2="); //The answers vary due to round
  off error
```

Scilab code Exa 19.12 value f0 and duty cycle

```
1 clc;
2 ra=3000;
```

```
3 rb=2700;
4 c1=0.000000033;
5 f0=(1.44/((ra+2*rb)*c1));
6 dutycycle=((ra+rb)/(ra+2*rb))*100;
7 PW=0.693*((ra+rb)*c1);
8 disp('kHz',f0/1000,"f0=");//The answers vary due to
   round off error
9 disp('%',dutycycle,"dutycycle=");//The answers vary
   due to round off error
10 disp('mS',floor(PW*1000000),"PW=");//The answers
   vary due to round off error
```

Chapter 20

Thyristors and Optoelectronics Devices

Scilab code Exa 20.1 Current surge

```
1 clc;  
2 t=0.018;  
3 I=50;  
4 D=(I^2)*t;  
5 if (D <= 145) then  
6     disp('device can handle this surge');  
7 end
```

Scilab code Exa 20.2 duration of surge

```
1  
2 clc;  
3 D=60; //I^2*t(rated) value  
4 Is=100;  
5 tmax=(D)/(Is)^2;  
6 disp('ms',tmax*1000,"tmax="); //The answers vary due  
    to round off error
```

Scilab code Exa 20.3 highest surge current

```
1 clc;
2 D=60; //I^2*t(rated) value
3 ts=0.020;
4 Ismax=(D/ts)^0.5;
5 disp('A',Ismax,"Ismax="); //The answers vary due to
    round off error
```

Scilab code Exa 20.4 noise amplitude for false triggering

```
1 clc;
2 R2=2400;
3 R1=240;
4 Vdc=(1.25)*((R2/R1)+1);
5 disp('V',Vdc,"Vdc="); //The answers vary due to round
    off error
```

Scilab code Exa 20.5 Maximum peak voltage

```
1 clc;
2 n=0.8;
3 Vbb=18;
4 Vp=(n*Vbb+0.7);
5 disp('V',Vp,"Vp="); //The answers vary due to round
    off error
```

Scilab code Exa 20.6 wavelength

```
1 clc ;  
2 c=3*10^(17) ;  
3 f=150*10^(12) ;  
4 lemda=c/f ;  
5 disp( 'nm' ,lemda ,”lemda=” ) ;
```

Chapter 21

Discrete and Integrated voltage Regulators

Scilab code Exa 21.1 line regulation

```
1 clc;  
2 Vout=0.000010;  
3 Vin=5;  
4 linein=Vout/Vin;  
5 disp('uV/V',linein*1000000,"linein="); //The answers  
    vary due to round off error
```

Scilab code Exa 21.2 load regulation

```
1 clc;  
2 vn1=5;  
3 vf1=4.9998;  
4 I1=0.020;  
5 loadre=(vn1-vf1)/I1;  
6 disp('uA/mA',loadre*100,"loadre="); //The answers  
    vary due to round off error
```

Scilab code Exa 21.3 allowable input voltage

```
1 clc;
2 Vout=8;
3 Vd=40;
4 Vin=Vout+Vd;
5 disp('V',Vin,"Vin="); //The answers vary due to round
    off error
```

Scilab code Exa 21.4 regulated dc output

```
1 clc;
2 R2=2400;
3 R1=240;
4 Vdc=(1.25)*((R2/R1)+1);
5 disp('V',Vdc,"Vdc="); //The answers vary due to round
    off error
```

Scilab code Exa 21.5 dc average of the load voltage

```
1 Ton=0.000005;
2 Toff=0.000010;
3 Vin=24;
4 Vave=Vin*(Ton/(Ton+Toff));
5 disp('V',Vave,"Vave="); //The answers vary due to
    round off error
```
