

Scilab Textbook Companion for
An Introduction to Electrical Machines and
Transformers
by G. Mcphersion¹

Created by
Rohan Singla
Electrical Technology
Electrical Engineering
Thapar University
College Teacher
None
Cross-Checked by
Spandana

July 30, 2019

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: An Introduction to Electrical Machines and Transformers

Author: G. Mcpherson

Publisher: John Wiley, NY

Edition: 2

Year: 1990

ISBN: 978-0-471-63529-1

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 What machines and transformers have in common	5
2 Synchronous Machines	10
3 Transformers	20
4 Induction or Asynchronous Machines	39
5 Direct Current Machines	52
6 Single Phase Machines	58
8 Forces And Torques In Electromagnetic Systems	63

List of Scilab Codes

Exa 1.1	Find efficiency of the 5 horsepower three induction motor operating at half load and also find power lost as heat	5
Exa 1.2	Calculate efficiency and output power when losses are 365 Watts in Example1	6
Exa 1.3	Find hysteresis loss in core A and B	6
Exa 1.4	Find voltage induced at 30Hz eddycurrent loss at 60Hz hysteresis loss at 60Hz	7
Exa 1.5	Find the kVA load for the transformer to operate at maximum efficiency	8
Exa 1.6	Find full load speed regulation of the motor	9
Exa 1.7	Find voltage regulation for unity power factor and zero point seven pf lagging	9
Exa 2.1	Find flux per pole off the synchronous machine	10
Exa 2.2	Determine the coil pitch and pitch factor . .	10
Exa 2.3	If the armature winding is star connected find the phase voltage on line to line basis	11
Exa 2.4	1Find horsepower being delivered to the pump2Rheostat setting for motor to operate at zero point 8 power factor leading3kVAR supplied by motor at zero point eight power factor leading .	12
Exa 2.5	Find new plant power factor and percent decrease in line current from improved power factor	13
Exa 2.6	What should be the kVAR rating of a synchronous condenser to correct the original power factor to zero point 9	15

Exa 2.7	Calculate the excitation requirement for the alternator	16
Exa 2.8	Find field current and open circuit voltage and maximum kVAR	17
Exa 2.10	Find initial current and current at the end of two cycles	18
Exa 3.1	1Voltage to be applied to the transformer to result in rated voltage at secondary terminals 2Calculate the coupling factors and coefficient of coupling	20
Exa 3.2	1Find the turns ratio a 2primary and secondary induced voltages E1 and E2 3primary current and secondary voltages	21
Exa 3.3	1Find the secondary current 2primary current and impedance seen by the line 3Output power and volt amperes and input power and volt amperes	23
Exa 3.4	Find turns ratio of transformer and voltage levels on application of 10 W power to the speaker	24
Exa 3.5	Find core and copper losses and efficiency .	25
Exa 3.6	Find the primary terminal voltage	26
Exa 3.7	Find the primary voltage required to induce 240 volts at secondary terminals at full load when supplying zero point eight pf lagging and leading	28
Exa 3.8	Find the full voltage regulation at zero point eight pf lagging and leading	29
Exa 3.9	Find voltage regulation at full load and zero point eight pf lagging	30
Exa 3.10	Find the ratings and turns ratio of a three phase transformer to transform 10000kVA from 230kV to 4160V	30
Exa 3.11	Find the voltage regulation at full load and zero point eight pf lagging	32
Exa 3.12	Find Magnitude of current in secondary of each transformer	34
Exa 3.13	Find efficiency of transformer for a power factor of zero point nine at full load and half load	35

Exa 3.14	Open circuit and short circuit test on transformer	36
Exa 4.1	Calculate air gap power and developed mechanical power and output power and efficiency	39
Exa 4.2	Find slip and operating speed and developed torque and output torque	40
Exa 4.3	Calculate performance at 1746 rev per min and starting current and torque	41
Exa 4.4	Find the pull out torque and slip at which it occurs	44
Exa 4.5	Find speed at half of the load and the corresponding outpt in horsepower	45
Exa 4.6	Will the mootor run hotter or cooler if voltage drops to 90 percent	46
Exa 4.7	Calculate performance of motor at given slip	47
Exa 4.8	Upper limit of the starting current at 230v .	50
Exa 4.9	Find the starting line current and torque with provided compensation	50
Exa 5.1	Find out the power developed and the torque and determination of mode of operation of the machine	52
Exa 5.2	Find torque developed by the motor and speed and armature curent for a torque of 300 Newton metre	53
Exa 5.3	Find speed of the motor when it develops a torque of 300 Newton metre	54
Exa 5.4	Find the terminal voltage at full load and no load and voltage regulation	55
Exa 5.5	Find the efficiency and input horsepower requirements under given conditions	56
Exa 6.1	Find the performance of a single phase motor under provided conditions	58
Exa 6.2	Calculate the starting torque for the motor under provided parametres	59
Exa 8.2	1Find forces on plunger at 1A rms 2Voltage applied for the current to flow 3Force for a coil current of 1 A	63

Chapter 1

What machines and transformers have in common

Scilab code Exa 1.1 Find efficiency of the 5 horsepower three induction motor operating at half load

```
1  clc
2
3  horsepower=2.5 //rating of induction motor in
    horsepower at half load
4  V1=230 //terminal voltage of motor in volts
5  I1=7 //load current of motor in amperes
6  pf=0.8 //power factor of the machine
7  Pin=sqrt(3)*V1*I1*pf //input power in watts
8  mprintf(" Pin=%f W\n",Pin)//The answer may vary due
    to roundoff error
9  Whp=746 //watts per hp
10 Pout=horsepower*Whp //output power in watts
11 mprintf(" Pout=%f W\n",Pout)
12 mprintf(" Efficiency=%f\n",Pout/Pin)//The answer may vary due
    to roundoff error //efficiency of the machine
13 mprintf(" Losses=Pin-Pout=%f W\n",Pin-Pout)//The
    answer may vary due to roundoff error //losses in
    the machine in watts
```

Scilab code Exa 1.2 Calculate efficiency and output power when losses are 365 Watt

```
1 clc
2
3 //the below exmaple is an extension of Ex1_1.sce
4 V1=230 //terminal voltage of machine in volts
5 I1=7 //current drawn by machine in amperes
6 pf=0.8 //power factor of machine
7 Pin=sqrt(3)*V1*I1*pf //from Ex1_1 //input power in
   watts
8 Losses=365 //in watts
9 Pout=Pin-Losses //output power in watts
10 Whp=746 //watts per hp
11 mprintf("  =1-(Losses/Input)=%f\n",1-(Losses/Pin))
   //The answer may vary due to roundoff error //
   efficiency of the machine
12 mprintf(" Pout=%f W\n",Pout)//The answer may vary due
   to roundoff error
13 mprintf(" Pout=%fhp",Pout/Whp)//The asnwer may vary
   due to roundoff error //output power in
   horsepower
```

Scilab code Exa 1.3 Find hysteresis loss in core A and B

```
1 clc
2 f=60 //frequency of voltage source in Hz
3 x=1.9 //Steinmetz coefficient
4 V=80 //applied sinusoidal voltage in volts
5 t=100 //no of turns wound on a coil
6 hc=500 //hysteresis coefficient
7 w=2*pi*f //angular frequency in rads/sec
```

```

8 phimax=(sqrt(2)*V)/(t*w)//maximum value of flux in
   the core in webers
9 mprintf(" phimax=%fWb\n",phimax)//the answer may vary
   due to roundoff error
10 A1=0.0025 //cross-sectional area of core in metre
   square
11 Bmax1=phimax/A1 //flux density in core A in tesla
12 mprintf(" Bmax=%fT\n",Bmax1)//the answer may vary due
   to roundoff error
13 lfe1=0.5 //mean flux path length of core A in meters
14 VolA=A1*lfe1 //volume of core A in metre cube
15 mprintf(" VolA=%f metre cube\n",VolA)
16 //for core A
17 Ph1=VolA*f*hc*(Bmax1^x) //hysteresis loss in core A
   in watts
18 mprintf(" Ph=%f W\n",Ph1)//the answer may vary due to
   roundoff error
19 //for core B
20 A2=A1*3 //cross sectional area of core B in metre
   square
21 lfe2=0.866 //mean flux path length of core B in
   metres
22 Bmax2=phimax/A2 //flux density in core B in tesla
23 VolB=A2*lfe2 //volume of core B in metre cubes
24 Ph2=VolB*f*hc*(Bmax2^x) //hysteresis loss of core B
   in watts
25 mprintf(" Ph=%f W\n",Ph2)//the answer may vary due to
   roundoff error

```

Scilab code Exa 1.4 Find voltage induced at 30Hz eddycurrent loss at 60Hz hysteresis

```

1 clc
2 V1=240 //voltage applied to a winding of transformer
   (three phase) in volts
3 f1=60 //initial applied frequency in Hz

```

```

4 f2=30 //reduced frequency in Hz
5 Phe1=400 //core loss in watts at f1 frequency
6 Phe2=169 //core losses in watts at f2 frequency
7 mprintf("V2=%dV\n", (f2*V1)/f1) //voltage at 30 Hz
  frequency
8 mprintf("Ph+e/f=Ch+Ce*f\n") //equation for
  claculating hysteresis and eddy current loss
  coefficients
9 a=[1 f1;1 f2] //left hand side matix for the
  equation above
10 b=[Phe1/f1;Phe2/f2] //right hand side matrix for the
  equation above
11 c=inv(a)*b
12 Ch=c(1,:) //hysteresis loss coefficient in W/Hz
13 Ce=c(2,:) //eddy current loss coefficient in W/(Hz*Hz
  )
14 mprintf("Ph=%fW\n", Ch*f1) //ans may vary due to
  roundoff error //hysteresis loss in watts at 60
  Hz
15 mprintf("Pe=%fW\n", Ce*f1*f1) //ans may vary due to
  roundoff error //eddy current loss at 60 Hz in
  watts

```

Scilab code Exa 1.5 Find the kVA load for the transformer to operate at maximum ef

```

1 clc
2 Pk=75 //core loss of transfoer in watts
3 R=0.048 //internal resistance in ohms
4 V2=240 // secondary voltage in volts
5 I2=sqrt(Pk/R) //secondary current in amperes
6 mprintf(" I2=%f A\n", I2) //ans may vary due to
  roundoff error
7 mprintf(" |S|=V2*I2=%d VA", V2*I2) //The answer in the
  textbook is wrong //output volt ampere of
  transformer

```

Scilab code Exa 1.6 Find full load speed regulation of the motor

```
1 clc
2 sfl=1746 //speed at full load in rev/min
3 snl=1799.5 //speed at no load in rev/min
4 mprintf(" Voltage Regulation=%f" ,(snl-sfl)/sfl) //the
   ans may vary due to round of error
```

Scilab code Exa 1.7 Find voltage regulation for unity power factor and zero point

```
1 clc
2 Vn1=27.3 //no load voltage in volts
3 Vf11=24 //full load voltage at power factor 1 in
   volts
4 mprintf(" (Vn1-Vf1/Vf1)=%f\n" ,(Vn1-Vf11)/Vf11) //ans
   may vary due to roundoff error
5 Vf12=22.1 //full load voltage at power factor 0.7 in
   volts
6 mprintf(" Voltage Regulation=%f" ,(Vn1-Vf12)/Vf11)
```

Chapter 2

Synchronous Machines

Scilab code Exa 2.1 Find flux per pole off the synchronous machine

```
1 clc
2 L=0.25 //length of stator stack in metre
3 r=0.15 //radius of stator stack in metres
4 BImax=0.96 //peak value of air gap flux density in
   tesla
5 P=6 //no of machine poles
6 phi=(4*L*r*BImax)/P //flux per pole in webers
7 mprintf(" =%fWb",phi)
```

Scilab code Exa 2.2 Determine the coil pitch and pitch factor

```
1 clc
2 //the example below is an extension of Ex2_1
3 L=0.25 //length of stator stack in metres
4 r=0.15 //radius of stator stack in metres
5 BImax=0.96 //peak value of air gap flux density in
   tesla
6 P=6 //no of machine poles
```

```

7 phi=(4*L*r*BImax)/P //flux per pole in webers
8 //above comes from Ex2_1
9 span=5 //span of each coil given by no of slots
10 edps=30 //electrical degrees per slot in degrees
11 p=span*edps//coil pitch in degrees
12 mprintf("p=%d \n",span*edps)
13 Nc=2//turns of coil
14 Kp=sin(((p/2)*%pi)/180) //pitch factor //degree
    being converted to radians before calculation
15 mprintf("Kp=sin(p/2)=%f\n",Kp) //the ans may vary
    due to roundoff error
16 mprintf(" cmax =Nc*Kp*   =%fWb turns\n",Nc*Kp*phi)//
    max flux linkage //ans may vary due to roundoff
    error
17 ns=1000 //machine speed in rev/min
18 p=6 //no of poles
19 f=(p*ns)/120 //frequency at given speed in Hertz
20 mprintf(" f=%dHz\n",f)
21 mprintf("Ec=sqrt(2)*   *f*Nc*kp*   =%fV\n",sqrt(2)*%pi
    *f*Nc*Kp*phi)//ans may vary due to roundoff error
    //voltage induced at above frequency

```

Scilab code Exa 2.3 If the armature winding is star connected find the phase volta

```

1 clc
2 //the example below is an extension of Ex2_1 and
    Ex2_2
3 S1=36 //no of slots
4 q1=3 //no of phases
5 p=6 //no of poles
6 Nc=2 //no of turns per coil
7 L=0.25 //length of stator stack in metres
8 r=0.15 //radius of stator stack in metres
9 BImax=0.96 //peak value of air gap flux density in
    tesla

```

```

10 P=6 //no of machine poles
11 phi=(4*L*r*BImax)/P //flux per pole in webers
12 span=5 //span of each coil given by no of slots
13 edps=30 //electrical degrees per slot in degrees
14 p=span*edps//coil pitch in degrees
15 Nc=2//turns of coil
16 kp=sin(((p/2)*%pi)/180) //pitch factor //degree
    being converted to radians before calculation
17 ns=1000 //machine speed in rev/min
18 p=6 //no of poles
19 f=(p*ns)/120 //frequency at given speed in Hertz
20 Ec=sqrt(2)*%pi*f*Nc*kp*phi//voltage induced at above
    frequency
21 n=S1/(q1*p)
22 mprintf("n=S1/(q1*p)=%f\n",n) //coils per group
23 edps=30 //electrical degrees per slot //equal to
    as per textbook
24 kd=(sin((n*edps*%pi)/(180*2)))/(n*sin((edps/2)*%pi
    /180)) //distribution factor of the machine //
    degree converted to radian for calculation
25 mprintf("kd=sin(n* /2)/n*sin( /2)=%f\n",kd)//ans
    may vary due to roundoff error
26 mprintf("|Egroup|=n*Ec*kd=%fV\n",n*Ec*kd)//ans may
    vary due to roundoff error
27 mprintf("| E | =p*|Egroup|=%fV\n",p*n*Ec*kd)//ans may
    vary due to roundoff error
28 mprintf("sqrt(3)* E =%dV\n",sqrt(3)*n*Ec*kd*p)//ans
    may vary due to roundoff error
29 stp=n*Nc*p //series turns per phase //equal to N
    in textbook
30 mprintf(" N =n*Nc*p=%dturns\n",stp)
31 mprintf("| E | =sqrt(2)* * N * f* *kp*kd=%fV",sqrt
    (2)*%pi*stp*f*kp*kd*phi) //ans may vary due to
    round off error //induced phase winding

```

Scilab code Exa 2.4 1Find horsepower being delivered to the pump2Rheostat setting

```
1 clc
2 V1=2300 //terminal voltage of synchronous motor in
    volts
3 I1=8.8 //minimum line current in ampere
4 P=sqrt(3)*V1*I1
5 mprintf("P=%fKW\n",P/1000)//power drawn from the
    line //ans may vary due to round off error
6 pf=0.8 //operating power factor
7 mprintf("HP=P/746=%fhp\n",P/746)//ans may vary due
    to round off error //conversion of power to hp
    requires division by 746
8 S=P/(pf*1000) //total volt amperes of motor in kVA
9 mprintf("Q=|S| sin    m=|S| sin cos -1(pf)=%fkVAR",S*
    sin(acos(pf))) //kVAR supplied by motor to the
    system //ans may vary due to roundoff error
```

Scilab code Exa 2.5 Find new plant power factor and percent decrease in line current

```
1 clc
2 //the following code contains userdefined fucntion
    complexstring
3 function s=complexstring(a)
4
5     if imag(a)>=0 then
6         s=sprintf(' %g+%gi',real(a),imag(a))
7     else
8         s=sprintf(' %g%gi',real(a),imag(a))
9
10    end
11    funcprot(0)
12 endfunction
13 Load=5000 //load of the plant in kW
14 pf1=0.8 //power factor of load(lagging)
```



```

15 pf2=0.9 //power factor of induction motor
16 pf3=0.8 //power factor of synchronous motor
17 Hp=500 //rating of induction motor to be replaced in
    hp
18 Pout=0.746*Hp //output power of induction motor in
    kW
19 Eta=0.96 //efficiency of the induction motor equal
    to in textbook
20 Sp=Load+(Load*tan(acos(pf1)))*%i //original complex
    power of load in kVA
21 disp('Sp=' + complexstring(Sp)+'kVA')
22 Pin=Pout/Eta //input power in kW
23 mprintf(" Pin=%fkW\n",Pin)//complex power of
    induction motor //the ans may vary due to round
    off error
24 Sm=Pin+(Pin*tan(acos(pf2)))*%i
25 disp('Sm=' +complexstring(Sm)+'kVA')//the ans may
    vary due to round off error //complex power of
    induction motor
26 mprintf("\n")
27 Ss=Pin-(Pin*tan(acos(pf3)))*%i
28 disp('Ss=' +complexstring(Ss)+'kVA')//complex power
    of synchronous machine //the ans may vary due to
    round off error
29 mprintf("\n")
30 Qm=(Pin*tan(acos(pf2)))*%i//reactive power of
    induction motor in kVAR
31 Qs=(-1*(Pin*tan(acos(pf3)))*%i)//reactive power of
    synchronous motor in kVAR
32 Sp1=Sp-Qm+Qs
33 disp('Sp1=' +complexstring(Sp1)+'kVA')//new plant
    requirement ,equal to Sp' in textbook
34 mprintf("\n")
35 pha=acos(real(Sp1)/abs(Sp1)) //phase angle of Sp1 in
    radians
36 mprintf("New power factor=%f\n",cos(pha))//new power
    factor //the ans may vary due to round off error
37 invl=abs(Sp)//initial value of complex power in kVA

```

```

38 fnvl=abs(Sp1) //final value of complex power in kVA
39 mprintf("Percent reduction=%f%c\n",(((invl-fnvl)/
    invl)*100),'%')//the ans may vary due to round
    off error

```

Scilab code Exa 2.6 What should be the kVAR rating of a synchronous condenser to c

```

1  clc
2  //the example below is an extension of Ex2_5
3  //the following code contains userdefined fucntion
    complexstring
4  function s=complexstring(a)
5
6      if imag(a)>=0 then
7          s=sprintf('%g+%gi',real(a),imag(a))
8      else
9          s=sprintf('%g%gi',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 Load=5000 //load of the plant in kW
15 pf1=0.8 //power factor of load(lagging)
16 Sp=Load+(Load*tan(acos(pf1)))*%i //original complex
    power of load in kVA
17 disp('Sp='+complexstring(Sp)+'kVA')
18 pf2=0.9 //new power factor
19 Qp1=real(Sp)*tan(acos(0.9)) //reactive power, equal
    to Qp' in textbook
20 mprintf("Qp'=%fkVAR\n",Qp1)//the ans vary due to
    roundoff error
21 Qp=imag(Sp)
22 mprintf("Qs=%fkVAR",Qp1-Qp)//KVAR to be supplied by
    synchronous condenser

```

Scilab code Exa 2.7 Calculate the excitation requirement for the alternator

```
1  clc
2
3  //the code below uses userdefined complexstring
   function
4  function s=complexstring(a)
5
6
7      if imag(a)>=0 then
8          s=sprintf('%g+%gi',real(a),imag(a))
9      else
10         s=sprintf('%g%gi',real(a),imag(a))
11
12     end
13     funcprot(0)
14 endfunction
15 VLB=2400 //line to base voltage in volts
16 V1=VLB/sqrt(3) //reference phasor in volts //ans
   may vary due to roundoff error
17 mprintf("V1=%fV\n",V1)
18 kVAB=9375 //rated kVA
19 I1B=(kVAB*1000)/(sqrt(3)*VLB)
20 pf=0.8 //power factor
21 mprintf("I1B=%fA\n",I1B) //ans may vary due to
   roundoff error
22 I1=I1B*exp((-1)*%i*(acos(pf)))
23 disp('I1='+complexstring(I1)+'A')//ans may vary due
   to roundoff error
24 mprintf("\n")
25 x1=0.1//in ohms
26 disp('E =V1+jI1x1='+complexstring(V1+%i*I1*x1)+'V')
   //ans may vary due to roundoff error
27 mprintf("\n")
```

```

28 disp('sqrt3 * | E | = ' + complexstring((abs(V1+%i*I1*x1))
    *sqrt(3))+ 'V')
29 Ifu=110 //value in ampere,dc
30 Ifs=149 //value in ampere,dc
31 ks=Ifs/Ifu
32 mprintf(" ks=%f\n",ks) //ans may vary due to roundoff
    error
33 m1=(abs((V1+%i*I1*x1)))/Ifs //equal to m' in
    textbook
34 mprintf(" m = | E | / Ifs = %f \n",m1) //ans may vary
    due to roundoff error
35 xdu=0.8 //in ohms
36 xd=x1+((xdu-x1)/ks)
37 mprintf(" xd=x1+(xdu-x1)/ks=%f \n",xd) //ans may vary
    due to roundoff error
38 Ef=V1+(%i*I1*xd)
39 disp('Ef=' + complexstring(Ef)+ 'V') //ans may vary due
    to roundoff error
40 mprintf("\n")
41 mprintf(" If=%fA\n",abs(Ef)/m1) //ans may vary due to
    roundoff error

```

Scilab code Exa 2.8 Find field current and open circuit voltage and maximum VAR

```

1 clc
2 VLB=2400 //line to base voltage in volts
3 Ix=2005 //current in amperes
4 xda=VLB/(sqrt(3)*Ix)
5 mprintf(" xda=%f \n",xda) //ans may vary due to
    roundoff error
6 Ifv=116 //current in amperes
7 ma1=VLB/(sqrt(3)*Ifv) //equal to ma' in textbook
8 mprintf(" ma = VLB/Ifv = %f \n",ma1) //ans may vary due
    to roundoff error
9 //from ex 2_7

```

```

10 V1=VLB/sqrt(3) //reference phasor in volts
11 kVAB=9375 //rated kVA
12 I1B=(kVAB*1000)/(sqrt(3)*VLB)//current in amperes
13 pf=0.8 //power factor
14 I1=I1B*exp((-1)*%i*(acos(pf)))//current in amperes
15 Ef=V1+%i*I1*xda
16 disp('Ef=' + string(Ef) + 'V')//ans may vary due to
    roundoff error
17 mprintf(" If=|Ef|/ ma =%fA\n",abs(Ef)/ma1)//ans may
    vary due to roundoff error
18 Voc=2960 //line to line volatge in Volts
19 mprintf(" V1oc=%fV\n",Voc/sqrt(3))//ans may vary due
    to roundoff error
20 If=240 //current in amperes
21 Efmax=ma1*If
22 mprintf(" Efmax=%dV\n",Efmax)//ans in textbook is
    wrong
23 I1max=(Efmax-V1)/xda //ans in textbook is wrong
24 mprintf(" I1max=%fA\n",I1max)//ans may vary due to
    roundoff error
25 mprintf(" Qmax=%fMVAR",sqrt(3)*VLB*I1max*(10^-6))//
    ans may vary due to roundoff error

```

Scilab code Exa 2.10 Find initial current and current at the end of two cycles

```

1 clc
2 xd=1 //in ohms per unit
3 xd1=0.3 //in ohms per unit
4 xd2=0.2 //in ohms per unit
5 Td2=0.03 //time in seconds
6 Td1=1 //time in seconds
7 MVA=100 //rating in mega volt ampere
8 V=16000 //voltage in volts
9 I2pu=1/xd2
10 mprintf(" I p u    =%dper unit\n",I2pu)

```

```

11 Ib=(MVA*(10^6))/(sqrt(3)*V)
12 mprintf(" Ib=%fA\n",Ib)//ans may vary due to roundoff
    error
13 mprintf(" I    =%fA\n",I2pu*Ib)//ans in textbook is
    wrong
14 I1=1/xd1 //current in per unit
15 mprintf(" I  =Efo/xd =%fper unit\n",I1)//ans may
    vary due to roundoff error
16 Iss=1/xd//current in per unit
17 mprintf(" Iss=Efo/xd=1 per unit\n")
18 t=2/60 //time in seconds
19 mprintf(" I=%fper unit\n", (I2pu-I1)*exp(-t/Td2)+(I1-
    Iss)*exp(-t/Td1)+1)//ans may vary due to roundoff
    error
20 t=10 //time in seconds
21 mprintf(" I=%fper unit\n", (I2pu-I1)*exp(-t/Td2)+(I1-
    Iss)*exp(-t/Td1)+1)//ans may vary due to roundoff
    error

```

Chapter 3

Transformers

Scilab code Exa 3.1 1Voltage to be applied to the transformer to result in rated v

```
1  clc
2  //code uses userdefined function complexstring
3  function s=complexstring(a)
4
5
6      if imag(a)>=0 then
7          s=sprintf( '%g+%gi', real(a), imag(a))
8      else
9          s=sprintf( '%g%gi', real(a), imag(a))
10
11      end
12      funcprot(0)
13  endfunction
14  r2=0.02;
15  X11=20 //in ohm
16  x1=0.05 //in ohm
17  X22=2000 //in ohm
18  x2=5 //in ohm
19  Xm1=X11-x1
20  Xm2=X22-x2
21  mprintf("Xm1=X11-x1=%f \n", Xm1)
```

```

22 mprintf("Xm2=X22—x2=%f \n",Xm2)
23 X12=sqrt(Xm1*Xm2)
24 mprintf("X12=sqrt(Xm1*Xm2)=%f \n",X12) //ans may
    vary due to roundoff error
25 kVA=10 //rated kVA
26 V2=1000 //secondary voltage in volts
27 I2=(kVA*(10^3))/V2 //rated current
28 mprintf("I2=ratedkVA*1000/raated V2=%dA\n",I2)
29 Z1=V2/I2 //load impedance
30 I1=((Z1+r2+(%i*X22))*I2)/(%i*X12) //ans may vary due
    to roundoff error
31 disp('I1=(Z1+r2+jwL22)*I2/wL12*I1=' + complexstring(I1
    )+ 'A')
32 r1=0.01 //in ohm
33 V1=((r1+(%i*X11))*I1)-( %i*X12*I2)
34 disp('V1=(r1+jwL11)I1-jwL12I2=' + complexstring(V1)+ 'V
    ') //ans may vary due to roundoff error
35 k1=Xm1/X11
36 k2=Xm2/X22
37 mprintf("k1=%f\n",k1)
38 mprintf("k2=%f\n",k2)
39 k=sqrt(k1*k2)
40 mprintf("k=sqrt(k1*k2)=%f\n",k)

```

Scilab code Exa 3.2 1Find the turns ratio a 2primary and secondary induced voltage

```

1 clc
2 //code contains user defined function complexstring
3 function s=complexstring(a)
4
5
6     if imag(a)>=0 then
7         s=sprintf('%g+%gi',real(a),imag(a))
8     else
9         s=sprintf('%g%gi',real(a),imag(a))

```



```

10
11     end
12     funcprot(0)
13 endfunction
14 i2=141.4 //load current max val in amperes
15 r2=0.02 //secondary resistance in ohms
16 V2=707/sqrt(2)
17 pha=-30 //phase angle of load current with reference
        with reference voltage in degrees
18 I2=(i2/sqrt(2))*exp(%i*pha*3.14/180) //ans may vary
        due to roundoff error ,conversion of degrees in
        radian for calculation
19 mprintf("V2=%dV\n",V2)
20 disp('I2='+complexstring(I2)+'A')
21 disp('Secondary drop I2r2 is='+complexstring(I2*r2)+
        'V') //ans may vary due to roundoff error
22 L12=3*(10^(-4)) //secondary leakage inductance in
        henry
23 w=377 //angular frequency of the supply in rad/sec
24 x2=w*L12 //secondary leakage reactance
25 mprintf("x2=%f \n",x2)
26 E12=(I2*%i*x2) //ans may vary due to roundoff error
27 disp('-E12=I2jx2='+complexstring(E12)+'V')
28 E2=V2+(r2+(%i*x2))*I2 //ans may vary due to roundoff
        error
29 disp('E2='+complexstring(E2)+'V')
30 N1=300 //primary winding turns
31 N2=30 //secondary turns
32 a=N1/N2
33 mprintf("a=N1/N2=%d\n",a)
34 E1=a*E2 //ans may vary due to roundoff error
35 disp('E1=aE2='+complexstring(E1)+'V')
36 Iex1=0.707 //magnitude of exciting current of
        transformer in amperes
37 paex=-80 //phase angle of exciting current in
        degrees with reference voltage
38 Iex=(Iex1/sqrt(2))*exp(%i*paex*3.14/180) //ans may
        vary due to roundoff error ,conversion of degrees

```

```

    to radians for calculation
39 I1=(I2/a)+Iex//ans may vary due to roundoff error
40 disp('I1='+complexstring(I1)+'A')
41 mprintf("Actual ratio=I2/I1=%f\n",abs(I2)/abs(I1))//
    ans may vary due to roundoff error
42 L11=0.03 //leakage inductance of primary in henry
43 E11=%i*w*L11*I1//ans may vary due to roundoff error
44 disp('E11=jwL11I1='+complexstring(E11)+'V')
45 r1=2 //primary winding resistance in ohms
46 I1r1=I1*r1//ans may vary due to roundoff error
47 disp('I1r1='+complexstring(I1r1)+'V')
48 V1=E1+I1r1+E11//ans may vary due to roundoff error
49 disp('V1=E1+I1r1+E11='+complexstring(V1)+'V')
50 mprintf("Actual voltage ratio is V1/V2=%f\n",abs(V1)
    /abs(V2))//ans may vary due to roundoff error

```

Scilab code Exa 3.3 1Find the secondary current 2primary current and impedance see

```

1 clc
2 //the code uses userdefined function complexstring
3 function s=complexstring(a)
4
5
6     if imag(a)>=0 then
7         s=sprintf('%g+%gi',real(a),imag(a))
8     else
9         s=sprintf('%g%gi',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 E1=2400 //primary voltage rating in volts
15 E2=240 //secondary voltage rating in volts
16 z=2 //magnitude of impedance connected to secondary
    terminals in ohms

```

```

17 pha1=36.9 //phase angle of impedance connected with
    reference in degrees
18 a=E1/E2
19 mprintf("a=%d\n",a)
20 V1=2200 // applied primary voltage to transformer in
    volts
21 V2=V1/a
22 mprintf(" |V2|=|V1|/a=%dV\n",V2)
23 I2=V2/(z*exp(pha1*%i*3.14/180))//ans in textbook is
    wrong,conversion of degree to radian for
    calculation
24 disp('I2='+complexstring(I2)+'A')
25 I1=I2/a //ans may vary due to roundoff error
26 disp('I1=I2/a='+complexstring(I1)+'A')
27 Zin=V1/I1
28 disp('Zin=V1/I1='+complexstring(Zin)+' ')
29 S2=V2*I2
30 pf=0.8 //power factor of load
31 mprintf(" |S2|=|V2| | I2|=%fkVA\n", (abs(V2)*abs(I2))
    /1000)
32 mprintf(" P2=|S2|*cos 2=%fkW\n", (abs(S2)*pf)/1000)
33 mprintf(" |S1|=|V2| | I1|=%fkVA\n", (abs(V1)*abs(I1))
    /1000)
34 mprintf(" P1=|S1|cos 1=%fkW\n", ((abs(V1)*abs(I1))*
    cos(pha1*3.14/180))/1000)//ans may vary due to
    roundoff error,conversion of degree to radian for
    calculation

```

Scilab code Exa 3.4 Find turns ratio of transformer and voltage levels on applicat

```

1 clc
2 Z=4 //impedance of loudspeaker in ohms
3 Zin=500 //impedance of audio line in ohms
4 a=sqrt(Zin/Z)//ans may vary due to roundoff error
5 mprintf("a=sqrt(Zin/Z)=%f\n",a)//ans may vary due to

```

```

        roundoff error
6 P2=10 //audio power in watts
7 V2=sqrt(40) //ans may vary due to roundoff error
8 mprintf("V2=4*P2=%fV\n",V2) //ans may vary due to
        roundoff error
9 V1=a*V2
10 mprintf("V1=aV2=%fV\n",V1)

```

Scilab code Exa 3.5 Find core and copper losses and efficiency

```

1 clc
2 //code uses a userdefined function complexstring
3 function s=complexstring(a)
4
5
6     if imag(a)>=0 then
7         s=sprintf('%g+%gi',real(a),imag(a))
8     else
9         s=sprintf('%g%gi',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 V2=120 //reference voltage in volts
15 kVA=16.67*(10^3) //kVA rating of transformer
16 I2=kVA/V2 //secondary current aat unity pf
17 mprintf("I2=kVA/V2=%fA\n",I2) //ans may be wrong due
        to roundoff error
18 r2=0.00519 //secondary winding resistance in ohms
19 x2=0.0216 //secondary winding reactance in ohms
20 a=7200/120
21 E2=V2+(I2*(r2+(%i*x2))) //secondary induced voltage
        //ans may be wrong due to roundoff error
22 disp('E2=V2+I2(r2+jx2)='+complexstring(E2)+'V')
23 E1=a*E2 //ans may be wrong due to roundoff error

```

```

24 disp('E1=' + complexstring(E1) + 'V')
25 Rc=311000
26 Ihe=E1/Rc
27 disp('core loss current=' + complexstring(Ihe) + 'A')
28 Phe=((abs(Ihe))^2)*Rc//ans may be wrong due to
    roundoff error
29 mprintf("Core loss Ph+e=|Ih+e|^2*Rc=%fW\n",Phe)
30 Xm=54800
31 disp('I =E1/jXm=' + complexstring(E1/(%i*Xm)) + 'A')//
    ans may be wrong due to roundoff error
32 Iex=Ihe+(E1/(%i*Xm))
33 disp('Iex=Ih+e+I ='+complexstring(Iex)+'A')//ans
    may be wrong due to roundoff error
34 I1=Iex+(I2/a)
35 disp('I1=Iex+I2/a=' + complexstring(I1) + 'A')//ans may
    be wrong due to roundoff error
36 r1=18.7 //primary side resistance
37 x1=77.8
38 V1=E1+(I1*(r1+(%i*x1)))
39 disp('V1=E1+I1(r1+jx1)=' + complexstring(V1) + 'V')//ans
    in the textbook is wrong
40 Pcu=(((abs(I1))^2)*r1)+(((abs(I2))^2)*r2)//copper
    loss
41 mprintf("Pcu=%fW\n",Pcu)//ans may be wrong due to
    roundoff error
42 mprintf("Efficiency =output watts/output+losses=%f\
n",16670/(16670+Pcu+Phe))//ans may be wrong due
    to roundoff error

```

Scilab code Exa 3.6 Find the primary terminal voltage

```

1 clc
2 //extension of Ex3_1
3 //uses a userdefined function complexstring
4 function s=complexstring(a)

```

```

5
6
7     if imag(a) >= 0 then
8         s=sprintf('%g+%gi', real(a), imag(a))
9     else
10        s=sprintf('%g%gi', real(a), imag(a))
11
12    end
13    funcprot(0)
14 endfunction
15 I2=10
16 V2=1000
17 r2=1
18 X11=20 //in ohm
19 x1=0.05 //in ohm
20 X22=2000 //in ohm
21 x2=5 //in ohm
22 Xm1=X11-x1
23 Xm2=X22-x2
24 X12=sqrt(Xm1*Xm2)
25 V12=V2+I2*(r2+(%i*(X22-X12))) //ans may vary due to
    roundof error
26 disp('V12='+complexstring(V12)+'V')
27 I1=I2+(V12/(%i*X12)) //ans may vary due to roundof
    error
28 disp('I1='+complexstring(I1)+'A')
29 r1=0.01
30 V1=V12+(I1*(r1+(%i*(X11-X12)))) //ans may vary due to
    roundof error
31 disp('V1='+complexstring(V1)+'V')
32 a=0.1
33 Zeq1=r1+(a*a*r2)+( %i*(x1+(a*a*x2))) //ans may vary
    due to roundof error
34 disp('Zeq1='+complexstring(Zeq1)+' ')
35 V1=(a*V2)+(I2^Zeq1/a) //ans may vary due to roundof
    error
36 disp('V1='+complexstring(V1)+'V')

```

Scilab code Exa 3.7 Find the primary voltage required to induce 240 volts at second

```
1  clc
2  //the code uses a userdefined function complexstring
3  function s=complexstring(a)
4
5
6      if imag(a)>=0 then
7          s=sprintf('%g+%gi',real(a),imag(a))
8      else
9          s=sprintf('%g%gi',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 r1=3
15 r2=0.03
16 x1=15
17 x2=0.15
18 V1B=2400 //primary side voltage
19 V2B=240 //secondary side voltage
20 a=V1B/V2B
21 Zeq2=(r1/(a^2))+r2+(%i*((x1/(a^2))+x2)) //ans may
    vary due to roundoff error
22 disp('Zeq2='+complexstring(Zeq2)+' ')
23 SB=10000 // rated kva of the transformer
24 V2B=240
25 I2B=SB/V2B
26 mprintf(" I2B=%fA\n",I2B) //ans may vary due to
    roundoff error
27 //with V2 reference
28 //0.8 pf lagging
29 I2=I2B*exp(%i*(-1)*acos(0.8)) //ans may vary due to
    roundoff error
```

```

30 disp('I2=' + complexstring(I2) + 'A')
31 V2=240
32 V1=a*(V2+I2*Zeq2) //ans may vary due to roundoff
    error
33 disp('V1/a=' + complexstring(V1/a) + 'V')
34 mprintf(" |V1|=%fV\n", abs(V1))
35 //0.8 pf leading
36 I2B=SB/V2B
37 I2=I2B*exp(%i*acos(0.8)) //ans may vary due to
    roundoff error
38 V1=a*(V2+(I2*Zeq2)) //ans may vary due to roundoff
    error
39 disp('V1=' + complexstring(V1/a) + 'V')
40 mprintf(" |V1|=%fV\n", abs(V1)) //ans may vary due to
    roundoff error

```

Scilab code Exa 3.8 Find the full voltage regulation at zero point eight pf lagging

```

1  clc
2  //example below is an extension of Ex3_7
3  //values below from Ex3_7
4  V2B=240 //secndary side voltage
5  a=10
6  //0.8 pf lagging
7  V1=2496.44
8  V=V1/a //secondary voltage at full load
9  mprintf(" |V1/a|=%fV\n", V)
10 Regulation=(V-V2B)/V2B //ans may vary due to
    roundoff error
11 mprintf(" Regulation=(|V1/a|-V2B)/V2B=%f\n",
    Regulation)
12 //0.8 pf leading
13 V1=2347.8
14 V=V1/a
15 mprintf("V at 0.8 pf leading=%fV\n", V)

```



```
16 mprintf(" Regulation=%f\n" ,(V-V2B)/V2B)
```

Scilab code Exa 3.9 Find voltage regulation at full load and zero point eight pf 1

```
1 clc
2 //code uses undefined function
3 function s=complexstring(a)
4
5
6     if imag(a)>=0 then
7         s=sprintf(' %g+%gi ',real(a),imag(a))
8     else
9         s=sprintf(' %g%gi ',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 pf=0.8 //power factor of full load
15 I2=1 //magnitude of load current in amperes in per
    unit system
16 I2pu=I2*exp(%i*(-1)*acos(pf))//-1 comes due to
    lagging power factor
17 disp(' I2pu=' +complexstring(I2pu)+'A')
18 pres=2 //percent resistance in ohms
19 preact=5 //percent reactance in ohms
20 Zeqpu=(pres/100)+( %i*(preact/100))
21 disp(' Zeqpu=' +complexstring(Zeqpu)+' ')
22 V1pu=1+(I2pu*Zeqpu)
23 disp(' V1pu=' +complexstring(V1pu)+'V')
24 Regulation=abs(V1pu)-1
25 mprintf(" |V1pu|-1=%f\n" ,Regulation)
```

Scilab code Exa 3.10 Find the ratings and turns ratio of a three phase transformer

```

1  clc
2  SB=10000000 //rating of transformer
3  VL1B=230000 //voltage rating
4  IL1B=SB/(sqrt(3)*VL1B)
5  mprintf(" IL1B=%fA\n", IL1B)
6  VL2B=4160
7  IL2B=SB/(sqrt(3)*VL2B)
8  mprintf(" IL2B=%fA\n", IL2B)
9  //star delta connected
10 mprintf(" Rated kVA=SB/1000=%fkVA\n", SB/1000)
11 mprintf(" Rated I1=I1B=IL1B=%fA\n", IL1B)
12 mprintf(" Rated I2=I2B=IL2B/sqrt(3)=%fA\n", IL2B/sqrt
    (3))
13 VL1=230 //rating in kV
14 VL2=4160//rating in kV
15 mprintf(" Rated V1=V1B=VL1/sqrt(3)=%fkV\n", VL1/sqrt
    (3))
16 mprintf(" V2=V2B=%fV\n", VL2)
17 mprintf(" turns ratio=V1B/V2B=%f\n", (VL1*1000)/(VL2*
    sqrt(3)))
18 mprintf("kVA per phase=%dkVA\n", 3333)
19 //delta star connected
20 mprintf(" Rated kVA=%fkVA\n", SB/1000)
21 mprintf(" kVa per phase=%dkVA\n", 3333)
22 mprintf(" V1B=VL1B=%fkV\n", VL1)
23 mprintf(" V2B=VL2B/sqrt(3)=%fV\n", VL2/sqrt(3))
24 mprintf(" I1B=IL1B/sqrt(3)=%fA\n", IL1B/sqrt(3))
25 mprintf(" I2B=IL2B=%fA\n", IL2B)
26 mprintf(" a=V1B/V2B=%f\n", (VL1B*sqrt(3))/VL2B)
27
28 //delta delta connected
29 mprintf(" Rated kVA=%fkVA\n", SB/1000)
30 mprintf("kVA per phase=%dkVA\n", 3333)
31 mprintf(" V1B=%fKV\n", VL1B/1000)
32 mprintf(" V2B=%fV\n", VL2B)
33 mprintf(" I1B=%fA\n", IL1B/sqrt(3))
34 mprintf(" IL2B=%fA\n", IL2B/sqrt(3))
35 mprintf(" a=%f\n", VL1B/VL2B)

```

Scilab code Exa 3.11 Find the voltage regulation at full load and zero point eight

```
1  clc
2  //the code uses userdefined function complexstring
3  function s=complexstring(a)
4
5
6      if imag(a)>=0 then
7          s=sprintf( '%g+%gi', real(a), imag(a))
8      else
9          s=sprintf( '%g%gi', real(a), imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 //delta connected
15 // sol 1
16 V1B=7200 //primary voltage in volts
17 VL1B=7200 //primary voltage in volts
18 kVA=50 //kva rating
19 IL1B=(kVA*1000)/((sqrt(3))*VL1B)//ans may vary due
    to roundoff error
20 mprintf(" IL1B=%fA\n", IL1B)
21 I1B=IL1B/sqrt(3)//ans may vary due to roundoff error
22 mprintf(" I1B=%fA\n", I1B)
23 //star connected
24 VL2B=208 //seconadry voltage in volts
25 V2B=VL2B/sqrt(3)//ans may vary due to roundoff error
26 mprintf(" V2B=%fV\n", VL2B/sqrt(3))
27 IL2B=(kVA*1000)/(sqrt(3)*VL2B)//ans may vary due to
    roundoff error
28 mprintf(" IL2B=%fA\n", IL2B)
29 I2B=IL2B
30 a=V1B/V2B//ans may vary due to roundoff error
```

```

31 mprintf(" a=%f\n",a)
32 Z2B=V2B/I2B//ans may vary due to roundoff error
33 mprintf(" Z2B=V2B/I2B= %f \n",Z2B)
34 Reqpu=0.012 //percent resistance in ohms
35 Xeqpu=0.05 //percent reactance in ohms
36 Zeqpu=Reqpu+(%i*Xeqpu)
37 mprintf(" Zeqpu=%f      with phase angle of %f degrees
      \n",abs(Zeqpu),(acos(Reqpu/(abs(Zeqpu))))*180/%pi
      )//ans may vary due to roundoff error ,conversion
      of radians to degree
38 Zeq2=Z2B*Zeqpu//ans may vary due to roundoff error
39 mprintf(" Zeq2=%f      with a phase angle of %f degrees\
      n",abs(Zeq2),(acos(real(Zeq2)/abs(Zeq2)))*180/%pi
      )//ans may vary due to roundoff error ,conversion
      of radians to degree
40 pf=0.8 //power factor of load
41 I2=IL2B*exp(%i*(-1)*acos(pf))//ans may vary due to
      roundoff error,-1 comes due to the lagging power
      factor
42 mprintf(" I2=%fA with a phase angle of %f degrees\n",
      abs(I2),(-1)*(acos(real(I2)/abs(I2)))*180/%pi)//
      ans may vary due to roundoff error ,conversion of
      radians to degree
43 V2=120 //seconadry voltage in volts
44 V1=a*(V2+(I2*Zeq2))//ans may vary due to roundoff
      error
45 mprintf(" V1=%fV with a phase angle of %f degrees\n",
      abs(V1/a),(acos(real(V1)/abs(V1)))*180/%pi)//ans
      may vary due to roundoff error ,conversion of
      radians to degree
46 Regulation=(abs(V1/a)-V2)/V2//ans may vary due to
      roundoff error
47 mprintf(" Regulation=%f\n",Regulation)
48 //sol 2(per unit method)
49 I2pu=exp(%i*(-1)*acos(pf)) //seconadry current in
      per unit in amperes
50 V2pu=1 //seconadry voltage in per unit in volts
51 V1pu=V2pu+(I2pu*Zeqpu)

```

```

52 mprintf("V1pu=%fV with a phase angle of %f degrees\n
    ",abs(V1pu),(acos(real(V1pu)/abs(V1pu)))*180/%pi)
    //ans may vary due to roundoff error
53 Regulation=(abs(V1/(a*V2B))-(V2B/V2B))/(V2B/V2B)
54 mprintf("Regulation=%f\n",Regulation)//ans may vary
    due to roundoff error

```

Scilab code Exa 3.12 Find Magnitude of current in secondary of each transformer

```

1  clc
2  //the code uses a userdefined function complexstring
3  function s=complexstring(a)
4
5
6      if imag(a)>=0 then
7          s=sprintf('%g+%gi',real(a),imag(a))
8      else
9          s=sprintf('%g%gi',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 kVAL=100 //kva required for supply
15 kVAM=20 //kVA rating of motor of the air
    conditioning compressor
16 V=220 //supply voltage in volts
17 IL3=(kVAM*1000)/(sqrt(3)*V)
18 mprintf("IL3=%fA=|I2| of small transformer\n",IL3)
19 //abc sequence
20 ph1=36.9 //phase angle of motor current
21 IL3=IL3*exp(%i*(-1)*ph1*%pi/180)//-1 comes due to
    the lagging power factor,conversion of degree to
    radian for calculation
22 mprintf("Il3=%fA with a phase angle of %f degrees\n"
    ,abs(IL3),(-1)*ph1)//-1 comes due to the lagging

```

```

    power factor
23 disp('IL3='+complexstring(IL3)+'A')
24 ph2=30-25.8 //phase angle of I11
25 IL1=((kVAL*1000)/V)*exp(%i*(ph2)*%pi/180)
26 disp('IL1='+complexstring(IL1)+'A')
27 mprintf("IL1=%f with a phase angle of %f degrees\n",
    abs(IL1),ph2)
28 I2=IL3+IL1
29 disp('I2='+complexstring(I2)+'A')
30 mprintf("I2=%fA with a phase angle of %f degrees\n",
    abs(I2),(acos(real(I2)/abs(I2)))*180/%pi)
31 //acb sequence
32 ph3=30+25.8 //phase angle of I11 in degrees
33 IL1=abs(IL1)*exp(%i*(-1)*(ph3)*%pi/180) //-1 comes
    due to lagging power factor
34 disp('IL1='+complexstring(IL1)+'A')
35 mprintf("IL1=%f with a phase angle of %f degrees\n",
    abs(IL1),(-1)*ph3)//-1 comes due to the lagging
    power factor
36 I2=IL3+IL1
37 disp('I2='+complexstring(I2)+'A')
38 mprintf("I2=%fA with a phase angle of %f degrees\n",
    abs(I2),(acos(real(I2)/abs(I2)))*180/%pi)

```

Scilab code Exa 3.13 Find efficiency of transformer for a power factor of zero poi

```

1 clc
2 SB=300 //rating in kVA at full load
3 S=150 //kVA at half load
4 Phe=2.7 //core loss in kW
5 Phepu=Phe/SB //ans may vary due to roundoff error
6 mprintf("Phepu=%f\n",Phepu)
7 Reqpu=0.0140 //per unit resistance in ohms=per unit
    copper loss at full load in watts
8 pf=0.9 //power factor at full load

```

```

9 //efficiency at full load
10 mprintf(" fl =%f\n",pf/(pf+Phepu+Requ))//ans may
    vary due to roundoff error
11 //efficiency at half load
12 a=S/SB //ratio of kVA at half and full load
13 mprintf(" fl =%f\n", (a*pf)/((a*pf)+Phepu+(a*a*Requ)
    ))//ans may vary due to roundoff error
14 //for max efficiency
15 mprintf(" |S|/SB=sqrt (Phepu/Requ)=%fA\n", sqrt(Phepu/
    Requ))//ans may vary due to roundoff error

```

Scilab code Exa 3.14 Open circuit and short circuit test on transformer

```

1 clc
2 //open ckt short ckt test
3 //code uses userdefined function complexstring
4 function s=complexstring(a)
5
6
7     if imag(a)>=0 then
8         s=sprintf( '%g+%gi', real(a), imag(a))
9     else
10        s=sprintf( '%g%gi', real(a), imag(a))
11
12    end
13    funcprot(0)
14 endfunction
15 kVA=50 //kVA rating
16 Poc=500 //core loss in watts
17 Voc=208 //open ckt voltage in volts
18 Vphioc=Voc/sqrt(3)
19 mprintf(" V oc=Voc/sqrt(3)=%fV\n",Vphioc)//ans may
    vary due to roundoff error
20 Pphioc=Poc/3
21 mprintf(" P oc=Poc/3=%fW\n",Pphioc)//ans may vary

```

```

    due to roundoff error
22 Ioc=8 //open ckt current in amperes
23 mprintf("RcLV=V * V / P =%f \n", (Vphioc*Vphioc)/
    Pphioc)//ans may vary due to roundoff error
24 mprintf("Voc^2/Poc=%f \n", (Voc^2)/Poc)//ans may
    vary due to roundoff error
25 mprintf("sin oc=%f\n", sin(acos(Poc/(sqrt(3)*Ioc*Voc
    ))))//ans may vary due to roundoff error
26 mprintf("I =I oc *sin oc=%fA\n", Ioc*sin(acos(Poc
    /(sqrt(3)*Ioc*Voc))))//ans may vary due to
    roundoff error
27 mprintf("XmLV=V oc / I =%f \n", (Voc/sqrt(3))/(Ioc*
    sin(acos(Poc/(sqrt(3)*Ioc*Voc))))//ans may vary
    due to roundoff error
28 //short ckt
29 Psc=600 //copper loss in watts
30 Isc=4.011 //short circuit current in amperes
31 Vsc=370 //short circuit voltage in volts
32 ReqHV=(Psc/3)/((Isc/sqrt(3))^2)
33 mprintf("ReqHV=P sc / I sc ^2=%f \n", ReqHV)//ans may
    vary due to roundoff error
34 ZeqHV=Vsc/(Isc/sqrt(3))
35 mprintf("|ZeqHV|= V sc / I sc=%f \n", ZeqHV)//ans may
    vary due to roundoff error
36 XeqHV=sqrt((ZeqHV^2)-(ReqHV^2))
37 mprintf("XeqHV=%f \n", XeqHV)//ans may vary due to
    roundoff error
38 VHVB=7200//secondary side voltage in volts
39 VLVB=208/sqrt(3)//primary side voltage in volts
40 aV=VHVB/VLVB
41 mprintf("NHV/NLV=VHVB/VLVB=%f\n", aV)//ans may vary
    due to roundoff error
42 mprintf("RcHV=RcLV*aV*aV=%f \n", ((Vphioc*Vphioc)/
    Pphioc)*aV*aV)//ans in the textbook is wrong
43 mprintf("XmHV=XmLV*aV*aV=%f \n", (Voc/sqrt(3))/(Ioc*
    sin(acos(Poc/(sqrt(3)*Ioc*Voc))))*aV*aV)//ans in
    the textbook is wrong
44 ZeqLV=(ReqHV+(%i*XeqHV))/(aV*aV)

```



```

45 disp('ZeqLV=' + complexstring(ZeqLV) + ' ') //ans may
    vary due to roundoff error
46 fprintf("ZeqLV=%f ohms with a phase angle of %f
    degrees\n", abs(ZeqLV), (acos(real(ZeqLV)/abs(ZeqLV)
    ))) * 180 / %pi)
47 SB=50000 //rating of transformer
48 ZLVB=(Voc*Voc)/SB
49 fprintf("ZLVB=%f \n", ZLVB) //ans may vary due to
    roundoff error
50 Reqpu=(ReqHV/(aV*aV))/ZLVB
51 fprintf("Reqpu=%f \n", Reqpu) //ans may vary due to
    roundoff error
52 Xeqpu=(XeqHV/(aV*aV))/ZLVB
53 fprintf("Xeqpu=%f \n", Xeqpu) //ans may vary due to
    roundoff error
54 Zeqpu=Reqpu+(%i*Xeqpu)
55 disp('Zeqpu=' + complexstring(Zeqpu) + ' ') //ans may
    vary due to roundoff error
56 fprintf("Zeqpu=%f ohms with a phase angle of %f
    degrees\n", abs(Zeqpu), (acos(real(Zeqpu)/abs(Zeqpu)
    ))) * 180 / %pi)
57 V1pu=1+((exp(%i*(-1)*acos(0.8)))*Zeqpu)
58 disp('V1pu=' + complexstring(V1pu)) //ans may vary due
    to roundoff error
59 fprintf("V1pu=%fV with a phase angle of %f degrees\n
    ", abs(V1pu), (acos(real(V1pu)/abs(V1pu))) * 180 / %pi)
60 fprintf("Regulation=%f\n", (abs(V1pu)-1)) //ans may
    vary due to roundoff error
61 //full load efficiency
62 pf=0.8 //power factor of load
63 Phepu=Poc/SB
64 fprintf(" = cos / cos +Reqpu+Phepu=%f\n", pf/(pf+
    Reqpu+Phepu)) //ans may vary due to roundoff error
65 //second method
66 fprintf(" =%f\n", (SB*pf)/((SB*pf)+Poc+Psc))
67 //ans may vary due to roundoff error

```

Chapter 4

Induction or Asynchronous Machines

Scilab code Exa 4.1 Calculate air gap power and developed mechanical power and out

```
1  clc
2  SCL=1000 //stator copper loss in watts
3  V=460 //line voltage of induction motor in volts
4  I=25 //line current of motor in amperes
5  pf=0.85 //power factor of motor
6  Pin=sqrt(3)*V*I*pf //ans may vary due to roundoff
   error
7  mprintf(" Pin=%fW\n",Pin)
8  Pg=Pin-SCL //air gap power
9  mprintf(" Pg=%fW\n",Pg)//ans may vary due to
   roundoff error
10 RCL=500 //rotor copper loss in watts
11 Phe=800 //core loss in watts
12 Pfw=250 //winding and friction loss in Watts
13 PLL=200 //stray load loss in watts
14 DMP=Pg-RCL ///developed mechanical power in watts
15 mprintf("DMP=%fW\n",DMP)//ans may vary due to
   roundoff error
16 Prot=Phe+Pfw+PLL //power loss in rotor in watts
```

```

17 Pout=DMP-Prot
18 mprintf(" Pout=DMP-Prot=%fW\n",Pout)//ans may vary
    due to roundoff error
19 mprintf(" Horsepower=Pout/746=%fhp\n",Pout/746)//ans
    may vary due to roundoff error,conversion of
    watts to hp needs division by 746
20 mprintf(" =Pout/Pin=%f\n",Pout/Pin)//ans may vary
    due to roundoff error

```

Scilab code Exa 4.2 Find slip and operating speed and developed torque and output

```

1 clc
2 //this is an extension of Ex4_1
3 //following comes from Ex4_1
4 SCL=1000 //stator copper loss in watts
5 V=460 //line voltage of induction motor in volts
6 I=25 //line current of motor in amperes
7 pf=0.85 //power factor of motor
8 Pin=sqrt(3)*V*I*pf //ans may vary due to roundoff
    error
9 Pg=Pin-SCL //air gap power
10 RCL=500 //rotor copper loss in watts
11 Phe=800 //core loss in watts
12 Pfw=250 //winding and friction loss in Watts
13 PLL=200 //stray load loss in watts
14 DMP=Pg-RCL ///developed mechanical power in watts
15 Prot=Phe+Pfw+PLL //power loss in rotor in watts
16 Pout=DMP-Prot
17 //above is from Ex4_1
18 s=RCL/Pg
19 p=4 //no of poles
20 mprintf(" s=RCL/Pg=%f\n",s)//ans may vary due to
    roundoff error
21 ws=(4*pi*60)/p //synchronous angular frequency
22 mprintf(" ws=%frad/s\n",ws)//ans may vary due to

```

```

        roundoff error
23 ns=(120*60)/p
24 mprintf(" ns=%drev/min\n",ns)//ans may vary due to
        roundoff error
25 w=ws*(1-s)
26 n=ns*(1-s)
27 mprintf("w=ws(1-s)=%f rad/s\n",w)//ans may vary due
        to roundoff error
28 mprintf("n=ns(1-s)=%f rev/min\n",n)//ans may vary due
        to roundoff error
29 mprintf(" d =DMP/w=%fN-m\n",DMP/w)//ans may vary due
        to roundoff error
30 mprintf(" =Pout/w=%fN-m\n",Pout/w)//ans may vary
        due to roundoff error

```

Scilab code Exa 4.3 Calculate performance at 1746 rev per min and starting current

```

1  clc
2  //code uses userdefined function complexstring
3  function s=complexstring(a)
4
5
6      if imag(a)>=0 then
7          s=sprintf('%g+%gi',real(a),imag(a))
8      else
9          s=sprintf('%g%gi',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14
15 //induction machine parameters in ohms
16 r1=0.39 //primary resistance
17 r2=0.14 //secondary resistance
18 x1=0.35 //primary reactance

```

```

19 x2=0.35//secondary reactance
20 Xm=16//manetizing reactance
21 VL=220 //supply volatge in volts
22 f=60 //frequency in Hz
23 //part a
24 p=4 //no of poles
25 ns=(120*f)/p
26 mprintf("ns=%drev/min\n",ns)
27 n=1746 //running speed of motor in rev/min
28 s=(ns-n)/ns
29 mprintf("s=%f\n",s)
30 z2=(r2/s)+(i*x2)//ans may vary due to roundoff
    error
31 disp('Z2=' + complexstring(z2) + ' ')
32 mprintf("Z2=%fohm having a phase angle of %f degrees
    \n",abs(z2),(acos(real(z2)/abs(z2)))*180/%pi)
33 Zf=(i*Xm*z2)/(z2+(i*Xm))//ans may vary due to
    roundoff error
34 disp('Zf=' + complexstring(Zf) + ' ')
35 mprintf("Zf=%fohms having a phase angle of %f
    degrees\n",abs(Zf),(acos(real(Zf)/abs(Zf)))*180/
    %pi)
36 Rf=real(Zf)//ans may vary due to roundoff error
37 mprintf("Rf=%f \n",Rf)
38 Zin=r1+(i*x1)+Zf//ans may vary due to roundoff
    error
39 disp('Zin=r1+jx1+Zf=' + complexstring(Zin) + ' ')
40 mprintf("Zin=%fohms having a phase angle of %f
    degrees\n",abs(Zin),(acos(real(Zin)/abs(Zin)))
    *180/%pi)
41 Powerfactor=real(Zin)/abs(Zin)//ans may vary due to
    roundoff error
42 mprintf("Power facto=%f\n",Powerfactor)
43 I1=VL/(sqrt(3)*abs(Zin))
44 mprintf("|I1|=%fA\n",I1)//ans may vary due to
    roundoff error
45 Pin=sqrt(3)*I1*VL*Powerfactor
46 mprintf("Pin=%fW\n",Pin)//ans in the textbook is

```

```

wrong
47 Pg=3*I1*I1*Rf
48 fprintf("Pg=%fW\n",Pg)//ans in the textbook is wrong
49 DMP=(1-s)*Pg
50 fprintf("Developed power=(1-s)Pg=%fW\n",DMP)//ans in
the textbook is wrong
51 Prot=s*Pg //rotor copper losses
52 Pout=DMP-Prot//ans in the textbook is wrong
53 fprintf("Output power=%fW\n",Pout)
54 fprintf("Output horsepower=%f\n",Pout/746)//ans may
vary due to roundoff error,1 hp=746 watts
55 fprintf("Developed torque=%flb-ft\n",7.04*(Pg/ns))//
ans may vary due to roundoff error,1 N-m=7.04 lb-
ft ot torque
56 n=(1-s)*ns//ans may vary due to roundoff error
57 fprintf("Output torque=%flb-ft\n",7.04*(Pout/n))
58 fprintf("Efficiency=%f\n",Pout/Pin)
59 //part b
60 s=1 //machine at stanstill
61 z2=r2+(%i*x2)//ans may vary due to roundoff error
62 disp('Z2='+complexstring(z2)+' ')
63 fprintf("Z2=%fohm having a phase angle of %f degrees
\n",abs(z2),(acos(real(z2)/abs(z2)))*180/%pi)
64 Zf=(%i*Xm*z2)/(z2+(%i*Xm))//ans may vary due to
roundoff error
65 disp('Zf='+complexstring(Zf)+' ')
66 fprintf("Zf=%fohms having a phase angle of %f
degrees\n",abs(Zf),(acos(real(Zf)/abs(Zf)))*180/
%pi)
67 Zin=r1+(%i*x1)+Zf//ans may vary due to roundoff
error
68 disp('Zin='+complexstring(Zin)+' ')
69 fprintf("Zin=%fohms having a phase angle of %f
degrees\n",abs(Zin),(acos(real(Zin)/abs(Zin)))
*180/%pi)
70 I1=VL/(sqrt(3)*abs(Zin))//ans may vary due to
roundoff error
71 Rf=real(Zf)

```

```

72 mprintf(" Starting current=%fA\n",I1)
73 Pg=3*I1*I1*Rf
74 mprintf("Pg=%fW\n",Pg)//ans in the textbook is wrong
75 mprintf(" d =7.04*(Pg/ns)=%flb-ft\n",7.04*(Pg/ns))//
    ans may vary due to roundoff error,1 N-M=7.04 lb-
    ft of torque

```

Scilab code Exa 4.4 Find the pull out torque and slip at which it occurs

```

1  clc
2  //below is an extension of Ex4_3
3  //code uses userdefined function complexstring
4  function s=complexstring(a)
5
6
7      if imag(a)>=0 then
8          s=sprintf('%g+%gi',real(a),imag(a))
9      else
10         s=sprintf('%g%gi',real(a),imag(a))
11
12     end
13     funcprot(0)
14 endfunction
15 x1=0.35 //primary reactance in ohms
16 r1=0.39 //primary resistance in ohms
17 Xm=16 //magnetizing reactance
18 r2=0.14 //secondary resistance in ohms
19 x2=0.35 //secondary reactance in ohms
20 ws=188.5 //angular frequency in rad/sec
21 V=220 //rated voltage in volts
22 //part a
23 V1m=V/sqrt(3)//ans may vary due to roundoff error
24 VTH=V1m*(Xm/(Xm+x2))
25 mprintf("VTH=V1m=%fV\n",VTH)//ans may vary due to
    roundoff error

```

```

26 X1=x1
27 mprintf("X1=%f \n",X1)
28 R1=r1*(Xm/(x1+Xm))//ans may vary due to roundoff
    error
29 mprintf("R1=%f \n",R1)
30 mprintf(" max =%fN-m\n",((3/ws)*(VTH^2))/(2*(R1+sqrt
    ((R1^2)+((2*X1)^2))))//ans may vary due to
    roundoff error
31 //part b
32 sM=r2/sqrt((R1^2)+((X1+x1)^2))//ans may vary due to
    roundoff error
33 mprintf("sM=%f\n",sM)
34 mprintf("r2/sM=%f \n",r2/sM)//ans may vary due to
    roundoff error
35 Zf=((%i*Xm)*((r2/sM)+(%i*x2)))/((r2/sM)+(%i*(x2+Xm))
    )//ans may vary due to roundoff error
36 disp('Zf='+complexstring(Zf)+' ')
37 mprintf("Zf=%fohm having a phase angle of %f degrees
    \n",abs(Zf),(acos(real(Zf)/abs(Zf))*180/%pi)
38 z1=r1+(%i*x1)
39 Zin=z1+Zf
40 disp('Zin='+complexstring(Zin)+' ')//ans may vary
    due to roundoff error
41 mprintf("Zin=%fohm having a phase angle of %f
    degrees\n",abs(Zin),(acos(real(Zin)/abs(Zin)))
    *180/%pi)
42 I1=V1m/abs(Zin)
43 mprintf("I1=%fA\n",I1)//ans may vary due to roundoff
    error
44 Rf=real(Zf) //resistance in ohms
45 Pg=3*I1*I1*Rf//ans in the textbook is wrong
46 mprintf("Pg=%fW\n",Pg)
47 mprintf(" max =Pg/ws=%fN-m\n",Pg/ws)//ans may vary
    due to roundoff error

```

Scilab code Exa 4.5 Find speed at half of the load and the corresponding output in

```
1 clc
2 ns=1800 //synchronous speed in rev/min
3 n=1745 //initial speed in rev/min
4 hp=10 //hp rating of the motor horsepower(1 hp=746
    Watts)
5 s=(ns-n)/ns
6 mprintf("s=%f\n",s)//ans may vary due to roundoff
    error
7 s=s/2 //slip at half torque
8 n1=ns*(1-s)//ans may vary due to roundoff error
9 mprintf("n=ns(1-s)=%frev/min\n",n1)
10 //output at half torque
11 mprintf("New horsepower output=%fhp\n", (0.5*hp*n1)/n
    )//ans may vary due to roundoff error ,0.5 factor
    comes due to half torque
```

Scilab code Exa 4.6 Will the motor run hotter or cooler if voltage drops to 90 per

```
1 clc
2 V1m(1)=1 //reference voltage in volts
3 V1m(2)=0.9//reduced voltage in volts
4 ratio=(V1m(1)/V1m(2))^2 //ratio of s2/s1
5 mprintf("s2/s1=%f\n",ratio)//ans may vary due to
    roundoff error
6 mprintf("I2(2)/I2(1)=s2*V1m(2)/s1*V1m(1)=%f\n", (V1m
    (2)/V1m(1))*ratio)//ans may vary due to roundoff
    error
7 mprintf("(copperloss)2/(copperloss)1=(I2(2)/I2(1))
    ^2=%f\n", (V1m(1)/V1m(2))^2)//ans may vary due to
    roundoff error
8 s=0.03 //at 60Hz slip
9 ns=1800 //synchronous speed in rev/min
10 mprintf("Speed at 90 percent voltage=%frev/min\n",ns
```

```
*(1-(ratio*s)))//ans may vary due to roundoff
error
```

Scilab code Exa 4.7 Calculate performance of motor at given slip

```
1  clc
2  //code uses userdefined function complexstring
3  function s=complexstring(a)
4
5
6      if imag(a)>=0 then
7          s=sprintf('%g+%gi',real(a),imag(a))
8      else
9          s=sprintf('%g%gi',real(a),imag(a))
10
11     end
12     funcprot(0)
13 endfunction
14 //dc test
15 Vdc=13.8 //dc voltage in volts
16 Idc=13 //direct current in amperes
17 //no load test
18 Vnl=220 //applied no voltage in volts
19 f=60 //applied frequency in Hz
20 //blocked rotor test
21 VBR=23.5 //blocked rotor voltage in volts
22 f1=15 //frequency in Hz
23 Ia=12.8 //current of phase A
24 Ib=13.1 //current of phase B
25 Ic=12.9 //current of phase C
26 //from blocked rotor
27 IBR=(Ia+Ib+Ic)/3 //ans may vary due to roundoff
    error
28 mprintf("IBR=%fA\n",IBR)
29 ZBR=VBR/(sqrt(3)*IBR)
```

```

30 mprintf(" |ZBR|= %f \n", ZBR) //ans may vary due to
    roundoff error
31 P1=179 //power in watts
32 P2=290 //power in watts
33 PBR=P1+P2
34 mprintf("PBR=%fW\n", PBR)
35 RBR=PBR/(3*(IBR^2)) //ans may vary due to roundoff
    error
36 mprintf("RBR=%f \n", RBR)
37 mprintf(" BR =%f\n", (acos(PBR/(sqrt(3)*VBR*IBR)))
    *(180/%pi)) //ans may vary due to roundoff error
38 mprintf("X'BR=|ZBR|*sin BR=%f \n", ZBR*sin(acos(PBR
    /(sqrt(3)*VBR*IBR)))) //ans may vary due to
    roundoff error
39 XBR=(f/f1)*(ZBR*sin(acos(PBR/(sqrt(3)*VBR*IBR))))
40 mprintf("XBR=(fB/f1)*X'BR=%f \n", XBR) //ans may vary
    due to roundoff error
41 x1=0.4*XBR //designed reactance
42 x2=0.6*XBR //designed reactance
43 mprintf(" x1=%f \n", x1) //ans may vary due to
    roundoff error
44 mprintf(" x2=%f \n", x2) //ans may vary due to
    roundoff error
45 //from dc test
46 r1=0.5*(Vdc/Idc)
47 mprintf(" r1=%f \n", r1) //ans may vary due to
    roundoff error
48 r2=RBR-r1
49 mprintf(" r2=%f \n", r2) //ans may vary due to
    roundoff error
50 //from no load test
51 Ia=3.86 //current of phase A in amperes
52 Ib=3.86 //current of phase B in amperes
53 Ic=3.89 //current of phase C in amperes
54 Inl=(Ia+Ib+Ic)/3
55 mprintf(" Inl=%fA\n", Inl) //ans may vary due to
    roundoff error
56 Zn1=Vn1/(sqrt(3)*Inl)

```

```

57 fprintf("Znl=x1+Xm=%f \n",Znl)//ans may vary due to
    roundoff error
58 Xm=Znl-x1
59 fprintf("Xm=Znl-x1=%f \n",Xm)//ans may vary due to
    roundoff error
60 P1=550 //power in watts
61 P2=-350 //power in watts
62 Pnl=P1+P2
63 fprintf("Pnl=%fW\n",Pnl)//ans may vary due to
    roundoff error
64 Pfwc=Pnl-(3*Inl*Inl*r1)
65 fprintf("Pfwc=%fW\n",Pfwc)//ans may vary due to
    roundoff error
66 Prot=Pfwc
67 s=0.03
68 z2=(r2/s)+(i*x2)
69 disp('z2='+complexstring(z2)+' ')//ans may vary due
    to roundoff error
70 fprintf("Z2=%fohms with a phase angle of %fdegrees\n
",abs(z2),(acos(real(z2)/abs(z2)))*180/pi)
71 Zf=(z2*(i*Xm))/(z2+(i*Xm))
72 disp('Zf='+complexstring(Zf)+' ')//ans may vary due
    to roundoff error
73 fprintf("Zf=%fohms with a phase angle of %fdegrees\n
",abs(Zf),(acos(real(Zf)/abs(Zf)))*180/pi)
74 Rf=real(Zf)
75 Zin=r1+Zf+(i*x1)
76 disp('Zin='+complexstring(Zin)+' ')//ans may vary
    due to roundoff error
77 fprintf("Zin=%fohms with a phase angle of %fdegrees\
n",abs(Zin),(acos(real(Zin)/abs(Zin)))*180/pi)
78 fprintf("power factor=%f\n",(real(Zin)/abs(Zin))//
    ans may vary due to roundoff error
79 I1=Vnl/(sqrt(3)*abs(Zin))
80 fprintf("|I1|=%fA\n",I1)//ans may vary due to
    roundoff error
81 Pin=(sqrt(3)*(real(Zin)/abs(Zin))*I1*Vnl)//ans is
    wrong in textbook

```

```

82 mprintf("power drawn from line=sqrt(3)*VL*|I|*
    cos   =%fW\n",Pin)
83 Rf=real(Zf)
84 Pg=3*I1*I1*Rf
85 mprintf("Pg=%fW\n",Pg)//ans is wrong in textbook
86 DMP=Pg*(1-s)
87 mprintf("DMP=%fW\n",DMP)//ans is wrong in textbook
88 Pout=DMP-Prot
89 mprintf("output horsepower=%fhp\n",Pout/746)//ans
    may vary due to roundoff error,1 hp=746 watts
90 mprintf("  =Pout/Pin=%f\n",Pout/Pin)//ans may vary
    due to roundoff error

```

Scilab code Exa 4.8 Upper limit of the starting current at 230v

```

1 clc
2 kVA=6.3 //upper limit for kVA per horsepower
3 hp=10 //rating of induction motor in hp.(1 hp=746
    watts)
4 V=230 //voltage rating of the motor
5 I=(kVA*hp*1000)/(sqrt(3)*V)
6 mprintf(" I=%fA\n",I)//ans may vary due to roundoff
    error

```

Scilab code Exa 4.9 Find the starting line current and torque with provided compen

```

1 clc
2 vtap=0.8 //percentage voltage tap of compensator
3 hp=100 //rating of motor in horsepower,1 hp=746
    watts
4 n=1750 //rated speed of motor in rev/min
5 a=1/vtap //compensator turns ratio
6 V=2300 //voltage rating of induction motor in volts

```

```

7 I1=150 //current rating in amperes
8 mprintf("a=%f\n",a)
9 mprintf(" Voltage applied at starting of motor=%fV\n"
    ,V/a)
10 I1start=I1/a
11 mprintf(" I1start=(1840/2300)*150A=150/a=%fA\n" ,
    I1start)
12 IL=I1start/a
13 mprintf(" IL=I1start/a=%fA\n" ,IL)
14 tfl=hp*5252/n
15 mprintf(" fl =(hp*5252)/(rev/min)=%flb-ft\n" ,tfl)//
    ans may vary due to roundoff error
16 t=1.2*tfl //120 percent of the full load torque in
    lb-ft
17 mprintf(" st =360/a*a=%flb-ft\n" ,t/(a*a))//ans may
    vary due to roundoff error

```

Chapter 5

Direct Current Machines

Scilab code Exa 5.1 Find out the power developed and the torque and determination

```
1  clc
2  B=0.78 //flux density in tesla
3  A=200*(10^(-4))//cross sectional area in centimetre
   square
4  mprintf("Flux per pole    =B.A=%fWb\n",B*A)
5  C=95 //no of coils
6  Nc=2 //no of turns in each coil
7  Z=2*C*Nc
8  mprintf("Z=2*C*Nc=%fconductors\n",Z)
9  n=1200 //rotating speed in rev/min
10 w=(n/60)*(2*%pi)
11 mprintf("w=%frad/s\n",w)//ans may vary due to rounof
   error
12 a=2 //no of paths
13 p=4 //no of poles
14 Ka=(Z*p)/(2*%pi*a)
15 mprintf("Ka=%fV-s/Wb\n",Ka)//ans may vary due to
   rounof error
16 Eg=Ka*B*A*w
17 mprintf("Eg=Ka*   *w=%fV\n",Eg)//ans may vary due to
   rounof error
```

```

18 VT=250 //terminal voltage in volts
19 ra=0.2 //armature resistance in ohms
20 Ia=(VT-Eg)/ra
21 mprintf("Ia=%fA\n",Ia)//ans may vary due to roundoff
    error
22 Pin=VT*Ia
23 mprintf("Pin=%fW\n",Pin)//ans in textbook is wrong
24 mprintf("Armature copper loss=%fW\n",((Ia*Ia)*ra))//
    ans in textbook is wrong
25 Pd=Pin-((Ia*Ia)*ra)//ans in textbook is wrong
26 mprintf("Pd=Pin-coper loss=%fW\n",Pd)
27 mprintf(" d =Pd/w=%fN-m ",Pd/w)
28 cf=0.7376 //conversion factor for conversion from N-
    m to lb-ft
29 mprintf(" or %flb-ft ",(Pd/w)*cf)//ans may vary due to
    roundoff error

```

Scilab code Exa 5.2 Find torque developed by the motor and speed and armature cure

```

1 clc
2 I=100 //current drawn in amperes
3 ra=0.07 //armature resistance in ohms
4 Vt=230 //terminal voltage of motor in volts
5 mprintf("Eg*=VT*-Iara*=%fV\n",Vt-(I*ra))
6 n=1200 //speed of rotation in rev/min
7 mprintf("w*=%d rad/sec\n", (n/60)*2)
8 mprintf("Ka =Eg*/w*=%fV-s/rad\n", (Vt-(I*ra))/((n
    /60)*2*pi))//ans may vary due to roundoff error
9 Ia=100 //armature current in ampere
10 mprintf(" d =Ka Ia=%fN-m\n", (Ia*(Vt-(I*ra))/((n/60)
    *2*pi))//ans may vary due to roundoff error
11 Td=300 //torque in N-m
12 Ia=Td/((Vt-(I*ra))/((n/60)*2*pi))//ans may vary due
    to roundoff error
13 mprintf("Ia= d /Ka =%fA\n",Ia)

```



```

14 ra=0.07 //resistance in ohms
15 VT=230 //voltage in volts
16 w=(VT-Ia*ra)/((Vt-(I*ra))/((n/60)*2*pi))
17 mprintf("w=(VT-Iara)/Ka =%frad/sec\n",w)//ans may
    vary due to roundoff error

```

Scilab code Exa 5.3 Find speed of the motor when it develops a torque of 300 Newton

```

1 clc
2 //Ex5_3 uses a magnetization curve given in textbook
3 mprintf("At 1200 rev/min and shunt field current of
    0.7A Eg*=90V \n") //from magnetization curve
4 n=1200 //speed of rotation in rev/min
5 Eg1=90 //voltage in volts
6 wB=(n/60)*2
7 mprintf("wB=%d rad/sec\n",wB)
8 mprintf("Ka *=Eg*/wB=%fV-s/rad\n",Eg1/(wB*pi))//
    ans may vary due to roundoff error
9 Td=30 //torque in N-m
10 Ia=Td/(Eg1/(wB*pi))
11 mprintf("Ia= d /Ka *=%fA\n",Ia)//ans may vary due
    to roundoff error
12 VT=125 //voltage in volts
13 ra=0.2 //resistance in ohms
14 Eg=VT-(Ia*ra)
15 mprintf("Eg=%fV\n",Eg)//ans may vary due to roundoff
    error
16 w=Eg/((Eg1/(wB*pi)))
17 mprintf("w=Eg/Ka *=%frad/s\n",w)//ans may vary due
    to roundoff error
18 n=(w*60)/(2*pi)
19 mprintf("n=%frev/min\n",n)//ans may vary due to
    roundoff error
20 //other two techniques
21 //first technique

```

```

22 nB=1200 //speed in rev/min
23 n=nB*(Eg/Eg1)//ans may vary due to roundoff error
24 mprintf("n=%frev/min\n",n)
25 //second technique
26 mprintf(" d =%flb-ft\n",Td*0.738)//ans may vary due
    to roundoff error
27 mprintf("Ka' =Eg*/nB=%fV-min/rev\n",Eg/nB)
28 Ia=(Td*0.738)/(7.04*(Eg1/nB))//ans may vary due to
    roundoff error
29 mprintf("Ia= d /(7.04*Ka'* )=%fA\n",Ia)
30 n=Eg/(Eg1/nB)
31 mprintf("n=Eg/K' a =%frev/min\n",n)//ans may vary
    due to roundoff error

```

Scilab code Exa 5.4 Find the terminal voltage at full load and no load and voltage

```

1 clc
2 //Ex5_4 uses a figure given in textbook
3 Ia=50 //current in amperes
4 IB=50 //current in amperes
5 nB=1200 //speed in rev/min
6 ratio=0.01 //ratio of Nsc/Nf ,unit less
7 Isc=0.6*Ia //equation given in textbook
8 mprintf("Isc=%dA\n",Isc)
9 If=1.3 //field current in amperes
10 mprintf("If*=If+(Nsc/Nf)*Isc=%fA\n",If+(ratio*Isc))
11 Eg1=132.5 //voltage in volts
12 mprintf("Ka' =Eg*/nB=%fV-min/rev\n",Eg1/nB)//ans
    may vary due to roundoff error
13 n=1140 //speed in rev/min
14 Eg=n*(Eg1/nB)
15 mprintf("Eg=Ka' n=%fV\n",Eg)//ans may vary due to
    roundoff error
16 ra=0.2 //resistance in ohms
17 Ra=0.03+ra //by kirchodff's law and parallel

```

```

    combination or resistances
18 mprintf(" Ra=%f \n",Ra)
19 VTf1=Eg-(Ia*Ra)
20 mprintf(" VTf1=%fV\n",VTf1)//ans may vary due to
    roundoff error
21 mprintf(" If*=If+0=%fA\n",If)
22 Eg2=125 //voltage in volts
23 VTn1=Eg*(n/nB)
24 mprintf(" Eg=Eg*(n/nB)=%fV\n",VTn1)//ans may vary due
    to roundoff error
25 mprintf(" Voltage Regulation=(VTn1-VTf1)/VTf1=%f%c"
    ,((VTn1-VTf1)/VTf1)*100,'%') //ans may vary due
    to roundoff error

```

Scilab code Exa 5.5 Find the efficiency and input horsepower requirements under gi

```

1 clc
2 V=250 //voltage rating in volts
3 Pout=125000 //output power in watts
4 ra=0.025 //armature resistance in ohms
5 rsc=0.01 //resistance in ohms
6 rf=30 //field resistance in ohms
7 If=5 //field current in amperes
8 mprintf(" Shunt field copper loss=%dW\n",If*If*rf)
9 Iload=Pout/V
10 Ia=Iload+If
11 Isc=Iload+If
12 mprintf(" Ia=Isc=Iload+If=%dA\n",Ia)
13 mprintf(" Seires filed copper losses=%dW\n",Isc*Isc*
    rsc)
14 mprintf(" ACL=%fW\n",Ia*Ia*ra)//ans in textbook is
    wrong
15 mprintf(" Brush copper loss=2Ia=%dW\n",2*Ia)
16 mprintf(" Stray load loss=1%c of 125Kw=%fW\n", '%',
    ,0.01*Pout)

```

```

17 Prot=5000 //rotational loss in watts
18 losses=(If*If*rf)+(Isc*Isc*rsc)+(Ia*Ia*ra)+(2*Ia)
    +(0.01*Pout)+Prot //adding all losses
19
20 mprintf(" Efficiency=%f%c\n", (Pout/(Pout+losses))
    *100, '%') //ans may vary due to roundoff eror
21 rlosses=500 //rheostat losses in watts
22 Pin=Pout+losses+rlosses
23 mprintf(" Pin required=%fW\n", Pin) //ans in the
    textbook is wrong
24 Ia1=sqrt((Prot+(If*If*rf))/(ra+rsc))
25 mprintf(" Ia1=%fA\n", Ia1)

```

Chapter 6

Single Phase Machines

Scilab code Exa 6.1 Find the performance of a single phase motor under provided co

```
1  clc
2  //code uses a userdefined function complexstring
3  function s=complexstring(a)
4
5
6      if imag(a)>=0 then
7          s=sprintf( '%g+%gi', real(a), imag(a))
8      else
9          s=sprintf( '%g%gi', real(a), imag(a))
10
11      end
12      funcprot(0)
13  endfunction
14  r1m=1.9//resistance in ohms
15  x1m=2.6 //reactance in ohms
16  r2=3.6 //resistance in ohms
17  x2=2.6 //reactance in ohms
18  Xm=56 //magnetizing reactance in ohms
19  Prot=25 //rotational losses in watts
20  f=60 //supply frequency in Hz
21  z1m=r1m+(%i*x1m)
```

```

22 s=0.05 //slip
23 disp('Zlm=' + complexstring(z1m) + ' ')
24 Zf=((%i*Xm)*((r2/s)+(%i*x2)))/((%i*Xm)+(r2/s)+(%i*x2
    ))//ans may vary due to roundoff error
25 disp('Zf/2=' + complexstring(Zf/2) + ' ')
26 Zb=((%i*Xm)*((r2/(2-s))+(%i*x2)))/((%i*Xm)+(r2/(2-s)
    ))+(%i*x2)//ans may vary due to roundoff error
27 disp('Zb/2=' + complexstring(Zb/2) + ' ')
28 Vm=115 //voltage in volts
29 Im=Vm/((Zf/2)+(Zb/2)+z1m) //ans may vary due to
    roundoff error
30 Imf=Im
31 Imb=Im
32 disp('Im=' + complexstring(Im) + 'A')
33 Pin=Vm*abs(Im)*(real(Im)/abs(Im))//ans may vary due
    to roundoff error
34 mprintf(" Pin=%fW\n",Pin)
35 Pg=((abs(Im))^2)*(real(Zf/2)-real(Zb/2))//ans may
    vary due to roundoff error
36 mprintf(" Pg=Pgf-Pgb=%fW\n",Pg)
37 mprintf(" d =%fN-m\n",Pg/(2*pi*(f/2)))
38 DMP=Pg*(1-s)
39 mprintf("DMP=%fW\n",DMP)//ans may vary due to
    roundoff error
40 Pout=DMP-Prot
41 mprintf(" Pout=%fW\n",Pout)//ans may vary due to
    roundoff error
42 mprintf(" Efficiency=%f\n",Pout/Pin)//ans may vary
    due to roundoff error

```

Scilab code Exa 6.2 Calculate the starting torque for the motor under provided par

```

1 clc
2 //Ex6_2 is an extension of Ex6_1
3 //code uses userdefined function complexstring

```

```

4 function s=complexstring(a)
5
6
7     if imag(a)>=0 then
8         s=sprintf( '%g+%gi', real(a), imag(a))
9     else
10        s=sprintf( '%g%gi', real(a), imag(a))
11
12    end
13    funcprot(0)
14 endfunction
15 r1a=12//resistance in ohms
16 x1a=6.5//reactance in ohms
17 Xc=-20 //reactance in ohms
18 r1m=1.9 //from E6_1
19 x2=2.6 //from Ex6_1
20 s=1
21 a=1.6 //no unit
22 r2=3.6 //resistance in ohms
23 x2=2.6 //reactance in ohms
24 Xm=56 //magnetizing reactance in ohms
25 Vm=115 //applied voltage in volts
26 Zf=((%i*Xm)*((r2/s)+(%i*x2)))/((%i*Xm)+(r2/s)+(%i*x2
    ))//from Ex6_1
27 Zst=Zf
28 Zb=Zf
29 z1a=r1a+(%i*x1a)+(%i*Xc)
30 disp('z1a='+complexstring(z1a)+' ')//ans may vary
    due to roundoff error
31 mprintf("z1a=%fohm havinga phase angle of %f degrees
    \n", abs(z1a), (acos(real(z1a)/abs(z1a)))*180/%pi)
32 Z12=((1/2)*(z1a/(a*a)))-(r1m+(%i*x2))//ans in
    textbook is wrong
33 disp('Z12='+complexstring(Z12)+' ')//ans may vary
    due to roundoff error
34 mprintf("Z12=%fohm havinga phase angle of %f degrees
    \n", abs(Z12), (acos(real(Z12)/abs(Z12)))*180/%pi)
35 Vmf=(Vm/2)*(1-(%i/a))

```

```

36 disp('Vmf=' + complexstring(Vmf) + 'V') //ans may vary
    due to roundoff error
37 mprintf("Vmf=%fV having a phase angle of %f degrees\n
    ", abs(Vmf), (-1)*(acos(real(Vmf)/abs(Vmf)))*180/
    %pi)
38 Vmb=(Vm/2)*(1+(%i/a))
39 disp('Vmb=' + complexstring(Vmb) + 'V') //ans may vary
    due to roundoff error
40 mprintf("Vmb=%fV having a phase angle of %f degrees\
n", abs(Vmb), (acos(real(Vmb)/abs(Vmb)))*180/%pi)
41 Imf=11.77*exp(%i*(-1)*54.93*%pi/180) //textbook
    doesnt provide any formula or hint for this
    calculation
42 Imb=4.37*exp(%i*(-1)*19.7*%pi/180) //textbook doesnt
    provide any formula or hint for this calculation
43 disp('Imf=' + complexstring(Imf) + 'A') //ans may vary
    due to roundoff error
44 disp('Imb=' + complexstring(Imb) + 'A') //ans may vary
    due to roundoff error
45 mprintf("Imf=%fA having a phase angle of %f degrees\
n", 11.77, -54.93)
46 mprintf("Imb=%fA having a phase angle of %f degrees\
n", 4.37, -19.37)
47 mprintf(" st =%fN→m\n", (2*real(Zst)*((abs(Imf)^2)-(
    abs(Imb)^2)))/(60*%pi)) //ans may vary due to
    roundoff error
48 Im=Imf+Imb
49 disp('Im=' + complexstring(Im) + 'A') //ans may vary due
    to roundoff error
50 mprintf("Im=%fA having a phase angle of %f degrees\n"
    , abs(Im), (-1)*(acos(real(Im)/abs(Im)))*180/%pi)
51 Ia=(%i*(Imf-Imb))/a
52 disp('Ia=' + complexstring(Ia) + 'A') //ans may vary due
    to roundoff error
53 mprintf("Ia=%fA having a phase angle of %f degrees\n
    ", abs(Ia), (acos(real(Ia)/abs(Ia)))*180/%pi)
54 I=Im+Ia
55 disp('Line current=' + complexstring(I) + 'A') //ans may

```



```
    vary due to roundoff error
56 mprintf("I=%fA having a phase angle of %f degrees\n"
    , abs(I) , (-1)*(acos(real(I)/abs(I)))*180/%pi)
```

Chapter 8

Forces And Torques In Electromagnetic Systems

Scilab code Exa 8.2 1Find forces on plunger at 1A rms 2Voltage applied for the cur

```
1 clc
2 x=0.01 //length in metres
3 L=0.03+(270*x*x) //equation provided in the textbook
4 mprintf("L(0.01)=%fH\n",L)
5 w=377 //angular frequency in rad/sec
6 XL=w*L
7 mprintf("XL=wL=%f \n",XL)//ans may vary due to
   toundoff error
8 I=1 //current in ampere
9 V=I*XL
10 mprintf("V=IXL=%fV\n",V)//ans may vary due to
   toundoff error
11 a=540 //comes from an equation in textbook,unit is
   henry/metre
12 f=(1/2)*(a*x)
13 mprintf(" f=%fN\n",f)
```
