

Scilab Textbook Companion for  
Linear Integrated Circuits  
by D. R. Choudhury<sup>1</sup>

Created by  
Vishal Changlani  
Electronics and Telecommunication  
Electronics Engineering  
VES Institute of Technology  
College Teacher  
None  
Cross-Checked by  
None

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Linear Integrated Circuits

**Author:** D. R. Choudhury

**Publisher:** New Age, New Delhi

**Edition:** 4

**Year:** 2010

**ISBN:** 978-81-224-3098-1

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
2 Operational Amplifier	5
3 Operational Amplifier Characteristics	26
4 Operational Amplifier Circuits	32
5 Comparators and Waveform Generators	45
6 Voltage Regulator	51
7 Active Filters	55
8 555 Timer	67
10 D to A and A to D Converters	69

# List of Scilab Codes

Exa 2.1	Design an amplifier for given conditions . . .	5
Exa 2.2	To calculate various parameters for given circuit . . . . .	6
Exa 2.3	To design an amplifier using single op amp .	7
Exa 2.4	To determine the various parameters for Non inverting amplifier . . . . .	7
Exa 2.6	To determine the values of Rc and Re . . . .	8
Exa 2.7	To determine the various parameters for basic differential amplifier . . . . .	9
Exa 2.8	To determine the output voltages vo1 and vo2	11
Exa 2.9	To find the differential voltage gain . . . . .	12
Exa 2.10	To find the value of Resistor R1 . . . . .	13
Exa 2.11	To design a Wildar current source . . . . .	14
Exa 2.12	To determine the values of Ic1 Ic2 and Ic3 .	15
Exa 2.13	To determine the value of Io . . . . .	16
Exa 2.14	To determine the values of Ic1 Ic2 and Rc .	17
Exa 2.15	To find the emitter current in transistor Q3	18
Exa 2.16	To calculate the difference between V1 and V2 for the level shifter . . . . .	19
Exa 2.17	To calculate collector current in each transistor and the output voltage under quiescent condition along with open loop voltage gain	20
Exa 2.18	To perform the dc analysis and to compute overall voltage gain . . . . .	23
Exa 3.1	To design an inverting amplifier using 741 opamp . . . . .	26
Exa 3.2	To calculate maximum output offset voltage along with value of Rcomp . . . . .	27

Exa 3.3	To find the change in output voltage due to change in temperature . . . . .	28
Exa 3.4	To find the slew rate of the opamp whose output is shown in figure . . . . .	29
Exa 3.5	To determine maximum peak to peak input signal that can be applied without distorting the output . . . . .	29
Exa 3.6	To determine whether IC 741 can be used or not for given specifications . . . . .	30
Exa 4.1	To design an adder circuit using an operational amplifier . . . . .	32
Exa 4.2	To find the output voltage for the adder subtractor circuit . . . . .	33
Exa 4.3	To design an operational amplifier to differentiate an input signal . . . . .	34
Exa 4.4	To determine various parameters for a lossy integrator . . . . .	36
Exa 4.5	To find R1 and Rf values in the lossy integrator	39
Exa 4.6	To calculate output of an operational amplifier to a step input of magnitude V and compare it with output of a low pass RC circuit . . . . .	40
Exa 4.7	To show that output is given by a differential equation . . . . .	42
Exa 4.8	To show that output is integral of input . . . . .	43
Exa 4.9	To set up an analog simulation to generate a sinusoidal signal . . . . .	43
Exa 5.1	To plot the transfer curve for opamp with given conditions . . . . .	45
Exa 5.2	To determine the upper and lower threshold voltages . . . . .	47
Exa 5.3	To calculate time period of the negative and positive portion of the output waveform . . . . .	48
Exa 5.4	To design a phase shift oscillator to oscillate at 100 Hz . . . . .	49
Exa 6.1	To calculate the output current coming from 7805 . . . . .	51

Exa 6.2	To calculate component values to get desired output voltage . . . . .	53
Exa 7.1	Design a second order Butterworth low pass filter . . . . .	55
Exa 7.2	Design a fourth order Butterworth low pass filter . . . . .	57
Exa 7.3	To determine order of a low pass Butterworth filter . . . . .	58
Exa 7.4	Design a second order Butterworth high pass filter . . . . .	59
Exa 7.5	Design a wide band pass filter . . . . .	61
Exa 7.6	Design a 50 Hz active notch filter . . . . .	62
Exa 7.7	Design a wide band reject filter . . . . .	63
Exa 7.9	Design a switched capacitor integrator . . . . .	64
Exa 8.1	To calculate value of Capacitor . . . . .	67
Exa 8.2	To calculate various parameters of Astable multivibrator . . . . .	68
Exa 10.1	To calculate output voltage for given 9 bit input . . . . .	69
Exa 10.2	To calculate LSB MSB and full scale output for an 8 bit DAC . . . . .	70
Exa 10.3	To calculate output voltage for different input	70
Exa 10.4	To calculate value of the resistor R of the integrator . . . . .	71
Exa 10.5	To find the equivalent digital number . . . . .	72

## Chapter 2

# Operational Amplifier

Scilab code Exa 2.1 Design an amplifier for given conditions

```
1 // Exa 2.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 // An amplifier( Refer Fig. 2.5(a) )
9 Acl = -10; // Closed loop gain
10 Ri = 10 * 10^3; // Input resistance of amplifier( )
11
12 // Solution
13
14 // Since it is mentioned to design an amplifier , it
    means to calculate values for Rf(Feedback
    resistance) and R1.
15 disp("Referring Fig. 2.5(a), we choose R1 as 10 k
    i.e equal to input resistance of amplifier.");
16 R1 = Ri;
17 // Acl = -1 * Rf/R1;
18 // Therefore;
```



```

19 Rf= - Acl * Ri;
20 printf(' The calculated value of Rf(Feedback
    resistane) is Rf = %d k . \n',Rf/1000);

```

---

Scilab code Exa 2.2 To calculate various parameters for given circuit

```

1 // Exa 2.2
2
3 clc;
4 clear;
5
6 // Given data
7
8 // An amplifier as given in Fig. 2.5(b)
9 R1 = 10*10^3; //Input resistance of amplifier ( )
10 Rf = 100*10^3; // Feedback resistance of amplifier
    ( )
11 vi = 1; // Input voltage applied (Volts)
12 RL = 25*10^3; // Load resistance ( )
13
14 // Solution
15
16 i1 = vi/R1; //Input current(A)
17 printf(' The value of input current = i1 = %.1f mA.
    \n ',i1*1000);
18 vo = -1*(Rf/R1)*vi; // output voltage(V)
19 printf(' The value of output voltage = vo = %d V. \n
    ',vo);
20 iL = abs(vo)/RL; // Load current(A)
21 printf(' The value of load current = iL = %.1f mA.',
    iL*1000);
22 disp(" The direction of iL is as shown in Fig. 2.5(b)
    .");
23 // iTot = i1 + iL;
24 iTot = i1+iL; // Total current(A)

```

```

25 printf(' The value of total current = io = %.1f mA.
        ', iTot*1000);
26 disp(" In an inverting amplifier , for a +ive input ,
        output will be -ive , therefore the direction of
        io is as shown in Fig. 2.5(b).");

```

---

**Scilab code Exa 2.3** To design an amplifier using single op amp

```

1 // Exa 2.3
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Single op-amp amplifier .
9 ACL = 5; // Required gain(positive)
10
11 // Solution
12
13 disp(" Since the gain is positive , we have to make a
        non-inverting amplifier.");
14 disp(" Referring Fig. 2.7(a), select R1 = 10 k .");
15 R1 = 10*10^3; //Input resistance in
16 // Then from eqn. (2.20), we get , ACL = 1+ (Rf/R1);
17 // Therefore
18 Rf = (ACL-1)*R1; //Feedback resistance in
19 printf(' The calculated feedback resistance of
        amplifier i.e Rf = %d k .\n', Rf/1000);

```

---

**Scilab code Exa 2.4** To determine the various parameters for Non inverting amplifie

```

1 // Exa 2.4

```

```

2
3 clc;
4 clear;
5
6 // Given data
7
8 // Referring circuit given in Fig. 2.7(a)
9 R1= 5*103; //
10 Rf=20*103; //
11 Vi=1; // Input voltage(V)
12 RL=5*103; // Load resistor( )
13
14
15 // Solution
16
17 Vo= (1+(Rf/R1))*Vi; // Output voltage(V)
18 printf('The output voltage i.e vo = %d V. \n',Vo);
19 AcL=Vo/Vi; // Closed loop Gain
20 printf(' The closed loop gain i.e Acl = %d. \n',
    AcL);
21 IL=Vo/RL; // Output current(A)
22 printf(' The load current i.e iL = %d mA. \n',IL
    *1000);
23 I1=Vi/R1; // Input current(A)
24 Io=IL+I1; // Total current(A)
25 printf(' The output current i.e io = %.2f mA. \n',
    Io*1000);
26 disp("The op-amp output current Io flows outwards
    from the output junction.");

```

---

**Scilab code Exa 2.6** To determine the values of Rc and Re

```

1 // Exa 2.6
2
3 clc;

```

```

4 clear;
5
6 // Given data
7
8 // Referring circuit shown in Fig. 2.11(a)
9 B=200; // Current gain
10 Icq = 100*10^-6; // Amperes
11 ADM = 500; // Voltage gain for differential mode
    signal
12 CMRR_db = 80; // in dB(Common mode rejection ratio)
13
14 // Solution
15
16 // Since gm = Icq/Vt therefore ,
17 gm = Icq/(25*10^-3); // for Vt = 25 mV
18
19 printf('Using Eq. 2.50, we have ADM = -gm*Rc so from
    this we get Rc as ');
20 Rc =abs(- ADM/gm);
21 printf(' %d k . \n ',Rc/1000);
22 printf('Since CMRR = 80 dB converting it into non dB
    value so CMRR = ');
23 CMRR = 10^(CMRR_db/20);
24 printf(' %d. \n ',CMRR);
25 printf('Using Eq. 2.55, we get value of Re as ');
26 // CMRR = 1+ 2*gm*Re; therefore
27 Re = (CMRR-1)/(2*gm);
28 printf(' %.2f M . \n ',Re/10^6);

```

---

Scilab code Exa 2.7 To determine the various parameters for basic differential amp

```

1 // Exa 2.7
2
3 clc;
4 clear;

```

```

5
6 // Given data
7
8 // Fig. 2.11(a) shows the basic differential
  amplifier
9 Rc = 2*10^3; //
10 Re = 4.3*10^3; //
11 Vcc = 5 ; // Vcc = |VEE|
12 Bo = 200;
13 Vbe = 0.7; // Volts
14 Vt=25*10^-3; // Volts
15
16 // Solution
17
18 printf(' For V1 = V2 = 0, applying KVL for the base
  emitter loop , we may write ,');
19 printf('\n Vbe+2*(1+Bo)*Ibq*Re-Vee = 0.\n From
  this we get Ibq as ');
20 Ibq = (Vcc-Vbe)/(2*(1+Bo)*Re);
21 printf(' %.2f A . \n ',Ibq*10^6);
22 Icq = Bo*Ibq;
23 printf(' The value of Icq = %.3f mA. \n ',Icq*10^3);
24 Vo1 = Vcc - Rc*Icq;
25 printf(' The value of Vo1 = Vo2(due to symmetry) = %
  .3f V. \n ',Vo1);
26 Vceq = Vo1-(-Vbe);
27 printf(' The value of Vceq = %.3f V. \n ',Vceq);
28 gm = Icq/Vt;
29 r_pi = Bo/gm;
30 // using wq. 2.50 ADM = -gm*Rc;
31 ADM = -gm*Rc;
32 // using equation 2.53(a) Acm can be given as
33 ACM = (-Bo*Rc)/(r_pi+2*(1+Bo)*Re);
34
35 CMRR = ADM/ACM;
36 CMRR_db = 10*log(CMRR);
37 printf(' The remaining values are as follows: \n
  ADM = %.2f. \n ACM = %.2f. \n CMRR = %.1f = %.1

```

```
f dB.\n',ADM,ACM,CMRR,CMRR_db);
```

---

**Scilab code Exa 2.8** To determine the output voltages vo1 and vo2

```
1 // Exa 2.8
2
3 clc;
4 clear;
5
6 // Given data
7
8 // With reference to differential amplifier designed
   in example 2.6
9 // 2 applied inputs are
10 t = [0 :1:100]; // time in mSec
11 v1= 15*sin(2*pi*60*t) + 5*sin(2*pi*1000*t); //
   in mV
12 v2 = 15*sin(2*pi*60*t) - 5*sin(2*pi*1000*t); //
   in mV
13 fi = 60; // frequency of interference signal(Hz)
14 fo = 1000; // frequency at which signal is to be
   processed(Hz)
15
16 // Solution
17
18 // We know from Example 2.6
19 gm=4; // m
20 Rc=125 ; // k
21 Re= 1.25; // k
22 Bo=200;
23 r_pi= Bo/gm; // in k
24
25 ADM=-500; // from example 2.6(given)
26 // From eq. 2.53(a) we get ACM as
27 ACM = (-Bo*Rc)/(r_pi*1000+2*(1+Bo)*Re);
```

```

28 printf(' The value of ACM = %.2f \n',ACM);
29 // from eqns 2.56(a and b)
30 vDM = (v1-v2)/2;
31 vCM = (v1+v2)/2;
32
33 //from Eq. 2.57(a and b)
34 vo1 = ADM*vDM+ACM*vCM;
35 vo2 = -ADM*vDM + ACM*vCM;
36
37 printf(' Therefore final equations are- \n');
38 disp(" vo1 = -2500*sin(2*%pi*1000*t) -0.75*sin(2*%pi
      *60*t) mV ");
39 disp(" vo2 = 2500*sin(2*%pi*1000*t) -0.75*sin(2*%pi
      *60*t) mV");

```

---

**Scilab code Exa 2.9** To find the differential voltage gain

```

1 // Exa 2.9
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A differential amplifier with single ended output
9 // Referring circuit given in Fig. 2.9
10 Bo = 100; // current gain
11 Re = 150; //
12 Rc = 10*10^3; //
13 IQ = 0.5*10^-3; // mA
14 VT = 25*10^-3; // mV
15
16 // Solution
17
18 ICQ = IQ/2;

```

```

19 gm = ICQ/VT; // in
20 r_pi = Bo/gm;
21
22 printf(' The differential mode gain for a single
        stage is found from the equivalent circuit shown
        in fig.(ii)\n on page no. 64 and is equal to ');
23 ADM = (1/2)*(Bo*Rc/(r_pi+(1+Bo)*Re));
24 printf(' %d V/V. \n', round(ADM));
25 printf(' \n We can see that sign of ADM is positive
        because the output is taken at the collector of
        Q2\n whereas input is applied at the base of Q1.
        \n');

```

---

**Scilab code Exa 2.10** To find the value of Resistor R1

```

1 // Exa 2.10
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A current mirror as shown in Fig. 2.16
9 Ic = 1; // mA
10 Vcc = 10; // Volts
11 B = 125;
12 Vbe = 0.7; // Volts
13
14 // Solution
15
16 // Case(1)- When Ic = 1mA.
17 printf(' From equations 2.67 and 2.68 we get R1 as -
        \n\n');
18 // Ic = (B/(B+2))*((Vcc-Vbe)/R1);
19 // Therefore

```



```

20 R1 = (B/(B+2))*((Vcc-Vbe)/Ic);
21 printf(' The value of R1 when Ic = 1 mA is R1 = %.2 f
      k . \n',R1);
22
23 // Now case(2)- when Ic = 10 A .
24 Ic1 = 10*10^-3; // in mA
25 R2 = (B/(B+2))*((Vcc-Vbe)/Ic1);
26 printf(' The value of R1 when Ic = 10 A is R1 = %d
      k . \n',R2);

```

---

**Scilab code Exa 2.11** To design a Wildar current source

```

1 // Exa 2.11
2
3 clc;
4 clear;
5
6 // Given data
7
8 Io=10*10^-6; // Output current(A)
9 Vcc= 10; // Volts
10 B=125; // current gain
11 Vbe=0.7; // Voltage between base and emitter(V)
12 Vt=25*10^-3; // volt equivalent of temperature at
      room temperature(V)
13
14 //Solution
15
16 disp(" Let Iref = 1 mA then using equation 2.79, we
      get- ");
17
18 Iref=1*10^-3; // we choose
19
20 R1=(Vcc-Vbe)/Iref;
21 printf('\n The value of R1 = %.1 f k . \n',R1/1000)

```

```

    ;
22
23 disp(" Using equation 2.74 , we get-");
24 Re=(Vt/((1+1/B)*Io))*log(Iref/Io);
25 printf('\n The value of Re = %.1f k . \n',Re/1000)
    ;
26
27 disp(" Thus, it is clearly seen that Wildar circuit
    allows the generation of small currents using
    relatively small resistors.");

```

---

**Scilab code Exa 2.12** To determine the values of  $I_{c1}$   $I_{c2}$  and  $I_{c3}$

```

1 // Exa 2.12
2
3 clc;
4 clear;
5
6 // Given data
7
8 //Referring fig No. 2.21, we get
9
10 Vcc=9; // Volts
11 Vbe=0.7; // Volts
12 R1=30*10^3; //
13 Re=1.94; //
14 B=125; // current gain
15 VT = 25*10^-3; // Volts
16
17 // Solution
18
19 Iref= (Vcc-Vbe)/R1;
20 printf(' The value of Iref = %.3f mA. \n ',Iref
    *1000);
21 // Also at Node A.- Iref=Ic+3*Ib. i.e Ic = Iref*(B/(

```

```

    B+2))
22 // Assuming IB3 of widlar source negligible.
23 // Therefore putting back value of Iref we get
    values of Ic1
24 Ic=Iref*(B/(B+3));
25 Ic_mA = Ic*1000; // in mA
26
27 printf('\n The value of Ic1 = Ic2 = %.3f mA. \n ',
    Ic*10^3);
28 // Calculating Ic3 using eqn 2.74 ;
29
30 // Re = (VT/(Ic3*(1+1/B)))*ln(ic_mA/Ic3);
31 // Re - (VT/(Ic3*(1+1/B)))*ln(ic_mA/Ic3) = 0;
32
33 deff('y = f(x)', 'y = (Re-(VT*log(Ic_mA/x))/(x
    *(1+1/B)))'); // here x = Ic3
34 [x,v,info]= fsolve(0.01,f);
35
36 printf(' \n By trial and error method, we get Ic3 =
    %.4f mA.\n',x);

```

---

**Scilab code Exa 2.13** To determine the value of  $I_o$

```

1 // Exa 2.13
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Refering Fig. 2.24 we get ,
9
10 B=100; // Current gain
11 Vbe=0.7; // Volts
12 Vcc=5; // Volts

```

```

13 R1= 10*10^3; //
14
15 // Solution
16
17 printf(' Referring to circuit shown in Fig. 2.24 and
        using KVL we get Iref as ');
18 // KVL for loop 1
19 // Vcc-Vbe-R1*Iref+Vcc = 0;
20 // Therefore
21 Iref= (2*Vcc-Vbe)/R1;
22 printf(' %.2f mA. \n',Iref*1000);
23 // At emitter node E., Iref=2*Ie (Assuming identical
        transistors
24 //Then;
25 Ic= B*Iref/(2*(1+B));
26
27 printf(' Due to mirror effect , Io = Ic1 = Ic = %.2
        f mA. \n ',Ic*1000);

```

---

**Scilab code Exa 2.14** To determine the values of Ic1 Ic2 and Rc

```

1 // Exa 2.14
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Fig. 2.25 shows circuit for current example
9 Vo = 6; // Volts
10 B = 200;
11 R1 =15; // k
12 R2 = 2.8; // k
13 Vcc = 12; // volts
14 Vbe = 0.7; // Volts

```

```

15
16 // Solution
17
18 Iref = (Vcc-Vbe)/R1;
19 I1 = Vbe/R2;
20
21 // At node A- Iref = Ic1 + 2IB + I1;
22 //           Iref = Ic1*(1+2/B)+I1;
23 // Therefore; we get Ic1 as-
24 Ic1 = (Iref-I1)/(1+2/B);
25 printf(' The value of Ic1 = %.3f mA.\n',Ic1 );
26 printf(' The value of Ic2 = Ic1 due to mirror
    effect. ');
27 // by KVL to outer loop we get Rc value
28 // 12V = Ic2*Rc +Vo;
29 Rc = (Vcc-Vo)/Ic1;
30 printf('\n The value of Rc = %d k . \n',Rc);

```

---

**Scilab code Exa 2.15** To find the emitter current in transistor Q3

```

1 // Exa 2.15
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Referring Fig. 2.26, we get
9 Vcc=10; // Volts
10 R1= 4.7*10^3; // k Ohms
11 B=100; // Current gain(>>1)
12 Vbe=0.75; // Volts
13
14 // Solution
15

```

```

16 disp(" Node    A    is at transistor Q1, Node
      B    is at transistor Q2 and Node    C    is
      at transistor Q3.");
17
18 printf('\n From Fig. 2.26 at node    A    . I = Ic1
      + Ib1 + I 1    ...Eqn(1) ');
19 printf(' \n Also at node    B    . I 1    = Ic2 + Ib3
      . ');
20 printf('\n Putting value of I 1    in eqn(1) we get
      I = (approximately) 2Ic. \n');
21
22 I = (Vcc-Vbe)/R1; // By o h m s law
23
24 printf('\n The calculated value of I = %.2f mA. \n'
      , I*1000);
25
26 Ic3 = I/2;
27
28 printf(' The collector current of Q3 is equal to the
      collector current of Q1 and Q2 due to mirror
      action. \n Therefore, the emitter current IE3 =
      Ic3 = Ic = I/2 = %.2f mA. \n ',Ic3*1000);

```

---

**Scilab code Exa 2.16** To calculate the difference between V1 and V2 for the level s

```

1 // Exa 2.16
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A level shifter as shown in fig. 2.31
9 // Assuming Ideal silicon transistors
10 Vbe = 0.7; // Volts

```

```

11 // B(current gain) has very large values
12 Vcc = 15; // Volts
13 Rc = 10*10^3; //
14 Re = 5000; //
15
16 // Solution
17
18 printf(' From fig. 2.31 we get that, transistors Q1
        and Q2 form a current mirror.\n');
19 printf(' so Ic1 = Ic2 = I and that can be found by
        Ohms law as ');
20 I = (Vcc - Vbe)/Rc; //
21 printf(' I = Ic2 = %.2f mA. \n', I*1000 );
22 printf(' Now, the difference V1-V2 can be found
        using KVL as ');
23 dV = Vbe + I * Re; // KVL between end points
24 printf(' %.2f V. \n',dV);

```

---

**Scilab code Exa 2.17** To calculate collector current in each transistor and the out

```

1 // Exa 2.17
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Fig. 2.33- Internal circuit of Motorola MC 1530
9 B = 100;
10 Vbe = 0.7; Vd = 0.7; Vcc = 6; Vee = 6; Vo = 5; Vt=
    0.026; // Volts
11 // Vt = volt equivalent of temperasture at room
    temperature
12 R1 = 2.2; R2 = 7.75; R3 = 7.75; R4 = 1.5; R5 = 3.2;
    R6 = 1.5; R7 = 3;

```

```

13 R8 = 3.4; R9 = 6; R10 = 30; R11 = 5; // All in k
14
15 // Solution
16
17 printf(' The d.c. analysis is performed by assuming
        that both the inverting and non-inverting
        terminals are at ground potential. ');
18
19 Vbn1 = (-Vee+Vd+Vd)*R5/(R4+R5);
20 printf('\n The voltage Vbn1 at base of transistor
        Q1 w.r.t ground N = %.2f V. \n',Vbn1);
21 I1 = (Vee + Vbn1 - Vbe)/R1;
22 printf('\n The current through emitter of Q1 i.e I1
        = %.3f mA. \n',I1);
23 printf(' If the base current of Q1 is neglected ,
        then Iq(current through collector of Q1) = I1 = %
        .3f mA. \n',I1);
24
25 printf('\n under dc conditions , half of the Iq flows
        through each transistors Q2 and Q3. Therefore Ic2
        = Ic3 = %.3f mA. \n',(I1/2));
26 Vc2 = Vcc - R2*(I1/2);
27 printf(' The voltage at collector of Q2 and Q3 = Vc2
        = Vc2 = %.2f V. \n',Vc2);
28 printf('\n By looking at the Internal circuit , the
        voltages at the base of Q4 and Q5 i.e Vb4 = Vb5
        = %.2f V. \n',Vc2);
29 Ve4 = Vc2 - Vbe;
30 printf(' The dc voltage at the emitter of Q4 = Ve4 =
        %.2f V.\n',Ve4);
31 I6 = Ve4/R6;
32 printf('\n The current through R6 = %.3f mA. \n',I6
        );
33 printf(' This current divides equally in transistors
        Q4 and Q5 i.e Ic4 = Ic5 = %.3f mA. \n',(I6/2));
34 Vc5 = Vcc-(I6/2)*R7;
35 Ve6 = Vc5-Vbe;
36 printf('\n The collector voltage of Q5i.e Vc5 and

```



```

        emitter voltage of Q6 i.e are %.2f V and %.2f V
        respectively. \n',Vc5,Ve6);
37 I8 = (Vee-Vd)/R8;
38 printf(' Transistors Q7 along with diode D3 forms a
        current mirror of the type shown in fig. 2.15.
        Hence, Ic7 = I8 = %.2f mA. \n',I8);
39
40 Vb8 = Vbe + Vd - Vee;
41 printf('\n The voltage at the base of Q8 i.e Vb8 = %
        .2f V. \n',Vb8);
42 I9 = (Ve6-Vb8)/R9;
43 I10 = I8-I9;
44 printf(' The currents along resistors R9 and R10 are
        %.2f mA and %.2f mA respectively. \n',I9,I10 );
45
46 Vo_dc = I10*R10 + Vb8;
47 printf(' The voltage at output terminal = %.2f V (
        approximately 0) as expected. \n',Vo_dc);
48
49 printf('\n\n');
50 printf('////////////////////////////////////FOR over all
        voltage gain////////////////////////////////////\n\n');
51 h_fe = 100;
52 printf(' we first calculate the voltage gain of the
        differential amplifier stages.\n');
53 // since Ic2 = Ic3 = Ic4 = Ic5 = approx 0.50 mA
54 Ic = 0.5; // in mA
55 h_ie = h_fe*Vt/Ic;
56
57 RL2 = (1/R2 + 1/h_ie)^-1;
58 RL3 = RL2;
59
60 Av1 = h_fe*RL2/h_ie;
61 printf(' The output of the first stage is double
        ended, its differential gain is given as %d. \n',
        Av1);
62
63 Av2 = -(1/2)*(h_fe*R7/h_ie);

```

```

64 printf(' The output of the second stage is single
        ended, so its differential gain is %.1f. \n',Av2)
        ;
65
66 printf(' The third stage is emitter follower , so ,
        Av3 = (approximately)1. \n');
67 Av3 = 1;
68 Av4 =- R10/R9;
69 printf(' The last output stage uses voltage shunt
        feedback network R9–R10, \n So, Av4 = (
        appromately) %d. \n',Av4);
70
71 Av = Av1 * Av2 * Av3 * Av4;
72 printf(' \n\n Hence the over all op–amp gain is , Av
        = %d. \n ' ,Av);

```

---

**Scilab code Exa 2.18** To perform the dc analysis and to compute overall voltage gain

```

1 // Exa 2.18
2
3 clc;
4 clear;
5
6 // Given data
7
8 // op–amp circuit as shown in Fig. 2.35
9 h_fe = 100;
10 Vbe = 0.7; Vcc = 15; Vee = 15; Vt = 0.025; // Volts
11 // Vt = volt equivalent at room temperature
12 R1 = 20; R2 = 20; R3 = 28.6; R6 = 3; R8 = 2.3;
13 R9 = 3; Ra = 15.7; // All in k
14
15 // Solution
16
17 printf('It can be seen that the circuit has the four

```

```

    stages: \n Dual-input , differential output. \n
    Dual-input , single ended output. \n Level
    translator. \n Emitter follower.\n ');
18
19 printf('\n\n For d.c. analysis , assume that the
    input terminals are shorted to ground.\n');
20 I = (Vee-Vbe)/R3;
21 printf(' The reference current I of the current
    minor Q3-Q4 is obtained as I = %.1f mA. \n',I);
22 printf('\n Due to current mirror action , Icq4 = I =
    %.1f mA and Icq1 = Icq2 = Icq/2 = %.3f mA. \n',I,
    I/2);
23 Vcq1 = Vcc-(I/2)*R1;
24 printf(' The collector voltages for Q1 and Q2 are
    Vcq1 = Vcq2 = %d V. \n',Vcq1);
25 Veq5 = Vcq1-Vbe;
26 printf('\n The voltage at emitter of Q5 and Q6 is
    Veq5 = Veq6 = %.1f V. \n',Veq5);
27 Icq7=4*I;
28 printf(' Since the area of Q7 is 4 times that of Q3
    and Q4, the transistor Q7 supplies a current Icq7
    = %d mA. \n',Icq7);
29 printf('\n Thus, collector currents of Q5 and Q6 are
    Icq5 = Icq6 = %d mA. \n',Icq7/2 );
30 Vcq6 = Vcc-(Icq7/2)*R6;
31 printf(' Hence, collector voltage of Q6 is Vcq6 = %d
    V. \n',Vcq6);
32 Veq8 = Vcq6+Vbe;
33 printf('\n This causes a voltage at the emitter of
    pnp transistor Qr i.e Veq8 = %.1f V. \n',Veq8);
34 Ieq8 = (Vcc-Veq8)/R8;
35 printf(' The emitter current of Q8 i.e Ieq8 = %d mA.
    \n',Ieq8);
36 Va = -Vee + Ieq8*Ra;
37 printf('\n The voltage Va at the collector of Q8 i.e
    Vcq8 or the base of Q9 i.e Vbq9 = %.1f V. \n',Va
    );
38 printf(' Since the emitter of Q9 will be 0.7 V below

```

```

        the base terminal, \n the voltage at the output
        terminal 6 is 0 V as is expected.');
```

39

```

40 Vo = 0; // output voltage (Volts)
41 Ieq9 = (Vo-(-Vee))/R9;
42 printf('\n\n The emitter current of Q9 i.e Ieq9 = %d
        mA. \n',Ieq9);
43
44 printf('\n\n//////////////////////////////////////////a.c. analysis
        ////////////////////////////////////////////\n\n');
```

45

```

46 h_ie1 = (h_fe*Vt)/(I/2);
47 printf(' The ac emitter resistance of the transistor
        Q1-Q2 is h_ie = %.1f k . \n',h_ie1);
48 h_ie5 = (h_fe*Vt)/(Icq7/2);
49 printf(' The ac emitter resistance of the transistor
        Q5-Q6 is h_ie = %.1f k . \n',h_ie5);
50 RL1 = (1/R1 + 1/h_ie5)^-1;
51 printf(' Since , emitter of Q5-Q6 is at ground
        potential under ac conditions,\n the effective
        load for Q1-Q2 is RL1 = RL2 = %.1f k .\n',RL1);
52 ADM1 = (h_fe*RL1)/h_ie1;
53 printf(' The voltage gain of first differential
        stage is ADM1 = %d. \n',ADM1);
54 ADM2 = (-1/2)*(h_fe*R6)/h_ie5;
55 printf(' The voltage gain of second differential
        stage is ADM2 = (approximately) %d. \n',ADM2);
56 A3 = -Ra/R8;
57 printf(' The gain of the level translator stage is
        A3 = %.2f. \n',A3);
58 printf(' The last stage is emitter follower , so its
        voltage gain Av4 = (approximately) 1.');
```

59 Av4 = 1;

```

60 Av = ADM1 * ADM2 * A3 * Av4;
61 printf('\n\n So, the overall voltage gain is Av = %d
        . \n',Av);
```

---

## Chapter 3

# Operational Amplifier Characteristics

Scilab code Exa 3.1 To design an inverting amplifier using 741 opamp

```
1 // Exa 3.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 //Fig. 3.1(e) shows an inverting amplifier
9 ACL = -10; // open loop gain of ap-amp 741
10 R1 = 10*10^6; // Input impedance in
11
12 // Solution
13
14 printf(' In fig. 3.1(e), to set input impedance Ri =
15         10 M , pick R1 = 10 M . ');
16 // since , ACL = - Rf/R1;
17 // Therefore ,
18 Rf = -ACL*R1;
19 printf('\n The calculated value of Rf = %d M . \n
```

```

    ',Rf/10^6);
19 printf(' Choose Rt = 47 k . \n ');
20 Rt = 47*10^3; //
21 Rs = (Rt^2)/(Rf-2*Rt);
22 printf(' Calculated Rs = %d . ',Rs);

```

---

**Scilab code Exa 3.2** To calculate maximum output offset voltage along with value of

```

1 // Exa 3.2
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Fig. 3.2(b) represents the non-inverting
   amplifier
9 R1 = 1000; //
10 Rf = 10000; //
11 Vios = 0.01; // Volts
12 Ib = 300*10^-9; // Amperes
13 Ios = 50*10^-9; // Amperes
14
15 // Solution
16
17 printf(' From equation 3.24, we get VoT = ');
18 VoT = (1+(Rf/R1))*Vios + Rf*Ib ;
19 printf(' %d mV. \n ',VoT*1000);
20
21 Rcomp = 1/((1/R1) + (1/Rf)); // Rf || R1
22 printf(' The value of Rcomp needed to reduce the
   effect of Ib is %.1f . \n ',Rcomp);
23 printf(' With Rcomp in the circuit , VoT = ');
24 VoT1 = (1+(Rf/R1))*Vios + Rf*Ios;
25 printf(' %.1f mV. \n ' , VoT1*10^3);

```

```

26 printf('\n It can be seen from this example that it
    is the input offset voltage which is more
    responsible\n for producing an output offset
    voltage compared to input bias current Ib or the
    input offset current Ios.');
```

---

```

27 // The answer provided in the textbook is wrong.
```

**Scilab code Exa 3.3** To find the change in output voltage due to change in temperature

```

1 // Exa 3.3
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A non-inverting amplifier
9 G=100; // Gain of amplifier at 25 degree celsius
10 T1 = 25; // degree celsius
11 T2 = 50; // degree celsius
12 VoT=0.15; // Offset voltage drift in mV/
    degreecelsius
13
14 // Solution
15
16 printf(' Input offset voltage due to temperature
    rise = ');
17 Vos=VoT*(T2-T1);
18 printf(' %.2f mV. \n ',Vos);
19 printf(' Due to this input change, the output
    voltage will change by ');
20 Vo=Vos*G;
21 printf(' %d mV. \n ',Vo);
22 printf(' This could represent a very major shift in
    the output voltage.');
```

---

**Scilab code Exa 3.4** To find the slew rate of the opamp whose output is shown in fi

```
1 // Exa 3.4
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Fig. 3.13 shows output of an op-amp voltage
   follower
9 F =2; // frequency in MHz
10 Vipp= 8; // Input voltage (Peak to peak) in volts
11
12 // Solution
13
14 printf(' Since the frequency is given we can get
   time period as T = %.1f sec . \n\n',1/F);
15
16 printf(' Since , the slew rate is defined as the
   maximum rate of change of the output, \n so from
   Fig. 3.13, it can be seen that , maximum change
   in output is 6V in 0.25 sec .');
17
18 dVo=6;
19 dT=0.25 ; // sec
20 SR=dVo/dT;
21
22 printf('\n\n Therefore , the slew rate of the op-amp
   = %d V/ sec . \n',SR);
```

---

**Scilab code Exa 3.5** To determine maximum peak to peak input signal that can be app



```

1 // Exa 3.5
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A 741C op-amp is used
9 G=50; // Gain of op-amp
10 F=20*10^3; // Voltage gain Vs frequency curve is
    flat upto this frequency(Hz)
11
12 // Solution
13
14 printf(' The slew rate for 741C is 0.5 V/ sec . \n')
    ;
15 SR=0.5; // V/ sec
16 printf(' From Eq. 3.51, we can get Vm as : ');
17 // SR = 2*pi*f*Vm/10^6; // V/ sec
18 Vm = SR*10^6/(2*pi*F);
19 printf('%.2f V. \n ',Vm);
20 Vpp=2*Vm;
21 printf(' The peak to peak output voltage = %.2f V. \
    n',Vpp);
22 printf(' Hence, for the output to be undistorted
    sine wave, the maximum input signal should be
    less than %d mV peak to peak.\n',(Vpp*10^3)/G);

```

---

**Scilab code Exa 3.6** To determine whether IC 741 can be used or not for given speci

```

1 // Exa 3.6
2
3 clc;
4 clear all;
5

```

```

6 // Given data
7
8 Vinpp=500; // Peak to peak input voltage in mV
9 Vopp= 3; // Peak to peak output voltage in V
10 Tr= 4; // Rise time in sec
11
12 // Solution
13
14 printf('Since the output has a peak amplitude
        greater than 1 volt , the slew rate is the
        limiting factor.\n ');
15
16 // The slew rate = dVo/dT;
17
18 printf('\n From the definition of rise time, it is
        time the output takes to change from 10 to 90
        percent of the final value. \n \n Therefore ,the
        change in the output voltage dVo in 4 microsec is
        equal to :');
19 dVo = (0.9-0.1)*Vopp;
20 printf(' %.1f V. \n',dVo);
21
22 SR = dVo/Tr;
23 printf(' The slew rate is %.1f V/ sec . \n ',SR);
24 printf('\n Since , the slew rate of 741 is 0.5 V sec
        , it is too slow and cannot be used.');
```

---

# Chapter 4

## Operational Amplifier Circuits

Scilab code Exa 4.1 To design an adder circuit using an operational amplifier

```
1 // Exa 4.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 // To design an adder circuit as shown in Fig. 4.2(a
9 // )
10 //  $V_o = -(0.1*V_1+V_2+10*V_3)$ ;
11 //  $V_1, V_2, V_3$  are the inputs
12
13 // Solution
14 printf(' The output in Fig. 4.2(a) is - \n  $V_o = -[($ 
15 //  $R_f/R_1)*V_1 + (R_f/R_2)*V_2 + (R_f/R_3)*V_3]. '$  ');
16 printf('\n The desired output is -\n  $V_o = [(0.1)*V_1$ 
17 //  $+ (1)*V_2 + (10)*V_3]. '$  ');
18 printf('\n\n Comparing above two equations, ');
19 printf('\n We can say, Let  $R_f = 10 \text{ k}$  ,  $R_1 = 100 \text{ k}$ 
20 // and  $R_2 = 10 \text{ k}$  and  $R_3 = 1 \text{ k}$  .\n');
```

```
18 printf('\n Thus, the desired output expression is
    obtained.');
```

---

**Scilab code Exa 4.2** To find the output voltage for the adder subtractor circuit

```
1 // Exa 4.2
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Added-subtractor as shown in fig. 4.4(a).
9 R1=40*10^3; //
10 R2=25*10^3; //
11 R3=10*10^3; //
12 R4=20*10^3; //
13 R5=30*10^3; //
14 Rf=50*10^3; //
15 V1=2; // Volts
16 V2=3; // Volts
17 V3=4; // Volts
18 V4=5; // Volts
19
20 // Solution
21
22 printf('The negative sum is obtained by setting V3=
    V4=0. Thus,\n ');
23 Vo1=-(Rf/R1)*V1-(Rf/R2)*V2;
24 printf(' Vo1 = %.1f Volts. \n ',Vo1);
25 printf('\n Now set V1=V2=0 to find the output
    voltage due to V3 and V4. \n The voltage Vo2 at
    the positive terminal due to V3 and V4 can be
    found by using superposition theorem as shown in
    Fig. 4.4(b) as \n ');
```

```

26
27 R1le1=( 1/R4 + 1/R5)^-1;
28 R1le11=(1/R3+1/R5)^-1;
29 Vo2= (R1le1/(R3+R1le1))*V3+ (R1le11/(R1le11+R4))*V4;
30 printf(' Vo2 = %.3f Volts. \n ',Vo2 );
31 printf('\n The output voltage Vo3 due to V3 and V4
    now can be determined from the equivalent circuit
    of Fig. 4.4(c) as \n ');
32 R1le12=(1/R1+1/R2)^-1;
33 Vo3=(1+(Rf/R1le12))*Vo2;
34 printf(' Vo3 = %.3f Volts. \n ',Vo3);
35 printf('\n The total output voltage V0 is given as
    sum of Vo1 + Vo3.\n ');
36 Vout=Vo1+Vo3;
37 printf(' The output voltage = %.3f Volts. \n ',Vout)
    ;
38 printf('\n\n The equivalent circuit at various in
    between steps are shown in Fig. 4.4(b-c).');

```

---

**Scilab code Exa 4.3** To design an operational amplifier to differentiate an input s

```

1 // Exa 4.3
2
3 clc;
4 clear;
5
6 // Given data
7
8 // An op-amp differentiator
9 fa = 100; // Hz
10 Vpp = 1; // Volts
11
12 // Solution
13
14 printf('Select , Fa = fmax = 100 Hz.\n');

```

```

15 printf(' Let , C1 = 0.1 F .\n');
16 C1 = 0.1*10^-6; // Farads
17 // since Fa = 1/(2*pi*Rf*C1);
18 // Therefore ,
19 Rf = 1/(2*pi*fa*C1);
20 printf(' Therefore , the calculated value of Rf = %.1
      f k . \n',Rf/1000);
21
22 printf(' Select , fb = 10*Fa = 1000 Hz.\n');
23 fb = 1000; // Hz
24 // Therefore
25 R1 = 1/(2*pi*fb*C1);
26 printf(' The calculated value of R1 = %.2 f k . \n',
      R1/1000);
27 // Since , RfCf = R1C1
28 // Therefore we get ,
29 Cf = R1*C1/Rf;
30 printf(' The calculated value of Cf = %.2 f F . \n',
      Cf*10^6);
31
32 printf('\n\n For a sinusoidal input - \n\n');
33 disp(" since , vi = sin(2*pi*100*t), ");
34 disp("From Eq. 4.69, vo = -Rf*C1* d/dt(vi), ");
35 disp("Above equation yield following result once
      solved- vo = -cos(2*pi*100*t).");
36 printf('\n The input and output waveforms are shown
      in Graphic window 0 ans 1 respectively. \n\n');
37 // plotting wave forms
38
39 t = [0:%pi:13*pi];
40 figure(0);
41
42 a=gca(); // Handle on axes entity
43 a.x_location = "origin";
44 a.y_location = "origin";
45 plot2d(t,sin(2*pi*100*t));
46 title('Sine-wave-input ', "color", "Red", "fontsize", 3);
47 figure(1);

```

```

48
49 a=gca(); // Handle on axes entity
50 a.x_location = "origin";
51 a.y_location = "origin";
52 plot2d(t,-cos(2*pi*100*t));
53 title('Cosine-wave-output','color',"blue","fontsize"
      ,3);
54
55 printf('\n For a square wave input -\n\n');
56 printf('\n For a square wave input, say 1 V peak and
      1 KHz,\n The output waveform will consist of
      positive and negative spikes of magnitude Vsat\n
      which is approximately 13 V for 15 V op-amp
      power supply.\n\n');
57 printf(' During the timeperiods for which input is
      constant at 1V, the differentiated output
      will be zero. \n However, when input transits
      between 1V levels, \n the slope of the input is
      infinite for an ideal square wave. \n\n The
      output, therefore, gets clipped to about 13V
      for a 15 V op-amp power supply. ');
58
59 printf('\n\n The output of a square wave input is a
      spike output as shown in Fig. 4.22(b). \n');

```

---

**Scilab code Exa 4.4** To determine various parameters for a lossy integrator

```

1 // Exa 4.4
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Referring integrator circuit in Fig. 4.23(c)

```

```

 9 R1 = 10*1000; //
10 Rf = 100*10^3; //
11 Cf = 10*10^-9; // Farads
12
13
14 // Solution
15
16 printf('For the given component values, the lower
        frequency limit of integration fa is ');
17 fa = 1/(2*pi*Rf*Cf);
18 printf('%d Hz \n\n',fa);
19 printf(' For 99 percent accuracy, the input
        frequency should be at least one decade above fa.
        \n However, there is an limit up to which
        circuit will integrate and is determined by the
        frequency response of op-amp.\n However, as input
        frequency is increased, the output amplitude
        reduces as the gain of the integration falls\n at
        a rate of 6 dB/octave.\n\n' );
20
21 // case(1): Sine wave input
22 printf(' case(1) : For sine Wave Input \n');
23 printf('\n\n For a input of 1 V peak sine wave at 5
        kHz, the integral of vi(t)=1*sin(2*pi*5000*t) is
        cosine function.\n');
24 t1 = 0:%pi:100*pi;
25 disp("Input Function - vi = sin(2*pi*5000*t);");
26 disp("Output Function - vo = 0.318*cos(2*pi*5000*t)
        ;");
27 printf(' The input and output waveforms are depicted
        in Graphic window # 0\n');
28
29 vi = sin(2*pi*5000*t1); // Input
30 vo = 0.318*cos(2*pi*5000*t1); // Output
31
32 a=gca(); // Handle on axes entity
33 a.x_location = "origin";
34 a.y_location = "origin";

```



```

35 plot(t1,vi,'ro-');
36 plot(t1,vo,'o-b');
37 legend(["Input Function","Output Function"]);
38 xlabel("time ");
39 ylabel("Vi,Vo");
40 title("Sine wave plot");
41
42 // case(2): Step input
43 printf('\n\n case(2) : Step input\n');
44 printf('\n\n If input is a step voltage vi = 1V for
      0<t<=0.3msec, then the output voltage at t = 0.3
      ms is ');
45 vos = (-1/(R1*Cf))*integrate('1','x',0,0.3*10^-3);
46 printf('%d V \n',vos);
47 printf('\n The output voltage is a ramp function
      with a slope of 10V/ms and is shown in graphic
      window #1\n');
48 yi = [1,1,1,1,1,1,1,1,1,1,1,1];
49 t2 = 0:0.1:1; // time in milli sec
50 yo = -10*t2;
51 figure(1);
52 a=gca(); // Handle on axes entity
53 a.x_location = "origin";
54 a.y_location = "origin";
55 plot(t2,yi,'ro-');
56 plot(t2,yo,'o-b');
57 legend(["Input Function","Output Function"]);
58 xlabel("Time in millisec");
59 ylabel("Vi,Vo");
60 title("Step plot");
61
62 // case(3): square wave input
63 printf('\n\n case(3): Square wave input \n');
64 printf('\n\n The output waveform for an input of 5
      kHz, 1 V peak square wave. \n It can be seen that
      input is of constant amplitude of 1 V from 0 to
      0.1 msec and -1 V from 0.1 ms to 0.2 ms.\n Thus,
      the expected output waveform will be a triangular

```

```

        wave. ');
65 vosq = -(1/(R1*Cf))*integrate('1','x',0,0.1*10^-3);
66 printf('\n The peak value of the output for first
        half cycle is %.1f V \n',vosq);
67 printf('\n Both input and output waveforms are
        depicted in graphic window #3\n');
68 t3 = 0:0.1*10^-3:10^-3;
69 zi = [1,-1,1,-1,1,-1,1,-1,1,-1,1];
70 zo =
        [0.5,-0.5,0.5,-0.5,0.5,-0.5,0.5,-0.5,0.5,-0.5,0.5];

71 figure(2);
72 a=gca(); // Handle on axes entity
73 a.x_location = "origin";
74 a.y_location = "origin";
75 plot2d2(t3,zi,2);
76 plot2d(t3,zo,4);
77 legend(["Input Function","Output Function"]);
78 xlabel("Time in sec");
79 ylabel("Vi,Vo");
80 title("Square wave plot");

```

---

Scilab code Exa 4.5 To find R1 and Rf values in the lossy integrator

```

1 // Exa 4.5
2
3 clc;
4 clear;
5
6 // Given data
7
8 App = 20; // peak gain in dB
9 A = 17; // Actual gain in dB
10 w = 10000; // Angular Frequency in rad/sec
11 C = 0.01*10^-6; // Farads

```

```

12
13 // Solution
14
15 printf('From Eq.(4.84) , we see that gain is at its
        peak when w = 0.\n Therefore , 20*log(Rf/R1) =
        20.\n');
16
17 // Therefore ,
18 // Rf = 10 R1; .....Eq. (1)
19 z = 10; // z is ratio of Rf/R1
20 printf(' i.e Rf/R1 = %d. \n',z );
21 printf(' At w = 10^4 rad/sec , gain in dB is down
        from its peak of 20 dB. \n Therefore , converging
        gain to dB in Eq.(4.84) and substituting for w
        ,C, and Rf/R1 we can get value of Rf.\n\n');
22 // 20*log10          10          = 17 dB
23 //          _____
24 //          sqrt(1 + [10^4*10^-8*Rf]^2)
25
26 deff('y=f(x)', 'y = 20*log10( 10 / sqrt(1+[10^-4*x
        ]^2))-17'); // x is Rf( )
27 [x,v,info] = fsolve(10,f);
28 printf(' The calculated value of Rf is %d .
        Rounding off to nearest possible value i.e 10
        k . \n',x);
29 Rf = 10000; //
30 printf(' Since we have ratio of Rf by R1 so , \n
        The value of R1 can be given as R1 = %d k .
        \n',0.1*(Rf/1000)); //as R1/Rf = 0.1

```

---

**Scilab code Exa 4.6** To calculate output of an operational amplifier to a step input

```

1 // Exa 4.6
2
3 clc;

```

```

4 clear;
5
6 // Given data
7
8 //Referring circuit in Fig. 4.26
9 // An op amp integrator and a low pass Rc circuit)
10
11 // Solution
12
13 printf(' Figure (4.26) is a simple op-amp integrator
      where Millers theorem is applied across the
      feedback capacitor Cf. \n The input time constant
      T = R1*Cf*(1-Av). \n Therefore , vi = V*(1-e^(-t/
      T)); ');
14 printf(' \n Therefore , vo = Av*Vi = Av* V*(1-e^(-t/
      R1*Cf*(1-Av))); ');
15 printf(' \n By expanding e^(-t/..) series by Taylors
      Expansion method we will reach to following
      approximation ');
16 printf(' \n vo      (-V*t/R1*Cf) * [1- t/(2*R1*Cf*(1-
      Av))];    if Av>>1 ...eq (1) ');
17 printf(' \n \n ');
18 printf(' Also , we know that for a low pass RC
      integrating circuit network(without op-amp) the
      output vo for a step input of V becomes \n ');
19 printf(' For a large Rc, vo      (V*t)/R*C) * (1 - t
      /(2*R*C) .. eq(2) '); //Eq(2)
20 printf(' \n \n ');
21 printf(' It can be seen that the output voltages of
      both circuits varies aproximately linearly with
      time(for large RC) and \n for either case ,
      derivative(vo) = V/RC. \n However, the second
      term in both the expression represent deviation
      from the linearity. \n we see that op-amp
      integrator is more linear than the simple RC
      circuit by a factor of 1/(1-Av).\n ');

```

---

Scilab code Exa 4.7 To show that output is given by a differential equation

```

1 // Exa 4.7
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Referring Circuit in Fig. 4.27
9
10 // Solution
11
12 printf(' The transfer gain of the circuit is - \n')
    ;
13 printf(' Vo(s) = -Zf = (R2+R3)+s*C*R2*R3 \n');
14 printf(' ----- \n');
15 printf(' Vi(s) = R1 = R1*(1+s*C*R3)\n');
16
17 printf('\n i.e R1(1+s*C*R3)*Vo(s) + [(R2+R3)+s*C*R2*R3
    ]*Vi(s) = 0.\n');
18 printf('\n\n Writing above equation in time domain
    ( s d /dt), we get,\n');
19 printf('\n R1 + C*R3*R1(d/dt Vo(t)) + [(R2+R3)+c*R2*
    R3]*(d/dt Vi(t)) = 0 ... eq(1)\n\n');
20
21 printf(' Since , vi(t) = V, \n Therefore , d/dt Vi(t)
    = 0.\n\n');
22 printf(' Therefore eq(1) becomes- \n C*(d/dt vo) +
    vo/R3 + V/R1 + (R2/R1*R3)*V = 0.\n');
23 printf(' \n Thus, output vo(t) is given by a
    differential equation as shown above. \n');

```

---

Scilab code Exa 4.8 To show that output is integral of input

```
1 // Exa 4.8
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Referring Fig. (4.28) -Non- inverting terminal
  integrator
9
10 // Solution
11
12 printf(' The voltage at the (+) input terminal of
  the op-amp due to potential divider is,\n');
13 printf(' V(+) = 1/ s*C * Vi(s)\n');
14 printf(' -----\n');
15 printf(' R+ 1/ s*C \n\n');
16 printf(' The output voltage Vo(s) fot the non-
  inverting amplifier is - \n');
17 printf(' Vo(s) = (1 + 1/(s*C*R))*V(+) = Vi(s) / (s*R
  *C).\n\n');
18 printf(' Hence in time domain, we get , vo = (1/(R*C)
  ) vi dt .\n');
19 printf(' Hence proved. \n');
```

---

Scilab code Exa 4.9 To set up an analog simulation to generate a sinusoidal signal

```
1 // Exa 4.9
2
3 clc;
```

```

4 clear;
5
6 // Given data
7
8 // To generate a sinusoidal signal 10 sin 3t.
9
10 // Solution
11
12 printf('Let us first obtain a differential equation
        whose solution is 10 sin 3t.\n');
13 printf(' Let x(t) = 10 sin 3t -----eq(1)\n');
14 printf(' The first derivative of this i.e. dx(t) =
        30 cos 3t -----eq(2)\n');
15 printf(' The second derivative of this i.e. d2x(t) =
        -90 sin 3t = -9*x(t) \n');
16 printf('\n Therefore , required differential equation
        is d2x(t)+9*x(t)=0. \n\n');
17
18 printf(' The initial condition is obtained by
        putting t=0 in eq(1&2), \n x(0)=0 and dx(0) = 30.
        \n' );
19 printf(' Assuming that d2x(t) is available , x(t) can
        be obtained by integrating x twice.\n The
        complete setup is shown in Fig. 4.31-Simulation
        of 10 sin 3t.\n');

```

---

# Chapter 5

## Comparators and Waveform Generators

Scilab code Exa 5.1 To plot the transfer curve for opamp with given conditions

```
1 // Exa 5.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A comparator as shown in Fig. 5.7(a)
9 Aol=50000; // open loop gain of op-amp
10 Vz=9; // Volts
11 Vd=0.7; // cutoff voltage
12
13 // Solution
14
15 // case 1
16 printf(' Since AOL =      , even a small positive or
        negative voltage at the input drives the output
        to +- Vsat. \n This causes Vz1 or Vz2 to break
        down, giving output voltage vo = +-(Vz+Vd)= ');
```



```

17 Vsat = Vz+Vd;
18 printf(' %.1f V. \n The same is shown in Graphic
    Window No. 0 \n', Vsat);
19 Vi= [-1:0.1:1];
20 for i=1:21
21     if(Vi(i)<0)
22         Vo(i)=-Vsat;
23     elseif(Vi(i)==0)
24         Vo(i)=Vsat;
25     else
26         Vo(i)=Vsat;
27
28     end
29 end
30 set(gca(),"grid",[1,1]);
31 a=gca(); // Handle on axes entity
32 a.x_location = "origin";
33 a.y_location = "origin";
34 plot2d2(Vi,Vo);
35 title('Transfer curve for ideal op-amp condition',
    color","blue","fontsize",3);
36
37
38 // case 2
39
40 DellVi = Vsat/Aol; // Zener breaks down after +
    Dell_Vi
41 scf(1);
42 Vi= [-1:0.1:1];
43 for i=1:21
44     if(Vi(i)<0)
45         Vo(i)=-Vsat;
46     elseif(Vi(i)==0)
47         Vo(i)=DellVi;
48     else
49         Vo(i)=Vsat;
50
51     end

```

```

52 end
53 set(gca(),"grid",[1,1]);
54 a=gca(); // Handle on axes entity
55 a.x_location = "origin";
56 a.y_location = "origin";
57 plot(Vi,Vo,'ro-');
58 title('Transfer curve for practical op-amp condition
        ','color","blue","fontsize",3);
59
60 printf('\n\n Now since, Vi = %.3f mV. The
        zeners break down after + %.3f mV \n
        as shown in the transfer curve depicted in Graphic Windows
        No. 1',DellVi*1000,DellVi*1000);

```

---

Scilab code Exa 5.2 To determine the upper and lower threshold voltages

```

1 // Exa 5.2
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Circuit of Schmitt trigger
9
10 R2=100; // Ohms
11 R1=50*10^3; // Ohms
12 Vref=0; //Volts
13 Vi=1; // peak to peak(Volts)
14 Vsat=14; // sSaturation voltage (Volts)
15
16 // Solution
17
18 printf('Using Equations (5.1) and (5.2), we get
        calculated values as follows -\n ');

```

```

19 Vut=(R2*Vsat)/(R1+R2);
20 printf(' Upper threshold voltage (VUT) = %d mV. \n '
        ,round(Vut*1000));
21 Vlt=(R2*-Vsat)/(R1+R2);
22 printf(' Lower threshold voltage (VLT) = %d mV. \n '
        ,round(Vlt*1000));

```

---

**Scilab code Exa 5.3** To calculate time period of the negative and positive portion

```

1 // Exa 5.3
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A Schmitt trigger as shown in fig. 5.9– circuit
   for example 5.3
9
10 VUT=0; // Upper threshold(V)
11 VH=0.2; // Hysteresis width(V)
12 F=1000; // Hz
13 Vpp=4; // peak to peak voltage(V)
14
15 // Solution
16
17 // Since VH=VUT-VLT
18 VLT=VUT-VH;
19
20 // From fig. 5.9, the angle can be calculated as
21 // VLT = (Vpp/2)* sin(%pi+ );
22 // Rearranging above equation
23 Theta = asin(VLT/-(Vpp/2)); // in radians
24 T= 1/F; // Time period(sec)
25

```

```

26 //  $\omega T = 2 * \pi * F * T = 0.1$ 
27 // Rearranging
28 Ttheta= Theta/(2*%pi*F);
29
30 T1=T/2 + Ttheta;
31 T2=T/2 - Ttheta;
32
33 printf('The duration of positive pulse(T1) = %.3 f
        msec and duration of negative pulse(T2) = %.3 f
        msec. \n ',T1*1000,T2*1000);

```

---

**Scilab code Exa 5.4** To design a phase shift oscillator to oscillate at 100 Hz

```

1 // Exa 5.4
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Phase shift oscillator as given in Fig. 5.15
9
10 F=100; // Oscillation frequency(Hz)
11
12
13 // Solution
14
15 printf(' Let C=0.1 microFarads , then from Eq. (5.25)
        we can get value of R. \n ');
16 R = 1/(sqrt(6)*2*%pi*10^-7*F);
17
18 printf(' The value of R as calculated = %.2 f k . \n
        ',R/1000);
19
20 printf(' To prevent overloading of the amplifier by

```

```
RC network , R1 <= 10*R. \n');
21 R1=10*R;
22 printf(' Therefore R1 = %d k . \n ',round(R1/1000)
);
23 // Since Rf = 29*R1;
24 Rf= 29*round(R1/1000); // k
25 printf(' Since Rf = 29*R1, therefore value of Rf =
%d k . \n ',Rf);
```

---

# Chapter 6

## Voltage Regulator

Scilab code Exa 6.1 To calculate the output current coming from 7805

```
1 // Exa 6.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 // IC 7805 is specified
9 Veb_on=1; // Volts
10 B=15; // Current gain
11 R1=100; // Load 1( )
12 R2=5; // Load 2( )
13 R3=1; // Load 3( )
14
15 // Solution
16
17 // Case(1)
18 printf(' Load = 100 \n\n');
19 printf('For IC 7805, the output voltage across the
    load will be 5 V.\n ');
20 V1=5; // Voltage across load
```

```

21 IL1=V1/R1;
22 VR1= 7 * IL1; // Voltage across R1
23 printf('The output current coming from 7805 = IL1 =
      Io = Ii = %d mA. \n ',IL1*1000);
24 printf('The voltage across R1 = %.2f V which is less
      than 0.7 V. Hence Q1 is off. \n ',VR1);
25 printf('So Ic1 = 0. ');
26 printf('\n\n');
27
28
29
30 // Case(2)
31 printf(' Load = 5 \n ');
32 printf('\n For IC 7805, the output voltage across
      the load will be 5 V.\n ');
33 V2=5; // Voltage across load
34 IL2=V2/R2;
35 VR2= 7 * IL2; // Voltage across R2
36 printf('The output current coming from 7805 = IL2 =
      Io = Ii = %d A. \n ',IL2);
37 printf('Assume that the entire current comes through
      regulator and that Q1 is OFF. Now the voltage
      drop across R1 is equal to %d V.\n Thus,our
      assumption is wrong and Q1 is ON.\n ',VR2);
38
39 // From equation 6.10-  $IL2 = 1A = (B+1)*Io - B*V_{eb\_on}/R2$ ;
40 // Therefore
41  $Io2 = (IL2 + (B*V_{eb\_on})/7) / (B+1)$ ;
42 // From equation 6.6-  $IL2 = 1A = Ic2 + Io2$ ;
43 // Therefore
44  $Ic2 = IL2 - Io2$ ;
45 printf('Using equations 6.6 and 6.10 we got values
      as Io2 = %d mA and Ic2 = %d mA. \n ',Io2*1000,Ic2
      *1000);
46 printf('\n\n');
47
48

```

```

49
50 // Case(3)
51 printf(' Load = 1 \n');
52 printf('\n For IC 7805, the output voltage across
the load will be 5 V.\n ');
53 V3=5; // Voltage across load
54 IL3=V2/R3;
55 VR3= 7 * IL3; // Voltage across R3
56 printf('The output current coming from 7805 = IL3 =
Io = Ii = %d A. \n ',IL3);
57 printf('Assume that the entire current comes through
regulator and that Q1 is OFF. Now the voltage
drop across R1 is equal to %d V.\n Thus,our
assumption is wrong and Q1 is ON.\n ',VR3);
58
59 // From equation 6.10-  $IL3 = 5A = (B+1)*Io - B*V_{eb\_on}/R3$ ;
60 // Therefore
61 Io3 = (IL3+(B*Veb_on)/7)/(B+1);
62 // From equation 6.6-  $IL3 = 5A = Ic3+Io3$ ;
63 // Therefore
64 Ic3= IL3-Io3;
65 printf('Using equations 6.6 and 6.10 we got values
as Io3 = %d mA and Ic3 = %.3f Amp. \n ',Io3*1000,
Ic3);

```

---

Scilab code Exa 6.2 To calculate component values to get desired output voltage

```

1 // Exa 6.2
2
3 clc;
4 clear;
5
6 // Given data
7

```



```

8  /// Referring Fig. 6.5– Adjustable regulator
9  Vo= 7.5; // Volts
10
11 // Solution
12
13 printf(' From the data sheet of 7805, IQ=4.2 mA.
        Say, we choose IR1 = 25 mA.\n ');
14 IQ = 0.0042; // Amperes
15 IR1 = 0.025; //Amperes
16 printf(' The voltage across load for 7805 is 5 Volts
        .\n ');
17 VR=5; // Volts
18 R1 = VR/IR1;
19 printf(' Thus, calculated value of R1 = %d . \n ',
        R1);
20
21 printf(' We have to choose R2 as to develop a
        voltage of 2.5 V across it. So, R2 comes out to
        be,\n ');
22 R2= 2.5/(IR1+IQ);
23 printf(' The value of R2 = %d . \n ',int(R2));

```

---

# Chapter 7

## Active Filters

Scilab code Exa 7.1 Design a second order Butterworth low pass filter

```
1 // Exa 7.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 n=2; // Second order Butterworth filter
9 fL=1000; // Higher cut off frequency(Hz)
10
11 // Solution
12
13 printf('Let C = 0.1 F . \n');
14 C=0.1*10^-6; // Farads
15
16 // Since fL = 1/(2 * %pi * R*C);
17 // Therefore;
18 R = 1/(2*%pi*fL*C);
19 printf('The calculated value of R = %.1f k . \n',
        R/1000);
20
```

```

21 printf(' From Table 7.1, for n=2, the damping factor
      alpha = 1.414. ');
22 alpha=1.414;
23 A0 = 3-alpha;
24 printf('\n Then the pass band gain A0 = %.3f. \n',A0
      );
25 printf('\n');
26 printf(' The transfer function of the normalized
      second order Butterworth filter is
      1.586      ');
27 printf('\n
      _____ ');
28 printf('\n
      Sn^2+1.414*Sn+1 ');
29
30 // Since Af= 1 + Rf/Ri = 1 + 0.586;
31 printf('\n Since A0= 1.586 so Let Rf = 5.86 k and
      Ri = 10 k to make A0 = 1.586. ');
32
33 printf(' \n The circiuit realized is as shown in
      Fig. 7.4 with component value as mentioned above.
      ');
34
35 printf('\n\n\n Frequency , f in Hz      Gain
      magnitude in dB 20 log(vo/vi)\n');
36 // Frequency Response
37 x=[0.1*fL,0.2*fL,0.5*fL,1*fL,5*fL,10*fL]
38 for i = 1:1:6
39     response(i) = 20*log10(A0/(sqrt(1+(fL/x(i))^4)
      ));
40     printf(' %d      %.2
      f      \n',x(i),response(i));
41 end

```

---

Scilab code Exa 7.2 Design a fourth order Butterworth low pass filter

```
1 // Exa 7.2
2
3 clc;
4 clear;
5
6 // Given data
7
8 n=4; // Fourth order Butterworth low-pass filter
9 fH=1000; // Hz
10
11 // Solution
12
13 printf('Let C = 0.1 F . \n');
14 C=0.1*10^-6; // Farads
15 // Since fH = 1/(2 * %pi * R*C);
16 // Therefore;
17 R = 1/(2*%pi*fH*C);
18 printf(' The calculated value of R = %.1f k . \n',R
        /1000);
19
20 printf(' From Table 7.1, for n=4, we get two damping
        factors namely,\n alpha1 = 0.765 and alpha2 =
        1.848. ');
21 alpha1=0.765;
22 alpha2=1.848;
23 A01 = 3-alpha1;
24 A02 = 3-alpha2;
25 printf('\n');
26 printf('\n Then the pass band gain A01 = %.3f and
        A02 = %.3f. \n',A01,A02);
27 printf('\n');
28 printf(' The transfer function of the normalized
```

```

        second order low-pass Butterworth filter is
        2.235                1.152                ');
29 printf('\n
        _____ * _____ ');
30 printf('\n
        Sn^2+0.765*Sn+1      Sn^2+1.848*Sn+1 ');
31
32 // Since A01= 1 + Rf/Ri = 1 + 1.235;
33 printf('\n Since A01= 2.235 so Let Rf1 = 12.35 k
        and Ri1 = 10 k to make A01 = 2.235.' );
34 printf('\n Since A02= 1.152 so Let Rf2 = 15.20 k
        and Ri1 = 100 k to make A01 = 1.152.' );
35
36 printf(' \n The circiuit realized is as shown in
        Fig. 7.7 with component value as mentioned above.
        ');

```

---

**Scilab code Exa 7.3** To determine order of a low pass Butterworth filter

```

1 // Exa 7.3
2
3 clc;
4 clear;
5
6 // Given data
7
8 Attn=40; // Attenuation in dB
9 x=2; // x= ratio of W to Wh
10
11 // Solution
12
13 printf(' Using equation 7.26,\n');
14

```

```

15 // 20*log(H(jw)/A0)=-40; // -ve since it is
    attenuation
16 // gives
17 // H(jw)/A0 = 10^-2 = 0.01
18 // so
19 // (0.01)^2 = 1/(1+2^(2*n));
20 // or 2^2n = 10^4 - 1;
21 // solving for n, we get
22
23 n=log(10^(4) -1)/(2*log(2));
24 printf(' The calculated value of n = %.2f. \n',n);
25 printf(' Since order of filter must be an integer
    so, n = %d. \n',round(n));

```

---

Scilab code Exa 7.4 Design a second order Butterworth high pass filter

```

1 // Exa 7.4
2
3 clc;
4 clear;
5
6 // Given data
7
8 n=2; // Second order Butterworth filter
9 fH=1000; // Lower cut off frequency(Hz)
10
11 // Solution
12
13 printf('Let C = 0.1 F . \n');
14 C=0.1*10^-6; // Farads
15
16 // Since fH = 1/(2 * %pi * R*C);
17 // Therefore;
18 R = 1/(2*%pi*fH*C);
19 printf(' The calculated value of R = %.1f k . \n',

```

```

        R/1000);
20
21 printf(' From Table 7.1, for n=2, the damping factor
        alpha = 1.414. ');
22 alpha=1.414;
23 A0 = 3-alpha;
24 printf('\n Then the pass band gain A0 = %.3f. \n',A0
        );
25 printf('\n');
26 printf(' The transfer function of the normalized
        second order low-pass Butterworth filter is
        1.586          ');
27 printf('\n
        _____');
28 printf('\n
        Sn ^2+1.414*Sn+1 ');
29
30 // Since Af= 1 + Rf/Ri = 1 + 0.586;
31 printf('\n Since A0= 1.586 so Let Rf = 5.86 k    and
        Ri = 10 k    to make A0 = 1.586. ');
32
33 printf(' \n The circiuit realized is as shown in
        Fig. 7.4 with component value as mentioned above.
        ');
34
35 printf('\n By considering minimum DC offset
        condition , the modified value of R and C comes
        out to be R = 1.85 k    and C=0.086 F . ');
36 printf('\n\n\n Frequency , f in Hz          Gain
        magnitude in dB 20 log(vo/vi)\n');
37 // Frequency Response
38 x=[0.1*fH,0.2*fH,0.5*fH,1*fH,5*fH,10*fH]
39 for i = 1:1:6
40     response(i) = 20*log10(A0/(sqrt(1+(x(i)/fH)^4)
        ));
41     printf(' %d                                %.2

```

```

                                f      \n',x(i),response(i));
42 end

```

---

### Scilab code Exa 7.5 Design a wide band pass filter

```

1 // Exa 7.5
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A wide-band pass filter
9 fL=400; // Lower cutoff frequency (Hz)
10 fH=2000; // Higher cutoff frequency (Hz)
11 A0=4; // passband gain
12
13 // Solution
14
15 printf('Since, the pass band gain is 4. so each of
        LPF and HPF section may be designed to give gain
        of 2,\n that is Ao=1+ (Rf/Ri) = 2.\n So, Rf and
        Ri should be equal. \n Let Rf=Ri=10 k for each
        of LPF and HPF sections. ');
16
17 disp("");
18 disp("");
19 disp("For HPF, fL=400 Hz.");
20 printf(' Assume C2=0.01 F . ');
21 C2=0.01*10^-6; // Farads
22 // Since fL= 1/(2*%pi*R2*C2);
23 // Therefore
24 R2= 1/(2*%pi*C2*fL);
25 printf(' \n The calculated value of R = %.1f k . ',
        int(R2)/1000);

```



```

26
27 disp("");
28 disp("");
29 disp("For LPF, fH=2000 Hz.");
30 printf(' Assume C1=0.01 F . ');
31 C1=0.01*10^-6; // Farads
32 // Since fH= 1/(2*pi*R1*C1);
33 // Therefore
34 R1= 1/(2*pi*C1*fH);
35 printf('\n The calculated value of R = %.2f k . ',
        R1/1000);
36
37 disp("");
38 disp("");
39
40 fo=sqrt(fL*fH);
41 Q=fo/(fH-fL);
42
43 printf(' The value of cutoff frequency = %.1f Hz.\n
        ',fo);
44 printf('\n The quality factor = %.2f (<10) since
        wide passband filter . ',Q);

```

---

#### Scilab code Exa 7.6 Design a 50 Hz active notch filter

```

1 // Exa 7.6
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A notch filter
9 fo=50; // cutoff frequency for notch filter (Hz)
10

```

```

11 //Solution
12
13 printf('As Given fo=50 Hz. Let C=0.1 F .');
14 C=0.1*10^-6; // Farads
15 // since fo=1/(2*pi*R*C);
16 // Therefore R =
17 R=1/(2*pi*fo*C);
18 printf(' \n For R/2, take two resistors of 31.8 k
        Ohms in parallel and for 2C,\n take two 0.1
        microFarads capacitors in parallel to make the
        twin-T notch filter\n as shown in Fig. 7.15(a) on
        page no. 279 where resistors R1 and R2 are for
        adjustment of gain.\n ')

```

---

#### Scilab code Exa 7.7 Design a wide band reject filter

```

1 // Exa 7.7
2
3 clc;
4 clear;
5
6 // Given data
7 fH= 400; // Higher cutoff frequency(Hz)
8 fL=2000; // lower cutoff frequency(Hz)
9 Ao=2; // Pass band gain
10
11 // Solution
12
13 disp(" For HPF, fL=2 kHz.");
14 disp(" Assume C2=0.1 F . ");
15 C2=0.1*10^-6; // Farads
16 // Since fL= 1/(2*pi*R*C2);
17 // Therefore
18 RL= 1/(2*pi*C2*fL);
19 printf(' The calculated value of R = %d .',int(RL))

```

```

    );
20 printf('\n Let R = 800 .');
21 // Since  $A_o=A_{o2} = 1+ (R_f/R_i)$ ;
22 disp("Let  $R_f = R_i =10$  k (say) to give  $A_{O2}$  of 2.");
23 disp("");
24 disp("");
25 disp("For LPF,  $f_L=400$  Hz.");
26 disp("Assume  $C_1=0.1$  F . ");
27  $C_1=0.1*10^{-6}$ ; // Farads
28 // Since  $f_H= 1/(2*\%pi*R*C_1)$ ;
29 // Therefore
30  $RF= 1/(2*\%pi*C_1*f_H)$ ;
31 printf(' The calculated value of R = %d .',int(RF)
    );
32 printf('\n Let R = 4 k .');..
33 // Since  $A_o=A_{o1} = 1+ (R_f/R_i)$ ;
34 disp("Let  $R_f = R_i =10$  k (say) to give  $A_{O1}$  of 2.");
35
36 disp("");
37 disp("");
38
39 disp("The schematic arrangement and the frequency
    response is shown in figs. 7.16(a,b) on page no.
    280.")

```

---

### Scilab code Exa 7.9 Design a switched capacitor integrator

```

1 // Exa 7.9
2
3 clc;
4 clear;
5
6 // Given data
7
8 fo=10; // Hz

```

```

9
10 // Solution
11
12 disp(" For a switched capacitor integrator , assume
      fCK=1000 Hz.");
13 fCK=1000; // Hz
14 disp(" From Eq. (7.129) on page no. 293, we get , ")
      ;
15 disp(" Cf/C1 =x= fCK/(2*%pi*fo). "); // x = ratio
      of Cf by C1
16 x=fCK/(2*%pi*fo);
17 disp(" Lets choose cF=15.9 pF.");
18 cF=15.9*10^-12; // Farads
19 C1=cF/x;
20 printf(' By calculation C1 = %d pF.\n ',round(C1
      *10^12));
21 disp(" For RC integrator , select R1=1.6*10^6 .") ;
22 R1=1.6*10^6; //
23 cF1=1/(2*%pi*R1*fo);
24 printf(' By calculation cF = %d nF. \n',round(cF1
      *10^9));
25 disp("");
26 printf(' The values of R1 = 1.6 mHz and cF = 10nF
      are not quite practical for a monolithic circuit
      .\n From this , it is obvious that switched
      capacitor circuits are more practical so far as
      IC fabrication is concerned.\n So it can be seen
      that an SC integrator requires very low values
      of capacitance compared to lossy integrator. ');
27 disp("");
28 printf(' If a resistor R2 is placed in parallel
      with the feedback capacitor cF of Fig. 7.26(a) , a
      lossy or practical integrator is obtained. \n
      The transfer function for this circuit is given
      in Eq. (7.130) and (7.131) on page no. 294. ');
29
30 printf('\n \n The switched capacitor implementation
      of Fig. 7.26(a) is shown in Fig. 7.26(b)\n

```

where resistors R1 and R2 have been replaced by  
switched capacitors C1 and C2 and its MOS version  
is in Fig. 7.26(c).');

---

# Chapter 8

## 555 Timer

Scilab code Exa 8.1 To calculate value of Capacitor

```
1 // Exa 8.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Monostable multivibrator
9 R=100*10^3; //
10 T=100*10^-3; // Time delay (sec)
11
12 // Solution
13 printf(' Using Eqn.(8.2) on page no.313, we get, ');
14 //T= 1.1*R*C;
15 C=T/(1.11*R);
16 printf(' C = %.1f F .\n From the graph of Fig.8.6
    on page no. 314, the value of C is found to be
    0.9 F also.\n',C*10^6);
```

---

Scilab code Exa 8.2 To calculate various parameters of Astable multivibrator

```
1 // Exa 8.2
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Astable multivibrator
9 Ra=6.8*10^3; //
10 Rb=3.3*10^3; //
11 C=0.1*10^-6; // F
12
13 // Solution
14
15 disp("By using Eq. (8.11) on page no. 320 we get ,
      tHigh as");
16
17 tHigh=0.69*(Ra+Rb)*C; // Time required to charge
      from 1/3 Vcc to 2/3 Vcc
18 printf(' tHIGH = %.1 f mSec. \n',tHigh*1000);
19 disp("By using Eq. (8.12) on page no. 320 we get ,
      tLow as");
20
21 tLow=0.69*(Rb)*C; // Time required to discharge
      from 2/3 Vcc to 1/3 Vcc
22 printf(' tLOW = %.2 f mSec. \n',tLow*1000);
23
24 disp("By using Eq. (8.13) on page no. 320 we get ,
      free running frequency as");
25 f= 1.45/((Ra+2*Rb)*C);
26 printf(' f = %.2 f kHz. \n\n',f/1000);
27
28 D= Rb/(Ra+2*Rb);
29 printf(' The duty cycle D = %.2 f (%d percent).\n ' ,
      D,round(D*100));
```

---

# Chapter 10

## D to A and A to D Converters

Scilab code Exa 10.1 To calculate output voltage for given 9 bit input

```
1 // Exa 10.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 //9-bit DAC
9 step = 10.3; // mV
10 y=[1 0 1 1 0 1 1 1 1];
11 n = 9; // since 9 bit DAC
12
13 // Solution
14
15 i = n;
16 add = 0;
17 while(i>0)
18     op = step*2^(i-1)*y((n+1)-i);
19     i = i-1;
20     add = add + op
21     end
```



```
22 printf('The output voltage for input 101101111 is %  
    .2f V. \n',add*10^-3);
```

---

**Scilab code Exa 10.2** To calculate LSB MSB and full scale output for an 8 bit DAC

```
1 // Exa 10.2  
2  
3 clc;  
4 clear;  
5  
6 // Given data  
7  
8 // 8 bit DAC  
9 n = 8;  
10 Vmin = 0; // Volts  
11 Vmax = 10; // Volts  
12  
13 // Solution  
14  
15 printf(' For a 8-bit DAC :-\n\n');  
16 LSB = 1/2^n;  
17 LSB10 = LSB*Vmax;  
18 printf('  LSB = %.3f V (i.e. 1/256).\n',LSB10);  
19 MSB10 = (1/2)*Vmax;  
20 printf('  MSB = %d V.\n',MSB10);  
21 fso = (Vmax-LSB10);  
22 printf('  Full scale output = %.3f V. \n',fso);
```

---

**Scilab code Exa 10.3** To calculate output voltage for different input

```
1 // Exa 10.3  
2  
3 clc;
```

```

4 clear;
5
6 // Given data
7
8 // D/A converter is used
9 Vmin = 0; // Voltage
10 Vmax = 10; // Voltage
11 ip1 = [1 0]; // for a 2-bit D/A converter(input 1)
12 ip2 = [0 1 1 0]; // for a 4-bit DAC(input 2)
13 ip3 = [1 0 1 1 1 1 0 0 ]; // for a 8-bit DAC(input
    3)
14
15 // Solution
16 V01 = Vmax*(ip1(1)*2^(-1)+ip1(2)*2^(-2)); // output
    1
17 printf(' The output voltage for input1 = [10] is %d
    V. \n ',V01);
18 V02 = Vmax*(ip2(1)*2^(-1)+ip2(2)*2^(-2)+ip2(3)
    *2^(-3)+ip2(4)*2^(-4)); // Output 2
19 printf(' The output voltage for input2 = [0110] is %
    .2f V. \n ',V02);
20 V03 = Vmax*(ip3(1)*2^(-1)+ip3(2)*2^(-2)+ip3(3)
    *2^(-3)+ip3(4)*2^(-4)+ip3(5)*2^(-5)+ip3(6)*2^(-6)
    +ip3(7)*2^(-7)+ip3(8)*2^(-8)); // Output 3
21 printf(' The output voltage for input3 = [10111100]
    is %.2f V. \n ',V03);

```

---

Scilab code Exa 10.4 To calculate value of the resistor R of the integrator

```

1 // Exa 10.4
2
3 clc;
4 clear;
5
6 // Given data

```

```

7
8 // A 16 bit dual slope ADC is specified
9 n = 16; // 16 bit counter
10 CR = 4*10^6; // clock rate in Hz
11 Vimax = 10; // Maximum input voltage
12 Vomax= -8; // Maximum integrator output voltage
13 C = 0.1*10^-6; // Capacitor(Farads)
14
15 // Solution
16
17 //Referring Eqn 10.4, 10.5, 10.6, 10.7 given on page
    no 364 and 365;
18
19 T1 = 2^n/CR; // Time Period
20 // For the integrator
21 // dell Vo= (-1/RC)*Vmax*T1;
22 // Therefore
23 R = -(Vimax*T1)/(Vomax*C); // Resistor value
24 printf('The value of resistor R of the integrator is
    %d k . \n ',round(R/1000));

```

---

**Scilab code Exa 10.5** To find the equivalent digital number

```

1 // Exa 10.5
2
3 clc;
4 clear;
5
6 // Given data
7
8 // A 16bit dual slope ADC is specified
9 Va = 4.129; // Input analog Voltage
10 Vr= 8; // Maximum integrator output voltage(
    Reference Voltage)
11 n=16; // 16 bit counter

```

```

12
13 // Solution
14
15 disp("Referring to Eqn 10.7 on page no. 365 we get,"
      )
16 // Va = Vr*(N/2^n);
17 N = round(Va * 2^n / Vr); // Digital count
18 printf(' The digital count N = %d for which the
      binary equivalent = \n',N);
19
20 // code to convert decimal to binary weuivalent
21 Nbin = [000000000000000000];
22 while (N > 0 & n > 0)
23     if (modulo(N,2)== 0)
24         Nbin(n)=0;
25     else
26         Nbin(n)=1;
27 end
28 n=n-1;
29 N=int(N/2);
30 end
31 disp((Nbin)');

```

---