

Scilab Textbook Companion for
Problems in Electrical Engineering
by P. Smith ¹

Created by
Mohd Asif
B. Tech
Electronics Engineering
Uktu
College Teacher
None
Cross-Checked by
None

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Problems in Electrical Engineering

Author: P. Smith

Publisher: CBS Publisher

Edition: 9

Year: 2003

ISBN: 9788123908588

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Appendix Solved problems	5

List of Scilab Codes

Exa 1.2	Voltage Gradients	5
Exa 1.3	Current required	6
Exa 1.4	Exciting current	7
Exa 1.5	Voltage across 100 ohm	8
Exa 1.6	frequency for attenuation	9
Exa 1.7	Voltage across capacitor	10
Exa 1.8	Circuit current	11
Exa 1.9	Value of L	11
Exa 1.10	Star and Delta Connection	12
Exa 1.11	Line current and power	13
Exa 1.12	Wattmeter reading	14
Exa 1.13	Current and power	15
Exa 1.14	transient component of current	16
Exa 1.15	Additional resistance required	17
Exa 1.16	Reading of electrostatic voltmeter	18
Exa 1.17	Deflection	19
Exa 1.18	Power dissipated	20
Exa 1.19	potential difference	21
Exa 1.20	Plate resistance	21
Exa 1.21	equation of FM wave	22
Exa 1.22	carrier power and efficiency	23
Exa 1.23	Series and Parallel equivalent circuit	24
Exa 1.24	Characteristic wave impedance	24
Exa 1.25	capacitance ratio	26
Exa 1.26	Resistor values	27
Exa 1.27	conversion efficiency	27
Exa 1.28	Cyrrent and Voltage gain	28
Exa 1.29	Current gain BW product	30

Exa 1.30	Vgs and gm	31
Exa 1.31	Bandwidth of redesigned amplifier	31
Exa 1.32	Critical inductance	32
Exa 1.33	Current in each armature	32
Exa 1.34	Efficiency and regulation	33
Exa 1.35	load factor	34
Exa 1.36	shunt field turns	35
Exa 1.37	New speed	36
Exa 1.38	Speed of the machine	37
Exa 1.39	Generator efficiency	38
Exa 1.40	Voltage drop	39
Exa 1.41	All day efficiency	41
Exa 1.42	Current drawn by the transformer	42
Exa 1.43	Percentage reduction in stator voltage	43
Exa 1.44	Torque ratio	44
Exa 1.45	cross section of windings	44
Exa 1.46	Starting torque	45
Exa 1.47	Resistance of all section	46
Exa 1.48	temperature rise	47
Exa 1.49	Regulation at full load voltage	48
Exa 1.50	Power output	49
Exa 1.51	power output	50
Exa 1.52	filament diameter	50
Exa 1.53	filament diameter	51
Exa 1.54	Torque ratio	51
Exa 1.55	cross section of primary winding	52
Exa 1.56	auto transformation ratio	53
Exa 1.57	temperature rise	54
Exa 1.58	Torque ratio	54
Exa 1.59	Regulation	55
Exa 1.60	diameter of filament	56
Exa 1.61	Potential difference	56
Exa 1.62	Power dissipated	57
Exa 1.63	Deflection	58
Exa 1.64	Reading on voltmeter	59
Exa 1.65	Additional resistance	60
Exa 1.66	current after t sec	61
Exa 1.67	Power factor	61

Exa 1.68	Wattmeter reading	62
Exa 1.69	Line and Phase Current	63
Exa 1.70	Wattmeter readings	64
Exa 1.71	expression of current	65
Exa 1.72	Resistance required	66
Exa 1.73	Reading of electrostatic voltmeter	67
Exa 1.74	Power and Power factor	68
Exa 1.75	carrier power under modulated condition . .	69
Exa 1.76	Resistance and reactance	69

Chapter 1

Appendix Solved problems

Scilab code Exa 1.2 Voltage Gradients

```
1 // Ex 2 Page 340
2
3 clc;clear;close;
4 // Given
5 t1=2; // mm
6 t2=5; // mm
7 t3=7; // mm
8 eps1=3; // dielectric constant
9 eps2=4; // dielectric constant
10 eps3=6; // dielectric constant
11 eps0=1/36/%pi*10^-9; // dielectric constant
12 d=10/100 ;// m
13 V=1500 // V
14 //E1*t1+E2*t2+E3*t3=V
15 //Voltage Gradients :
16 // using eps1*E1=eps2*E2=eps3*E3
17 E1=V/(t1+(eps1/eps2)*t2+(eps1/eps3)*t3) // V/mm
18 E1=E1*10 // V/cm
19 E2=eps1*E1/eps2 // V/cm
20 E3=eps1*E1/eps3 // V/cm
21 printf("Voltage Gradients :\n      for A : %.f V/cm\n")
```

```

        for B : %.f V/cm\n      for C : %.f V/cm",E1,E2,E3
    )
22
23 A = %pi*d^2
24 W1=1/2*eps0*eps1*E1^2*10^4*A*t1*10^-3; // J
25 W2=1/2*eps0*eps2*E2^2*10^4*A*t2*10^-3; // J
26 W3=1/2*eps0*eps3*E3^2*10^4*A*t3*10^-3; // J
27 W1=W1*10^6 ; // uJ
28 W2=W2*10^6 ; // uJ
29 W3=W3*10^6 ; // uJ
30 printf("\nEnergy stored :\n      for A : %.1f uJ\n
      for B : %.1f uJ\n      for C : %.1f uJ",W1,W2,W3)
31
32
33 // Answer in the textbook are not accurate

```

Scilab code Exa 1.3 Current required

```

1 // Ex 3 Page 341
2
3 clc;clear;close;
4 // Given
5 N=680; // turns
6 fi=1.6*10^3 ; // Wb
7 d1=4/100 ; // m
8 d2=24/100; //m
9 l=0.6; //m
10 mu0=4*pi/10^7 ; // constant
11
12
13 // For air gap :
14 A=d1^2 ; // m^2
15 Bg=fi/A ; // weber/m^2
16 Hg=Bg/mu0; //AT/m
17 mmf1=0.001/mu0 ; // AT

```

```

18
19 // For central limb :
20 A=d1^2; // m^2
21 Bc=fi/A ; //weber/m^2
22 Hc=900; //AT/m (from magnetization curve)
23 mmf2=Hc*d2 ; // AT
24
25
26 // For side limb :
27 fi=1/2*fi ; // Wb
28 A=d1^2; // m^2
29 Bc=fi/A ; //weber/m^2
30 Hc=520; //AT/m (from magnetization curve)
31 mmf3=Hc*l ; // AT
32
33 mmf_total = mmf1+mmf2+mmf3; // AT
34 i=mmf_total/N ; // A
35 printf("Current required = %0.2f A",i)
36
37
38 // Answer in the textbook are not accurate

```

Scilab code Exa 1.4 Exciting current

```

1 // Ex 4 Page 343
2
3 clc;clear;close;
4 // Given
5
6 D=15/100 ; // m
7 A=10/10**-4; //m^2
8 N=200; // turns
9 fi=1.6*10^3 ; // Wb
10 B=1 ; //weber/m^2
11 mu0=4*pi/10^7 ; // constant

```

```

12 mur=500 ;// constant
13 lg=2/1000; //m
14
15
16 // without air gap
17 l=%pi*D;//m
18 R=l/mu0/mur/A; //A/Wb
19 fi=B*A; //Wb
20 mmf=fi*R; //AT
21 I=mmf/N;//A
22 L=N**2/R/10**6; //mH
23 E=1/2*L*I^2/100; //J
24
25
26 // with air gap
27 Rg=lg/mu0/A; //A/Wb
28 Rt=R+Rg; //A/Wb
29 fi=B*A; //Wb
30 mmf=fi*Rt; //AT
31 I2=mmf/N;//A
32 L2=N**2/Rt/10**6; //mH
33 E2=1/2*L2*I2^2/100; //J
34
35 printf("\t\tWithout air gap") With air gap")
36 printf("\nExciting current %.2f A" ,I,I2) %.2f A
37 printf("\nInductance %.1f mH" ,L,L2) %.1f mH
38 printf("\nStored Energy %.3f J" ,E,E2) %.3f J
39
40
41 // Answer in the textbook are not accurate

```

Scilab code Exa 1.5 Voltage across 100 ohm

```

1 // Ex 5 Page 344
2
3 clc;clear;close;
4 // Given
5
6 VA=60; //V
7 I=0.6; //A
8 // (VB-VA)/20+(VB-VC)/20+VB/20-I=0
9 //3*VB-VC=72 for node B eqn(1)
10 // (VC-VA)/50+(VC-VB)/30+(VC-12)/50+VC/100=0
11 // -5*VB+10*VC=144 eqn (2)
12 A=[3 -1;-5 10];
13 B=[72;144];
14 X=A**-1*B;
15 VB=X(1); //V
16 VC=X(2); //V
17 printf("Voltage across 100 ohm = %.1f V",VC)
18 VC=24; //V
19 VB=(72+VC)/3 ; // from eqn(1)
20 // Node C
21 // (VC-VA)/50+(VC-VB)/20+(VC-12)/50+VC/100+VC/R=0
22 // eqn (3)
23 R=100*VC/(144+5*VB-10*VC); //ohm
24 printf("\nR=% .1f ohm",R)

```

Scilab code Exa 1.6 frequency for attenuation

```

1 // Ex 6 Page 346
2
3 clc;clear;close;
4 // Given
5
6 Ro=600; //ohm
7 fc=2*1000; //Hz
8 alfa=10; //dB

```

```

9
10
11 L=Ro/%pi/fc*1000; //mH
12 C=1/(%pi*Ro*fc)*10**6; //uF
13 alfa=alfa/8.686; //nepers
14 f=fc*cosh(alfa/2)/1000; //kHz
15 printf("\nat f = %.2f kHz, the above filter will
         have required attenuation.",f)

```

Scilab code Exa 1.7 Voltage across capacitor

```

1 // Ex 7 Page 347
2
3 clc;clear;close;
4 // Given
5 //v=100*sin (314*t )
6 R=25; //ohm
7 C=80; //uF
8 omega=314; //radian
9 Vm=100; //V
10
11 Xc=1/omega/(C*10**-6); //ohm
12 Z=sqrt(R**2+Xc**2); //ohm
13 Im=Vm/Z; //A
14 theta=atan(Xc/R); //radian
15 printf("equation for instant current:")
16 mprintf("\n i=%f sin (%f*t+%f) ",Im,omega,theta)
17 P=(Im/sqrt(2))*2*R; //W
18 mprintf("\n Power consumed = %f W",P)
19 Vcm=Im*Xc; //V
20 //(when i=Im/2)
21 i=0.5*Im; //A
22 //vc=Vcm*sin (314*t+theta-%pi/2)
23 //i=Im*sin (314*t+theta)
24 tt=asin(i/Im); //radian tt=314*t+theta

```

```
25 vcm=Vcm*sin(tt-%pi/2)
26 mprintf ("\n Voltage across capacitor = %.1f V(+ve &
-ve)", abs(vcm))
```

Scilab code Exa 1.8 Circuit current

```
1 // Ex 8 Page 348
2
3 clc;clear;close;
4 // Given
5
6 Z1=(6.25+%i*1.25); //ohm
7 Z2=(5+%i*0); //ohm
8 //Z3=(5-%i*XC); // ohm
9 V=100; //V
10 f=50; //Hz
11 //Z23=(250+5*Xc**2)/(100+Xc**2)-%i*(25*Xc)/(100+Xc
    **2)
12 //for in phase condition imag part must be zero
13 //5*Xc**2-100*Xc+5*100=0
14 A=[5 -100 500]; // polynomial
15 XC=roots(A);
16 XC=XC(1); //ohm
17 C=1/(2*pi*f*XC)*10**6; //uF
18 printf ("Capacitance of XC = %.f uF", C)
19 Z=XC; //ohm
20 I=V/Z; //A
21 P=I**2*Z/1000; //kW
22 printf ("\n Circuit current = %.f A and power = %.f
    kW", I, P)
```

Scilab code Exa 1.9 Value of L

```

1 // Ex 9 Page 349
2
3 clc;clear;close;
4 // Given
5
6 omega_o=600; // rad/s
7 omega=400; // rad/s
8 R=3; // ohm
9 IBYIo=1/2; // ratio
10
11
12 fo=omega_o/2/%pi; //Hz
13 f=omega/2/%pi; //Hz
14 // I/Io=1/(sqrt(1+Q**2*(f/fo-fo/f)**2))
15 Q=sqrt(1/IBYIo**2-1)/(fo/f-f/fo)
16 //Q=1/omega_0/R/C
17 C=1/omega_o/R/Q*10**6; //uF
18 //Q=omega_0*L/R
19 L=Q*R/omega_o*1000; //mH
20 printf("L = %.1f mH\n C=% .f uF",L,C)

```

Scilab code Exa 1.10 Star and Delta Connection

```

1 // Ex 10 Page 350
2
3 clc;clear;close;
4 // Given
5
6 V=400; //V
7 f=50; //Hz
8 n=3; //no of phase
9 R=100; //ohm
10
11 //Star connection
12 Vph=V/sqrt(n); //V

```

```

13 Iph=Vph/R; //A
14 IL=Iph; //A
15 cos_fi=1; // for only resistor load
16 P=sqrt(3)*V*IL*cos_fi/1000; //kW
17 printf("Star Connection : P=%f kW",P)
18 //Delta Connection
19
20 Vph=V; //V
21 Iph=Vph/R; //A
22 IL=sqrt(3)*Iph; //A
23 VL=Vph; //V
24 P=sqrt(3)*VL*IL*cos_fi/1000; //kW
25 printf("\n Delta Connection : P=%f kW",P)

```

Scilab code Exa 1.11 Line current and power

```

1 // Ex 11 Page 351
2
3 clc; clear; close;
4 // Given
5 Rab=6; Rbc=8; Rca=4; //ohm
6 Vab=100*expm(%i*0); //V
7 Vbc=100*expm(%i*-120*pi/180); //V
8 Vca=100*expm(%i*120*pi/180); //V
9 Zab=6+%i*8; //ohm
10 Zbc=8+%i*6; //ohm
11 Zca=4-%i*3; //ohm
12
13 //Phase current
14 Iab=Vab/Zab; //A
15 Ibc=Vbc/Zbc; //A
16 Ica=Vca/Zca; //A
17 printf("Phase Current:")
18 [r,t]=polar(Iab)
19 printf("\n Iab=%f angle=%f degree ",r,t*180/pi)

```

```

20 [r,t]=polar(Ibc)
21 printf("\n Ibc=%f angle=%f degree ",r,t*180/pi)
22 [r,t]=polar(Ica)
23 printf("\n Ica=%f angle=%f degree ",r,t*180/pi)
24 //Line current
25 Iaa=Iab-Ica;//A
26 Ibb=Ibc-Iab;//A
27 Icc=Ica-Ibc;//A
28 printf("\n\n Line Current:")
29 [r,t]=polar(Iaa)
30 printf("\n Iaa=%f angle=%f degree ",r,t*180/pi)
31 [r,t]=polar(Ibb)
32 printf("\n Ibb=%f angle=%f degree ",r,t*180/pi)
33 [r,t]=polar(Icc)
34 printf("\n Icc=%f angle=%f degree ",r,t*180/pi)
35 //Power Consumed
36 Wab=abs(Iab)^2*Rab;//W
37 Wbc=abs(Ibc)^2*Rbc;//W
38 Wca=abs(Ica)^2*Rca;//W
39 W=Wab+Wbc+Wca;//W
40 W=W/1000;//kW
41 printf("\n\n Total Power , W=%f kW",W)
42 //Answer wrong for line current in the textbook.

```

Scilab code Exa 1.12 Wattmeter reading

```

1 // Ex 12 Page 353
2
3 clc;clear;close;
4 // Given
5 VRY=200*expm(%i*0); //V
6 VYB=200*expm(%i*-120*pi/180); //V
7 VBR=200*expm(%i*120*pi/180); //V
8
9

```

```

10 ZA=10*expm(%i*60*%pi/180); //ohm
11 ZB=10*expm(%i*0*%pi/180); //ohm
12 ZC=10*expm(%i*60*%pi/180); //ohm
13
14 //Phase current
15 IRY=VRY/ZA; //A
16 IYB=VYB/ZB; //A
17 IBR=VBR/ZC; //A
18
19 IR=IRY-IBR; //A
20 PVA=conj(VRY)*IR; //W
21 printf("Wattmeter W1 reading=%f W", real(PVA))
22 IB=IBR-IYB; //A
23 PVB=conj(-VYB)*IB; //W
24 printf("\n Wattmeter W2 reading=%f W or %f kW",
real(PVB), real(PVB)/1000)

```

Scilab code Exa 1.13 Current and power

```

1 // Ex 13 Page 354
2
3 clc; clear; close;
4 // Given
5 //v=250*sin(omega*t)+50*sin(3*omega*t+%pi/3)+20*sin
  (5*omega*t+5*pi/6)
6 V1=250; V3=50; V5=20; //V
7 fi1=0; fi3=60; fi5=150; //degree
8 R=20; //ohm
9 L=0.05; //H
10 omega=314; //rad/s
11
12 X1=omega*L; //ohm
13 Z1=R+%i*X1; //ohm
14 X3=3*omega*L; //ohm
15 Z3=R+%i*X3; //ohm

```

```

16 X5=5*omega*L; //ohm
17 Z5=R+%i*X5; //ohm
18 [r1,t1]=polar(Z1);
19 [r3,t3]=polar(Z3);
20 [r5,t5]=polar(Z5);
21 printf("expression for current:")
22 printf("\n i = %.2f*sin(omega*t-%.1f)+%.1f*sin(3*
    omega*t%.1f)+%.2f*sin(5*omega*t-%.1f)" ,V1/r1,fi1-
    t1*180/%pi,V3/r3,fi3-t3*180/%pi,V5/r5,fi5-t5*180/
    %pi)
23
24 I1m=V1/r1; //A
25 I3m=V3/r3; //A
26 I5m=V5/r5; //A
27 Irms=sqrt(I1m^2/2+I3m^2/2+I5m^2/2); //A
28 Vrms=sqrt(V1^2/2+V3^2/2+V5^2/2); //A
29 printf("\n Irms=%.f A\n Vrms=%.f V" ,Irms,Vrms)
30 P=Irms^2*R; //W
31 printf("\n Total Power , P=%.f W" ,P)
32 cosfi=P/Vrms/Irms; //Power factor
33 printf("\n Power factor = %.2f" ,cosfi)

```

Scilab code Exa 1.14 transient component of current

```

1 // Ex 14 Page 355
2
3 clc;clear;close;
4 // Given
5 f=50; //Hz
6 Vm=400; //V
7 R=10; //ohm
8 L=0.1; //H
9 t=0.02; //sec
10 XL=2*pi*f*L; //ohm
11 Z=R+%i*XL; //ohm

```

```

12 Im=Vm/abs(Z); //A
13 fi=atan(XL/R); // degree
14 lambda=L/R; //sec
15 printf(" expression for current :")
16 printf("\n i = %.1f*sin(314*t-%.3f)+0.95*e**(-100*t)
      ",Im,fi)
17 i = Im*sin(314*t-fi)+0.95*e**(-100*t); //A
18 printf("\n current after 0.02 sec is : %0.1f A",i)
19 i2=Im*(0.95*e**(-100*t)); //A
20 printf("\n transient component is : %0.2f A",i2)

```

Scilab code Exa 1.15 Additional resistance required

```

1 // Ex 15 Page 356
2
3 clc;clear;close;
4 // Given
5 C=5*10**-6; //F
6 L=2; //H
7 R=200; //ohm
8
9 if R<2*sqrt(L/C) then
10   printf(" Since R<2sqrt(L/C) , the circuit is
           originally oscillatory .")
11 end
12
13 a=R/2/L
14 omega = sqrt(1/L/C-R^2/4/L^2); //rad/s
15 // i=Im*e**(-a*t)*sin(omega*t+fi)
16 // at t=0 sec
17 i0=0; //A
18 vc=10; //V
19 fi=asin(i0); //degree
20 //L*di/dt=vc at t=0
21 Im=poly([0], 'Im')

```

```

22 function i=current(t)
23     i=Im*expm(-a*t)*sin(omega*t+fi)
24 endfunction
25 // i=Im*expm(-a*t)*sin(omega*t+fi)
26 LdiBYdt=L*numderivative(current,0)
27 temp = coeff(LdiBYdt)
28 Im=vc/temp(2)
29 printf("\n Expression for current :\n i = %.3f*exp
    (-%dt)*sin(%1 ft)",Im,a,omega)
30 Rn=2*sqrt(L/C); //ohm
31 Rad=Rn-R; //ohm
32 printf("\n\n Additional resistance required = %d ohm
    ",Rad)

```

Scilab code Exa 1.16 Reading of electrostatic voltmeter

```

1 // Ex 16 Page 357
2
3 clc;clear;close;
4 // Given
5 //i=0.5+0.3*sin(omega*t)-0.2*sin(2*omega*t)
6 I0=0.5; I1m=0.3; I2m=-0.2; //from above expression
7 Iav=I0; //A
8 R=1000; //ohm
9 L=1/1000; //H
10
11 Irms=sqrt(I0**2+(I1m/sqrt(2)**2+(I2m/sqrt(2)**2)));
    //A
12 printf("Reading of hot wire instrument = %.3f A",
    Irms)
13 VR=Irms*R; //V
14 printf("\n Reading of electrostatic voltmeter across
    1000 ohm = %d V",VR)
15 //vl_dash=L*di/dt=300*cos(w*t)-400*cos(2*w*t)
16 v11=300;v12=4;//V

```

```
17 v1=sqrt((300/sqrt(2))**2+(400/sqrt(2))**2)
18 printf("\n Reading of electrostatic voltmeter across
1 mH inductor = %d V",v1)
```

Scilab code Exa 1.17 Deflection

```
1 // Ex 17 Page 358
2
3 clc;clear;close;
4 // Given
5 R=80; //ohm
6 V=2; //V
7 l=50; //cm
8 vd=.1; //V
9 emf=1.43; //V
10 Rc=850; //ohm
11 sg=17.5; //mm/uA
12 df=1; //mm
13
14
15 I=R/V; //A
16 Rw=vd/I; //ohm (Resistance of side wire)
17 Id=df/sg*10**-6; //A (current for 1mm deflection)
18 el=1/sg*Rc; //uV
19 printf("The limit of error = %.1f uV",el)
20 Rw1=0.2/l*Rw; //ohm (for 2cm slide wire)
21 dV=I*Rw1*1000; //mV (Change in voltage from null
point)
22 r1=emf/I; //ohm (tapped portion)
23 r2=r1*22.8/R; //ohm
24 Ig=dV/1000/(Rc+r2); //A
25 d=dV/1000/(Rc+r2)/Id; //mm
26 printf("\n Deflection = %.1f mm",d)
```

Scilab code Exa 1.18 Power dissipated

```
1 // Ex 18 Page 359
2
3 clc; clear; close;
4 // Given
5 R=50; //ohm
6 Vrms=100; //V
7 Rd1=50; //ohm
8 Rd2=100; //ohm
9
10Vm=Vrms/sqrt(2); //V
11//v=Vm*sin(theta)
12Rf=R+Rd1; //ohm
13Rb=R+Rd2; //ohm
14// i_f=v/Rf;//A
15// i_b=v/Rb;//A
16Irms=1/2/%pi*(integrate('sqrt(2)*sin(theta))**2',,
theta',0,%pi)+integrate('sqrt(2)/3*sin(theta))**2',theta',%pi,2*%pi))
17Iav=1/2/%pi*(integrate('sqrt(2)*sin(theta)',theta',
0,%pi)+integrate('sqrt(2)/3*sin(theta)',theta',
%pi,2*%pi))
18printf("reading of hot wire ammeter = %.2f A",Irms)
19printf("\n reading of moving coil ammeter = %.2f A",
Iav)
20P=1/2*(Vrms**2/Rf+Vrms**2/Rb); //W
21printf("\n\n Power taken from the mains = %.1f W",P)
22Pc=Irms**2*R; //W
23Pd=P-Pc; //W
24printf("\n Power dissipated in rectifying device =
%d W",Pd)
25//Answer wrong in the textbook.
```

Scilab code Exa 1.19 potential difference

```
1 // Ex 19 Page 361
2
3 clc;clear;close;
4 // Given
5 d=1/100; //m
6 S=-1/100; //m
7 Ve=2; //kV
8 theta=30; //degree
9 e=1.6*10**-19; //C
10 m=9.67*10**-31; //kg
11
12 u=sqrt(2*e*Ve*1000/m); //m/s
13 uy=u*sind(theta); //m/s
14 vy=0; //since final velocity =0
15 //vy**2-uy**2=2*ay*S
16 ay=(vy**2-uy**2)/2/S; //m**2/s
17 //ay=e/m*V/d
18 V=ay*m*d/e; //V
19 printf(" Required potential difference = %.f V" ,V)
```

Scilab code Exa 1.20 Plate resistance

```
1 // Ex 20 Page 361
2
3 clc;clear;close;
4 // Given
5 //Ia=0.0004*(Va+40*Vg)**(3/2); // mA --eqn (1)
6 Va=250; //V
7 Vg=-3; //V
8 //mu=delVa/delVg
```

```

9 // differentiation wrt Vg eqn(1)
10 // (4*10**-6*3/2*(Va+40*Vg))**(1/2)*(mu+40)=0
11 mu=-40; //constant
12 printf("Amplification factor , mu = %.f",mu)
13 //differentiation wrt Va eqn(1)
14 // delIa/delVa=(4*10**-6*3/2*(Va+40*Vg))**(1/2)
15 // *(0+40)
15 gm=(4*10**-6*3/2)*(Va+40*Vg)**(1/2)*(0+40)*1000; //
16 mA/V or S
16 printf("\n Mutual conductance , gm = %.2f S",gm)
17 //differentiation wrt Ia eqn(1) keeping Vg constant
18 //1=(4*10**-6)*3/2*(Va+40*Vg)**(1/2)*(delVa/delIa+0)
19 //ra=delVa/delIa
20 ra=1/((4*10**-6)*3/2*(Va+40*Vg)**(1/2))
21 printf("\n Plate resistance , ra = %.1f kohm",ra
15 /1000)

```

Scilab code Exa 1.21 equation of FM wave

```

1 // Ex 21 Page 363
2
3 clc;clear;close;
4 // Given
5 fc=25*10**6; //Hz
6 fm=400; //Hz
7Vm=4; //V
8 del=10*10**3; //Hz
9 wc=2*pi*fc; //rad/s
10wm=2*pi*fm; //rad/s
11 m=del/fm; //modulation index
12 mf=m; mp=m; //modulation index
13 printf("General equation of FM wave is:")
14 printf("\n v=%d*sin (%.2e*t+%d*sin (%d*t)",Vm,wc,mf,wm
15 )
15 printf("\n\n General equation of PM wave is:")

```

```

16 printf("\n v=%d*sin(%f*t+%d*sin(%d*t)",Vm,wc,mp,wm
)
17 // Changing modulating frequency
18 fm_new=2*10**3; //Hz
19 a=fm_new/fm; //increase in angular frequency
20 printf("\n\n Now equation of FM wave is:")
21 printf("\n v=%d*sin(%f*t+%d*sin(%d*t)",Vm,wc,mf,a*
wm)
22 printf("\n\n Now equation of PM wave is:")
23 printf("\n v=%d*sin(%f*t+%d*sin(%d*t)",Vm,wc,mp,a*
wm)

```

Scilab code Exa 1.22 carrier power and efficiency

```

1 // Ex 22 Page 363
2
3 clc;clear;close;
4 // Given
5 Ebb=300; //V
6 Ibb=20; //A
7 Emm=150; //V
8 Po=4.5*10**3; //W
9
10 m=Emm/Ebb; //modulation index
11 Pbb=Ebb*Ibb
12 eta=Po/Pbb*100; //%
13 P=Po*(1+m**2/2); //W
14 Pdo=Pbb-Po; //W
15 Pd=Pdo*(1+m**2/2); //W
16 printf(" modulation index = %.1f",m)
17 printf("\n carrier power under modulated condition =
%0.2f kW",P/1000)
18 printf("\n plate circuit efficiency = %.f percent",
eta)
19 printf("\n plate dissipation under unmodulated

```

```
    condition = %.1f kW" ,Pdo/1000)
20 printf("\n plate dissipation under modulated
    condition = %.2f kW" ,Pd/1000)
```

Scilab code Exa 1.23 Series and Parallel equivalent circuit

```
1 // Ex 23 Page 364
2
3 clc;clear;close;
4 // Given
5 Zo=50; //ohm
6 VSWR=2; // ratio
7 //lm=0.2*lamda
8 lmBYlamda=0.2
9 betaINT0lamda=2*pi
10 rho=(VSWR-1)/(VSWR+1); // reflection coefficient
11 theta=2*betaINT0lamda*lmBYlamda; // radian
12 //exp(j*theta)=cos(theta)+%i*sin(theta)
13 ZL=Zo*(1-rho*(cos(theta)+%i*sin(theta)))/(1+rho*(cos
    (theta)+%i*sin(theta))); //ohm
14 Rs=real(ZL); //ohm
15 Xs=abs(imag(ZL)); //ohm( capacitive )
16 printf("Series equivalent circuit:")
17 printf("\n Rs = %0.1f ohm",Rs)
18 printf("\n Xs = %0.1f ohm",Xs)
19 YL=(1/ZL)*1000; //mS
20 Rp=1000/real(YL); //ohm
21 Xp=1000/imag(YL); //ohm
22 printf("\n\n Parallel equivalent circuit:")
23 printf("\n Rp = %0.1f ohm",Rp)
24 printf("\n Xp = %0.1f ohm",Xp)
```

Scilab code Exa 1.24 Characteristic wave impedance

```

1 // Ex 24 Page 366
2
3 clc;clear;close;
4 // Given
5 b=3; //cm
6 a=4.5; //cm
7 f=9*10**9; //Hz
8 v=3*10**10; //cm/s
9 lamda=v/f; //cm
10
11 printf("\n For TE10 mode:")
12 m=1; // for TE10 mode
13 lamda_c = 2*a/m; //cm
14 rho=sqrt(1-(lamda/lamda_c)**2)
15 lamda_g=lamda/rho; //cm
16 vg=rho*v; //cm/s
17 vp=v/rho; //cm/s
18 ZTE=120*pi*rho; //ohm
19
20 printf("\n cutoff wavelength = %.f cm",lamda_c)
21 printf("\n guide wavelength = %.2f cm",lamda_g)
22 printf("\n Group velocity = %.1e m/s",vg/100)
23 printf("\n Phase velocity = %.1e m/s",vp/100)
24 printf("\n Characteristic wave impedance = %.f ohm",
ZTE)
25
26 printf("\n\n For TM11 mode:")
27 m=1;n=1 // for TE10 mode
28 lamda_c = 2/sqrt((m/a)**2+(n/b)**2); //cm
29 rho=sqrt(1-(lamda/lamda_c)**2)
30 lamda_g=lamda/rho; //cm
31 vg=rho*v; //cm/s
32 vp=v/rho; //cm/s
33 ZTM=120*pi*rho; //ohm
34 printf("\n cutoff wavelength = %.f cm",lamda_c)
35 printf("\n guide wavelength = %.2f cm",lamda_g)
36 printf("\n Group velocity = %.1e m/s",vg/100)
37 printf("\n Phase velocity = %.1e m/s",vp/100)

```

```
38 printf("\n Characteristic wave impedance = %.f ohm" ,  
ZTM)
```

Scilab code Exa 1.25 capacitance ratio

```
1 // Ex 25 Page 367  
2  
3 clc;clear;close;  
4 // Given  
5 fs_max=1600; //kHz  
6 fs_min=500; //kHz  
7 IF=465; //kHz  
8  
9 fr=fs_max/fs_min; //ratio  
10 C_ratio = fr**2; //Cs_max/Cs_min  
11 //Part (a)  
12 fo_min=IF+fs_min; //kHz  
13 fo_max=IF+fs_max; //kHz  
14 fr_o=fo_max/fo_min; //frequency ratio for oscillator  
15 C_ratio_o = fr_o**2; //Cs_max/Cs_min  
16 printf(" part(a):")  
17 printf("\n For fo>fs , the range of fo : %.f to %.f  
kHz" ,fo_min,fo_max)  
18 printf("\n frequency ratio = %.2f" ,fr_o)  
19 printf("\n capacitance ratio = %.2f" ,C_ratio_o)  
20  
21 //Part (b)  
22 fo_min=-IF+fs_min; //kHz  
23 fo_max=-IF+fs_max; //kHz  
24 fr_o=fo_max/fo_min; //frequency ratio for oscillator  
25 C_ratio_o = fr_o**2; //Cs_max/Cs_min  
26 printf("\n\n part(b):")  
27 printf("\n For fo>fs , the range of fo : %.f to %.f  
kHz" ,fo_min,fo_max)  
28 printf("\n frequency ratio = %.1f" ,fr_o)
```

```
29 printf("\n capacitance ratio = %.1f",C_ratio_o)
30 //ans wrong for part b in the book.
```

Scilab code Exa 1.26 Resistor values

```
1 // Ex 26 Page 368
2
3 clc;clear;close;
4 // Given
5 Ic=3; //mA
6 hfe=45; //unitless
7 Vcc=12; //V
8 VBE=0.5; //V
9 S=0.05; //stability factor
10 Beta=45; //unitless
11
12 RR=Vcc/2/(Ic*10**-3); //ohm (let RL+Re=RR)
13 //Re=20% of (Re+Rl)
14 Re=RR*20/100; //ohm
15 RL=RR-Re; //ohm
16 Ve=(Ic+Ic/Beta)*10**-3*Re; //V
17 Vb=Ve+VBE; //V
18 //S=Re/Rb=0.5 => Rb=Re/S
19 R1=Vcc*Re/S/Vb/1000; //kohm
20 // Vb/Vcc = R2/(R2+R1)
21 R2=Vb*R1/(Vcc-Vb); //kohm
22 printf("Resistor values are : ")
23 printf("\n RL=%2f kohm",RL/1000)
24 printf("\n Re=%2f kohm",Re/1000)
25 printf("\n R1=%2f kohm",R1)
26 printf("\n R2=%2f kohm",R2)
```

Scilab code Exa 1.27 conversion efficiency

```

1 // Ex 27 Page 369
2
3 clc;clear;close;
4 // Given
5 Vcc=50; //V
6 Vmin=10; //V
7 Pd=40; //W
8
9
10 Vo=Vcc-Vmin; //V
11 K=Vo/Vcc; //constant
12 Rdash=2*Vcc**2/%pi/Pd*(K-%pi*K**2/4); //ohm
13 Po=K**2*Vcc**2/2/Rdash; //W
14 eta=%pi*K/4*100; //%
15
16 printf("load presented by transformer = %.1f ohm" ,
      Rdash)
17 printf("\n load power output = %.1f W",Po)
18 printf("\n conversion efficiency = %.1f percent",eta
      )

```

Scilab code Exa 1.28 Cyrrrent and Voltage gain

```

1 // Ex 28 Page 370
2
3 clc;clear;close;
4 // Given
5 Rs=1000; //ohm
6 Rc1=2*1000; //ohm
7 Re2=2*1000; //ohm
8 //CE configuration
9 hie=1100; //ohm
10 hre=2.5*10**-4;
11 hfe=50;
12 hoe=25*10**-6; //s

```

```

13 //CC configuration
14 hic=1.1; //kohm
15 hrc=1;
16 hfc=-51;
17 hoc=25*10**-6; //s
18
19 printf(" for 2nd stage(CC stage)") )
20 AI2=-hfc/(1+hoe*Re2); //current gain
21 Ri2=hic+hrc*AI2*Re2; //kohm
22 Av2=AI2*Re2/Ri2; //Voltage Gain
23 printf("\n current gain = %.2f",AI2)
24 printf("\n Input impedance = %.2f kohm",Ri2/1000)
25 printf("\n Voltage gain = %.2f",Av2)
26
27 printf("\n\n for 1st stage(CE stage)") )
28 RL1=Rc1*Ri2/(Rc1+Ri2); //kohm
29 AI1=-hfe/(1+hoe*RL1); //current gain
30 printf("\n current gain = %.2f",AI1)
31 Ri1=hie+hre*AI1*RL1; //kohm
32 printf("\n Input impedance = %.2f kohm",Ri1/1000)
33 Av1=AI1*RL1/Ri1; //Voltage gain
34 printf("\n Voltage gain = %.2f",Av1)
35 Ro1=1/(hoe-hfe*hre/(hie+100)); //ohm
36 printf("\n Output impedance = %.2f kohm",Ro1/1000)
37 Ro1dash=Ro1*Rc1/(Ro1+Rc1); ////ohm
38 printf("\n Output impedance taking Rc1 into account
      = %.2f kohm",Ro1dash/1000)
39
40 printf("\n\n for overall amplifier")
41 Ro=1/(hoc*100-hfc*hrc/(hic+Ro1dash)); //ohm
42 printf("\n Output impedance = %.2f ohm",Ro)
43 Rodash=Ro*Re2*1000/(Ro1+Re2*1000); ////ohm
44 printf("\n Output impedance taking Re2 into account
      = %.2f ohm",Rodash)
45 AI=AI1*AI2*Rc1/(Ri2+Rc1); // current gain
46 printf("\n current gain = %.2f",AI)
47 Av=Av1*Av2; //voltage gain
48 printf("\n Voltage gain = %.2f",Av)

```

49 // answer is wrong for overall amplifier in the book.

Scilab code Exa 1.29 Current gain BW product

```
1 // Ex 29 Page 372
2
3 clc;clear;close;
4 // Given
5 fT=6*10**6; //Hz
6 hfe=50;
7 Rs=500; //ohm
8 gm=0.04; //S
9 rbb_dash=100; //ohm
10 Cc=10*10**-12; //F
11 RL=1; //kohm
12
13 rbe=hfe/gm; //ohm
14 Ce=gm/2/%pi/fT; //F
15 C=Ce+Cc*(1+gm*RL); //F
16 hie=rbb_dash+rbe; //ohm
17 R=(Rs+rbb_dash)*rbe/((Rs+rbb_dash)+rbe); //ohm
18 f2=1/2/%pi/R/C; //Hz
19 printf("Voltage gain upper BW frequency = %.2f MHz" ,
   f2/10**6)
20 AIS=-hfe*Rs/(Rs+hie); //current gain
21 printf("\n Current gain = %.2f",AIS)
22 AVS=-hfe*RL*1000/(Rs+hie); //voltage gain
23 printf("\n Voltage gain = %.2f",AVS)
24 AVSf2=AVS*f2; //Hz
25 printf("\n Voltage gain BW product = %.2f MHz",abs(
   AVSf2/10**6))
26 AISf2=AIS*f2; //Hz
27 printf("\n Current gain BW product = %.2f MHz",abs(
   AISf2/10**6))
28
```

29 // answer in the textbook are wrong.

Scilab code Exa 1.30 Vgs and gm

```
1 // Ex 30 Page 373
2
3 clc;clear;close;
4 // Given
5 VP=-2; //V
6 IDSS=1.75/1000; //A
7 VDD=24; //V
8 ID=1/1000; //A
9 VP=0.2; //V (pinch off voltage)
10
11 VGS=(1-sqrt(ID/IDSS))*VP; //V
12 gmo=-2*IDSS/VP; //S
13 gm=gmo*(1-VGS/VP); //S
14 Rs=-VGS/ID; //ohm
15
16 printf("VGS=%f V",VGS)
17 printf("\n gm = %f mS",gm*1000)
18 printf("\n Rs = %f ohm",Rs)
19 //Ans are wrong in the book.
```

Scilab code Exa 1.31 Bandwidth of redesigned amplifier

```
1 // Ex 31 Page 374
2
3 clc;clear;close;
4 // Given
5 G=37; //dB
6 f1=50; //Hz
7 f2=18.7*1000; //Hz
```

```

8 BW1=f2; //Hz ( f2-f1 ~=f2 )
9
10
11 A1=10** (G/20); //Gain
12 A3=sqrt(A1); //Gain
13 RL1BYRL2=A1/A3; // ratio
14 RL2BYRL1=A3/A1; // ratio
15 //BW=2*pi*Cd*RL
16 BW1BYBW2=RL2BYRL1;
17 BW2BYBW1=RL1BYRL2;
18 f2dash=f2*sqrt(sqrt(2)-1);
19 BW2=BW2BYBW1*f2dash; //Hz
20 printf(" Bandwidth of redesigned amplifier , BW=%f
kHz" ,BW2/1000)

```

Scilab code Exa 1.32 Critical inductance

```

1 // Ex 32 Page 375
2
3 clc; clear; close;
4 // Given
5 L=30; //H
6 C=10*10**-6; //F
7 RL=8*10**3; //ohm
8 f=50; //Hz
9
10 r=sqrt(2)/12/(2*pi*f)**2/L/C*100; //%
11 Lc=2*RL/6/(2*pi*f); //H
12 printf(" ripple factor = %.1f percent" ,r)
13 printf("\n Critical inductance , Lc=%.1f H" ,Lc)

```

Scilab code Exa 1.33 Current in each armature

```

1 // Ex 33 Page 376
2
3 clc;clear;close;
4 // Given
5 V=500; //V
6 Pp=1500*10**3; //W (+ve side)
7 Pn=2000*10**3; //W (-ve side)
8
9 P=Pp+Pn; //W
10 I=P/V; //A
11 Ip=Pp/(V/2); //A
12 In=Pn/(V/2); //A
13 Iob=In-Ip; //A
14 Ia=Iob/2; //A
15 printf("Current supplied by the main generator = %.f
A",I)
16 printf("\n Current supplied on +ve side = %.f A",Ip)
17 printf("\n Current supplied on -ve side = %.f A",In)
18 printf("\n out-off balance Current = %.f A",Iob)
19 printf("\n Current in each armature = %.f A",Ia)

```

Scilab code Exa 1.34 Efficiency and regulation

```

1 // Ex 34 Page 377
2
3 clc;clear;close;
4 // Given
5 l=20; //km
6 P=10000; //kW
7 V=11; //kV
8 pf=0.707; //lagging
9 R=0.02; //ohm/km/phase
10 X=0.07; //ohm/km/phase
11
12 //for pf = 0.707

```

```

13
14 IL=P*10**3/sqrt(3)/(V*1000)/pf; //A
15 VRphase=V*1000/sqrt(3); //V
16 R_phase=1*R; //ohm
17 X_phase=1*X; //ohm
18 Z_phase=R_phase+%i*X_phase; //ohm
19 Vd_phase=IL*(pf-%i*pf)*Z_phase; //V
20 VS=(Vd_phase+VRphase); //V
21 regulation=(VS-VRphase)/VRphase*100; //%
22 printf("regulation = %.f percent", regulation)
23 PL=3*IL^2*R_phase/1000; //kW
24 Po=P+PL; //kW
25 eta=P/Po*100; //%
26 printf("\n Efficiency = %.f percent", eta)
27
28 // for pf2=0.9; // lagging
29 pf=0.9; // lagging
30 IL=P*10**3/sqrt(3)/(V*1000)/pf; //A
31 VRphase=V*1000/sqrt(3); //V
32 R_phase=1*R; //ohm
33 X_phase=1*X; //ohm
34 Z_phase=R_phase+%i*X_phase; //ohm
35 Vd_phase=IL*(pf-%i*.435)*Z_phase; //V
36 VS=(Vd_phase+VRphase); //V
37 regulation=(VS-VRphase)/VRphase*100; //%
38 printf("\n\n regulation = %.1f percent", regulation)
39 PL=3*IL^2*R_phase/1000; //kW
40 Po=P+PL; //kW
41 eta=P/Po*100; //%
42 printf("\n Efficiency = %.f percent", eta)
43 //ans wrong for 2nd part in the book.

```

Scilab code Exa 1.35 load factor

1 // Ex 35 Page 378

```

2
3 clc;clear;close;
4 // Given
5 C1=1.2; //Rs
6 C2=5; //Rs
7 P1=100; //W
8 P2=30; //W
9 t=1000; //hours
10 Ce=60; //Rs/kW/annum for max demand
11 Cee=3 ; // paise/unit for extra
12
13 //first lamp
14 C11=C1*t; // paise / hour
15 dmax1=P1/1000; //kW/hour
16 Cmax1=Ce*100*dmax1/(24*365); // paise/hour
17 CE1=Cee*dmax1; //// paise / hour
18 CT1=C11+Cmax1+CE1; //paise (total cost per hour)
19 printf("lamp1 : Total cost/hour = %.3f paise",CT1)
20 //second lamp
21 C12=C2*t; // paise / hour
22 dmax2=P2/1000; //kW/hour
23 Cmax2=Ce*100*dmax2/(24*365); // paise/hour
24 CE2=Cee*dmax2; //// paise / hour
25 CT2=C12+Cmax2+CE2; //paise (total cost per hour)
26 printf("\n lamp2 : Total cost/hour = %.2f paise",CT2
    )
27 printf("\n on comparing cost it is clear lamp1 will
        be more economical. ")
28 //let load factor = x
29 //C11+Cmax1/x+CE1=C12+Cmax2/x+CE2
30 x=(Cmax1-Cmax2)/(C12+CE2-C11-CE1)*100; // % load
        factor
31 printf("\n\n load factor = %.f percent",x)

```

Scilab code Exa 1.36 shunt field turns

```

1 // Ex 36 Page 379
2
3 clc;clear;close;
4 // Given
5 p=4; //pole
6 I1=143; //A
7 Z=492; //armature conductors
8 theta=10; //degree
9 I2=10; //A
10
11 Ia=I1+I2; //A
12 Iw=Ia/2; //A for wave sound
13 Il=Ia/4; //for lap sound
14 //part(a)
15 ATw=Z*Iw*theta/360; //AT
16 nw=ATw/theta; //turns
17 printf("(a) extra shunt field turns required = %d",
nw)
18
19 //part(b)
20 ATL=Z*Il*theta/360; //AT
21 nl=ATL/theta; //turns
22 printf("\n (b) extra shunt field turns required = %d
",nl)
23 //answer wrong for part(a) in the book.

```

Scilab code Exa 1.37 New speed

```

1 // Ex 37 Page 380
2
3 clc;clear;close;
4 // Given
5 Wh=250; //W
6 We=100; //W
7 N=1000/60; //rps

```

```

8
9 A=Wh/N; //constant
10 B=We/N**2; //constant
11 Wnew=1/2*(Wh+We); //W
12 //Wnew=A*N1+B*N1**2
13 p=[B,A,-Wnew]; //polynomial for N1
14 N1=roots(p); //rps
15 N1=N1(2)*60; //rpm//discarding -ve value
16 printf("New speed will be %.f rpm",N1)

```

Scilab code Exa 1.38 Speed of the machine

```

1 // Ex 38 Page 381
2
3 clc;clear;close;
4 // Given
5 P=50; //kW
6 V=250 //V
7 N1=400; //rpm
8 Ra=0.02; //ohm
9 Rf=50; //ohm
10 Pi=50; //kW
11 Vin=250; //V
12 Vd=1; //V per Brush
13
14 I=P*10**3/V //A
15 Ish=V/Rf; //A
16 Ia=I+Ish; //A
17 Va=Ia*Ra; //V
18 Vbd=2*Vd; //V
19 Eb1=V+Va+Vbd; //V
20
21
22 //as motor
23 I=P*10**3/V //A

```

```

24 Ish=V/Rf; //A
25 Ia=I-Ish; //A
26
27 Va=Ia*Ra; //V
28 Vbd=2*Vd; //V
29 Eb2=V-Va-Vbd; //V
30 N2=(Eb2/Eb1)*N1; //rpm
31 printf("Speed of the machine running as shunt motor
          = %.f rpm", N2)

```

Scilab code Exa 1.39 Generator efficiency

```

1 // Ex 39 Page 383
2
3 clc;clear;close;
4 // Given
5 VL=250; //V
6 Is=50; //A
7 Ia=380; //A
8 If1=5; //A
9 If2=4.2; //A
10 ra=0.02; //ohm
11
12 //Machine Losses:
13 ma_cu_loss=Ia**2*ra; //W (motor armature cu loss)
14 ga_cu_loss=(Ia-Is)**2*ra; //W (generator armature cu
     loss)
15 P=VL*Is; //W
16 stray_loss=P-ma_cu_loss-ga_cu_loss; //W
17 stray_loss_per_machine=stray_loss/2; //W
18
19 //Motor efficiency
20 field_cu_loss=VL*If2; //W
21 total_loss=ma_cu_loss+field_cu_loss+
           stray_loss_per_machine; //W

```

```

22 Pin_motor=(VL*Ia)+(VL*ra); //W
23 Pout_motor=Pin_motor-total_loss; //W
24 Eff=Pout_motor/Pin_motor*100; //%
25 printf("Motor efficiency = %.f percent",Eff)
26
27
28 //Generator efficiency
29 field_cu_loss=VL*If1; //W
30 total_loss=ga_cu_loss+field_cu_loss+
    stray_loss_per_machine; //W
31 Pout_generator=VL*(Ia-Is); //W
32 Pin_generator=Pout_generator+total_loss; //W
33 Eff=Pout_motor/Pin_motor*100; //%
34 printf("\n Generator efficiency = %.f percent",Eff)

```

Scilab code Exa 1.40 Voltage drop

```

1 // Ex 40 Page 384
2
3 clc;clear;close;
4 // Given
5 KVA=4; //kVA
6 V1=200 //V
7 V2=400 //V
8 f=50; //Hz
9 Io1=0.8; //A
10 P1=70; //W
11 Vs2=17.5; //V
12 Is2=9; //A
13 P2=50; //W
14
15 // full load
16 I_loss=P1; //W
17 I2=KVA*1000/V2; //A
18 Cu_loss=(I2/Is2)**2*P2; //W

```

```

19 Zo2=Vs2/Is2; //ohm
20 Ro2=P2/Is2**2; //ohm
21 Xo2=sqrt(Zo2**2-Ro2**2); //ohm
22
23 // (a)
24 printf("Full load efficiency : ")
25 // unity pf
26 pf=1; //power factor
27 Output=KVA*pf; //kW
28 Losses=Cu_loss+I_loss; //W
29 eta=Output*1000/(Output*1000+Losses)*100; //%
30 printf("\n at unity power factor = %.1f percent",eta
    )
31 // 0.8 pf
32 pf=0.8; //power factor
33 Output=KVA*pf; //kW
34 eta=Output*1000/(Output*1000+Losses)*100; //%
35 printf("\n at 0.8 power factor = %.1f percent",eta)
36
37 // (b)
38 // (i) unity pf
39 Vd=I2*Ro2; //V
40 V22=V2-Vd; //V
41 printf("\n\n Voltage drop at unity pf = %.1f V",V22)
42 // (i) 0.8 pf lagging
43 pf=0.8; //power factor
44 Vd=I2*(Ro2*pf+Xo2*sqrt(1-pf**2)); //V
45 V22=V2-Vd; //V
46 printf("\n Voltage drop at 0.8 pf lagging = %.1f V",
    V22)
47 // (i) 0.8 pf leading
48 pf=0.8; //power factor
49 Vd=I2*(Ro2*pf-Xo2*sqrt(1-pf**2)); //V
50 V22=V2-Vd; //V
51 printf("\n Voltage drop at 0.8 pf leading = %.1f V",
    V22)

```

Scilab code Exa 1.41 All day efficiency

```
1 // Ex 41 Page 385
2
3 clc;clear;close;
4 // Given
5 KVA=15; //kVA
6 pf=1;
7 eff=98/100; //efficiency
8
9 L1=2; //kW
10 pf1=0.5; //lagging
11 t1=12; //hours
12 L2=12; //kW
13 pf2=0.8; //lagging
14 t2=6; //hours
15 L3=18; //kW
16 pf3=0.9; //lagging
17 t3=6; //hours
18
19 Po=KVA*pf; //kW
20 Pin=Po/eff; //kW
21 Losses=Pin-Po; //kW
22 Cu_loss=Losses/2; //kW
23 I_loss=Losses/2; //kW
24
25 KVA1=L1/pf1; //kVA
26 KVA2=L2/pf2; //kVA
27 KVA3=L3/pf3; //kVA
28 Cu_loss1=Cu_loss*(KVA1/KVA2)**2; //kW
29 Cu_loss2=Cu_loss*(KVA2/KVA2)**2; //kW
30 Cu_loss3=Cu_loss*(KVA3/KVA2)**2; //kW
31
32 Cu_loss_t1=Cu_loss1*t1; //kW
```

```

33 Cu_loss_t2=Cu_loss2*t2; //kW
34 Cu_loss_t3=Cu_loss3*t3; //kW
35 Cu_loss_total=Cu_loss_t1+Cu_loss_t2+Cu_loss_t3; //kW
36 I_loss24=I_loss*24; //Wh
37
38 Po24=L1*t1+L2*t2+L3*t3; //kWh
39 Pi24=Po24+Cu_loss_total+I_loss24; //kWh
40 eff_allday=Po24/Pi24*100; //%
41 printf("All day efficiency = %.f percent", eff_allday
)

```

Scilab code Exa 1.42 Current drawn by the transformer

```

1 // Ex 42 Page 386
2
3 clc;clear;close;
4 // Given
5 V1=250; //V
6 V2=150; //V
7 Vs1=200; //V
8 Load1=5; //kW
9 pf1=0.8; //lagging
10 Load2=2; //kW
11 pf2=1; //unity
12 Vs2=100; //V
13
14 I1=Load1*1000/V1/pf1; //A
15 t1_ratio=V1/Vs1; //
16 Ip1=I1*t1_ratio; //A at 0.8 pf (current drawn by
primary)
17
18 I2=Load2*1000/Vs2/pf2; //A
19 t2_ratio=Vs2/V2; //
20 Ip2=I2*t2_ratio; //A at 0.8 pf (current drawn by
primary)

```

```

21
22 Ipx=Ip1*pf1+Ip2; //A
23 Ipy=Ip1*sqrt(1-pf1**2); //A
24 I3=sqrt(Ipx**2+Ipy**2); //A
25 printf("Current drawn by the transformer=%f A",I3)
26 pf=Ip1/I3; //power factor
27 printf("\n power factor = %.1f lagging",pf)

```

Scilab code Exa 1.43 Percentage reduction in stator voltage

```

1 // Ex 43 Page 387
2
3 clc;clear;close;
4 // Given
5 R2=0.03; //ohm
6 X2=0.18; //ohm
7 Ns=100; //rpm
8 s1=3; //%
9
10
11 Nfl=(100-s1); //rpm ( full load speed )
12 N2=Nfl/2; //rpm
13 s2=(Ns-N2)/Ns*100; //%
14 V1BYV2=sqrt(s2/s1*(R2**2+(s1/100*X2)**2)/(R2**2+(s2
    /100*X2)**2)); //from torque equation
15 //let V1=V12BYV1 V2=1
16 V1=V1BYV2; //V
17 V2=1; //V
18 V12BYV1=(V1-1)/V1*100; // % reduction in the stator (
    V12=V1-V2)
19 printf("Percentage reduction in stator voltage = %.f
    percent",V12BYV1)
20 fi=atan(s2/100*X2/R2); //radian
21 pf=cos(fi); //power factor
22 printf("\n power factor = %.1f",pf)

```

Scilab code Exa 1.44 Torque ratio

```
1 // Ex 44 Page 388
2
3 clc;clear;close;
4 // Given
5 zo=1+%i*1; //ohm
6 zi=0.2+%i*4; //ohm
7 Ri=real(zi) ; //ohm
8 Ro=real(zo) ; //ohm
9
10 //at standstill
11 s=1; // at standstill
12 Zo=sqrt(real(zo)**2+imag(zo)**2); //ohm
13 Zi=sqrt(real(zi)**2+imag(zi)**2); //ohm
14 ToBYTi=Ro/Ri*(Zi/Zo)**2; //torque ratio
15 printf("(a) at standstill , To:Ti = %d:1",ToBYTi)
16
17 //at s=0.5
18 s=0.05; //%
19 Zo=sqrt(real(zo)**2/s**2+imag(zo)**2); //ohm
20 Zi=sqrt(real(zi)**2/s**2+imag(zi)**2); //ohm
21 ToBYTi=Ro/Ri*(Zi/Zo)**2; //torque ratio
22 printf("\n (b) at s=0.05 , To:Ti = %.1f:1",ToBYTi)
```

Scilab code Exa 1.45 cross section of windings

```
1 // Ex 45 Page 389
2
3 clc;clear;close;
4 // Given
```

```

5 Edc=500; //V
6 fim=.085; //Wb
7 f=50; //Hz
8 E1=11000; //V
9 P=1500; //kW
10 p=8; //pole
11 pf=0.9
12 V=500; //V
13 J=3; //A/mm^2
14
15 E2=Edc/sqrt(2)//V
16 N2=E2/4.44/f/fim; //no. of turns
17 N1=E1/E2*N2; //no. of turns
18 printf("no. of turns in primary = %d",N1)
19 printf("\n no. of turns in secondary = %d",N2)
20 Idc=P*10**3/V;//A
21 eta=1; //because of no loss
22 ISR=0.472*Idc/(eta*pf)
23 A1=ISR/J*10**-6; //m^2 (cross section area)
24 I1=N2/N1*ISR;//A
25 A2=I1/J*10**-6; //m**2 (cross section area of primary
winding)
26 printf("\n\n cross section of primary winding=%e m
^2",A1)
27 printf("\n cross section of secondary winding=%e m
^2",A2)
28 //ans in the book are not accurate.

```

Scilab code Exa 1.46 Starting torque

```

1 // Ex 46 Page 391
2
3 clc;clear;close;
4 // Given
5 IscBYIf1=5; // as Isc=5* If1

```

```

6 ILByIf1=3; // as IL <= 3* If1
7 sf=5; //%
8
9 //IL=K**2*ISC
10 //dividing by If1
11 K=sqrt(ILByIf1/IscBYIf1)*100; //%
12 TstBYTf=(K/100)**2*IscBYIf1*sf/100*100; // % //ratio
    of torque
13 printf("Suitable auto transformation ratio = %.1f",K)
14 printf("\n Starting torque Tst = %.f percent of full
    -load torque",TstBYTf)
15 //ans wrong in the textbook.

```

Scilab code Exa 1.47 Resistance of all section

```

1 // Ex 47 Page 391
2
3 clc;clear;close;
4 // Given
5 V=500; //V
6 ns=60; //slots
7 nc=20; //conductor/slot
8 ra=1.31; //ohm
9 Tmax=218; //N-m
10 fi=23*10**-3; //Wb
11
12 Tmin=Tmax/1.5 //N-m
13 Z=ns*nc; //no of conductors
14 Ia=Tmax/(.159*fi*Z); //A
15 Imax=1.5*Ia; //A
16 I1=Imax; //A
17 I2=Ia; //A
18 R1=V/I1; //ohm
19 n= log(R1/ra)/log(I1/I2)+1; //no of studs

```

```

20 N=n-1; //no of section
21 printf("no of studs = %d and no. of section = %d",n,
N)
22 R2=R1*(I2/I1); //ohm
23 R3=R2*(I2/I1); //ohm
24 R4=R3*(I2/I1); //ohm
25 R1s=R1-R2; //ohm
26 R2s=R2-R3; //ohm
27 R3s=R3-R4; //ohm
28 R4s=R4-ra; //ohm
29 printf("\n\n Resistance of 1st section = %.2f ohm" ,
R1s)
30 printf("\n Resistance of 2nd section = %.2f ohm" ,R2s
)
31 printf("\n Resistance of 3rd section = %.2f ohm" ,R3s
)
32 printf("\n Resistance of 4th section = %.2f ohm" ,R4s
)

```

Scilab code Exa 1.48 temperature rise

```

1 // Ex 48 Page 393
2
3 clc;clear;close;
4 // Given
5 theta1=20; //degree C
6 theta2=35; //degree C
7 t1=0.5; //hour
8 t2=1; //hour
9 theta_m_dashBYthetam=80/100; //temperature rise
10
11 //theta=theta_m*(1-e**(-t / alfa ))
12 //theta1/theta2=(1-%e**(-t1 / alfa ))/(1-%e**(-t2 / alfa ))
13 ee1=theta2/theta1-1; //let ee1=exp(-1/2/ alfa )

```

```

14 theta_m=theta1/(1-ee1); //degree C
15 theta_2=theta_m*(1-ee1**4); // degree C ( after 2
    hours)
16 printf("temperature rise after 2 hours full load = %
        .f degree C",theta_2)
17 alfa=-1/2*log(ee1); //hour
18 alfa_dash=theta_m_dashBYthetam*alfa; //hour
19 theta_m_dash=theta_m_dashBYthetam*theta_m
20 theta_dash=theta_m_dash*(1-%e**(-t2/alfa))
21 printf("\n temperature rise of cold water after 1
        hour = %.f degree C",theta_dash)
22 //ans of 2nd part is wrong in the book.

```

Scilab code Exa 1.49 Regulation at full load voltage

```

1 // Ex 49 Page 394
2
3 clc;clear;close;
4 // Given
5 u=30; //degree
6 m=3; //no of phases
7
8 //Id=sqrt(2)*Vs*X*(1-cosd(u))*sin(%pi/m)
9 IdBYVs_dash=m/2/%pi*(1-cosd(u))*sin(%pi/m)*sqrt(2);
    //load current/Vs
10 //where IdBYVs_dash = m/%pi*IdX/2
11 EdoBYVs=sqrt(2)*m/%pi*sin(%pi/m); //dc output voltage
    /Vs with no overlap
12 EduBYVs=EdoBYVs-IdBYVs_dash; //dc output voltage/Vs
    with overlap
13 //part (a)
14 Reg1=(EdoBYVs-EduBYVs)/EdoBYVs*100; //% ( regulation )
15 printf("Regulation at no load voltage = %.1f percent
        ",Reg1)
16 //part (b)

```

```

17 Reg2=(EdoBYVs-EduBYVs)/EduBYVs*100; //% ( regulation )
18 printf("\n Regulation at full load voltage = %.1f
    percent",Reg2)

```

Scilab code Exa 1.50 Power output

```

1 // Ex 50 Page 395
2
3 clc;clear;close;
4 // Given
5 I12=2000; //A ( I12=I1+I2 )
6 R1=0.04; //ohm
7 R2=0.025; //ohm
8 rf1=25; //ohm
9 rf2=20; //ohm
10 E1=440; //V
11 E2=420; //V
12
13 //E-Vad=V where Vad=I1+V/rf1
14 //V*(1+R1/rf1)+R1*I1=E1//eqn(1)
15 //V*(1+R2/rf2)-I1*R2=E2-I12*R2// eqn(2)
16 A=[(1+R1/rf1),R1;(1+R2/rf2),-R2]; // matrix for
    solution
17 B=[E1;E2-I12*R2]; //matrix for solution
18 X=A**-1*B; //solution
19 V=X(1); //V
20 I1=X(2); //A
21 I2=I12-I1; //A
22 printf("Current for each machine = %.f A & %.f A ", 
    I1,I2)
23 Po1=V*I1; //W
24 Po2=V*I2; //W
25 printf("\n Power output for each machine = %.1f kW &
    %.1f kW",Po1/1000,Po2/1000)
26 //ans in the book are wrong.

```

Scilab code Exa 1.51 power output

```
1 // Ex 51 Page 396
2
3 clc;clear;close;
4 // Given
5 ZA=0.15+0.5*%i; //ohm
6 ZB=0.1+0.6*%i; //ohm
7 EA=207; //V
8 EB=205; //V
9 ZL=2+1.5*%i; //ohm
10
11 IA=(EA*ZB+(EA-EB)*ZL)/(ZA*ZB+ZL*(ZA+ZB)); //A
12 IB=(EB*ZA-(EA-EB)*ZL)/(ZA*ZB+ZL*(ZA+ZB)); //A
13 V2=(IA+IB)*ZL; //V
14 fi_A=atand(imag(V2)/real(V2))-(atand(imag(IA))/real(
    IA)))
15 pf_A=cosd(fi_A); //lag
16 printf(" pf transformer A = %.2f lag",pf_A)
17 fi_B=atand(imag(V2)/real(V2))-(atand(imag(IB))/real(
    IB)))
18 pf_B=cosd(fi_B); //lag
19 printf("\n pf transformer B = %.2f lag",pf_B)
20 PA=abs(V2*IA*pf_A); //W
21 printf("\n power output transformer A = %.f W",PA)
22 PB=abs(V2*IB*pf_B); //W
23 printf("\n power output transformer B = %.f W",PB)
24 //Power output ans are wrong in the book.
```

Scilab code Exa 1.52 filament diameter

```
1 // Ex 52 Page 397
2
3 clc;clear;close;
4 // Given
5 d1=0.05*10**-3; //mm
6 l1=100*10**-2; //m
7 i2BYi1=1/4; //current ratio
8 //(d2/d1)**(3/2)=i2BYi1
9 d2=(i2BYi1)**(2/3)*d1*10**6; //um
10 l2=1/2*l1*d1/d2*10**6; //m
11 printf(" filament length = %.2f m" ,l2)
12 printf("\n filament diameter = %.f um" ,d2)
```

Scilab code Exa 1.53 filament diameter

```
1 // Ex 53 Page 398
2
3 clc;clear;close;
4 // Given
5 d1=0.10*10**-3; //mm
6 l1=150*10**-2; //m
7 i2BYi1=1/3; //current ratio
8 //(d2/d1)**(3/2)=i2BYi1
9 d2=(i2BYi1)**(2/3)*d1*10**6; //um
10 l2=1/2*l1*d1/d2*10**6; //m
11 printf(" filament length = %.1f m" ,l2)
12 printf("\n filament diameter = %.f um" ,d2)
```

Scilab code Exa 1.54 Torque ratio

```
1 // Ex 54 Page 398
2
3 clc;clear;close;
```

```

4 // Given
5 zo=2+%i*2; //ohm
6 zi=0.5+%i*4; //ohm
7 Ri=real(zi) ;//ohm
8 Ro=real(zo) ;//ohm
9
10 //at standstill
11 s=1; // at standstill
12 Zo=sqrt(real(zo)**2+imag(zo)**2); //ohm
13 Zi=sqrt(real(zi)**2+imag(zi)**2); //ohm
14 ToBYTi=Ro/Ri*(Zi/Zo)**2; //torque ratio
15 printf("(a) at standstill , To:Ti = %d:1",ToBYTi)
16
17 //at s=0.5
18 s=0.05; //%
19 Zo=sqrt(real(zo)**2/s**2+imag(zo)**2); //ohm
20 Zi=sqrt(real(zi)**2/s**2+imag(zi)**2); //ohm
21 ToBYTi=Ro/Ri*(Zi/Zo)**2; //torque ratio
22 printf("\n (b) at s=0.05 , To:Ti = %.f:10",ToBYTi*10)

```

Scilab code Exa 1.55 cross section of primary winding

```

1 // Ex 55 Page 400
2
3 clc;clear;close;
4 // Given
5 Edc=250; //V
6 fim=.065; //Wb
7 f=50; //Hz
8 E1=6000; //V
9 P=1500; //kW
10 p=8; //pole
11 pf=0.9
12 V=400; //V
13 J=3; //A/mm^2

```

```

14
15 E2=Edc/sqrt(2)//V
16 N2=E2/4.44/f/fim; //no. of turns
17 N1=E1/E2*N2; //no. of turns
18 printf("no. of turns in primary = %d",N1)
19 printf("\n no. of turns in secondary = %d",N2)
20 Idc=P*10**3/V;//A
21 eta=1; //because of no loss
22 ISR=0.472*Idc/(eta*pf)
23 A1=ISR/J*10**-6; //m^2 (cross section area)
24 I1=N2/N1*ISR;//A
25 A2=I1/J*10**-6; //m**2 (cross section area of primary
winding)
26 printf("\n\n cross section of primary winding=%e m
^2",A1)
27 printf("\n cross section of secondary winding=%e m
^2",A2)

```

Scilab code Exa 1.56 auto transformation ratio

```

1 // Ex 56 Page 400
2
3 clc;clear;close;
4 // Given
5 IscBYIf1=4; // as Isc=5*If1
6 ILByIf1=3; // as IL <= 3*If1
7 sf=4; //%
8
9 //IL=K**2*ISC
10 //dividing by If1
11 K=sqrt(ILByIf1/IscBYIf1)*100; //%
12 TstBYTf=(K/100)**2*IscBYIf1*sf/100*100; // % // ratio
of torque
13 printf("Suitable auto transformation ratio = %.1f",K
)

```

```
14 printf("\n Starting torque Tst = %.f percent of full  
-load torque",TstBYTf)
```

Scilab code Exa 1.57 temperature rise

```
1 // Ex 57 Page 401  
2  
3 clc;clear;close;  
4 // Given  
5 theta1=30; //degree C  
6 theta2=45; //degree C  
7 t1=0.5; //hour  
8 t2=1; //hour  
9 theta_m_dashBYthetam=60/100; //temperature rise  
10  
11 //theta=theta_m*(1-e**(-t / alfa ))  
12 //theta1/theta2=(1-%e**(-t1 / alfa ))/(1-%e**(-t2 / alfa ))  
13 ee1=theta2/theta1-1; //let ee1=exp(-1/2/ alfa )  
14 theta_m=theta1/(1-ee1); //degree C  
15 theta_2=theta_m*(1-ee1**4); // degree C (after 2  
hours)  
16 printf("temperature rise after 2 hours full load = %  
.f degree C",theta_2)  
17 alfa=-1/2*log(ee1); //hour  
18 alfa_dash=theta_m_dashBYthetam*alfa; //hour  
19 theta_m_dash=theta_m_dashBYthetam*theta_m  
20 theta_dash=theta_m_dash*(1-%e**(-t2/alfa))  
21 printf("\n temperature rise of cold water after 1  
hour = %.f degree C",theta_dash)
```

Scilab code Exa 1.58 Torque ratio

```

1 // Ex 58 Page 401
2
3 clc;clear;close;
4 // Given
5 zo=2+%i*3; //ohm
6 zi=0.5+%i*5; //ohm
7 Ri=real(zi) ;//ohm
8 Ro=real(zo) ;//ohm
9
10 //at standstill
11 s=1; // at standstill
12 Zo=sqrt(real(zo)**2+imag(zo)**2); //ohm
13 Zi=sqrt(real(zi)**2+imag(zi)**2); //ohm
14 ToBYTi=Ro/Ri*(Zi/Zo)**2; //torque ratio
15 printf("at slip=0, To:Ti = %d:1",ToBYTi)
16
17 //at s=0.5
18 s=0.05; //%
19 Zo=sqrt(real(zo)**2/s**2+imag(zo)**2); //ohm
20 Zi=sqrt(real(zi)**2/s**2+imag(zi)**2); //ohm
21 ToBYTi=Ro/Ri*(Zi/Zo)**2; //torque ratio
22 printf("\n at s=0.05, To:Ti = %.f:10",ToBYTi*10)

```

Scilab code Exa 1.59 Regulation

```

1 // Ex 59 Page 402
2
3 clc;clear;close;
4 // Given
5 u=45; //degree
6 m=3; //no of phases
7
8 //Id=sqrt(2)*Vs*X*(1-cosd(u))*sin(%pi/m)
9 IdBYVs_dash=m/2/%pi*(1-cosd(u))*sin(%pi/m)*sqrt(2);
    //load current/Vs

```

```

10 // where IdBYVs_dash = m/%pi*IdX/2
11 EdoBYVs=sqrt(2)*m/%pi*sin(%pi/m); //dc output voltage
   /Vs with no overlap
12 EduBYVs=EdoBYVs-IdBYVs_dash; //dc output voltage/Vs
   with overlap
13 // part (a)
14 Reg1=(EdoBYVs-EduBYVs)/EdoBYVs*100; //% ( regulation )
15 printf(" part(a) Regulation at no load voltage = %.f
   percent",Reg1)
16 // part (b)
17 Reg2=(EdoBYVs-EduBYVs)/EduBYVs*100; //% ( regulation )
18 printf("\n part(b) Regulation at full load voltage =
   %.f percent",Reg2)

```

Scilab code Exa 1.60 diameter of filament

```

1 // Ex 60 Page 402
2
3 clc;clear;close;
4 // Given
5 d1=0.15*10**-3; //mm
6 l1=150*10**-2; //m
7 i2BYi1=1/4; // current ratio
8 //(d2/d1)**(3/2)=i2BYi1
9 d2=(i2BYi1)**(2/3)*d1*10**6; //um
10 l2=1/2*l1*d1/d2*10**6; //m
11 printf(" length of filament = %.2f m",l2)
12 printf("\n diameter of filament = %.f um",d2)

```

Scilab code Exa 1.61 Potential difference

```

1 // Ex 61 Page 403
2

```

```

3 clc;clear;close;
4 // Given
5 d=5/100; //m
6 S=-4/100; //m
7 Ve=3; //kV
8 theta=45; //degree
9 e=1.6*10**-19; //C
10 m=9.67*10**-31; //kg
11
12 u=sqrt(2*e*Ve*1000/m); //m/s
13 uy=u*sind(theta); //m/s
14 vy=0; //since final velocity =0
15 //vy**2-uy**2=2*ay*S
16 ay=(vy**2-uy**2)/2/S; //m**2/s
17 //ay=e/m*V/d
18 V=ay*m*d/e; //V
19 printf("Potential difference = %.f V",V)

```

Scilab code Exa 1.62 Power dissipated

```

1 // Ex 62 Page 403
2
3 clc;clear;close;
4 // Given
5 R=150; //ohm
6 Vrms=200; //V
7 Rd1=65; //ohm
8 Rd2=140; //ohm
9
10Vm=Vrms/sqrt(2); //V
11//v=Vm*sin(theta)
12Rf=R+Rd1; //ohm
13Rb=R+Rd2; //ohm
14//i_f=v/Rf; //A
15//i_b=v/Rb; //A

```

```

16 Irms=1/2/%pi*(integrate('(sqrt(2)*sin(theta))**2', 'theta', 0, %pi)+integrate('(sqrt(2)/3*sin(theta))**2', 'theta', %pi, 2*pi))
17 Iav=1/2/%pi*(integrate('sqrt(2)*sin(theta)', 'theta', 0, %pi)+integrate('sqrt(2)/3*sin(theta)', 'theta', %pi, 2*pi))
18 printf(" reading of ammeter 1= %.2f A", Irms)
19 printf("\n reading of ammeter 2 = %.2f A", Iav)
20 P=1/2*(Vrms**2/Rf+Vrms**2/Rb); //W
21 printf("\n\n Power taken from the mains = %.1f W", P)
22 Pc=Irms**2*R; //W
23 Pd=P-Pc; //W
24 printf("\n Power dissipated in rectifying device = %d W", Pd)
25 //Answer wrong in the textbook.

```

Scilab code Exa 1.63 Deflection

```

1 // Ex 63 Page 404
2
3 clc; clear; close;
4 // Given
5 R=180; //ohm
6 V=4; //V
7 l=75; //cm
8 vd=.4; //V
9 emf=1.9; //V
10 Rc=850; //ohm
11 sg=17.5; //mm/uA
12 df=2; //mm
13
14
15 I=R/V; //A
16 Rw=vd/I; //ohm
17 Id=df/sg*10**-6; //A

```

```

18 el=1/sq*Rc; //uV
19 printf("error limit = %.1f uV",el)
20 Rw=0.2/l*Rw; //ohm (for 2cm slide wire)
21 dV=I*Rw*1000; //mV
22 r1=emf/I; //ohm
23 r2=r1*22.8/R; //ohm
24 Ig=dV/1000/(Rc+r2); //A
25 d=dV/1000/(Rc+r2)/Id; //mm
26 printf("\n Deflection = %.1f mm",d)

```

Scilab code Exa 1.64 Reading on voltmeter

```

1 // Ex 64 Page 405
2
3 clc;clear;close;
4 // Given
5 // i=0.25+0.25*sin(omega*t)-0.25*sin(2*omega*t)
6 I0=0.25; I1m=0.25; I2m=-0.25; //from above expression
7 Iav=I0; //A
8 R=800; //ohm
9 L=1/1000; //H
10
11 Irms=sqrt(I0**2+(I1m/sqrt(2)**2+(I2m/sqrt(2)**2)));
    //A
12 printf("Reading on hot wire instrument = %.3f A",
    Irms)
13 VR=Irms*R; //V
14 printf("\n Reading on electrostatic voltmeter across
        800 ohm = %d V",VR)
15 //vl_dash=L*di/dt=300*cos(w*t)-400*cos(2*w*t)
16 v11=300; v12=4; //V
17 vl=sqrt((300/sqrt(2))**2+(400/sqrt(2))**2)
18 printf("\n Reading on electrostatic voltmeter across
        1 mH inductor = %d V",vl)

```

Scilab code Exa 1.65 Additional resistance

```
1 // Ex 65 Page 406
2
3 clc;clear;close;
4 // Given
5 C=6*10**-6; //F
6 L=2.5; //H
7 R=300; //ohm
8
9
10 a=R/2/L
11 omega = sqrt(1/L/C-R^2/4/L^2); //rad/s
12 // i=Im*e**(-a*t)*sin(omega*t+fi)
13 // at t=0 sec
14 i0=0; //A
15 vc=10; //V
16 fi=asin(i0); //degree
17 //L*di/dt=vc at t=0
18 Im=poly([0], 'Im')
19 function i=current(t)
20     i=Im*expm(-a*t)*sin(omega*t+fi)
21 endfunction
22 // i=Im*expm(-a*t)*sin(omega*t+fi)
23 LdiBYdt=L*numderivative(current,0)
24 temp = coeff(LdiBYdt)
25 Im=vc/temp(2)
26 Rn=2*sqrt(L/C); //ohm
27 Rad=Rn-R; //ohm
28 printf("Additional resistance required = %d ohm", Rad
)
```

Scilab code Exa 1.66 current after t sec

```
1 // Ex 66 Page 407
2
3 clc;clear;close;
4 // Given
5 f=50; //Hz
6 Vm=500; //V
7 R=20; //ohm
8 L=0.15; //H
9 t=0.03; // sec
10 XL=2*pi*f*L; //ohm
11 Z=R+%i*XL; //ohm
12 Im=Vm/abs(Z); //A
13 fi=atan(XL/R); //degree
14 lambda=L/R; //sec
15 i = Im*sin(314*t-fi)+0.95*e**(-100*t); //A
16 printf("\n current after 0.03 sec is : %0.1f A",i)
17 i2=Im*(0.95*e**(-100*t)); //A
18 printf("\n transient component is : %0.2f A",i2)
```

Scilab code Exa 1.67 Power factor

```
1 // Ex 67 Page 407
2
3 clc;clear;close;
4 // Given
5 //v=350*sin(omega*t)+80*sin(3*omega*t+%pi/3)+40*sin
  (5*omega*t+5*pi/6)
6 V1=350; V3=80; V5=40; //V
7 fi1=0; fi3=60; fi5=150; //degree
8 R=20; //omh
9 L=0.05; //H
10 omega=314; //rad/s
11
```

```

12 X1=omega*L; //ohm
13 Z1=R+%i*X1; //ohm
14 X3=3*omega*L; //ohm
15 Z3=R+%i*X3; //ohm
16 X5=5*omega*L; //ohm
17 Z5=R+%i*X5; //ohm
18 [r1,t1]=polar(Z1);
19 [r3,t3]=polar(Z3);
20 [r5,t5]=polar(Z5);
21 I1m=V1/r1;//A
22 I3m=V3/r3;//A
23 I5m=V5/r5;//A
24 Irms=sqrt(I1m^2/2+I3m^2/2+I5m^2/2); //A
25 Vrms=sqrt(V1^2/2+V3^2/2+V5^2/2); //A
26 printf("\n Irms=%f A\n Vrms=%f V",Irms,Vrms)
27 P=Irms^2*R; //W
28 printf("\n Total Power , P=%f W",P)
29 cosfi=P/Vrms/Irms; //Power factor
30 printf("\n Power factor = %f",cosfi)

```

Scilab code Exa 1.68 Wattmeter reading

```

1 // Ex 68 Page 408
2
3 clc;clear;close;
4 // Given
5 VRY=200*expm(%i*0); //V
6 VYB=200*expm(%i*-120*pi/180); //V
7 VBR=200*expm(%i*120*pi/180); //V
8
9
10 ZA=10*expm(%i*60*pi/180); //ohm
11 ZB=10*expm(%i*0*pi/180); //ohm
12 ZC=10*expm(%i*60*pi/180); //ohm
13

```

```

14 //Phase current
15 IRY=VRY/ZA; //A
16 IYB=VYB/ZB; //A
17 IBR=VBR/ZC; //A
18
19 IR=IRY-IBR; //A
20 PVA=conj(VRY)*IR; //W
21 printf("Wattmeter W1 reading=%f W", real(PVA))
22 IB=IBR-IYB; //A
23 PVB=conj(-VYB)*IB; //W
24 printf("\n Wattmeter W2 reading=%f W or %f kW",
real(PVB), real(PVB)/1000)

```

Scilab code Exa 1.69 Line and Phase Current

```

1 // Ex 69 Page 409
2
3 clc;clear;close;
4 // Given
5 Rab=6; Rbc=8; Rca=4; //ohm
6 Vab=100*expm(%i*0); //V
7 Vbc=100*expm(%i*-120*pi/180); //V
8 Vca=100*expm(%i*120*pi/180); //V
9 Zab=6+%i*8; //ohm
10 Zbc=8+%i*6; //ohm
11 Zca=4-%i*3; //ohm
12
13 //Phase current
14 Iab=Vab/Zab; //A
15 Ibc=Vbc/Zbc; //A
16 Ica=Vca/Zca; //A
17 printf("Phase Current:")
18 [r,t]=polar(Iab)
19 printf("\n Iab=%f angle=%f degree ", r, t*180/pi)
20 [r,t]=polar(Ibc)

```

```

21 printf("\n Ibc=%f angle=%f degree ",r,t*180/pi)
22 [r,t]=polar(Ica)
23 printf("\n Ica=%f angle=%f degree ",r,t*180/pi)
24 //Line current
25 Iaa=Iab-Ica;//A
26 Ibb=Ibc-Iab;//A
27 Icc=Ica-Ibc;//A
28 printf("\n\n Line Current:")
29 [r,t]=polar(Iaa)
30 printf("\n Iaa=%f angle=%f degree ",r,t*180/pi)
31 [r,t]=polar(Ibb)
32 printf("\n Ibb=%f angle=%f degree ",r,t*180/pi)
33 [r,t]=polar(Icc)
34 printf("\n Icc=%f angle=%f degree ",r,t*180/pi)
35 //Power Consumed
36 Wab=abs(Iab)^2*Rab;//W
37 Wbc=abs(Ibc)^2*Rbc;//W
38 Wca=abs(Ica)^2*Rca;//W
39 W=Wab+Wbc+Wca;//W
40 W=W/1000;//kW
41 printf("\n\n Total Power , W=%f kW",W)
42 //Answer wrong for line current in the textbook.

```

Scilab code Exa 1.70 Wattmeter readings

```

1 // Ex 70 Page 410
2
3 clc;clear;close;
4 // Given
5 VRY=300*expm(%i*0); //V
6 VYB=300*expm(%i*-90*pi/180); //V
7 VBR=300*expm(%i*90*pi/180); //V
8
9
10 ZA=10*expm(%i*60*pi/180); //ohm

```

```

11 ZB=10*expm(%i*0*%pi/180); //ohm
12 ZC=10*expm(%i*60*%pi/180); //ohm
13
14 //Phase current
15 IRY=VRY/ZA; //A
16 IYB=VYB/ZB; //A
17 IBR=VBR/ZC; //A
18
19 IR=IRY-IBR; //A
20 PVA=conj(VRY)*IR; //W
21 printf("W1 reading=%f W",real(PVA))
22 IB=IBR-IYB; //A
23 PVB=conj(-VYB)*IB; //W
24 printf("\\n W2 reading=%f W or %.f kW",real(PVB),
real(PVB)/1000)

```

Scilab code Exa 1.71 expression of current

```

1 // Ex 71 Page 411
2
3 clc; clear; close;
4 // Given
5 f=50; //Hz
6 Vm=500; //V
7 R=20; //ohm
8 L=0.2; //H
9 t=0.02; //sec
10 XL=2*%pi*f*L; //ohm
11 Z=R+%i*XL; //ohm
12 Im=Vm/abs(Z); //A
13 fi=atan(XL/R); //degree
14 lambda=L/R; //sec
15 printf("expression for current:")
16 printf("\\n i = %.1f*sin(314*t-%.3f)+0.95*e**(-100*t )
",Im,fi)

```

```

17 i = Im*sin(314*t-fi)+0.95*e**(-100*t); //A
18 printf("\n current after 0.02 sec is : %0.1f A", -i)
19 i2=Im*(0.95*e**(-100*t)); //A
20 printf("\n transient component is : %0.2f A", i2)

```

Scilab code Exa 1.72 Resistance required

```

1 // Ex 72 Page 411
2
3 clc; clear; close;
4 // Given
5 R=200; //ohm
6 L=2; //H
7 C=5*10**-6; //F
8
9
10
11 if R<2*sqrt(L/C) then
12 printf("Since R<2sqrt(L/C), the circuit is
           originally oscillatory .")
13 end
14
15 a=R/(2*L)
16 omega = sqrt(1/L/C-R^2/4/L^2); //rad/s
17 //i=Im*e**(-a*t)*sin(omega*t+fi)
18 //at t=0 sec
19 i0=0; //A
20 vc=10; //V
21 fi=asin(i0); //degree
22 //L*di/dt=vc at t=0
23 Im=poly([0], 'Im')
24 function i=current(t)
25     i=Im*expm(-a*t)*sin(omega*t+fi)
26 endfunction
27 //i=Im*expm(-a*t)*sin(omega*t+fi)

```

```

28 LdiBYdt=L*numderivative(current,0)
29 temp = coeff(LdiBYdt)
30 Im=vc/temp(2)
31 printf("\n\n Expression for current :\n i = %.3f *"
         "exp(-%dt)*sin(%f ft)",Im,a,omega)
32 Rn=2*sqrt(L/C); //ohm
33 Rad=Rn-R; //ohm
34 printf("\n\n Resistance required = %d ohm",Rad)

```

Scilab code Exa 1.73 Reading of electrostatic voltmeter

```

1 // Ex 73 Page 412
2
3 clc;clear;close;
4 // Given
5 // i=0.5+0.3*sin(omega*t)-0.2*sin(2*omega*t)
6 I0=0.5; I1m=0.3; I2m=-0.2; //from above expression
7 Iav=I0; //A
8 R=1000; //ohm
9 L=1/1000; //H
10
11 Irms=sqrt(I0**2+(I1m/sqrt(2)**2+(I2m/sqrt(2)**2)));
    //A
12 printf("Reading of hot wire instrument = %.3f A",
        Irms)
13 VR=Irms*R; //V
14 printf("\n Reading of electrostatic voltmeter across
        1000 ohm = %d V",VR)
15 //vl_dash=L*di/dt=300*cos(w*t)-400*cos(2*w*t)
16 v11=300;v12=4; //V
17 vl=sqrt((300/sqrt(2))**2+(400/sqrt(2))**2)
18 printf("\n Reading of electrostatic voltmeter across
        1 mH inductor = %d V",vl)

```

Scilab code Exa 1.74 Power and Power factor

```
1 // Ex 74 Page 412
2
3 clc;clear;close;
4 // Given
5 //v=350*sin (omega*t)+80*sin (3*omega*t+%pi/3)+40*sin
   (5*omega*t+5*%pi/6)
6 V1=250;V3=50;V5=30;//V
7 fi1=0;fi3=60;fi5=90;//degree
8 R=20;//ohm
9 L=0.05;//H
10 omega=314;//rad/s
11
12 X1=omega*L;//ohm
13 Z1=R+%i*X1;//ohm
14 X3=3*omega*L;//ohm
15 Z3=R+%i*X3;//ohm
16 X5=5*omega*L;//ohm
17 Z5=R+%i*X5;//ohm
18 [r1,t1]=polar(Z1);
19 [r3,t3]=polar(Z3);
20 [r5,t5]=polar(Z5);
21 I1m=V1/r1;//A
22 I3m=V3/r3;//A
23 I5m=V5/r5;//A
24 Irms=sqrt(I1m^2/2+I3m^2/2+I5m^2/2); //A
25 Vrms=sqrt(V1^2/2+V3^2/2+V5^2/2); //A
26 printf("\n Irms=%f A\n Vrms=%f V",Irms,Vrms)
27 P=Irms^2*R;//W
28 printf("\n Total Power , P=%f W",P)
29 cosfi=P/Vrms/Irms;//Power factor
30 printf("\n Power factor = %.2f",cosfi)
```

Scilab code Exa 1.75 carrier power under modulated condition

```
1 // Ex 75 Page 414
2
3 clc;clear;close;
4 // Given
5 Ebb=400;//V
6 Emm=250;//V
7 Ibb=25;//A
8 Po=2.5*10**3;//W
9
10 m=Emm/Ebb;//modulation index
11 Pbb=Ebb*Ibb
12 eta=Po/Pbb*100;//%
13 P=Po*(1+m**2/2);//W
14 Pdo=Pbb-Po;//W
15 Pd=Pdo*(1+m**2/2);//W
16 printf("\n carrier power under modulated condition =\n %.2f kW",P/1000)
17 printf("\n plate circuit efficiency = %.f percent",eta)
18 printf("\n plate dissipation under unmodulated\n condition = %.1f kW",Pdo/1000)
19 printf("\n plate dissipation under modulated\n condition = %.2f kW",Pd/1000)
```

Scilab code Exa 1.76 Resistance and reactance

```
1 // Ex 76 Page 414
2
3 clc;clear;close;
4 // Given
```

```

5  Zo=50; //ohm
6  VSWR=2; // ratio
7  //lm=0.2*lamda
8  lmBYlamda=0.2
9  betaINT0lamda=2*pi
10 rho=(VSWR-1)/(VSWR+1); // reflection coefficient
11 theta=2*betaINT0lamda*lmBYlamda; // radian
12 //exp(j*theta)=cos(theta)+%i*sin(theta)
13 ZL=Zo*(1-rho*(cos(theta)+%i*sin(theta)))/(1+rho*(cos(theta)+%i*sin(theta))); //ohm
14 Rs=real(ZL); //ohm
15 Xs=abs(imag(ZL)); //ohm (capacitive)
16 printf("\n Rs = %0.1 f ohm",Rs)
17 printf("\n Xs = %0.1 f ohm",Xs)
18 YL=(1/ZL)*1000; //mS
19 Rp=1000/real(YL); //ohm
20 Xp=1000/imag(YL); //ohm
21 printf("\n Rp = %0.1 f ohm",Rp)
22 printf("\n Xp = %0.1 f ohm",Xp)

```
