

Scilab Textbook Companion for
A Textbook Of Applied Electronics
by R S Sedha¹

Created by
Akhil
M.teh
Physics
CUSAT
College Teacher
None
Cross-Checked by
None

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: A Textbook Of Applied Electronics

Author: R S Sedha

Publisher: S Chand & Company Ltd. New Delhi

Edition: 3

Year: 2008

ISBN: 8121927838

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
3 Electricity and Ohms Law	5
4 DC Resistive Circuits	28
5 Kirchhoffs Laws and Network Theorems	39
6 A C Fundamentals	47
7 Passive Circuit Elements	51
9 Voltage and Current Sources	55
10 Semiconductors	64
12 PN Junction Diode	81
13 Special Purpose Diodes and Opto Electronic Devices	92
14 Bipolar Junction Transistor	97
15 BJT Characteristics	107
16 Field Effect Transistor	109

17 Thyristors	112
19 Rectifiers and Filters	116
20 Regulated Power Supplies	125
21 Controlled Rectifiers	145
22 BJT Biasing and Stabilization	149
24 Singly Stage BJT Amplifiers	172
25 Hybrid Parameters	186
26 Multistage BJT Amplifiers	200
27 Power Amplifiers	212
28 Tuned Amplifiers	224
29 Feedback Amplifiers	228
30 Field Effect Transistor Amplifiers	240
31 Sinusoidal Oscillators	253
32 Non Sinusoidal Oscillators	266
33 Wave Shaping	271
34 Time Base Circuits	273
35 Operational Amplifiers OP Amps	276
36 Basic Op Amp Applications	287

List of Scilab Codes

Exa 3.1	number of upperclass students who will go to the party	5
Exa 3.2	number of upperclass students who will go to the party	5
Exa 3.3	$A1 \cup A2 \cup A3 \cup A4$	6
Exa 3.4	cars that do not have any options	6
Exa 3.5	Total number of ways to paint 12 offices so that 3 of them	7
Exa 3.6	$A1 \cup A2 \cup A3 \cup A4$	8
Exa 3.7	Number of possible ways in which a house keeper can serve spaghetti dinner three times each week	8
Exa 3.8	Total number of ways	9
Exa 3.9	The probability of getting an even number .	10
Exa 3.10	Total number of ways to paint 12 offices so that 3 of them	11
Exa 3.11	The resistance of silver wire	11
Exa 3.12	Resistance at 800 degree celsius	12
Exa 3.13	Resistance at 80 degree celsius	13
Exa 3.14	Resistance of wire at 200 degree celsius . . .	14
Exa 3.15	The conductance of gold conductor	15
Exa 3.16	The conductance of gold conductor	15
Exa 3.17	The Resistance	16
Exa 3.18	The conductance	16
Exa 3.19	Current in the power line	17
Exa 3.20	The maximum safe voltage	17
Exa 3.21	The voltage that must be applied to the relay coil to energize it	18

Exa 3.22	Resistance that must be inserted into the circuit of each segment	18
Exa 3.23	The value of resistance	19
Exa 3.24	The rate at which electrical energy	20
Exa 3.25	The power consumed by the toaster	20
Exa 3.26	Current through filament	21
Exa 3.27	The energy used	21
Exa 3.28	The energy used	22
Exa 3.29	The input current	23
Exa 3.30	The number of bulbs required	23
Exa 3.31	Power consumed by relay coil	24
Exa 3.32	Power rating	24
Exa 3.33	Resistance of the heating element	25
Exa 3.34	Maximum new current	25
Exa 3.36	Battery will last for	26
Exa 4.1	Total resistance of circuit	28
Exa 4.2	Equivalent Resistance	28
Exa 4.4	Resistance must be added in order to accomplish the reduction in current	29
Exa 4.5	The voltage drop across R1	30
Exa 4.7	The power dissipated by R1	31
Exa 4.8	Power dissipated in the circuit when R3 and R2	31
Exa 4.9	Current through circuit when R2	33
Exa 4.10	Current drawn by R2 branch	34
Exa 4.11	The Equivalent Resistance	34
Exa 4.12	The equivalent resistance	35
Exa 4.14	Current in the circuit	36
Exa 4.15	Power supplied in case of Short across DE	36
Exa 5.1	Value of the current I1	39
Exa 5.2	Value of R	39
Exa 5.3	The value of R	40
Exa 5.4	Value of IB	41
Exa 5.5	Thevenins equivalent Voltage	42
Exa 5.6	Current through load resistance	43
Exa 5.8	The value of R _{th}	44
Exa 5.11	Maximum load resistance	45
Exa 5.12	The value of power transmitted to the receiver	45

Exa 5.13	Load resistance	46
Exa 6.1	Time period by one cycle	47
Exa 6.2	Time period of rectified input	47
Exa 6.3	Frequency and Time period of the sine wave	48
Exa 6.4	Time period	49
Exa 6.5	RMS value	49
Exa 7.4	The coil inductance	51
Exa 7.5	Coefficient of coupling	52
Exa 7.6	d c resistance of coil	52
Exa 7.7	Capacitance of parallel plate capacitor . . .	53
Exa 7.8	Thickness of dielectric	54
Exa 9.1	Voltage drop across internal resistance . . .	55
Exa 9.2	Terminal Voltage	56
Exa 9.3	Variation in terminal voltage	57
Exa 9.4	The internal resistance of the source	59
Exa 9.5	Variation of current from the short circuit current	60
Exa 9.6	Current source value	61
Exa 9.7	Equivalent voltage source	61
Exa 9.8	Equivalent voltage source	62
Exa 10.1	Length of wire	64
Exa 10.3	Mobility of electrons	65
Exa 10.5	Contribution by electron	65
Exa 10.6	Concentration of free electrons	66
Exa 10.7	Intrinsic concentration	67
Exa 10.8	Conductivity of silicon	68
Exa 10.9	Donor concentration	69
Exa 10.10	Electron concentration	70
Exa 10.11	Density of electrons	71
Exa 10.12	Length of the silicon would be	71
Exa 10.13	For n type silicon hole concentration	72
Exa 10.15	Resistivity of doped silicon	73
Exa 10.16	Conductivity of intrinsic silicon	75
Exa 10.17	Coefficient of holes	76
Exa 10.18	Electron mobility	77
Exa 10.19	Number of conduction electrons	77
Exa 10.20	Number of electron carriers	78
Exa 10.21	Mobility of charge carriers	79

Exa 10.22	Value of Hall coefficient	80
Exa 12.1	Current through diode	81
Exa 12.2	Diode current	81
Exa 12.3	Value of n	82
Exa 12.4	Current at 400 k	83
Exa 12.5	Voltage drop across a silicon diode	83
Exa 12.6	Dynamic resistance in forward direction	84
Exa 12.8	Maximum forward current	85
Exa 12.9	Voltage drop across the diode	86
Exa 12.10	Value of VD	86
Exa 12.11	Current through the circuit	87
Exa 12.12	Voltage across the resistor	88
Exa 12.13	Total current through the circuit	88
Exa 12.14	Total current through the circuit	89
Exa 12.15	Output Voltage in case 1	90
Exa 13.1	The value of IZM for the device	92
Exa 13.2	The maximum power dissipation for the device	93
Exa 13.3	Resistance of the zener diode	93
Exa 13.4	Terminal voltage of the zener diode	94
Exa 13.5	Tuning range for the circuit	95
Exa 13.6	Frequency of 5th harmonic	96
Exa 14.1	Base current	97
Exa 14.2	Common Base current gain	97
Exa 14.3	Base current	98
Exa 14.4	IC	99
Exa 14.5	Value of beta when alpha is 0.975	99
Exa 14.6	The value of emitter current	100
Exa 14.7	Collector current	101
Exa 14.8	Base current	102
Exa 14.9	Value of collector current	102
Exa 14.10	Collector current	103
Exa 14.11	Beta of the transistor	104
Exa 14.12	Value of collector current	105
Exa 14.13	Collector current when IB is 0.25 mA	105
Exa 15.1	Maximum power dissipation at 70 degree Celsius	107
Exa 16.4	The value of transconductance	109
Exa 16.6	The value of ID when VGS is 6 V	110

Exa 17.1	Therefore the device will not be destroyed	112
Exa 17.2	Maximum allowable time	113
Exa 17.3	Peak point voltage of the circuit	113
Exa 17.4	Intrinsic stand off ratio	114
Exa 19.2	The value of dc load current	116
Exa 19.3	Average value of load power	117
Exa 19.4	Maximum a c voltage required at the input	118
Exa 19.6	The dc output voltage	118
Exa 19.7	The dc output voltage	119
Exa 19.9	The value of Vdc	120
Exa 19.10	New Value of inductance	121
Exa 19.11	Value of capacitance	122
Exa 19.12	Capacitance	123
Exa 19.13	Ripple factor for 50 Hz supply	124
Exa 20.1	The value of line regulation	125
Exa 20.2	The change in output voltage	126
Exa 20.3	Line regulation	126
Exa 20.4	Full load Voltage	127
Exa 20.5	Change in output voltage	127
Exa 20.6	Load voltage	128
Exa 20.8	Minimum value of load resistance	129
Exa 20.9	Maximum value of zener current	130
Exa 20.10	Maximum value of RS	131
Exa 20.11	Magnitude of regulating resistance should be between	132
Exa 20.12	Minimum value of Zener current	133
Exa 20.13	For safety purpose RS should be 220 ohm	134
Exa 20.14	The minimum value of voltage level at input	135
Exa 20.15	Base current	136
Exa 20.16	Current through Zener	137
Exa 20.17	Maximum value of R	138
Exa 20.18	Value of Resistance R3	140
Exa 20.19	Vout	141
Exa 20.21	Regulated dc output voltage	142
Exa 20.22	Regulated dc output voltage	143
Exa 21.1	Angular firing control when load power P is 25 W	145

Exa 21.4	The value of resistance to limit the average current to 0.5 A	146
Exa 21.5	Chopper duty cycle	147
Exa 21.6	Average value of dc voltage	148
Exa 22.3	The value of base current	149
Exa 22.4	The collector current	150
Exa 22.5	The value of collector current	151
Exa 22.7	VCE of the transistor	152
Exa 22.10	When VBB is 0 V LED	153
Exa 22.11	Collector current	153
Exa 22.13	IB	154
Exa 22.14	In case 1 Collector junction	155
Exa 22.15	The value of R1	156
Exa 22.16	Base resistance	158
Exa 22.17	DC bias current	158
Exa 22.18	Collector current	159
Exa 22.19	Emitter current	161
Exa 22.20	The percentage change in collector current .	162
Exa 22.21	Operating point values	163
Exa 22.22	The value of R1	164
Exa 22.23	Emitter current	165
Exa 22.24	Collector to Emitter VCE	166
Exa 22.28	The value of emitter current	167
Exa 22.30	Base voltage	168
Exa 22.32	The operating point values	169
Exa 24.1	Input resistance looking into the base . . .	172
Exa 24.2	The base current	173
Exa 24.3	Input resistance looking into the base . . .	174
Exa 24.4	Input resistance looking into the base . . .	175
Exa 24.5	a.c output voltage	176
Exa 24.6	The output voltage	178
Exa 24.7	The voltage gain	179
Exa 24.8	Voltage gain	180
Exa 24.9	Av	181
Exa 24.11	Input resistance looking directly into the base	183
Exa 25.1	h ₁₁	186
Exa 25.2	Input resistance of the amplifier stage . . .	187
Exa 25.3	Current gain	188

Exa 25.4	Voltage gain	189
Exa 25.5	Ai	190
Exa 25.6	The value of input resistance	192
Exa 25.7	The value of input resistance of amplified stage	193
Exa 25.8	Input resistance of the stage	194
Exa 25.9	Input impedance	195
Exa 25.10	Input resistance of the circuit	197
Exa 25.11	Value of h _{fb}	198
Exa 25.12	Current gain	198
Exa 26.1	Overall voltage gain	200
Exa 26.2	Overall voltage gain	201
Exa 26.3	Input resistance of first and scond stage . .	202
Exa 26.4	Voltage gain of stage one and two	203
Exa 26.5	Voltage gain of first stage	205
Exa 26.6	Voltage gain of first stage	206
Exa 26.7	Overall voltage gain	208
Exa 26.8	Overall voltage gain	210
Exa 27.2	Overall compliance PP of the amplifier . . .	212
Exa 27.3	Voltage gain	213
Exa 27.4	Collector efficiency	214
Exa 27.5	The a c power output	215
Exa 27.6	Total power within the circuit	215
Exa 27.7	Collector efficiency	216
Exa 27.8	The effective resistance	218
Exa 27.9	Turns ratio	218
Exa 27.10	The maximum power delievered to load . . .	219
Exa 27.11	Maximum undistorted a c output power . . .	219
Exa 27.13	Power delivered to the load	220
Exa 27.14	The power drawn from the source	221
Exa 27.15	Maximum power output	222
Exa 27.16	The d c input power	222
Exa 28.1	The resonant frequency	224
Exa 28.2	Resonant frequency	224
Exa 28.3	Bandwidth of the circuit	225
Exa 28.4	The Q factor	226
Exa 28.5	The Q factor	226
Exa 28.6	The value of circuit impedance at resonance	227

Exa 29.1	The voltage gain of an amplifier with negative feedback	228
Exa 29.2	The percentage of the negative feedback	228
Exa 29.3	The fraction of the output that	229
Exa 29.4	The value of voltage gain without negative feedback	230
Exa 29.5	Value of feedback ratio	230
Exa 29.6	The value of voltage gain without feedback	231
Exa 29.7	The percentage change in closed loop gain	232
Exa 29.8	The value of Av	233
Exa 29.9	Amout of feedback required when BW is 1MHz	233
Exa 29.11	The value of input resistance with feedback	234
Exa 29.14	Voltage gain with feedback	235
Exa 29.15	Voltage gain without feedback	236
Exa 29.16	Voltage gain with feedback	237
Exa 30.1	Value of drain to source voltage	240
Exa 30.3	Value of RS	241
Exa 30.5	Value of RD	242
Exa 30.6	Value of RD	243
Exa 30.7	Value of VGS	244
Exa 30.8	Voltage gain	245
Exa 30.9	Voltage gain	245
Exa 30.10	Input resistance	246
Exa 30.11	Voltage gain	247
Exa 30.12	Voltage gain	248
Exa 30.13	Output voltage	249
Exa 30.17	Voltage gain	249
Exa 30.18	Amplifier voltage gain	250
Exa 30.19	Input resistance	251
Exa 31.1	Inductance	253
Exa 31.2	It will work at frequency of	253
Exa 31.3	Frequency of oscillations	254
Exa 31.4	Frequency of oscillations	255
Exa 31.5	Frequency of oscillations	256
Exa 31.6	Range of capacitance required	256
Exa 31.7	Capacitance required	257
Exa 31.8	Required voltage gain	258
Exa 31.9	Frequency of oscillation	259

Exa 31.10	The range of inductance required	260
Exa 31.11	The oscillation frequency if C2	261
Exa 31.12	Frequency of oscillation	261
Exa 31.13	Series resonant frequency	262
Exa 31.14	Value of drain resistance	263
Exa 31.18	Value of capacaitor C	264
Exa 31.19	Value of the capacitor C	265
Exa 32.2	Frequency of oscillation	266
Exa 32.3	Time period of oscillation	266
Exa 32.4	Value of C1 capacitor	267
Exa 32.8	The pulse width	268
Exa 32.9	Resistance required	269
Exa 32.12	Time period	269
Exa 33.2	Output peak voltage	271
Exa 33.3	The peak value of input voltage	272
Exa 34.1	Frequency of sweep	273
Exa 34.2	Value of R with C	274
Exa 35.1	The common mode rejection ratio	276
Exa 35.2	The common mode gain	277
Exa 35.3	The maximum operating frequency for the amplifier	277
Exa 35.4	The maximum operating frequency for TLO 741	278
Exa 35.5	Maximum allowable input voltage Vin . . .	279
Exa 35.6	The maximum possible output value could be between	279
Exa 35.7	The value of output voltage increases from	280
Exa 35.8	Output voltage of the inverting amplifier . .	281
Exa 35.9	Closed loop gain	282
Exa 35.10	Closed loop gain	283
Exa 35.11	ACL	284
Exa 35.12	Output voltage	285
Exa 35.14	Output voltage	286
Exa 36.1	Capacitance required in the circuit	287
Exa 36.2	Minimum non linear operating frequency . .	288
Exa 36.3	Maximum linear operating frequency	288
Exa 36.4	The frequency of oscillations	289

Chapter 3

Electricity and Ohms Law

Scilab code Exa 3.1 number of upperclass students who will go to the party

```
1 clear//  
2  
3 // Variables  
4  
5 W = 75.0      //Work done (in Joules)  
6 Q = 50.0      //Charge produced (in Coulomb)  
7  
8 // Calculation  
9 V = W/Q      //Voltage between battery terminals (in  
    Volts)  
10  
11 // Result  
12 printf("\n Terminal voltage of a battery is %0.3f  
        V.", V)
```

Scilab code Exa 3.2 number of upperclass students who will go to the party

```
1 clear//
```

```
2
3 // Variables
4
5 V = 1.5      // Voltage (in Volts)
6 E = 7.5      // Energy produced (in Joules)
7
8 // Calculation
9 Q = E/V      // Charge separated ( in Coulomb )
10
11 // Result
12 printf("\n The Amount of charge separated by the
battery is %0.3f C.",Q)
```

Scilab code Exa 3.3

```
1 clear //
2
3 // Variables
4
5 Q = 7.5          // Charge (in Coulomb)
6 t = 0.5          // Time (in minute)
7
8 // Calculation
9
10 t = 0.5 * 60    // Time (in seconds)
11 I= Q/t          // Current (in Ampere)
12
13 // Result
14
15 printf("\n The current in the element is %0.3f A."
,I)
```

Scilab code Exa 3.4 cars that do not have any options

```
1 clear//  
2  
3 //Variables  
4  
5 I = 5 //Current (in Ampere)  
6 Q = 4 * 10**-3 //Charge (in Coulomb)  
7  
8 //Calculation  
9 t = Q/I //time (in seconds)  
10  
11 //Result  
12 printf("\n Time in which the 4 mC of charge flows  
through this element is %0.3f ms.",t * 10**3)
```

Scilab code Exa 3.5 Total number of ways to paint 12 offices so that 3 of them

```
1 clear//  
2  
3 //Variables  
4  
5 I = 0.3 //Current (in Ampere)  
6 W = 9.45 //Heat (in Joules)  
7 t = 5 //Time (in seconds)  
8  
9 //Calculation  
10  
11 Q = I * t  
12 V = W/Q //Voltage (in Volts)  
13  
14 //Result  
15  
16 printf("\n The voltage across filament is %0.3f  
volts.",V)
```

Scilab code Exa 3.6 A1unionA2unionA3unionA4

```
1 clear//  
2  
3 // Variables  
4  
5 p = 2.83 * 10**-8      // Resistivity (in ohm-meter)  
6 w = 0.5                 // width (in meter)  
7 t = 2 * 10**-3          // thickness (in meter)  
8 l = 1                   // length (in meter)  
9  
10 // Calculation  
11  
12 A = w * t              // Area of cross-section (in  
    metersquare)  
13 R = p*l/A               // Resistance (in ohm)  
14  
15 // Result  
16  
17 printf("\n The resistance between left end and right  
    end is %0.3f micro-ohm.",R * 10**6)
```

Scilab code Exa 3.7 Number of possible ways in which a house keeper can serve spaghetti

```
1 clear//  
2  
3 //Case 1:  
4  
5 // Variables  
6  
7 w = 0.01                 // width (in meter)  
8 h = 0.01                 // height (in meter)
```

```

9 l = 0.50           //length (in meter)
10 p = 3.5 * 10**-5 //Resistivity (in ohm-meter)
11
12 //Calculation
13
14 A = w * h         //Area of cross section (in
                     metersquare)
15 R = p*l/A         //Resistance (in ohm)
16
17 //Result 1:
18
19 printf("\n Resistance in case 1 is : %0.3f ohm.",R)
20
21 //Case 2:
22
23 //Variables
24
25 w = 0.50          //width (in meter)
26 h = 0.01          //height (in meter)
27 l = 0.01          //length (in meter)
28
29 //Calculation
30
31 A = w * h         //Area of cross section (in
                     metersquare)
32 R = p*l/A         //Resistance (in ohm-meter)
33
34 //Result
35
36 printf("\n Resistance in case 2 is: %0.3f ohm.",R)

```

Scilab code Exa 3.8 Total number of ways

```
1 clear//
```

```

2
3 // Variables
4
5 l = 120           //length of wire (in meter)
6 d = 0.25 * 10**-2 //Diameter of cross section (
7          in meter)
8 p = 1.7 * 10**-8  // Resistivity (in ohm-meter)
9
10 // Calculation
11 r = d/2          //Radius of cross section (in
12          meter)
13 A = %pi *r*r     //Area of cross section (in
14          metersquare)
15 R = p*l/A        // Resistance (in ohm)
16
17 printf("\n Resistance of the wire is %0.3f ohm.",R
)

```

Scilab code Exa 3.9 The probability of getting an even number

```

1 clear //
2
3 // Variables
4
5 p = 2.8 * 10**-8    // Resistivity (in ohm-meter)
6 d = 0.15 * 10**-2   //Diameter of wire (in meter)
7 R = 10               // Resistance (in ohm)
8
9 // Calculation
10
11 A = %pi *d*d/4     //Area of cross section (in
12          metersquare)

```

```
12 l = R*A/p           //Length of wire (in meter)
13
14 //Result
15
16 printf("\n Length of the wire is %0.0f meter.",l)
```

Scilab code Exa 3.10 Total number of ways to paint 12 offices so that 3 of them

```
1 clear//
2
3 // Variables
4
5 p = 1.7 * 10**-8           // Resistivity (in ohm-
    meter)
6 l = 2 * 150                // Length (in meter)
7 R = 0.722                  // Resistance (in ohm)
8
9 // Calculation
10
11 A = p*l/R                // Area of cross section
    (in metersquare)
12 d = (A * 4 / %pi)**0.5   // diameter of wire (in
    meter)
13
14 //Result
15
16 printf("\n Diameter of the wire is : %0.0f mm.",d
    * 10**3)
```

Scilab code Exa 3.11 The resistance of silver wire

```
1 clear//
2
```

```

3 // Variables
4
5 lc = 200                                //Length of copper wire (
     in meter)
6 Rc = 1.5                                 //Resistance of Copper
     wire(in ohm)
7 pc = 1.7 * 10**-8                         //Resistivity of (in ohm
     -meter)
8 ls = 10                                  //Length of silver wire (
     in meter)
9 ps = 1.6 * 10**-8                         //Resistivity of Silver (
     in ohm-meter)
10
11 // Calculation
12
13 A = pc * lc / Rc                        //Area of cross section (
     in metersquare)
14 Rs = ps * ls / A                         //Resistance of silver
     wire(in ohm)
15
16 // Result
17
18 printf("\n The resistance of silver wire is %0.2f
     ohm.",Rs)

```

Scilab code Exa 3.12 Resistance at 800 degree celsius

```

1 clear //
2
3 // Variables
4
5 T1 = 800                                //
     Temperature (in celsius degeree)
6 T2 = 2250                                //
     Temperature (in celsius degeree)

```

```

7 R20 = 3.49                                //
    Resistance at 20 degree celsius (in ohm)
8 alpha20 = 4.5 * 10**-3                      //
    Temperature coefficient at 20 degree celsius (in
    per degree Celsius)
9
10 //Calculation
11
12 R800 = R20 * (1 + alpha20*(T1 - 20))      //
    Resistance at 800 degree celsius (in ohm)
13 R2250 = R20 * (1 + alpha20*(T2-20))        //
    Resistance at 2250 degree celsius (in ohm)
14
15 //Result
16
17 printf("\n Resistance at 800 degree celsius is %0.1
    f ohm.\n\nResistance at 2250 degree celsius is
    %0.3f",R800,R2250)

```

Scilab code Exa 3.13 Resistance at 80 degree celsius

```

1 clear//
2
3 // Variables
4
5 T1 = 20                                     // Temperature (
    in degree celsius)
6 R1 = 10000                                    // Resistance at
    20 degree celsius (in ohm)
7 T2 = -25                                      // Temperature (
    in degree celsius)
8 alpha = 0.0039                                 // Temperature
    coefficient at 20 degree celsius (in per degree
    Celsius)
9

```

```

10 // Calculation
11
12 R80 = R1*(1 + alpha*(80 - T1)) // Resistance at
     80 degree celsius (in ohm)
13 RT2 = R1*(1 + alpha*(-25 - T1)) // Resistance at
     -25 degree celsius (in ohm)
14
15 // Result
16
17 printf("\n Resistance at 80 degree celsius is %0.1f
          kilo-ohm.\nResistance at -25 degree celsius is
          %0.1f kilo-ohm.", R80*10**-3, RT2*10**-3)

```

Scilab code Exa 3.14 Resistance of wire at 200 degree celsius

```

1 clear//
2
3 // Variables
4
5 p = 14 * 10**-8 // Resistivity of
     gold (in ohm-meter)
6 alpha = 5.8 * 10**-4 // Temperature
     coefficient (in per degree celsius)
7 l = 3 //Length (in meter
     )
8 d = 13 * 10**-6 //diameter of wire
9
10 // Calculation
11
12 A = %pi * d * d / 4 //Area of cross-
     section (in metersquare)
13 R = p * l /A //Resistance of
     wire at 20 degree celsius (in ohm)
14 R1 = R*(1 + alpha*(200-20))
15 // Result

```

```
16
17 printf("\n Resistance of wire at 200 degree celsius
      is %0.1f ohm.",R1)
```

Scilab code Exa 3.15 The conductance of gold conductor

```
1 clear//
2
3 //Variables
4
5 R = 10*10**-3           //Resistance (in ohm)
6
7 //Calculation
8
9 G = 1/R                 //Conductance (in siemens)
10
11 //Result
12
13 printf("\n The conductance of gold conductor is %0
      .3f siemens.",G)
```

Scilab code Exa 3.16 The conductance of gold conductor

```
1 clear//
2
3 //Variables
4
5 R = 10.0*10**3          //Resistance (in ohm)
6
7 //Calculation
8
9 G = 1/R                 //Conductance (in siemens)
10
```

```
11 // Result
12
13 printf("\n The conductance of gold conductor is %0
.3f siemens.",G)
```

Scilab code Exa 3.17 The Resistance

```
1 clear//
2
3 //Variables
4
5 G = 50*10**-6           // Conductance (in siemens)
6
7 // Calculation
8
9 R = 1/G                 // Resistance (in ohm)
10
11 // Result
12
13 printf("\n The Resistance is %0.3f kilo-ohm.",R *
10**-3)
```

Scilab code Exa 3.18 The conductance

```
1 clear//
2
3 //Variables
4
5 V = 18                  // Voltage (in volts)
6 I = 60*10**-6            // current (in Ampere)
7
8 // Calculation
9
```

```
10 R = V/I // Resistance (in ohm)
11 G = 1/R // Conductance (in siemens)
12
13 // Result
14
15 printf("\n The conductance is %0.2f micro-siemens.
", G * 10**6)
```

Scilab code Exa 3.19 Current in the power line

```
1 clear//
2
3 // Variables
4
5 R = 600.00 // Resistance (in ohm)
6 V = 230.00 // Voltage (in volts)
7
8 // Calculation
9
10 I = V/R // Current (in Ampere)
11
12 // Result
13
14 printf("\n Current in the power line is %0.3f A.", I)
```

Scilab code Exa 3.20 The maximum safe voltage

```
1 clear//
2
3 // Variables
4
5 R = 8 // Resistance (in ohm)
```

```
6 I = 2.5 // Current (in Ampere)
7
8 // Calculation
9
10 V = I*R // Voltage (in volts)
11
12 // Result
13
14 printf("\n The maximum safe voltage is %0.3f volts
. ",V)
```

Scilab code Exa 3.21 The voltage that must be applied to the relay coil to energize

```
1 clear //
2
3 // Variables
4
5 R = 1.5 * 10**3 // Resistance (in ohm)
6 I = 16 * 10**-3 // Current (in Ampere)
7
8 // Calculation
9
10 V = I*R // Voltage (in volts)
11
12 // Result
13
14 printf("\n The voltage that must be applied to the
relay coil to energize it is %0.3f volts.",V)
```

Scilab code Exa 3.22 Resistance that must be inserted into the circuit of each seg

```
1 clear //
2
```

```

3 // Variables
4
5 I = 20 * 10**-3           // Current per segment (
    in Ampere)
6 V = 5                      // Voltage (in volts)
7
8 // Calculation
9
10 R = V/I                   // Resistance (in ohm)
11
12 // Result
13
14 printf("\n Resistance that must be inserted into the
        circuit of each segment is %0.3f ohm.",R)

```

Scilab code Exa 3.23 The value of resistance

```

1 clear//
2
3 // Variables
4
5 V = 7 * 2                  // Voltage : 7 div * (2 V/
    div) (in volts)
6 I = 5 * 5 * 10**-3         // Current : 5 div * (5 *
    10**-3) (in Ampere)
7
8 // Calculation
9
10 R = V/I                   // Resistance (in ohm)
11
12 // Result
13
14 printf("\n The value of resistance is %0.3f ohm.",R)

```

Scilab code Exa 3.24 The rate at which electrical energy

```
1 clear//  
2  
3 // Variables  
4  
5 W = 64000           //Heat produced (in  
                      Joules)  
6 t = 40             //time (in seconds)  
7  
8 // Calculation  
9  
10 P = W/t           //Rate at which  
                      electrical energy is converted into heat energy (in watt)  
11  
12 // Result  
13  
14 printf("\n The rate at which electrical energy is  
                      converted into heat energy is : %0.3f W.",P)
```

Scilab code Exa 3.25 The power consumed by the toaster

```
1 clear//  
2  
3 // Variables  
4  
5 I = 5               //Current (in Ampere)  
6 V = 230              //Voltage (in volts)  
7  
8 // Calculation  
9
```

```
10 P = V*I //Power consumed (in watt)
11
12 //Result
13
14 printf("\n The power consumed by the toaster is: %0
.3f watt.",P)
```

Scilab code Exa 3.26 Current through filament

```
1 clear//
2
3 //Variables
4
5 P = 36.0 //Power consumed (in watt)
6 V = 230.0 //Voltage (in volts)
7
8 //Calculation
9
10 I = P/V //Current (in Ampere)
11
12 //Result
13
14 printf("\n Current through filament is %0.3f A.",I
)
```

Scilab code Exa 3.27 The energy used

```
1 clear//
2
3 //Variables
4
5 P = 150 *12/1000.0 //Power consumed by 12
bulbs (in kilowatt)
```

```
6 t = 10.0 //Time (in hours)
7
8 //Calculation
9
10 W = P * t //Energy used (in kWh)
11
12 //Result
13
14 printf("\n The energy used is %0.3f kWh.",W)
```

Scilab code Exa 3.28 The energy used

```
1 clear //
2
3 //Variables
4
5 Ps = 500.0 //Power of stereo
   system (in watt)
6 Pa = 2400.0 //Power of air
   conditioner (in watt)
7 t = 3 //time (in hours)
8
9 //Calculation
10
11 P = (Ps + Pa)/1000 //Total power consumed
   (in kilowatt)
12 W = P * t //Energy used (in
   kilowatthour)
13
14 //Result
15
16 printf("\n The energy used is %0.3f kWh.",W)
```

Scilab code Exa 3.29 The input current

```
1 clear//  
2  
3 // Variables  
4  
5 V = 230.0          //Voltage (in volts)  
6 P = 180.0          //Power (in watt)  
7  
8 // Calculation  
9  
10 I = P/V           //Current (in Ampere)  
11  
12 // Result  
13  
14 printf("\n The input current is %0.3f A.",I)
```

Scilab code Exa 3.30 The number of bulbs required

```
1 clear//  
2  
3 // Variables  
4  
5 V = 24.0           //Voltage (in volts)  
6 I = 2.0            //Current (in Ampere)  
7 Pb = 0.5           //Power rating of each  
                     light bulb (in watt)  
8  
9 // Calculation  
10  
11 P = V * I          //Maximum power (in  
                     watt)  
12 P80 = P * 0.8       //80 percentage of power  
                     rating (in watt)  
13 n = (P80/Pb)        //Number of bulbs
```

```
    required
14
15 // Result
16
17 printf("\n The number of bulbs required is %0.3f ."
       ,n)
```

Scilab code Exa 3.31 Power consumed by relay coil

```
1 clear //
2
3 // Variables
4
5 R = 750.0           // Resistance (in ohm)
6 I = 32.0            // Current (in milliAmpere)
7
8 // Calculation
9
10 P = I**2 * 10**-6 * R // Power (in watt)
11
12 // Result
13
14 printf("\n Power consumed by relay coil is %0.3f
      mW. " ,P*1000)
```

Scilab code Exa 3.32 Power rating

```
1 clear //
2
3 // Variables
4
5 R = 36.0           // Resistance (in ohm)
6 V = 230.0           // Voltage (in volts)
```

```
7
8 // Calculation
9
10 P = V**2/R           //Power (in watt)
11
12 // Result
13
14 printf("\n Power rating is %0.3f kW.",P/1000)
```

Scilab code Exa 3.33 Resistance of the heating element

```
1 clear //
2
3 // Variables
4
5 P = 36           //Power (in watt)
6 V = 230.0        //Voltage (in volts)
7
8 // Calculation
9
10 R = V**2/P      //Resistance (in ohm)
11
12 // Result
13
14 printf("\n Resistance of the heating element is %0
.0f ohm.",R)
```

Scilab code Exa 3.34 Maximum new current

```
1 clear //
2
3 //Case a :
4
```

```

5 // Variables
6
7 R = 8.0           // Resistance (in ohm)
8 P1 = 60.0         //Power (in watt)
9
10 // Calculation
11
12 I1 = (P1/R)**0.5 // Current (in Ampere)
13
14 //Case b :
15
16 // Variables
17
18 R = 8.0           //Resistance (in ohm)
19 P2 = 120.0         //Power (in watt)
20
21 // Calculation
22
23 I2 = (P2/R)**0.5 // Current (in Ampere)
24
25 // Result
26
27 printf("\n Maximum new current is %0.2f A.\ \
    nMaximum new current is %0.2f A.", I1, I2)

```

Scilab code Exa 3.36 Battery will last for

```

1 clear //
2
3 // Variables
4
5 V = 6.0           //voltage (in volts)
6 C = 2.0           //Capacity of battery (in
    Ampere-hour)
7 P = 1.2           //Power rating (in watt)

```

```
8
9 // Calculation
10
11 R = V**2 / P           // Resistance (in ohm)
12 I = V/R                // Current (in Ampere)
13 t = C/I                // time (in hour)
14
15 // Result
16
17 printf("\n Battery will last for %0.3f hours.",t)
```

Chapter 4

DC Resistive Circuits

Scilab code Exa 4.1 Total resistance of circuit

```
1 clear//  
2  
3 // Variables  
4  
5 R1 = 220          // Resistance (in ohm)  
6 R2 = 470          // Resistance (in ohm)  
7 R3 = 560          // Resistance (in ohm)  
8 R4 = 910          // Resistance (in ohm)  
9  
10 // Calculation  
11  
12 R = R1 + R2 + R3 + R4      // Net Resistance (in ohm)  
13  
14 // Result  
15  
16 printf("\n Total resistance of circuit is %0.3f  
          ohm.", R)
```

Scilab code Exa 4.2 Equivalent Resistance

```

1 clear//
2
3 //Variables
4
5 R1 = 4                      //Resistance (in kilo-ohm)
6 R2 = 6                      //Resistance (in kilo-ohm)
7 R3 = 2                      //Resistance (in kilo-ohm)
8
9 //Calculation
10
11 R = R1 + R2 + R3          //Equivalent Resistance (in
    kilo-ohm)
12
13 //Result
14
15 printf("\n Equivalent Resistance is %0.3f kilo-ohm
    ." ,R)

```

Scilab code Exa 4.4 Resistance must be added in order to accomplish the reduction

```

1 clear//
2
3 //Variables
4
5 I = 250 * 10**-3            //Current (in Ampere)
6 R = 1.5 * 10**3             //Resistance (in ohm)
7
8 //Calculation
9
10 Vs = I * R                //Source voltage (in
    volts)
11 I1 = 0.75 * I              //New current (in Ampere
    )
12 R1 = Vs / I1               //New Resistance (in ohm
    )

```

```

13 R2 = R1 - R          // Resistance to be added
    ( in ohm)
14
15 // Result
16
17 printf("\n %0.3f ohm Resistance must be added in
        order to accomplish the reduction in current.",R2
    )

```

Scilab code Exa 4.5 The voltage drop across R1

```

1 clear //
2
3 // Variables
4
5 R1 = 2.2           // Resistance (in kilo-ohm)
6 R2 = 1             // Resistance (in kilo-ohm)
7 R3 = 3.3           // Resistance (in kilo-ohm)
8 V2 = 6             // Voltage drop across R2 (
    in volts)
9
10 // Calculation
11
12 I = V2 / R2       // Current in the circuit (
    in milli-Ampere)
13 V1 = R1 * I         // Voltage drop across R1 (
    in volts)
14 V3 = R3 * I         // Voltage drop across R3 (
    in volts)
15
16 // Result
17 printf("\n The voltage drop across R1 is %0.3f V
        and the voltage drop across R3 is %0.3f V.",V1,
    V3)

```

Scilab code Exa 4.7 The power dissipated by R1

```
1 clear//  
2  
3 // Variables  
4  
5 R2 = 100          // Resistance R2 (in ohm)  
6 I = 0.3           // Current (in Ampere)  
7 VT = 120          // Voltage (in volts)  
8  
9 // Calculation  
10  
11 RT = VT / I     // Total Resistance (in ohm)  
12 R1 = RT - R2    // Resistance R1 (in ohm)  
13 P1 = I**2 * R1   // Power dissipated by R1 (in  
                    watt)  
14 P2 = I**2 * R2   // Power dissipated by R2 (in  
                    watt)  
15  
16 // Result  
17  
18 printf("\n The power dissipated by R1 is %0.3f W.\n"  
        "The power dissipated by R2 is %0.3f W.",P1,P2)
```

Scilab code Exa 4.8 Power dissipated in the circuit when R3 and R2

```
1 clear//  
2  
3 // Variables  
4  
5 V = 6             // Voltage (in volts)  
6 R1 = 1             // Resistance (in ohm)
```

```

7 R2 = 2 // Resistance (in ohm)
8 R3 = 3 // Resistance (in ohm)
9
10 //Case (a):
11
12 // Calculation
13
14 RT = R1 + R2 + R3 // Equivalent Resistance (in
15 ohm)
15 I = V / RT // Current (in Ampere)
16 P = I**2 * RT // Power dissipated (in watt)
17
18 // Result
19
20 printf("\n Power dissipated in the entire circuit is
21 %0.3f W.",P)
22 //Case (b):
23
24 // Calculation
25
26 RT = R1 + R2 // Equivalent Resistance (in
27 ohm)
27 I = V / RT // Current (in Ampere)
28 P = I**2 * RT // Power dissipated (in watt)
29
30 // Result
31
32 printf("\n Power dissipated in the circuit when R2
33 is shortened is %0.3f W.",P)
34 // Case (c):
35
36 // Calculation
37
38 R = R1 // Resistance (in ohm)
39 I = V / R // Current (in Ampere)
40 P = I**2 * R // Power dissipated (in watt)

```

```
41
42 printf("\n Power dissipated in the circuit when R3
        and R2 is shortened is %0.3f W.",P)
```

Scilab code Exa 4.9 Current through circuit when R2

```
1 clear //
2
3 // Variables
4
5 V = 10.0                      //Voltage (in volts)
6 R1 = 10**6                     //Resistance (in ohm)
7 R2 = 10 * 10**3                //Resistance (in ohm)
8
9 //Case (a):
10
11 // Calculation
12
13 RT = R1 + R2                 //Total Resistance (in ohm)
14 I = V / RT                   //Current (in Ampere)
15
16 // Result
17
18 printf("\n Current through the circuit is %0.3f A.
        ",I)
19
20 //Case (b):
21
22 // Calculation
23
24 RT = R1                      //Total Resistance (in ohm)
25 I = V / RT                   //Current (in Ampere)
26
27 // Result
28
```

```
29 printf("\n Current through circuit when R2 is  
shortened is %0.3f A.", I)
```

Scilab code Exa 4.10 Current drawn by R2 branch

```
1 clear//  
2  
3 // Variables  
4  
5 IT = 750          // Current (in milli-Ampere)  
6 I1 = 200          // Current (in milli-Ampere)  
7 I3 = 150          // Current (in milli-Ampere)  
8  
9 // Calculation  
10  
11 I2 = IT - (I1 + I3)    // Current through R2 (in milli  
-Ampere)  
12  
13 // Result  
14  
15 printf("\n Current drawn by R2 branch is %0.3f mA.  
", I2)
```

Scilab code Exa 4.11 The Equivalent Resistance

```
1 clear//  
2  
3 // Variables  
4  
5 V = 12.0          // Voltage (in volts)  
6 R1 = 4.0          // Resistance (in ohm)  
7 R2 = 6.0          // Resistance (in ohm)  
8 R3 = 12.0         // Resistance (in ohm)
```

```

9
10 // Calculation
11
12 Req = 1/(1/R1 + 1/R2 + 1/R3) // Equivalent
   resistance (in ohm)
13 I1 = V/R1
14 I2 = V/R2
15 I3 = V/R3
16
17 // Result
18
19 printf("\n The Equivalent Resistance is %0.3f ohm
      .\nThe Current through R1 , R2 , R3 are %0.3f A
      , %0.3f A, %0.3f A.",Req,I1,I2,I3)

```

Scilab code Exa 4.12 The equivalent resistance

```

1 clear //
2
3 // Variables
4
5 R1=10;R2=10;
6
7 // Calculation
8
9 Req = R1*R2 / (R1 + R2) // Equivalent Resistance (
   in kilo -ohm)
10
11 // Result
12
13 printf("\n The equivalent resistance is %0.3f kilo
      -ohm.",Req)

```

Scilab code Exa 4.14 Current in the circuit

```
1 clear//  
2  
3 // Variables  
4  
5 PR1 = 1.0/8           //1/8 watt resistor (in watt  
6 PR2 = 1.0/4           //1/4 watt resistor (in watt  
7 PR3 = 1.0/2           //1/2 watt resistor (in watt  
8 RT = 2400.0          //total resistance (in ohm)  
9  
10 // Calculation  
11  
12 PT = PR1 + PR2 + PR3 //Total power dissipated (in  
13 watt)  
14 I = (PT/RT)**0.5      //Current (in Ampere)  
15 Vs = I * RT          //Applied voltage (in volts)  
16 R1 = PR1 / I**2       //R1 resistor (in ohm)  
17 R2 = PR2 / I**2       //R2 resistor (in ohm)  
18 R3 = PR3 / I**2       //R3 resistor (in ohm)  
19 // Result  
20  
21 printf("\n Current in the circuit is %0.3f A.\n"  
        "Applied Voltage is %0.3f V.\nValue of R1 is  
        %0.3f ohm.\nValue of R2 is %0.3f ohm.\nValue  
        of R3 is %0.3f ohm.", I, Vs, R1, R2, R3)
```

Scilab code Exa 4.15 Power supplied in case of Short across DE

```
1 clear//  
2
```

```

3 // Variables
4
5 V = 6.0 // Applied
      voltage (in volts)
6 R0 = 0.2 // Resistance
      (in ohm)
7 R1 = 2.0 // Resistance
      (in ohm)
8 R2 = 3.0 // Resistance
      (in ohm)
9 R3 = 6.0 // Resistance
      (in ohm)
10
11 // Calculation
12
13 Req = 1 / (1/R1 + 1/R2 + 1/R3) // Equivalent
      Resistance (in ohm)
14 R = R0 + Req // Total
      Resistance (in ohm)
15 I = V/R // Current (
      in Ampere)
16 V0 = I * R0 // Voltage
      drop across R0 (in volts)
17 Veq = V - V0 // Voltage
      drop across Req (in volts)
18 I1 = Veq / R1 // Current
      through R1 (in Ampere)
19 I2 = Veq / R2 // Current
      through R2 (in Ampere)
20 I3 = Veq / R3 // Current
      through R3 (in Ampere)
21 P = V * I // Power
      supplied by the voltage source (in volts)
22 IO = V/R0 // Current in
      case of 'Short' across DE (in Ampere)
23 P0 = V * IO // Power
      dissipated in case of 'Short' (in watt)
24

```

```
25 // Result
26
27 printf("\n Total Resistance is %0.3f ohm.",R)
28 printf("\n Branch Currents :\nThrough R1 = %0.3f A
          .\nThrough R2 = %0.3f A.\nThrough R3 = %0.3f
          A.",I1,I2,I3)
29 printf("\n Current supplied by voltage source is %0
          .3f A.",I)
30 printf("\n Power supplied by the voltage source is
          %0.3f W.",P)
31 printf("\n Current supplied in case of Short across
          DE is %0.3f A.",I0)
32 printf("\n Power supplied in case of Short across DE
          is %0.3f A.",P0)
```

Chapter 5

Kirchhoffs Laws and Network Theorems

Scilab code Exa 5.1 Value of the current I1

```
1 clear//  
2  
3 //Variables  
4  
5 IT = 20           //Total current (in milli-Ampere)  
6 I2 = 4            //Current (in milli-Ampere)  
7  
8 //Calculation  
9  
10 I1 = IT - I2    //Current (in milli-Ampere)  
11  
12 //Result  
13  
14 printf("\n Value of the current I1 is %0.3f mA.",  
        I1)
```

Scilab code Exa 5.2 Value of R

```
1 clear//  
2  
3 // Variables  
4  
5 I = 1           // Current (in Ampere)  
6  
7 // Calculation  
8  
9 // Applying Kirchoff's voltage law:  
10 // (1 * 3) + (1 * R) + (1 * 4) - 12 = 0  
11  
12 R = 5          // Resistance (in ohm)  
13  
14 // Result  
15  
16 printf("\n Value of R is %0.3f ohm.", R)
```

Scilab code Exa 5.3 The value of R

```
1 clear//  
2  
3 // Variables  
4  
5 Vs = 100        // Source Voltage (in volts)  
6 I = 5           // Current entering the circuit (in  
7             Ampere)  
8 IL = 5          // Current leaving the circuit (in  
9             Ampere)  
10 R15 = 15         // Resistor of 15 ohm (in ohm)  
11 V15 = 30         // Voltage across 15 ohm resistor (in  
12             ohm)  
13  
14 // Calculation
```

```

12
13 I1 = V15 / R15      // Current through 15 ohm resistor
   (in Ampere)
14 IA = I + I1         // Current entering junction A (in
   Ampere)
15 // Applying Kirchoff's current law
16 I2 = I + I1         // Current through 5 ohm resistor (in
   Ampere)
17 IB = I2             // Current entering juction B (in
   Ampere)
18 IR = IA - IL        // Current through R (in Ampere)
19 // Applying Kirchoff's voltage law
20 // (7 * 5) + (2 *R) - 100 + 30 =0
21 R = 35.0/2
22
23 // Result
24
25 printf("\n The value of R is %0.3f ohm.",R)

```

Scilab code Exa 5.4 Value of IB

```

1 clear //
2
3 // Variables
4
5 V = 25           // Source voltage (in volts)
6 RB = 99          // Resistance (in kilo-ohm)
7 RC = 2           // Resistance (in kilo-ohm)
8 RE = 1           // Resistance (in kilo-ohm)
9 VCE = 5          // Voltage across C and E (in volts)
10
11 // Calculation
12
13 // Applying Kirchoff's Voltage law:
14 // IB*RB + VBE + IE*RE -V = 0

```

```

15 //IB*RB + VBE + (IB + IC)*RE - VCC = 0
16 //100*IB + IC = 24
17 //IB + 3*IC = 20
18 IC = 1976.0/299
19 IB = 20 - (3 * 6.61)
20
21 //Result
22
23 printf("\n Value of IB is %0.3f mA.\nValue of IC
           is %0.3f mA.", IB, IC)

```

Scilab code Exa 5.5 Thevenins equivalent Voltage

```

1 clear //
2
3 //Variables
4
5 VS1 = 5           //Voltage source 1 (in volts)
6 VS2 = 3           //Voltage source 2 (in volts)
7 V6 = 0            //Voltage drop across 6 ohm
                    resistor when AB is open (in volts)
8 R1 = 6            //Resistor (in ohm)
9 R2 = 4            //Resistor (in ohm)
10
11 //Calculation
12
13 I = 5.0/4        //Current through 4 ohm resistor
                    (in Ampere)
14 V = I * R2       //Voltage drop across 4 ohm
                    Resistor (in volts)
15 VOC = VS2 + V6 + V //Open circuit voltage (in volts)
16 Rth = R1
17
18 //Result
19

```

```
20 printf("\n Thevenins equivalent Voltage is %0.3f V  
.\n Thevenins equivalent resistance is %0.3f ohm  
. ",VOC,Rth)
```

Scilab code Exa 5.6 Current through load resistance

```
1 clear//  
2  
3 // Variables  
4  
5 V = 25.0 // Source  
    voltage (in volts)  
6 R1 = 100.0 //  
    Resistance (in ohm)  
7 R2 = 75.0 //  
    Resistance (in ohm)  
8 R3 = 50.0 //  
    Resistance (in ohm)  
9 R4 = 25.0 //  
    Resistance (in ohm)  
10 RL = 250.0 //Load  
    resistance (in ohm)  
11  
12 // Calculation  
13  
14 I = V / (R1 + R2 + R3) // Series  
    current (in Ampere)  
15 VR2 = I * R2 // Voltage  
    drop across R2  
16 VOC = VR2 //Open  
    circuit voltage (in volts)  
17 Vth = VOC //Thevenin's  
    equivalent voltage (in volts)  
18 Rth = R4 + R2*(R1 + R3)/(R1 + R2 + R3) //Thevenin's  
    equivalent resistance (in ohm)
```

```
19 IL = Vth/(Rth + RL)
20
21 // Result
22
23 printf("\n Thevenins equivalent voltage is %0.3f V
. and resistance in %0.3f ohm.",Vth,Rth)
24 printf("\n Current through load resistance is %0.3f
A.",IL)
```

Scilab code Exa 5.8 The value of Rth

```
1 clear //
2
3 // Variables
4
5 R1 = 0.6 // Resistance (in ohm)
6 R2 = 0.6 // Resistance (in ohm)
7 R3 = 0.8 // Resistance (in ohm)
8 R4 = 0.8 // Resistance (in ohm)
9
10 // Calculation
11
12 Rth = R3 + R4*(R1 + R2)/(R4 + (R1 + R2)) // Thevenin's resistance (in ohm)
13
14 // Result
15
16 printf("\n The value of Rth is %0.3f ohm.",Rth)
```

Scilab code Exa 5.11 Maximum load resistance

```
1 clear//  
2  
3 // Variables  
4  
5 Vth = 100 //Thevenin Voltage ( in micro-volts )  
6 Rth = 50 //Thevenin Resistance ( in ohm )  
7  
8 // Calculation  
9  
10 RL = Rth //Maximum Load Resistance ( in ohm )  
11 PL = (Vth/(Rth + RL))**2 *RL //Maximum load power ( in pico-watt )  
12  
13 // Result  
14 printf("\n Maximum load resistance is %0.3f ohm.\nMaximum load power is %0.3f pW.",RL,PL)
```

Scilab code Exa 5.12 The value of power transmitted to the receiver

```
1 clear//  
2  
3 // Variables  
4  
5 VTH = 20.0 * 10**-3 //Thevenin's Voltage ( in volts )  
6 RTH = 300.0 //Thevenin's Resistance ( in ohm )  
7 RL = 300.0 //Load Resistance ( in ohm )  
8
```

```
9 // Calculation
10
11 PL = (VTH/(RTH + RL))**2 * RL      // Power across load
     resistance (in watt)
12
13 // Result
14
15 printf("\n The value of power transmitted to the
     receiver is %0.2f micro-watt.",PL*10**6)
```

Scilab code Exa 5.13 Load resistance

```
1 clear //
2
3 // Variables
4
5 R1 = 5.0                      // resistance (in ohm)
6 R2 = 2.0                      // resistance (in ohm)
7 R3 = 3.0                      // resistance (in ohm)
8
9 // Calculation
10
11 Req = R2 * R3 / (R2 + R3)    // Equivalent resistance
     (in ohm)
12 RL = R1 + Req
13
14 // Result
15
16 printf("\n Load resistance is %0.3f ohm.",RL)
```

Chapter 6

A C Fundamentals

Scilab code Exa 6.1 Time period by one cycle

```
1 clear//  
2  
3 // Variables  
4  
5 t = 1.0          //time (in milliseconds)  
6 n = 10.0         //number of cycles  
7  
8 // Calculation  
9  
10 T = t/n        //Time period (in milliseconds)  
11  
12 // Result  
13  
14 printf("\n Time period by one cycle is %0.3f ms.",  
T)
```

Scilab code Exa 6.2 Time period of rectified input

```

1 clear//
2
3 //Variables
4
5 t = 0.01           //Time period of positive half
cycle (in seconds)
6
7 //Calculation
8
9 t1 = 0.01           //Time period of negative half
cycle (in seconds)
10 T = t + t1        //Time period of one complete
cycle (in seconds)
11
12 //Result
13
14 printf("\n Time period of rectified input is %0.3f
s.",T)

```

Scilab code Exa 6.3 Frequency and Time period of the sine wave

```

1 clear//
2
3 //Variables
4
5 n = 5.0             //number of cycles
6 t = 10.0            //time period (in micro-
seconds)
7
8 //Calculation
9
10 f = n / t          //frequency (in Mega-hertz)
11 T = 1/f             //Time period (in micro-
seconds)
12

```

```
13 // Result
14
15 printf("\n Frequency and Time period of the sine
           wave is %0.3f MHz and %0.3f micro-seconds.",f
           ,T)
```

Scilab code Exa 6.4 Time period

```
1 clear //
2
3 // Variables
4
5 f = 69.0                      //frequency (in Mega-hertz)
6
7 // Calculation
8
9 T = 1/f                        //Time period (in micro-
           seconds)
10
11 // Result
12
13 printf("\n Time period is %0.2f ns.",T * 10**3)
```

Scilab code Exa 6.5 RMS value

```
1 clear //
2
3 // Variables
4
5 Vmax = 20.0                     //Voltage (in millivolts)
6
7 // Calculation
8
```

```
9 Vrms = 0.707 * Vmax      //Rms Voltage (in milli-volts
    )
10 Vdc = 0.637 * Vmax      //Average value of signal (in
    milli-volts)
11
12 // Result
13
14 printf("\n RMS value is %0.3f mV.\nAverage value
    is %0.3f mV.", Vrms, Vdc)
```

Chapter 7

Passive Circuit Elements

Scilab code Exa 7.4 The coil inductance

```
1 clear//  
2  
3 // Variables  
4  
5 N = 150.0          //Number of turns  
6 mur = 3540.0       // Relative  
    permeability (in H/m)  
7 mu0 = 4*%pi * 10 **-7      // Absoulte permeability  
    (in H/m)  
8 l = 0.05           // coil length (in  
    meter)  
9 A = 5 * 10**-4      // Area of cross -  
    section (in metersquare)  
10  
11 // Calculation  
12  
13 L = (mur * mu0 * A * N**2)/l      // Coil inductance (  
    in Henry)  
14  
15 // Result  
16
```

```
17 printf("\n The coil inductance is %0.2f Henry.",L)
```

Scilab code Exa 7.5 Coefficient of coupling

```
1 clear//  
2  
3 //Variables  
4  
5 L1 = 40.0 //Inductance (in  
    micro-Henry)  
6 L2 = 80.0 //Inductance (in  
    micro-Henry)  
7 M = 11.3 //Mutual Inductance (  
    in micro-Henry)  
8  
9 //Calculation  
10  
11 k = M/(L1 * L2)**0.5 //Coefficient of  
    Coupling  
12  
13 //Result  
14  
15 printf("\n Coefficient of coupling is %0.2f .",k)
```

Scilab code Exa 7.6 d c resistance of coil

```
1 clear//  
2  
3 //Variables  
4  
5 Q = 90.0 //Q-factor  
6 L = 15.0 * 10**-6 //Inductance (in Henry)  
7 f = 10.0 * 10**6 //Frequency (in Hertz)
```

```

8
9 // Calculation
10
11 Ro = 2*%pi*f*L/Q      //d.c. resistance (in ohm)
12
13 // Result
14
15 printf("\n d.c. resistance of coil is %0.1f ohm.", Ro)

```

Scilab code Exa 7.7 Capacitance of parallel plate capacitor

```

1 clear //
2
3 // Variables
4
5 k = 5.0           // dielectric constant
6 A = 0.04          // Plate area (in meter-
    square)
7 d = 0.02          // Thickness of dielectric (
    in meter)
8 eps0 = 8.85 * 10**-12 // Absolute permittivity (
    in kg*m**3*s**-3*A**-2)
9
10 // Calculation
11
12 C = eps0 * k * A / d // Capacitance (in Farad)
13
14 // Result
15
16 printf("\n Capacitance of parallel plate capacitor
    is %0.3f pF.", C * 10**12)

```

Scilab code Exa 7.8 Thickness of dielectric

```
1 clear//  
2  
3 // Variables  
4  
5 k = 1200.0 // dielectric constant  
6 A = 0.2 //Plate area (in meter-  
square)  
7 eps0 = 8.85 * 10**-12 // Absolute permittivity  
// (in kg*m**3*s**-3*A**-2)  
8 C = 0.428 // Capacitance (in micro  
-farad)  
9  
10 // Calculation  
11  
12 d = eps0 * k * A / C // thickness of  
dielectric (in meter)  
13  
14 // Result  
15  
16 printf("\n Thickness of dielectric is %0.2f mm.", d  
* 10**9)
```

Chapter 9

Voltage and Current Sources

Scilab code Exa 9.1 Voltage drop across internal resistance

```
1 clear//  
2  
3 // Variables  
4  
5 V = 1.5 //Source Voltage (in  
    volts)  
6 RS = 0.2 //Resistance (in ohm)  
7 RL = 1 //Load Resistance (in  
    ohm)  
8  
9 // Calculation  
10  
11 RT = RS + RL //Total Resistance (in  
    ohm)  
12 I = V / RT //Current (in Ampere)  
13 VAB = I * RL //Voltage drop across AB  
    (in volts)  
14 VR = V - VAB //Voltage drop due to  
    internal resistance (in volts)  
15  
16 // Result
```

```
17
18 printf("\n Voltage drop across internal resistance
      is %0.3f volts.",VR)
```

Scilab code Exa 9.2 Terminal Voltage

```
1 clear//
2
3 // Variables
4
5 VS = 1.5                                //Source Voltage (in
     volts)
6 RS = 0.4                                //Resistance (in ohm)
7 RL = 2.0                                //Load Resistance (in
     ohm)
8
9 // Calculation
10
11 RT = RS + RL                           //Total Resistance (in
     ohm)
12 I = VS/ RT                             //Current (in Ampere)
13 VT = I * RL                            //Terminal Voltage (in
     volts)
14 PL = I**2 * RL                          //Power dissipated by
     load resistor (in watt)
15 PS = I**2 * RT                          //Power Supplied by the
     voltage source (in watt)
16 eff = PL / PS                           //Efficiency of the
     circuit
17
18 // Result
19
20 printf("\n Terminal Voltage is %0.3f V.\nPower
      dissipated by 2 ohm resistor is %0.2f W.\n
      Efficiency of the circuit is %0.2f .",VT,PL,eff)
```

)

Scilab code Exa 9.3 Variation in terminal voltage

```
1 clear//  
2  
3 //Case a.1:  
4  
5 //Variables  
6 VT = 1.25  
7 VS = 6.0 //Source Voltage (in  
8 RS = 2.0 //Resistance (in ohm)  
9 //When RL is 2 ohm  
10 RL = 2.0 //Load Resistance (in  
ohm)  
11  
12 //Calculation  
13  
14 RT = RS + RL //Total Resistance (in  
ohm)  
15 I = VS / RT //Current in the Circuit  
(in Ampere)  
16 VT1 = I * RL //Terminal Voltage (in  
volts)  
17  
18 //Result  
19  
20 printf("\n Terminal voltage when RL is 2 ohm : %0.3  
f V.",VT1)  
21  
22 //Case a.2:  
23  
24 //Variables  
25
```

```

26 //When RL is 20 ohm
27 RL = 20.0                                //Load Resistance (in
                                              ohm)
28
29 // Calculation
30
31 RT = RS + RL                            //Total Resistance (in
                                              ohm)
32 I = VS / RT                             //Current in the Circuit
                                              (in Ampere)
33 VT2 = I * RL                            //Terminal Voltage (in
                                              volts)
34
35 // Result
36
37 printf("\n Terminal voltage when RL is 20 ohm : %0
          .2f V.",VT)
38 printf("\n Variation in terminal voltage is %0.3f
          V.",(VT2-VT1)/VT2)
39
40 //Case b.1:
41
42 // Variables
43
44 RS = 100.0                                //Resistance (in ohm)
45 //When RL is 10 kilo -ohm
46 RL = 10.0 * 10**3                         //Load Resistance (in
                                              ohm)
47
48 // Calculation
49
50 RT = RS + RL                            //Total Resistance (in
                                              ohm)
51 I = VS / RT                             //Current in the
                                              circuit (in Ampere)
52 VT = I * RL                            //Terminal Voltage (in
                                              volts)
53

```

```

54 // Result
55
56 printf("\n Terminal voltage when RL is 100 kilo-ohm
      is : %0.2f V.", VT)
57
58 // Case b.2:
59
60 // Variables
61
62 // When RL is 100 kilo-ohm
63 RL = 100.0 * 10**3           // Load Resistance (in
                                ohm)
64
65 // Calculation
66
67 RT = RS + RL               // Total Resistance (in
                                ohm)
68 I = VS / RT                // Current in the
                                circuit (in Ampere)
69 VT1 = I * RL                // Terminal Voltage (in
                                volts)
70
71 // Result
72
73 printf("\n Terminal voltage when RL is 100 kilo-ohm
      is : %0.3f V.", VT1)
74 printf("\n Variation in terminal voltage is %0.3f
      V.", (VT1 - VT) / VT1)

```

Scilab code Exa 9.4 The internal resistance of the source

```

1 clear //
2
3 // Variables
4

```

```

5 VS = 12.0 //Source Voltage (in
               volts)
6 VT = 10.0 //Terminal Voltage (in
               volts)
7 RL = 10.0 //Load resistance (in
               ohm)
8
9 // Calculation
10
11 RS = RL*(VS / VT - 1) //Internal Resistance (
                           in ohm)
12
13 // Result
14
15 printf("\n The internal resistance of the source is
           %0.3f ohm.",RS)

```

Scilab code Exa 9.5 Variation of current from the short circuit current

```

1 clear //
2
3 // Variables
4
5 IS = 30.0 //Current (in milli-Ampere)
6 RS = 15.0 //Source resistance (in
             kilo-ohm)
7
8 // Calculation
9
10 RL = RS / 20.0 //Load Resistance (in kilo-
                     ohm)
11 IL = IS * RS/(RL +RS) //Load Current (in Ampere)
12
13
14 // Result

```

```
15
16 printf("\n Largest value of load resistance to
      provide constant current is %0.3f ohm.",RL
      *10***3)
17 printf("\n Variation of current from the short-
      circuit current is %0.4f .", (IS-IL)/IS)
```

Scilab code Exa 9.6 Current source value

```
1 clear //
2
3 //Variables
4
5 VS = 12.0          //Source Voltage (in
      volts)
6 RS = 3.0          //Source resistance (in
      ohm)
7
8 //Calculation
9
10 IS = VS / RS     //Source current (in
      Ampere)
11
12 //Result
13
14 printf("\n Current source value is %0.3f A.",IS)
```

Scilab code Exa 9.7 Equivalent voltage source

```
1 clear //
2
3 //Variables
4
```

```

5 IS = 5.0                      //Source current (in
                                milli-Ampere)
6 RS = 2.0                      //Source resistance (in
                                kilo-ohm)
7
8 //Calculation
9
10 VS = IS * RS                //Voltage source (in
                                volts)
11
12 //Result
13
14 printf("\n Equivalent voltage source is %0.3f V.", VS)

```

Scilab code Exa 9.8 Equivalent volage source

```

1 clear//
2
3 //Variables
4
5 IS =1.5                      //Source current (in milli-
                                Ampere)
6 RS = 2                         //Source resistance (in kilo-
                                -ohm)
7
8 //Calculation
9
10 RL = 10*40/(10+40)           //Load Reistance (in kilo-
                                ohm)
11 IL = IS * RS/(RL +RS)         //Load current (in milli-
                                Ampere)
12 IL2 = IL * 10/(10 +40)        //Current through part 2 (in
                                milli-Ampere)
13 VS = IS * RS                 //Souce voltage (in volts)

```

```
14
15 // Result
16
17 printf("\n current through 40 kilo-ohm resistor is
18 %0.3f mA.", IL2)
19 printf("\n Equivalent voltage source is %0.3f V.",
```

Chapter 10

Semiconductors

Scilab code Exa 10.1 Length of wire

```
1 clear//  
2  
3 // Variables  
4  
5 R = 1000.0 //Resistance (in  
    ohm)  
6 sig = 5.8 * 10**7 //Conductivity  
    in (Siemen per meter)  
7 d = 10**-3 //diameter (in  
    meter)  
8 E = 10 * 10**-3 //Eletric field  
    (in Volt per meter)  
9  
10 //Calculation  
11  
12 l = R *sig * %pi * d**2 /4 //length (in meter)  
13 J = sig * E //Current  
    density (in Ampere per metersquare)  
14  
15 //Result  
16
```

```
17 printf("\n Length of wire is %0.2f km.\nCurrent  
desity is %0.3f A/(m*m) .",1/1000,J)
```

Scilab code Exa 10.3 Mobility of electrons

```
1 clear//  
2  
3 //Variables  
4  
5 n = 5.8 * 10**28           //number of free  
    electrons (in per cubic-meter)  
6 p = 1.54 * 10**-8          //resistivity (in  
    ohm-meter)  
7 q = 1.6 * 10**-19          //charge (in  
    Coulomb)  
8 m = 9.1 * 10**-31          //mass of electron  
    (in kg)  
9  
10 //Calculation  
11  
12 sig = 1/p                //conductivity (in  
    siemen per meter)  
13 mu = sig /(q * n)         //mobility (in  
    meter-square/volt-second)  
14 t = mu * m / q            //time (in second)  
15  
16 //Result  
17  
18 printf("\n Mobility of electrons is %0.6f m**2/V-s  
.\\nRelaxation time is %0.6f ps.",mu,t*10**12)
```

Scilab code Exa 10.5 Contribution by electron

```

1 clear//
2
3 //Variables
4
5 ni = 1.41 * 10**16           //intrinsic
   concentration (in per cubic-metre)
6 un = 0.145                   //mobility of
   electrons in germanium (in metre-square/volt-
   second)
7 up = 0.05                     //mobility of
   holes in germanium (in metre-square/volt-second)
8 q = 1.6 * 10**-19            //charge of
   electron (in Coulomb)
9
10 //Calculation
11
12 sig = q * ni * (un + up)    //Conductivity
   of germanium (in siemen per metre)
13
14 //Result
15
16 printf("\n Intrinsic conductivity of silicon is %0
   .3f S/m.",sig)
17 printf("\n Contribution by electron is %0.3f S/m."
   ,q*ni*un)
18 printf("\n Contribution by hole is %0.3f S/m."
   ,q*ni*up)

```

Scilab code Exa 10.6 Concentration of free electrons

```

1 clear//
2
3 //Variables
4
5 l = 0.2 * 10**-3             //length (in

```

```

        meter)
6 A = 0.04 * 10**-6                                //Area of cross
          section (in square-meter)
7 V = 1                                              //Voltage (in
          volts)
8 I = 8 * 10**-3                                    //current (in
          Ampere)
9 un = 0.13                                         //mobility of
          electron (in m**2 per volt-second)
10 q = 1.6 * 10**-19                                 //charge on
          electron (in Coulomb)
11
12 // Calculation
13
14
15 R = V/I                                         //Resistance (
          in ohm)
16 p = R * A/l                                     //Resistivity (
          in ohm-meter)
17 sig = 1/p                                       //Conductivity
          (in siemen per meter)
18 n = sig / (q * un)                               //concentration
          (in per cubic-meter)
19 J = I/A                                         //current
          density (in Ampere per square-meter)
20 v = J/(n*q)
21
22 // Result
23
24 printf("\n Concentration of free electrons is %e m
          **-3.\nDrift velocity is %0.3f m/s.",n,v)

```

Scilab code Exa 10.7 Intrinsic concentration

```
1 clear//
```

```

2
3 // Variables
4
5 p = 0.47                                // Resistivity (in
   ohm-meter)
6 q = 1.6 * 10**-19                         // charge on
   electron (in Coulomb)
7 un = 0.39                                 // mobility of
   electron in germanium (in m**2 per volt-second)
8 up = 0.19                                  // mobility of hole
   in germanium (in m**2 per volt-second)
9
10 // Calculation
11
12 sig = 1/p                                 // Conductivity (in
   siemen per meter)
13 ni = sig / (q *(un +up))                  // intrinsic
   concentration (in per cubic-meter)
14
15 // Result
16
17 printf("\n Intrinsic concentration is %0.3f m**-3.
   ",ni)

```

Scilab code Exa 10.8 Conductivity of silicon

```

1 clear //
2
3 // Variables
4
5 ND = 10**21                                // Donor concentration (
   in per cubic-meter)
6 NA = 5 * 10**20                             // Acceptor concentration
   (in per cubic-meter)
7 un = 0.18                                   // mobility of electron

```

```

    in silicon (in m**2 per volt-second)
8 q = 1.6 * 10**-19           //charge on electron (in
                               Coulomb)
9
10
11 // Calculation
12
13 n = ND -NA                //net donor density (in
                               per cubic-meter)
14 sig = n * q * un          //Conductivity (in
                               Siemen per meter)
15
16 // Result
17
18 printf("\n Conductivity of silicon is %0.3f (ohm-
meter)**-1.",sig)

```

Scilab code Exa 10.9 Donor concentration

```

1 clear //
2
3 // Variables
4
5 p = 100.0                  // resistivity (in ohm-meter)
6 q = 1.6 * 10**-19          // Charge on a electron (in
                               Coulomb)
7 un = 0.36                   // donor concentration (in per
                               cubic-meter)
8
9 // Calculation
10
11 sig = 1/p                  // conductivity (in siemen per
                               meter)
12 n = sig /(q * un)          // intrinsic concentration (in
                               per cubic-meter)

```

```

13 ND = n                      //Donor concentration (in per
                                cubic-meter)
14
15 //Result
16
17 printf("\n Donor concentration is %0.3f m**-3." ,ND
        )

```

Scilab code Exa 10.10 Electron concentration

```

1 clear//
2
3 // Variables
4
5 ND = 2 * 10**14              //Donor atom
                                concentration (in atoms per cubic-centimeter)
6 NA = 3 * 10**14              //Acceptor atom
                                concentration (in atoms per cubic-centimeter)
7 ni = 2.3 * 10**19            //intrinsic
                                concentration (in atoms per cubic-centimeter)
8
9 // Calculation
10
11 n = ni**2 / NA              //concentration
                                of electrons (in electrons per cubic-centimeter)
12 p = ni**2 / ND              //concentration
                                of holes (in holes per cubic-centimeter)
13
14 // Result
15
16 printf("\n Electron concentration is %0.3f
          electrons/cm**3.\nHole concentration is %0.3f
          holes/cm**3." ,n ,p)

```

Scilab code Exa 10.11 Density of electrons

```
1 clear//  
2  
3 // Variables  
4  
5 ND = 5 * 10**8          //Donor atom  
    concentration (in atoms per cubic-centimeter)  
6 NA = 6 * 10**16         //Acceptor atom  
    concentration (in atoms per cubic-centimeter)  
7 ni = 1.5 * 10**10        //intrinsic  
    concentration (in atoms per cubic-centimeter)  
8  
9 // Calculation  
10  
11 n = ni**2/NA           //number of  
    electrons (in per cubic-centimeter)  
12 p = ni**2/ND            //number of  
    holes (in per cubic-centimeter)  
13  
14 // Result  
15  
16 printf("\n Density of electrons is %0.3f cm**-3.\n"  
    "nDensity of holes is %0.3f cm**-3.",n,p)
```

Scilab code Exa 10.12 Length of the silicon would be

```
1 clear//  
2  
3 // Variables  
4  
5 d = 0.001                //diameter (in meter)
```

```

6 ND = 10**20           //Number of
                         phosphorus ions (in per cubic-meter)
7 R = 1000              //Resistance (in ohm)
8 un = 0.1               //mobility (in meter-
                         square per volt-second)
9 q = 1.6 * 10**-19      //charge on electron
                         (in Coulomb)
10
11 // Calculation
12
13 n = ND               //Number of free
                         electron (in per cubic-meter)
14 sig = q*n*un          //conductivity (in
                         Siemen per meter)
15 A = %pi * d**2 / 4     //Area of cross section (
                         in meter-square)
16 l = R * sig * A        //length (in meter)
17
18 // Result
19
20 printf("\n Length of the silicon would be %0.3f mm
. ",l*1000)

```

Scilab code Exa 10.13 For n type silicon hole concentration

```

1 clear//
2
3 // Variables
4
5 q = 1.6 * 10**-19      //Charge on electron (
                         in Coulomb)
6 sig = 100.0             //Conductivity of Ge (
                         in per ohm-centimeter)
7 sig1 = 0.1               //Conductivity of Si (
                         in per ohm-centimeter)

```

```

8 ni = 1.5 * 10**10           //intrinsic
    conductivity for Si (in per cubic-centimeter)
9 un = 3800.0                  //mobility of electrons
    for Ge (in square-centimetermeter per volt-
    second)
10 up = 1800.0                 //mobility of holes for
    Ge (in square-centimeter per volt-second)
11 un1 = 1300.0                //mobility of electrons
    for Si (in square-centimetermeter per volt-
    second)
12 up1 = 500.0                 //mobility of holes for
    Si (in square-centimeter per volt-second)
13 ni1 = 2.5 * 10**13          //intrinsic
    concentration for Ge (in per cubic-centimeter)
14
15 // Calculation
16
17 p = sig / (q * up)          //Concentration of p-
    type germanium (in cubic-centimeter)
18 n = ni1**2 / p              //Concentration of
    electrons in germanium (in cubic-centimeter)
19 n1 = sig1 / (q * un1)        //Concentration of N-
    type silicon (in cubic-centimeter)
20 p1 = ni1**2 / n1            //Concentration of
    holes in silicon (in cubic-centimere)
21
22 // Result
23
24 printf("\n For p-type germanium , hole concentration
    is %0.3f /cm**3.\nFor p-type germanium , electron
    concentration is %0.3f /cm**3.",p,n)
25 printf("\n For n-type silicon , hole concentration is
    %0.3f /cm**3.\nFor n-type silicon , electron
    concentration is %0.3f /cm**3.",p1,n1)

```

Scilab code Exa 10.15 Resistivity of doped silicon

```
1 clear//  
2  
3 // Variables  
4  
5 un = 1350 // mobility of  
    electrons (in centimeter-square per volt-second)  
6 up = 480 // mobility of  
    holes (in centimeter-square per volt-second)  
7 ni = 1.52 * 10**10 // intrinsic  
    concentration (in per cubic-centimeter)  
8 Nsi = 4.96 * 10**22 //  
    concentration of silicon (in per cubic-centimeter  
)  
9 q = 1.6 * 10**-19 // charge on  
    electron (in Coulomb)  
10  
11 // Calculation  
12  
13 sigi = q * ni * (un + up) // conductivity  
    of intrinsic silicon (in per ohm-centimeter)  
14 ND = Nsi/(50 * 10**6) // Number of  
    donor atoms (per cubic-centimeter)  
15 n = ND // Number of  
    free electrons (in per cubic-centimeter)  
16 p = ni**2/n // number of  
    holes (in per cubic-centimeter)  
17 sig = q * n * un // conductivity  
    of doped silicon (in per ohm-centimeter)  
18 p = 1/sig // resistivity  
    (in ohm-centimeter)  
19  
20 // Result  
21  
22 printf("\n Resistivity of doped silicon is %0.2f  
    ohm-cm.", p)
```

Scilab code Exa 10.16 Conductivity of intrinsic silicon

```
1 clear//Variables
2
3 up = 0.048 //hole mobility (in
    meter-square per volt-second)
4 un = 0.135 //electron mobility
    (in meter-square per volt-second)
5 q = 1.602 * 10**-19 //charge on electron
    (in Coulomb)
6 Nsi1 = 5 * 10**28 //concentration of
    intrinsic silicon (in atoms per cubic-meter)
7 ni = 1.5 * 10**16 //number of electron
    -hole pairs (per cubic-meter)
8 alpha = 0.05 //temperature
    coefficient (in per degree Celsius)
9 dT = 14 //change in
    temperature (in degree celsius)
10
11 //Calculation
12
13 sig1 = q * ni * (un + up) //conductivity of
    intrinsic silicon (in per ohm-meter)
14 NA = Nsi1/10**7 //Number of indium
    atoms (in per cubic-meter)
15 p = NA //Number of holes (
    in per cubic meter)
16 n = ni**2/p //Number of free
    electrons (in per cubic-meter)
17 sig2 = q * p * up //Conductivity of
    doped silicon (in per ohm-meter)
18 sig34 = sig1*(1 + alpha * dT) //Conductivity at 34
    degree Celsius (in per ohm-meter)
19
```

```

20 // Result
21
22 printf("\n Conductivity of intrinsic silicon is %0
.5f per ohm-meter.\nConductivity of doped
Silicon is %0.2f per ohm-meter.\nConductivity
of silicon at 34 degree Celsius is %0.5f per
ohm-meter.",sig1,sig2,sig34)

```

Scilab code Exa 10.17 Coefficient of holes

```

1 clear//
2
3 // Variables
4
5 un = 3600.0 * 10**-4           // mobility of
   electrons (in meter-square per volt-second)
6 up = 1700.0 * 10**-4           // mobility of holes
   (in meter-square per volt-second)
7 k = 1.38 * 10**23             // Boltzmann
   constant
8 T = 300.0                      // Temperature (in
   kelvin)
9
10 // Calculation
11
12 VT = T/11600                  // Voltage (in volts
   )
13 Dp = up * VT                  // Coefficient of
   holes (in meter-square per second)
14 Dn = un * VT                  // Coefficient of
   electrons (in meter-square per second)
15
16 // Result
17
18 printf("\n Coefficient of holes is %0.6f m**2/s.\n"

```

```
nCoefficient of electrons is %0.4f m**2/s." ,Dp ,  
Dn)
```

Scilab code Exa 10.18 Electron mobility

```
1 clear//  
2  
3 // Variables  
4  
5 RH = 160 // Hall coefficient (in  
cubic-centimeter per Coulomb)  
6 p = 0.16 // Resistivity (in ohm-  
centimeter)  
7  
8 // Calculation  
9  
10 sig = 1/p // Conductivity (in per ohm-  
centimeter)  
11 un = sig * RH // Electron mobility (in  
centimeter-square per volt-second)  
12  
13 // Result  
14  
15 printf("\n Electron mobility is %0.3f cm**2/V-s." ,  
un)
```

Scilab code Exa 10.19 Number of conduction electrons

```
1 clear//  
2  
3 // Variables  
4  
5 I = 50 // Current (in Ampere)
```

```

6 B = 1.2 //Magnetic field (in Weber
            per meter-square)
7 t = 0.5 * 10**-3 //thickness (in meter)
8 VH = 100 //Hall voltage (in volts)
9 q = 1.6 * 10**-19 //Charge on electron (in
                      Coulomb)
10
11 // Calculation
12
13 n = B * I / (VH * q * t) //number of conduction
                           electrons (in per cubic-meter)
14
15 // Result
16
17 printf("\n Number of conduction electrons is %0.3f
           m**-3.", n)

```

Scilab code Exa 10.20 Number of electron carriers

```

1 clear //
2
3 // Variables
4
5 p = 20 * 10**-2 // Resistivity (in ohm-
                    meter)
6 u = 100 * 10**-4 // mobility (in meter-
                     square per volt-second)
7 q = 1.6 * 10**-19 // charge on
                      electron (in Coulomb)
8
9 // Calculation
10
11 sig = 1/p //Conductivity (in per
              ohm-meter)
12 n = sig / (q * u) //number of electron

```

```

    carriers (in per cubic-meter)
13
14 // Result
15
16 printf("\n Number of electron carriers is %0.1f m
        **-3.", n)

```

Scilab code Exa 10.21 Mobility of charge carriers

```

1 clear //
2
3 // Variables
4
5 RH = 3.66 *10**-4                      // Hall
       coefficient (in cubic-meter per Coulomb)
6 p = 8.93 * 10 **-3                       // Resistivity (in
       ohm-meter)
7 q = 1.6 * 10**-19                        // Charge on
       electron (in Coulomb)
8
9 // Calculation
10
11 sig = 1/p                                // Conductivity (
       in per ohm-meter)
12 u = sig * RH                             // mobility (in
       meter-square per volt-second)
13 n = 1 / (RH * q)                          // Density of
       charge carriers (in per cubic-meter)
14
15 // Result
16
17 printf("\n Mobility of charge carriers is %0.3f m
        **2/V-s.\nDensity of charge carriers is %0.3f m
        **-3.", u, n)

```

Scilab code Exa 10.22 Value of Hall coefficient

```
1 clear//  
2  
3 // Variables  
4  
5 p = 9 * 10**-3           // Resistivity (in ohm-meter  
6 up = 0.03                 // Mobility (in meter-square  
    per volt-second)  
7  
8 // Calculation  
9  
10 sig = 1/p                // Conductivity (in per ohm-  
    meter)  
11 RH = up / sig             // Hall coefficient (in  
    cubic-meter per Coulomb)  
12  
13 // Result  
14  
15 printf("\n Value of Hall-coefficient is %0.3f m  
    **3/C.", RH)
```

Chapter 12

PN Junction Diode

Scilab code Exa 12.1 Current through diode

```
1 clear//  
2  
3 // Variables  
4  
5 IO = 2 * 10**-7          //Current (in Ampere)  
6 VF = 0.1                  //Forward voltage (in  
    volts)  
7  
8 // Calculation  
9  
10 I = IO * (exp(40*VF)-1) // Current through diode  
    (in Ampere)  
11  
12 // Result  
13  
14 printf("\n Current through diode is %0.2f micro-  
    Ampere.", I*10**6)
```

Scilab code Exa 12.2 Diode current

```

1 clear//
2
3 //Variables
4
5 VF = 0.22                                //Forward voltage (in
     volts)
6 T = 298.0                                 //Temperature (in
      kelvin)
7 I0 = 10**-3                               //Current (in Ampere)
8 n = 1
9
10 //Calculation
11
12 VT = T/11600                             //Volt equivalent of
      temperature (in volts)
13 I = I0*(exp(VF/(n*VT))-1)                //Diode Current (in
      Ampere)
14
15 //Result
16
17 printf("\n Diode current is %0.1f A.",I)

```

Scilab code Exa 12.3 Value of n

```

1 clear//
2
3 //Variables
4
5 I1 = 0.5 * 10**-3                         //Diode current1 (in
      Ampere)
6 V1 = 340 * 10**-3                          //Voltage1 (in volts)
7 I2 = 15 * 10**-3                           //Diode current2 (in
      Ampere)
8 V2 = 440 * 10**-3                          //Voltage2 (in volts)
9

```

```
10 // Calculation
11
12 n = 4/log(30)           //By solving both the
   given equations
13
14 // Result
15
16 printf("\n Value of n is %0.2f .",n)
```

Scilab code Exa 12.4 Current at 400 k

```
1 clear //
2
3 // Variables
4
5 I300 = 10 * 10**-6          // Current at 300
   kelvin (in Ampere)
6 T1 = 300                   // Temperature (in
   kelvin)
7 T2 = 400                   // Temperature (in
   kelvin)
8
9 // Calculation
10
11 I400 = I300 * 2**((T2-T1)/10) // Current at 400
   kelvin (in Ampere)
12
13 // Result
14
15 printf("\n Current at 400 k is %0.1f mA.", I400
   *10**3)
```

Scilab code Exa 12.5 Voltage drop across a silicon diode

```

1 clear//
2
3 //Variables
4
5 rb = 2           //bulk resistance (in ohm)
6 IF = 12 * 10**-3 //Forward current (in Ampere)
7
8 //Calculation
9
10 VF = 0.6 + IF * rb //Voltage drop (in volts)
11
12 //Result
13
14 printf("\n Voltage drop across a silicon diode is
%0.3f V.",VF)

```

Scilab code Exa 12.6 Dynamic resistance in forward direction

```

1 clear//
2
3 //Variables
4
5 T = 398.0          //Temperature (in
kelvin)
6 IO = 30 * 10**-6    //Reverse saturation
current (in Ampere)
7 V = 0.2            //Voltage (in volts)
8
9 //Calculation
10
11 VT = T/11600       //Volt equivalent of
temperature (in volts)
12 I = IO * (exp(V/VT)-1) //Diode current (in
Ampere)
13 rac = VT/IO * exp(-V/VT) //dynamic resistance in

```

```

        forward direction (in ohm)
14 rac1 = VT/I0 * exp(V/VT)      //dynamic resistance in
        reverse direction (in ohm)
15
16 // Result
17
18 printf("\n Dynamic resistance in forward direction
        is %0.2f ohm.\nDynamic resistance in backward
        direction is %0.3f Mega-ohm.",rac,rac1/10**6)

```

Scilab code Exa 12.8 Maximum forward current

```

1 clear //
2
3 //Variables
4
5 PDmax = 0.5          //power dissipation (in
        watt)
6 VF = 1                //Forward voltage (in volts
        )
7 VBR = 150             //Breakdown voltage (in
        volts)
8
9 //Calculation
10
11 IFmax = PDmax/VF      //Maximum forward current (
        in Ampere)
12 IR = PDmax/VBR        //Breakdown current that
        burns out the diode (in Ampere)
13
14 //Result
15
16 printf("\n Maximum forward current is %0.3f A.\\
        nBreakdown current that burns out the diode is
        %0.2f mA.",IFmax,IR*10**3)

```

Scilab code Exa 12.9 Voltage drop across the diode

```
1 clear//  
2  
3 //Variables  
4  
5 R = 330 //Resistance (in ohm)  
6 VS = 5 //Source voltage (in volts  
 )  
7  
8 //Calculation  
9  
10 VD = VS //Voltage drop across  
diode (in volts)  
11 VR = 0 //Voltage drop across the  
resistance (in volts)  
12 I = 0 //Current through circuit  
13  
14 //Result  
15  
16 printf("\n Voltage drop across the diode is %0.3f  
V.\nVoltage drop across the resistance is %0.3f  
V.\nCurrent through the circuit is %0.3f A.",  
VD,VR,I)
```

Scilab code Exa 12.10 Value of VD

```
1 clear//  
2  
3 //Variables  
4
```

```

5 VS = 12.0                                //Source coltage (in
    volts)
6 R = 470.0                                 //Resistance (in ohm)
7
8 // Calculation
9
10 VD = 0                                    //Voltage drop across
    diode (in volts)
11 VR = VS                                   //Value of VR (in volts)
12 I = VS/R                                  //Current (in Ampere)
13
14 // Result
15
16 printf("\n Value of VD is %0.3f V.\nValue of VR is
    %0.3f V.\nCurrent through the circuit is %0.2
    f mA.", VD, VR, I*10**3)

```

Scilab code Exa 12.11 Current through the circuit

```

1 clear//
2
3 // Variables
4
5 VS = 6                                     //Source voltage (in volts)
6 R1 = 330                                    //Resistance (in ohm)
7 R2 = 470                                    //Resistance (in ohm)
8 VD = 0.7                                    //Diode voltage (in volts)
9
10 // Calculation
11
12 RT = R1 + R2                             //Total Resistance (in ohm)
13 I = (VS - 0.7)/RT                         //Current through the diode
14
15 // Result
16

```

```
17 printf("\n Current through the circuit is %0.3f mA  
.", I * 10**3)
```

Scilab code Exa 12.12 Voltage across the resistor

```
1 clear//  
2  
3 // Variables  
4  
5 VS = 5 //Source voltage (in volts)  
6 R = 510 //Resistance (in ohm)  
7 VF = 0.7 //Forward voltage drop (in  
volts)  
8  
9 // Calculation  
10  
11 VR = VS - VF //Net voltage (in volts)  
12 I = VR / R //Current through the diode  
13  
14 // Result  
15  
16 printf("\n Voltage across the resistor is %0.3f V  
.\\nThe circuit current is %0.2f mA.", VR, I  
*10**3)
```

Scilab code Exa 12.13 Total current through the circuit

```
1 clear//  
2  
3 // Variables  
4  
5 VS = 6 //Source voltage (in  
volts)
```

```

6 VD1=0.7;VD2=0.7;
7 R = 1.5 * 10**3 // Resistance (in ohm)
8
9 // Calculation
10
11 I = (VS - VD1 - VD2)/R // Current (in Ampere)
12
13 // Result
14
15 printf("\n Total current through the circuit is %0
.3f mA.",I * 10**3)

```

Scilab code Exa 12.14 Total current through the circuit

```

1 clear//
2
3 // Variables
4
5 VS = 12 //Source voltage (
    in volts)
6 R1 = 1.5 * 10**3 //Resistance (in
    ohm)
7 R2 = 1.8 * 10**3 //Resistance (in
    ohm)
8 VD1=0.7;VD2=0.7;
9
10 // Calculation
11
12 RT = R1 + R2 //Total Resistance
    (in ohm)
13 I = (VS - VD1 - VD2)/RT //Current (in
    Ampere)
14
15 // Result
16

```

```
17 printf("\n Total current through the circuit is %0
.3f mA.", I * 10**3)
```

Scilab code Exa 12.15 Output Voltage in case 1

```
1 clear //
2
3 // Variables
4
5 R = 3.3 * 10**3           // Resitance (in ohm)
6
7 // Calculation
8
9 // Case (a)
10
11 V11=0; V21=0;
12 V01 = 0                  // Output Voltage (in
    volts)
13
14 // Case (b)
15
16 V21 = 0                  // Voltage (in volts)
17 V22 = 5                  // Voltage (in volts)
18 V02 = V22 - 0.7          // Output voltage (in
    volts)
19
20 // Case (c)
21
22 V31 = 5                  // Voltage (in volts)
23 V32 = 0                  // Voltages (in volts)
24 V03 = V31 - 0.7          // Output voltage (in
    volts)
25
26 // Case (d)
27
```

```
28 V41=5;V42=5;
29 V04 = V41 - 0.7           //Output voltage (in
                           volts)
30
31 // Result
32
33 printf("\n Output Voltage in case 1 is %0.3f V.\nOutput
          Voltage in case 2 is %0.3f V.\nOutput
          Voltage in case 3 is %0.3f V.\nOutput Voltage
          in case 4 is %0.3f V.",V01,V02,V03,V04)
```

Chapter 13

Special Purpose Diodes and Opto Electronic Devices

Scilab code Exa 13.1 THe value of IZM for the device

```
1 clear//  
2  
3 // Variables  
4  
5 PZM = 500 //Power rating of  
       zener diode (in milli-watt)  
6 VZ = 6.8 //Zener voltage  
       rating (in volts)  
7  
8 // Calculation  
9  
10 IZM = PZM / VZ //Maximum value of  
       zener current (in milli-Ampere)  
11  
12 // Result  
13  
14 printf("\n THe value of IZM for the device is %0.1f  
mA.", IZM)
```

Scilab code Exa 13.2 The maximum power dissipation for the device

```
1 clear//  
2  
3 // Variables  
4  
5 PZM = 500                                //Power rating  
      of zener diode (in milli-watt)  
6 df = 3.33                                 //derating  
      factor (in milli-watt)  
7 T1 = 75                                    //Temperature  
      (in degree Celsius)  
8 T2 = 50                                     //Temperature  
      (in degree Celsius)  
9  
10 // Calculation  
11  
12 Tdf = df * (T1 - T2)                      //Total  
      derating factor (in milli-watt)  
13 PZ = PZM - Tdf                            //Maximum  
      power dissipating for the device (in milli-watt)  
14  
15 // Result  
16  
17 printf("\n The maximum power dissipation for the  
device is %0.3f mW." ,PZ)
```

Scilab code Exa 13.3 Resistance of the zener diode

```
1 clear//  
2  
3 // Variables
```

```

4
5 IZ1 = 20                                // Reverse current (in
     milli-Ampere)
6 IZ2 = 30                                // Reverse current (in
     milli-Ampere)
7 VZ1 = 5.6                                 // Zener voltage (in
     volts)
8 VZ2 = 5.65                               // Zener voltage (in
     volts)
9
10 // Calculation
11
12 dIZ = IZ2 - IZ1                         // Change in reverse
     current (in milli-Ampere)
13 dVZ = VZ2 - VZ1                         // Change in zener
     voltage (in volts)
14 rZ = dVZ / (dIZ * 10**-3)                // Resistance of
     device (in ohm)
15
16 // Result
17
18 printf("\n Resistance of the zener diode is %0.3f
     ohm.",rZ)

```

Scilab code Exa 13.4 Terminal voltage of the zener diode

```

1 clear //
2
3 // Variables
4
5 VZ = 4.7                                  // Zener voltage (
     in volts)
6 rZ = 15                                    // Resistance (in
     ohm)
7 IZ = 20 * 10**-3                          // Current (in

```

```

        Ampere)
8
9 // Calculation
10
11 VZ1 = VZ + IZ * rZ           // Terminal voltage
   of a zener diode (in volts)
12
13 // Result
14
15 printf("\n Terminal voltage of the zener diode is
   %0.3f V.",VZ1)

```

Scilab code Exa 13.5 Tuning range for the circuit

```

1 clear //
2
3 // Variables
4
5 C1min=5;C2min=5;Cmin=5;
6 C1max=50;C2max=50;Cmax=50;
7 L = 10                         //
   Inductance (in milli-Henry)
8
9 // Calculation
10
11 CTmin = C1min * C2min / (C1min + C2min)      //
   Total minimum capacitance (in pico-farad)
12 CTmin = CTmin * 10**-12                      //
   Total minimum capacitance (in farad)
13 L = 10 * 10**-3                            //
   Inductance (in Henry)
14 f0max = 1/(2*pi*(L*CTmin)**0.5)            //
   Maximum resonant frequency (in Hertz)
15 CTmax = C1max * C2max / (C1max + C2max)      //
   Total maximum capacitance (in pico-farad)

```

```

16 CTmax = CTmax * 10**-12 //  

    Total minimum capacitance (in farad)  

17 f0min = 1/(2*pi*(L*CTmax)**0.5) //  

    Minimum resonant frequency (in Hertz)  

18  

19 // Result  

20  

21 printf("\n Tuning range for the circuit is between  

    %0.0f kHz and %0.0f MHz.", f0min*10**-3, f0max  

    *10**-6)

```

Scilab code Exa 13.6 Frequency of 5th harmonic

```

1 clear//  

2  

3 // Variables  

4  

5 T = 0.04 * 10**-6 //Time period  

    (in seconds)  

6  

7 // Calculation  

8  

9 f = 1/T //Frequency ( in Hertz)  

10 f = f * 10**-6 //Frequency ( in Mega-Hertz)  

11 f5 = 5 * f //%th -  

    harmonic (in Mega-Hertz)  

12  

13 // Result  

14  

15 printf("\n Frequency of 5th harmonic is %0.3f MHz.  

    ", f5)

```

Chapter 14

Bipolar Junction Transistor

Scilab code Exa 14.1 Base current

```
1 clear//  
2  
3 // Variables  
4  
5 IE = 10                      // Emitter current (in  
       milli-Ampere)  
6 IC = 9.8                       // Collector current (in  
       milli-Ampere)  
7  
8 // Calculation  
9  
10 IB = IE - IC                 // Base current (in milli  
      -Ampere)  
11  
12 // Result  
13  
14 printf("\n Base current is %0.3f mA.", IB)
```

Scilab code Exa 14.2 Common Base current gain

```

1 clear//
2
3 //Variables
4
5 IE = 6.28                      //Emitter current (in
       milli-Ampere)
6 IC = 6.20                       //Collector current (
       in milli-Ampere)
7
8 //Calculation
9
10 alpha = IC / IE                //Common base current
      gain
11
12 //Result
13
14 printf("\n Common-Base current gain is %0.3f .",alpha)

```

Scilab code Exa 14.3 Base current

```

1 clear//
2
3 //Variables
4
5 alpha = 0.967                   //common base current
      gain
6 IE = 10                         //Emitter current (in
      milli-Ampere)
7
8 //Calculation
9
10 IC = alpha * IE                //Collector current (
      in milli-Ampere)
11 IB = IE - IC                  //Base current (in

```

```
    milli-Ampere)
12
13 // Result
14
15 printf("\n Base current is %0.3f mA." ,IB)
```

Scilab code Exa 14.4 IC

```
1 clear//
2
3 // Variables
4
5 IE = 10                      // Emitter current (in
       milli-Ampere)
6 alpha = 0.987                  // common base current
       gain
7
8 // Calculation
9
10 IC = alpha * IE              // Collector current (
      in milli-Ampere)
11 IB = IE - IC                // Base current (in
      milli-Ampere)
12
13 // Result
14
15 printf("\n IC is %0.3f mA.\nIB is %0.3f mA." ,IC ,
       IB)
```

Scilab code Exa 14.5 Value of beta when alpha is 0.975

```
1 clear//
2
```

```

3 // Variables
4
5 alpha1 = 0.975           //common base
   current gain
6 beta1 = 200.0            //common emitter
   current gain
7
8 // Calculation
9
10 beta = alpha1 / (1-alpha1) //common emitter
   current gain
11 alpha = beta1 / (beta1 + 1) //common base
   current gain
12
13 // Result
14
15 printf("\n Value of beta when alpha = 0.975 is %0.3
f .\nValue of alpha when beta = 200 is %0.3f .",
beta ,alpha)

```

Scilab code Exa 14.6 The value of emitter current

```

1 clear //
2
3 // Variables
4
5 beta = 100.0           //common emitter
   current gain
6 IC = 40.0               //Collector current (
   in milli-Ampere)
7
8 // Calculation
9
10 IB = IC / beta         //Base current (in
   milli-Ampere)

```

```

11 IE = IB + IC           //Emitter current (in
                           milli-Ampere)
12
13 //Result
14
15 printf("\n The value of emitter current is %0.3f
mA.",IE)

```

Scilab code Exa 14.7 Collector current

```

1 clear//
2
3 //Variables
4
5 beta = 150.0           //common emitter
                           current gain
6 IE = 10                //Emitter current (in
                           milli-Ampere)
7
8 //Calculation
9
10 alpha = beta / (beta + 1) //common base current
                           gain
11 IC = alpha * IE         //Collector current (
                           in milli-Ampere)
12 IB = IE - IC           //Base current (in
                           milli-Ampere)
13
14 //Result
15
16 printf("\n Collector current is %0.2f mA.\nBase
current is %0.2f mA.",IC,IB)

```

Scilab code Exa 14.8 Base current

```
1 clear//  
2  
3 // Variables  
4  
5 beta = 170.0          //common emitter  
    current gain  
6 IC = 80.0             //Collector current (in  
    in milli-Ampere)  
7  
8 // Calculation  
9  
10 IB = IC / beta       //Base current (in  
    milli-Ampere)  
11 IE = IB + IC         //Emitter current (in  
    milli-Ampere)  
12  
13 // Result  
14  
15 printf("\n Base current is %0.2f mA.\n Emitter  
    current is %0.2f mA.", IB, IE)
```

Scilab code Exa 14.9 Value of collector current

```
1 clear//  
2  
3 // Variables  
4  
5 IB = 0.125            //Base current (in  
    milli-Ampere)  
6 beta = 200.0           //common emitter  
    current gain  
7  
8 // Calculation
```

```

9
10 IC = IB * beta // Collector current
   (in milli-Ampere)
11 IE = IC + IB // Emitter current (
   in milli-Ampere)
12
13 // Result
14
15 printf("\n Value of collector current is %0.3f mA
   .\nValue of emitter current is %0.3f mA.",IC,IE
)

```

Scilab code Exa 14.10 Collector current

```

1 clear//
2
3 // Variables
4
5 IE = 12.0 // Emitter current (
   in milli-Ampere)
6 beta = 140.0 //common emitter
   current gain
7
8 // Calculation
9
10 IB = IE / (1 + beta) //Base current (in
   milli-Ampere)
11 IC = IE - IB // Collector current
   (in milli-Ampere)
12
13 // Result
14
15 printf("\n Collector current is %0.3f mA.\nBase
   current is %0.3f mA.",IC,IB)

```

Scilab code Exa 14.11 Beta of the transistor

```
1 clear//  
2  
3 // Variables  
4  
5 IB = 105 * 10**-3 //Base current (in  
milli-Ampere)  
6 IC = 2.05 //Collector  
current (in milli-Ampere)  
7  
8 //Calculation  
9  
10 beta = IC / IB //Common base  
current gain  
11 alpha = beta / (1 + beta) //Common emitter  
current gain  
12 IE = IB + IC //Emitter current  
(in milli-Ampere)  
13 IC1 = IC + 0.65 //New collector  
current (in milli-Ampere)  
14 IB1 = IB + 27 * 10**-3 //New base current  
(in milli-Ampere)  
15 beta1 = IC1 / IB1 //New value of  
beta  
16  
17 //Result  
18  
19 printf("\n Beta of the transistor is %0.1f .\nalpha  
of the transistor is %0.2f .\nEmitter current  
is %0.3f mA.\nNew value of beta is %0.2f .",  
beta, alpha, IE, beta1)
```

Scilab code Exa 14.12 Value of collector current

```
1 clear//  
2  
3 // Variables  
4  
5 alpha = 0.98 //common  
    base current gain  
6 ICO = 5 * 10**-3 //Leakage  
    current (in milli-Ampere)  
7 IB = 100 * 10**-3 //Base  
    current (in milli-Ampere)  
8  
9 // Calculation  
10  
11 IC = (alpha * IB + ICO)/ (1 - alpha) //  
    Collector current (in milli-Ampere)  
12 IE = IC + IB //Emitter  
    current (in milli-Ampere)  
13  
14 // Result  
15  
16 printf("\n Value of collector current is %0.3f mA  
    .\nValue of emitter current is %0.3f mA.", IC, IE  
)
```

Scilab code Exa 14.13 Collector current when IB is 0 25 mA

```
1 clear//  
2  
3 // Variables  
4
```

```

5 ICB0 = 10 * 10**-3 //Leakage
    current (in milli-Ampere)
6 beta=50;hFE=50;
7 T2 = 50.0 //Temperature
    (in degree Celsius)
8 T1 = 27.0 //Temperature
    (in degree Celsius)
9
10 // Calculation
11
12 //Case (a)
13
14 IB = 0.25 //Base current
    (in milli-Ampere)
15 IC = beta * IB + (1 + beta)* ICB0 //Value of new
    collector current (in milli-Ampere)
16
17 //Case (b)
18
19 ICB01 = ICB0 * 2**((T2 - T1)/10) //ICBO at 50
    degree celsius (in milli-Ampere)
20 IC1 = beta * IB + (1 + beta)* ICB01 //Value of new
    collector current (in milli-Ampere)
21
22 // Result
23
24 printf("\n Collector current when IB = 0.25 mA is
    %0.3f mA.\nCollector current at 50 degree
    Celsius is %0.2f mA.",IC,IC1)

```

Chapter 15

BJT Characteristics

Scilab code Exa 15.1 Maximum power dissipation at 70 degree Celsius

```
1 clear//  
2  
3 // Variables  
4  
5 PDmax = 500 //Maximum  
    Power dissipation at 25 degree Celsius (in milli-  
    watt)  
6 DF = 2.28 //derating  
    factor (in milli-watt per degree Celsius)  
7 T = 70 //Temperaure  
    (in degree Celsius)  
8  
9 //Calculation  
10  
11 PDmax70 = PDmax - DF * (T - 25) //Maximum  
    Power dissipation at 70 degree Celsius (in milli-  
    watt)  
12  
13 //Result  
14  
15 printf("\n Maximum power dissipation at 70 degree
```

Celsius is %0.0f mW.” , PDmax70)

Chapter 16

Field Effect Transistor

Scilab code Exa 16.4 The value of transconductance

```
1 clear//  
2  
3 // Variables  
4  
5 VGS1 = -3.1 //Gate-Source  
    voltage (in volts)  
6 VGS2 = -3.0 //Gate-Source  
    voltage (in volts)  
7 ID1 = 1.0 //Drain current  
    (in milli-Ampere)  
8 ID2 = 1.3 //Drain current  
    (in milli-Ampere)  
9  
10 // Calculation  
11  
12 dVGS = VGS2 - VGS1 //Change in  
    Gate-Source voltage (in volts)  
13 dID = ID2 - ID1 //Change in  
    Drain current (in milli-Ampere)  
14 gm = dID / dVGS //  
    Transconductance (in milli-Ampere per volt)
```

```

15
16 // Result
17
18 printf("\n The value of transconductance is %0.3f
mA/V.", gm)

```

Scilab code Exa 16.6 The value of ID when VGS is 6 V

```

1 clear //
2
3 // Variables
4
5 IDon = 10.0                                // Drain
       current (in milli-Ampere)
6 VGS = -12.0                                  // Gate-Source
       voltage (in volts)
7 VGSth = -3.0                                 // Threshold
       Gate-Source voltage (in volts)
8 VGS1 = -6.0                                   // Gate-Source
       voltage in another case (in volts)
9
10 // Calculation
11
12 K = IDon/(VGS - VGSth)**2                  //
       Transconductance (milli-Ampere per volt)
13 ID = (K) * (VGS1 - VGSth)**2    // Drain current (in
       milli-Ampere)
14
15
16 // Result
17
18 printf("\n Since the value of VGS is negative for
       the enhancement-type MOSFET , this indicated that
       device is P-channel .")
19 printf("\n The value of ID when VGS = -6 V is %0.3f

```

mA. " , ID)

Chapter 17

Thyristors

Scilab code Exa 17.1 Therefore the device will not be destroyed

```
1 clear//  
2  
3 // Variables  
4  
5 I = 40 //Current (in milli-  
Ampere)  
6 t = 15 * 10**-3 //time (in seconds)  
7 CFS = 93 //Circuit fusing rate (  
in Ampere-square second)  
8  
9 // Calculation  
10  
11 SCR = I**2 * t //Surge in the device (  
in Ampere-square second)  
12  
13 // Result  
14  
15 printf("\n Since value of SCR i.e. %0.3f A**2s is  
less than CFS i.e. %0.3f A**2s.",SCR,CFS)  
16 printf("\n Therefore the device will not be  
destroyed.")
```

Scilab code Exa 17.2 Maximum allowable time

```
1 clear//  
2  
3 //Variables  
4  
5 SCR=75.0; I2t=75.0;  
6 IS = 100.0 //Current (in Ampere)  
7  
8 //Calculation  
9  
10 tmax = I2t / IS**2 //Maximum allowable time  
    (in seconds)  
11  
12 //Result  
13  
14 printf("\n Maximum allowable time is %0.3f ms.",  
        tmax * 10***3)
```

Scilab code Exa 17.3 Peak point voltage of the circuit

```
1 clear//  
2  
3 //Variables  
4  
5 VD = 0.7 //Voltage (in volts)  
6 n = 0.75 //Intrinsic stand-off  
    ratio  
7 VBB = 12 //Base Voltage (in  
    volts)  
8
```

```

9 // Calculation
10
11 VP = n * VBB + VD           //Peak-point voltage (
    in volts)
12
13 // Result
14
15 printf("\n Peak - point voltage of the circuit is
    %0.3f V.", VP)

```

Scilab code Exa 17.4 Intrinsic stand off ratio

```

1 clear //
2
3 // Variables
4
5 rB1 = 4.0                      // Resistance (in kilo-
    ohm)
6 rB2 = 2.5                      // Resistance (in kilo-
    ohm)
7 VBB = 15.0                     //Base voltage (in
    volts)
8 VD = 0.7                        //Voltage (in volts)
9
10 // Calculation
11
12 n = rB1 / (rB1 + rB2)         // Intrinsic stand-off
    ratio
13 VP = n * VBB + VD             //Peak-point voltage (
    in volts)
14
15 // Result
16
17 printf("\n Intrinsic stand off ratio is %0.4f .\
    nPeak-point voltage is %0.f ", n, VP)

```


Chapter 19

Rectifiers and Filters

Scilab code Exa 19.2 The value of dc load current

```
1 clear//  
2  
3 // Variables  
4  
5 RL = 20 //Load resistance (in  
       kilo-ohm)  
6 V2 = 24 //Secondary voltage (  
       in volts)  
7  
8 // Calculation  
9  
10Vm = 2**0.5 * V2 //Maximum value of  
    secondary voltage (in volts)  
11Im = Vm / RL //Maximumj value of  
    load current (in milli-Ampere)  
12Idc = 0.318 * Im //dc current (in  
    milli-Ampere)  
13  
14 // Result  
15  
16 printf("\n The value of dc load current is %0.3f
```

mA.” , Idc)

Scilab code Exa 19.3 Average value of load power

```
1 clear//  
2  
3 //Variables  
4  
5 V1 = 230 //Primary voltage (in volts  
)  
6 N2byN1 = 1.0/2.0 //Turns ratio  
7 RL = 200 //Resistance (in ohm)  
8  
9 //Calculation  
10  
11 V2 = V1 * N2byN1 //Secondary voltage (in  
volts)  
12Vm = 2**0.5 * V2 //Maximum value of  
secondary voltage (in volts)  
13 Im = Vm / RL //Maximum value of load  
current (in Ampere)  
14 Pm = Im**2 * RL //Maximum value of load  
power (in watt)  
15 Vdc = 0.318 *Vm //Average value of load  
power (in watt)  
16 Idc = Vdc / RL //Average value of load  
current (in Ampere)  
17 Pdc = Idc**2 * RL //Average value of load  
power (in watt)  
18  
19 //Result  
20  
21 printf("\n Maximum value of load power is %0.1f W.  
", Pm)  
22 printf("\n Average value of load power is %0.1f W.
```

” ,Pdc)

Scilab code Exa 19.4 Maximum a c voltage required at the input

```
1 clear//  
2  
3 // Variables  
4  
5 Vdc = 30.0 //Average value of  
    voltage (in volts)  
6 RL = 600.0 //Load resistance (in  
    ohm)  
7 Rf = 25.0 //forward resistance (in  
    ohm)  
8  
9 // Calculation  
10  
11 Idc = Vdc / RL //Average value of  
    load current (in Ampere)  
12 Im = (%pi * Idc) //Maximum value of load current (in Ampere)  
13  
14 Vinmax = Im * (Rf + RL) //Maximum a.c. voltage  
    required at the input (in volts)  
15  
16 // Result  
17  
18 printf("\n Maximum a.c. voltage required at the  
    input is %0.3f V.",Vinmax)
```

Scilab code Exa 19.6 The dc output voltage

```
1 clear//
```

```

2
3 // Variables
4
5 V1 = 230.0 // primary voltage ( in
   volts )
6 N2byN1 = 1.0/4.0 // Turns ratio
7 RL = 200 // Load resistance ( in ohm)
8 fin = 50 // Frequency ( in hertz )
9
10 // Calculation
11
12 V2 = V1 * N2byN1 // Secondary voltage ( in
   volts )
13Vm = 2**0.5 * V2 // Maximum value of voltage
14Vdc = 0.636 * Vm // Average value of voltage
15PIV = Vm // peak inverse voltage ( in
   volts )
16fout = 2 * fin // Output frequency ( in
   volts )
17
18 // Result
19
20 printf("\n The dc output voltage is %0.1f V.\nPeak
   inverse Voltage of a diode is %0.1f V.\nOutput
   frequency is %0.3f HZ.",Vdc,PIV,fout)

```

Scilab code Exa 19.7 The dc output voltage

```

1 clear //
2
3 // Variables
4
5 V1 = 230.0 // primary voltage ( in

```

```

    volts)
6 N2byN1 = 1.0/5.0          //Turns ratio
7 RL = 100                   //Load resistance (in ohm)
8
9 // Calculation
10
11 V2 = V1 * N2byN1         //Secondary voltage (in
    volts)
12 VS = V2 / 2              //Voltage between center -
    tap and either end of secondary winding (in
    volts)
13Vm = 2**0.5 * VS          //Maximum value of voltage
    (in volts)
14 Vdc = 2/%pi * Vm          //Averaage value of Voltage (
    in volts)
15 PIV = 2 * Vm              //Peak inverse voltage (in
    volts)
16 n = 0.812                 //Efficiency of full wave
    rectifier
17
18 // Result
19
20 printf("\n The dc output voltage is %0.1f V.\nPeak
    inverse voltage is %0.0f V.\nRectification
    efficiency is %0.3f .",Vdc,PIV,n)

```

Scilab code Exa 19.9 The value of Vdc

```

1 clear//
2
3 // Variables
4
5 Vs = 150.0                  //Voltage (in volts)
6 Idc = 2.0                    //Average value of current (in
    Ampere)

```

```

7
8 // Calculation
9
10 Vdc = 2.34 * Vs           // Average value of voltage (in
    volts)
11 Ipi = 1/0.955 * Idc      // Peak current per diode (in
    Ampere)
12 Iavg = 2.0/3.0           // Average current per diode (
    in AMPere)
13 Pdc = Vdc * Idc          // Average power delivered to
    the load (in watt)
14
15 // Result
16
17 printf("\n The value of Vdc is %0.3f V.\nPeak
        current through each diode is %0.1f A.\nAverage
        current through each diode is %0.2f A.\nAverage
        power delivered to the load is %0.3f W.",Vdc,
        Ipi,Iavg,Pdc)

```

Scilab code Exa 19.10 New Value of inductance

```

1 clear //
2
3 // Case (a):
4
5 // Variables
6
7 f = 50.0                      // Frequency (in
    Hertz)
8 g = 0.05                       // Ripple factor
9 RL = 100.0                      // Resistance (
    in ohm)
10 w = 2 * %pi * f                // Angular frequency
    (in radians per second)

```

```

11
12 // Calculation
13
14 L = RL / (3 * 2**0.5 * w * g)           // Inductance (
15   in Henry)
16 // Result
17
18 printf("\n Value of inductance is %0.1f H.",L)
19
20 // Case (b):
21
22 // Variables
23
24 f = 400.0                                // Frequency (in
25   Hertz)
26 g = 0.05                                  // Ripple factor
27 RL = 100.0                                 // Resistance (
28   in ohm)
29 w = 2 * %pi * f                          // Angular frequency
30   (in radians per second)
31
32 // Calculation
33
34 L = RL / (3 * 2**0.5 * w * g)           // Inductance (
35   in Henry)
36 // Result
37
38 printf("\n New Value of inductance is %0.3f H.",L)

```

Scilab code Exa 19.11 Value of capacitance

```

1 clear //
2

```

```

3 // Variables
4
5 Vdc = 30.0 // Average value of
    voltage (in volts)
6 RL = 1.0 // Resistance (in
    kilo-ohm)
7 gamma = 0.01 // Ripple factor
8 f = 50 // Frequency (in
    Hertz)
9 // Calculation
10
11 C = 2890.0 / (gamma * RL) // Capacitance (in
    nano Farad)
12
13 // Result
14
15 printf("\n Value of capacitance is %0.3f micro-
    Farad.", C * 10**-3)

```

Scilab code Exa 19.12 Capacitance

```

1 clear //
2
3 // Variables
4
5 Vdc = 12.0 // Average value of
    voltage (in volts)
6 Idc = 100.0 // Average value of
    current (in milli-Ampere)
7 gamma = 0.01 // Ripple factor
8 L = 1.0 // Inductance (in Henry
    )
9
10 // Calculation
11

```

```

12 C = 1.195 / (gamma * L)           // Capacitance
13
14 // Result
15
16 printf("\n Capacitance is %0.3f micro-Farad.", C)

```

Scilab code Exa 19.13 Ripple factor for 50 Hz supply

```

1 clear//
2
3 // Variables
4
5 Idc = 0.2                         // Average value
       of current (in Ampere)
6 Vdc = 30.0                         // Average value
       of voltage (in volts)
7 C1=100.0;C2=100.0;
8 L = 5.0                            // Inductance (
       in Henry)
9 f = 50.0                           // Frequency (in
       Hertz)
10
11 // Calculation
12
13 RL = Vdc / Idc                   // Load
       resistance (in ohm)
14 gamma = 5700.0 / (C1 * C2 * RL * L) // Ripple factor
15
16 // Result
17
18 printf("\n Ripple factor for 50 Hz supply is %0.3f
       .", gamma)

```

Chapter 20

Regulated Power Supplies

Scilab code Exa 20.1 The value of line regulation

```
1 clear//  
2  
3 // Variables  
4  
5 dVL = 100.0 * 10**-6          //Change in  
    output voltage (in volts)  
6 dVin = 5.0                     //Change in  
    input voltage (in volts)  
7  
8 // Calculation  
9  
10 LR = dVL / dVin             //Line  
    regulation (in volt per volt)  
11  
12 // Result  
13  
14 printf("\n The value of line regulation is %0.3f  
    micro-volt/volt.",LR * 10**6)
```

Scilab code Exa 20.2 The change in output voltage

```
1 clear//  
2  
3 // Variables  
4  
5 LR = 1.4 //Line regulation ( in  
       micro-volt per volt )  
6 dVS = 10 //Change in source  
       voltage ( in volts )  
7  
8 // Calculation  
9  
10 dVL = LR * dVS //Change in output  
       voltage ( in micro-volts )  
11  
12 // Result  
13  
14 printf("\n The change in output voltage is %0.3f  
       micro-volt .",dVL)
```

Scilab code Exa 20.3 Line regulation

```
1 clear//  
2  
3 // Variables  
4  
5 dIL = 40.0 //Change in current (   
       in milli-Ampere )  
6 VNL = 8.0 //Voltage under no  
       load ( in volts )  
7 VFL = 7.995 //Voltage under full  
       load ( in volts )  
8  
9 // Calculation
```

```

10
11 LR = (VNL - VFL) / dIL           // Line regulation (in
   milli-volt per milli-Ampere)
12
13 // Result
14
15 printf("\n Line regulation is %0.3f mV/mA.", LR *
   10**3)

```

Scilab code Exa 20.4 Full load Voltage

```

1 clear //
2
3 // Variables
4
5 LR = 10.0                      // Load
   regulation (in micro-volt per milli-Ampere)
6 VNL = 5.0                       // No load
   Voltage (in volts)
7 dIL = 20.0                      // Change in
   current (in milli-Ampere)
8
9 // Calculation
10
11 VFL = VNL - LR * dIL * 10**-6    // Full load
   Voltage (in volts)
12
13 // Result
14
15 printf("\n Full load Voltage is %0.3f V.", VFL)

```

Scilab code Exa 20.5 Change in output voltage

```
1 clear//  
2  
3 //Variables  
4  
5 V0 = 10  
    in volts)  
6 LR = 0.00002  
    //Line regulation  
7  
8 //Calculation  
9  
10 dV = LR * V0  
    voltage (in volts)  
11  
12 //Result  
13  
14 printf("\n Change in output voltage is %0.3f mV.",  
        dV * 10**3)
```

Scilab code Exa 20.6 Load voltage

```
1 clear//  
2  
3 //Variables  
4  
5 VS = 30.0 //Source voltage (in  
    volts)  
6 RS = 240.0 //Series resistance (in  
    ohm)  
7 Vz = 12.0 //Zener voltage (in  
    volts)  
8 RL = 500.0 //Load resistance (in  
    ohm)  
9  
10 //Calculation  
11
```

```

12 VL = VZ // Voltage drop across
            load (in volts)
13 IS = (VS - VZ) / RS // Current through RS (in
            Ampere)
14 VRS = IS * RS // Voltage drop across
            series resistance (in volts)
15 IL = VL / RL // Load current (in
            Ampere)
16 IZ = IS - IL // Zener current (in
            Ampere)
17
18 // Result
19
20 printf("\n Load voltage is %0.3f V.\nVoltage drop
            across series resistance is %0.3f V.\nCurrent
            through Zener diode is %0.3f A.",VL,VRS,IZ)

```

Scilab code Exa 20.8 Minimum value of load resistance

```

1 clear //
2
3 // Variables
4
5 VS = 24.0 // Source voltage (
            in volts)
6 RS = 500.0 // Series resistance
            (in ohm)
7 VZ = 12.0 // Zener Voltage (in
            volts)
8 IZmin = 3.0 // Minimum Zener
            current (in milli-Ampere)
9 IZmax = 90.0 // Maximum Zener
            current (in milli-Ampere)
10 rZ = 0.0 // Zener resistance
            (in ohm)

```

```

11
12 // Calculation
13
14 IS = (VS - VZ) / RS           // Current through
15   RS (in Ampere)
15 ILmax = IS - IZmin * 10**-3    // Maximum value of
16   load Current (in Ampere)
16 RLmin = VZ / ILmax           // Minimum value of
17   Load resistance (in ohm)
17
18 // Result
19
20 printf("\n Minimum value of load resistance is %0.0
f ohm.", RLmin)

```

Scilab code Exa 20.9 Maximum value of zener current

```

1 clear //
2
3 // Variables
4
5 VZ = 10.0                      // Zener
6   voltage (in volts)
6 RS = 1.0                        // Series
7   Resistance (in kilo-ohm)
7 RL = 2.0                         // Load
8   Resistance (in kilo-ohm)
8 VSmin = 22.0                     //
9   Minimum source voltage (in volts)
9 VSmax = 40                       //
10  Maximum source voltage (in volts)
10
11 // Calculation
12
13 IL = VZ / RL                   // Load

```

```

        current (in milli-Ampere)
14 IZmax = (VSmax - VZ) / RS - IL           // Maximum value of zener current (in milli-Ampere)
15 IZmin = (VSmin - VZ) / RS - IL           // Minimum value of zener current (in milli-Ampere)
16
17 //Result
18
19 printf("\n Maximum value of zener current is %0.3f
          mA.\nMinimum value of zener current is %0.3f
          mA.", IZmax ,IZmin)

```

Scilab code Exa 20.10 Maximum value of RS

```

1 clear// 
2
3 // Variables
4
5 VZ = 10.0                                // Zener
      voltage (in volts)
6 VSmin = 13.0                               // Minimum
      source voltage (in volts)
7 VSmax = 16.0                               // Maximum
      source voltage (in volts)
8 ILmin = 10.0                                // Minimum
      load current (in milli-Ampere)
9 ILmax = 85.0                                // Maximum
      load current (in milli-Ampere)
10 IZmin = 15.0                               // Minimum
      zener current (in milli-Ampere)
11
12 // Calculation
13
14 RSmax = (VSmin - VZ)/ (IZmin + ILmax)    // Maximum
      value of RS (in kilo-ohm)

```

```

15 IZmax = (VSmax - VZ) / RSmax - ILmin //Maximum
      zener current (in milli-Ampere)
16 PZmax = IZmax * 10**-3 * VZ           //Maximum
      power dissipation in zener (in watt)
17
18 // Result
19
20 printf("\n Maximum value of RS is %0.3f ohm.\n"
         "Maximum power dissipation be the zener diode is
          %0.3f W.", RSmax*10**3, PZmax)

```

Scilab code Exa 20.11 Magnitude of regulating resistance should be between

```

1 clear //
2
3 // Variables
4
5 VSmin = 19.5                                //Minimum
      source voltage (in volts)
6 VSmax = 22.5                                  //Maximum
      source voltage (in volts)
7 RL = 6.0 * 10**3                               //Load
      resistance (in ohm)
8 VZ = 18.0                                     //Zener
      voltage (in volts)
9 IZmin = 2.0 * 10**-6                           //Minimum
      zener current (in Ampere)
10 PZmax = 60.0 * 10**-3                         //Maximum
      power dissipation (in watt)
11 rZ = 20.0                                     //Zener
      resistance (in ohm)
12 VL = VZ                                      //Voltage
      across load resistance (in volt)
13
14 // Calculation

```

```

15
16 IZmax = (PZmax / rZ)**0.5           //Maximum
   value of zener current (in milli-Ampere)
17 IL = VL / RL                         //Load
   current (in milli-Ampere)
18 RSmax = (VSmin - VZ) / (IZmin + IL)    //Maximum
   value of regulating resistance (in kilo-ohm)
19 RSmin = (VSmax - VZ) / (IZmax + IL)    //Minimum
   value of regulating resistance (in kilo-ohm)
20
21 // Result
22
23 printf("\n Magnitude of regulating resistance should
   be between %0.1f ohm and %0.0f ohm.",RSmin,
   RSmax)

```

Scilab code Exa 20.12 Minimum value of Zener current

```

1 clear//
2
3 // Variables
4
5 VSmin = 8.0                      //Minimum source
   voltage (in volts)
6 VSmax = 12                        //Maximum source
   voltage (in volts)
7 RS = 2.2                          //Resistance (in kilo
   -ohm)
8 VZ = 5.0                          //Zener voltage (in
   volts)
9 RL = 10.0                         //Load resistance (in
   kilo-ohm)
10 VL = VZ                           //Voltage across load
   (in volts)
11

```

```

12 // Calculation
13
14 ISmin = (VSmin - VZ) / RS           //Minimum value of
   input current (in milli-Ampere)
15 ISmax = (VSmax - VZ) / RS           //Maximum value of
   input current (in milli-Ampere)
16 IL = VL / RL                      //Load current (in
   milli-Ampere)
17 IZmin = ISmin - IL                //Minimum Zener
   current (in milli-Ampere)
18 IZmax = ISmax - IL                //Maximum Zener
   current (in milli-Ampere)
19
20 // Result
21
22 printf("\n Minimum value of Zener current is %0.3f
   mA.\nMaximum value of Zener current is %0.3f
   mA.", IZmin, IZmax)

```

Scilab code Exa 20.13 For safety purpose RS should be 220 ohm

```

1 clear //
2
3 // Variables
4
5 V0=5.0; VL=5.0;
6 IL = 20.0                      //Load current (in
   milli-Ampere)
7 PZmax = 500.0                   //Maximum power
   dissipation in zener (in milli-watt)
8 VSmin = 9.0                      //Minimum source
   voltage (in volts)
9 VSmax = 15.0                     //Maximum source
   voltage (in volts)
10 VZ = 5

```

```

11 IZ =20
12 // Calculation
13
14 IZmax = PZmax / VZ           //Maximum zener
   current (in milli-Ampere)
15 ISmax = IL + IZ             //Maximum input
   current (in milli-Ampere)
16 RSmin = (VSmax - VZ)/(IZmax + IL) //Minimum value of
   regulating resistance (in kilo-ohm)
17 IZ = (VSmin - VZ)/ RSmin - IL    //Minimum value of
   zener current
18
19 // Result
20
21 printf("\n Input varies from the normal 12 v within
   the range of ± 3 V.")
22 printf("\n Zener current vary from %0.3f mA to %0
   .3f mA.", IZ, IZmax)
23 printf("\n For safety purpose RS should be 220 ohm."
   )

```

Scilab code Exa 20.14 The minimum value of voltage level at input

```

1 clear //
2
3 // Variables
4
5 RS = 500.0           //
   Series resistance (in ohm)
6 RL = 1.0             //
   resistance (in kilo-ohm)
7 VZ = 10.0            //
   Zener voltage (in volts)
8 IZmin = 5.0          //
   Minimum Zener current (in milli-Ampere)

```

```

9 IZmax = 55.0 //  

    Maximum Zener current (in milli-Ampere)  

10  

11 // Calculation  

12  

13 IL = VZ / RL //Load  

    current (in milli-Ampere)  

14 VSmin = (IL + IZmin) * RS * 10**-3 + VZ //  

    Minimum value of input voltage (in volts)  

15 VSmax = (IL + IZmax) * RS * 10**-3 + VZ //  

    Maximum value of input voltage (in volts)  

16  

17 // Result  

18  

19 printf("\n The minimum value of voltage level at  

    input is %0.3f V and the maximum is %0.3f V."  

    ,VSmin ,VSmax)

```

Scilab code Exa 20.15 Base current

```

1 clear//  

2  

3 //Variables  

4  

5 VS = 15.0 //Input voltage (in  

    volts)  

6 RS = 33.0 //Series resistance (in  

    ohm)  

7 beta = 100.0 //common-emitter current  

    gain  

8 RL = 100.0 //Load resistance (in  

    ohm)  

9 VZ = 10.0 //Voltage across zener  

    diode (in volts)  

10 VBE = 0.7 //Voltage across base

```

```

        and emitter
11
12 // Calculation
13
14 VL = VZ + VBE           // Load voltage (in volts
    )
15 IL = VL / RL            // Load current (in
    Ampere)
16 IS = (VS - VL) / RS    // Current through RS (in
    Ampere)
17 IC = IS - IL            // Collector current (in
    Ampere)
18 IB=IC/beta;IZ=IC/beta;
19
20 // Result
21
22 printf("\n Load voltage is %0.3f V.",VL)
23 printf("\n Load current is %0.3f mA.",IL * 10**3)
24 printf("\n Current through Rs is %0.1f mA.",IS *
    10**3)
25 printf("\n Collector current is %0.1f mA.",IC*
    10**3)
26 printf("\n Base current is %0.0f micro-A.",IB *
    10**6)

```

Scilab code Exa 20.16 Current through Zener

```

1 clear //
2
3 // Variables
4
5 VS = 15.0                  // Input voltage (in
    volts)
6 VZ = 8.3                   // Zener voltage (in
    volts)

```

```

7 beta = 100.0 //Common-emitter
    current gain
8 R = 1.8 //Resistance (in kilo
    -ohm)
9 RL = 2.0 //Resistance (in kilo
    -ohm)
10 VBE = 0.7 //Voltage across base
    -emitter junction (in volts)
11
12 // Calculation
13
14 VL = VZ - VBE //Voltage across load
    (in volts)
15 VCE = VS - VL //Collector to
    emitter voltage (in volts)
16 IR = (VS - VZ)/ R //Current through R (
    in milli-Ampere)
17 IL = VL / RL //Load current (in
    milli-Ampere)
18 IB = IL / beta //Base current (in
    milli-Ampere)
19 IZ = IR - IB //Current through
    Zener (in milli-Ampere)
20
21 // Result
22
23 printf("\n Load voltage is %0.3f V.",VL)
24 printf("\n Collector to Emitter voltage is %0.3f V
    .",VCE)
25 printf("\n Current through R is %0.2f mA.",IR)
26 printf("\n Load current is %0.3f mA.",IL)
27 printf("\n Base current is %0.3f micro-A.",IB *
    10***3)
28 printf("\n Current through Zener is %0.2f mA.",IZ)

```

Scilab code Exa 20.17 Maximum value of R

```
1 clear//  
2  
3 // Variables  
4  
5 IZmin = 0                                //Minimun Zener  
    current (in Ampere)  
6 ILmax = 2.0                                //Maximum load current  
    (in Ampere)  
7 VL = 12.0                                  //Voltage across load  
    (in volts)  
8 VSmin = 15.0                                //Minimum Input  
    voltage (in volts)  
9 VSmax = 20.0                                //Maximum Input  
    Voltage (in volts)  
10 beta = 100                                 //common emitter  
    current gain  
11 VBE = 0.5                                  //Voltage between base  
    -emitter junction (in volts)  
12 VZ = 12.5                                  //Voltage across zener  
    diode (in volts)  
13 IZmin = 1.0 * 10**-3                      //Current through  
    Zener diode  
14 ICmax = ILmax                            //Maximum Collector  
    current (in Ampere)  
15  
16 // Calculation  
17  
18 IBmax = ICmax / beta                     //Maximum collector  
    current  
19 IR = IBmax + IZmin                      //Current through  
    resistance R (in Ampere)  
20 Rmax = (VSmin - VZ) / IR                //Maximum value of  
    resistance R (in ohm)  
21 IZmax = (VSmax - VZ) / Rmax            //Maximum value of  
    Zener current (in Ampere)  
22 PZmax = VZ * IZmax                      //Maximum power
```

```

        dissipation in Zener Diode (in watt)
23 PRmax = (VSmax - VZ) * IZmax //Maximum power
        dissipated in Resistance R (in watt)
24 VCEmax = VSmax - VL           //Maximum value of
        collector-to-emitter voltage (in volts)
25 PDmax = VCEmax * ILmax       //Maximum power
        dissipation of the transistor (in watt)
26
27 // Result
28
29 printf("\n Maximum value of R is %0.0f ohm.\n"
        "Maximum power dissipation of the zener diode is
        "%0.2f W.\nMaximum power dissipation of
        resistance R is %0.2f W.\nMaximum power
        dissipation of the transistor is %0.3f W.",Rmax
        ,PZmax,PRmax,PDmax)

```

Scilab code Exa 20.18 Value of Resistance R3

```

1 clear//
2
3 // Variables
4
5 VL = 12.0                         // Voltage across load
        (in volts)
6 IL = 200.0                          // Load current (in
        milli-Ampere)
7 VS = 30.0                           // Source voltage (in
        volts)
8 RS = 10.0                            // Series resistance (
        in ohm)
9 beta1=150.0;hfe1=150.0;
10 beta2=100.0;hfe2=100.0;
11 IC1 = 10.0                          // Collector current (
        in milli-Ampere)

```

```

12 VBE1 = 0.7 // Emitter-to-Base
    voltage1 (in volts)
13 VBE2 = 0.7 // Emitter-to-Base
    voltage2 (in volts)
14 VZ=6.0;VR=6.0;
15 RZ = 10.0 // Resistance of zener
    diode (in ohm)
16 IZ = 20.0 // Current through
    zener diode (in milli-Ampere)
17 ID = 10.0 * 10**-3 // Current (in Ampere)
18 I1 = 10.0 * 10**-3 // Current (in Ampere)
19
20 // Calculation
21
22 RD = (VL - VZ) / ID // Resistance (in ohm)
23 V2 = VZ + VBE2 // Voltage (in volts)
24 R1 = (VL - V2)/I1 // Value of resistance
    R1 (in ohm)
25 R2 = R1 * (V2 / (VL - V2)) // Value of resistance
    R2 (in ohm)
26 IB1 = (IL + I1 + ID) / beta1 // Base Current IB1 (
    in Ampere)
27 I = IB1 + IC1 // Current through
    resistance R3 (in Ampere)
28 R3 = (VS - (VBE1 + VL))/I // Value of resistance
    (in ohm)
29
30 // Result
31
32 printf("\n Value of Resistance RD is %0.3f ohm.\ \
    nValue of Resistance R1 and R2 is %0.3f ohm and \
    %0.3f ohm.",RD,R1,R2)
33 printf("\n Value of Resistance R3 is %0.1f kilo- \
    ohm.",R3)

```

Scilab code Exa 20.19 Vout

```
1 clear//  
2  
3 // Variables  
4  
5 VS = 25.0 //Source voltage (in  
    volts)  
6 VZ = 15.0 //Zener voltage (in volts  
    )  
7 RL = 1.0 //Load resistance (in  
    kilo-ohm)  
8 VBE = 0.7 //Emitter-to-Base voltage  
    (in volts)  
9  
10 // Calculation  
11  
12 Vout = VZ/2 + VBE //Output voltage (in  
    volts)  
13 IL = Vout / RL //Load current (in milli-  
    Ampere)  
14 IE1 = IL //Current (in milli-  
    Ampere)  
15 VCE1 = VS - Vout //Collector-To-Emitter  
    voltage (in volts)  
16 P1 = VCE1 * IE1 //Power dissipated (in  
    watt)  
17  
18 // Result  
19  
20 printf("\n Vout is %0.3f V.\nIL is %0.3f mA.\n"  
    "IE1 is %0.3f mA.\nP1 is %0.3f W.",Vout,IL,  
    IE1,P1)
```

Scilab code Exa 20.21 Regulated dc output voltage

```

1 clear//
2
3 //Variables
4
5 R1 = 220.0          //Resistance1 (in ohm)
6 R2 = 1.5 * 10**3    //Resistance2 (in ohm)
7 VREF = 1.25         //Reference voltage (in
                      volts)
8
9 //Calculation
10
11 Vo = VREF * (R2/R1 + 1) //Regulated dc output
                           voltage (in volts)
12
13 //Result
14
15 printf("\n Regulated dc output voltage is %0.2f V.
           ", Vo)

```

Scilab code Exa 20.22 Regulated dc output voltage

```

1 clear//
2
3 //Variables
4
5 R1 = 240.0          //Resistance1 (in ohm)
6 R2 = 2.4 * 10**3    //Resistance2 (in ohm)
7 VREF = 1.25         //Reference voltage (in
                      volts)
8
9 //Calculation
10
11 Vo = VREF * (R2/R1 + 1) //Regulated dc output
                           voltage (in volts)
12

```

```
13 // Result  
14  
15 printf("\n Regulated dc output voltage is %0.3f V.  
" ,V0)
```

Chapter 21

Controlled Rectifiers

Scilab code Exa 21.1 Angular firing control when load power P is 25 W

```
1 clear//  
2  
3 // Variables  
4  
5 RL = 100.0 //  
    Resistance (in ohm)  
6 Vm = 300.0 //  
    Maximum voltage (in volts)  
7 P1 = 25.0 //Load  
    power1 (in watt)  
8 P2 = 80.0 //Load  
    power2 (in watt)  
9  
10 // Calculation  
11  
12 Vdc = Vm / (2 * %pi) //dc  
    voltage (in volts)  
13 //When power is 25 watt  
14 cosinealpha = (P1 * RL / Vdc**2)**0.5 -1 // cos  
    of alpha  
15 alpha = acos(cosinealpha) //Value of
```

```

        alpha (in radians)
16
17 //When power is 80 watt
18 cosinealpha1 = (P2 * RL / Vdc**2)**0.5 -1      //cos
    of alpha
19 alpha1 = acos(cosinealpha1)                      //Value of
    alpha (in radians)
20 //Result
21
22 printf("\n Angular firing control when load power P
    = 25 W is %0.2f degree.\nAngular firing control
    when load power P = 80 W is %0.2f degree.", 
    alpha*180.0/%pi, alpha1*180.0/%pi)

```

Scilab code Exa 21.4 The value of resistance to limit the average current to 0.5 A

```

1 clear //
2
3 //Variables
4
5 Idc = 0.5                                //dc
    current (in Ampere)
6 Vrms = 100.0                               //Rms
    voltage (in volts)
7 alpha = 45.0                                //
    Firing angle (in degree)
8 Idc = 0.5                                //dc
    current (in Ampere)
9
10 //Calculation
11
12 alpharad = alpha * %pi / 180.0           //Firing
    angle (in radians)
13Vm = 2**0.5 * Vrms                         //Peak
    voltage (in volts)

```

```

14 Vdc = Vm / (2 * %pi)*(1 + cos(alpharad)) // Average
      voltage (in volts)
15 RL = Vdc / Idc                                // Load
      resistance (in ohm)
16
17 // Result
18
19 printf("\n The value of resistance to limit the
      average current to 0.5 A is %0.2f ohm.",RL)

```

Scilab code Exa 21.5 Chopper duty cycle

```

1 clear //
2
3 // Variables
4
5 TON = 30.0           // Chopper ON time (in milli-
      second)
6 TOFF = 10.0          // Chopper OFF time (in milli-
      second)
7
8 // Calculation
9
10 T = TON + TOFF     // Total time (in milli-second)
11 cdc = TON / T       // Chopper duty cycle
12 f = 1 / T           // Chopping frequency (in Hertz
      )
13
14 // Result
15
16 printf("\n Chopper duty cycle is %0.3f .\n Chopping
      frequency is %0.3f Hz.",cdc,f*10**3)

```

Scilab code Exa 21.6 Average valuye of dc voltage

```
1 clear//  
2  
3 // Variables  
4  
5 TON = 30.0 //Chopper ON time (in  
    millisecond)  
6 TOFF = 10.0 //Chopper OFF time (in  
    millisecond)  
7 Vdc = 200.0 //dc voltage (in volts)  
8  
9 // Calculation  
10  
11 T = TON + TOFF //Total time (in milli-  
    second)  
12 cdc = TON / T //Chopper duty cycle  
13 VL = Vdc * cdc //dc output voltage (in  
    volts)  
14  
15 // Result  
16  
17 printf("\n Average valuye of dc voltage is %0.3f V  
. ", VL)
```

Chapter 22

BJT Biasing and Stabilization

Scilab code Exa 22.3 The value of base current

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 25.0 //Source voltage (in  
    volts)  
6 RC = 820.0 //Collector Resistance  
    (in ohm)  
7 RB = 180.0 //Base Resistance (in  
    kilo-ohm)  
8 beta = 80.0 //Common-Emitter  
    current gain  
9  
10 // Calculation  
11  
12 IB = VCC / RB //Base current (in  
    milli-Ampere)  
13 IC = beta * IB //Collector current (in  
    milli-Ampere)  
14 VCE = VCC - IC * RC * 10**-3 //Collector-to-Emitter  
    voltage (in volts)
```

```
15
16 // Result
17
18 printf("\n The value of base current is %0.2f mA.\\"  
    "The value of Collector current is %0.2f mA.\\"  
    "The value of Collector-to-Emitter voltage is %0  
.2f V.",IB,IC,VCE)
```

Scilab code Exa 22.4 The collector current

```
1 clear// Variables
2
3 VBB = 2.7
4 RB = 40.0
5 VCC = 10.0
6 RC = 2.5
7 VBE = 0.7
8 beta = 100.0
9
10 // Calculation
11
12 IB = (VBB - VBE)/RB
13 IC = beta * IB
14
15 // Result
16
17 printf("\n The base current is %0.3f mA.",IB)
18 printf("\n The collector current is %0.3f mA.",IC)
```

Scilab code Exa 22.5 The value of collector current

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 5.0 // Source voltage (in  
    volts)  
6 RC = 5.0 // Collector  
    resistance (in kilo-ohm)  
7 VBB = 5.0 // Base voltage (in  
    volts)  
8 RB = 100.0 // Base Resistance (in  
    kilo-ohm)  
9 VBE = 0.7 // Emitter-to-Base  
    Voltage (in volts)  
10 beta = 30.0 // Common-Emitter  
    current gain  
11  
12 // Calculation  
13  
14 IB = (VBB - VBE)/RB // Base Current (in  
    milli-Ampere)  
15 IC = beta * IB // Collector Current (in  
    milli-Ampere)  
16 IC1 = VCC / RC // Collector Current (in  
    milli-Ampere)  
17  
18 // Result  
19  
20 printf("\n The value of collector current is for  
operation in saturation region is %0.3f mA.\nSince %0.3f mA is greater than %0.3f mA ,  
therefore it will operate in saturation region.",
```

IC1 , IC , IC1)

Scilab code Exa 22.7 VCE of the transistor

```
1 clear//  
2  
3 //Variables  
4  
5 VCC = 20.0                                //Source voltage (in  
       volts)  
6 RC = 2.0                                    //Collector  
       resistance (in kilo-ohm)  
7 RB = 400.0                                   //Base Resistance (in  
       kilo-ohm)  
8 beta = 100.0                                 //Common-Emitter  
       current gain  
9 RE = 1.0                                     //Emitter Resistance  
       (in kilo-ohm)  
10  
11 //Calculation  
12  
13 IB = VCC / (RB + beta * RE)                //Base current (in  
       milli-Ampere)  
14 IC = beta * IB                             //Collector Current  
       (in milli-Ampere)  
15 VCE = VCC - IC * (RC + RE)                 //Collector-to-  
       Emitter Voltage (volts)  
16  
17 //Result  
18  
19 printf("\n VCE of the transistor is %0.3f V.\nVCC  
       of the transistor is %0.3f V.\nIB of the  
       transistor is %0.3f mA.\nIC of transistor is  
       %0.3f mA.",VCE,VCC,IB,IC)
```

Scilab code Exa 22.10 When VBB is 0 V LED

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 5.0                                //Source voltage ( in volts )  
6 RE = 100.0                                 //Emitter resistance ( in kilo-ohm )  
7 VBE = 0.7                                  //Emitter-base Voltage ( in volts )  
8  
9 // Calculation  
10  
11 //Case 1 : when VBB = 0.2 V ->OFF  
12 //Case 2: when VBB = 3 V ->ON  
13  
14 // Result  
15  
16 printf("\n When VBB = 0 V , LED is in OFF condition  
.\nWhen VBB = 3 V , LED is in ON condition.")
```

Scilab code Exa 22.11 Collector current

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 25.0                                 //Source voltage ( in volts )
```

```

6  RC = 820.0                                // Collector
      resistance (in ohm)
7  RB = 180.0 * 10**3                         //Base Resistance
      (in ohm)
8  beta = 80.0                                 //Common-Emitter
      current gain
9  VBE = 0.7                                   //Emitter-to-Base
      Voltage (in volts)
10 RE = 200.0                                   //Emitter
      resistance (in kilo-ohm)

11
12 // Calculation
13
14 IC = (VCC -VBE)/(RE + RB / beta)          // Collector
      current (in milli-Ampere)
15 VCE = VCC - IC * RC                         // Collector-to-
      Emitter voltage (in volts)
16 S = 1 + beta                               // Stability factor
17
18 // Result
19
20 printf("\n Collector current is %0.1f mA.\n"
      "Collector-to-Emitter voltage is %0.3f V.\n"
      "Stability factor is %0.3f ." ,IC*10***3 ,VCE ,S)

```

Scilab code Exa 22.13 IB

```

1 clear//
2
3 // Variables
4
5 VCC = 10.0                                    // Source voltage (
      in volts)
6 RC = 2.0 * 10***3                            // Collector
      resistance (in ohm)

```

```

7 RB = 100.0 * 10**3 //Base Resistance
    (in ohm)
8 beta = 50.0          //Common-Emitter
    current gain
9 VBE = 0.7            //Emitter-to-Base
    Voltage (in volts)
10
11 // Calculation
12
13 IB = (VCC - VBE)/(RB + beta * RC) //Base current (in
    Ampere)
14 IC = beta * IB                  //Collector
    current (in Ampere)
15 IE = IC                        //Emitter current
    (in Ampere)
16 S = 1 + beta                  //Stability factor
17
18 // Result
19
20 printf("\n IB is %0.3f mA.\nIC is %0.3f mA.\nIE
    is %0.3f mA.", IB*10***3, IC*10***3, IE*10***3)

```

Scilab code Exa 22.14 In case 1 Collector junction

```

1 clear //
2
3 // Variables
4
5 //When VC = 0 volts
6 VCC = 9.0                      //Source
    voltage (in volts)
7 RB = 220.0                      //Base
    Resistance (in kilo-ohm)
8 RC = 3.3                         //Collector
    Resistance (in kilo-ohm)

```

```

9 VBE = 0.3 //Emitter-
    to-Base voltage (in volts)
10 beta = 100.0 //Common
    emitter current gain
11
12 // Calculation
13
14 IB = (VCC - VBE)/((RB + beta*RC)* 10**3) //Base
    current (in Ampere)
15 IC = beta * IB //Collector
    current (in Ampere)
16 VCE = VCC - IC * RC * 10**3 //Collector
    -to-emitter voltage (in volts)
17 VC = VCE //Collector
    voltage (in volts)
18 ICRC = VCC //Voltage (
    in volts)
19
20 //When VC = 9 volts
21 IB1 = 16.0 //Base
    current (in micro-Ampere)
22 IC1 = beta * IB1 //Collector
    current (in micro-Ampere)
23 RC1 = 0 //Collector
    Resistance (in ohm)
24
25 // Result
26
27 printf("\n In case 1, Collector junction is short
    circuited.\nIn case 2, Collector resistance is
    short circuited. " )

```

Scilab code Exa 22.15 The value of R1

```
1 clear//
```

```

2
3 // Variables
4
5 VCC = 12.0 //Source
   voltage (in volts)
6 RE = 100.0 //Emitter
   Resistance (in ohm)
7 RC = 3.3 //Collector
   Resistance (in kilo-ohm)
8 IE = 2.0 //Emitter
   current (in milli-Ampere)
9 VBE = 0.7 //Emitter-
   to-Base Voltage (in volts)
10 alpha = 0.98 //Common
    base current gain
11 R2 = 20.0 ///
    Resistance (in kilo-ohm)
12
13 // Calculation
14
15 IC = alpha * IE //Collector
   current (in milli-Ampere)
16 VB = VBE + IE * RE * 10***-3 //Base
   voltage (in volts)
17 VC = VCC - IC * RC //Collector
   voltage (in volts)
18 IR2 = VC / (R2) //Current
   through resistance 2 (in milli-Ampere)
19 IB = IE - IC //Base
   current (in milli-Ampere)
20 IR1 = IR2 + IB //Current
   through resistance 1 (in milli-Ampere)
21 R1 = (VC - VB) / IR1 //Value of
   the resistance (in kilo-ohm)
22
23 // Result
24
25 printf("\n The value of R1 is %0.1f kilo-ohm.",R1)

```

Scilab code Exa 22.16 Base resistance

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 24.0 // Source  
    voltage (in volts)  
6 RE = 270.0 // Emitter  
    Resistance (in ohm)  
7 RC = 10.0 // Collector  
    Resistance (in kilo-ohm)  
8 VBE = 0.7 // Emitter-  
    to-Base Voltage (in volts)  
9 beta = 45.0 // Common  
    emitter current gain  
10 VCE = 5.0 // Collector  
    -to-Emitter voltage (in volts)  
11  
12 // Calculation  
13  
14 IC = (VCC - VCE) / RC // Collector  
    current (in milli-Ampere)  
15 RB = ((VCC - VBE) / IC - RC) * beta // Base  
    Resistance (in kilo-ohm)  
16  
17 // Result  
18  
19 printf("\n Base resistance is %0.2f kilo-ohm.",RB)
```

Scilab code Exa 22.17 DC bias current

```

1 clear//
2
3 //Variables
4
5 VCC = 3.0                                //Source
6 RB = 33.0                                 //Base
7 RC = 1.8                                  //Collector
8 VBE = 0.7                                 //Emitter-
9 beta = 90.0                                //Common
10                                         emitter current gain
11 //Calculation
12
13 IB = (VCC - VBE) / (RB + beta * RC)      //Base
14                                         current (in milli-Ampere)
15 IC = beta * IB                            //Collector
16                                         current (in milli-Ampere)
17 VCE = VCC - IC * RC                      //Collector
18                                         -to-emitter voltage (in volts)
19 S = (1 + beta)/(1 + beta*RC/(RC + RB))   //Stability
20                                         factor
21
22 //Result
23
24 printf("\n DC bias current is %0.2f mA.\nDC bias
25 voltage is %0.1f V.\nStability factor is %0.1f
26 .",IC,VCE,S)

```

Scilab code Exa 22.18 Collector current

```
1 clear//
```

```

2
3 // Variables
4
5 VCC = 10.0 // Source
   voltage (in volts)
6 RE = 500.0 // Emitter
   Resistance (in ohm)
7 RC = 1.0 // 
   Collector Resistance (in kilo-ohm)
8 R1 = 10.0 // 
   Resistance (in kilo-ohm)
9 R2 = 5.0 // 
   Resistance (in kilo-ohm)
10 VBE = 0.7 // Emitter-
   to-Base Voltage (in volts)
11 beta = 100.0 // Common
   emitter current gain
12
13 // Calculation
14
15 VB = VCC * (R2 / (R1 + R2)) // Base
   voltage (in volts)
16 VE = VB - VBE // Emitter
   voltage (in volts)
17 IE = VE / RE // Emitter
   current (in Ampere)
18 IC = IE // 
   Collector current (in Ampere)
19 VCE = VCC - IC * (RC * 10**3 + RE) // 
   Collector-to-Emitter voltage (in volts)
20
21 // Result
22
23 printf("\n Collector current is %0.2f mA.\n"
   "Collector-to-Emitter voltage is %0.3f V.", IC
   *10**3, VCE)

```

Scilab code Exa 22.19 Emitter current

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 15.0 //Source  
    voltage (in volts)  
6 RE = 2.0 //Emitter  
    Resistance (in kilo-ohm)  
7 RC = 1.0 //  
    Collector Resistance (in kilo-ohm)  
8 R1 = 10.0 //  
    Resistance (in kilo-ohm)  
9 R2 = 5.0 //  
    Resistance (in kilo-ohm)  
10 VBE = 0.7 //Emitter  
    -to-Base Voltage (in volts)  
11  
12 // Calculation  
13  
14 Vth = VCC * (R2 / (R1 + R2)) //  
    Thevenin's voltage (in volts)  
15 Rth = R1 * R2 / (R1 + R2) //  
    Thevenin's equivalent resistance (in kilo-ohm)  
16 IE = (Vth - VBE) / (RE) //Emitter  
    current (in milli-Ampere)  
17 VCE = VCC - IE * (RC + RE) //  
    Collector-to-Emitter voltage (in volts)  
18  
19 // Result  
20  
21 printf("\n Emitter current is %0.3f mA.\nThe value  
        of collector-to-emitter voltage is %0.3f V.",
```

IE , VCE)

Scilab code Exa 22.20 The percentage change in collector current

```
1 clear//  
2  
3 //Variables  
4  
5 VCC = 12.0 // Source  
    voltage (in volts)  
6 RE = 100.0 // Emitter  
    Resistance (in ohm)  
7 RC = 1.0 //  
    Collector Resistance (in kilo-ohm)  
8 R1 = 25.0 //  
    Resistance (in kilo-ohm)  
9 R2 = 5.0 //  
    Resistance (in kilo-ohm)  
10 VBE = 0.7 // Emitter  
    -to-Base Voltage (in volts)  
11 betamin = 50.0 //Common  
    emitter current gain (min)  
12 betamax = 150.0 //Common  
    emitter current gain (max)  
13  
14 // Calculation  
15  
16 Vth = VCC * (R2 /(R1 + R2)) //  
    Thevenin's voltage (in volts)  
17 Rth = R1 * R2 / (R1 + R2) * 10**3 //  
    Thevenin's equivalent resistance (in ohm)  
18 IE1 = (Vth - VBE)/(RE + Rth/betamin) // Emitter  
    current (in Ampere)  
19 IE2 = (Vth - VBE)/(RE + Rth/betamax) // Emitter  
    current (in Ampere)
```

```

20 perc_change = (IE2 - IE1) / IE1 * 100      //  

    Percentage change in the value of beta  

21  

22 // Result  

23  

24 printf("\n The percentage change in collector  

    current is %0.1f .",perc_change)

```

Scilab code Exa 22.21 Operating point values

```

1 clear//  

2  

3 // Variables  

4  

5 VCC = 9.0                                // Source  

    voltage (in volts)  

6 RE = 680.0                                 // Emitter  

    Resistance (in ohm)  

7 RC = 1.0                                   //  

    Collector Resistance (in kilo-ohm)  

8 R1 = 33.0                                  //  

    Resistance (in kilo-ohm)  

9 R2 = 15.0                                   //  

    Resistance (in kilo-ohm)  

10 VBE = 0.7                                  // Emitter  

    -to-Base Voltage (in volts)  

11  

12 // Calculation  

13  

14 VB = VCC * R2 / (R1 + R2)                 // Base  

    voltage (in volts)  

15 VE = VB - VBE                            // Emitter  

    voltage (in volts)  

16 IE = VE / RE                             // Emitter  

    current (in Ampere)

```

```

17 IC = IE //  

    Collector current (in Ampere)  

18 VRC = IC * RC * 10**3 //Voltage  

    across collector resistance (in volts)  

19 VC = VCC - VRC //  

    Collector voltage (in volts)  

20 VCE = VC - VE //  

    Collector-to-emitter voltage (in volts)  

21  

22 //Result  

23  

24 printf("\n Operating point values are IC = %0.1f  

    mA and VCE = %0.3f V.", IC*10**3, VCE)

```

Scilab code Exa 22.22 The value of R1

```

1 clear//  

2  

3 //Variables  

4  

5 VCC = 5.0 //Source  

    voltage (in volts)  

6 RE = 0.3 //Emitter  

    Resistance (in kilo-ohm)  

7 IC = 1.0 //  

    Collector Current (in milli-Ampere)  

8 beta = 100.0 //Common  

    emitter current gain  

9 VCE = 2.5 //  

    Collector-to-Emitter voltage (in volts)  

10 VBE = 0.7 //Emitter  

    -to-Base Voltage (in volts)  

11 ICO = 0 //Reverse  

    saturation current (in Ampere)  

12 R2 = 10.0 //

```

```

    Resistance (in kilo -ohm)
13
14
15 // Calculation
16
17 IE = IC                                // Emitter
     current (in milli -Ampere)
18 RC = (VCC - VCE) / IE - RE              // /
     Collector resistance (in kilo -ohm)
19 VE = IE * RE                            // Emitter
     voltage (in volts)
20 VB = VE + VBE                          // Base
     voltage (in volts)
21 R1 = VCC / VB * R2 - R2                // /
     Resistance1 (in kilo -ohm)
22
23 // Result
24
25 printf("\n The value of R1 is %0.3f kilo -ohm and
           value of RC is %0.3f ohm.",R1,RC*10**3)

```

Scilab code Exa 22.23 Emitter current

```

1 clear //
2
3 // Variables
4
5 VCC = 20.0                                // Source
     voltage (in volts)
6 RE = 5.0                                    // Emitter
     Resistance (in kilo -ohm)
7 RC = 1.0                                     // /
     Collector Resistance (in kilo -ohm)
8 R1 = 10.0                                    // /
     Resistance (in kilo -ohm)

```

```

9 R2 = 10.0 //  

    Resistance (in kilo-ohm)  

10 VBE = 0.7 //Emitter  

    -to-Base Voltage (in volts)  

11  

12 // Calculation  

13  

14 VB = VCC * R2 / (R1 + R2) //Voltage  

    (in volts)  

15 VE = VB - VBE //Emitter  

    voltage (in volts)  

16 IE = VE / RE //Emitter  

    current (in milli-Ampere)  

17 IC = IE //  

    Collector current (in milli-Ampere)  

18 VCE = VCC - IC * RC //  

    Collector-to-emitter voltage (in volts)  

19 VC = VCE + VE //  

    Collector potential (in volts)  

20  

21 // Result  

22  

23 printf("\n Emitter current is %0.3f mA.\nValue of  

    VCE is %0.3f V.\nValue of collector potential  

    is %0.3f V.", IE, VCE, VC)

```

Scilab code Exa 22.24 Collector to Emitter VCE

```

1 clear//  

2  

3 // Variables  

4  

5 VCC = 8.0 //Source voltage  

    (in volts)  

6 VRC = 0.5 //Voltage across

```

```

    collector resistance (in volts)
7 RC = 800.0                                // Collector
    resistance (in ohm)
8 alpha = 0.96                                 //common base
    current gain
9
10 //Calculation
11
12 VCE = VCC - VRC                          // Collector-to-
    emitter voltage (in volts)
13 IC = VRC / RC                            // Collector
    current (in milli-Ampere)
14 IE = IC / alpha                          // Emitter
    current (in milli-Ampere)
15 IB = IE - IC                           // Base current (
    in milli-Ampere)
16
17 //Result
18
19 printf("\n Collector-to-Emitter VCE is %0.3f V.\ \
nBase current is %0.3f mA.",VCE,IB*10***3)

```

Scilab code Exa 22.28 The value of emitter current

```

1 clear //
2
3 // Variables
4
5 VEE = 10.0                                  // Emitter Bias
    Voltage (in volts)
6 VCC = 10.0                                  // Source
    voltage (in volts)
7 RC = 1.0                                    // Collector
    Resistance (in kilo-ohm)
8 RE = 5.0                                     // Emitter

```

```

        Resistance (in kilo -ohm)
9 RB = 50.0                                //Base
        Resistance (in kilo -ohm)
10 VBE = 0.7                                 //Emitter-to-
        Base Voltage (in volts)
11
12 //Calculation
13
14 VE = -VBE                                  //Emitter
        voltage (in volts)
15 IE = (VEE - VBE)/ RE                      //Emitter
        current (in milli -Ampere)
16 IC = IE                                     //Collector
        current (in milli -Ampere)
17 VC = VCC - IC * RC                         //Collector
        voltage (in volts)
18 VCE = VC - VE                             //Collector-to-
        Emitter voltage (in volts)
19
20 //Result
21
22 printf("\n The value of emitter current is %0.3f
        mA.\nThe value of collector current is %0.3f mA
        .\nThe value of collector-to-emitter voltage is
        %0.3f V.",IE,IC,VCE)

```

Scilab code Exa 22.30 Base voltage

```

1 clear //
2
3 // Variables
4
5 VCC = 12.0                                    // Source
        voltage (in volts)
6 RE = 1.0                                       //

```

```

    Emitter Resistance (in kilo-ohm)
7  RC = 2.0                                //
    Collector Resistance (in kilo-ohm)
8  R1 = 100.0                               //
    Resistance (in kilo-ohm)
9  R2 = 20.0                                 //
    Resistance (in kilo-ohm)
10 VBE = -0.2                                //
    Emitter-to-Base Voltage (in volts)
11 beta = 100.0                               //Common
    emitter current gain
12
13 // Calculation
14
15 VB = -VCC * R2 / (R1 + R2)                //Base
    voltage (in volts)
16 VE = VB - VBE                            //
    Emitter voltage (in volts)
17 IE = -VE / RE                           //
    Emitter current (in milli-Ampere)
18 IC = IE                                  //
    Collector current (in milli-Ampere)
19 VC = -(VCC - IC * RC)                   //
    Collector voltage (in volts)
20 VCE = VC - VE                           //
    Collector-to-emitter voltage (in volts)
21
22 // Result
23
24 printf("\n Base voltage is %0.3f V.\nEmitter
    voltage is %0.3f V.\nCollector voltage is %0.3
    f V.\nCollector current is %0.3f mA.\nEmitter
    current is %0.3f mA.\nCollector-to-emitter
    voltage is %0.3f V.",VB,VE,VC,IC,IE,VCE)

```

Scilab code Exa 22.32 The operating point values

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 4.5 //  
   Source voltage (in volts)  
6 RE = 0.27 //  
   Emitter Resistance (in kilo-ohm)  
7 RC = 1.5 //  
   Collector Resistance (in kilo-ohm)  
8 R1 = 27.0 //  
   Resistance (in kilo-ohm)  
9 R2 = 2.7 //  
   Resistance (in kilo-ohm)  
10 VBE = 0.3 //  
   Emitter-to-Base Voltage for germanium (in volts)  
11 beta = 44.0 //  
   Common emitter current gain  
12  
13 // Calculation  
14  
15 VB = - VCC * R2 / (R1 + R2) // Base  
   voltage (in volts)  
16 VE = VB - (-VBE) //  
   Emitter voltage (in volts)  
17 IE = VE / RE //  
   Emitter current (in milli-Ampere)  
18 IC = IE //  
   Collector current (in milli-Ampere)  
19 VRC = -IC * RC //  
   Voltage across collector resistance (in volts)  
20 VC = -(VCC - VRC) //  
   Collector voltage (in volts)  
21 VCE = -(-VC - (-VE)) //  
   Collector-to-emitter voltage (in volts)  
22
```

```
23 // Result  
24  
25 printf("\n The operating point values are IC = %0.3  
f mA and VCE = %0.2f V.", -IC, VCE)
```

Chapter 24

Singly Stage BJT Amplifiers

Scilab code Exa 24.1 Input resistance looking into the base

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 10.0                                //Source voltage (in volts)  
6 RC = 10.0                                    //Collector resistance (in kilo-ohm)  
7 RB = 1.0 * 10**3                            //Base resistance (in kilo-ohm)  
8 beta = 100.0                                 //Common emitter current gain  
9 VBE = 0.7                                    //Emitter-to-Base Voltage (in volts)  
10  
11 // Calculation  
12  
13 IB = (VCC - VBE) / RB                      //Base current (in milli-Ampere)  
14 IC = beta * IB                             //Collector current (in milli-Ampere)
```

```

15 IE = IC                                //Emitter current
    (in milli-Ampere)
16 r1e = 25.0 / IE * 10**-3                //a.c resistance
    of emitter diode (in kilo-ohm)
17 R1 = beta * r1e                         //Input resistance
    looking directly into the base (in kilo-ohm)
18 Ris = RB * R1/(RB + R1)                 //Stage input
    resistance (in kilo-ohm)
19 Ro = RC                                //Output
    resistance (in kilo-ohm)
20 Av = RC / r1e                           //Voltage gain
21
22 // Result
23
24 printf("\n Input resistance looking into the base is
        %0.2f kilo-ohm.\nInput resistance of the stage
        is %0.3f kilo-ohm.\nOutput resistance is %0.3
        f kilo-ohm.\nVoltage gain is %0.3f .",R1,Ris,Ro
        ,Av)

```

Scilab code Exa 24.2 The base current

```

1 clear//
2
3 // Variables
4
5 Ri = 2.5                                //Input resistance
    (in kilo-ohm)
6 Av = 200.0                               //Voltage gain
7 Vs = 5.0 * 10**-3                         //Input signal
    voltage (in volts)
8 beta = 50.0                               //Common emitter
    current gain
9
10 // Calculation

```

```

11
12 IB = Vs / Ri //Base current (in
    milli-Ampere)
13 IC = beta * IB //Collector current
    (in milli-Ampere)
14 Ai = beta //Current gain
15 Ap = Ai * Av //Power gain
16 Gp = 10 * log10(Ap) //dB power gain (in
    decibel)
17
18 //Result
19
20 printf("\n The base current is %0.3f mA.\nThe
    collector current is %0.3f mA.\nThe power gain
    is %0.3f .\nThe dB power gain is %0.3f dB.",IB
    ,IC,Ap,Gp)

```

Scilab code Exa 24.3 Input resistance looking into the base

```

1 clear//
2
3 //Variables
4
5 VCC = 20.0 //Source voltage (
    in volts)
6 RC = 5.0 //Collector
    resistance (in kilo-ohm)
7 RE = 1.0 //Emitter
    resistance (in kilo-ohm)
8 RB = 100.0 //Base resistance (
    in kilo-ohm)
9 beta = 150.0 //Common emitter
    current gain
10
11 //Calculation

```

```

12
13 IC = VCC / (RE + RB/beta)           // Collector current
   (in milli-Ampere)
14 IE = IC                                // Emitter current (
   in milli-Ampere)
15 r1e = 25.0 / IE * 10**-3             // a.c. resistance
   of emitter diode (in kilo-ohm)
16 Ri = beta * (r1e + RE)                // Input resistance
   looking directly into the base (in kilo-ohm)
17 Ris = RB * Ri / (RB + Ri)            // Input resistance
   of the stage (in kilo-ohm)
18 Av = RC / RE                          // Voltage gain
19 Gp = 10 * log10(Av)                  // dB power gain (in
   decibel)
20
21 // Result
22
23 printf("\n Input resistance looking into the base is
   %0.0f kilo-ohm.\nInput resistance of the stage
   is %0.0f kilo-ohm.\nVoltage gain is %0.3f .\
   ndB voltage gain is %0.0f dB.",Ri,Ris,Av,Gp)

```

Scilab code Exa 24.4 Input resistance looking into the base

```

1 clear//
2
3 // Variables
4
5 VCC = 12.0                            // Source voltage (
   in volts)
6 RC = 10.0 * 10**3                      // Collector
   resistance (in ohm)
7 RE = 1.0 * 10**3                       // Emitter
   resistance (in ohm)
8 RB = 500.0 * 10**3                     // Base resistance (

```

```

        in ohm)
9 beta = 50.0                                //Common emitter
    current gain

10
11 // Calculation
12
13 IC = VCC / (RE + RB/beta)                  //Collector current
    (in Ampere)
14 IE = IC                                     //Emitter current (
    in Ampere)
15 r1e = 25.0 / IE * 10**-3                   //a.c. resistance
    of emitter diode (in ohm)
16 Ri = beta * (r1e)                           //Input resistance
    looking directly into the base (in ohm)
17 Ris = RB * Ri / (RB + Ri)                  //Input resistance
    of the stage (in ohm)
18 Av = RC / r1e                               //Voltage gain
19 AV1 = RC / RE                               //New voltage gain
20
21 // Result
22
23 printf("\n Input resistance looking into the base is
        %0.0 f ohm.\nInput resistance of the stage is
        %0.1 f kilo-ohm.\nVoltage gain is %0.2 f .\nNew
        Voltage gain is %0.3 f .",Ri,Ris,Av,AV1)

```

Scilab code Exa 24.5 a c output voltage

```

1 clear //
2
3 // Variables
4
5 VCC = 30.0                                    //Source voltage (
    in volts)
6 RC = 10.0                                     //Collector

```

```

        resistance (in kilo-ohm)
7 RE = 8.2                                //Emitter
        resistance (in kilo-ohm)
8 RL = 3.3                                //Load resistance
        (in kilo-ohm)
9 beta = 200.0                             //Common emitter
        current gain
10 VBE = 0.7                               //Emitter-to-Base
        Voltage (in volts)
11 R1 = 47.0                                //Resistance (in
        kilo-ohm)
12 R2 = 15.0                                //Resistance (in
        kilo-ohm)
13 Vs = 5.0                                 //a.c voltage (in
        milli-volts)
14
15 // Calculation
16
17 Vth = VCC * R2 / (R1 + R2)              //Thevenin's
        voltage (in volts)
18 Rth = R1 * R2 / (R1 + R2)              //Thevenin's
        equivalent voltage (in volts)
19 IE = (Vth - VBE)/(RE + Rth/beta)      //Emitter current
        (in milli-Ampere)
20 r1e = 25.0 / IE                         //a.c. resistance
        of emitter diode (in ohm)
21 rL = RC * RL/(RC + RL)                  //a.c load seen by
        the amplifier (in kilo-ohm)
22 Av = rL * 10**3 / r1e                   //Voltage gain
23 vo = Av * Vs                           //Output voltage (
        in volts)
24 Ri = beta * r1e * 10**-3                //Input resistance
        looking directly into the base (in ohm)
25 Ris = Rth * Ri / (Rth + Ri)           //input resistance
        of the stage (in ohm)
26
27 // Result
28

```

```
29 printf("\n a.c output voltage is %0.2f mV.\nInput  
impedance for the circuit is %0.0f kilo-ohm.",  
vo,Ris)
```

Scilab code Exa 24.6 The output voltage

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 10.0  
    voltage (in volts) // Source  
6 RC = 5.0  
    resistance (in kilo-ohm) // Collector  
7 RE = 1.0  
    resistance (in kilo-ohm) // Emitter  
8 beta = 50.0  
    emitter current gain // Common  
9 VBE = 0.7  
    Base Voltage (in volts) // Emitter-to-  
10 R1 = 50.0  
    in kilo-ohm) // Resistance (in kilo-ohm)  
11 R2 = 10.0  
    in kilo-ohm) // Resistance (in kilo-ohm)  
12 Vs = 10.0  
    (in milli-volts) // a.c voltage  
13 RS = 600.0 * 10**-3  
    resistance (in kilo-ohm) // Source  
14  
15 // Calculation  
16  
17 Vth = VCC * R2 / (R1 + R2)  
    voltage (in volts) // Thevenin's  
18 Rth = R1 * R2 / (R1 + R2)  
    equivalent voltage (in volts) // Thevenin's
```

```

19 IE = (Vth - VBE)/(RE + Rth/beta)           // Emitter
      current (in milli-Ampere)
20 r1e = 25.0 / IE * 10**-3                   // a.c.
      resistance of emitter diode (in kilo-hm)
21 Ris = Rth * beta*r1e/(Rth + beta*r1e) // input
      resistance of the stage (in ohm)
22 rL = RC * R1/(RC + R1)                     // a.c load
      seen by the amplifier (in kilo-ohm)
23 Av = rL / r1e                            // Voltage gain
24 vin = Vs * Ris / (Ris + RS)             // input
      voltage (in milli-volts)
25 vo = Av * vin                           // Output
      voltage (in milli-volts)
26 Avs = Av * vin / Vs                    // Overall
      voltage gain
27
28 // Result
29
30 printf("\n The output voltage is %0.3f V.\nThe
      overall voltage gain is %0.2f ." ,vo*10**-3 ,Avs)

```

Scilab code Exa 24.7 The voltage gain

```

1 clear //
2
3 // Variables
4
5 VCC = 12.0                         // Source
      voltage (in volts)
6 RC = 4.0                            // Collector
      resistance (in kilo-ohm)
7 RE = 3.3                            // Emitter
      resistance (in kilo-ohm)
8 beta = 120.0                         // Common
      emitter current gain

```

```

9 VBE = 0.7 // Emitter-to-
               Base Voltage (in volts)
10 R1 = 60.0 // Resistance (
               in kilo-ohm)
11 R2 = 30.0 // Resistance (
               in kilo-ohm)
12
13 // Calculation
14
15 Vth = VCC * R2 / (R1 + R2) // Thevenin's
               voltage (in volts)
16 Rth = R1 * R2 / (R1 + R2) // Thevenin's
               equivalent voltage (in volts)
17 IE = (Vth - VBE)/(RE + Rth/beta) // Emitter
               current (in milli-Ampere)
18 r1e = 25.0 / IE * 10**-3 // a.c.
               resistance of emitter diode (in kilo-ohm)
19 rL = RC // Load
               resistance (in kilo-ohm)
20 Av = RC / r1e // Voltage gain
21
22 // Result
23
24 printf("\n The voltage gain is %0.1f .",Av)

```

Scilab code Exa 24.8 Voltage gain

```

1 clear //
2
3 // Variables
4
5 VCC = -18.0 // Source
               voltage (in volts)
6 RC = 4.3 // Collector
               resistance (in kilo-ohm)

```

```

7 RE = 1.0 // Emitter
             resistance (in kilo -ohm)
8 beta = 200.0 //Common
               emitter current gain
9 VBE = -0.7 // Emitter-to-
               Base Voltage (in volts)
10 R1 = 39.0 // Resistance (
               in kilo -ohm)
11 R2 = 8.2 // Resistance (
               in kilo -ohm)
12 RL = 3.0 // Load
               resistance (in kilo -ohm)
13
14 // Calculation
15
16 Vth = VCC * R2 / (R1 + R2) // Thevenin 's
               voltage (in volts)
17 Rth = R1 * R2 / (R1 + R2) // Thevenin 's
               equivalent voltage (in volts)
18 IC = (Vth - VBE)/(RE + Rth/beta) // Collector
               current (in milli -Ampere)
19 IE = -IC // Emitter
               current (in milli -Amper)
20 r1e = 30.0/IE * 10**-3 // a . ac
               resistance (in kilo -ohm)
21 Ris = Rth * beta*r1e/(Rth + beta*r1e) // input
               resistance of the stage (in ohm)
22 rL = RC * RL / (RC + RL) // a . c . load
               resistance (in kilo -ohm)
23 Av = rL / r1e // Voltage gain
24
25 // Result
26
27 printf("\n Voltage gain is %0.1f ." ,Av)

```

Scilab code Exa 24.9 Av

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 20.0 //Source  
    voltage (in volts)  
6 RC = 5.7 //Collector  
    resistance (in kilo-ohm)  
7 RE = 1.0 //Emitter  
    resistance (in kilo-ohm)  
8 beta = 100.0 //Common  
    emitter current gain  
9 VBE = 0.7 //Emitter-to-  
    Base Voltage (in volts)  
10 R1 = 100.0 //Resistance (in kilo-ohm)  
11 R2 = 10.0 //Resistance (in kilo-ohm)  
12 Vs = 10.0 * 10**-3 //a.c voltage  
    (in volts)  
13 RS = 100.0 * 10**-3 //Source  
    resistance (in kilo-ohm)  
14  
15 //Calculation  
16  
17 Vth = VCC * R2 / (R1 + R2) //Thevenin's  
    voltage (in volts)  
18 Rth = R1 * R2 / (R1 + R2) //Thevenin's  
    equivalent resistance (in kilo-ohm)  
19 IE = (Vth - VBE) / (RE + Rth/beta) //Emitter  
    current (in milli-Ampere)  
20 r1e = 25.0 / IE * 10**-3 //a.c.  
    resistance of emitter diode (in kilo-ohm)  
21 Ris = Rth * beta*r1e / (Rth + beta*r1e) //input  
    resistance of the stage (in ohm)  
22 rL = RC //Load
```

```

        resistance (in kilo -ohm)
23 Av = rL / r1e                                // Voltage gain
24 vin = Vs * Ris / (Ris + RS)                  // input
      voltage (in milli -volts)
25 vo = Av * vin                                // Output
      voltage (in milli -volts)
26 Avs = Av * vin / Vs                          // Overall
      voltage gain
27
28 // Result
29
30 printf("\n Av is %0.3f .\nRi is %0.2f ohm.\nVo is
      %0.2f V.\nAvs is %0.2f ." ,Av ,Ris*10**3 ,vo ,Avs
)

```

Scilab code Exa 24.11 Input resistance looking directly into the base

```

1 clear //
2
3 // Variables
4
5 VCC = 10.0                                     // Source
      voltage (in volts)
6 RC = 5.0                                       // Collector
      resistance (in kilo -ohm)
7 rE = 500 * 10**-3                               // Emitter
      resistance (in kilo -ohm)
8 beta = 50.0                                     // Common
      emitter current gain
9 VBE = 0.7                                       // Emitter-to-
      Base Voltage (in volts)
10 R1 = 50.0                                      // Resistance (
      in kilo -ohm)
11 R2 = 10.0                                      // Resistance (
      in kilo -ohm)

```

```

12 Vs = 100.0 * 10**-3 //a.c voltage
    (in volts)
13 RS = 600.0 * 10**-3 //Source
    resistance (in kilo-ohm)
14 RL = 50.0 //Load
    resistance (in kilo-ohm)
15 RE1 = 500.0 * 10**-3 //Resistance (
    in kilo-ohm)

16
17 // Calculation
18
19 Vth = VCC * R2 /(R1 + R2) //Thevenin 's
    voltage (in volts)
20 Rth = R1 * R2 / (R1 + R2) //Thevenin 's
    equivalent resistance (in kilo-ohm)
21 RE = RE1 + rE //Emitter
    total resistance (in kilo-ohm)
22 IE = (Vth - VBE)/(RE + Rth/beta) //Emitter
    current (in milli-Ampere)
23 r1e = 25.0 / IE * 10**-3 //a.c.
    resistance (in kilo-ohm)
24 Ri = beta * (rE + r1e) //Input
    resistance directly into the base (in kilo-ohm)
25 Ris = Rth * Ri/(Rth + Ri) //Input
    resistance of the stage (in kilo-ohm)
26 rL = RC * RL / (RC + RL) //a.c. load
    resistance (in kilo-ohm)
27 Av = rL/(rE + r1e) //Voltage gain
28 Avs = Av * Ris / (RS + Ris) //Overall
    voltage gain
29 Vo = Avs * Vs //Output
    voltage (in volts)
30
31 // Result
32
33 printf("\n Input resistance looking directly into
        the base is %0.1f kilo-ohm.\nInput resistance
        of the stage is %0.2f kilo-ohm.\nVoltage gain

```

is %0.3f .\nOverall voltage gain is %0.2f .\nOutput voltage is %0.2f V.",Ri,Ris,Av,Avs,Vo)

Chapter 25

Hybrid Parameters

Scilab code Exa 25.1 h11

```
1 clear//  
2  
3 // Variables  
4  
5 R1 = 6.0                      //Resistance (in ohm)  
6 R2 = 4.0                      //Resistance (in ohm)  
7 R3 = 4.0                      //Resistance (in ohm)  
8  
9 // Calculation  
10 //Let i1 = 10 A and v2 = 10 V.  
11 i1 = 10.0                     //Assumed current (in  
    Ampere)  
12 v2 = 10.0                     //Assumed voltage (in  
    volts)  
13 //Parameters h11 and h21  
14  
15 h11 = R1 + R2 * R3/(R2 + R3) //Input resistance  
    looking from the input terminals (in ohm)  
16 i2 = -i1 / 2                  //Current2 (in Ampere)  
17 h21 = i2/i1                   //h21  
18
```

```

19 // Parameters h12 and h22
20
21 v1 = v2/2                                // Voltage1 (in volts)
22 h12 = v1 / v2                            // h12
23 rnet = R2 + R3                          // Output resistance (in
    ohm)
24 h22 = 1/rnet                            // h22 (in mhos)
25
26 // Result
27
28 printf("\n h11 : %0.3f \n h21 : %0.3f \n h12 : %0
    .3f \n h22 : %0.3f ",h11,h21,h12,h22)

```

Scilab code Exa 25.2 Input resistance of the amplifier stage

```

1 clear//
2
3 // Variables
4
5 hie = 1.0 * 10**3                         // hie (in ohm
    )
6 hre = 1.0 * 10**-4                         // hre
7 hoe = 100.0 * 10**-6                        // hoe (in mho
    )
8 RC = 1.0 * 10**3                           // Collector
    resistance (in ohm)
9 RS = 1000.0                                 // Source
    resistance (in ohm)
10 hfe=50.0;beta=50.0;
11
12 // Calculation
13
14 rL = RC                                    // a.c. load
    resistance (in ohm)
15 Ai = -hfe /(1 + hoe * rL)                  // Current

```

```

        gain of a transistor
16 Ri = hie + hre * Ai * rL           //Input
    resistance looking directly into the base (in ohm
)
17 Ris = Ri                           //Input
    resistance of the amplified stage (in ohm)
18 dh = hie * hoe - hre * hfe         //Change in h
19 Ro = (RS + hie)/(RS * hoe + dh)   //Output
    resistance looking directly into collector (in
ohm)
20 Ros = Ro * rL /(Ro + rL)          //Output
    resistance of the amplified stage (in ohm)
21 Ais = Ai * RS / (RS + Ris)        //Current
    gain of amplified stage
22 Av = Ai * rL / Ri                //Voltage
    gain of transistor
23 Avs = Av * Ris / (RS + Ris)      //Voltage
    gain of amplified stage
24
25 // Result
26
27 printf("\n Input resistance of the amplifier stage
    is %0.0f ohm.\nOutput resistance of amplifier
    stage is %0.0f ohm.\nCurrent gain of amplified
    stage is %0.1f \nVoltage gain of amplifier stage
    is %0.1f .",Ris,Ros,Ais,Avs)

```

Scilab code Exa 25.3 Current gain

```

1 clear//
2
3 // Variables
4
5 hie = 1.1 * 10**3                  //hie (in ohm
)

```

```

6 hre = 2.5 * 10**-4                                //hre
7 hoe = 25.0 * 10**-6                               //hoe (in mho
8 )                                                 )
9 RS = 1000.0                                         //Source
10      resistance (in ohm)
11 hfe=50.0;beta=50.0;
12 rL = 1000.0                                         //ac.c load
13      resistance (in ohm)
14
15 // Calculation
16
17
18 // Result
19
20 printf("\n Current gain is %0.2f \nInput impedance
21      is %0.1f \nVoltage gain is %0.2f ",Ai,Ri,Av)

```

Scilab code Exa 25.4 Voltage gain

```

1 clear //
2
3 // Variables
4
5 RC = 4.0 * 10**3                                     //Collector resistance
6      (in ohm)
7 RB = 40.0 * 10**3                                    //Base resistance (in
8      ohm)
9 RS = 10.0 * 10**3                                    //Source resistance (
10     in ohm)

```

```

8 hie = 1100.0 //hie (in ohm)
9 hfe = 50.0 //hfe
10 hre=0; hoe=0; dh=0;
11
12 // Calculation
13
14 RB2 = RB //Resistance (in kilo-
    ohm)
15 rL = RC * RB2 /(RC +RB2) //a.c. load resistance
    (in ohm)
16 Ai = -hfe //Current gain
17 Ri = hie //Input resistance of
    the amplifier looking into the base (in ohm)
18 Av = Ai * rL / Ri //Voltage gain
19 RB1 = RB/(1 - Av) //Resistance (in ohm)
20 Ris = Ri * RB1 / (Ri + RB1) //Input resistance
    looking from source terminals (in ohm)
21 Ro = "infinite" //Output resistance (
    in ohm)
22 Ros = rL //Output resistance of
    the stage (in ohm)
23 Avs = Av * Ris / (RS + Ris) //Voltage gain of the
    stage
24
25 // Result
26
27 printf("\n Voltage gain is %0.1f .\nInput
    resistance is %0.0f ohm.\nOutput resistance is
    %0.0f ohm.",Avs,Ris,Ros)

```

Scilab code Exa 25.5 Ai

```

1 clear //
2
3 // Variables

```

```

4
5 hie = 1.1 * 10**3 // hie (in
    ohm)
6 hre = 2.5 * 10**-4 //hre
7 hoe = 25.0 * 10**-6 //hoe (in
    mho)
8 RS = 10000.0 //Source
    resistance (in ohm)
9 hfe=50.0;beta=50.0;
10 rL = 1000.0 //ac.c load
    resistance (in ohm)
11 RB = 200.0 * 10**3 //Feedback
    resistor (in ohm)
12 RC = 5.0 * 10**3 //Collector
    resistance (in ohm)
13
14 // Calculation
15
16 rL = RC * RB / (RC + RB) //a.c. load
    resistance (in ohm)
17 Ai = hfe /(1 + hoe * rL) //Current
    gain
18 Ri = hie + hre * Ai * rL //Input
    resistance of the amplifier looking into the base
    (in ohm)
19 Av = Ai * rL / Ri //Voltage
    gain
20 RB1 = RB/(1 - (-17.4)) //
    Resistance (in ohm)
21 Ris = Ri * RB1 / (Ri + RB1) //Input
    resistance looking from source terminals (in ohm
    )
22 Avs = Av * Ris / (RS + Ris) //Voltage
    gain of the stage
23
24 // Result
25
26 printf("\n Ai is %0.2f \nAv is %0.2f \nAvs is %0

```

```
.1 f \nRi is %0.3 f kilo -ohm." ,Ai ,Av ,Avs ,Ri  
*10**-3)
```

Scilab code Exa 25.6 The value of input resistance

```
1 clear//  
2  
3 //Variables  
4  
5 hib = 28.0 //hib (in ohm)  
6 hfb = -0.98 //hfb  
7 hrb = 5.0 * 10**-4 //hrb  
8 hob = 0.34 * 10**-6 //hoh (in Siemen)  
9 rL = 1.2 * 10**3 //a.c. load resistance  
    (in ohm)  
10 RS = 0.0 //Source resistance (in  
    ohm)  
11  
12 //Calculation  
13  
14 Ai = -(hfb/(1 + hob * rL)) //Current gain  
15 Ri = hib + hrb * Ai * rL //Input resistance (in  
    ohm)  
16 dh = hib * hob - hrb * hfb //change in h  
17 Ro = (RS + hib)/(RS*hib + dh) //Output resistance (in  
    ohm)  
18 Av = Ai * rL / Ri //Voltage gain  
19  
20 //Result  
21  
22 printf("\n The value of input resistance is %0.1f  
    ohm.\nThe value of output resistance is %0.0f  
    kilo -ohm.\nThe value of current gain is %0.2f  
    .\nThe value of voltage gain is %0.0f .",Ri,Ro  
    *10**-3,Ai,Av)
```

Scilab code Exa 25.7 The value of input resistance of amplified stage

```
1 clear//  
2  
3 //Variables  
4  
5 hic = 2.0 * 10**3 //hic ( in ohm)  
6 hfc = -51.0 //hfe  
7 hrc = 1.0 //hrc  
8 hoc = 25.0 * 10**-6 //hoc ( in mho)  
9 rL=5.0*10**3;RE=5.0*10**3;  
10 RS = 1.0 * 10**3 //Source  
    resistance (in ohm)  
11 R1=10.0*10**3;R2=10.0*10**3;  
12  
13 //Calculation  
14  
15 Ai = -hfc / (1 + hoc * rL) //  
    Current gain  
16 Ri = hic + hrc * Ai * rL //Input  
    resistance (in ohm)  
17 Ris = (R1*R2*Ri)/(Ri*R1 + Ri*R2 + R1*R2) //Input  
    resistance of the amplified stage (in ohm)  
18 Ro = -(RS + hic)/hfc //Output  
    resistance (in ohm)  
19 Ros = Ro * RE / (Ro + RE) //Input  
    resistance of the amplified stage (in ohm)  
20 Ais = Ai * RS / (RS + Ris) //  
    Current gain of amplified stage  
21 Av = Ai * rL / Ri //  
    Voltage gain  
22 Avs = Av * Ris / (RS + Ris) //
```

```

    Voltage gain of amplified stage
23
24 // Result
25
26 printf("\n The value of input resistance of
           amplified stage is %0.0f ohm.\nThe value of
           output resistance of amplified stage is %0.f
           kilo-ohm.\nThe value of current gain of amplified
           stage is %0.1f .\nThe value of voltage gain of
           amplified stage is %0.3f .",Ris,abs(Ros),Ais,
           Avs)

```

Scilab code Exa 25.8 Input resistance of the stage

```

1 clear //
2
3 // Variables
4
5 hie = 1500.0                                     //hie (
      in ohm)
6 hfe = 50.0                                       //hfe
7 hre = 50.0 * 10**-4                               //hre
8 hoe = 20.0 * 10**-6                               //hoe
9 R1 = 20.0 * 10**3                                //
      Resistance (in ohm)
10 R2 = 10.0 * 10**3                                //
      Resistance (in ohm)
11 RC = 5.0 * 10**3                                 //
      Collector resistance (in ohm)
12 RE = 1.0 * 10**3                                 //
      Emitter resistance (in ohm)
13 RL = 10.0 * 10**3                                //Load
      resistance (in ohm)
14 RS = 0                                         //
      resistance (in ohm)

```

```

15
16 // Calculation
17
18 Ai = -hfe
19 rL = RC * RL / (RC + RL) // a . c .
   load resistance (in ohm)
20 Ri = hie // Input
   resistance (in ohm)
21 Ris = (R1*R2*Ri)/(Ri*R1 + Ri*R2 + R1*R2) // Input
   resistance of the amplified stage (in ohm)
22 Ro = 1 / hoe // Output
   resistance (in ohm)
23 Ros = Ro * rL / (Ro + rL) // Output
   resistance of the stage (in ohm)
24 Av = Ai * rL / Ri // 
   Voltage gain
25 Avs = Av * Ris / (RS + Ris) // 
   Voltage gain of the stage
26 Ais = Ai // 
   Current gain of the stage
27
28 // Result
29
30 printf("\n Input resistance of the stage is %0.2f
          kilo-ohm.\nOutput resistance of the stage is %0
          .1f kilo-ohm.\nVoltage gain of the stage is %0
          .0f .\nCurrent gain of the stage is %0.3f .",
          Ris*10**-3,Ros*10**-3,Avs,Ai)

```

Scilab code Exa 25.9 Input impedance

```

1 clear //
2
3 // Variables
4

```

```

5  RC = 12.0 * 10**3 // Collector
    resistance (in ohm)
6  RL = 4.7 * 10**3 // Load
    resistance (in ohm)
7  R1 = 33.0 * 10**3 // Resistance
    (in ohm)
8  R2 = 4.7 * 10**3 // Resistance
    (in ohm)
9  IC = 1.0 * 10**-3 // Collector
    current (in Ampere)
10 hiemin = 1.0 * 10**3 // hie
    minimum (in ohm)
11 hiemax = 5.0 * 10**3 // hie
    maximum (in ohm)
12 hfemin = 70.0 // Current
    gain minimum
13 hfemax = 350.0 // Current
    gain maximum
14
15 // Calculation
16
17 hie = (hiemin * hiemax)**0.5 // hie (in
    ohm)
18 hfe = (hfemin * hfemax)**0.5 // current
    gain
19 Ri = hie // input
    resistance (in ohm)
20 Ris = (R1*R2*Ri)/(Ri*R1+Ri*R2+R1*R2) // Input
    resistance of the amplified stage (in ohm)
21 Ai = hfe // Current
    gain of transistor
22 rL = RC * RL / (RC + RL) // a.c. load
    resistance (in ohm)
23 Avs=Ai*rL/Ri;Av=Ai*rL/Ri;
24
25 // Result
26
27 printf("\n Input impedance is %0.2f kilo-ohm.\\"
```

```
nOverall voltage gain is %0.1f .",Ris*10**-3,Avs  
)
```

Scilab code Exa 25.10 Input resistance of the circuit

```
1 clear//  
2  
3 //Variables  
4  
5 RB = 330.0 * 10**3 //Base  
    resistance (in ohm)  
6 RC = 2.7 * 10**3 //Collector  
    resistance (in ohm)  
7 hfe = 120.0 //current gain  
8 hie = 1.175 * 10**3 //hie (in ohm)  
9 hoe = 20 * 10**-6 //hoe (in  
    Ampere per volt)  
10  
11 //Calculation  
12  
13 Ri = hie //Input  
    resistance of transistor (in ohm)  
14 Ris = hie * RB /(hie + RB) //Input  
    resistance of the circuit (in ohm)  
15 Ro = 1 / hoe //Output  
    resistance of transistor (in ohm)  
16 Ros = Ro * RC / (Ro + RC) //Output  
    resistance of the circuit (in ohm)  
17 Ai = hfe //Current gain  
    of the circuit  
18 Avs = Ai * RC / Ri //Overall  
    voltage gain  
19  
20 //Result  
21
```

```
22 printf("\n Input resistance of the circuit is %0.2f  
kilo-ohm.\nOutput resistance of the circuit is  
%0.2f kilo-ohm.\nCurrent gain of the circuit is  
%0.3f .\nVoltage gain of the circuit is %0.1f  
. ",Ris*10**-3,Ros*10**-3,Ai,Avs)
```

Scilab code Exa 25.11 Value of hfb

```
1 clear//  
2  
3 // Variables  
4  
5 hfe = 50.0 // Current gain  
6  
7 // Calculation  
8  
9 hfb = -hfe / (1 + hfe) //hfb  
10 hfc = -(1 + hfe) //hfc  
11  
12 // Result  
13  
14 printf("\n Value of hfb = %0.2f .\nValue of hfc =  
%0.3f .",hfb,hfc)
```

Scilab code Exa 25.12 Current gain

```
1 clear//  
2  
3 // Variables  
4  
5 hie = 1100.0 //hie (in ohm)  
6 hre = 2.5 * 10**-4 //hre  
7 hfe = 50.0 // Current gain
```

```

8  hoe = 24.0 * 10**-6           //hoe ( in
    Ampere per volt )
9  rL=10.0*10***3;RL=10.0*10***3;
10 RS = 1.0 * 10***3           //Source
    resistance ( in ohm )
11
12 //Calculation
13
14 hic = hie                   //hic ( in ohm )
15 hrc = (1 - hre)             //hrc
16 hfc = -(1 + hfe)            //hfc
17 Ai = -(hfc/(1 + hoe * rL)) //Current gain
18 Ri = hic + hrc * Ai * rL   //Input
    resistance ( in ohm )
19 Av = Ai * rL / Ri          //Voltage gain
20
21 // Result
22
23 printf("\n Current gain is %0.1f .\nInput
    resistance is %0.1f kilo-ohm.\nVoltage gain is
    %0.3f .",Ai,Ri*10***-3,Av)

```

Chapter 26

Multistage BJT Amplifiers

Scilab code Exa 26.1 Overall voltage gain

```
1 clear//  
2  
3 // Variables  
4  
5 Av1 = 10.0                      //Voltage gain1  
6 Av2 = 20.0                      //Voltage gain2  
7 Av3 = 40.0                      //Voltage gain3  
8  
9 // Calculation  
10  
11 Av = Av1 * Av2 * Av3          //Voltage gain  
12 Gv1 = 20 * log10(Av1)          //dB voltage  
    gain1  
13 Gv2 = 20 * log10(Av2)          //dB voltage  
    gain2  
14 Gv3 = 20 * log10(Av3)          //dB voltage  
    gain3  
15 Gv = Gv1 + Gv2 + Gv3          //dB voltage  
    gain  
16  
17 // Result
```

```
18
19 printf("\n Overall voltage gain is %0.3f .\nTotal
      dB voltage gain is %0.0f dB.",Av,Gv)
```

Scilab code Exa 26.2 Overall voltage gain

```
1 clear//
2
3 // Variables
4
5 n = 3                      //Number of amplified
                                stages
6 Vin1 = 0.05                 //Input to first stage (
                                in volts peak-to-peak)
7 Vout3 = 150.0                //Output of final stage
                                (in volts peak-to-peak)
8 Av1 = 20.0                  //Voltage gain of first
                                stage
9 Vin3 = 15.0                 //Input of final stage (
                                in volts peak-to-peak)
10
11 // Calculation
12
13 Av = Vout3 / Vin1          //Overall voltage gain
14 Av3 = Vout3 / Vin3          //Voltage gain of third
                                stage
15 Av2 = Av / (Av1 * Av3)      //Voltage gain of second
                                stage
16 Vin2 = Vin3 / Av2          //Input voltage gain of
                                second stage
17
18 // Result
19
20 printf("\n Overall voltage gain is %0.3f .\nVoltage
      gain of 2nd and 3rd stage is %0.3f and %0.3f
```

```
.\\nInput voltage of the second stage is %0.3f  
Vpk-pk .” ,Av ,Av2 ,Av3 ,Vin2)
```

Scilab code Exa 26.3 Input resistance of first and scond stage

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 10.0 //Source voltage (in volts)  
6 RC = 5.0 * 10**3 //Collector resistance (in ohm)  
7 RB = 1.0 * 10**6 //Base resistance (in ohm)  
8 RE = 1.0 * 10**3 //Emitter resistance (in ohm)  
9 RL = 10.0 * 10**3 //Load resistance (in ohm)  
10 beta1=100.0;beta2=100.0;  
11  
12 // Calculation  
13  
14 IE = VCC /(RE + RB/beta1) //Emitter current (in Ampere)  
15 r1e = 25.0/IE * 10**-3 //a.c. emitter diode resistance (in ohm)  
16 Ri1 = beta1 * r1e //Input resistance of first stage (in ohm)  
17 Ri2 = beta2 * r1e //Input resistance of second stage (in ohm)  
18 Ro1 = RC * Ri2 / (RC + Ri2) //Output resistance of first stage (in ohm)  
19 Ro2 = RC * RL / (RC + RL) //Output resitance of second stage (in ohm)
```

```

20 Av1 = Ro1 / r1e           // Voltage gain of
    first stage
21 Av2 = Ro2 / r1e           // Voltage gain of
    second stage
22 Av = Av1 * Av2           // Overall voltage
    gain
23 Gv = 20 * log10(Av)      // Overall dB
    voltage gain
24
25 // Result
26
27 printf("\n Input resistance of first and scond stage
        is %0.0f ohm and %0.0f ohm.\nOutput
        resistance of first and second stage is %0.1f
        ohm and %0.1f ohm.\nVoltage gain of first and
        second stage is %0.0f and %0.1f .\nOverall
        voltage gain and dB voltage gain is %0.0f and
        %0.1f dB.",Ri1,Ri2,Ro1,Ro2,Av1,Av2,Av,Gv)

```

Scilab code Exa 26.4 Voltage gain of stage one and two

```

1 clear //
2
3 // Variables
4
5 VCC = 15.0                  // Source voltage (
    in volts)
6 RC = 3.3 * 10**3            // Collector
    resistance (in ohm)
7 RE = 1.0 * 10**3            // Emitter
    resistance (in ohm)
8 RL = 10.0 * 10**3          // Load resistance
    (in ohm)
9 R1 = 33.0 * 10**3          // Resistance (in
    ohm)

```

```

10 R2 = 8.2 * 10**3 //Resistance (in
ohm)
11 beta1=100.0;beta2=100.0;
12 VBE = 0.7 //Emitter-to-base
voltage (in volts)
13
14 //Calculation
15
16 Vth = VCC * R2 / (R1 + R2) //Thevenin's
voltage (in volts)
17 Rth = R1 * R2 / (R1 + R2) //Thevenin's
equivalent resistance (in ohm)
18 IE = (Vth - VBE)/(RE + Rth/beta1) //Emitter current
(in Ampere)
19 r1e = 25.0/IE * 10**-3 //a.c. emitter
resistance (in ohm)
20 Ri2 = beta1 * r1e //Input resistance
of second stage (in ohm)
21 Ro1 = RC * Ri2 / (RC + Ri2) //Output
resistance of first stage (in ohm)
22 Ro2 = RC * RL /(RC + RL) //Output
resistance of second stage (in ohm)
23 Av1 = Ro1 / r1e //Voltage gain of
the first stage
24 Av2 = Ro2 / r1e //Voltage gain of
second stage
25 Av = Av1 * Av2 //Overall voltage
gain
26 Gv = 20 * log10(Av) //Overall voltage
(in decibels)
27
28 //Result
29
30 printf("\n Voltage gain of stage one and two are as
follows %0.2f and %0.2f .\nOverall voltage
gain is %0.0f .\nOverall voltage gain in
decibels is %0.1f dB.",Av1,Av2,Av,Gv)

```

Scilab code Exa 26.5 Voltage gain of first stage

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 10.0                                //Source voltage (in volts)  
6 RB = 470.0 * 10**3                          //Base resistance (in ohm)  
7 RE = 1.0 * 10**3                            //Emitter resistance (in ohm)  
8 RL = 1.0 * 10**3                            //Load resistance (in ohm)  
9 a = 4.0                                     //Turn's ratio  
10 beta1=50.0;beta2=50.0;  
11 VBE = 0.7                                   //Emitter-to-base voltage (in volts)  
12  
13 // Calculation  
14  
15 IE = VCC/ (RE + RB/beta1)                  //Emitter current (in Ampere)  
16 r1e = 25.0 / IE * 10**-3                   //a.c. emitter diode resistance (in ohm)  
17 Ri1 = RB*beta1*r1e/(RB+beta1*r1e)          //Input resistance of first stage (in ohm)  
18 Ri2 = RB*beta2*r1e/(RB+beta2*r1e)          //Input resistance of Second stage (in ohm)  
19 R1i2 = a**2 * Ri2                         //Input resistance of the second stage transformed to primary side (in ohm)  
20 Ro1 = R1i2                                  //Output resistance of second stage (in ohm)
```

```

21 R1o2 = a**2 * RL           //Output
    resistance of the second stage transformed to the
    primary side (in ohm)
22 Av1 = Ro1/r1e             //Voltage gain of
    first stage
23 Av2 = R1o2/r1e           //Voltage gain of
    second stage
24 Av = Av1 * Av2           //Overall voltage
    gain
25 Gv = 20 * log10(Av)      //Overall voltage
    gain (in decibels)
26
27 // Result
28
29 printf("\n Voltage gain of first stage is %0.1f .\ \
nVoltage gain of second stage is %0.1f .\ \
nOverall voltage gain is %0.0f .\ nOverall \
voltage gain in decibels is %0.0f dB.",Av1,Av2,
Av,Gv)

```

Scilab code Exa 26.6 Voltage gain of first stage

```

1 clear //
2
3 // Variables
4
5 VCC = 12.0                  //Source voltage
    (in volts)
6 R1 = 100.0 * 10**3          //Resistance (in
    ohm)
7 R2 = 20.0 * 10**3           //Resistance (in
    ohm)
8 R3 = 10.0 * 10**3           //Resistance (in
    ohm)
9 R4 = 2.0 * 10**3            //Resistance (in

```

```

        ohm)
10 R5 = 10.0 * 10**3 //Resistance (in
        ohm)
11 R6 = 2.0 * 10**3 //Resistance (in
        ohm)
12 beta1=100.0;beta2=100.0;
13
14 // Calculation
15
16 Vth = VCC * R2 / (R1 + R2) //Thevenin's
        voltage (in volts)
17 IE1 = Vth / R4 //Emitter current
        (in Ampere)
18 r1e = 25.0 / IE1 * 10**-3 //a.c. emitter
        diode resistance (in ohm)
19 VR6 = VCC - IE1 * R3 //Voltage across
        resistance6 (in volts)
20 IE2 = VR6 / R6 //Emitter
        current2 (in Ampere)
21 r1e2 = 25.0 / IE2 * 10**-3 //a.c. emitter
        diode resistance2 (in ohm)
22 Ri2 = beta2*(r1e2 + R6) //Input
        resistance of second stage (in ohm)
23 Ro1 = R3 * Ri2 /(R3 + Ri2) //Output
        resistance of first stage (in ohm)
24 Ro2 = R5 //Output
        resistance of second stage (in ohm)
25 Av1 = Ro1/(r1e + R4) //Voltage gain of
        first stage
26 Av2 = Ro2/(r1e2 + R6) //Voltage gain of
        second stage
27 Av = Av1 * Av2 //Overall voltage
        gain
28
29 // Result
30
31 printf("\n Voltage gain of first stage is %0.1f .\\" nVoltage gain of second stage is %0.1f .\"

```

nOverall voltage gain is %0.2f . ” ,Av1 ,Av2 ,Av)

Scilab code Exa 26.7 Overall voltage gain

```
1 clear//  
2  
3 //Variables  
4  
5 VCC = 10.0 //Source voltage  
    (in volts)  
6 R1 = 800.0 //Resistance (in  
    ohm)  
7 R2 = 200.0 //Resistance (in  
    ohm)  
8 R3 = 600.0 //Resistance (in  
    ohm)  
9 R4 = 200.0 //Resistance (in  
    ohm)  
10 R5 = 100.0 //Resistance (in  
    ohm)  
11 R6 = 1000.0 //Resistance (in  
    ohm)  
12 beta1=100.0;beta2=100.0;  
13 VBE = 0.7 //Emitter-to-  
    base voltage (in volts)  
14  
15 //Calculation  
16  
17 VR2 = VCC * (R2 / (R1 + R2)) //Voltage across  
    resistance2 (in volts)  
18 IE1 = (VR2 - VBE)/R2 //Emitter  
    current of Q1 transistor (in Ampere)  
19 IC1 = IE1 //Collector  
    current of Q1 transistor (in Ampere)  
20 VC1 = VCC - IC1 * R3 //Voltage at the
```

```

        collector of Q1 transistor (in volts)
21 VE1 = IE1 * R4                                //Voltage at the
        emitter of Q1 transistor (in volts)
22 VCE1 = VC1 - VE1                            //Collector-to-
        emitter voltage of Q1 transistor (in volts)
23 VE2 = VC1 - (-VBE)                          //Voltage at the
        emitter of Q2 transistor (in volts)
24 IE2 = (VCC - VE2)/R6                         //Emitter
        current of Q2 transistor (in Ampere)
25 IC2 = IE2                                    //Collector-
        current of Q2 transistor (in Ampere)
26 VC2 = IC2 * R5                             //Voltage at the
        collector of Q2 transistor (in volts)
27 VCE2 = VC2 - VE2                           //Collector-to-
        emitter voltage of Q2 transistor (in volts)
28
29 r1e1 = 25.0 / IE1 * 10**-3                  //a.c. emitter
        diode resistance of Q1 transistor (in ohm)
30 r1e2 = 25.0 / IE2 * 10**-3                  //a.c. emitter
        diode resistance of Q2 transistor (in ohm)
31 Ri2 = beta2 * (r1e2 + R6)                   //Input
        resistance of second stage (in ohm)
32 Ro1 = R3 * Ri2 / (R3 + Ri2)                 //Output
        resistance of first stage (in ohm)
33 Av1 = Ro1 / (r1e1 + R4)                     //Voltage gain
        of first stage
34 Av2 = 1.0                                     //Voltage gain
        of second stage
35 Av = Av1 * Av2                               //Overall
        voltage gain
36
37 // Result
38
39 printf("\n Emitter current of Q1 transistor is %0.3
        f mA.\nCollector current of Q1 transistor is %0
        .3 f mA.\nEmitter current of Q2 transistor is %0
        .3 f mA.\nCollecotr-current of Q2 transistor is
        %0.3 f mA.",IE1*10**3,IC1*10**3,IE2*10**3,IC2

```

```

*10**3)
40 printf("\n Collector-to-emitter voltage of Q1
        transistor is %0.3f v.\nCollector-to-emitter
        voltage of Q2 transistor is %0.3f .",VCE1,VCE2)
41 printf("\n Overall voltage gain is %0.2f .",Av)

```

Scilab code Exa 26.8 Overall voltage gain

```

1 clear//
2
3 // Variables
4
5 VCC = 10.0                                //Source voltage (
    in volts)
6 RE = 1.5 * 10**3                            //Emitter
    resistance (in ohm)
7 R1 = 30.0 * 10**3                           //Resistance (in
    ohm)
8 R2 = 20.0 * 10**3                           //Resistance (in
    ohm)
9 beta1 = 150.0                               //Common emitter
    current gain
10 beta2 = 100.0                               //Common emitter
    current gain
11 VBE = 0.7                                  //Emitter-to-base
    voltage (in volts)
12
13 // Calculation
14
15 Ai = beta1 * beta2                         //Overall current
    gain of transistor
16 VR2 = VCC * R2/(R1 + R2)                   //Voltage across
    resistor2 (in volts)
17 VB2 = VR2 - VBE                            //Voltage at the
    base of Q2 (in volts)

```

```

18 VE2 = VB2 - VBE                         // Voltage at the
                                             emitter of Q2 (in volts)
19 IE2 = VE2 / RE                           // Emitter current
                                             of Q2 (in Ampere)
20 r1e2 = 25.0/IE2 * 10**-3                 // a.c. emitter
                                             diode resistance of Q2 (in ohm)
21 IB2 = IE2 / beta2                        // Base current of
                                             Q2 (in Ampere)
22 IE1 = IB2                               // Emitter current
                                             of Q2
23 r1e1 = 25.0/IE1 * 10**-3                 // a.c. emitter
                                             diode resistance of Q1 (in ohm)
24 Ri1 = R1 * R2/(R1 + R2)                  // Total input
                                             resistance (in ohm)
25 Av = RE/(r1e1/beta2 + r1e2 + RE)       // Overall voltage
                                             gain
26
27 // Result
28
29 printf("\n The overall current gain is %0.3f .",Ai)
30 printf("\n The a.c. emitter diode resistance of Q1
                                             transistor is %0.1f ohm.\nThe a.c. emitter
                                             diode resistance of Q2 transistor is %0.2f ohm.
                                             ",r1e1,r1e2)
31 printf("\n Total input resistance is %0.3f kilo-
                                             ohm.",Ri1 * 10**-3)
32 printf("\n Overall voltage gain is %0.2f .",Av)

```

Chapter 27

Power Amplifiers

Scilab code Exa 27.2 Overall compliance PP of the amplifier

```
1 clear//  
2  
3 // Variables  
4  
5 VCC = 20.0 //Source voltage (in volts)  
6 R1 = 10.0 //Resistance (in kilo-ohm)  
7 R2 = 1.8 //Resistance (in kilo-ohm)  
8 RC = 620.0 * 10**-3 //Collector resistance (in kilo-ohm)  
9 RE = 200.0 * 10**-3 //Emitter resistance (in kilo-ohm)  
10 RL = 1.2 //Load resistance (in kilo-ohm)  
11 beta = 180.0 //Common emitter current gain  
12 VBE = 0.7 //Emitter-to-Base voltage (in volts)  
13
```

```

14 // Calculation
15
16 VB = VCC * (R2 / (R1 + R2))           // Voltage drop
   across R2 (in volts)
17 VE = VB - VBE                         // Voltage at the
   emitter (in volts)
18 IE = VE / RE                          // Emitter current
   (in milli-Ampere)
19 IC = IE                               // Collector
   current (in milli-Ampere)
20 VCE = VCC - IE*(RC + RE)             // Collector-to-
   emitter voltage (in volts)
21 ICEQ = IC                            // Collector
   current at Q (in milli-Ampere)
22 VCEQ = VCE                           // Collector-to-
   emitter voltage at Q (in volts)
23 rL = RC * RL/(RC + RL)              // a.c. load
   resistance (in kilo-ohm)
24 PP = 2 * ICEQ * rL                  // Compliance of
   the amplifier (in volts)
25
26 // Result
27
28 printf("\n Overall compliance (PP) of the amplifier
   is %0.2f V.", PP)

```

Scilab code Exa 27.3 Voltage gain

```

1 clear //
2
3 // Variables
4
5 r1e = 8.0                                // a.c. load
   resistance (in ohm)
6 RC = 220.0                                 // Collector

```

```

    resistance (in ohm)
7 RE = 47.0                                // Emitter resistance
     (in ohm)
8 R1 = 4.7 * 10**3                          // Resistance (in ohm
     )
9 R2 = 470.0                                // Resistance (in ohm
     )
10 beta = 50.0                               //Common emitter
     current gain
11
12 // Calculation
13
14 rL = RC                                    //Load resistance (
     in ohm)
15 Av = rL / r1e                             //Voltage gain
16 Ai = beta                                 //Current gain
17 Ap = Av * Ai                            //Power gain
18
19 // Result
20
21 printf("\n Voltage gain is %0.3f and Power gain is
     %0.3f ." ,Av ,Ap)

```

Scilab code Exa 27.4 Collector efficiency

```

1 clear //
2
3 // Variables
4
5 Ptrdc = 20.0                                //dc Power (in
     watt)
6 Poac = 5.0                                   //ac Power (in
     watt)
7
8 // Calculation

```

```

9
10 ne = Poac / Ptrdc          // Collector
   efficiency
11 P = Ptrdc                  // Power rating
   of the transistor
12
13 // Result
14
15 printf("\n Collector efficiency is %0.3f percentage
   .\nPower rating of the transistor is %0.3f W." ,
   ne*100 , P)

```

Scilab code Exa 27.5 The a c power output

```

1 clear //
2
3 // Variables
4
5 Pcdc = 10.0          //dc power (in watt)
6 ne = 0.32            //efficiency
7
8 // Calculation
9
10 Poac = ne * Pcdc / (1 - ne)    //a.c. power output (
   in watt)
11
12 // Result
13
14 printf("\n The a.c. power output is %0.1f W." , Poac
)

```

Scilab code Exa 27.6 Total power within the circuit

```

1 clear//
2
3 //Variables
4
5 nc = 0.5                                //Efficiency
6 VCC = 24.0                                 //Source voltage (in
                                              volts)
7 Poac = 3.5                                 //a.c. power output (
                                              in watt)
8
9 //Calculation
10
11 Ptrdc = Poac / nc                         //dc power (in watt)
12 Pcdc = Ptrdc - Poac                      //Power dissipated as
                                              heat (in watt)
13
14 //Result
15
16 printf("\n Total power within the circuit is %0.3f
          W.\nThe power Pcdc = %0.3f W is dissipated in
          the form of heat within the transistor collector
          region.",Ptrdc,Pcdc)

```

Scilab code Exa 27.7 Collector efficiency

```

1 clear//
2
3 //Variables
4
5 VCC = 20.0                                  //Supply voltage (
                                              in volts)
6 VCEQ = 10.0                                 //Collector-to-
                                              emitter voltage (in volts)
7 ICQ = 600.0 * 10**-3                        //Collector current
                                              (in Ampere)

```

```

8 RL = 16.0                                //Load resistance (
    in ohm)
9 Ip = 300.0 * 10**-3                      //Output current
    variation (in Ampere)
10
11 // Calculation
12
13 Pindc = VCC * ICQ                       //dc power supplied
    (in watt)
14 PRLdc = ICQ**2 * RL                      //dc power consumed
    by load resistor (in watt)
15 I = Ip / 2**0.5                           //r.m.s. value of
    Collector current (in Ampere)
16 Poac = I**2 * RL                          //a.c. power across
    load resistor (in ohm)
17 Ptrdc = Pindc - PRLdc                     //dc power
    delivered to transistor (in watt)
18 Pcdc = Ptrdc - Poac                      //dc power wasted
    in transistor collector (in watt)
19 no = Poac / Pindc                        //Overall
    efficiency
20 nc = Poac / Ptrdc                        //Collector
    efficiency
21
22 // Result
23
24 printf("\n Power supplied by the d.c. source to the
    amplifier circuit is %0.3f W.",Pindc)
25 printf("\n D.C. power consumed by the load resistor
    is %0.3f W.",PRLdc)
26 printf("\n A.C. power developed across the load
    resistor is %0.3f W.",Poac)
27 printf("\n D.C. power delivered to the transistor is
    %0.3f W.",Ptrdc)
28 printf("\n D.C. power wasted in the transistor
    collector is %0.3f W.",Pcdc)
29 printf("\n Overall efficiency is %0.3f .",no)
30 printf("\n Collector efficiency is %0.1f percentage

```

```
. ” ,nc * 100)
```

Scilab code Exa 27.8 The effective resistance

```
1 clear//  
2  
3 //Variables  
4  
5 a = 15.0 //Turns ratio  
6 RL = 8.0 //Load resistance (in  
ohm)  
7  
8 //Calculation  
9  
10 R1L = a**2 * RL //Effective resistance  
(in ohm)  
11  
12 //Result  
13  
14 printf("\n The effective resistance is %0.3f kilo -  
ohm.",R1L * 10**-3)
```

Scilab code Exa 27.9 Turns ratio

```
1 clear//  
2  
3 //Variables  
4  
5 RL = 16.0 //Load resistance (in  
ohm)  
6 R1L = 10.0 * 10**3 //Effective resistance  
(in ohm)  
7
```

```

8 // Calculation
9
10 a = (R1L / RL)**0.5           //Turns ratio
11
12 // Result
13
14 printf("\n Turns ratio is %0.3f : 1.",a)

```

Scilab code Exa 27.10 The maximum power delivered to load

```

1 clear//
2
3 // Variables
4
5 RL = 8.0                      //Load resistance (in ohm)
6 a = 10.0                       //Turns ratio
7 ICQ = 500.0 * 10**-3          //Collector current (in Ampere)
8
9 // Calculation
10
11 R1L = a**2 * RL               //Effective load (in ohm)
12 Poac = 1.0/2* ICQ**2 * R1L   //Maximum power delivered (in watt)
13
14 // Result
15
16 printf("\n The maximum power delivered to load is %0.3f W.",Poac)

```

Scilab code Exa 27.11 Maximum undistorted ac output power

```

1 clear//
2
3 //Variables
4
5 Ptrdc = 100.0 * 10**-3           //Maximum collector
   dissipated power (in watt)
6 VCC = 10.0                      //Source voltage (
   in volts)
7 RL = 16.0                       //Load resistance (
   in ohm)
8 no=0.5; nc=0.5;
9
10 // Calculation
11
12 Poac = no * Ptrdc             //Maximum
   undistorted a.c. output power (in watt)
13 ICQ = 2 * Poac / VCC          //Quiescent
   collector current (in Ampere)
14 R1L = VCC / ICQ                // Effective load
   resistance (in ohm)
15 a = (R1L / RL)**0.5
16
17 // Result
18
19 printf("\n Maximum undistorted a.c. output power is
   %0.3f W.\nQuiescent collector current is %0.3f
   A.\nTransformer turns ratio is %0.0f .",Poac,
   ICQ,a)

```

Scilab code Exa 27.13 Power delivered to the load

```

1 clear//
2
3 //Variables
4

```

```

5 RL = 1.0 * 10**3 //Load resistance
    (in ohm)
6 IC = 10.0 * 10**-3 //Collector
    current (in Ampere)
7
8 // Calculation
9
10 PL = IC**2 * RL //Load power (in
    watt)
11
12 // Result
13
14 printf("\n Power delivered to the load is %0.3f W.
    ",PL)

```

Scilab code Exa 27.14 The power drawn from the source

```

1 clear //
2
3 // Variables
4
5 RL = 8.0 //Load resistance (in ohm
    )
6 VP = 16.0 //Peak output voltage (in
    volts)
7
8 // Calculation
9
10 P = VP**2 / (2 * RL) //Power drawn from the
    source (in watt)
11
12 // Result
13
14 printf("\n The power drawn from the source is %0.3f
    W.",P)

```

Scilab code Exa 27.15 Maximum power output

```
1 clear//  
2  
3 //Variables  
4  
5 Pcdc = 10.0          //Power rating of amplifier  
      (in watt)  
6 n = 0.785           //Maximum overall  
      efficiency  
7  
8 //Calculation  
9  
10 PT = 2 * Pcdc       //Total power dissipation  
      of two transistors (in watt)  
11 Poac = (PT * n) / (1-n) //Maximum power output (in  
      watt)  
12  
13 //Result  
14  
15 printf("\n Maximum power output is %0.2f W.",Poac)
```

Scilab code Exa 27.16 The d c input power

```
1 clear//  
2  
3 //Variables  
4  
5 no = 0.6            //efficiency  
6 Pcdc = 2.5          //Maximum collector  
      dissipation of each transistor (in watt)
```

```
7
8 // Calculation
9
10 PT = 2 * Pcdc           // Total power dissipation
   of two transistors (in watt)
11 Pindc = PT / (1 - no)    //dc input power (in watt)
12 Poac = no * Pindc       //ac output power (in watt)
13
14 // Result
15
16 printf("\n The d.c. input power is %0.3f W.\nThe a
   .c. output power is %0.3f W.",Pindc,Poac)
```

Chapter 28

Tuned Amplifiers

Scilab code Exa 28.1 The resonant frequency

```
1 clear//  
2  
3 // Variables  
4  
5 L = 150.0 * 10**-6          // Inductance (in Henry)  
6 C = 100.0 * 10**-12         // Capacitance (in Farad)  
7  
8 // Calculation  
9  
10 fo = 0.159 / (L * C)**0.5   // Resonant frequency (in  
    Hertz)  
11  
12 // Result  
13  
14 printf("\n The resonant frequency is %0.1f MHz." ,  
        fo * 10**-6)
```

Scilab code Exa 28.2 Resonant frequency

```

1 clear//
2
3 //Variables
4
5 L = 100.0 * 10**-6           //Inductance (in Henry)
6 C = 100.0 * 10**-12          //Capacitance (in Farad)
7 R = 5.0                      //Resistance (in ohm)
8
9 //Calculation
10
11 fo = 0.159 / (L * C)**0.5   //Resonant frequency (in
                                Hertz)
12 Zp = L / (C*R)              //Circuit impedance at
                                resonance (in ohm)
13
14 //Result
15
16 printf("\n Resonant frequency is %0.3f MHz.\n"
        "Circuit impedance at resonance is %0.3f kilo-
        ohm.", fo*10**-6, Zp*10**-3)

```

Scilab code Exa 28.3 Bandwidth of the circuit

```

1 clear//
2
3 //Variables
4
5 fo = 1.0 * 10**6             //Resonant frequency (in
                                Hertz)
6 Qo = 100.0                    //Quality factor
7
8 //Calculation
9
10 BW = fo / Qo                //Bandwidth (in Hertz)
11

```

```
12 // Result
13
14 printf("\n Bandwidth of the circuit is %0.3f kHz."
       ,BW * 10**-3)
```

Scilab code Exa 28.4 The Q factor

```
1 clear//
2
3 //Variables
4
5 fo = 1600.0 * 10**3           //Resonant frequency (in
                                Hertz)
6 BW = 10.0 * 10**3            //Bandwidth (in Hertz)
7
8 //Calculation
9
10 Qo = fo / BW                //Quality factor
11
12 //Result
13
14 printf("\n The Q-factor is %0.3f .",Qo)
```

Scilab code Exa 28.5 The Q factor

```
1 clear//
2
3 //Variables
4
5 fo = 2.0 * 10**6             //Resonant frequency (in
                                Hertz)
6 BW = 50.0 * 10**3            //Bandwidth (in Hertz)
7
```

```

8 // Calculation
9
10 Qo = fo / BW           // Quality factor
11
12 // Result
13
14 printf("\n The Q-factor is %0.3f .",Qo)

```

Scilab code Exa 28.6 The value of circuit impedance at resonance

```

1 clear//
2
3 // Variables
4
5 fo = 455.0 * 10**3          // Resonant frequency (in
                                Hertz)
6 BW = 10.0 * 10**3           // Bandwidth (in Hertz)
7 XL = 1255.0                 // Inductive reactance (in
                                ohm)
8
9 // Calculation
10
11 Qo = fo / BW               // Quality factor
12 R = XL / Qo                // Resistance (in ohm)
13 L = XL / (2*pi*fo)         // Inductance (in Henry)
14 C = 1 / (XL*2*pi*fo)       // Capacitance (in Farad)
15 Zp = L / (C*R)              // Circuit impedance (in
                                ohm)
16
17 // Result
18
19 printf("\n The value of circuit impedance at
resonance is %0.0f kilo-ohm.",Zp * 10**-3)

```

Chapter 29

Feedback Amplifiers

Scilab code Exa 29.1 The voltage gain of an amplifier with negative feedback

```
1 clear//  
2  
3 // Variables  
4  
5 Av = 400.0          //Voltage gain  
6 beta = 0.1          //feedback ratio  
7  
8 // Calculation  
9  
10 A1v = Av / (1 + beta * Av)      //Voltage gain with  
    negative feedback  
11  
12 // Result  
13  
14 printf("\n The voltage gain of an amplifier with  
    negative feedback is %0.2f .",A1v)
```

Scilab code Exa 29.2 The percentage of the negative feedback

```

1 clear//
2
3 //Variables
4
5 Av = 100.0           //Voltage gain
6 A1v = 20.0           //Voltage gain with
                      negative feedback
7
8 //Calculation
9
10 beta = (Av/A1v - 1) / Av      //feedback ratio
11
12 //Result
13
14 printf("\n The percentage of the negative feedback
          is %0.3f",beta * 100)

```

Scilab code Exa 29.3 The fraction of the output that

```

1 clear//
2
3 //Variables
4
5 Av = 1000.0          //Voltage gain
6 A1v = 10.0            //Voltage gain with
                      negative feedback
7
8 //Calculation
9
10 beta = (Av/A1v - 1) / Av      //feedback ratio
11
12 //Result
13
14 printf("\n The fraction of the output that is
          feedback to the input is %0.3f .",beta)

```

Scilab code Exa 29.4 The value of voltage gain without negative feedback

```
1 clear//  
2  
3 //Variables  
4  
5 V1o=12.5;Vo=12.5;  
6 Vin = 1.5 //Input voltage with  
    feedback (in volts)  
7 Vin = 0.25 //Input voltage  
    without feedback (in volts)  
8  
9 //Calculation  
10  
11 Av = Vo / Vin //Voltage gain  
    without negative feedback  
12 A1v = V1o / Vin //Voltage gain with  
    negative feedback  
13 beta = (Av/A1v - 1) / Av //feedback ratio  
14  
15 //Result  
16  
17 printf("\n The value of voltage gain without  
    negative feedback is %0.3f .\nThe value of  
    voltage gain with negative feedback is %0.2f .\\"  
    "The value of beta is %0.3f .",Av,A1v,beta)
```

Scilab code Exa 29.5 Value of feedback ratio

```
1 clear//  
2
```

```

3 // Variables
4
5 Av = 60.0                                // Voltage gain
6 A1v = 80.0                                // Voltage gain with
     negative feedback
7
8 // Calculation
9
10 beta = (1 - Av/A1v) / Av                // feedback ratio
11 beta1 = 1/Av                             // feedback ratio
     which causes oscillation
12
13 // Result
14
15 printf("\n Value of feedback ratio is %0.3f .\nThe
     percentage of feedback which causes oscillation
     is %0.1f percentage.",beta,beta1*100)

```

Scilab code Exa 29.6 The value of voltage gain without feedback

```

1 clear//
2
3 // Variables
4
5 A1v = 100.0                                // Voltage gain with
     negative feedback
6 Vin = 50.0 * 10**-3                         // Input voltage
     without feedback (in volts)
7 V1in = 0.6                                    // Input voltage
     with feedback (in volts)
8
9 // Calculation
10
11 V1o = A1v * V1in                          // Output voltage
     with feedback (in volts)

```

```

12 Vo = V1o                                //Output voltage
    without feedback (in volts)
13 Av = Vo / Vin                            //Voltage gain
    without feedback
14 beta = (Av/A1v - 1) / Av                //feedback ratio
15
16 //Result
17
18 printf("\n The value of voltage gain without
    feedback is %0.3f .\nThe value of voltage gain
    with feedback is %0.3f .",Av,A1v)

```

Scilab code Exa 29.7 The percentage change in closed loop gain

```

1 clear//
2
3 // Variables
4
5 Av = 800.0                                //Voltage
    gain
6 beta = 0.05                                //
    Feedback ratio
7 dAvbyAv = 20.0                             //
    Percentage change in open loop gain
8
9 // Calculation
10
11 dA1vbyA1v = 1 / (1 + beta*Av)*dAvbyAv    //
    Percentage change in closed loop gain
12
13 //Result
14
15 printf("\n The percentage change in closed loop gain
    is %0.1f percentage.",dA1vbyA1v)

```

Scilab code Exa 29.8 The value of Av

```
1 clear//  
2  
3 // Variables  
4  
5 A1v = 100.0 // Voltage  
   gain with feedback  
6 dA1vbyA1v = 0.01 // Percentage  
   change in closed loop gain  
7 dAvbyAv = 0.20 // Percentage  
   change in open loop gain  
8  
9 // Calculation  
10  
11 betamultAvplus1 = dAvbyAv/dA1vbyA1v // Product of  
   feedback ratio and voltage ratio plus one  
12 Av = A1v * betamultAvplus1 // Voltage  
   gain without feedback  
13 beta = betamultAvplus1 / Av // Feedback  
   ratio  
14  
15 // Result  
16  
17 printf("\n The value of Av is %0.3f .\nThe value of  
   beta is %0.3f ." ,Av ,beta)
```

Scilab code Exa 29.9 Amout of feedback required when BW is 1MHz

```
1 clear//  
2  
3 // Variables
```

```

4
5 Av = 100.0 // Voltage gain without
   feedback
6 BW = 200.0 * 10**3 // Bandwidth without
   feedback (in Hertz)
7 beta = 0.05 // Feedback ratio
8 BWn = 1.0 * 10**6 // New bandwidth
   without feedback (in Hertz)
9
10 // Calculation
11
12 BW1 = (1 + beta*Av) * BW // Bandwidth with
   feedback (in Hertz)
13 A1v = Av/(1 + beta*Av) // Voltage gain with
   feedback
14 beta1 = (BWn/BW - 1)/Av // Amount of feedback
   required
15
16 // Result
17
18 printf("\n The new bandwidth is %0.3f kHz.\nThe
   new gain is %0.1f .",BW1*10**-3,A1v)
19 printf("\n Amout of feedback required when BW = 1MHz
   is %0.3f percentage.",beta1 * 100)

```

Scilab code Exa 29.11 The value of input resistance with feedback

```

1 clear//
2
3 // Variables
4
5 Rin = 4.2 * 10**3 // Input
   resistance (in ohm)
6 Av = 220.0 // Voltage gain
   without feedback

```

```

7 beta = 0.01                                //Feedback
    ratio
8 f1 = 1.5 * 10**3                          //Cut off
    frequency without feedback (in Hertz)
9 f2 = 501.5 * 10**3                         //Cut off
    frequency with feedback (in Hertz)
10
11 // Calculation
12
13 R1i = (1 + beta * Av) * Rin           //Input
    resistance of feedback amplifier (in ohm)
14 f11 = f1 / (1 + beta * Av)            //New cut off
    frequency without feedback (in Hertz)
15 f21 = (1 + beta * Av) * f2            //New cut off
    frequency with feedback (in Hertz)
16
17 // Result
18
19 printf("\n The value of input resistance with
    feedback is %0.3f kilo-ohm.\nNew cut off
    frequency without feedback is %0.0f Hz.\nNew
    cut off frequency with feedback is %0.3f kHz."
    ,R1i*10**-3,f11,f21*10**-3)

```

Scilab code Exa 29.14 Voltage gain with feedback

```

1 clear //
2
3 // Variables
4
5 Av = 300.0                                //Voltage gain without
    feedback
6 Ri = 1.5 * 10**3                           //Input resistance (in
    ohm)
7 Ro = 50.0 * 10**3                          //Output resistance (

```

```

    in ohm)
8 beta = 1.0/15.0           // feedback ratio
9
10 // Calculation
11
12 A1v = Av/ (1 + beta*Av)   // Voltage gain with
    feedback
13 R1i = (1 + beta* Av)* Ri // Input resistance
    with feedback (in ohm)
14 R1o = Ro/(1 + beta * Av) // Output resistance
    with feedback (in ohm)
15
16 // Result
17
18 printf("\n Voltage gain with feedback is %0.1f .\n"
        "Input resistance with feedback is %0.3f kilo-
        ohm.\nOutput resistance with feedback is %0.1f
        kilo -ohm.",A1v,R1i*10**-3,R1o*10**-3)

```

Scilab code Exa 29.15 Voltage gain without feedback

```

1 clear //
2
3 // Variables
4
5 hfe = 100.0                  // hfe
6 hie = 2.0 * 10**3             // hie (in
    ohm)
7 Re1 = 100.0                  // Emitter
    resistance (in ohm)
8 R1 = 15.0 * 10**3             //
    Resistance (in ohm)
9 R2 = 5.6 * 10**3              //
    Resistance (in ohm)
10 Rc = 470.0                   // Collector

```

```

    resistance (in ohm)
11
12 // Calculation
13
14 Ai = hfe                                // Current
     gain
15 Av = Ai * Rc / hie                      // Voltage
     gain
16 Ri = (R1*R2*hie)/(R1*R2+R2*hie+R1*hie) // Input
     resistance (in ohm)
17 beta = Re1 / Rc                          // feedback
     ratio
18 A1v = Av / (1 + beta * Av)               // Voltage
     ratio with feedback
19 R1i = Ri*(1 + beta * Av)                 // Input
     resistance with feedback (in ohm)
20
21 // Result
22
23 printf("\n Voltage gain without feedback is %0.3f
         .\nInput resistance without feedback is %0.0f
         kilo-ohm.\nVoltage gain with feedback is %0.2f
         .\nInput resistance with feedback is %0.1f kilo
         -ohm.",Av,Ri,A1v,R1i)

```

Scilab code Exa 29.16 Voltage gain with feedback

```

1 clear //
2
3 // Variables
4
5 hfe = 99.0                                  // hfe
6 hie = 2.0 * 10**3                            // hie (in ohm
8
7 Rc = 22.0 * 10**3                           // Load

```

```

        resistor of frist stage (in ohm)
8 R4 = 100.0                                //Emitter
        resistance of first stage (in ohm)
9 R1 = 220.0 * 10**3                         //Biasing
        resistor of second stage (in ohm)
10 R2 = 22.0 * 10**3                          //Biasing
        resistor of second stage (in ohm)
11 R1c = 4.7 * 10**3                           //Load
        resistance of second stage (in ohm)
12 R3 = 7.8 * 10**3                            //Feedback
        resistor from collector of second stage to
        emitter of first stage (in ohm)

13
14 //Calculation
15
16 Ri = hie                                     //Input
        resistance of first stage (in ohm)
17 Ro1 = (1/Rc + 1/R1 + 1/R2 + 1/hie)**-1    //Output
        resistance of first stage (in ohm)
18 Ri2 = hie                                     //Input
        resistance of second stage (in ohm)
19 Ro2 = R1c * (R3 + R4)/(R1c + R3 + R4)     //Output
        resistance of second stage (in ohm)
20 Av1 = hfe * Ro1 / hie                        //Voltage
        gain of first stage
21 Av2 = hfe * Ro2 / hie                        //Voltage
        gain of second stage
22 Av = Av1 * Av2                               //Overall
        voltage gain without feedback
23 beta = R4 / (R3 + R4)                        //Feedback
        ratio
24 Ri1 = Ri*(1 + beta*Av)                      //Input
        resistance with feedback (in ohm)
25 R1o2 = Ro2 / (1 + beta * Av)                 //Output
        resistance with feedback (in ohm)
26 A1v = Av / (1 + beta * Av)                  //Overall
        voltage gain with feedback
27

```

```
28 // Result
29
30 printf("\n Voltage gain without feedback is %0.1f
.\\nInput resistance of first stage without
feedback is %0.3f kilo-ohm.\\nInput resistance
of second stage without feedback is %0.3f kilo-
ohm.\\nOutput resistance of first stage without
feedback is %0.2f kilo-ohm.\\nOutput resistance
of second stage without feedback is %0.2f kilo-
ohm .",Av,Ri*10**-3,Ri2*10**-3,Ro1*10**-3,Ro2
*10**-3)
31 printf("\n Voltage gain with feedback is %0.1f .\\
nInput resistance with feedback is %0.2f kilo-
ohm.\\nOutput resistance with feedback is %0.3f
kilo-ohm.",A1v,Ri1*10**-3,R1o2*10**-3)
```

Chapter 30

Field Effect Transistor Amplifiers

Scilab code Exa 30.1 Value of drain to source voltage

```
1 clear//  
2  
3 // Variables  
4  
5 ID = 5.0 * 10**-3           // Drain current (in  
     Ampere)  
6 VDD = 10.0                  // Voltage (in volts)  
7 RD = 1.0 * 10**3            // Drain resistance (  
     in ohm)  
8 RS = 500.0                  // Source resistance (  
     in ohm)  
9  
10 // Calculation  
11  
12 VS = ID * RS             // Source voltage (in  
     volts)  
13 VD = VDD - ID * RD        // Drain voltage (in  
     volts)  
14 VDS = VD - VS            // Drain-Source
```

```

    voltage (in volts)
15 VGS = -VS                                //Gate-to-source
    voltage (in volts)
16
17 // Result
18
19 printf("\n Value of drain-to-source voltage is %0.3
f V.\nValue of Gate-to-source voltage is %0.3f
V." ,VDS ,VGS)

```

Scilab code Exa 30.3 Value of RS

```

1 clear //
2
3 // Variables
4
5 ID = 1.5 * 10**-3                         //Drain current (
    in Ampere)
6 IDSS = 5.0 * 10**-3                         //Drain-to-source
    current (in Ampere)
7 Vp = -2.0                                     //Voltage (in
    volts)
8 VDS = 10.0                                    //Drain-to-source
    voltage (in volts)
9 VDD = 20.0                                     //Supply voltage
    (in volts)
10
11 // Calculation
12
13 VGS = (1 - ID/IDSS)*Vp                      //Gate-to-Source
    voltage (in volts)
14 VS = -VGS                                     //Source voltage
    (in volts)
15 RS = VS / ID                                  //Source
    resistance (in ohm)

```

```

16 RD = (VDD - VDS) / ID - RS           // Drain
      resistance (in ohm)
17
18 // Result
19
20 printf("\n Value of RS is %0.0f ohm.\nValue of RD
      is %0.1f kilo-ohm.",RS,RD*10**-3)

```

Scilab code Exa 30.5 Value of RD

```

1 clear//
2
3 // Variables
4
5 VP=5.0; VGSoff=5.0;
6 IDSS = 12.0 * 10**-3                  // Drain-to-
      source current (in Ampere)
7 VDD = 12.0                            // Drain voltage
      (in volts)
8 ID = 4.0 * 10**-3                    // Drain current
      (in Ampere)
9 VDS = 6.0                            // Drain-to-
      source voltage (in volts)
10
11 // Calculation
12
13 VGS = (1 - (ID / IDSS)**0.5)*VGSoff // Gate-to-source
      voltage (in volts)
14 VS = VGS                            // Source voltage
      (in volts)
15 RS = VS / ID                        // Source
      resistance (in ohm)
16 RD = (VDD - VDS) / ID                // Drain
      resistance (in ohm)
17

```

```

18 // Result
19
20 printf("\n Value of RD is %0.3f kilo-ohm.\nValue
      of RS is %0.0f ohm.", RD*10**-3, RS)

```

Scilab code Exa 30.6 Value of RD

```

1 clear //
2
3 // Variables
4
5 IDSS = 10.0 * 10**-3                      // Drain-to-
       source current (in Ampere)
6 VDD = 20.0                                     // Drain
       voltage (in volts)
7
8 // Calculation
9
10 IDQ = IDSS / 2                                // Drain
        current at Q point (in Ampere)
11 VDSQ = VDD / 2                                // Drain-to-
        source voltage at Q point (in volts)
12 VGS = -2.2                                     // Gate-to-
        source voltage (in volts)
13 ID = 5.0 * 10**-3                             // Drain
        current (in Ampere)
14 RD = (VDD - VDSQ) / ID                         // Drain
        resistance (in ohm)
15 VS = - VGS                                     // Source
        voltage (in volts)
16 RS = VS / ID                                   // Source
        resistance (in ohm)
17
18 // Result
19

```

```

20 printf("\n Operating point is ID = %0.3f mA and
      VDS = %0.3f V.",IDQ*10**3,VDSQ)
21 printf("\n Value of RD is %0.3f kilo-ohm and RS is
      %0.3f ohm.",RD*10**-3,RS)

```

Scilab code Exa 30.7 Value of VGS

```

1 clear //
2
3 // Variables
4
5 VDD = 20.0
      in volts)                                //Supply voltage (
6 RD = 2.5 * 10**3
      (in ohm)                                 //Drain resistance
7 RS = 1.5 * 10**3
      resistance (in ohm)                      //Source
8 R1 = 2.0 * 10**6
      ohm)                                     //Resistance (in
9 R2 = 250.0 * 10**3
      ohm)                                     //Resitance (in
10 ID = 4.0 * 10**-3
      in Ampere)                               //Drain current (
11
12 // Calculation
13
14 VG = VDD * R2 / (R1 + R2)
      volts)                                   //Gate voltage (in
15 VS = ID * RS
      in volts)                               //Source voltage (
16 VGS = VG - VS
      voltage (in volts)                     //Gate-to-source
17 VD = VDD - ID * RD
      in volts)                               //Drain voltage (
18

```

```
19 // Result
20
21 printf("\n Value of VGS is %0.1f V. and value of
      VDS is %0.3f V.", VGS, VD-VS)
```

Scilab code Exa 30.8 Voltage gain

```
1 clear//
2
3 //Variables
4
5 gm = 4.0 * 10**-3                      //
      Transconductance (in Siemen)
6 RD = 1.5 * 10**3                         //Drain
      resistance (in ohm)
7
8 // Calculation
9
10 Av = -gm * RD                           //Voltage
      gain
11
12 //Result
13
14 printf("\n Voltage gain is %0.3f .", Av)
```

Scilab code Exa 30.9 Voltage gain

```
1 clear//
2
3 //Variables
4
5 gm = 2.5 * 10**-3                      //
      Transconductance (in Ampere per volt)
```

```

6 rd = 500.0 * 10**3 // Resistance
    (in ohm)
7 RD = 10.0 * 10**3 // Load
    resistance (in ohm)
8
9 // Calculation
10
11 rL = RD * rd / (RD + rd) // a.c.
    equivalent resistance (in ohm)
12 Av = -gm * rL // Voltage
    gain
13
14 // Result
15
16 printf("\n Voltage gain is %0.1f .", Av)

```

Scilab code Exa 30.10 Input resistance

```

1 clear //
2
3 // Variables
4
5 gm = 2.0 * 10**-3 // Transconductance (in Ampere per volt)
6 rd = 40.0 * 10**3 // Resistance
    (in ohm)
7 RD = 20.0 * 10**3 // Drain
    resistance (in ohm)
8 RG = 100.0 * 10**6 // Gate
    resistance (in ohm)
9
10 // Calculation
11
12 rL = RD * rd / (RD + rd) // a.c.
    equivalent resistance (in ohm)

```

```

13 Av = -gm * rL // Voltage
    gain
14 R1i = RG //input
    resistance (in ohm)
15 R1o = rL //output
    resistance (in ohm)
16
17 // Result
18
19 printf("\n Voltage gain is %0.1f .",Av)
20 printf("\n Input resistance is %0.3f Mega-ohm.\ \
nOutput resistance is %0.1f kilo-ohm.",R1i
    *10**-6,R1o*10**-3)

```

Scilab code Exa 30.11 Voltage gain

```

1 clear //
2
3 //Variables
4
5 gm = 2.0 * 10**-3 // Transconductance (in Ampere per volt)
6 rd = 10.0 * 10**3 // Resistance (in ohm)
7 RD = 50.0 * 10**3 // Drain resistance (in ohm)
8
9 // Calculation
10
11 rL = RD * rd / (RD + rd) // a.c. equivalent resistance (in ohm)
12 Av = - gm * rL // Voltage gain
13
14 // Result

```

```
15
16 printf("\n Voltage gain is %0.2f .",Av)
```

Scilab code Exa 30.12 Voltage gain

```
1 clear//
2
3 // Variables
4
5 RD = 100.0 * 10**3                                // Drain
       resistance (in ohm)
6 gm = 1.6 * 10**-3                                 //
       Transconductance (in Ampere per volt)
7 rd = 44.0 * 10**3                                  //
       (in ohm)
8 Cgs = 3.0 * 10**-12                               //
       gate-to-source (in Farad)
9 Cds = 1.0 * 10**-12                               //
       drain-to-source (in Farad)
10 Cgd = 2.8 * 10**-12                              //
       gate-to-drain (in Farad)
11
12 // Calculation
13
14 rL = RD * rd / (RD + rd)                         //
       resistance (in ohm)
15 Av = -gm * rL                                     //
       gain
16
17 // Result
18
19 printf("\n Voltage gain is %0.1f ",Av)
```

Scilab code Exa 30.13 Output voltage

```
1 clear//  
2  
3 // Variables  
4  
5 gm = 4500.0 * 10**-6          //  
       Transconductance (in Ampere per volt)  
6 RD = 3.0 * 10**3              //Drain  
       resistance (in ohm)  
7 RL = 5.0 * 10**3              //Load  
       resistance (in ohm)  
8 Vin = 100.0 * 10**-3          //Input  
       voltage (in volts)  
9 ID = 2.0 * 10**-3             //Drain  
       current (in Ampere)  
10  
11 // Calculation  
12  
13 rL = RD * RL / (RD + RL)    //a.c. load  
       resistance (in ohm)  
14 vo = -gm * rL * Vin          //Output  
       voltage (in volts)  
15  
16 // Result  
17  
18 printf("\n Output voltage is %0.3f V.", vo)
```

Scilab code Exa 30.17 Voltage gain

```
1 clear//  
2  
3 // Variables  
4  
5 vin = 2.0 * 10**-3           //Input
```

```

        voltage (in volts)
6 gm = 5500.0 * 10**-6                                //
    Transconductance (in Siemen)
7 R1=1.0*10**6;R2=1.0*10**6;
8 RS = 5.0 * 10**3                                     // Source
    resistance (in ohm)
9 RL = 2.0 * 10**3                                     // Load
    resistance (in ohm)

10
11 // Calculation
12
13 Av = RS / (RS + 1/gm)                               // Voltage
    gain
14 R1i = R1 * R2 / (R1 + R2)                           // Input
    resistance (in ohm)
15 R1o = RS * 1/gm /(RS + 1/gm)                         // Output
    resistance (in ohm)
16 Vo = RL / (RL + R1o) * Av * vin                   // Output
    voltage (in volts)

17
18 // Result
19
20 printf("\n Voltage gain is %0.3f .\nInput
    resistance is %0.3f Mega-ohm.\nOutput
    resistance is %0.1f ohm.\nOutput voltage is %0
    .2f mV.",Av,R1i*10**-6,R1o,Vo*10**3)

```

Scilab code Exa 30.18 Amplifier voltage gain

```

1 clear//
2
3 // Variables
4
5 gm = 2500.0 * 10**-6                                //
    Transconductance (in Amper per volt)

```

```

6 RD = 10.0 * 10**3 // Drain
    resistance (in ohm)
7 RS = 2.0 * 10**3 // Source
    resistance (in ohm)
8
9 // Calculation
10
11 Av = gm * RD // Voltage
    gain
12 R1i = RS * 1/gm / (RS + 1/gm) // Input
    resistance (in ohm)
13
14 // Result
15
16 printf("\n Amplifier voltage gain is %0.3f .\nInput resistance is %0.0f ohm.",Av,R1i)

```

Scilab code Exa 30.19 Input resistance

```

1 clear //
2
3 // Variables
4
5 gmo = 5.0 * 10**-3 // Maximum
    transconductance (in Siemen)
6 RD = 1.0 * 10**3 // Drain
    resistance (in ohm)
7 RS = 200.0 // Source
    resistance (in ohm)
8 ID = 5.0 * 10**-3 // Drain
    current (in Ampere)
9
10 // Calculation
11
12 R1i = RS * 1/gmo / (RS + 1/gmo) // Input

```

```

    resistance (in ohm)
13 VS = ID * RS                                // Source
    voltage (in volts)
14 VGS = VS                                     // Gate-to-
    Source voltage (in volts)
15 IDSS = 2 * ID                                 // Supply
    current (in Ampere)
16 VGSoff = -2 * IDSS / ID                      // Gate-to-
    source cut off voltage (in volts)
17 gm = gmo * (1 - abs(VGS / VGSoff))          // /
    Transconductance (in Siemen)
18 Av = gm * RD                                  // Voltage
    gain
19
20 // Result
21
22 printf("\n Input resistance is %0.3f ohm.\n a . c .
    voltage gain is %0.3f .",R1i ,Av)

```

Chapter 31

Sinusoidal Oscillators

Scilab code Exa 31.1 Inductance

```
1 clear//  
2  
3 // Variables  
4  
5 fo = 22.0 * 10**3 //  
   Frequency (in Hertz)  
6 C = 2.0 * 10**-9 //  
   Capacitance (in Farad)  
7  
8 // Calculation  
9  
10 L = (0.159/fo)**2/C //  
    Inductance (in Henry)  
11  
12 // Result  
13  
14 printf("\n Inductance is %0.3f H.",L)
```

Scilab code Exa 31.2 It will work at frequency of

```

1 clear//
2
3 //Variables
4
5 fo = 2.2 * 10**6 //Frequency
   (in Hertz)
6
7 //Calculation
8
9 f1o = fo * 2**0.5 //New
   frequency (in Hertz)
10
11 //Result
12
13 printf("\n It will work at frequency of %0.2f MHz
   when capacitance is reduced by 50 percentage.", f1o * 10**-6)

```

Scilab code Exa 31.3 Frequency of oscillations

```

1 clear//
2
3 //Variables
4
5 C = 100.0 * 10**-12 //Capacitance (
   in Farad)
6 L1 = 30.0 * 10**-6 //Inductance1 (
   in Henry)
7 L2 = 1.0 * 10**-8 //Inductance2 (
   in Henry)
8
9 //Calculation
10
11 L = L1 + L2 //Net
   inductance (in Henry)

```

```

12 fo = 1/(2*pi*(L * C)**0.5)           // Frequency of
   oscillations (in Hertz)
13
14 // Result
15
16 printf("\n Frequency of oscillations is %0.1f ",fo
   *10**-6)

```

Scilab code Exa 31.4 Frequency of oscillations

```

1 clear//
2
3 // Variables
4
5 L1 = 1000.0 * 10**-6                  // Inductance1
   (in Henry)
6 L2 = 100.0 * 10**-6                   // Inductance2
   (in Henry)
7 M = 20.0 * 10**-6                     // Mutual
   Inductance (in Henry)
8 C = 20.0 * 10**-12                    // Capacitance
   (in Farad)
9
10 // Calculation
11
12 L = L1 + L2 + 2 * M                 // Net
   inductance (in Henry)
13 fo = 1/(2*pi*(L * C)**0.5)           // Frequency of
   oscillations (in Hertz)
14
15 // Result
16
17 printf("\n Frequency of oscillations is %0.3f ",fo
   *10**-6)

```

Scilab code Exa 31.5 Frequency of oscillations

```
1 clear//  
2  
3 // Variables  
4  
5 C = 1.0 * 10**-9 // Capacitance  
    (in Farad)  
6 L1 = 4.7 * 10**-3 // Inductance1  
    (in Henry)  
7 L2 = 47.0 * 10**-6 // Inductance2  
    (in Henry)  
8  
9 // Calculation  
10  
11 L = L1 + L2 // Net  
    inductance (in Henry)  
12 fo = 1/(2*pi*(L * C)**0.5) // Frequency of  
    oscillations (in Hertz)  
13  
14 // Result  
15  
16 printf("\n Frequency of oscillations is %0.2f ",fo  
    *10**-3)
```

Scilab code Exa 31.6 Range of capacitance required

```
1 clear//  
2  
3 // Variables  
4
```

```

5 L1 = 2.0 * 10**-3 //  

   Inductance1 (in Henry)  

6 L2 = 20.0 * 10**-6 //  

   Inductance2 (in Henry)  

7 fomin = 950.0 * 10**3 //  

   Frequency minimum (in Hertz)  

8 fomax = 2050.0 * 10**3 //  

   Frequency maximum (in Hertz)  

9  

10 // Calculation  

11  

12 L = L1 + L2 //Net  

   inductance (in Henry)  

13 C1 = 1.0/(4 * %pi**2*(L*fomin**2)) //Capacitance1  

   (in Farad)  

14 C2 = 1.0/(4 * %pi**2*(L*fomax**2)) //Capacitance2  

   (in Farad)  

15  

16 // Result  

17  

18 printf("\n Range of capacitance required is %0.2 f  

   pF and %0.1 f pF.", C2*10**12, C1*10**12)

```

Scilab code Exa 31.7 Capacitance required

```

1 clear//  

2  

3 // Variables  

4  

5 L1 = 0.1 * 10**-3 //  

   Inductance1 (in Henry)  

6 L2 = 10.0 * 10**-6 //  

   Inductance2 (in Henry)  

7 M = 20.0 * 10**-6 //Mutual  

   Inductance (in Hnery)

```

```

8 fo = 4110.0 * 10**3 //  

    Frequency (in Hertz)  

9  

10 // Calculation  

11  

12 L = L1 + L2 + 2*M //Net  

    inductance (in Henry)  

13 C = 1.0/(4 * %pi**2 * L*fo**2) // Capacitance  

    (in Farad)  

14 beta = L2 / L1 //Feedback  

    ratio  

15 Av = 1/beta // Voltage  

    gain  

16  

17 // Result  

18  

19 printf("\n Capacitance required is %0.4f pF.\n"  

    "nVoltage gain for sustained condition is %0.3f ."  

    ",C*10**12 ,Av)

```

Scilab code Exa 31.8 Required voltage gain

```

1 clear//  

2  

3 // Variables  

4  

5 C1 = 0.001 * 10**-6 //  

    Capacitance (in Farad)  

6 C2 = 0.01 * 10**-6 //  

    Capacitance (in Farad)  

7 L = 5.0 * 10**-6 //  

    Inductance (in Henry)  

8  

9 // Calculation  

10

```

```

11 Av = C2 / C1                                // Voltage
      gain
12 C = C1 * C2 / (C1 + C2)                      // Net
      capacitance (in Farad)
13 fo = 1 /(2*pi*(L * C)**0.5)                  // Frequency (in
      Hertz)
14
15 // Result
16
17 printf("\n Required voltage gain is %0.3f .\\" 
      nFrequency of oscillation is %0.2f   Mhz.",Av,fo
      *10**-6)

```

Scilab code Exa 31.9 Frequency of oscillation

```

1 clear //
2
3 // Variables
4
5 C1 = 0.1 * 10**-6                            // Capacitance (
      in Farad)
6 C2 = 1.0 * 10**-6                            // Capacitance (
      in Farad)
7 L = 470.0 * 10**-6                            // Inductance (in
      Henry)
8
9 // Calculation
10
11 C = C1 * C2/ (C1 + C2)                      // Net
      capacitance (in Farad)
12 fo = 1 /(2*pi*(L * C)**0.5)                  // Frequency (in
      Hertz)
13
14 // Result
15

```

```
16 printf("\n Frequency of oscillation is %0.2f kHz."
,fo * 10**-3)
```

Scilab code Exa 31.10 The range of inductance required

```
1 clear//  
2  
3 // Variables  
4  
5 C1 = 100.0 * 10**-12 //  
    Capacitance (in Farad)  
6 C2 = 7500.0 * 10**-12 //  
    Capacitance (in Farad)  
7 fomin = 950.0 * 10**3 // Frequency  
    minimum (in Hertz)  
8 fomax = 2050.0 * 10**3 // Frequency  
    maximum (in Hertz)  
9  
10 // Calculation  
11  
12 C = C1 * C2/ (C1 + C2) // Net  
    capacitance (in Farad)  
13 L1 = 1.0/(4 * %pi**2*(C*fomin**2)) // Inductance1 ( in Henry)  
14 L2 = 1.0/(4 * %pi**2*(C*fomax**2)) // Inductance2 ( in Henry)  
15  
16 // Result  
17  
18 printf("\n The range of inductance required is from  

    %0.0f micro-Henry to %0.0f micro-Henry.",L2  

    *10**6 ,L1*10**6)
```

Scilab code Exa 31.11 The oscillation frequency if C2

```
1 clear//  
2  
3 // Variables  
4  
5 fo = 450.0 * 10**3           //Frequency (in  
   Hertz)  
6 //Let us assume  
7 C1=10.0*10**-6;C2=10.0*10**-6;C=10.0*10**-6;  
8 C21 = 2 * C2                //Capacitance (in  
   Farad)  
9  
10 // Calculation  
11  
12 fo1 = fo * (3.0/4.0)**0.5    //New Frequency (in  
   Hertz)  
13  
14 // Result  
15  
16 printf("\n The oscillation frequency if C2 is  
doubled is %0.1f kHz.",fo1 * 10**-3)
```

Scilab code Exa 31.12 Frequency of oscillation

```
1 clear//  
2  
3 // Variables  
4  
5 C1 = 0.1 * 10**-6           //Capacitance (in  
   Farad)  
6 C2 = 1.0 * 10**-6           //Capacitance (in  
   Farad)  
7 C3 = 100.0 * 10**-12        //Capacitance (in  
   Farad)
```

```

8 L = 470.0 * 10**-6                                // Inductance (in
   Henry)
9
10 // Calculation
11
12 C = (1.0/C1 + 1.0/C2 + 1.0/C3)**-1           // Capacitance (
   in Farad)
13 fo = 1/(2*pi*(L*C)**0.5)                      // Frequency (in
   Hertz)
14
15 // Result
16
17 printf("\n Frequency of oscillation is %0.1f kHz."
   , fo * 10**-3)

```

Scilab code Exa 31.13 Series resonant frequency

```

1 clear //
2
3 // Variables
4
5 L = 0.33                                         // Inductance (in
   Henry)
6 C1 = 0.065 * 10**-12                            // Capacitance (in
   Farad)
7 C2 = 1.0 * 10**-12                              // Capacitance (in
   Farad)
8 R = 5.5 * 10**3                                 // Resistance (in ohm)
9
10 // Calculation
11
12 fs = 1/(2*pi*(L*C1)**0.5) // Series Resonant
   frequency (in Hertz)
13 Qfactor = 2*pi*fs*L/R          // Q-factor
14

```

```

15 // Result
16
17 printf("\n Series resonant frequency is %0.2f MHz
.\\nQ-factor of the crystal is %0.1f .",fs
*10**-6,Qfactor)

```

Scilab code Exa 31.14 Value of drain resistance

```

1 clear//
2
3 // Variables
4
5 gm = 5000.0 * 10**-6 // Transconductance (in mho)
6 rd = 40.0 * 10**3 // Resistance (in ohm)
7 R = 10.0 * 10**3 // Resistance (in ohm)
8 fo = 1.0 * 10**3 // Frequency (in Hertz)
9 Av = 40.0 // Voltage gain
10
11 // Calculation
12
13 C = 1/(2*pi*(R)*6**0.5*fo) // Capacitance (in Farad)
14 rL = Av / gm // a.c. load resistance (in ohm)
15 RD = (rL * rd)/(rd-rL) // Drain resistance (in ohm)
16
17 // Result
18
19 printf("\n Value of capacitor is %0.5f micro-Farad

```

```
    .",C* 10**6)
20 printf("\n Value of drain resistance is %0.3f kilo
      -ohm.",RD * 10**-3)
```

Scilab code Exa 31.18 Value of capacaitor C

```
1 clear//
2
3 // Variables
4
5 fo = 2.0 * 10**3 // Frequency (in Hertz)
6 hie = 2.0 * 10**3 // hie (in ohm)
7 R1 = 20.0 * 10**3 // Resistance (in ohm)
8 R2 = 80.0 * 10**3 // Resistance (in ohm)
9 RC = 10.0 * 10**3 // Collector Resistance (in ohm)
10 R = 8.0 * 10**3 // Resistance (in ohm)
11
12 // Calculation
13
14 C = 1/(2*pi*R)*(1/(6 + 4*RC/R)**0.5)/fo // Capacitance (in Farad)
15 hfe = 23 + 29 * R/RC + 4* RC /R // Current gain
16 Ri = (1/R1 + 1/R2 + 1/hie)**-1 // Input resistance (in ohm)
17 R3 = R - Ri // Feedback resistor (in ohm)
18
19 // Result
```

```
20
21 printf("\n Value of capacaitor C is %0.3f micro-
   Farad.\nValue of transistor gain is hfe >= %0.3f
   .\nValue of feedback resistor R3 is %0.1f kilo
   -ohm.",C*10**6,hfe,R3*10**-3)
```

Scilab code Exa 31.19 Value of the capacitor C

```
1 clear//
2
3 //Variables
4
5 fo = 10.0 * 10**3                      //Frequency
   (in Hertz)
6 R = 100.0 * 10**3                       //
   Resistance (in ohm)
7
8 //Calculation
9
10 C = 1/(2*pi*R*fo)                      //Capacitance (
    in Farad)
11
12 //Result
13
14 printf("\n Value of the capacitor C is %0.0f pico-
   Farad.",C * 10**12)
```

Chapter 32

Non Sinusoidal Oscillators

Scilab code Exa 32.2 Frequency of oscillation

```
1 clear//  
2  
3 // Variables  
4  
5 R1=20.0*10**3; R2=20.0*10**3; R=20.0*10**3;  
6 C1=100.0*10**-12; C2=100.0*10**-12; C=100.0*10**-12;  
7  
8 // Calculation  
9  
10 f = 1/(1.38 * R * C) // Frequency  
    (in Hertz)  
11  
12 // Result  
13  
14 printf("\n Frequency of oscillation is %0.0f kHz."  
    , f * 10**-3)
```

Scilab code Exa 32.3 Time period of oscillation

```

1 clear//
2
3 //Variables
4
5 R1 = 2.0 * 10**3           //Resistance (in ohm)
6 R2 = 20.0 * 10**3          //Resistance (in ohm)
7 C1 = 0.01 * 10**-6         //Capacitance (in Farad)
8 C2 = 0.05 * 10**-6         //Capacitance (in Farad)
9
10 //Calculation
11
12 T = 0.69*(R1*C1 + R2*C2) //Time periode of
     oscillation (in seconds)
13 f = 1/T                   //Frequency of oscillation
     (in Hertz)
14
15 //Result
16
17 printf("\n Time period of oscillation is %0.1f ms
     .\nFrequency of oscillation is %0.2f kHz.",T
     *10**3,f*10**-3)

```

Scilab code Exa 32.4 Value of C1 capacitor

```

1 clear//
2
3 //Variables
4
5 T1 = 1.0 * 10**-6           //Pulse width (in
     seconds)
6 f = 100.0 * 10**3            //Frequency (in
     Hertz)
7 R1=10.0*10**3;R2=10.0*10**3;
8
9 //Calculation

```

```

10
11 T = 1/f                                //Time period of
   oscillation (in seconds)
12 C1 = T1 / 0.69 / R1                      //Capacitance (in
   Farad)
13 T2 = T - T1                            //Time period (in
   seconds)
14 C2 = T2 / 0.69 / R2                      //Capacitance (in
   Farad)
15
16 // Result
17
18 printf("\n Value of C1 capacitor is %0.0f pico-
   Farad.\nValue of C2 capacitor is %0.0f pico-
   Farad.",C1*10**12,C2*10**12)

```

Scilab code Exa 32.8 The pulse width

```

1 clear// 
2
3 // Variables
4
5 R1 = 2.2 * 10**3                         // Resistance (
   in ohm)
6 C1 = 0.01 * 10**-6                        // Capacitance (
   in Farad)
7
8 // Calculation
9
10 tp = 1.1 * R1 * C1                       // Pulse width (
   in seconds)
11
12 // Result
13
14 printf("\n The pulse width is %0.3f micro-second ."

```

```
,tp * 10**6)
```

Scilab code Exa 32.9 Resistance required

```
1 clear//  
2  
3 //Variables  
4  
5 C = 1000.0 * 10**-12           // Capacitance (in  
   Farad)  
6 tp = 10.0 * 10**-6            // Pulse width (in  
   seconds)  
7 T = 60.0 * 10**-6             // time period (in  
   seconds)  
8  
9 // Calculation  
10  
11 R1 = tp / (1.1 * C)          // Resistance (in  
   ohm)  
12  
13 // Result  
14  
15 printf("\n Resistance required is %0.2f kilo-ohm."  
   ,R1 * 10**-3)
```

Scilab code Exa 32.12 Time period

```
1 clear//  
2  
3 //Variables  
4  
5 f = 50.0 * 10**3              // Frequency (in Hertz  
   )
```

```

6 duty_cycle = 0.6 //Duty cycle
7 C = 0.0022 * 10**-6 //Capacitance (in
                         Farad)
8
9 // Calculation
10
11 T = 1/f //Time period (in
             seconds)
12 t1 = duty_cycle * T //time intervall (in
             seconds)
13 t2 = T - t1 //time interval2 (in
             seconds)
14 R2 = t2 / (0.7 * C) //Resistance (in ohm)
15 R1 = t1 / (0.7 * C) - R2 //Resistance (in ohm)
16
17 // Result
18
19 printf("\n Time period is %0.3f ms.\n t1 is %0.3f
             ms.\n t2 is %0.3f ms.\n R2 is %0.2f kilo-ohm.\n
             R1 is %0.1f kilo-ohm.", T*10**3, t1*10**3, t2
             *10**3, R2*10**-3, R1*10**-3)

```

Chapter 33

Wave Shaping

Scilab code Exa 33.2 Output peak voltage

```
1 clear//  
2  
3 // Variables  
4  
5 Vpk = 1.0 //Peak-to-peak voltage  
    (in volts)  
6 Tby2 = 0.1 //Half-period (in  
    seconds)  
7 tau = 0.25 //Time constant (in  
    seconds)  
8  
9 // Calculation  
10  
11 Vc = 0.5 * exp(-Tby2/tau) //Output voltage (in  
    volts)  
12  
13 // Result  
14  
15 printf("\n Output peak voltage is %0.1f V.", Vc)
```

Scilab code Exa 33.3 The peak value of input voltage

```
1 clear//  
2  
3 // Variables  
4  
5 RC = 250.0 * 10**-12 //Time  
    constance (in seconds)  
6 Vomax = 50.0 //Maximum  
    output voltage (in volts)  
7 tau = 0.05 * 10**-6 //time (in  
    seconds)  
8  
9 // Calculation  
10  
11 alpha = Vomax / RC // alpha (in  
    volt per second)  
12 Vp = alpha * tau //Peak  
    voltage (in volts)  
13  
14 // Result  
15  
16 printf("\n The peak value of input voltage is %0.3f  
    kV.", Vp * 10**-3)
```

Chapter 34

Time Base Circuits

Scilab code Exa 34.1 Frequency of sweep

```
1 clear//  
2  
3 // Variables  
4  
5 R = 100.0 * 10**3 //  
    Resistance (in ohm)  
6 C = 0.4 * 10**-6 //  
    Capacitance (in Farad)  
7 n = 0.57 //  
    Ratio of peak-peak voltage to the supply voltage  
8  
9 // Calculation  
10  
11 f = 1 / (2.3 * R * C * log10(1/(1-n))) //  
    Frequency (in Hertz)  
12  
13 // Result  
14  
15 printf("\n Frequency of sweep is %0.2f Hz.", f)
```

Scilab code Exa 34.2 Value of R with C

```
1 clear//  
2  
3 // Variables  
4  
5 n = 0.62 // Ratio  
   of peak-peak voltage to the supply voltage  
6 R = 5.0 * 10**3 //  
   Resistance (in ohm)  
7 C = 0.05 * 10**-6 //  
   Capacitor (in Farad)  
8  
9 // Calculation  
10  
11 T = 2.3 * R * C * log10(1/(1-n)) //Time  
   period of oscillation (in seconds)  
12 f = 1/T //  
   Frequency of oscillation (in Hertz)  
13 f1 = 50.0 //New  
   frequency (in Hertz)  
14 T1 = 1/f1 //New  
   time period of oscillation (in seconds)  
15 R1 = T1 / (2.3 * C * log10(1/(1-n))) //New  
   Resistance (in ohm)  
16 f2 = 50.0 //  
   Another new frequency (in Hertz)  
17 C2 = 0.5 * 10**-6 //  
   Capacitance (in Farad)  
18 T2 = 1/f2 //  
   Another new time period (in seconds)  
19 R2 = T2 / (2.3 * C2 * log10(1/(1-n))) //New  
   Resistance (in ohm)  
20
```

```
21 // Result
22
23 printf("\n The time period and frequency of
        oscillation in case 1 is %0.2f ms and %0.0f
        Hz.", T*10**3, f)
24 printf("\n New value of R is %0.0f kilo-ohm.", R1 *
        10**-3)
25 printf("\n Value of R with C is 0.5 micro-Farad is
        %0.1f kilo-ohm.", R2 * 10**-3)
```

Chapter 35

Operational Amplifiers OP Amps

Scilab code Exa 35.1 The common mode rejection ratio

```
1 clear//  
2  
3 // Variables  
4  
5 Adm = 200000.0          // Differential  
      gain  
6 Acm = 6.33              // Common mode gain  
7  
8 // Calculation  
9  
10 CMRR = 20 * log10(Adm / Acm)    // Common-mode  
      rejection ratio (in Decibels)  
11  
12 // Result  
13  
14 printf("\n The common-mode rejection ratio is %0.0 f  
      dB.", CMRR)
```

Scilab code Exa 35.2 The common mode gain

```
1 clear//  
2  
3 // Variables  
4  
5 CMRR = 90.0          //Common-mode  
    rejection ratio (in Decibels)  
6 Adm = 30000.0        // Differential gain  
7  
8 // Calculation  
9  
10 Acm = 10**(-CMRR/20.0) * Adm //Common-mode gain  
11  
12 // Result  
13  
14 printf("\n The common-mode gain is %0.3f .",Acm)
```

Scilab code Exa 35.3 The maximum operating frequency for the amplifier

```
1 clear//  
2  
3 // Variables  
4  
5 Slew_rate = 0.5 * 10**6          //Slew rate  
    (in volt per second)  
6 Vpk = 100.0 * 10**-3           //Peak-to-  
    peak voltage (in volts)  
7  
8 // Calculation  
9
```

```

10 fmax = Slew_rate / (2 * %pi * Vpk) //Maximum
    operating frequency (in Hertz)
11
12 // Result
13
14 printf("\n The maximum operating frequency for the
    amplifier is %0.0f kHz.", fmax * 10**-3)

```

Scilab code Exa 35.4 The maximum operating frequency for TLO 741

```

1 clear//
2
3 // Variables
4
5 Slew_rate1 = 0.5 * 10**6                      //Slew
    rate (in volt per second)
6 Slew_rate2 = 13.0 * 10**6                       //Slew
    rate (in volt per second)
7 Vpk = 10.0                                       //Peak-to-
    peak voltage (in volts)
8
9 // Calculation
10
11 fmax = Slew_rate1 / (2 * %pi * Vpk) //Maximum
    operating frequency1 (in Hertz)
12 fmax1 = Slew_rate2 / (2 * %pi * Vpk) //Maximum
    operating frequency2 (in Hertz)
13
14 // Result
15
16 printf("\n The maximum operating frequency for TLO
    741 is %0.3f kHz.\nThe maximum opearng
    frequency for TLO 81 is %0.1f kHz.", fmax
    *10**-3, fmax1*10**-3)

```

Scilab code Exa 35.5 Maximum allowable input voltage Vin

```
1 clear//  
2  
3 // Variables  
4  
5 ACL = 200.0          //Closed loop voltage  
      gain  
6 Vout = 8.0           //Output voltage (in  
      volts)  
7  
8 // Calculation  
9  
10 Vin = - Vout / ACL //Input a.c. voltage (in  
      volts)  
11  
12 // Result  
13  
14 printf("\n Maximum allowable input voltage (Vin) is  
      %0.3f mV." ,abs(Vin * 10**3))
```

Scilab code Exa 35.6 The maximum possible output value could be between

```
1 clear//  
2  
3 // Variables  
4  
5 ACL = 150.0          //Closed loop voltage  
      gain  
6 Vin = 200.0 * 10**-3 //Input a.c. voltage (in  
      volts)  
7 V = 12.0              //Voltage (in volts)
```

```

8
9 // Calculation
10
11 Vout = ACL * Vin           //Output voltage (in
   volts)
12 Vpkplus = V -2.0          //maximum positive peak
   voltage (in volts)
13 Vpkneg = -V + 2.0         //maximum negative
   peagk voltage (in volts)
14
15 // Result
16
17 printf("\n The maximum possible output value could
   be between %0.3f V and %0.3f V.",Vpkplus,
   Vpkneg)

```

Scilab code Exa 35.7 The value of output voltage increases from

```

1 clear //
2
3 // Variables
4
5 R1 = 1.0 * 10**3           // Resistance (in
   volts)
6 R2 = 10.0 * 10**3          // Resistance (in
   volts)
7 vinmin = 0.1                // Input voltage
   minimum (in volts)
8 vinmax = 0.4                // Input voltage
   maximum (in volts)
9
10 // Calculation
11
12 ACL = R2 / R1             // Closed loop voltage
   gain

```

```

13 Voutmin = ACL * vinmin           //Minimum output
      voltage (in volts)
14 Voutmax = ACL * vinmax          //Maximum output
      voltage (in volts)
15
16 // Result
17
18 printf("\n The value of output voltage increases
      from %0.3f V to %0.3f V.",Voutmin,Voutmax)

```

Scilab code Exa 35.8 Output voltage of the inverting amplifier

```

1 clear //
2
3 // Variables
4
5 R1 = 1.0 * 10**3                  // Resistance (in
      ohm)
6 R2 = 2.0 * 10**3                  // Resistance (in
      ohm)
7 V1 = 1.0                         // Voltage (in
      volts)
8
9 // Calculation
10
11 ACL = R2 / R1                   // Closed loop
      voltage gain
12 vo = ACL * V1                  // Output voltage
      (in volts)
13
14 // Result
15
16 printf("\n Output voltage of the inverting amplifier
      is %0.3f V.",vo)

```

Scilab code Exa 35.9 Closed loop gain

```
1 clear//  
2  
3 // Variables  
4  
5 R2 = 100.0 * 10**3          // Resistance (in  
       ohm)  
6 R1 = 10.0 * 10**3          // Resistance (in  
       ohm)  
7 ACM = 0.001                // Common-mode  
       gain  
8 Slew_rate = 0.5 * 10**6    // Slew rate (in  
       volt per second)  
9 Vpk = 5.0                  // Peak voltage (in  
       volts)  
10  
11 // Calculation  
12  
13 ACL = R2 / R1            // Closed loop  
       voltage gain  
14 Zin = R1                  // Input  
       impedance of the circuit (in ohm)  
15 Zout = 80.0                // Output  
       impedance of the circuit (in ohm)  
16 CMRR = ACL / ACM         // Common mode  
       rejection ratio  
17 fmax = Slew_rate / (2*pi*Vpk) // Maximum frequency  
       (in Hertz)  
18  
19 // Result  
20  
21 printf("\n Closed-loop gain is %0.3f .\nInput  
       impedance is %0.3f kilo-ohm.\nOutput impedance
```

```
is %0.3f ohm.\nCommon-mode rejection ratio is  
%0.3f .\nMaximum operating frequency is %0.1f  
kHz.",ACL,Zin*10**-3,Zout,CMRR,fmax*10**-3)
```

Scilab code Exa 35.10 Closed loop gain

```
1 clear//  
2  
3 // Variables  
4  
5 R2 = 100.0 * 10**3 //Resistance (in  
ohm)  
6 R1 = 10.0 * 10**3 //Resistance (in  
ohm)  
7 Slew_rate = 0.5 * 10**6 //Slew rate (in  
volt per second)  
8 Vpk = 5.5 //Peak voltage (  
in volts)  
9 RL = 10.0 * 10**3 //Load resistance  
(in ohm)  
10 ACM = 0.001 //Common mode  
gain  
11  
12 // Calculation  
13  
14 ACL = (1 + R2/R1) //Closed loop  
voltage gain  
15 CMRR = ACL / ACM //Common-mode  
rejection ratio  
16 vin = 1.0 //Voltage (in  
volts)  
17 Vout = ACL * vin //Output voltage  
(in volts)  
18 Vpk = 5.5 //Peak-to-peak  
voltage (in volts)
```

```

19 fmax = Slew_rate/(2*pi*Vpk)      //Maximum frequency (
    in Hertz)
20
21 // Result
22
23 printf("\n Closed loop gain is %0.3f .\nCMRR is %0
    .3f .\nMaximum operating frequency is %0.2f   kHz
    ." ,ACL ,CMRR ,fmax*10**-3)

```

Scilab code Exa 35.11 ACL

```

1 clear//  

2  

3 // Variables  

4  

5 ACL = 1.0                                //Closed loop  

    gain  

6 Acm = 0.001                               //Common mode  

    gain  

7 Slew_rate = 0.5 * 10**6                     //Slew rate (in  

    Volt per second)  

8  

9 // Calculation  

10  

11 CMRR = ACL / Acm                         //Common-mode  

    rejection ratio  

12 vin = 1.0                                  //Voltage (in  

    volts)  

13 Vout = ACL * vin                          //Output voltage  

    (in volts)  

14 Vpk = 3.0                                   //Peak-to-peak  

    voltage (in volts)  

15 fmax = Slew_rate/(2*pi*Vpk)      //Maximum frequency (
    in Hertz)
16

```

```
17 // Result
18
19 printf("\n ACL is %0.3f .\nCMRR is %0.3f .\n fmax
      is %0.1f kHz.", ACL, CMRR, fmax*10**-3)
```

Scilab code Exa 35.12 Output voltage

```
1 clear//
2
3 // Variables
4
5 V1 = 0.1
      Voltage (in volts) //
6 V2 = 1.0
      Voltage (in volts) //
7 V3 = 0.5
      Voltage (in volts) //
8 R1 = 10.0 * 10**3
      Resistance (in ohm) //
9 R2 = 10.0 * 10**3
      Resistance (in ohm) //
10 R3 = 10.0 * 10**3
      Resistance (in ohm) //
11 R4 = 22.0 * 10**3
      Resistance (in ohm) //
12
13 // Calculation
14
15 Vout = (-R4/R1*V1) + (-R4/R2*V2) + (-R4/R3*V3)
      // Output voltage (in volts)
16
17 // Result
18
19 printf("\n Output voltage is %0.3f V.", abs(Vout))
```

Scilab code Exa 35.14 Output voltage

```
1 clear//  
2  
3 // Variables  
4  
5 V1 = -2.0  
    //Voltage (in volts)  
6 V2 = 2.0  
    //Voltage (in volts)  
7 V3 = -1.0  
    //Voltage (in volts)  
8 R1 = 200.0 * 10**3  
    //Resistance (in ohm)  
9 R2 = 250.0 * 10**3  
    //Resistance (in ohm)  
10 R3 = 500.0 * 10**3  
    //Resistance (in ohm)  
11 Rf = 1.0 * 10**6  
    //Resistance (in ohm)  
12  
13 // Calculation  
14  
15 Vout = (-Rf/R1*V1) + (-Rf/R2*V2) + (-Rf/R3*V3)  
    //Output voltage (in volts)  
16  
17 //Result  
18  
19 printf("\n Output voltage is %0.3f V.", Vout)
```

Chapter 36

Basic Op Amp Applications

Scilab code Exa 36.1 Capacitance required in the circuit

```
1 clear//  
2  
3 // Variables  
4  
5 R1 = 1.0 * 10**3           // Resistance (in ohm)  
6 R2 = 100.0 * 10**3         // Resistance (in ohm)  
7 f1 = 159.0                 // Frequency (in  
Hertz)  
8  
9 // Calculation  
10  
11 C = 1.0/(2*pi*R2*f1)     // Capacitance (in Farad)  
12  
13 // Result  
14  
15 printf("\n Capacitance required in the circuit is  
%0.2f micro-Farad.", C * 10**6)
```

Scilab code Exa 36.2 Minimum non linear operating frequency

```
1 clear//  
2  
3 // Variables  
4  
5 R1 = 1.0 * 10**3           // Resistance (in ohm  
6 )  
7 Rf = 51.0 * 10**3           // Resistance (in ohm  
8 )  
9 Cf = 0.01 * 10**-6          // Capacitance (in  
10 Farad)  
11  
12 // Calculation  
13  
14 f = 1.0/(2*pi*Rf*Cf)      // Frequency (in Hertz)  
15 fmin = 10*f                //Minimum frequency  
16 required (in Hertz)  
17  
18 // Result  
19  
20  
21 printf("\n The cut-off frequency of an integrator  
22 circuit is %0.0 f Hz.",f)  
23 printf("\n Minimum non-linear operating frequency is  
24 %0.0 f Hz.",fmin)
```

Scilab code Exa 36.3 Maximum linear operating frequency

```
1 clear//  
2  
3 // Variables  
4
```

```

5 R1 = 10.0 * 10**3 // Resistance (in ohm)
6 C1 = 0.01 * 10**-6 // Capacitor (in Farad)
7
8 // Calculation
9
10 f2 = 1.0/(2*pi*R1*C1) // Frequency (in Hertz)
11 fmax = f2 / 10.0 // Maximum linear operating frequency (in Hertz)
12
13 // Result
14
15 printf("\n Cut-off frequency is %0.1f Hz.", f2)
16 printf("\n Maximum linear operating frequency is %0.0f Hz.", fmax)

```

Scilab code Exa 36.4 The frequency of oscillations

```

1 clear //
2
3 // Variables
4
5 R1=51.0*10**3; R2=51.0*10**3;
6 C1=0.001*10**-6; C2=0.001*10**-6; C=0.001*10**-6;
7
8 // Calculation
9
10 fo = 1.0/(2*pi*R1*C1) // Resonant frequency (in Hertz)
11
12 // Result
13
14 printf("\n The frequency of oscillations is %0.1f"

```

Hz . ” , f o)
