

Scilab Textbook Companion for  
Introduction To Power Electronics  
by V. Jagannathan<sup>1</sup>

Created by  
Rijwan  
B. Tech  
Computer Engineering  
UTU  
College Teacher  
None  
Cross-Checked by  
None

April 14, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Introduction To Power Electronics

**Author:** V. Jagannathan

**Publisher:** Prentice-Hall of India Pvt.Ltd

**Edition:** 1

**Year:** 2009

**ISBN:** 9788120323995

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>2 Power Switching Devices and their Characteristics</b>	<b>5</b>
<b>3 AC to DC Converters</b>	<b>17</b>
<b>4 AC to AC Converters</b>	<b>31</b>
<b>5 DC to DC Converters</b>	<b>36</b>
<b>7 Power Controllers their Applications</b>	<b>39</b>

# List of Scilab Codes

Exa 2.1	Value of VA . . . . .	5
Exa 2.2	min duration of gating pulse . . . . .	5
Exa 2.3	gate power dissipation . . . . .	6
Exa 2.4	resistance in series . . . . .	7
Exa 2.5	duty cycle of triggering pulse . . . . .	7
Exa 2.6	value of R and C . . . . .	8
Exa 2.7	no of scr to be connected . . . . .	9
Exa 2.8	value of series resistance . . . . .	10
Exa 2.9	average power loss . . . . .	10
Exa 2.10	minimum gate pulse width . . . . .	11
Exa 2.11	gate source resistance . . . . .	11
Exa 2.12	value of resistance . . . . .	12
Exa 2.13	average on state current . . . . .	13
Exa 2.14	design a snubber circuit . . . . .	14
Exa 2.15	one cycle surge current rating . . . . .	16
Exa 3.1	average current and power . . . . .	17
Exa 3.2	average current . . . . .	18
Exa 3.3	PIV of thyristor . . . . .	18
Exa 3.4	Power factor of supply . . . . .	20
Exa 3.5	average and rms current . . . . .	20
Exa 3.6	average load current . . . . .	21
Exa 3.7	average load voltage . . . . .	22
Exa 3.8	average load voltage and current . . . . .	22
Exa 3.9	rms value of current . . . . .	23
Exa 3.10	emf on load side . . . . .	24
Exa 3.11	average load voltage and current . . . . .	24
Exa 3.12	average load voltage and current . . . . .	25
Exa 3.13	output voltage and power . . . . .	26

Exa 3.14	average load voltage and current . . . . .	27
Exa 3.15	average load voltage and current . . . . .	28
Exa 3.16	firing angle and overlap angle . . . . .	28
Exa 3.17	load resistance and source inductance . . . .	29
Exa 4.1	load voltage and rms current . . . . .	31
Exa 4.2	average and rms value of scr current . . . .	32
Exa 4.3	load voltage and rms current . . . . .	33
Exa 4.4	rms load voltage and rms current . . . . .	33
Exa 4.5	max voltage and current . . . . .	34
Exa 4.7	control range of firing angle . . . . .	35
Exa 5.1	average load current . . . . .	36
Exa 5.2	duty ratio and chopping frequency . . . .	37
Exa 5.3	chopping frequency . . . . .	37
Exa 5.5	new output voltage . . . . .	38
Exa 7.1	speed of motor . . . . .	39
Exa 7.2	duty ratio . . . . .	39
Exa 7.3	triggering angle . . . . .	40
Exa 7.4	average armature current . . . . .	41

# Chapter 2

## Power Switching Devices and their Characteristics

Scilab code Exa 2.1 Value of VA

```
1 //Ex 2.1 page 67
2
3 clc;
4 clear;
5 close;
6
7 V1=1; //V across SCR
8 IG=0; //A
9 Ih=2; //mA holding current
10 R=50; //ohm
11
12 // Applying kirchoff law
13 //VA-(IAK*R)-V1=0
14 VA=(Ih*10**-3*R)+V1; //V (let IAK=Ih)
15 printf('VA = %.2 f V',VA)
```

---

### Scilab code Exa 2.2 min duration of gating pulse

```
1 //Ex 2.2 page 67
2
3 clc;
4 clear;
5 close;
6
7 diBYdt=1000; //A/s (rate of rise of current)
8 il=10; //mA (latching current = diBYdt * tp)
9 tp=il*10**-3/diBYdt; //s
10 printf('Minimum duration of gating pulse = %.f micro
           s ',tp*10**6)
```

---

### Scilab code Exa 2.3 gate power dissipation

```
1 //Ex 2.3 page 68
2
3 clc;
4 clear;
5 close;
6
7 m=16; // V/A (gradient)
8 t_on=4; // us
9 IG=500; // mA
10 VS=15; // V
11
12 VG=m*IG/1000; // V
13 //Load line equation
14 //VG=VS-IG*RS
15 RS=(VS-VG)/(IG/1000) ; // ohm
16 Pg=VS*(IG/1000)**2 ; // W
17 printf('Gate power dissipation = %.f W',Pg)
18 printf('\n Resistance to be connected = %.f ohm',RS)
```

---

### Scilab code Exa 2.4 resistance in series

```
1 //Ex 2.4 page 68
2
3 clc;
4 clear;
5 close;
6
7 // VG=0.5+8*IG -- eqn(1)
8 f=400; // Hz
9 delta=0.1 ; // (Duty Cycle)
10 P=0.5; //W
11 VS=12; // V
12
13 Tp=1/f*10**6; // us
14 // P= VG*IG -- eqn(2)
15 // solving eqn 1 and 2
16 //8*IG*IG**2+0.5*IG-P=0
17 p=[8, 0.5, -P] // polynomial for IG
18 IG=roots(p) ;// A
19 IG=IG(2) ;// A (discarding -ve value)
20 VG=0.5+8*IG; // V
21 // VS=VG+IG*RS
22 RS=(VS-VG)/IG
23 printf('Value of resistance to be added in series =
% .2 f ohm', RS)
```

---

### Scilab code Exa 2.5 duty cycle of triggering pulse

```
1 //Ex 2.5 page 69
2
3 clc;
```

```

4 clear;
5 close;
6
7 // VG=10*IG --- eqn(1)
8 PGM=5; // W
9 PGav=.5; // W
10 VS=12; // V
11 Tp=20; // us
12
13 // PGM = VG*IG where VG=10*IG
14 IG=sqrt(PGM/10); // A
15 VG=10*IG; // V
16 // During the application of pulse VS = VG+(IG*RS)
17 RS=(VS-VG)/IG; // ohm
18 f=PGav/(PGM*Tp*10**-6)/1000; // kHz
19 delta=f*1000*Tp*10**-6; // Duty Cycle
20 printf('Value of resistance to be connected in
           series = %.2f ohm',RS)
21 printf('\n Triggering frequency = %.2f kHz ',f)
22 printf('\n Duty Cycle = %.1f ',delta)
23 // Note : ans in the textbook is not accurate.

```

---

### Scilab code Exa 2.6 value of R and C

```

1 //Ex 2.6 page 70
2
3 clc;
4 clear;
5 close;
6
7 VS=3; // kV
8 IS=750; // A
9
10 VD=800; // V
11 ID=175; // A

```

```

12 dr=30/100; // de-rating factor
13 IB=8; //mA
14 delQ=30; // u Coulomb
15 // dr = 1-IS/np*ID
16 np = round(IS/(1-dr)/(ID)) ; // no. of parallel
   string
17 ns = round(VS*1000/(1-dr)/(VD)) ; // no. of series
   string
18 R=(ns*VD-VS*1000)/(ns-1)/(IB/1000)/1000; //kohm
19 C=(ns-1)*delQ*10**-6/(ns*VD-VS*1000)
20 printf('Value of R = %.2f kohm',R)
21 printf('\n Value of C = %.2e F',C)

```

---

### Scilab code Exa 2.7 no of scr to be connected

```

1 //Ex 2.7 page 71
2
3 clc;
4 clear;
5 close;
6
7 VS=4; // kV
8 IS=800; // A
9
10 VD=800; // V
11 ID=200; // A
12 dr=20/100; // de-rating factor
13 // for series connection
14 ns = ceil(VS*1000/(1-dr)/(VD)) ; // no. of series
   string
15 // for parallel connection
16 np = round(IS/(1-dr)/(ID)) ; // no. of parallel
   string
17 printf('\n no. of series connection = %d',ns)
18 printf('\n no. of parallel connection = %d',np)

```

---

### Scilab code Exa 2.8 value of series resistance

```
1 //Ex 2.8 page 72
2
3 clc;
4 clear;
5 close;
6
7 IS1=100; // A
8 IS2=150; // A
9 vd1=2.1; // V
10 vd2=1.75; // V
11 I=250; // A
12
13 rf1=vd1/IS1; // ohm
14 rf2=vd2/IS2; // ohm
15 // Equating voltage drops
16 // vd1+IS1*re = vd2+IS2*re
17 re=(vd1-vd2)/(IS2-IS1)
18 printf(' Series resistance = %.3f ohm ',re)
```

---

### Scilab code Exa 2.9 average power loss

```
1 //Ex 2.9 page 72
2
3 clc;
4 clear;
5 close;
6
7 Vf1=1; // V
8 If1=0; //A
```

```

9 Vf2=1.9; // V
10 If2=60; //A
11 IT=20*pi; // A
12 // PAV = 1/T*integrate (VT*IT ,0 ,T)*dt = ITAV+0.015*
    IRMS**2
13 ITAV=IT/%pi; //A
14 ITRMS=IT/2; // A
15 dt=ITAV+0.015*ITRMS**2; // W
16 printf('Average power loss = %.1f W',dt)

```

---

### Scilab code Exa 2.10 minimum gate pulse width

```

1 //Ex 2.10 page 73
2
3 clc;
4 clear;
5 close;
6
7 R=10; // ohm
8 L=0.1; // H
9 delta_i=20/1000; // A
10 Vs=230; // V
11 f=50; // Hz
12 theta=45; // degree
13
14 delta_t = L*delta_i/Vs; // s
15 delta_t = delta_t*10**6; // micro s
16 printf('Minimum gate pulse width = %.1f micro s',
    delta_t)

```

---

### Scilab code Exa 2.11 gate source resistance

```
1 //Ex 2.11 page 73
```

```

2
3 clc;
4 clear;
5 close;
6
7 m=3*10***3; // gradient (VG/IG)
8 VS=10; // V
9 PG=0.012; // W
10 // IG = VG/m & PG=VG*IG
11 VG=sqrt(PG*m)
12 IG=VG/m ; // A
13 RS=(VS-VG)/IG/1000; // kohm
14 printf('gate source resistance = %.1f kohm ',RS)

```

---

### Scilab code Exa 2.12 value of resistance

```

1 //Ex 2.12 page 74
2
3 clc;
4 clear;
5 close;
6
7 VS=300; // V
8 delta_i = 50/1000; // A
9 R=60; // ohm
10 L=2; // H
11 TP=40*10**-6; // s
12
13 I1=VS/L*TP; // A (at the end of pulse)
14 // as I1 << delta_i
15 I2=delta_i; // A (anode current with RL load)
16
17 Rdash = VS/(I2-I1)/1000; // kohm
18 printf('Value of resistance = %.2f kohm ',Rdash)

```

---

### Scilab code Exa 2.13 average on state current

```
1 //Ex 2.13 page 74
2
3 clc;
4 clear;
5 close;
6
7 Im=50; // A
8
9 printf('For half sine wave current : \n')
10 // theta=180;// degree
11 theta=180; // degree
12 Iav=Im/%pi;// A
13 Irms=Im/2;// A
14 FF=Irms/Iav;// form factor
15 ITav=Im/FF ; // A
16 printf('( i) Average ON State current = %.2f A\n', ITav)
17
18 // theta=90;// degree
19 theta=90; // degree
20 Iav=Im/2/%pi;// A
21 Irms=Im/2/sqrt(2); // A
22 FF=Irms/Iav;// form factor
23 ITav=Im/FF ; // A
24 printf('( ii) Average ON State current = %.2f A\n', ITav)
25
26 // theta=180;// degree
27 theta=180; // degree
28 Iav=Im*0.0213;// A
29 Irms=Im*0.0849;// A
30 FF=Irms/Iav;// form factor
```

```

31 ITav=Im/FF ; // A
32 printf( '( i i ) Average ON State current = %.2f A\n' ,
ITav)
33
34 printf( '\n For rectangular wave current : \n')
35 // theta=180;// degree
36 theta=180;// degree
37 Iav=Im/2;// A
38 Irms=Im/sqrt(2); // A
39 FF=Irms/Iav; // form factor
40 ITav=Im/FF ; // A
41 printf( '( i ) Average ON State current = %.2f A\n' ,
ITav)
42 // theta=90;// degree
43 theta=90; // degree
44 Iav=Im/4; // A
45 Irms=Im/2; // A
46 FF=Irms/Iav; // form factor
47 ITav=Im/FF ; // A
48 printf( '( i i ) Average ON State current = %.2f A\n' ,
ITav)
49
50 // theta=180;// degree
51 theta=180; // degree
52 Iav=Im/12; // A
53 Irms=Im/2/sqrt(3); // A
54 FF=Irms/Iav; // form factor
55 ITav=Im/FF ; // A
56 printf( '( i ) Average ON State current = %.2f A\n' ,
ITav)

```

---

### Scilab code Exa 2.14 design a snubber circuit

1 //Ex 2.14 page 76

```

2
3 clc;
4 clear;
5 close;
6
7 VS=500; // V
8 IP=250; // A
9 diBYdt=60; // A/micro-s
10 dvaBYdt=200; // V/micro-s
11 RL=20; // ohm
12 r=0.65; // ohm
13 eps=0.65 ; // damping ratio
14
15 F=2; // saftety factor
16 IP=IP/2; // A
17 diBYdt=60/2; // A/micro-s
18 dvaBYdt=200/2; // V/micro-s
19 L=VS/diBYdt; // uH
20 R=L*10**6/VS*dvaBYdt/10**6; // ohm
21 printf('Value of L = %.2f micro H',L)
22 printf('\n Value of R = %.1f ohm',R)
23
24 Ip=VS/RL+VS/R; // A
25 if Ip > IP then
26     printf('\n Value of Ip = %.1f A is greater than
              permissible peak current = %.1f A\n change
              the value of Rs',Ip,IP)
27     Rs=6; //ohm
28 end
29 Ip=VS/RL+VS/Rs; // A
30 Cs=(2*eps/Rs)**2*L; // micro F
31 printf('\n Value of C = %.2f micro F',Cs)
32
33 //load combination current Cs*dv/dt = Vs/(Rs+RL)
34
35 Cs=0.4; // uF ( reduced value of Cs)
36 Rs=6; //ohm
37 dvBYdt = VS/(Rs+RL)/Cs; // V/(micro-s)

```

```
38 printf ('\n Value of dv/dt = %.1f V/(micro-s) ',dvBYdt
    )
39 disp ('This is less than the specified max. value.
        Hence the choice is correct .')
40
41 //Answer in the textbook is wrong. In last part RL+
    Rs = 18 is taken in place of 26
```

---

### Scilab code Exa 2.15 one cycle surge current rating

```
1 //Ex 2.15 page 77
2
3 clc;
4 clear;
5 close;
6
7 Isb=3000; // A
8 f=50; // Hz
9 I=sqrt((Isb**2*1/2/f)*f) ; // A
10 I2t=I**2/2/f; // sq.A/s
11 printf ('I sq. by t rating = %d A**2/s ',ceil(I2t))
```

---

# Chapter 3

## AC to DC Converters

Scilab code Exa 3.1 average current and power

```
1 //Ex 3.1 page 117
2
3 clc;
4 clear;
5 close;
6
7 R=100; // ohm
8 Vs=230; // V
9 f=50; // Hz
10 alpha=45; // degree
11
12 Vo=Vs*sqrt(2)/2/%pi*(1+cosd(alpha)); // V
13 Io=Vo/R; // A
14 printf('Average current = %.4f A',Io)
15 Vor=Vs/sqrt(2)*sqrt(1/180*((180-alpha)+sind(2*alpha)
    /2)); // V
16 Ior=Vor/R; // A
17 P=Ior**2*R; // W
18 printf('\n Power delivered = %.2f W',P)
19
20 //Ans in the textbook is not accurate.
```

---

### Scilab code Exa 3.2 average current

```
1 //Ex 3.2 page 118
2
3 clc;
4 clear;
5 close;
6
7 R=10; // ohm
8 E=165; // V
9 //vt=330*sin(314*t)
10Vm=330; // V
11f=314/2/%pi; // Hz
12alpha1=asin(E/Vm); // radian
13alpha2=%pi-alpha1; // radian
14Io=1/2/%pi/R*(2*Vm*cos(alpha1)-E*(alpha2-alpha1)); //
A
15P=E*Io; // W
16
17 printf('Power supplied to battery = %d W',P)
```

---

### Scilab code Exa 3.3 PIV of thyristor

```
1 //Ex 3.3 page 119
2
3 clc;
4 clear;
5 close;
6
7 //v2t = 325*sin(w*t)
8 R=20; // ohm
```

```

9 alfa=45; // degree
10 vm=325; // V
11 V=230; // V
12 printf(' part (a)\n')
13 Vo=vm/2/%pi*(1+cosd(alfa)) ; // V
14 Io=Vo/R; // A
15 printf(' dc voltage Vo = %.1f V', Vo)
16 printf('\n & Current Io = %.3f A', Io)
17 printf('\n\n part (b)\n')
18 Vor=vm/2/sqrt(%pi)*sqrt((%pi-%pi/180*alfa)+1/2*sind
    (2*alfa)); // V
19 Ior=Vor/R; // A
20 printf(' rms voltage Vor = %.3f V', Vor)
21 printf('\n & Current Ior = %.3f A', Ior)
22 printf('\n\n part (c)')
23 Pdc=Vo*Io; // W
24 Pac=Vor*Ior; // W
25 eta=Pdc/Pac; // rectification efficiency
26 printf("\n dc Power = %.2f W", Pdc)
27 printf("\n ac Power = %.2f W", Pac)
28 printf("\n Rectification efficiency = %.4f", eta)
29 printf('\n\n part (d)')
30 FF=Vor/Vo; // form factor
31 RF=sqrt(FF**2-1)
32 printf('\n Form factor = %.3f ', FF)
33 printf('\n Ripple factor = %.3f ', RF)
34 printf('\n\n part (e)')
35 VA=V*Ior; // VA
36 TUF=Pdc/V/Ior; // Transformer Utilization factor
37 printf("\n VA rating = %.1f VA", VA)
38 printf("\n Transformer Utilization factor = %.4f",
    TUF)
39 printf('\n\n part (f)')
40 Vp=vm; // V
41 printf("\n Peak inverse voltage = %d V", Vp)

```

---

### Scilab code Exa 3.4 Power factor of supply

```
1 //Ex 3.4 page 120
2
3 clc;
4 clear;
5 close;
6
7 R=10; // ohm
8 E=165; // V
9 //vt=330*sin(314*t)
10 Vm=330; // V
11 Vs=233; // V
12 f=314/2/%pi; // Hz
13 theta1=asin(E/Vm); // radian
14 //alpha2=%pi-alpha1;// radian
15 Io=1/2/%pi/R*(2*Vm*cos(theta1)-E* (%pi-2*theta1)); //
A
16 printf(' (a) Average value of current = %.2f A',Io)
17 P=E*Io; // W
18 printf ('\n (b) Power supplied to battery = %d W',P)
19 Ior=sqrt(1/2/%pi/R**2*((%pi-2*theta1)*(Vs**2+E**2)+
Vm**2*sin(2*theta1)-4*Vm*E*cos(theta1))); // A
20 Pr=Ior**2*R; // W
21 printf ('\n (c) Power dissipated in the resistor = %
.2f W',Pr)
22 pf=(Pr+P)/Vs/Ior; // power factor
23 printf ('\n (d) Power factor = %.4f ',pf)
```

---

### Scilab code Exa 3.5 average and rms current

```
1 //Ex 3.5 page 122
```

```

2
3 clc;
4 clear;
5 close;
6
7 R=20; // ohm
8 V=230; // V
9 f=50; // Hz
10 alpha=30; // degree
11Vm=V*sqrt(2); //V
12 Vo=Vm/%pi*(1+cos(alpha*pi/180)); // V
13 printf('Average load voltage = %.1f V', Vo)
14 Io=Vo/R; // A
15 printf('\n Average load current = %.2f A', Io)
16 Vor=V/sqrt(%pi)*sqrt((%pi-alpha*pi/180)+sin(2*alpha
    *%pi/180)/2); // V
17 Ior=Vor/R; // A
18 printf('\n rms load current = %.2f A', Ior)
19 Iav=Io/2; //A
20 printf('\n Average thyristor current = %.2f A', Iav)
21 Irms=Ior/sqrt(2); // A
22 printf('\n rms thyristor current = %.3f A', Irms)

```

---

### Scilab code Exa 3.6 average load current

```

1 //Ex 3.6 page 122
2
3 clc;
4 clear;
5 close;
6
7 R=10; // ohm
8 L=100/1000; // H
9 E=100; // V
10 Vs=230; // V

```

```

11 f=50; // Hz
12 alpha = 45; // degree
13 Vm=Vs*sqrt(2); // V
14 Vo=2*Vm/%pi*cos(alpha*%pi/180); // V
15 Io=(Vo-E)/R; // A
16 printf('Average load current = %.3f A', Io)

```

---

### Scilab code Exa 3.7 average load voltage

```

1 //Ex 3.7 page 123
2
3 clc;
4 clear;
5 close;
6
7 R=2; // ohm
8 L=0.3; // H
9 E=100; // V
10 Vs=230; // V
11 f=50; // Hz
12 alpha = 30; // degree
13 Vm=Vs*sqrt(2); // V
14 Vo=2*Vm/%pi*cos(alpha*%pi/180); // V
15 printf(' Average load voltage = %.2f V', Vo)
16 Io=(Vo)/R; // A
17 printf('\n Average load current = %.2f A', Io)
18 Is=Io; // A
19 Is1=4*Io/%pi/sqrt(2); // A
20 PF=Vo*Io/Vs/Is; // power factor
21 printf('\n Power factor = %.4f', PF)

```

---

### Scilab code Exa 3.8 average load voltage and current

```

1 //Ex 3.8 page 123
2
3 clc;
4 clear;
5 close;
6
7 R=5; // ohm
8 L=1; // H
9 E=10; // V
10 Vs=230; // V
11 f=50; // Hz
12 alpha = 45; // degree
13Vm=Vs*sqrt(2); // V
14 Vo=Vm/%pi*(1+cos(alpha*pi/180)); // V
15 printf(' Average load voltage = %.2f V', Vo)
16 Io=(Vo-E)/R; // A
17 printf('\n Average load current = %.2f A', Io)
18 PF=(Io**2*R+E*Io)/Vs/Io; // power factor
19 printf('\n Power factor = %.4f', PF)

```

---

### Scilab code Exa 3.9 rms value of current

```

1 //Ex 3.9 page 124
2
3 clc;
4 clear;
5 close;
6
7 R=50; // ohm
8 Vs=230; // V
9 f=50; // Hz
10 alpha = 30; // degree
11Vm=Vs*sqrt(2); // V
12 Vo=2*Vm/%pi*cos(alpha*pi/180); // V
13 printf(' (i) Average voltage across 50 ohm resistor

```

```
= %.2f V', Vo)  
14 Io=(Vo)/R; // A  
15 Ior=Io/sqrt(2); // A  
16 printf('\n (ii) rms current = %.4f A', Ior)
```

---

### Scilab code Exa 3.10 emf on load side

```
1 //Ex 3.10 page 124  
2  
3 clc;  
4 clear;  
5 close;  
6  
7 R=2; // ohm  
8 Vs=230; // V  
9 f=50; // Hz  
10 alpha = 120; // degree  
11 Ia=10; // A  
12  
13 Vo=2*sqrt(2)*Vs*cos(alpha*pi/180)/pi  
14 V=Ia*R-Vo; // V  
15 printf('emf on load side = %.2f V', V)
```

---

### Scilab code Exa 3.11 average load voltage and current

```
1 //Ex 3.11 page 125  
2  
3 clc;  
4 clear;  
5 close;  
6  
7 Vs=230; // V  
8 Io=5; // A
```

```

9 alpha = 45; // degree
10 printf('part(i)')
11 Vo=2*sqrt(2)*Vs/%pi*cos(alpha*%pi/180); // V
12 printf('\n dc output voltage = %.1f V',Vo)
13 Pi=Vo*Io; // W
14 printf('\n Active power = %.1f W',Pi)
15 Qi=2*sqrt(2)*Vs/%pi*sin(alpha*%pi/180)*Io; // VAR
16 printf('\n Reactive power = %.1f VAR',Qi)
17 printf('\n\n part(ii)')
18 R=Vo/Io; // ohm
19 Vo=sqrt(2)*Vs/%pi*(1+cos(alpha*%pi/180)); // V
20 printf('\n dc output voltage = %.1f V',Vo)
21 Io=Vo/R; // A
22 Pi=Vo*Io; // W
23 printf('\n Active power = %.1f W',Pi)
24 Qi=sqrt(2)*Vs/%pi*sin(alpha*%pi/180)*Io; // VAR
25 printf('\n Reactive power = %.0f VAR',Qi)
26 printf('\n\n part(iii)')
27 Vo=sqrt(2)*Vs/%pi/2*(1+cos(alpha*%pi/180)); //
28 printf('\n Average load voltage = %.0f V',Vo)
29 Io=Vo/R; // A
30 printf('\n Average load current = %.2f A',Io)

```

---

### Scilab code Exa 3.12 average load voltage and current

```

1 //Ex 3.12 page 126
2
3 clc;
4 clear;
5 close;
6
7 R=20; // ohm
8 Vs=400; // V
9 f=50; // Hz
10 alpha = 30; // degree

```

```

11
12 Vm=Vs*sqrt(2); // V
13 Vo=3*Vm/%pi*cos(alpha*pi/180); // V
14 Io=Vo/R; // A
15 printf ('\n Average load voltage = %.3f V', Vo)
16 printf ('\n Average load current = %.3f A', Io)

```

---

### Scilab code Exa 3.13 output voltage and power

```

1 //Ex 3.13 page 126
2
3 clc;
4 clear;
5 close;
6
7 n=3; // no. of phase
8 Vs=400; // V
9 f=50; // Hz
10 Io=100; // A
11 alpha = 60; // degree
12
13 Vm=Vs*sqrt(2); // V
14 Vo=n*Vm/%pi*cos(alpha*pi/180); // V
15 Po=Vo*Io; // W
16 printf ('( i )')
17 printf ('\n Output voltage = %.0f V', Vo)
18 printf ('\n Output power = %.0f W', Po)
19 printf ('\n\n ( ii )')
20 Iav=Io*2*pi/3/2/%pi; // A
21 printf ('\n average current through thyristor = %.2f
A', Iav)
22 Ior=sqrt(Io**2*2*pi/3/2/%pi); // A
23 printf ('\n rms current through thyristor = %.2f A',
Ior)
24 Ip=Io; //A

```

```

25 printf ('\n peak current through thyristor = %.2f A' ,
26     Ip)
26 printf ('\n\n ( i i )')
27 PIV=sqrt(2)*Vs; //V
28 printf ('\n PIV of thyristor = %.1f V',PIV)
29 // Ans in the book is not accurate.

```

---

### Scilab code Exa 3.14 average load voltage and current

```

1 //Ex 3.14 page 127
2
3 clc;
4 clear;
5 close;
6
7 n=3; // no. of phase
8 R=60; // ohm
9 Vs=400; // V
10 alpha = 30; // degree
11
12 Vm=Vs*sqrt(2); // V
13 Vo=3*Vm/%pi*cos(alpha*pi/180); // V
14 Io=Vo/R; // A
15 Is=Io*sqrt(2/3); // A
16 P=Io**2*R; // W
17 pf=P/sqrt(3)/Vs/Is; // power factor
18
19 printf ('\n Average load voltage = %.3f V',Vo)
20 printf ('\n Average load current = %.1f A',Io)
21 printf ('\n input power factor(lag) = %.4f ',pf)
22 // Note : Ans in the textbook is wrong as in
// calculation for pf Io is used in place of Is

```

---

### Scilab code Exa 3.15 average load voltage and current

```
1 //Ex 3.15 page 127
2
3 clc;
4 clear;
5 close;
6
7 n=3; // no. of phase
8 R=50; // ohm
9 Vs=400; // V
10 f=50; // Hz
11 alpha = 45; // degree
12
13Vm=Vs*sqrt(2); // V
14 Vo=3*Vm/2/%pi*(1+cos(alpha*pi/180)); // V
15 Io=Vo/R; // A
16 printf ('\n Average load voltage = %.2f V', Vo)
17 printf ('\n Average load current = %.2f A', Io)
```

---

### Scilab code Exa 3.16 firing angle and overlap angle

```
1 //Ex 3.16 page 128
2
3 clc;
4 clear;
5 close;
6
7 n=3; // no. of phase
8 Vs=400; // V
9 f=50; // Hz
10 Ls=5/1000; // H
11 Io=20; // A
12 Ri=1; // ohm
13 Vdc=400; // V
```

```

14
15 Vo=Vdc+Io*Ri; // V
16 // Vo=3*Vm/%pi*cos(alpha*pi/180)-3*2*%pi*f*Ls/%pi*
   Io
17 Vm=sqrt(2)*Vs; // V
18 alpha=acos((Vo+3*2*%pi*f*Ls/%pi*Io)/(3*Vm/%pi))*180/
   %pi; // degree
19
20 // Vo=3*Vm/%pi*cos((alpha+mu)*%pi/180)-3*2*%pi*f*Ls/
   %pi*Io
21 mu=acos((Vo-3*2*%pi*f*Ls/%pi*Io)/(3*Vm/%pi))*180/%pi
   -alpha; // degree
22 printf('\n Firing angle = %.2f degree',alpha)
23 printf('\n Overlap angle = %.2f degree',mu)
24 // ans in the textbook is not accurate.

```

---

### Scilab code Exa 3.17 load resistance and source inductance

```

1 //Ex 3.17 page 128
2
3 clc;
4 clear;
5 close;
6
7
8 n=3; // no. of phase
9 Vs=400; // V
10 f=50; // Hz
11 alpha = %pi/4; // radian
12 Io=10; // A
13 Vo=360; // V
14
15 // Vo=n*Vs*sqrt(2)/%pi/sqrt(2)-3*2*%pi*f*Ls*Io/%pi
16 Ls=(n*Vs*sqrt(2)/%pi/sqrt(2)-Vo)/(3*2*%pi*f)/(Io/%pi
   )*1000; // mH

```

```
17 R=Vo/Io; // ohm
18 printf(' Load resistance = %.f ohm ',R)
19 printf('\n Source inductance = %.1f mH ',Ls)
20 // Vo = n*Vs*sqrt(2)/%pi*cos(alpha+mu)+3*2*%pi*f*Ls*
   Io/%pi
21 mu=acos((Vo-3*2*%pi*f*Ls/1000*Io/%pi)/(n*Vs*sqrt(2) /
   %pi))-alpha; // radian
22 mu=mu*180/%pi; // degree
23 printf('\n Overlap angle = %.d degree ',mu)
```

---

# Chapter 4

## AC to AC Converters

Scilab code Exa 4.1 load voltage and rms current

```
1 //Ex 4.1 page 158
2
3 clc;
4 clear;
5 close;
6
7
8 R=5; // ohm
9 Vs=230; // V
10 f=50; // Hz
11 alpha = 120; // degree
12
13 Vor=Vs*sqrt(1/%pi*(%pi-alpha*pi/180+sin(2*alpha*pi
    /180)/2)); // V
14 printf ('\n rms load voltage = %.2f V', Vor)
15 Ior=Vor/R; // A
16 printf ('\n rms load current = %.2f A', Ior)
17 Irms=Ior/sqrt(2); //A
18 printf ('\n rms thyristor current = %.2f A', Irms)
19 pf=sqrt(1/%pi*((%pi-alpha*pi/180)+sin(2*alpha*pi
    /180)/2)); // power factor
```

```
20 printf ('\n input power factor = %.3f ', pf)
```

---

### Scilab code Exa 4.2 average and rms value of scr current

```
1 //Ex 4.2 page 158
2
3 clc;
4 clear;
5 close;
6
7
8 R=10; // ohm
9 Vs=230; // V
10 f=50; // Hz
11 nc=18; // conducting cycles
12 noff=32; // off cycles
13
14 k=nc/(nc+noff); // duty ratio
15 Vor=Vs*sqrt(k); // V
16 Po=Vor**2/R; // W
17 Pi=Po; // W (losses are negligible)
18 Ior=Vor/R; //A
19 pf=Po/Vs/Ior; //W
20 Im=Vs*sqrt(2)/R; //A
21 Irms=Im*sqrt(k)/2; //A
22 Iav=k*Im/%pi; //A
23 printf ('\n (a) rms output voltage = %.0f V', Vor)
24 printf ('\n (b) Power output to load = %.1f W', Po)
25 printf ('\n (c) Power input to regulator = %.1f W',
Pi)
26 printf ('\n (d) input power factor = %.1f ', pf)
27 printf ('\n (e) average scr current = %.3f A', Iav)
28 printf ('\n rms scr current = %.3f A', Irms)
```

---

### Scilab code Exa 4.3 load voltage and rms current

```
1 //Ex 4.3 page 159
2
3 clc;
4 clear;
5 close;
6
7
8 R=10; // ohm
9 Vs=230; // V
10 f=50; // Hz
11 alpha = 90; // degree
12
13 Vor=Vs*sqrt(1/%pi*(%pi-alpha*pi/180+sin(2*alpha*pi
    /180)/2)); // V
14 Ior=Vor/R; // A
15 P=Ior**2*R; // W
16 pf=Vor/Vs; // power factor
17 printf('\n rms load voltage = %.2f V', Vor)
18 printf('\n rms load current = %.2f A', Ior)
19 printf('\n power input = %.2f W', P)
20 printf('\n load power factor = %.1f ', pf)
```

---

### Scilab code Exa 4.4 rms load voltage and rms current

```
1 //Ex 4.4 page 160
2
3 clc;
4 clear;
5 close;
6
```

```
7
8 R=30; // ohm
9 Vs=230; // V
10 f=50; // Hz
11 alpha = 45; // degree
12
13 Vor=Vs*sqrt(1/%pi*(%pi-alpha*pi/180+sin(2*alpha*pi
    /180)/2)); // V
14 Ior=Vor/R; // A
15 printf ('\n rms load voltage = %.2f V', Vor)
16 printf ('\n rms load current = %.2f A', Ior)
```

---

### Scilab code Exa 4.5 max voltage and current

```
1 //Ex 4.5 page 160
2
3 clc;
4 clear;
5 close;
6
7
8 R=10; // ohm
9 Vs=230; // V
10 f=50; // Hz
11 fi = 45; // degree
12
13 Vmax=Vs; // V(max supply voltage)
14 XL=R*tan(fi*pi/180); // ohm
15 Z=XL*sqrt(2); // ohm
16 Imax=Vs/Z; //A
17
18 printf ('\n max load voltage = %.2f V', Vmax)
19 printf ('\n max load current = %.3f A', Imax)
20 printf ('\n range of delay angle = %d to %d', 0, fi)
```

---

### Scilab code Exa 4.7 control range of firing angle

```
1 //Ex 4.7 page 161
2
3 clc;
4 clear;
5 close;
6
7
8 R=3; // ohm
9 wL=4; //ohm
10 Vs=230; // V
11 f=50; // Hz
12
13 fi=atan(wL/R)*180/%pi; //degree
14 printf('\n (i) control range of firing angle = %.2f
    to pi',fi)
15 Imax=Vs/sqrt(R**2+wL**2); // A
16 printf ('\n (ii) max rms load current = %.f A', Imax)
17 Pmax=Imax**2*R; //W
18 printf ('\n (iii) max power input to load = %.f W',
    Pmax)
19 pf_max=Pmax/Vs/Imax; // power factor
20 printf ('\n (iv) max power factor = %.1f ', pf_max)
21 Ithrms=Imax/sqrt(2); // A
22 Ithav=Ithrms/1.57; // A
23 printf ('\n (v) max rms thyristor current = %.3f A',
    Ithrms)
24 printf ('\n      max average thyristor current = %.3f
    A', Ithav)
```

---

# Chapter 5

## DC to DC Converters

Scilab code Exa 5.1 average load current

```
1 //Ex 5.1 page 184
2
3 clc;
4 clear;
5 close;
6
7 R=10; // ohm
8 Vs=230; // V
9 f=1*1000; // Hz
10 Ton=0.4; // ms
11 k=0.4 ; // duty cycle
12
13 Vo=Vs*k; //V
14 Ioav=Vo/R; // A
15 Vor=Vs*sqrt(k); // V
16 Po=Vor**2/R; // W
17 printf ('\n Average load current = %.1f A', Ioav)
18 printf ('\n Power delivered = %.2f W', Po)
```

---

### Scilab code Exa 5.2 duty ratio and chopping frequency

```
1 //Ex 5.2 page 185
2
3 clc;
4 clear;
5 close;
6
7 R=5; // ohm
8 Vs=300; // V
9 f=1*1000; // Hz
10 Ton=20; // ms
11 Toff=10; // ms
12
13 k= Ton/(Ton+Toff); // duty ratio
14 f=1000/(Ton+Toff); //Hz
15 Voav=Vs*k; // V
16 Ioav=Voav/R; // A
17 printf('\n duty ratio = %.3f',k)
18 printf('\n chopping frequency = %.2f Hz',f)
19 printf('\n Average load voltage = %.2f V', Voav)
20 printf('\n Average load current = %.2f A', Ioav)
```

---

### Scilab code Exa 5.3 chopping frequency

```
1 //Ex 5.3 page 185
2
3 clc;
4 clear;
5 close;
6
7 Vs=400; //V
8 alfa=0.25; // duty cycle
9 delta_I=10; // A
10 L=0.5; // H
```

```

11 R=0; // ohm
12
13 Vo=alfa*Vs; //V
14 //Vo+L*di/dt=Vs --- putting dt=Ton & di=delta_I
15 Ton=delta_I/((Vs-Vo)/L)*1000; // ms
16 T=Ton/alfa; // ms
17 f=1/T*1000; //Hz
18 printf ('\n chopping frequency = %d Hz',f)

```

---

### Scilab code Exa 5.5 new output voltage

```

1 //Ex 5.5 page 186
2
3 clc;
4 clear;
5 close;
6
7 Vs=220; //V
8 Vo=660; // V
9 Toff=100; // micro s
10
11 //Vo=Vs/(1- alfa )
12 alfa=1-Vs/Vo; // duty cycle
13 // alfa=Ton/(Ton+Toff)
14 Ton=alfa*Toff/(1-alfa); // micro s
15 T=Ton+Toff; //micro s
16 printf ('Pulse width of output voltage , Ton = %d
           micro s & T = %d micro s ',Ton,T)
17 //( ii ) reduce pulse width by 50%
18 Ton=Ton/2; // micro s
19 Toff=T-Ton; // micro s
20 alfa=Ton/(Ton+Toff); // duty cycle
21 Vo=Vs/(1-alfa); // V
22 printf ('\n New output voltage = %d V',Vo)

```

---

# Chapter 7

## Power Controllers their Applications

Scilab code Exa 7.1 speed of motor

```
1 //Ex 7.1 page 260
2
3 clc;
4 clear;
5 close;
6
7 N1=1000; // rpm
8 Va1=200; // V
9 alfa=60; // degree
10 Va2=230; // V
11
12 N2=2*Va2*sqrt(2)*cos(alfa*pi/180)*N1/Va1/pi
13 printf ('\n Speed of motor = %d rpm',N2)
14 // ans in the textbook is not accurate.
```

---

Scilab code Exa 7.2 duty ratio

```
1 //Ex 7.2 page 260
2
3 clc;
4 clear;
5 close;
6
7 N1=1100; // rpm
8 Va1=220; // V
9 N2=900; // rpm
10
11 Va2=Va1*N2/N1; // V
12 delta=Va2/Va1; // duty ratio
13 printf ('\n duty ratio = %.2f', delta)
```

---

### Scilab code Exa 7.3 triggering angle

```
1 //Ex 7.3 page 261
2
3 clc;
4 clear;
5 close;
6
7 N1=900; // rpm
8 Va1=198; // V
9 N2=500; // rpm
10 Vs=230; // V
11
12 Va2=Va1*N2/N1; // V
13 // 2*sqrt(2)*Vs*cos( alfa )/%pi=Va2
14 alfa=acos(Va2/(2*sqrt(2)*Vs)*%pi)*180/%pi; // degree
15
16 printf ('\n triggering angle = %.1f degree', alfa)
```

---

### Scilab code Exa 7.4 average armature current

```
1 //Ex 7.4 page 261
2
3 clc;
4 clear;
5 close;
6
7 Vs=230; // V
8 Ton=10; // ms
9 Toff=25; // ms
10 Ra=2; //ohm
11 N=1400; // rpm
12 k=0.5; // V/rad/s (back emf constant)
13 kt=0.5; // NM-A**-1 (torque constant)
14
15 Eb=N*2*pi*k/60; // V
16 Va=Vs*Ton/(Toff); // V
17 Ia=(Va-Eb)/Ra; // A
18 T=kt*Ia; // Nm
19 printf ('\n average armature current = %.2f A', Ia)
20 printf ('\n torque = %.3f Nm', T)
```

---