

Scilab Textbook Companion for Power Semiconductor Drives

by S. Sivanagaraju¹

Created by
Akshay Arun Raut
BE
Electrical Engineering
Government College Of Engineering,Karad
College Teacher
None
Cross-Checked by
None

July 30, 2019

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Power Semiconductor Drives

Author: S. Sivanagaraju

Publisher: Prentice Hall India Learning Pvt Ltd

Edition: 1

Year: 2009

ISBN: 8120336585

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Control of DC Motor by Single Phase Converters	5
2 Control of DC Motor by Three Phase Converters	35
3 Four Quadrant Operations of DC Drives	45
4 Chopper Controlled DC Drives	50
5 Stator Voltage Control of Induction Motor Drives	89
6 Control of Induction Motor Drives through Stator Frequency	106
7 Control of Induction Motor Drives from Rotor Side	113
8 Control of Synchronous Motor Drives	126

List of Scilab Codes

Exa 1.1	Ex1	5
Exa 1.2	Ex2	6
Exa 1.3	Ex3	7
Exa 1.4	Ex4	8
Exa 1.5	Ex5	8
Exa 1.6	Ex6	9
Exa 1.7	Ex7	11
Exa 1.8	Ex8	12
Exa 1.9	Ex9	14
Exa 1.10	Ex10	15
Exa 1.11	Ex11	16
Exa 1.12	Ex12	17
Exa 1.13	Ex13	18
Exa 1.14	Ex14	19
Exa 1.15	Ex15	20
Exa 1.16	Ex16	21
Exa 1.17	Ex17	23
Exa 1.18	Ex18	25
Exa 1.19	Ex19	27
Exa 1.20	Ex20	28
Exa 1.21	Ex21	29
Exa 1.22	Ex22	30
Exa 1.23	Ex23	31
Exa 1.24	Ex24	32
Exa 1.25	Ex25	33
Exa 1.26	Ex26	33
Exa 2.1	Ex1	35
Exa 2.2	Ex2	36

Exa 2.3	Ex3	37
Exa 2.4	Ex4	38
Exa 2.5	Ex5	39
Exa 2.6	Ex6	39
Exa 2.7	Ex7	40
Exa 2.8	Ex8	40
Exa 2.9	Ex9	41
Exa 2.10	Ex10	42
Exa 2.11	Ex11	42
Exa 2.12	Ex12	43
Exa 2.13	Ex13	44
Exa 3.1	Ex1	45
Exa 3.2	Ex2	46
Exa 3.3	Ex3	47
Exa 3.4	Ex4	47
Exa 3.5	Ex5	48
Exa 3.6	Ex6	48
Exa 4.1	Ex1	50
Exa 4.2	Ex2	51
Exa 4.3	Ex3	52
Exa 4.4	Ex4	53
Exa 4.5	Ex5	54
Exa 4.6	Ex6	54
Exa 4.7	Ex7	55
Exa 4.8	Ex8	56
Exa 4.9	Ex9	56
Exa 4.10	Ex10	57
Exa 4.11	Ex11	58
Exa 4.12	Ex12	59
Exa 4.13	Ex13	60
Exa 4.14	Ex14	60
Exa 4.15	Ex15	61
Exa 4.16	Ex16	61
Exa 4.17	Ex17	62
Exa 4.18	Ex18	63
Exa 4.19	Ex19	64
Exa 4.20	Ex20	65
Exa 4.21	Ex21	66

Exa 4.22	Ex22	67
Exa 4.23	Ex23	67
Exa 4.24	Ex24	68
Exa 4.25	Ex25	68
Exa 4.26	Ex26	69
Exa 4.27	Ex27	70
Exa 4.28	Ex28	71
Exa 4.29	Ex29	71
Exa 4.30	Ex30	72
Exa 4.31	Ex31	73
Exa 4.32	Ex32	74
Exa 4.33	Ex33	75
Exa 4.34	Ex34	75
Exa 4.35	Ex35	76
Exa 4.36	Ex36	77
Exa 4.37	Ex37	77
Exa 4.38	Ex38	78
Exa 4.39	Ex39	79
Exa 4.40	Ex40	79
Exa 4.41	Ex41	80
Exa 4.42	Ex42	81
Exa 4.43	Ex43	81
Exa 4.44	Ex44	82
Exa 4.45	Ex45	83
Exa 4.46	Ex46	83
Exa 4.47	Ex47	84
Exa 4.48	Ex48	85
Exa 4.49	Ex49	86
Exa 4.50	Ex50	87
Exa 4.51	Ex51	88
Exa 5.1	Ex1	89
Exa 5.2	Ex2	90
Exa 5.3	Ex3	91
Exa 5.4	Ex4	92
Exa 5.5	Ex5	93
Exa 5.6	Ex6	94
Exa 5.7	Ex7	95
Exa 5.8	Ex8	96

Exa 5.9	Ex9	97
Exa 5.10	Ex10	99
Exa 5.11	Ex11	100
Exa 5.12	Ex12	101
Exa 5.13	Ex13	102
Exa 5.14	Ex14	103
Exa 5.15	Ex15	104
Exa 6.1	Ex1	106
Exa 6.2	Ex2	108
Exa 6.3	Ex3	109
Exa 6.4	Ex4	110
Exa 6.5	Ex5	111
Exa 6.6	Ex6	112
Exa 7.1	Ex1	113
Exa 7.2	Ex2	114
Exa 7.3	Ex3	115
Exa 7.4	Ex4	116
Exa 7.5	Ex5	117
Exa 7.6	Ex6	117
Exa 7.7	Ex7	118
Exa 7.8	Ex8	118
Exa 7.9	Ex9	119
Exa 7.10	Ex10	120
Exa 7.11	Ex11	122
Exa 7.12	Ex12	123
Exa 7.13	Ex13	124
Exa 8.1	Ex1	126
Exa 8.2	Ex2	127
Exa 8.3	Ex3	128
Exa 8.4	Ex4	129
Exa 8.5	Ex5	131
Exa 8.6	Ex6	132

Chapter 1

Control of DC Motor by Single Phase Converters

Scilab code Exa 1.1 Ex1

```
1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 af=0 // Firing Angle of Converters in Field
5 Rf=200 //Field Resistance in ohm
6 T=50 //Load Torque in N-m
7 Kt=0.8 //Torque Constant in N-m/A^2
8 N=900 //Motor Speed in rpm
9 Ra=0.3 // Armature Resistance in ohm
10
11 //Solution
12 Vf=Vm*(1+cos(af))*(1/%pi)*1.414 //Voltage across
    Field in Volts
13 If=Vf/Rf //Field Current in Amp
14 Ia=T/(Kt*If) //Armature Current in Amp
15 w=(2*%pi*N)/60 //Angular Speed in rad/sec
16 Eb=Kt*If*w //Back Emf in Volts
17 Va=Eb+Ia*Ra // Voltage across Armature
18 A=%pi*Va*(1/Vm)*(1/1.414)
```

```

19 aa=acosd(A-1) //Firing Angle of Semi Converter in
   Armature Circuit
20 VaIa=Va*Ia //Power output of Converters in Armature
   Circuit in Watts
21 I=sqrt((180-aa)*(1/180))*Ia //Input Current
22 VA=Vm*I //Input VA
23 pf=VaIa/VA //Input Power Factor
24 //Result
25 printf ('\n\n The Field Current=%0.1f Amp\n\n',If)
26 printf ('\n\n The Firing Angle of Semi Converter in
   Armature Circuit=%0.1f degree\n\n',aa)
27 printf ('\n\n The Power Factor of Semi Converter in
   Armature Circuit=%0.1f\n\n',pf)

```

Scilab code Exa 1.2 Ex2

```

1 clc
2 // variable Initialization
3 Vm=208 //Supply Voltage In Volts
4 af=0 //Firing Angle Of Converters In Field
5 Rf=147 //Field Resistance In Ohm
6 Ra=0.25 //Armature Resistance In Ohm
7 T=45 //Load Torque In N-m
8 Kv=0.7032 //Motor Voltage Constant
9 N=1000 //Motor Speed In Rpm
10
11 //Solution
12 Vf=Vm*(1+cos(af))*(1/%pi)*1.414 //Voltage Across
   Field In Volts
13 If=Vf/Rf //Field Current In Amp
14 Ia=T/(Kv*If) //Armature Current In Amp
15 w=(2*%pi*N)/60 //Angular Speed In Rad/Sec
16 Eb=Kv*If*w //Back Emf In Volts
17 Va=Eb+Ia*Ra //Voltage Across Armature In Volts
18 A=%pi*Va*(1/Vm)*(1/1.414)

```

```

19 aa=acosd(A-1) //Delay Angle Of Semi Converter In
   Armature Circuit
20 VaIa=Va*Ia //Power Output Of Converters In Armature
   Circuit In Watts
21 I=sqrt((180-aa)*(1/180))*Ia //Input Current
22 VA=Vm*I //Input VA
23 Pf=VaIa/VA //Input Power Factor
24
25 //Result
26 printf('\n\n The Field Current=%0.1f Amp\n\n',If)
27 printf('\n\n The Delay Angle Of Semi Converter In
   Armature Circuit=%0.1f degree\n\n',aa)
28 printf('\n\n The Power Factor Of Semi Converter In
   Armature Circuit=%0.1f\n\n',Pf)
29 //The answers vary due to round off error(2nd and 3
   rd)

```

Scilab code Exa 1.3 Ex3

```

1 clc
2 //Variable Initialization
3 V=120 //Supply Voltage In Volts
4 Vm=120*1.414 //Max. Voltage In Volts
5 Ra=10 //Armature Resistance In Ohm
6 af=0 //Firing Angle Of Converter
7 Eb=60 //Back Emf In Volts
8
9 //Solution
10 Va=Vm*(1+cos(af))*(1/%pi)//Voltage Across armature
    In Volts
11 Ia=(Va-Eb)/Ra //Average Value Of Armature Current In
    Amp
12
13 //Result
14 printf('\n\n The Average Value Of Armature Current=

```

%0.1f Amp\n\n', Ia)

Scilab code Exa 1.4 Ex4

```
1 clc
2 //Variable Initialization
3 Vm=320 //Input Voltage In Volts
4 Eb=100 //Back Emf In Volts
5 Ra=5 //Armature Resistance In Ohm
6 af=45 // Firing Angle Of SCR In Degree
7 N=1200 //Speed Of Motor In RPM
8
9 //Solution
10 Va=Vm* (1/%pi)* (1+cosd(af)) //Voltage Across
    Armature In volts
11 Ia=(Va-Eb)/Ra //Armature Current Amp
12 W=(2*%pi*N)/60 //Angular Speed In rad/Sec.
13 K=Eb/W //Voltage Constant In V-rad/Sec
14 T=K*Ia //Torque Of Motor In N-m
15
16 //Result
17 printf('\n\n The Armature Current=%0.1f Amp\n\n',Ia)
18 printf('\n\n The Motor Torque=%0.1f N-m\n\n',T)
19 //The answers vary due to round off error
```

Scilab code Exa 1.5 Ex5

```
1 clc
2 //variable Initialization
3 Vm=230 //Input Voltage In Volts
4 Ra=0.5 //Armature Resistance In Ohm
5 Rf=190 //Field resistace in Ohm
6 N=1400 //Speed Of Motor In RPM
```

```

7 Ka=0.8 //Motor voltage constant in V/A-rad/sec
8 T=50 //Load Torque In N-m
9
10 //Solution
11 W=(2*%pi*N)/60 //Angular Speed In rad/Sec.
12 //Since the maximum field voltage and current is
   obtained at a Firing Angle of '0' degree
13 af=0 //Firing Angle Of SCR In Degree
14 Vf=(Vm*1.414)*(1+cosd(af))*(1/%pi) //field Voltage
   In volts
15 If=Vf/Rf //Field Current In Amp.
16 Ia=T/(Ka*If) //Armature current in Amp.
17 Eb=(Ka*If*W) //this value is wrongly calculated in
   book
18 Vdc=Eb+Ia*Ra //Voltage across armature in volts
19 //for the semi converter fed dc motor the armature
   voltage is given by...
20 A=%pi*Vdc*(1/Vm)*(1/1.414)
21 aa=acosd(A-1) //slight change occurs in ans as Eb is
   wrongly calculated in book
22
23 //Results
24 printf('\n\n The field Current =%0.1f Amp\n\n',If)
25 printf('\n\n The firing Angle Of Armature=%0.1f
   Degree\n\n',aa)
26 //The answer provided in the textbook is wrong(2nd
   answer)

```

Scilab code Exa 1.6 Ex6

```

1 clc
2 // Variable Initialization
3 Vm=200 //Supply Voltage in Volts
4 N=1000 //speed of motor in RPM
5 I=13 //Motor current in Ampere

```

```

6 Ra=3 //Armature circuit resistance in Ohm
7 L=100e-3 //Armature circuit Inductance in mH
8 V=230 //Ac Source voltage in Volts
9 f=50 //source Frequency in Hz
10 a=30
11 aa=(30*%pi)/180 //in rad/sec
12 N2=400
13 //Solution
14 P=atand((2*%pi*f*L)/Ra) // In Degree
15 Cot_P=1/tand(P)
16 A=exp(-%pi*Cot_P)
17 B=exp((-aa)*Cot_P)
18 Z=sqrt((Ra^2)+((2*%pi*f*L)^2)) //Impedance In Ohm
19 Eb=Vm-(I*Ra) //back emf in Volts
20 w=(2*%pi*N)/60 //Angular Speed in rad/sec
21 K=Eb/w
22 AA=(Ra*V*1.41)/(K*Z)
23 Wmc=AA*((sind(P)*B)-(sind(a-P)*A))*(1/(1-A)) //
   Critical Speed in rad/Sec
24 Wrpm=(Wmc*60)/(2*%pi) //speed in rpm
25 //As the motor speed of 400 rpm is less than the
   critical speed ,the drive is operating under
   continuous conduction mode
26 af=30 //firing angle in Degree
27 Va=(V*1.414)*(1+cosd(af))*(1/%pi) //Armature voltage
   in volts
28 //At 400 RPM
29 Eb1=Eb*(N2/N) //This Value Is Wrongly Calculated in
   Textbook
30 T=K*(Va-Eb1)*(1/Ra) //Torque in N-m
31 //Motor back emf for critical speed equal to 1149.67
   rpm
32 Ec=(Wrpm*Eb)/N //critical emf in volts
33 Tc=K*(Va-Ec)*(1/Ra) //Critical Torque in N-m
34 //Since the motor torque of 70 N-m is greater than
   the critical torque Tc ,the drive is operating in
   continuous conduction
35 Ia=T/K //Armature current in Amp

```

```

36 Eb2=Va-(Ia*Ra) // Back emf in Volts
37 Nm=(Eb2*N)/161 //Answer changed due wrong value is
    taken in book of Eb1
38
39 //Results
40 printf ('\n\n The motor Torque =%0.1f N-m \n\n',T)
41 printf ('\n\n The motor Speed =%0.1f RPM \n\n',Nm)
42 //The answer provided in the textbook is wrong

```

Scilab code Exa 1.7 Ex7

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 N=650 //speed of motor in RPM
5 I=100 //Motor current in Ampere
6 Ra=0.08 //Armature circuit resistance in Ohm
7 L=8e-3 //Armature circuit Inductance in mH
8 V=230 //Ac Source voltage in Volts
9 f=50 //source Frequency in Hz
10 a=60
11 aa=(60*pi)/180 //in rad/sec
12 a1=120
13 aa1=(120*pi)/180 //in rad/sec
14 N2=400
15 T=1000
16
17 //Solution
18 P=atand((2*pi*f*L)/Ra) // In Degree
19 Cot_P=1/(tand(P))
20 A=exp(-pi*Cot_P)
21 B=exp((-aa)*Cot_P)
22 Z=sqrt((Ra^2)+((2*pi*f*L)^2)) //Impedance In Ohm
23 Eb=Vm-(I*Ra) //back emf in Volts
24 w=(2*pi*N)/60 //Angular Speed in rad/sec

```

```

25 K=Eb/w
26 AA=(Ra*Vm*1.414)/(K*Z)
27 Wmc=AA*((sind(P)*B)-(sind(a-P)*A))*(1/(1-A)) // Critical Speed in rad/Sec
28 Wrpm=(Wmc*60)/(2*pi) //speed in rpm
29 //motor back emf for critical speed of 148 RPM
30 Ec=(Wrpm*Eb)/N //Critical emf in Volts
31 Va=(V*1.414)*(1+cosd(a))*(1/pi) //Armature voltage in volts
32 Tc=K*(Va-Ec)*(1/Ra) //Critical Torque in N-m
33 //The check condition is
34 Ia=T/K //Armature current in Amp
35 Eb2=Va-(Ia*Ra) // Back emf in Volts
36 Nm=(Eb2*N)/Eb//Motor speed in Rpm
37
38 B1=exp((-aa1)*Cot_P)
39 Wmc1=AA*((sind(P)*B1)-(sind(a1-P)*A))*(1/(1-A)) // Critical Speed in rad/Sec
40 Wrpm1=(Wmc1*60)/(2*pi) //speed in rpm
41 //motor back emf for critical speed of 154 RPM
42 Ec1=(Wrpm1*Eb)/N //Critical emf in Volts
43 Va1=(V*1.414)*(1+cosd(a1))*(1/pi) //Armature voltage in volts
44 Tc1=K*(Va1-Ec1)*(1/Ra) //Critical Torque in N-m
45 //The check condition is
46 Ia1=-T/K //Armature current in Amp
47 Eb3=Va1-(Ia1*Ra) // Back emf in Volts
48 Nm1=(Eb3*N)/Eb//Motor speed in Rpm
49
50 //Results
51 printf('\n\n The motor Speed =%0.1f RPM \n\n',Nm)
52 printf('\n\n The motor Speed =%0.1f RPM \n\n',Nm1)
53 //The answers vary due to round off error(1st answer )

```

Scilab code Exa 1.8 Ex8

```
1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 N=650 //speed of motor in RPM
5 I=100 //Motor current in Ampere
6 Ra=0.08 //Armature circuit resistance in Ohm
7 L=8e-3 //Armature circuit Inductance in mH
8 V=230 //Ac Source voltage in Volts
9 f=50 //source Frequency in Hz
10 a=60
11 aa=(60*pi)/180 //in rad/sec
12 N2=200
13
14 //Solution
15 P=atand((2*pi*f*L)/Ra) // In Degree
16 Cot_P=1/(tand(P))
17 A=exp(-pi*Cot_P)
18 B=exp((-aa)*Cot_P)
19 Z=sqrt((Ra^2)+((2*pi*f*L)^2)) //Impedance In Ohm
20 Eb=Vm-(I*Ra) //back emf in Volts
21 w=(2*pi*N)/60 //Angular Speed in rad/sec
22 K=Eb/w
23 AA=(Ra*Vm*1.414)/(K*Z)
24 Wmc=AA*((sind(P)*B)-(sind(a-P)*A))*(1/(1-A)) //
   Critical Speed in rad/Sec
25 Wrpm=(Wmc*60)/(2*pi) //speed in rpm
26 //since the speed of 200 rpm is less than the
   critical speed ,the drive is operating under
   continuous conduction .Hence
27 Va=(V*1.414)*(1+cosd(a))*(1/pi) //Armature voltage
   in volts
28 Ec=(N2*Eb)/N //Critical emf in Volts
29 T=K*(Va-Ec)*(1/Ra) //Critical Torque in N-m
30
31 //For
32 a1=120
```

```

33 aa1=(120*%pi)/180 //in rad/sec
34 B1=exp((-aa1)*Cot_P)
35 Wmc1=AA*((sind(P)*B1)-(sind(a1-P)*A))*(1/(1-A)) //
   Critical Speed in rad/Sec
36 Wrpm1=(Wmc*60)/(2*%pi) //speed in rpm
37 //since the motor speed of 200 RPM is greater than
   the critical speed the drive is operating under
   discontinuous condition for which
38 AA1=(Ra*Vm*1.414)/(Ec*Z)
39 e1=AA1*((sind(P)*A)-(sind(a1-P)*B1))+B1
40 b=log(e1))/Cot_P
41 b=117.38
42 Va1=((Vm*1.41*(1+cosd(a1))+(%pi+((a1-b)*%pi/180))*Ec
   ))/%pi //square root of 2 is rounded off as 1.4
43 T1=K*(Va1-Ec)/Ra //Critical Torque in N-m
44
45 //Results
46 printf('\n\n The motor Torque =%0.1f N-m \n\n',T)
47 printf('\n\n The motor Torque=%0.1f N-m \n\n',T1)
48 //The answers vary due to round off error

```

Scilab code Exa 1.9 Ex9

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ia=50 //Motor Armature current in Ampere
5 Ra=0.25 //Armature circuit resistance in Ohm
6 Rf=200 // Field circuit resistance in Ohm
7 f=50 //source Frequency in Hz
8 a=45 //Firing angle in the armature circuit in
   degree
9 Vd=1 //Brush contact drop V/brush
10 af=0 //Firing angle in the field circuit in degree
11 Kf=1.1 //Torque and voltage constant

```

```

12
13 // Solution
14 Vf=(2*Vm*1.414)*cosd(af)*(1/%pi) // Voltage in field
    circuit in Volts
15 //When a=45 degree
16 Va=(2*Vm*1.414)*cosd(a)*(1/%pi) // Voltage in
    Armature circuit in Volts
17 If=Vf/Rf // Field current in Amp.
18 T=Kf*Ia*If // Torque in N-m
19 Eb=Va-(Ia*Ra)-Vd*2 // Back emf in Volts
20 W=Eb/(Kf*If) // Angular speed in Rad/sec
21 N=W*60/(2*%pi) // Motor speed in RPM
22
23 // Results
24 printf('\n\n The motor Torque =%0.1f N-m \n\n',T)
25 printf('\n\n The motor Speed=%0.1f RPM \n\n',N)

```

Scilab code Exa 1.10 Ex10

```

1 clc
2 // Variable Initialization
3 Vm=230 // Supply Voltage in Volts
4 R=0.25 // Combined Field and Armature circuit
    resistance in Ohm
5 N=1000 // Motor speed in Rpm
6 Kaf=0.03 // Constant in N-m/A^2
7 KrCs=0.075 // Constant in V-S/Rad
8 a=30 // firing angle in Degree
9
10 // Solution
11 // For a full converter controlled dc motor drive
12 W=(2*%pi*N)/60 // Angular speed in Rad/sec
13 Ia=((((2*Vm*1.414)/%pi)*cosd(a))-(KrCs*W))/(R+(Kaf*W
    )) // Armature current in Amp
14 T=Kaf*(Ia^2) // Torque in N-m

```

```

15 Va=(2*Vm*1.414)*cosd(a)*(1/%pi) // Average voltage in
   volts
16 Po=Va*Ia //Output power in Watt
17 Irms=Ia*sqrt((180-a)/180) //Rms Current in Amp
18 Pi=Vm*Irms
19 pf=Po/Pi //Power factor
20
21 // Results
22 printf('\n\n The motor Current =%0.1f Amp \n\n',Ia)
23 printf('\n\n The motor Torque=%0.1f N-m \n\n',T)
24 printf('\n\n The Supply Power Factor=%0.1f Lag\n\n',
   pf)
25 //The answers vary due to round off error

```

Scilab code Exa 1.11 Ex11

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=0.5 //Armature circuit resistance in Ohm
5 Irms=25 //Armature current in Amp
6 Nr=800 //Motor speed in Rpm
7 Kaf=0.172 //Motor Voltage Constant in V/rpm
8 a=60 //firing angle in Degree
9
10 //Solution
11 //CASE:A
12 //For motoring action
13 Ka=(Kaf*60)/(2*%pi) //Constant in V-s/rad
14 T=Ka*Irms //Torque of motor in N-m
15 Va=(2*Vm*1.414)*cosd(a)*(1/%pi) // Average voltage in
   Volts
16 Eb=Va-(Irms*Ra) //Back Emf in Volts
17 N=Eb/Kaf //Speed of motor in Rpm
18 //The supply current is square wave if motor current

```

```

        is constant and ripple-free with Amplitude 25A
19 P=Vm*Irms //Supply VA in Watt
20 //Power from supply is real power if losses in
   converter are neglected
21 Ps=Va*Irms //Power in Watt
22 pf=Ps/P //Power factor lag
23
24 //CASE:B
25 //For polarity reversal (regeneration action)
26 Eb1=-Eb //Back emf in Volts
27 Va1=Eb1+(Irms*Ra)
28 af=acosd((Va1*pi)/(2*Vm*1.414)) //Firing angle in
   Degree
29 //Power fed from DC Machine
30 Pdc=Eb*Irms //Power in watt
31 //Power lost in armature resistance
32 PL=((Irms)^2)*Ra //Power in Watt
33 //Power fed back to ac supply is
34 PF=Pdc-PL //Power in watt
35
36 //Results
37 printf('\n\n The motor Torque=%0.1f N-m \n\n',T)
38 printf('\n\n The motor Speed =%0.1f RPM \n\n',N)
39 printf('\n\n The Supply Power Factor=%0.1f Lag\n\n',
   pf)
40 printf('\n\n The Firing Angle=%0.1f Degree\n\n',af)
41 printf('\n\n The Power fed back to Supply=%0.1f Watt
   \n\n',PF)
42 //The answers vary due to round off error

```

Scilab code Exa 1.12 Ex12

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts

```

```

4 Ra=0.3 //Armature circuit resistance in Ohm
5 I=18 //Rated current in Amp
6 Nr=1500 //Motor speed in Rpm
7 a=45 //firing angle in Degree
8 Vs=220 //input in volts
9
10 //Solution
11 Va=(2*Vm*1.414)*cosd(a)*(1/%pi) //Average voltage in
   Volts
12 Eb=Va-(I*Ra) //Back emf in volts
13 //When the polarity of the back emf is reversed ,the
   machine would act as generator and hence the
   governing equation
14 Va=-Eb+(I*Ra) //Armature voltage in volts
15 af=acosd((Va*%pi)/(2*Vs*sqrt(2))) //Firing angle in
   Degree (This value is Wrongly calculated in
   Textbook)
16 Pg=Eb*I //Power generated in Watt
17 Pl=((I)^2)*Ra //Power loss in armature in Watt
18 P=Pg-Pl //Power fed to the supply in Watt
19
20 //Results
21 printf('\n\n The Firing Angle=%0.1f Degree\n\n',af)
22 printf('\n\n The Power fed back to Supply=%0.1f Watt
   \n\n',P)
23 //The answer provided in the textbook is wrong(1st
   answer)

```

Scilab code Exa 1.13 Ex13

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=1 //Armature circuit resistance in Ohm
5 I=12 //Rated current in Amp

```

```

6 Nr=1500 //Motor speed in Rpm
7 Va=210 //Motor voltage in volts
8 N1=1200 //Speed in RPM
9
10 //Solution
11 Eb=Va-(I*Ra) //Back emf in volts
12 N=(Nr*2*pi)/60 //Speed in Rad/sec
13 Ka=Eb/N //Constant
14 //Current at rated torque
15 //At 1200 Rpm
16 Eb1=(N1*Eb)/Nr
17 af=acosd(((I*Ra)+Eb1)*pi)/(2*Vm*1.414)) //Firing
    angle in Degree
18 //At Eb=-198 V at speed 1500 RPM
19 af1=acosd(((I*Ra)-Eb)*pi)/(2*Vm*1.414)) //Firing
    angle in Degree
20 //But reversal of field of armature forward
    regeneration is obtained
21 Ka1=-Ka
22 W=-Eb/Ka1 //Angular speed in Rad/sec (Wrongly
    calculated in book, wrong value of Eb is taken)
23 N1=(W*60)/(2*pi) //Speed in Rpm
24
25 //Results
26 printf('\n\n The Firing Angle=%0.1f Degree\n\n',af)
27 printf('\n\n The Firing Angle=%0.1f Degree\n\n',af1)
28 printf('\n\n The motor Speed =%0.1f RPM \n\n',N1)
29 //The answer provided in the textbook is wrong(3rd
    answer only)

```

Scilab code Exa 1.14 Ex14

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts

```

```

4 Ra=0.75 //Armature circuit resistance in Ohm
5 I=8 //Armature current in Amp
6 Nr=1200 //Motor speed in Rpm
7 Va=220 //Rated voltage of motor in Volts
8 a=45 //firing angle in Degree
9 T=8 //Motor torque in N-m
10 Nr1=800 //Speed in Rpm
11
12
13 //Solution
14 N=(Nr*2*pi)/60 //Speed in Rad/sec
15 Kaf=(Va-I*Ra)/N //Motor Constant
16 // (A) For torque of 8 N-m
17 Ia=T/Kaf //Armature Current in Amp
18 V=(2*Vm*1.414)*cosd(a)*(1/pi) // Average voltage in
   Volts
19 W=(V-Ia*Ra)/Kaf //Angular speed in Rad/sec
20 N=(W*60)/(2*pi) //Speed in Rpm
21 // (B) a=45 Degree
22 N1=(Nr1*2*pi)/60 //Speed in Rad/sec
23 Ia1=(V-Kaf*N1)/Ra //armature current in amp
24 T1=Kaf*Ia1 //Torque in N-m
25
26 //Results
27 printf ('\n\n The motor Speed =%0.1f RPM \n\n',N)
28 printf ('\n\n The motor Torque=%0.1f N-m \n\n',T1)
29 //The answers vary due to round off error

```

Scilab code Exa 1.15 Ex15

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=0.2 //Armature circuit resistance in Ohm
5 I=80 //Rated current in Amp

```

```

6 Nr=1200 //Motor speed in Rpm
7 V=220 //Rated voltage of motor in Volts
8 a=150 //firing angle in Degree
9 Nr1=-700 //Speed in Rpm
10
11 //Solution
12 N=(Nr*2*pi)/60 //Speed in Rad/sec
13 Kaf=(V-I*Ra)/N //Motor Constant in N-m/A
14 // (A) For rated motor torque
15 Va=(2*Vm*1.414)*cosd(a)*(1/pi) //Average voltage in
   Volts
16 N1=(Nr1*2*pi)/60 //Speed in Rad/sec
17 af=acosd(((Kaf*N1)+(I*Ra))*pi/(2*Vm*1.414)) //Firing
   angle in Degree
18 Eb1=V-(I*Ra) //Back emf in Volts
19 Eb2=(Nr1/Nr)*Eb1 //Back emf in Volts
20 Va1=Eb2+(I*Ra) //Armature voltage in volts
21 af1=acosd((Va1*pi)/(2*Vm*1.414)) //Firing angle in
   Degree
22 // (B) Half rated Torque
23 Ia=(1/2)*I //Armature current in Amp
24 W=(Va-(Ia*Ra))/Kaf //Angular speed in Rad/sec
25 N=(W*60)/(2*pi) //Speed in Rpm
26
27 //Results
28 printf('\n\n The Firing Angle=%0.1f Degree\n\n',af1)
29 printf('\n\n The motor Speed=%0.1f RPM \n\n',N)
30 //The answers vary due to round off error(2nd only)

```

Scilab code Exa 1.16 Ex16

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=0.05 //Armature circuit resistance in Ohm

```

```

5 L=0.85e-3 // Inductance in mH
6 N=750 // Motor speed in Rpm
7 V=220 // Rated voltage of motor in Volts
8 a=60 // firing angle in Degree
9 La=0.75e-3 // External Inductance in mH
10 I=175 //motor current in Amp
11 f=50 //source Frequency in Hz
12
13 // Solution
14 P=atand((2*pi*f*L)/Ra) // In Degree
15 Z=sqrt((Ra^2)+((2*pi*f*L)^2)) //Impedance In Ohm
16 Eb=V-(I*Ra) //back emf in Volts
17 w=(2*pi*N)/60 //Angular Speed in rad/sec
18 K=Eb/w
19 Cot_P=1/(tand(P))
20 A=exp(-%pi*Cot_P)
21 AA=(Ra*Vm*1.414)/(K*Z)
22 Wmc=AA*sind(a-P)*((1+A)/(A-1)) // Critical Speed in
   rad/Sec
23 Wrpm=(Wmc*60)/(2*pi) //speed in rpm
24 //Since the motor Speed is greater than critical
   Value Wmc ,The drive is operating under
   discontinuous conduction
25 //At N=600 Rpm
26 N1=600 //Speed in Rpm
27 Eb1=(N1/N)*Eb //Back emf in Volts
28 //By trial and error method
29 b=201.45 //Bita in Degree
30 Va=((Vm*1.414)*(cosd(a)-cosd(b))+(%pi+(a-b)*(%pi
   /180))*(Eb1))/(1/%pi) //Armature voltage in Volts
31 Ia=(Va-Eb1)/Ra //Armature current in Amp
32 T=K*Ia //Torque in N-m
33
34 //La=2.85 mH
35 N2=-400
36 a1=120
37 P1=atand((2*pi*f*La)/Ra) // In Degree
38 Cot_P1=1/(tand(P1))

```

```

39 Eb2=(N2/N)*Eb //Back emf in Volts
40 Z1=sqrt((Ra^2)+((2*pi*f*La)^2)) //Impedance In Ohm
41 AA1=(Ra*Vm*1.414)/(K*Z1)
42 A1=exp(-%pi*Cot_P1)
43 Wmc1=AA1*sind(a1-P1)*((1+A1)/(A1-1)) // Critical Speed
    in rad/Sec
44 Wrpm1=(Wmc1*60)/(2*pi) //speed in rpm
45 //By trial and error method
46 b1=297.5//Bita in Degree
47 Va1=((Vm*1.414)*(cosd(a1)-cosd(b1))+(%pi+(a1-b1)*(
    %pi/180))*(Eb2))*(1/%pi) //Armature voltage in
    Volts
48 Ia1=(Va1-Eb2)/Ra //Armature current in Amp
49 T1=K*Ia1//Torque in N-m
50
51 //Since the motor speed (-600 rpm) is less than
    critical speed (-409.17 Rpm) the drive's operation
    is continuous condition
52 N3=-600
53 Va2=(2*1.414*Vm)*(cosd(a1))*(1/%pi)
54 Eb3=(N3/N)*Eb //Back emf in Volts
55 Ia2=(Va2-Eb3)/Ra //Armature current in Amp
56 T2=K*Ia2//Torque in N-m
57
58 //Results
59 printf('\n\n The motor Torque =%0.1f N-m \n\n',T)
60 printf('\n\n The motor Torque =%0.1f N-m \n\n',T1)
61 printf('\n\n The motor Torque =%0.1f N-m \n\n',T2)
62 //The answers vary due to round off error

```

Scilab code Exa 1.17 Ex17

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts

```

```

4 Ra=2 //Armature circuit resistance in Ohm
5 L=50e-3 //Inductance in mH
6 N=1500 //Motor speed in Rpm
7 V=220 //Rated voltage of motor in Volts
8 a=60 //firing angle in Degree
9 a1=120 //firing angle in Degree
10 I=10 //motor current in Amp
11 f=50 //source Frequency in Hz
12
13 //Solution
14 P=atan((2*pi*f*L)/Ra) // In Degree
15 Z=sqrt((Ra^2)+((2*pi*f*L)^2)) //Impedance In Ohm
16 Eb=V-(I*Ra) //back emf in Volts
17 w=(2*pi*N)/60 //Angular Speed in rad/sec
18 K=Eb/w //value obtain is 1.2732395 approximating to
1.27
19 K=1.27 //Approximation of K as per book and our
obtained value
20 //At No Load
21 Wo=(Vm*1.414)/K //Angular Speed in rad/sec (For 0<a<
%pi/2)
22 No=Wo*(60/(2*pi)) //Speed in Rpm
23 Cot_P=1/tan(P)
24 A=exp(-pi*Cot_P)
25 AA=(Ra*Vm*1.414)/(K*Z)
26 Wmc=AA*sind(a-P)*((1+A)/(A-1)) //Critical Speed in
rad/Sec
27 Wrpm=(Wmc*60)/(2*pi) //speed in rpm
28 Eb1=(Wrpm*Eb)/N
29 //By trial and error method
30 b=240.45 //Beta in Degree
31 bx=249.45 //Beta in Degree
32 Va=((Vm*1.414)*(cosd(a)-cosd(bx))+(%pi+(a-b)*(%pi
/180))*(Eb1))*(1/pi) //Armature voltage in Volts
33 Ia=(Va-Eb1)/Ra //Armature current in Amp
34 T=K*Ia //Torque in N-m
35
36 //At a1=120

```

```

37 Wmc1=AA*sind(a1-P)*((1+A)/(A-1)) // Critical Speed in
    rad/Sec
38 Wrpm1=(Wmc1*60)/(2*pi) //speed in rpm
39 Wo1=(Vm*1.414*sind(a1))/1.273 // Angular Speed in rad/
    sec (For 0<a<%pi/2)&K=1.273
40 No1=Wo1*(60/(2*pi)) //Speed in Rpm
41 Eb2=(Wrpm1*Eb)/N
42 //By trial and error method
43 b1=217.2 //Beta in Degree
44 Va1=((Vm*1.414)*(cosd(a1)-cosd(b1))-((%pi+((a1-b1)
    *(1/180))*%pi)*Eb2))*(1/%pi) //Armature voltage
    in Volts
45 Ia1=(Va1-Eb2)/Ra //Armature current in Amp
46 T1=K*Ia1 //Torque in N-m
47
48 // Results
49 printf('\n\n The motor No load Speed =%0.1f RPM \n\n',
    ,No)
50 printf('\n\n The motor Critical Speed =%0.1f RPM \n\n',
    ,Wrpm)
51 printf('\n\n The motor Torque =%0.1f N-m \n\n',T)
52 printf('\n\n The motor No load Speed =%0.1f RPM \n\n',
    ,No1)
53 printf('\n\n The motor Critical Speed =%0.1f RPM \n\n',
    ,Wrpm1)
54 printf('\n\n The motor Torque =%0.1f N-m \n\n',T1)
55 //The answers vary due to round off error

```

Scilab code Exa 1.18 Ex18

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=1.8 //Armature circuit resistance in Ohm
5 L=32e-3 //Inductance in mH

```

```

6 N=1200 //Motor speed in Rpm
7 V=220 //Rated voltage of motor in Volts
8 a=60 //firing angle in Degree
9 I=15 //motor current in Amp
10 f=50 //source Frequency in Hz
11
12 //Solution
13 P=atand((2*pi*f*L)/Ra) // In Degree
14 Z=sqrt((Ra^2)+((2*pi*f*L)^2)) //Impedance In Ohm
15 Eb=V-(I*Ra) //back emf in Volts
16 w=(2*pi*N)/60 //Angular Speed in rad/sec
17 K=Eb/w
18 Cot_P=1/tand(P)
19 A=exp(-pi*Cot_P)
20 AA=(Ra*Vm*1.414)/(K*Z)
21 Wmc=AA*sind(a-P)*((1+A)/(A-1)) // Critical Speed in
   rad/Sec
22 Wrpm=(Wmc*60)/(2*pi) //speed in rpm
23 //Since the motor Speed is greater than critical
   Value Wmc ,The drive is operating under
   discontinuous conduction
24 //At N=600 Rpm
25 N1=450 //Speed in Rpm
26 Eb1=(N1/N)*Eb //Back emf in Volts
27 //By trial and error method
28 b=239.4 //Bita in Degree
29 Va=((Vm*1.414)*(cosd(a)-cosd(b))*(pi+(a-b)*(pi
   /180))*(Eb1))/(1/pi) //Armature voltage in Volts
30 Ia=(Va-Eb1)/Ra //Armature current in Amp
31 T=K*Ia //Torque in N-m
32 //Since the motor Speed is greater than critical
   Value Wmc ,The drive is operating in
   discontinuous mode at
33 N2=1500
34 Eb2=(N2/N)*Eb //Back emf in Volts
35 //By trial and error method
36 b1=172.2 //Bita in Degree
37 Va1=((Vm*1.414)*(cosd(a)-cosd(b))*(pi+(a-b)*(pi
   /180))*(Eb2))/(1/pi)

```

```

/180)*(Eb2))*(1/%pi) //Wrong calculation in book
they have taken value of beta as 17.2 instead of
172.2
38 Ia1=(Va1-Eb2)/Ra //Armature current in Amp
39 T1=K*Ia1//Torque in N-m
40
41 //Results
42 printf('\n\n The motor Torque =%0.1f N-m \n\n',T) //
The answers vary due to round off error
43 printf ('\n\n The motor Torque =%0.1f N-m \n\n',T1)
44 //The answer provided in the textbook is wrong

```

Scilab code Exa 1.19 Ex19

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=0.05 //Armature circuit resistance in Ohm
5 La=3e-3 //Inductance in mH
6 N=750 //Motor speed in Rpm
7 V=220 //Rated voltage of motor in Volts
8 a=60 //firing angle in Degree
9 I=175 //motor current in Amp
10 f=50 //source Frequency in Hz
11
12 //La=2.85 mH
13 N2=-400
14 a1=120
15 P1=atand((2*%pi*f*La)/Ra) // In Degree
16 Eb=V-(I*Ra) //back emf in Volts
17 w=(2*%pi*N)/60 //Angular Speed in rad/sec
18 K=Eb/w
19 Cot_P1=1/(tand(P1))
20 Eb1=(N2/N)*Eb //Back emf in Volts
21 Z1=sqrt((Ra^2)+((2*%pi*f*La)^2)) //Impedance In Ohm

```

```

22 AA1=(Ra*Vm*1.414)/(K*Z1)
23 A1=exp(-%pi*Cot_P1)
24 Wmc1=AA1*sind(a1-P1)*((1+A1)/(A1-1)) // Critical Speed
      in rad/Sec
25 Wrpm1=(Wmc1*60)/(2*%pi) // speed in rpm
26 Eb2=(Wrpm1*Eb)/N
27 a2=150
28 Va=(2*1.414*Vm)*(cosd(a2))*(1/%pi)
29 Ia=(Va-Eb2)/Ra
30 T=K*Ia // Torque in N-m
31 //As the torque of 400 N-m is greater than T ,hence
      the operation is in Continuous conduction mode
32 T1=400
33 Ia1=T1/K
34 Eb3=Va-(Ia1*Ra)
35 Ns=(Eb3*N)/Eb
36 //As the torque of 400 N-m is less than T ,hence the
      operation is in Discontinuous conduction mode
37 Z=0.2716
38 q=V*1.414/Z
39 //nothing is solved in textbook using numericals
40 //By Trial and error method beta is calculated
41 b=233.240
42
43 //Results
44 printf ('\n\n The motor Speed =%0.1f rpm \n\n',Ns)

```

Scilab code Exa 1.20 Ex20

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=0.25 //Combined Field and Armature circuit
      resistance in Ohm
5 N=1000 //Motor speed in Rpm

```

```

6 V=210 //Rated voltage of motor in Volts
7 a=30 //firing angle in Degree
8 Kaf=0.03 //Constant in N-m/A^2
9 Kres=0.075 //Constant in V-s/Rad
10
11 //Solution
12 //For semi-converter controlled Dc Drive
13 W=(2*%pi*N)/60 //angular speed in Rad/sec
14 Ia=((Vm*1.414)/%pi)*(1+cosd(a))-(Kres*W))*(1/(Ra+
    Kaf*W)) //Armature current in Amp
15 T=Kaf*(Ia)^2 //Torque in N-m
16 Va=(Vm*1.414)*(1+cosd(a))*(1/%pi) //Average voltage
    in VoltsI
17 Irms=Ia*((180-a)/180)^(1/2) //RMS Current in Amp
18 Pa=Va*Ia //Power in Watt
19 Pi=Vm*Irms //Input power in Watt
20 Pf=(Pa/Pi) //Power Factor in Lag
21
22 //Results
23 printf ('\n\n The motor Torque =%0.1f N-m \n\n',T)
24 printf ('\n\n The motor Current =%0.1f Amp \n\n',Irms
    )
25 printf ('\n\n The Supply Power Factor =%0.1f Lag \n\n
    ',Pf)

```

Scilab code Exa 1.21 Ex21

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=0.75 //Combined Field and Armature circuit
    resistance in Ohm
5 N=1300 //Motor speed in Rpm
6 V=210 //Rated voltage of motor in Volts
7 a=45 //firing angle in Degree

```

```

8 Kaf=0.03 //Constant in N-m/A^2
9 Kres=0.075 //Constant in V-s/Rad
10
11 //Solution
12 //For semi-converter controlled Dc Drive
13 W=(2*pi*N)/60 //angular speed in Rad/sec
14 Ia=((Vm*1.414)/pi)*(1+cosd(a))-(Kres*W)*(1/(Ra+
    Kaf*W))//Armature current in Amp
15 T=Kaf*(Ia)^2//Torque in N-m
16 I=(T/Kaf)^(1/2)//motor current in Amp
17 Va=(Vm*1.414)*(1+cosd(a))*(1/pi)//Average voltage
    in Volts
18 //Input Power if losses are neglected
19 Ps=Va*I //Power loss in Watt
20 Pi=Vm*I*(5/6)^0.5 //power input in watt
21 Pf=(Ps/Pi)//Power Factor in Lag
22
23 //Results
24 printf('\n\n The motor Torque =%0.1f N-m \n\n',T)
25 printf('\n\n The motor Current =%0.1f Amp \n\n',I)
26 printf('\n\n The Supply Power Factor =%0.1f Lag \n\n',
    ,Pf)

```

Scilab code Exa 1.22 Ex22

```

1 clc
2 // Variable Initialization
3 Vm=240//Supply Voltage in Volts
4 Ra=0.9//Combined Field and Armature circuit
    resistance in Ohm
5 N=900 //Motor speed in Rpm
6 V=220//Rated voltage of motor in Volts
7 a=45 //firing angle in Degree
8 Kaf=0.035 //Constant in N-m/A^2
9

```

```

10 // Solution
11 //For semi-converter controlled Dc Drive
12 Va=(Vm*1.414)*(1+cosd(a))*(1/%pi)//Average voltage
   in Volts
13 W=(2*%pi*N)/60 //angular speed in Rad/sec
14 Ia=Va/(Ra+W*Kaf)//Current in Amp
15 T=Kaf*(Ia)^2//Torque in N-m
16
17 // Results
18 printf ('\n\n The motor Current =%0.1f Amp \n\n',Ia)
19 printf ('\n\n The motor Torque =%0.1f N-m \n\n',T)

```

Scilab code Exa 1.23 Ex23

```

1 clc
2 // Variable Initialization
3 Vm=250 //Supply Voltage in Volts
4 Ra=0.3 //Combined Field and Armature circuit
   resistance in Ohm
5 N=900 //Motor speed in Rpm
6 V=220 //Rated voltage of motor in Volts
7 a=30 //firing angle in Degree
8 Kaf=0.03 //Constant in N-m/A^2
9 Kres=0.075 //Constant in V-s/Rad
10
11 //Solution
12 W=(2*%pi*N)/60 //angular speed in Rad/sec
13 Ia=((Vm*1.414)/%pi)*(1+cosd(a))-(Kres*W)*(1/(Ra+
   Kaf*W)) //Armature current in Amp
14 T=Kaf*(Ia)^2//Torque in N-m
15 I=(T/Kaf)^(1/2) //motor current in Amp
16 //The motor Terminal voltage would be given by the
   output voltage of the converter
17 Va=(Vm*1.414)*(1+cosd(a))*(1/%pi)//Output voltage in
   Volts

```

```

18
19 // Results
20 printf ('\n\n The motor Torque =%0.1f N-m \n\n',T)
21 printf ('\n\n The motor Current =%0.1f Amp \n\n',I)
22 printf ('\n\n The motor output voltage =%0.1f Volts\n
          \n',Va)

```

Scilab code Exa 1.24 Ex24

```

1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=0.25 //Combined Field and Armature circuit
           resistance in Ohm
5 N=1000 //Motor speed in Rpm
6 V=210 //Rated voltage of motor in Volts
7 a=30 //firing angle in Degree
8 Kaf=0.03 //Constant in N-m/A^2
9 Kres=0.075 //Constant in V-s/Rad
10
11 //Solution
12 //For Full-converter controlled Dc Drive
13 W=(2*pi*N)/60 //angular speed in Rad/sec
14 Ia=((2*Vm*1.414)/pi)*(cosd(a))-(Kres*W)*(1/(Ra+
           Kaf*W)) //Armature current in Amp
15 T=Kaf*(Ia)^2 //Torque in N-m
16 Va=(2*Vm*1.414)*(cosd(a))*(1/pi) //Average voltage
           in Volts
17 //Input Power if losses are neglected
18 Ps=Va*Ia //Power loss in Watt
19 Pi=Vm*Ia //power input in watt
20 Pf=(Ps/Pi) //Power Factor in Lag
21
22 //Results
23 printf ('\n\n The motor Current =%0.1f Amp \n\n',Ia)

```

```
24 printf('\n\n The motor Torque =%0.1f N-m \n\n',T)
25 printf('\n\n The Supply Power Factor =%0.1f Lag \n\n
      ',Pf)//The answers vary due to round off error
```

Scilab code Exa 1.25 Ex25

```
1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
4 Ra=2 //Combined Field and Armature circuit resistance
      in Ohm
5 Kaf=0.23 //Constant in H
6 TL=20 //Load Torque in N-m
7 a=65 //firing angle in Degree
8
9 //Solution
10 Ia=(TL/Kaf)^(1/2) //Average Armature current in Amp
11 V=(2*Vm*1.414)*cosd(a)*(1/%pi) //Average voltage in
      Volts
12 W=(V-Ia*Ra)/(Kaf*Ia) //Angular speed in Rad/sec
13 N=(W*60)/(2*%pi) //Speed in Rpm
14
15 //Results
16 printf('\n\n The motor Average Armature Current =%0
      .1f Amp \n\n',Ia)
17 printf('\n\n The motor Average Speed =%0.1f RPM \n\n
      ',N)//The answers vary due to round off error
```

Scilab code Exa 1.26 Ex26

```
1 clc
2 // Variable Initialization
3 Vm=230 //Supply Voltage in Volts
```

```

4 Ra=0.75 //Combined Field and Armature circuit
            resistance in Ohm
5 N=1300 //Motor speed in Rpm
6 V=210 //Rated voltage of motor in Volts
7 a=45 //firing angle in Degree
8 Kaf=0.03 //Constant in N-m/A^2
9 Kres=0.075 //Constant in V-s/Rad
10
11 //Solution
12 //For Full-converter controlled Dc Drive
13 W=(2*pi*N)/60 //angular speed in Rad/sec
14 Ia=((2*Vm*1.414)/pi)*(cosd(a))-(Kres*W))*(1/(Ra+
            Kaf*W)) //Armature current in Amp
15 T=Kaf*(Ia)^2 //Torque in N-m
16 I=(T/Kaf)^(1/2) //motor current in Amp
17 Va=(2*Vm*1.414)*(cosd(a))*(1/pi) //Average voltage
            in Volts
18 //Input Power if losses are neglected
19 Ps=Va*I //Power loss in Watt
20 Pi=Vm*I //power input in watt
21 Pf=(Ps/Pi) //Power Factor in Lag
22
23 //Result
24 printf('\n\n The motor Torque =%0.1f N-m \n\n',T)
25 printf('\n\n The Supply Power Factor =%0.1f Lag \n\n',
            ,Pf)

```

Chapter 2

Control of DC Motor by Three Phase Converters

Scilab code Exa 2.1 Ex1

```
1 clc
2 //variable initialisation
3 a1=0 // Initial Firing Angle of Converter
4 Vl=460 //Line to Line Voltage in Volts
5 Ia=170 //armature Current in Ampere
6 Ra=0.0999 //Armature Resistance in ohm
7 K=0.33
8 a2=30
9 N1=1750 //Rotor Speed in rpm
10
11 //solution
12 Vm=(sqrt(2)/sqrt(3))*Vl
13 Va=(3*sqrt(3)/%pi)*Vm*cosd(a1)
14 Ia1=17
15 Eb1=Va-(Ia1*Ra)
16 N0=Eb1/K //no load Speed in rpm
17 Va2=Va*cosd(a2) //For alpha=30
18 Eb2=Va2-(Ia1*Ra)
19 N01=Eb2/K //No load speed at alpha=30
```

```

20 Eb3=K*N1//For Full load Condition
21 Va3=Eb3+(Ia*Ra)
22 a3=acosd(Va3/Va)
23 P=Va3*Ia
24 Irms=Ia*sqrt(((180-a3)/180))
25 Vph=Vl/sqrt(3)
26 pf=P/(3*Vph*Irms)//Power Factor
27 Eb4=Va3-(Ia1*Ra)
28 N4=Eb4/K
29 R=(N4-N1)*100/N1//Speed Regulation
30 printf ('\n\n No load speed at alpha 0=%0.1f rpm\n\n',
           NO)
31 printf ('\n\n No load speed at alpha 30=%0.1f rpm\n\n',
           N01)
32 printf ('\n\n The Firing Angle for rated speed=%0.1f \
n\n', a3)
33 printf ('\n\n Power Factor at rated speed=%0.1f\n\n',
           pf)
34 printf ('\n\n Speed Regulation=%0.1f\n\n', R)

```

Scilab code Exa 2.2 Ex2

```

1 clc
2 //variable initialisation
3 a1=0//Initial Firing Angle of Converter
4 Vl=460//Line to Line Voltage in Volts
5 Ia=150//armature Current in Ampere
6 Ra=0.0999//Armature Resistance in ohm
7 K=0.33
8 N1=1650//Rotor Speed in rpm
9 Ia1=15//armature Current for 2nd case in Ampere
10 //solution
11Vm=(sqrt(2)/sqrt(3))*Vl
12 Va=(3*sqrt(3)/%pi)*Vm*cosd(a1)
13 Eb1=Va-(Ia*Ra)

```

```

14 N0=Eb1/K//no load Speed in rpm
15 a2=45
16 Va2=Va*cosd(a2)
17 Eb2=Va2-(Ia*Ra)
18 N01=Eb2/K//No load speed at alpha=30
19 Eb3=K*N1
20 Va3=Eb3+(Ia*Ra)
21 a3=acosd(Va3/Va)
22 Irms=Ia*sqrt((180-a3)/180)
23 P1=3*(V1/sqrt(3))*Irms//Supply VA
24 P=Va3*Ia//Power input to motor
25 Pa=Va3*Ia
26 pf=Pa/P//Power Factor
27 Eb4=Va3-(Ia1*Ra)
28 N4=Eb4/K
29 R=(N4-N1)*100/N1//Speed Regulation
30 printf ('\n\n No load speed at alpha 0=%0.1f rpm\n\n',
           ,N0)
31 printf ('\n\n No load speed at alpha 45=%0.1f rpm\n\n',
           ,N01)
32 printf ('\n\n The Firing Angle for rated speed=%0.1f\
           \n\n',a3)
33 printf ('\n\n Supply Power at rated speed=%0.1f watts
           \n\n',P)
34 printf ('\n\n Power Factor at rated speed=%0.1f\n\n',
           pf)
35 printf ('\n\n Speed Regulation=%0.1f\n\n',R)
36 //The answers vary due to round off error

```

Scilab code Exa 2.3 Ex3

```

1 clc
2 //variable initialisation
3 Va=220 //supply voltage in volts
4 N1=1500 //speed in rpm

```

```

5 I=50 // current in ampere
6 Ra=0.5 //armature resistance in ohm
7 Vl=440 //line voltage in volts
8 f=50 //frequency in Hz
9 N2=1200 //speed in rpm
10
11 //solution
12 Vm=(Va*%pi)/(3*sqrt(3))
13 Vph=(Vl*(sqrt(2)))/(sqrt(3))
14 Xmer_ratio=Vph/Vm
15 Eb1=Va-(Ra*I)
16 Eb2=(N2/N1)*Eb1
17 Va=Eb2+Ra*I
18 a=acosd((Va*%pi)/(3*sqrt(3)*Vm))
19 N3=800
20 Eb3=(-N3/N1)*Eb1
21 Va1=Eb3+(2*I*Ra)
22 a1=acosd((Va1*%pi)/(3*sqrt(3)*Vm))
23 printf ('\n\n Transformer Turns Ratio=%0.1f\n\n', Xmer_ratio)
24 printf ('\n\n The Firing Angle=%0.1f\n\n', a)
25 printf ('\n\n The Firing Angle=%0.1f\n\n', a1)

```

Scilab code Exa 2.4 Ex4

```

1 clc
2 //variable initialisation
3 Va=220 //supply voltage in volts
4 N1=1500 //speed in rpm
5 Ra=2 //armature resistance in ohm
6 La=0.02836 //armature inductance in mH
7 f=50 //frequency in Hz
8
9 //solution
10 Vl=(Va*%pi)/(3*sqrt(2))

```

```
11 Vm=sqrt(2)*V1
12 printf ('\n\n The Source Voltage Required=%0.1f Volts
\n\n',Vm)
```

Scilab code Exa 2.5 Ex5

```
1 clc
2 //variable initialisation
3 V1=450 //terminal voltage in volts
4 Vd=30 //voltage drop in volts
5 V2=420 //input supply in volts
6 f=50 //frequency in Hz
7 a1=0 //Firing Angle of Converter
8 //solution
9 Vt=V1+Vd
10 V0_0=(3*sqrt(2))/(%pi)
11 V0_a=480
12
13 a2=acosd(V0_a/(V0_0*V2))
14 printf ('\n\n The Firing Angle=%0.1f\n\n',a2)
```

Scilab code Exa 2.6 Ex6

```
1 clc
2 //variable initialization
3 N=800 //speed in rpm
4 P=80000 //power in kw
5 V=440 //Supply voltage in volts
6 f=50 //Supply frequency in Hz
7 Ra=0.8 //armature resistance in ohm
8 k=0.2 //machine constant in V/rpm
9 Ia=160 //rated current in ampere
10
```

```

11 //solution
12 Vp=V/(sqrt(3))//Phase Voltage
13 Eb=k*N//Back emf in Volts
14 V2=Eb+(Ia*Ra)
15 a=acosd((V2*pi)/(3*sqrt(6)*Vp))
16 printf ('\n\n The Firing Angle=%0.1f\n\n',a)

```

Scilab code Exa 2.7 Ex7

```

1 clc
2 //variable initialisation
3 N=900 //speed in rpm
4 V=430 //Supply voltage in volts
5 Ia=20 //current in ampere
6 N1=900 //speed in rpm
7 N2=450 //speed in rpm
8 Ra=0.2 //armature resistance in ohm
9
10 //solution
11 V1=V/1.35
12 V2=((V-(Ia*Ra))/2)+Ia*Ra
13 a=acosd(V2/V)
14 printf ('\n\n The RMS Voltage per phase=%0.1f Volts\n
    \n',V2)
15 printf ('\n\n The Firing Angle=%0.1f\n\n',a)

```

Scilab code Exa 2.8 Ex8

```

1 clc
2 //Variable Initialisation
3 Vs=220//Supply Voltage in Volts
4 N=600//Rotor Speed in rpm
5 Ra=0.4//Armature Resistance in ohm

```

```

6 Rf=150 //Field Resistance in ohm
7 af=0 //Firing Angle for Maximum field current
8 aa=0 //Firing Angle for maximum Armature current
9 N2=1200 //Speed in rpm
10 T=120 //Torque in N-m
11 K=1.4 //Motor voltage Constant
12 //Solution
13 Vm=Vs/sqrt(3)
14 W=2*pi*N/60
15 Vf1=3*sqrt(3)*sqrt(2)*Vm*cosd(af)/pi
16 If1=Vf1/Rf //Field Current in Amp
17 Ia1=T/(K*If1)
18 Eb1=K*If1*W
19 Va1=Eb1+(Ia1*Ra)
20 aa1=acosd(Va1*pi/(3*sqrt(3)*sqrt(2)*Vm))
21 Va2=3*sqrt(3)*sqrt(2)*Vm*cosd(aa)/pi
22 Eb2=Va2-(Ia1*Ra)
23 N3=Eb2/(K*If1) //Speed in rad/s
24 N3rpm=N3*60/(2*pi) //Speed in Rpm
25 W2=N2*2*pi/60
26 If2=Eb2/(K*W2)
27 Vf2=If2*Rf
28 af1=acosd(Vf2*pi/(3*sqrt(3)*sqrt(2)*Vm))
29 printf('\n\n The Firing Angle=%0.1f\n\n',aa1)
30 printf('\n\n The Field Current=%0.1f Amp\n\n',N3rpm)
31 printf('\n\n The Field Current=%0.1f Amp\n\n',af1)

```

Scilab code Exa 2.9 Ex9

```

1 clc
2 //variable initialisation
3 V=440 //voltage in volts
4 P=100e+3 //power in Watts
5 N=900 //speed in rpm
6 V1=415 //supply voltage in volts

```

```
7
8 //solution
9 k=(3*sqrt(2))/pi
10 a=acosd(V/(k*V1))
11 V2=0.5*V//At 50% of rated speed
12 a1=acosd(V2/(k*V1))
13 printf ('\n\n The Firing Angle=%0.1f\n\n',a1)
```

Scilab code Exa 2.10 Ex10

```
1 clc
2 //variable initialization
3 P=80e+3 //power in Watt
4 Va1=440 //voltage in volts
5 N1=800 //speed in rpm
6 N2=600 //speed in rpm
7 Eb1=410 //Given back emf in volts
8 Vrms=415 //voltage in volts
9
10 //solution
11 Eb2=Eb1*(N2/N1)
12 Ia1=P/Va1
13 Ra=(Va1-Eb1)/Ia1
14 Ia2=0.75*Ia1//As motor is operating at 75% of rated
    torque
15 Va2=Eb2+(Ia2*Ra)
16 a=acosd(Va2*pi/(3*sqrt(2)*Vrms))
17 printf ('\n\n The Triggering Angle=%0.1f\n\n',a)
```

Scilab code Exa 2.11 Ex11

```
1 clc
2 //variable initialization
```

```

3 P=100e+3 //power in W
4 Va1=440 //Supply voltage in volts
5 N1=1000 //speed in rpm
6 N2=800 //speed in rpm
7 Eb1=410 //given Back EMF in volts
8 Vrms=415 //RMS voltage in volts
9 f=50 //Supply frequency in Hz
10
11 //solution
12 Eb2=Eb1*(N2/N1)
13 Ia1=P/Va1
14 Ra=(Va1-Eb1)/Ia1
15 Ia2=0.75*Ia1 //At 75% of rated torque
16 Va2=Eb2+(Ia2*Ra)
17 a=acosd((Va2*pi)/(3*sqrt(2)*Vrms))
18 printf('n\n The Firing Angle=%0.1f\n',a)

```

Scilab code Exa 2.12 Ex12

```

1 clc
2 //variable initialization
3 Php=100 //power in hp
4 P=Php*735.5 //power in Watts
5 Va1=440 //voltage in volts
6 N1=1000 //speed in rpm
7 N2=500 //speed in rpm
8 Eb1=430 //Given back EMF in volts
9 Vrms=415 //RMS voltage in volts
10
11 //solution
12 Eb2=Eb1*(N2/N1)
13 Ia1=P/Va1
14 Ra=10/Ia1
15 Ia2=0.85*Ia1
16 Va2=Eb2+Ia2*Ra //At 85% load and 500 rpm

```

```
17 a=acosd(Va2/(1.35*Vrms))
18 printf ('\n\n The Firing Angle=%0.1f\n\n',a)
```

Scilab code Exa 2.13 Ex13

```
1 clc
2 //variable initialisation
3 Va=230 //Supply voltage in volts
4 N1=1400 //speed in rpm
5 N2=600 //speed in rpm
6 N3=1400 //speed in rpm
7 Vdrop=15//Voltage drop in Volts
8 //solution
9 Eb1=Va-15
10 Eb2=Eb1*(N2/N1)
11 Va1=Eb2+Vdrop
12 a2=acosd(Va1/Va)
13 printf ('\n\n The Firing Angle=%0.1f\n\n',a2)
```

Chapter 3

Four Quadrant Operations of DC Drives

Scilab code Exa 3.1 Ex1

```
1 clc
2 //variable initialization
3 Vm= 220 //armature voltage in volts
4 N= 1000 //speed in rpm
5 N1= 900 // speed in rpm
6 Ia= 60 //armature current in ampere
7 Ra= 0.6 //armature resistance in ohm
8 a= 0
9 V= 165 //line voltage in volts
10
11 //solution
12 Eb1= Vm-Ia*Ra //back emf in volts
13 Eb2= (N1/N)*Eb1 //back emf in volts
14 Ea=Eb2+(Ia*Ra) //armature voltage in volts
15 Em= V*sqrt(2)
16 A=(((Ea*pi)/(3*Em)))
17 a1=acosd(A)
18 a2=180-a1
19 Ea1=V-(Ia*Ra) //armature voltage in volts
```

```

20 cosa1=((Ea/Em)*(%pi/3))
21 a11=acosd((Ea1*%pi)/(3*Em))
22 a22=180-a1
23 printf ('\n\n Firing Angle for motoring operations at
           rated motor torque and 900 or -900 rpm=%0.1f \n\n',
           a1)
24 printf ('\n\n Firing Angle for motoring operations at
           rated motor torque and 900 or -900 rpm=%0.1f \n\n',
           a2)
25 printf ('\n\n Firing Angle for braking operations at
           rated motor torque and 900 or -900 rpm=%0.1f \n\n',
           a11)
26 printf ('\n\n Firing Angle for braking operations at
           rated motor torque and 900 or -900 rpm=%0.1f \n\n',
           a22)
27 //The answers vary due to round off error

```

Scilab code Exa 3.2 Ex2

```

1 clc
2 // Variable Initialization
3 Vm=220 //armature voltage in volts
4 f=50 //frequency in Hz
5 Ra=10 //armature resistance in ohm
6 Lr=50e-3 //circulating inductance in mH
7 a1=30
8 a2=150
9
10 //solution
11 w=2*%pi*f
12 Em=sqrt(2)*220 //voltage in volts
13 cosa1=cosd(a1)
14 cosa2=cosd(a2)
15 Irmmax1=((2*Em)/(w*Lr))*(1-cosa1)
16 Irmmax2=((2*Em)/(w*Lr))*(1-cosa2)

```

```

17 Ip=(Em/Ra)
18 I1=Ip+Irmax1
19 I2=Ip+Irmax2
20 printf ('\n\n Peak Current of Converter 1=%0.1f Amp\n
           \n',I1)
21 printf ('\n\n Peak Current of Converter 2=%0.1f Amp\n
           \n',I2)

```

Scilab code Exa 3.3 Ex3

```

1
2 clc
3 // Variable initialization
4 F=50 //Supply Frequency In Hz
5 Vm=400 //Supply Voltage In Volts
6 Ip=20 //Peak Circulating Current In Ampere
7 A=60 //firing angle
8
9 // solution
10 Ea=Vm/(sqrt(3))
11 W=2*pi*F
12 Lr=[(3*sqrt(2)*Ea)/(W*Ip)]*(1-sind(A))
13 Lr1=Lr*1000//Inductance in mH
14 printf ('\n\n Inductance Value Needed=%0.1f mH\n\n',
           Lr1)
15 //The answer vary due to round off error

```

Scilab code Exa 3.4 Ex4

```

1 clc
2 // Variable Initiallization
3 F=50 //Supply Frequency In Hz
4 Erms=230 //RMS Voltage Per Phase In Volts

```

```
5 L=0.015 // Inductance In Henry
6 A1=60 // Firing Angle
7 A2=120 // Firing Angle
8
9
10
11
12 // solution
13 W=2*%pi*F
14 Icp=((3*sqrt(2)*Erms)/(W*L))*(1-sind(A1))
15 printf ('\n\n The Peak value of Circulating Current=
%0.1f Amp\n\n', Icp)
```

Scilab code Exa 3.5 Ex5

```
1 clc
2 // Variable Initiallization
3 Vm=400 // Supply Voltage In Volt
4 Ea1= 220// Voltage Of Motor In Volt
5 Ia=200 // Line Current In Ampere
6 Ra=0.05 // Armature Resistance In Ohm
7 N1=750 // Speed Of Motor In rpm
8 N2=600 // Speed Of Motor In rpm
9
10 // solution
11 Eb1=Ea1-(Ia*Ra)
12 Eb2=(N2/N1)*Eb1
13 Ea2=Eb2+(Ia*Ra)
14 A=acosd((Ea2*pi)/(Vm*3*sqrt(2)))
15 printf ('\n\n The Firing Angle of Rectifier=%0.1f\n\n
', A)
```

Scilab code Exa 3.6 Ex6

```

1 clc
2 // Variable Initiallization
3 Ea=400 // Voltage Of MOtor In Volt
4 Ia1=70 //Line Current In Ampere
5 Ia2=90 //Line Current In Ampere
6 Ra=0.3 //Armature Resistance In Ohm
7 N1=750 //Speed Of Motor In rpm
8 N2=300 //Speed Of Motor In rpm
9
10 //Solution
11 Eb1=Ea-(Ia1*Ra)
12 Eb2=(N2/N1)*Eb1
13 Rb=-((Eb2-Ea-Ia2*Ra)/Ia2)//Wrongly calculated in
   book , wrong value of Eb2 is taken
14 W1=(2*pi*N1)/60
15 Kt1=Eb1/W1
16 T1=Kt1*Ia1
17 W2=(2*pi*N2)/60
18 Kt2=Eb2/W2//Wrongly computed in textbook
19 T2=Kt2*Ia2//The answer provided in the textbook is
   wrong
20 printf('\n\n External resistance to be added=%0.1f
   ohm\n\n',Rb)
21 printf('\n\n Initial braking torque=%0.1f N-m\n\n',
   T1)
22 printf('\n\n braking torque at 300 rpm=%0.1f N-m\n\n',
   T2)
23 //The answer provided in the textbook is wrong(both)

```

Chapter 4

Chopper Controlled DC Drives

Scilab code Exa 4.1 Ex1

```
1 clc
2 //Variable Initialisation
3 V=230 //Input Voltage of motor in volts
4 Vdc=240 //Dc equivalent input to motor in Volts
5 Po=746 //Power rating of DC motor in Watt
6 N=500 //Rated Speed of Motor in rpm
7 Ia=4.1 //Armature Current in Ampere
8 Ra=7.56 //Armature resistance in ohm
9 La=55e-3 //Armature inductance in Henry
10 f=500 //Chopper Frequency
11 Tmin=5 //minimum load Torque in N-m
12 //Solution
13 T=(1/f) //Period of Chopper
14 w=2*pi*N*(1/60)
15 Eb=V-(Ia*Ra) //Back emf in Volts
16 k=Eb*(1/w)
17 Pin=V*Ia //Armature Power Input
18 L=Pin-Po-(Ia*Ia*Ra) //Rotational Loss
19 Ta=L/w
20 Ta1=Tmin+Ta //Average internal Torque in N-m
21 Ia1=Ta1/k
```

```

22 E0=Eb+(Ia1*Ra)
23 ton=(E0/Vdc)*T
24 ton11=ton*1000 //ton in microseconds
25 ta=(La/Ra)
26 A=log(((Eb/Vdc)*(%e^(T/ta)-1))+1)
27 ton1=A*ta
28 ton12=ton1*1000 //ton in microseconds
29 E01=(ton1/T)*Vdc
30 Ia2=(E01-Eb)/Ra
31 Ta2=k*Ia2
32 Tc=Ta2-Ta
33 printf ('\n\n ton for minimum load torque of 500rpm=%
            %0.1f 10^(-3)sec\n\n',ton11)
34 printf ('\n\n ton for current is continuous at 500rpm
            =%0.1f 10^(-3)sec\n\n',ton12)
35 if ton>ton1 then
            disp("Current (Ia) is continuous")
36 else
            disp("Current (Ia) is not continuous")
37 end
40 printf ('\n\n The coupling Torque for minimum value
            of ton obtain=%0.1f N-m\n\n',Tc)

```

Scilab code Exa 4.2 Ex2

```

1 clc
2 //Variable Initialisation
3 V=230 //Input Voltage of motor in volts
4 N=1750 //Rated Speed of Motor in rpm
5 Ia=74 //Armature Current in Ampere
6 Ra=0.180 //Armature resistance in ohm
7 Vdc=240 //Dc equivalent input to motor in Volts
8 f=500 //Chopper Frequency
9 W0=2*f*pi
10 la=2.93*10^(-3) //Armature inductance in Henry

```

```

11 // Solution
12 T=1/f // Period of Chopper
13 I0=Ia
14 W=2*pi*N/60
15 Eb=V-(Ia*Ra) // Back EMF in Volts
16 k=Eb/W
17 Ea=Vdc/2 // Average Voltage
18 Eb1=Ea-(Ia*Ra)
19 W1=Eb1/k
20 N1=W1*(60/(2*pi))
21 ton=T/2
22 Irms=((sqrt(2)*Vdc)/(%pi*W0*la))*sin(W0*ton/2)
23 Irms1=sqrt((I0^2)+(Irms^2))
24 k1=Irms/I0
25 I01=Ia/2 // Average Value of Source Current
26 Irms2=sqrt(2)*Ia/%pi
27 k2=Irms2/I01 // Source Current Ripple Factor
28 printf ('\n\n The Motor Speed=%0.1f rpm\n\n',N1)
29 printf ('\n\n The RMS Armature Current=%0.1f Amp\n\n',
           ,Irms1)
30 printf ('\n\n The RMS and line current ripple factor=
%0.1f\n\n',k2)

```

Scilab code Exa 4.3 Ex3

```

1 clc
2 //Variable Initialisation
3 Ia=50 //Armature Current in Ampere
4 Ea=440 //Input Voltage to armature in volts
5 N=1000 //Rated Speed of Motor in rpm
6 Ra=0.5 //Armature resistance in ohm
7 Ra1=10.5 //Armature resistance in ohm
8 Rf=100 //Field resistance in ohm
9 N1=400 //Speed of Motor in rpm
10 N2=800 //Speed of Motor in rpm

```

```

11 ton=2*10^(-3)
12 //Solution
13 If=Ea/Rf
14 Eb=Ea-(Ia*Ra)
15 Eb1=(N1/N)*Eb
16 E01=Eb1+(Ia*Ra1)
17 t1=(Ea/E01)*2*10^3
18 f1=1/t1
19 Eb2=(N2/N)*Eb
20 E02=Eb2+(Ia*Ra)
21 t2=(Ea/E02)*ton
22 f2=1/t2
23 printf ('\n\n The Chopping Frequency 1=%0.1f\n\n',f1)
24 printf ('\n\n The Chopping Frequency 2=%0.1f\n\n',f2)
25 //The answers vary due to round off error

```

Scilab code Exa 4.4 Ex4

```

1 clc
2 //Variable Initialisation
3 V=230 //Input Voltage of motor in volts
4 Ra=1.5 //Armature resistance in ohm
5 La=1e-3 //Armature inductance in ohm
6 Ia=15 //Armature Current in Ampere
7 k=0.05 //Voltage constant
8 //Solution
9 Eb=0 //when d=0
10 Ea=Eb+(Ia*Ra)
11 d=Ea/V
12 Eb1=V-(Ia*Ra)
13 //when d1=1
14 N=Eb1/k
15 printf ('\n\n Range of speed control is from 0 to %0
.1f\n\n',N)
16 printf ('\n\n The Duty Cycle is from%0.1f to 1\n\n',d

```

```
    )
17 //The answers vary due to round off error
```

Scilab code Exa 4.5 Ex5

```
1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage to armature in volts
4 N1=1000 //Rated Speed of Motor in rpm
5 N2=500 //Speed of Motor in rpm
6 Ia=24 //Armature Current in Ampere
7 Ra=2 //Armature resistance in ohm
8 Es=230 //Source voltage in Volts
9 //Solution
10 Eb1=Ea-(Ia*Ra)
11 Eb2=(N2/N1)*Eb1
12 E0=Eb2+(1.2*Ia*Ra)
13 d=E0/Es
14 printf ('\n\n The Duty Ratio=%0.1f\n\n',d)
15 //The answers vary due to round off error
```

Scilab code Exa 4.6 Ex6

```
1 clc
2 //Variable Initialisation
3 Ea=500 //Input Voltage to armature in volts
4 Ra=0.09 //Armature resistance in ohm
5 If=3 //Field Current in Ampere
6 K=1.527 //Voltage constant
7 T=560 //Torque Developed in N-m
8 N1=0 //Speed of Motor in rpm
9 d2=1 //duty ratio
10 //Solution
```

```

11 Ia=T/(K*If)
12 Eb=K*N1
13 d1=(Eb+(Ia*Ra))/Ea
14 N2=((d2*Ea)-(Ia*Ra))/(K*If)
15 N2r=N2*60/(2*pi)
16 d3=[0.2,0.4,0.6,0.8,1.0]
17 N3r=[556.56,1181.92,1807.28,2432.6,3058.0]
18 plot(d3,N3r)
19 xlabel ('Duty Interval')
20 ylabel ('Speed in RPM')

```

Scilab code Exa 4.7 Ex7

```

1 clc
2 //Variable Initialisation
3 Ra=0.08 //Armature resistance in ohm
4 Ea=450 //Input Voltage to armature in volts
5 Ia=275 //Armature Current in Ampere
6 If=3 //Field Current in Ampere
7 K=1.527 //Voltage constant
8 d=0.65 //Duty ratio
9 //Solution
10 Pin=d*Ea*Ia
11 E0=d*Ea
12 Eb=E0-(Ia*Ra)
13 W=Eb/(K*If)
14 N=W*60/(2*pi)
15 T=K*If*Ia
16 printf ('\n\n The Input power from Generator Source=%0.1f Watt\n\n',Pin)
17 printf ('\n\n The Speed of Motor=%0.1f rpm\n\n',N)
18 printf ('\n\n The Torque developed=%0.1f N-m\n\n',T)

```

Scilab code Exa 4.8 Ex8

```
1 clc
2 //Variable Initialisation
3 ton=15
4 toff=10
5 Ea=220 //Input Voltage to armature in volts
6 Km=0.4 //Voltage constant
7 N=1400 //Rated Speed of Motor in rpm
8 Ra=2 //Armature resistance in ohm
9 //Solution
10 d=ton/(ton+toff)
11 E0=d*Ea
12 W=2*pi*N/60
13 Ia=(E0-(Km*W))/Ra
14 printf ('\n\n The Average load Current=%0.1f Amp\n\n',
           Ia)
```

Scilab code Exa 4.9 Ex9

```
1 clc
2 //Variable Initialisation
3 Ea=200 //Input Voltage to armature in volts
4 Ia=20 //Armature Current in Ampere
5 Ra=0.4 //Armature resistance in ohm
6 k=0.1
7 N1=0 //Speed of Motor in rpm
8 //Solution
9 Eb1=k*N1
10 d1=(Eb1+(Ia*Ra))/Ea
11 d2=1
12 Eb2=d2*Ea-(Ia*Ra)
13 N2=Eb2/k
14 printf ('\n\n Range of speed control from 0 to %0.1f \
           \n\n', N2)
```

```

15 printf ('\n\n Range of duty cycle from %0.1f to 1\n\n
', d1)
16 //The answers vary due to round off error

```

Scilab code Exa 4.10 Ex10

```

1 clc
2 //Variable Initialisation
3 V=230 //Input Voltage of motor in volts
4 f=300 //Chopper Frequency
5 Tl=40 //Load Torque in N-m
6 N1=900 //Rated Speed of Motor in rpm
7 Ra=0 //Armature resistance in ohm
8 La=12e-3 //Inductance in Henry
9 k=2 //Motor Constant
10 //Solution
11 Ia=Tl/k
12 W=2*pi*N1/60
13 Eb=k*W
14 d=(Eb+(Ia*Ra))/V
15 t1=1/f
16 ton=d*t1
17 toff=(1-d)*t1
18 Z1=(V-Eb)/La
19 Z2=-Eb/La
20 A=Z1*ton //A=Imax-Imin
21 B=2*Ia //B=Imax+Imin
22 Imax=(A+B)/2
23 Imin=(B-A)/2
24
25 t=poly(0, 't');
26 x=Imin+Z1*t
27 y=Imax+Z2*t
28
29 disp (Imax , "Maximum Armature Current in Amp is")

```

```

30 disp (Imin ,”Minimum Armature Current in Amp is”)
31 disp (A ,”Armature Current Excursion in Amp is”)
32 disp (x ,”Armature Current During Ton in Amp is”)
33 disp (y ,”Armature Current During Toff in Amp is”)

```

Scilab code Exa 4.11 Ex11

```

1 clc
2 //Variable Initialisation
3 Ea=200//Input Voltage of motor in volts
4 Ra=0.12//Armature resistance in ohm
5 La=12e-3//Armature Inductance in ohm
6 K=2//Motor constant in V-s/rad
7 Eb=150//Motor back EMF
8 Ia=30//Armature Current in Ampere
9 f=300//Chopper Frequency
10 //Solution
11 T=1/f
12 d=(Eb+(Ia*Ra))/Ea
13 ton=d*T
14 toff=(1-d)*T
15 t=Ra/La
16 Ea1=Ea
17 Imin=poly(0 ,’Imin ’);
18 Ia1=((Ea1-Eb)/Ra)*(1-%e^(-ton*t))+(Imin*%e^(-ton*t))
19 disp (Ia1 ,”Imax is”)
20 Ea2=0
21 Imax=poly(0 ,’Imax ’);
22 Ia2=((Ea2-Eb)/Ra)*(1-%e^(-toff*t))+(Imax*%e^(-toff*t))
23 disp (Ia2 ,”Imin is”)
24 a=poly(0 ,’a ’);
25 b=poly(0 ,’b ’);
26 Imax1=(10.409+(0.975*(-9.96)))/(1-(0.975*0.992))//
   From above displayed values and rounding off

```

```

27 Imin1=(-9.960)+(0.992*Imax1)
28 Im=Imax1-Imin1//Armature Current Excursion
29 printf ('\n\n Maximum Armature Current=%0.1f Amp\n\n',
           ,Imax1)
30 printf ('\n\n Minimum Armature Current=%0.1f Amp\n\n',
           ,Imin1)
31 printf ('\n\n Armature Current Excursion=%0.1f Amp\n\n',
           ,Im)

```

Scilab code Exa 4.12 Ex12

```

1 clc
2 //Variable Initialisation
3 V=440//Input Voltage of motor in volts
4 Rf=100//Field resistance in ohm
5 Il=50//Load Current in Ampere
6 N1=900//Rated Speed of Motor in rpm
7 N2=300//Rated Speed of Motor in rpm
8 N3=400//Rated Speed of Motor in rpm
9 N4=600//Rated Speed of Motor in rpm
10 Ra=0.3//Armature resistance in ohm
11 ton=4e-3//On period of Chopper in sec
12 //Solution
13 If=V/Rf//Motor Field Current in Amp
14 Ia=Il-If//Armature Current in Amp
15 Eb1=V-(Ia*Ra)//Back EMF of Motor
16 Eb2=(N2/N3)*Eb1
17 V2=Eb2+(Ia*Ra)//Required Terminal Voltage in volts
18 T1=(V/V2)*ton//Chopping Period
19 f1=1/T1//Chopping Period
20 Eb3=(N4/N1)*Eb1//Back Emf at 600 rpm
21 V3=Eb3+(Ia*Ra)//Required Terminal Voltage in volts
22 T2=(V/V3)*ton//Chopping Period
23 f2=1/T2//Chopping Period
24 printf ('\n\n Frequency of chopper=%0.1f Hz\n\n',f2)

```

Scilab code Exa 4.13 Ex13

```
1 clc
2 //Variable Initialisation
3 ton=10 //On time of Chopper
4 toff=12 //Off time of Chopper
5 Ea=220 //Input Voltage of motor in volts
6 k=0.495 //Motor Voltage constant
7 W=146.60 //Rated Speed of Motor in rad/sec
8 Ra=2.87 //Armature resistance in ohm
9 //Solution
10 d=ton/(ton+toff) //Duty cycle ratio
11 Ia=((d*Ea)-(k*W))/Ra
12 printf ('\n\n Average load Current=%0.1f Amp\n\n',Ia)
13 //The answers vary due to round off error
```

Scilab code Exa 4.14 Ex14

```
1 clc
2 //Variable Initialisation
3 Ea=450 //Input Voltage of motor in volts
4 Ra=0.06 //Armature resistance in ohm
5 Kt=1.4 //Motor Voltage Constant
6 Ia=300 //Armature Current in Ampere
7 If=3.3 //Motor Field Current in Amp
8 d=0.7 //Duty cycle of Converter
9 //Solution
10 Pin1=Kt*Ea*Ia //Input Power
11 Re1=Ea/(Kt*Ia) //Equivalent Resistance
12 E01=Kt*Ea
13 Eb1=E01-(Ia*Ra)
```

```

14
15 Pin2=d*Ea*Ia
16 Re2=Ea/(d*Ia)
17 E02=d*Ea
18 Eb2=E02-(Ia*Ra)
19 N1=Eb2/(Kt*If)
20 N=N1*60/(2*pi)
21 T=Kt*Ia*If
22 printf ('\n\n Input Power=%0.1f KW\n\n',Pin1*10^-3)
23 printf ('\n\n Equivalent Resistance developed=%0.1f
ohm\n\n',Re1)
24 printf ('\n\n Motor Speed=%0.1f rpm\n\n',N)
25 printf ('\n\n Motor Torque=%0.1f N-m\n\n',T)

```

Scilab code Exa 4.15 Ex15

```

1 clc
2 //Variable Initialisation
3 Ea=210 //Input Voltage of motor in volts
4 Ia=25 //Armature Current in Ampere
5 Es=230
6 N1=1500 //Rated Speed of Motor in rpm
7 Ra=3 //Armature resistance in ohm
8 N2=800 //Rated Speed of Motor in rpm
9 //Solution
10 Ia2=1.5*Ia
11 Eb=Ea-(Ia*Ra)
12 Eb2=(N2/N1)*Eb
13 E0=Eb2+(Ia2*Ra)
14 d=E0/Es
15 printf ('\n\n Duty Ratio=%0.1f\n\n',d)

```

Scilab code Exa 4.16 Ex16

```

1 clc
2 //Variable Initialisation
3 Ea=200 //Input Voltage of motor in volts
4 Ia=20 //Armature Current in Ampere
5 Ra=0.33 //Armature resistance in ohm
6 La=11e-3 //Armature Inductance in ohm
7 N1=1200 //Rated Speed of Motor in rpm
8 N2=800 //Rated Speed of Motor in rpm
9 f=500 //Chopper Frequency in Hz
10 //Solution
11 T=1/f
12 t=Ra/La
13 t1=1/t
14 Eb1=Ea-(Ia*Ra)
15 Eb2=(N2/N1)*Eb1
16 E0=Eb2+(Ia*Ra)
17 d=E0/Ea
18 ton1=d*T
19 A=log(1+((Eb2/Ea)*(%e^(T/t1))-1))) //Ia2=0 & A=ton2/
    t
20 ton2=A*t1
21 printf ('\n\n Duty Cycle=%0.1f\n\n',ton2)
22 //The answer provided in the textbook is wrong(
    answer given in textbook is in invalid range)
23 if ton2<ton1 then disp('Current is Continuous')
24 end

```

Scilab code Exa 4.17 Ex17

```

1
2 clc
3 //Variable Initialisation
4 Ea=220 //Input Voltage of motor in volts
5 Ia=100 //Armature Current in Ampere
6 Ra=0.01 //Armature resistance in ohm

```

```

7 N1=1000 //Rated Speed of Motor in rpm
8 N2=500 //Rated Speed of Motor in rpm
9 //Solution
10 Eb1=Ea-(Ia*Ra)
11 Eb2=(N2/N1)*Eb1
12 Ea2=Eb2+(Ia*Ra)
13 d1=Ea2/Ea
14 Ea3=Eb2-(Ia*Ra)
15 d2=Ea3/Ea
16 printf ('\n\n Duty Ratio of Chopper in motoring
           operation=%0.1f\n\n',d1)
17 printf ('\n\n Duty Ratio of Chopper in breaking
           operation=%0.1f\n\n',d2)
18 //The answers vary due to round off error

```

Scilab code Exa 4.18 Ex18

```

1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 Ia=50 //Armature Current in Ampere
5 N1=800 //Rated Speed of Motor in rpm
6 Ra=0.4 //Armature resistance in ohm
7 d1=0.3 //Duty ratio for Motoring Operation
8 d2=0.6 //Duty ratio for Motoring Operation
9 d3=0.7 //Duty ratio for Braking Operation
10 d4=0.4 //Duty ratio for Braking Operation
11 //Solution
12 E01=d1*Ea
13 Eb1=Ea-(Ia*Ra)
14 Eb2=E01-(Ia*Ra)
15 N2=(Eb2/Eb1)*N1
16 E02=d2*Ea
17 Eb3=E02-(Ia*Ra)
18 N3=(Eb3/Eb1)*N1

```

```

19 E03=d3*Ea
20 Eb4=E03+(Ia*Ra)
21 N4=(Eb4/Eb1)*N1
22 E04=d4*Ea
23 Eb5=E04+(Ia*Ra)
24 N5=(Eb5/Eb1)*N1
25 printf ('\n\n Motor speed for Motoring Operation 1 =
    %0.1f rpm\n\n',N2)
26 printf ('\n\n Motor speed for Motoring Operation 2=%0
    .1f rpm\n\n',N3)
27 printf ('\n\n Motor speed for Braking Operation 1=%0
    .1f rpm\n\n',N4)
28 printf ('\n\n Motor speed for Braking Operation 2=%0
    .1f rpm\n\n',N5)

```

Scilab code Exa 4.19 Ex19

```

1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 d=0.95 //Maximum Duty Ratio
5 Ia1=100 //Armature Current in Ampere
6 Ia2=150 //Armature Current in Ampere
7 Ra=0.01 //Armature resistance in ohm
8 N1=1000 //Rated Speed of Motor in rpm
9 //Solution
10 Eb1=Ea-(Ia1*Ra)
11 E0=d*Ea
12 Eb2=E0+(Ia2*Ra)
13 N2=(Eb2/Eb1)*N1
14 Pin=E0*Ia2
15 printf ('\n\n Maximum Permissible MOtor Speed=%0.1f
    rpm\n\n',N2)
16 //The answers vary due to round off error

```

Scilab code Exa 4.20 Ex20

```
1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 Ia=30 //Armature Current in Ampere
5 Ia2=60 //Armature Current in Ampere
6 N1=1000 //Rated Speed of Motor in rpm
7 N2=800 //Rated Speed of Motor in rpm
8 Ra=0.7 //Armature resistance in ohm
9 d2=0.6 //Duty Ratio
10 d3=0.9 //Duty Ratio
11 d4=0.9 //Duty Ratio
12 //Solution
13 Eb1=Ea-(Ia*Ra)
14 Eb2=(N2/N1)*Eb1
15 E01=Eb2-(Ia*Ra)
16 d1=E01/Ea
17 E02=d2*Ea
18 Eb3=E02+(Ia*Ra)
19 N3=(Eb3/Eb1)*N1
20 E03=d3*Ea
21 Eb4=E03+(Ia2*Ra)
22 N4=(Eb4/Eb1)*N1
23 E04=d4*Ea
24 Pin=E04*Ia2
25 printf ('\n\n Duty Ratio Of Chopper=%0.1f\n\n',d1)
26 printf ('\n\n Motor Speed for duty ratio 0.6=%0.1f
    rpm\n\n',N3)
27 printf ('\n\n Maximum Allowable Speed=%0.1f rpm\n\n',
    N4)
28 printf ('\n\n Power Fed to Source=%0.1f KW\n\n',Pin
    *10^-3)
29 //The answers vary due to round off error
```

Scilab code Exa 4.21 Ex21

```
1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 Ia=150 //Armature Current in Ampere
5 Ra=0.06 //Armature resistance in ohm
6 N1=1000 //Rated Speed of Motor in rpm
7 N2=500 //Rated Speed of Motor in rpm
8 N4=1350 //Rated Speed of Motor in rpm
9 d3=0.91 //Duty Ratio
10 Ia2=2*Ia
11 //Solution
12 Eb1=Ea-(Ia*Ra)
13 Eb2=(N2/N1)*Eb1
14 E01=Eb2+(Ia*Ra)
15 d1=E01/Ea
16 E02=Eb2-(Ia*Ra)
17 d2=E02/Ea
18 E03=d3*Ea
19 Eb3=E03+(Ia2*Ra)
20 N3=(Eb3/Eb1)*N1
21 Pin=E03*Ia2
22 R=N1/N4 //Ratio of If1 and If2
23 printf ('\n\n Duty ratio for motoring operation=%0.1f\n',d1)
24 printf ('\n\n Duty ratio for braking operation=%0.1f\n',d2)
25 printf ('\n\n Maximum permissible motor Speed=%0.1f rpm\n',N3)
26 printf ('\n\n Ratio of If1 and If2=%0.1f\n',R)
```

Scilab code Exa 4.22 Ex22

```
1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 Ia=100 //Armature Current in Ampere
5 Ia2=1.5*Ia
6 Ra=0.01 //Armature resistance in ohm
7 Rb=2
8 N1=1000 //Rated Speed of Motor in rpm
9 N2=500 //Rated Speed of Motor in rpm
10 d2=0.5
11 //Solution
12 Eb1=Ea-(Ia*Ra)
13 Eb2=(N2/N1)*Eb1
14 d=(1-(((Eb2/Ia2)-Ra)/Rb)) //Wrongly solved in
    textbook
15 Eb3=Ia2*((1-d2)*Rb)+Ra
16 N3=(Eb3/Eb1)*N1
17 printf ('\n\n Duty Ratio of chopper=%0.1f\n\n',d) //
    The answer provided in the textbook is wrong
18 printf ('\n\n Motor Speed=%0.1f rpm\n\n',N3)
```

Scilab code Exa 4.23 Ex23

```
1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 Ia=150 //Armature Current in Ampere
5 Ia2=300 //torque is doubled
6 Ra=0.06 //Armature resistance in ohm
7 Rb=2.2
8 N1=1000 //Rated Speed of Motor in rpm
9 N2=700 //Rated Speed of Motor in rpm
10 d2=0.55
```

```
11 // Solution
12 Eb1=Ea-(Ia*Ra)
13 Eb2=(N2/N1)*Eb1
14 d=(1-(((Eb2/Ia2)-Ra)/Rb))
15 Eb3=Ia2*((1-d2)*Rb)+Ra)
16 N3=(Eb3/Eb1)*N1
17 printf ('\n\n Duty Ratio Of Chopper=%0.1f\n\n',d)
18 printf ('\n\n Motor Speed=%0.1f rpm\n\n',N3)
```

Scilab code Exa 4.24 Ex24

```
1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 N1=1200 //Rated Speed of Motor in rpm
5 N2=1000 //Rated Speed of Motor in rpm
6 Ia=15 //Armature Current in Ampere
7 Ia2=1.5*Ia
8 Ra=1.2 //Armature resistance in ohm
9 Rb=20
10 d2=0.5
11 //Solution
12 Eb1=Ea-(Ia*Ra)
13 Eb2=(N2/N1)*Eb1
14 d1=(1-((Eb2/Ia2)-Ra)/Rb))
15 Eb3=Ia*((1-d2)*Rb)+Ra)
16 N3=(Eb3/Eb1)*N1
17 printf ('\n\n Duty Ratio Of Chopper=%0.1f\n\n',d1)
18 printf ('\n\n Motor Speed=%0.1f rpm\n\n',N3)
```

Scilab code Exa 4.25 Ex25

```
1 clc
```

```

2 //Variable Initialisation
3 Ia=180 //Armature Current in Ampere
4 Ra=0.06 //Armature resistance in ohm
5 Rb=8
6 If=2 //Field Current in Ampere
7 d=0.5
8 K=1.527
9 //Solution
10 E0=Ia*Rb*(1-d)
11 Req=Rb*(1-d)+Ra
12 Pb=(Ia^2)*(Rb*(1-d))
13 Eb=E0+(Ia*Ra)
14 W=Eb/(K*If)
15 W1=(W*60)/(2*pi)
16 Ep=Ia*Rb
17 printf ('\n\n The Average Voltage across chopper=%0.1
f Volts\n\n',E0)
18 printf ('\n\n Equivalent Resistance of motor=%0.1 f
ohm\n\n',Req)
19 printf ('\n\n Power dissipated in braking resistor=%0
.1 f KW\n\n',Pb*10^-3)
20 printf ('\n\n The Motor Speed=%0.1 f rpm\n\n',W1)
21 printf ('\n\n Peak to Peak Voltage=%0.1 f Volts\n\n',
Ep)

```

Scilab code Exa 4.26 Ex26

```

1 clc
2 //Variable Initialisation
3 Ea=440 //Input Voltage of motor in volts
4 d=0.5 //Duty Ratio
5 Ia=200 //Armature Current in Ampere
6 Ra=0.15 //Armature resistance in ohm
7 K=1 //Motor Constant
8 //Solution

```

```

9 E0=(1-d)*Ea
10 Pr=E0*Ia
11 Wmin1=(Ia*Ra)/K
12 Wmin=Wmin1*60/(2*pi)
13 Wmax1=(Ea+(Ia*Ra))/K
14 Wmax=Wmax1*60/(2*pi)
15 Eb=E0+(Ia*Ra)
16 Wm1=Eb/K
17 Wm=Wm1*60/(2*pi)
18 printf ('\n\n The Power Returned=%0.1f KW\n\n',Pr
           *10^-3)
19 printf ('\n\n Minimum braking Speed=%0.1f rpm\n\n',
           Wmin)
20 printf ('\n\n Maximum braking Speed=%0.1f rpm\n\n',
           Wmax)//The answers vary due to round off error
21 printf ('\n\n Speed during Regenerative Braking=%0.1f
           rpm\n\n',Wm)

```

Scilab code Exa 4.27 Ex27

```

1 clc
2 //Variable Initialisation
3 Ia1=190 //Armature Current in Ampere
4 Ia2=0.9*Ia1
5 Ra=0.08 //Armature resistance in ohm
6 Ri=0.05
7 Ea=210 //Input Voltage of motor in volts
8 N1=950 //Rated Speed of Motor in rpm
9 N2=750 //Rated Speed of Motor in rpm
10 //Solution
11 Eb1=Ea-(Ia1*Ra)
12 Eb2=(N2/N1)*Eb1
13 Vi=Eb2-(Ia2*(Ra+Ri))
14 printf ('\n\n Internal Voltage of Source=%0.1f Volts\
           \n\n',Vi)

```

Scilab code Exa 4.28 Ex28

```
1 clc
2 //Variable Initialisation
3 Ea=210 //Input Voltage of motor in volts
4 Ia1=140 //Armature Current in Ampere
5 Ia2=2*Ia1
6 Ra=0.08 //Armature resistance in ohm
7 N1=1100 //Rated Speed of Motor in rpm
8 N2=1200 //Rated Speed of Motor in rpm
9 //Solution
10 Eb1=Ea-(Ia1*Ra)
11 Eb2=(N2/N1)*Eb1
12 Rb=((Eb2+Ea)/Ia2)-Ra
13 W=(2*pi*N2)/60
14 T1=(Eb2*Ia2)/W
15 Ia3=Ea/(Ra+Rb)
16 T2=T1*(Ia3/Ia2)
17 printf ('\n\n Resistance to be placed=%0.1f ohm\n\n', Rb)
18 printf ('\n\n Braking torque=%0.1f N-m\n\n', T1)
19 printf ('\n\n torque=%0.1f N-m\n\n', T2) //The answers
      vary due to round off error
```

Scilab code Exa 4.29 Ex29

```
1 clc
2 //Variable Initialisation
3 Ra=0.08 //Armature resistance in ohm
4 Rb=1.5
5 Rf=12
```

```

6 N=500 //Rated Speed of Motor in rpm
7 //Solution
8 If0=poly(0 , 'If0 ')
9 Eb0=poly(0 , 'Eb0 ')
10
11 If=[4.16 , 6.2 , 8.33 , 10.5 , 12.5 , 14.6 , 16.6 , 18.8 , 20]
12 Eb=[41.6 , 61.2 , 75 , 85 , 92 , 96.6 , 101 , 105 , 125]
13 W=2*pi*N/60
14 Ia=((Rb+Rf)/Rb)*If0
15 K=Eb0*(1/W)
16 If1=12.6
17 Eb1=102.2
18 for If0=If1
19     disp(Ia)
20 end
21 for Eb0=Eb1
22     disp(K)
23 end
24 If2=12.6
25 K2=1.75
26 Eb2=102.2
27 K1=Eb2*(1/W)
28 Ia2=9*If2
29 Eb3=(If2*Rf)+(Ia2*Ra) //Wrongly calculated in book
30 N2=Eb3*60/(K1*2*pi)
31 printf ('\n\n Motor Speed at which load is hold by
           motor=%0.1f rpm\n\n' ,N2) //The answer provided in
           the textbook is wrong

```

Scilab code Exa 4.30 Ex30

```

1 clc
2 //Variable Initialisation
3 Ra=0.08 //Armature resistance in ohm
4 T=300 //Torque in N-m

```

```

5 N=1000 //Rated Speed of Motor in rpm
6 Rf=12 //Field Winding Resistor in ohm
7 //Solution
8 Eb=poly(0, 'Eb')
9 W=2*pi*N/60
10 Pd=T*W
11 Ea=Eb-((Pd*Ra)/Eb)
12 If=20 //From previous Example
13 Ea1=Rf*If
14 Eb1=250 //From previous Example
15 Ia=(Eb1-Ea1)/Ra
16 If1=Ea1/Rf
17 Ir=Ia-If
18 Rb=Ea1/Ir
19 printf ('\n\n Braking Resistance=%0.1f ohm\n\n',Rb)

```

Scilab code Exa 4.31 Ex31

```

1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 Ia=200 //Armature Current in Ampere
5 Ra=0.02 //Armature resistance in ohm
6 N1=960 //Rated Speed of Motor in rpm
7 N2=350 //Rated Speed of Motor in rpm
8 N4=1200 //Rated Speed of Motor in rpm
9 d3=0.95
10 //Solution
11 Ia2=2*Ia
12 Eb1=Ea-(Ia*Ra)
13 Eb2=(N2/N1)*Eb1
14 E01=Eb2+(Ia*Ra)
15 d1=E01/Ea
16 Ea2=Eb2-(Ia*Ra)
17 d2=Ea2/Ea

```

```

18 Eam=d3*Ea
19 P=Eam*Ia2
20 Eb3=Eam+(Ia2*Ra)
21 N3=(Eb3/Eb1)*N1
22 Ifr=(N1/N4)
23 printf ('\n\n Duty ratio for motoring operation=%0.1f
           \n\n',d1)
24 printf ('\n\n Duty ratio for braking operation=%0.1f\
           \n\n',d2)
25 printf ('\n\n Maximum permissible motor Speed=%0.1f
           rpm\n\n',N3)
26 printf ('\n\n Field Current as Ratio of its rated
           value=%0.1f\n\n',Ifr)

```

Scilab code Exa 4.32 Ex32

```

1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 Ia=10 //Armature Current in Ampere
5 Ia2=2*Ia //Given condition for armature Current
6 Ia3=2*Ia //Given condition for armature Current
7 Ra=1.5 //Armature resistance in ohm
8 Rb=15 //Braking Resistance in ohm
9 N1=1500 //Rated Speed of Motor in rpm
10 N2=1200 //Rated Speed of Motor in rpm
11 //Solution
12 Eb1=Ea-(Ia*Ra)
13 Eb2=(N2/N1)*Eb1
14 d1=1-(((Eb2/Ia2)-Ra)/Rb)
15 d2=0.6 //Duty ratio
16 Eb3=Ia3*((1-d2)*Rb)+Ra
17 N3=(Eb3/Eb1)*N1
18 printf ('\n\n Duty ratio =%0.1f\n\n',d1)
19 printf ('\n\n motor Speed=%0.1f rpm\n\n',N3)

```

Scilab code Exa 4.33 Ex33

```
1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 Ia=50 //Armature Current in Ampere
5 Ra=0.4 //Armature resistance in ohm
6 N1=800 //Rated Speed of Motor in rpm
7 //Solution
8 T=poly(0, 'T')
9 W=2*pi*N1/60
10 Eb=Ea-(Ia*Ra)
11 K=Eb/W
12 d1=0.3
13 W1=((d1*Ea)/K)-(Ra/(K^2))*T
14 d2=0.6
15 W2=((d2*Ea)/K)-(Ra/(K^2))*T
16 d3=0.7
17 W3=((d3*Ea)/K)+(Ra/(K^2))*T
18 d4=0.4
19 W4=((d4*Ea)/K)+(Ra/(K^2))*T
20 disp(W1, 'Speed in terms of torque for motoring
    operation for duty ratio 0.3')
21 disp(W2, 'Speed in terms of torque for motoring
    operation for duty ratio 0.6')
22 disp(W3, 'Speed in terms of torque for Braking
    operation for duty ratio 0.7')
23 disp(W4, 'Speed in terms of torque for Braking
    operation for duty ratio 0.4')
```

Scilab code Exa 4.34 Ex34

```

1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 Ia=15 //Armature Current in Ampere
5 Ra=1.2 //Armature resistance in ohm
6 Rb=20 //Braking Resistance in ohm
7 Ia2=15*Ia
8 N1=1200 //Motor Speed in rpm
9 //Solution
10 Eb=Ea-(Ia*Ra)
11 Eb1=Ea-(Ia2*Ra)
12 d1=1-(((Eb1/Ia2)-Ra)/Rb)
13 d2=0.5 //Duty ratio
14 Eb2=Ia*((1-d2)*Rb)+Ra
15 N2=(Eb2/Eb)*N1
16 printf ('\n\n Duty ratio Of Chopper=%0.1f\n\n',d1)
17 printf ('\n\n Motor Speed=%0.1frpm\n\n',N2)

```

Scilab code Exa 4.35 Ex35

```

1 clc
2 //Variable Initialisation
3 Ea=400 //Input Voltage of motor in volts
4 Ia=200 //Armature Current in Ampere
5 d=0.5 //Duty Ratio
6 Ra=0.03 //Armature resistance in ohm
7 Rs=0.05
8 K=3e-3 //Motor Constant
9 //Solution
10 E0=d*Ea
11 Pin=E0*Ia //Input power in watt
12 R=Ra+Rs
13 Eb=E0-(Ia*R)
14 Wm=Eb/(K*Ia)
15 Wmrpm=Wm*30/%pi

```

```

16 T=K*(Ia^2)
17 printf ('\n\n Input Power From Source=%0.1f KW\n\n' ,
18 Pin*10^-3)
18 printf ('\n\n Motor Speed=%0.1f rpm\n\n' ,Wmrpm)
19 printf ('\n\n Motor Torque=%0.1f N-m\n\n' ,T)

```

Scilab code Exa 4.36 Ex36

```

1 clc
2 //Variable Initialisation
3 Ea=400 //Input Voltage of motor in volts
4 Ia=200 //Armature Current in Ampere
5 Ra=0.05 //Armature resistance in ohm
6 Rs=0.07
7 d=0.5 //Duty Ratio
8 K=5e-3 //Motor Constant
9 //Solution
10 E0=d*Ea
11 Pin=E0*Ia
12 Wm=((E0-Ia*(Ra+Rs))/(K*Ia))*(30/%pi)
13 T=K*(Ia^2)
14 printf ('\n\n Input Power From Source=%0.1f KW\n\n' ,
15 Pin*10^-3)
15 printf ('\n\n Motor Speed=%0.1f rpm\n\n' ,Wm)
16 printf ('\n\n Motor Torque=%0.1f N-m\n\n' ,T)

```

Scilab code Exa 4.37 Ex37

```

1 clc
2 //Variable Initialisation
3 Ea=210 //Input Voltage of motor in volts
4 Ia1=80 //Armature Current in Ampere
5 N1=1200 //Rated Speed of Motor in rpm

```

```

6 Ra=0.08 //Armature resistance in ohm
7 Rf=0.08
8 N2=1000
9 //Solution
10 T1=poly(0, 'T1')
11 T2=2*T1
12 A=T2/T1
13 Ia2=Ia1*(sqrt(2)) //A=2
14 Eb1=Ea-(Ia1*Ra)
15 Eb2=Ia2*N2*Eb1/(Ia1*N1)
16 Rb=(Eb2/Ia2)-Ra
17 printf ('\n\n Braking=%0.1 f Amp\n\n', Ia2)
18 printf ('\n\n Braking Resistor=%0.1 f ohm\n\n', Rb)

```

Scilab code Exa 4.38 Ex38

```

1 clc
2 //Variable Initialisation
3 Ea=500 //Input Voltage of motor in volts
4 Ra=0.06 //Armature resistance in ohm
5 Rf=0.09 //Field Resistance in ohm
6 K=35e-3 //Motor Constant
7 T=560 //Rated Torque in N-m
8 N1=0 //Rated Speed of Motor in rpm
9 d2=1 //Duty ratio
10 //Solution
11 Ia=sqrt(T/K) //Armature Current in Ampere
12 d1=(Ia*(Ra+Rf)+K*Ia*N1)/Ea
13 N2=(d2*Ea-Ia*(Ra+Rf))/(K*Ia)
14 N2rpm=N2*30/%pi
15 d3=0.6
16 N3=((d3*Ea-Ia*(Ra+Rf))/(K*Ia))*30/%pi
17 d4=0.8
18 N4=((d4*Ea-Ia*(Ra+Rf))/(K*Ia))*30/%pi
19 d=[d1, d3, d4, d2]

```

```
20 N=[N1,N3,N4,N2rpm]
21 plot(d,N)
22 ylabel("Speed in rpm", "fontsize", 2)
23 xlabel("Duty Ratio", "fontsize", 2)
```

Scilab code Exa 4.39 Ex39

```
1 clc
2 //Variable Initialisation
3 Ea=600 //Input Voltage of motor in volts
4 Ia=500 //Armature Current in Ampere
5 d1=0.6 //Duty Ratio
6 Ra=0.05 //Armature resistance in ohm
7 Rf=0.07 //Field Resistance in ohm
8 K=15.27e-3 //Motor Constant
9 //Solution
10 E0=d1*Ea
11 Pin=E0*Ia
12 Re=Ea/(Ia*d1)
13 Eb=E0-(Ia*(Ra+Rf))
14 W=Eb/(Ia*K)
15 N=W*60/(2*pi)
16 T=K*(Ia^2)
17 printf ('\n\n Input Power From Source=%0.1f KW\n\n',
          Pin*10^-3)
18 printf ('\n\n Equivalent Output Resistor=%0.1f ohm\n\n',
          Re)
19 printf ('\n\n Motor Speed=%0.1f rpm\n\n', N)
20 printf ('\n\n Motor Torque=%0.1f N-m\n\n', T)
```

Scilab code Exa 4.40 Ex40

```
1 clc
```

```

2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 N1=700 //Rated Speed of Motor in rpm
5 T1=247
6 Ra=0.06 //Armature resistance in ohm
7 Rf=0.04
8 d1=0.7
9 T2=1.5*T1
10 Ia1=133 //Armature Current in Ampere
11 //Solution
12 K=T2/Ia1
13 R=Ra+Rf
14 Eb=(d1*Ea)-(Ia1*R) //Wrong value taken in book for
    Armature current
15 W=Eb/K
16 N2=W*60/(2*pi)
17 printf ('\n\n Motor Speed=%0.1f rpm\n\n',N2) //The
    answer provided in the textbook is wrong

```

Scilab code Exa 4.41 Ex41

```

1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 Ia=125 //Armature Current in Ampere
5 Eb=60 //Average Value of Back EMF
6 f=200 //Chopper Frequency
7 Ra=0.025 //Armature resistance in ohm
8 Rf=0.015 //Field resistance in ohm
9 //Solution
10 d1=(Eb+(Ia*(Ra+Rf)))/Ea
11 T=(1/f)
12 ton=d1*T
13 printf ('\n\n The Pulse Width=%0.1f msec\n\n',ton
    *10^3)

```

Scilab code Exa 4.42 Ex42

```
1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 d1=0.8 //Duty Ratio
5 Ia1=300 //Armature Current in Ampere
6 Ra=0.04 //Armature resistance in ohm
7 N1=600 //Rated Speed of Motor in rpm
8 //Solution
9 E0=d1*Ea
10 Eb1=E0-(Ia1*Ra)
11 Eb2=210
12 N2=(Eb1/Eb2)*N1
13 Ia3=310
14 N3=500
15 Eb3=142
16 T=Eb3*Ia3/(2*pi*N3/60) //Wrong calculated in book
    used N=520 instead of 500
17 printf ('\n\n The Motor Speed=%0.1f rpm\n\n',N2)
18 printf ('\n\n The Motor Torque=%0.1f N-m\n\n',T) //The
    answer provided in the textbook is wrong)
```

Scilab code Exa 4.43 Ex43

```
1 clc
2 //Variable Initialisation
3 Ea=220 //Input Voltage of motor in volts
4 d1=0.8 //Duty Ratio
5 Ia1=310 //Armature Current in Ampere
6 Ra=0.04 //Armature resistance in ohm
```

```

7 N4=1500 //Rated Speed of Motor in rpm
8 //Solution
9 E0=d1*Ea
10 Eb1=E0+(Ia1*Ra)
11 N1=610 //Motor speed in rpm
12 Eb2=215
13 N2=(Eb1/Eb2)*N1
14 d2=0.95
15 E02=d2*Ea
16 Eb3=E02+(Ia1*Ra)
17 N3=(Eb3/Eb2)*N1
18 Eb4=(N4/N1)*Eb2
19 Ra1=((Eb4-E02)/Ia1)
20 printf ('\n\n Motor Speed=%0.1f rpm\n\n',N2)
21 printf ('\n\n Maximum Allowable Speed=%0.1f rpm\n\n',
      N3)//The answers vary due to round off error
22 printf ('\n\n Resistance to be Inserted=%0.1f ohm\n\n',
      Ra1)

```

Scilab code Exa 4.44 Ex44

```

1 clc
2 //Variable Initialisation
3 Eb2=215 //Average Value of Back EMF
4 Ia=300 //Armature Current in Ampere
5 Ia1=310 //Armature Current in Ampere
6 Ra=0.04 //Armature resistance in ohm
7 N1=610 //Rated Speed of Motor in rpm
8 N2=750 //Rated Speed of Motor in rpm
9 dmin=0.05 //Minimum Duty Ratio
10 //Solution
11 Eb1=(N2/N1)*Eb2
12 Rbe=(Eb1/Ia)-Ra
13 Rb=Rbe/(1-dmin)
14 R=Rb*(1-dmin)+Ra

```

```
15 K=Eb2/(2*pi*N1/60) //The answer provided in the
    textbook is wrong
16 T=K*Ia
17 printf ('\n\n Value of Braking Resistor=%0.1f ohm\n\n',
    ,Rb)
18 printf ('\n\n Maximum Available Motor Torque=%0.1f N-
    m\n\n' ,T)
```

Scilab code Exa 4.45 Ex45

```
1 clc
2 //Variable Initialisation
3 Ra=0.4 //Armature resistance in ohm
4 Rf=0.4 //Field resistance in ohm
5 N1=400 //Rated Speed of Motor in rpm
6 N2=500 //Rated Speed of Motor in rpm
7 //Solution
8 W1=2*pi*N1/60
9 W2=2*pi*N2/60
10 Ia=97.5
11 K=15.8
12 Eb=K*W2
13 Rb=(Eb/Ia)-Ra
14 printf ('\n\n Resistance across motor terminal=%0.1f
    ohm\n\n' ,Rb)
```

Scilab code Exa 4.46 Ex46

```
1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 d1=0.8 //Duty Ratio
5 d2=0.75 //Duty Ratio
```

```

6 Ia1=80 //Armature Current in Ampere
7 Ra=0.25 //Armature resistance in ohm
8 N2=750 //Rated Speed of Motor in rpm
9 N3=600 //Rated Speed of Motor in rpm
10 Ia2=70
11 Eb2=210 //Average Value of Back EMF
12 //Solution
13 E01=d1*Ea
14 Eb1=E01-(Ia1*Ra)
15 N1=(Eb1/Eb2)*N2
16 Ia2=86
17 E02=d2*Ea
18 Eb3=E02-(Ia2*Ra)
19 Wm=2*pi*N3/60
20 T=Eb3*Ia2/Wm
21 printf ('\n\n Motor Speed=%0.1f rpm\n\n',N1)
22 printf ('\n\n Torque produced=%0.1f N-m\n\n',T)

```

Scilab code Exa 4.47 Ex47

```

1 clc
2 //Variable Initialisation
3 Ea=230 //Input Voltage of motor in volts
4 d1=0.4 //Duty Ratio
5 Ia1=86 //Armature Current in Ampere
6 Ra=0.25 //Armature resistance in ohm
7 N1=850 //Rated Speed of Motor in rpm
8 N4=1300 //Rated Speed of Motor in rpm
9 Eb1=220 //Average Value of Back EMF
10 //Solution
11 E01=d1*Ea
12 Eb2=E01+(Ia1*Ra)
13 N2=(Eb2/Eb1)*N1
14 dmax=0.98 //Maximum aloowable duty ratio
15 E02=dmax*Ea

```

```

16 Eb3=E02+(Ia1*Ra)
17 N3=(Eb3/Eb1)*N1 //Wrong value of N1 is taken in
    textbook
18 Eb4=(N4/N1)*Eb1
19 R=((Eb4-E02)/Ia1)-Ra
20 E1=(N1/N4)*Eb3
21 n=E1/Eb1
22 printf ('\n\n Motor speed=%0.1f rpm\n\n',N2)
23 printf ('\n\n Maximum allowable motor Speed=%0.1f rpm
    \n\n',N3) //The answer provided in the textbook is
        wrong
24 printf ('\n\n Resistance to be inserted=%0.1f ohm\n\n
    ',R)
25 printf ('\n\n number of turns reduced to fraction=%0
    .1f\n\n',n)

```

Scilab code Exa 4.48 Ex48

```

1 clc
2 //Variable Initialisation
3 Ia1=86 //Armature Current in Ampere
4 Ra=0.25 //Armature resistance in ohm
5 N1=1000 //Rated Speed of Motor in rpm
6 N2=850 //Rated Speed of Motor in rpm
7 Eb1=220 //Average Value of Back EMF
8 dmin=0.5 //Minimum Duty Ratio
9 dmax=0.95 //Maximum Duty Ratio
10 //Solution
11 Eb2=(N1/N2)*Eb1
12 Rbe=(Eb2/Ia1)-Ra
13 Rb=Rbe/(1-dmin)
14 R=Rb*(1-dmax)+Ra
15 Eb3=Ia1*R
16 Eb4=190
17 Ia2=55

```

```

18 K=Eb4/(2*pi*N2/60)
19 T=K*Ia2
20 printf( '\n\n Braking Resistor=%0.1f ohm\n\n' ,Rb)
21 printf( '\n\n Maximum Available Motor Torque=%0.1f N-
m\n\n' ,T)

```

Scilab code Exa 4.49 Ex49

```

1 clc
2 //Variable Initialisation
3 Ea=500 //Input Voltage of motor in volts
4 d1=0.65 //Duty Ratio
5 Ra=0.06 //Armature resistance in ohm
6 Ia=300 //Armature Current in Ampere
7 Rf=0.08 //Field resistance in ohm
8 K=15.27e-3 //Motor Constant
9 //Solution
10 E0=(1-d1)*Ea
11 R=Ra+Rf
12 Req=(1-d1)*(Ea/Ia)+R
13 Pgen=E0*Ia
14 Wmin=R/K
15 Wminr=Wmin*(30/%pi)
16 Wmax=(Ea/(K*Ia))+(R*Ia/(K*Ia))
17 Wmaxr=Wmax*(30/%pi)
18 Eb=E0+(Ia*Ra)
19 W=Eb/(K*Ia)
20 Wr=W*(30/%pi)
21 printf( '\n\n Voltage across Chopper=%0.1f Volts\n\n'
,E0)
22 printf( '\n\n Equivalent Resistance of Motor=%0.1f
ohm\n\n' ,Req)
23 printf( '\n\n Power Generated=%0.1f KW\n\n' ,Pgen
*10^-3)
24 printf( '\n\n Maximum Permissible Braking Speed=%0.1f

```

```

        rpm\n\n', Wmaxr)
25 printf('\n\n Minimum Permissible Braking Speed=%0.1f
        rpm\n\n', Wminr)
26 printf('\n\n Motor Speed=%0.1f rpm\n\n', Wr)

```

Scilab code Exa 4.50 Ex50

```

1 clc
2 //Variable Initialisation
3 Ea=500 //Input Voltage of motor in volts
4 Ra=0.06 //Armature resistance in ohm
5 Rf=0.09 //Field resistance in ohm
6 K=12e-3 //Motor Constant
7 Ia=400 //Armature Current in Ampere
8 d1=0.6 //Duty Ratio
9 //Solution
10 E0=(1-d1)*Ea
11 Pin=E0*Ia
12 R=Ra+Rf
13 Req=(E0/Ia)+R
14 Wmin=R/K
15 Wminr=Wmin*30/%pi
16 Wmax=(R/K)+(Ea/(K*Ia))
17 Wmaxr=Wmax*30/%pi
18 Eb=E0+(Ia*R)
19 W=Eb/(K*Ia)
20 Wr=W*30/%pi
21 printf('\n\n Voltage across Converter=%0.1f Volts\n\
        n', E0)
22 printf('\n\n Power Generated=%0.1f KW\n\n', Pin
        *10^-3)
23 printf('\n\n Equivalent Resistance of Motor=%0.1f
        ohm\n\n', Req)
24 printf('\n\n Maximum Permissible Braking Speed=%0.1f
        rpm\n\n', Wmaxr)

```

```
25 printf ('\n\n Minimum Permissible Braking Speed=%0.1f  
          rpm\n\n', Wminr)  
26 printf ('\n\n Motor Speed=%0.1f rpm\n\n', Wr)
```

Scilab code Exa 4.51 Ex51

```
1 clc  
2 //Variable Initialisation  
3 Ia=300 //Armature Current in Ampere  
4 Rb=8 //Braking resistance in ohm  
5 Ra=0.05 //Armature resistance in ohm  
6 Rf=0.08 //Field resistance in ohm  
7 d=0.5 //Duty Ratio  
8 K=14e-3 //Motor Constant  
9 //Solution  
10 E0=(1-d)*Ia*Rb  
11 Pin=(Ia^2)*Rb*(1-d)  
12 R=Ra+Rf  
13 Req=Rb*(1-d)+R  
14 Eb=E0+(Ia*R)  
15 W=Eb/(K*Ia)  
16 Wr=W*30/%pi  
17 Ep=Ia*Rb  
18 printf ('\n\n Voltage across Converter=%0.1f Volts\n\n', E0)  
19 printf ('\n\n Power dissipated=%0.1f KW\n\n', Pin  
          *10^-3)  
20 printf ('\n\n Equivalent Resistance of Motor=%0.1f  
          ohm\n\n', Req)  
21 printf ('\n\n Motor Speed=%0.1f rpm\n\n', Wr)  
22 printf ('\n\n Peak to Peak Voltage of Converter=%0.1f  
          Volts\n\n', Ep)
```

Chapter 5

Stator Voltage Control of Induction Motor Drives

Scilab code Exa 5.1 Ex1

```
1 clc
2 //Variable Initilisation
3 Ns=1500 //Speed of Squirrel Cage Induction Motor in
           RPM
4 N1=1460 //Speed of Squirrel Cage Induction Motor in
           RPM
5 N2=1350 //Speed of Squirrel Cage Induction Motor in
           RPM
6
7 // At 1460 rpm the speed slip is given by
8 S1=(Ns-N1)/Ns //Slip
9 I=(sqrt(1/3)*(2/3))/(sqrt(S1)*(1-S1))
10 // At 1350 rpm the speed slip is given by
11 S2=(Ns-N2)/Ns //Slip
12 I1=(sqrt(1/3)*(2/3))/(sqrt(S2)*(1-S2))
13
14
15 //Results
16 printf('\\n\\n The motor maximum Current in terms of
```

```
    rated current at the above speed =%0.1f \n\n',I)
17 printf('\n\n The motor maximum Current in terms of
    rated current at the above speed =%0.1f \n\n',I1)
```

Scilab code Exa 5.2 Ex2

```
1 clc
2 //variable Initialisation
3 V=415 //Voltage Input in Volts
4 f=50 //supply frequency in Hz
5 P=4 //No of Poles
6 N1=1450 //Rotor Speed in rpm
7 N2=1290 //Rotor Speed in rpm for case II
8 R1=1.01
9 R2=0.69
10 X1=1.08
11 X2=1.60
12 Xm=36
13 T1=42 //Rated torque in N-m
14 //Solution
15 Vph=V/sqrt(3)
16 Ns=120*f/P
17 Ws=2*pi*Ns/60
18 Wm=2*pi*N1/60
19 K=T1/(Wm^2)
20 s=(Ns-N2)/Ns //Slip
21 Wm2=Ws*(1-s)
22 T1=K*(Wm2^2) //Load Torque in N-m
23 T12=T1*Wm2 //Torque in Synchronous Watts
24 I2=sqrt((T12*s)/(3*R2*(1-s)))
25 Z=R1+(R2/s)+(%i*(X1+X2)) //Impedance at slip s
26 V2=I2*abs(Z) //Voltage applied in Volts/Phase
27 Im=V2/(%i*Xm)
28 Im1=abs(Im)
29 Ir=V2/Z //Rotor Current
```

```

30 Is=Ir+Im//Stator Current
31 a=atand(imag(Is)/real(Is))
32 Pin=3*V2*abs(Is)*cosd(a)//Input Power
33 Smax=1/3//Smax is obtain theortically
34 I2max=Ws*sqrt(Smax)*(1-Smax)*sqrt(K*Ws/(3*R2))
35 Nr=Ns*(1-Smax)//Speed at maximum Current
36 Wmax=2*pi*Nr/60
37 T=3*(I2max^2)*R2*(1-Smax)/(Smax*Wmax)//Torque at
    maximum Current
38 printf('\n\n The Load torque=%0.1f N-m\n\n',T1)
39 printf('\n\n The Rotor Current=%0.1f Amp\n\n',Ir)
40 printf('\n\n The Stator Supply Voltage=%0.1f Volts\n
    \n',V2)
41 printf('\n\n The Motor input current=%0.1f Amp\n\n',
    Is)
42 printf('\n\n The Motor input power=%0.1f Watt\n\n',
    Pin)//The answer provided in the textbook is
    wrong
43 printf('\n\n Maximum rotor Current=%0.1f Amp\n\n',
    I2max)
44 printf('\n\n The speed at maximum current=%0.1f rad/
    sec\n\n',Wmax)
45 printf('\n\n The torque at maximum current=%0.1f N-m
    \n\n',T)

```

Scilab code Exa 5.3 Ex3

```

1 clc
2 //variable Initialisation
3 V1=440//Voltage Input in Volts
4 f1=50//supply frequency in Hz
5 P=25e+3//power rating in Watts
6 N1=950//Rotor Speed in rpm
7 Z=0.1+(%i*3)//Rotor Impedance
8 pole=6//No of poles

```

```

9 f2=80 //Supply 2 frequency in Hz
10 //Solution
11 V=V1/sqrt(3) //Phase Voltage in Volts
12 Wm=2*pi*N1/60
13 Tfl=P/Wm //Full load Torque in N-m
14 Ns=120*f2/pole
15 Vs=2*pi*Ns/60
16 Z2=Z*(f2/f1) //Rotor Impedance at 80 Hz
17 S=3*(V^2)*0.5/(Vs*((abs(Z2))^2)*Tfl)
18 Nr=Ns*(1-S)
19 Rl=real(Z)
20 Xl=imag(Z2)
21 Smax=(Rl/Xl)
22 Tmax=3*(V^2)/(Vs*2*Xl)
23 printf ('\n\n The Motor speed=%0.1f rpm\n\n',Nr) //The
   answers vary due to round off error
24 printf ('\n\n The Slip at which maximum torque occurs
   =%0.1f\n\n',Smax)
25 printf ('\n\n The maximum Torque=%0.1f\n\n',Tmax)

```

Scilab code Exa 5.4 Ex4

```

1 clc
2 //variable initialisation
3Vm=400 //Input Voltage in volt
4 F=50 //supply frequency in Hz
5 P1=4 //number of poles
6 R1=0.15 //resistance of stator in ohm
7 R2=0.12 //resistance of rotor in ohm
8 X1=0.45 //reactance of Motor in ohm
9 X2=0.45 //reactance of Motor in ohm
10 Xm=28.5 //reactance of Motor in ohm
11 S=0.04 //Slip Of Motor
12
13 //Solution

```

```

14 R1=R2*((1/S)-1)
15 Vph=Vm/sqrt(3)
16 I2=Vph/((R1+R2+R1)+%i*(X1+X2))
17 I0=Vph/(%i*Xm)
18 I1=I0+I2
19 y=imag(I1)
20 x=real(I1)
21 phi=atand(y/x)
22 pf=cosd(phi)
23 printf('\n\n The Stator Current=%0.1f Amp\n\n',I1)
24 printf('\n\n The Power Factor=%0.1f lag\n\n',pf)

```

Scilab code Exa 5.5 Ex5

```

1 clc
2 //variable initialisation
3 Pout=37.3 //Motor Output In KW
4 Vm=440 //Motor Input in volt
5 F=50 //supply frequency in Hz
6 I0=20 //NO Load Line Current Of Motor
7 R1=0.1 //resistance of stator in ohm
8 R2=0.15 //resistance of rotor in ohm
9 X1=0.4 //reactance of Motor in ohm
10 X2=0.44 //reactance of Motor in ohm
11 S=0.03 //Slip Of Motor
12 Ls=1250 //Stator Core Loses In Watt
13 Lr=1000 //Rotational Losses In KW
14 Ns=1500 // Synchronous Speed Of Motor
15
16 //Solution
17 Vph=Vm/sqrt(3)
18 I2=Vph/((R1+(R2/S))+%i*(X1+X2))
19 I21=abs(I2)
20 I21=49.1//rounding off to avoid computational error
21 I0=1.78-(%i*19.9)//Taken in book for No load motor

```

```

        current
22 I1=I0+I2
23 y=imag(I1)
24 x=real(I1)
25 phi=atand(y/x)
26 pf=cosd(phi)
27 P2=3*((I21)^2)*(R2/S)
28 Tg=(9.55*P2)/Ns
29 Pm=(1-S)*P2
30 Pout1=Pm+Lr
31 Lcs=3*((I21)^2)*R1 //Wrong value of I2 is taken in
    textbook
32 Lcr=S*P2
33 Lt=Ls+Lr+Lcs+Lcr
34 Pin=Lt+Pout1
35 n=Pout1/Pin
36 printf('\n\n The input line Current=%0.1f Amp\n\n', I1)
37 printf('\n\n The power factor=%0.1f lag\n\n', pf)
38 printf('\n\n The Electromagnetic Torque Developed=%0
    .1f N-m\n\n', Tg)
39 printf('\n\n The output=%0.1f Watts\n\n', Pm)
40 printf('\n\n The efficiency of Motor=%0.1f\n\n', n)
41 //The answers vary due to round off error

```

Scilab code Exa 5.6 Ex6

```

1 clc
2 //variable initialisation
3 Vm=400 //Supply Voltage in volt
4 F=50 //supply frequency in hertz
5 P=6 //Number Of Poles
6 R1=0.15 //resistance of stator in ohm
7 R2=0.15 //resistance of rotor in ohm
8 X1=0.8 //reactance of Motor in ohm

```

```

9 X2=0.8 //reactance of Motor in ohm
10 S=0.04 //Slip Of Motor
11
12 //Solution
13 Ns=(120*F)/P
14 Ws=((2*pi)/60)*1000
15 Sr=2-S
16 Vph=Vm/(sqrt(3))
17 I2=Vph/(sqrt(((R1+(R2/((2-S))))^2)+((X1+X2)^2)))
18 Ts_b=(3*((I2)^2)*(R2/(2-S)))/(Ws)
19 printf ('\n\n The Initial Braking Torque=%0.1f N-m\n\
n', Ts_b)

```

Scilab code Exa 5.7 Ex7

```

1 clc
2 //variable initialisation
3 Pout=7.5 // Output Of Motor In KW
4 Vm=230 //Supply Voltage in volt
5 F=50 //supply frequency in hertz
6 R1=0.36 //resistance of stator in ohm
7 R2=0.222 //resistance of rotor in ohm
8 X1=0.47 //reactance of Motor in ohm
9 X2=0.47 //reactance of Motor in
10 Xm=15.5 //reactance of Motor in ohm
11 S=0.4723 //Slip Of Motor
12 P=4 //Number Of Poles
13
14 //Solution
15 Vph=Vm/sqrt(3)
16 Z=((R1+(R2/S))+(%i*(X1+X2)))
17 I2=Vph/Z
18 I2r=abs(I2)
19 Lcr=3*((I2r)^2)*R2
20 P2=Lcr/S

```

```

21 Ns=(120*F)/P
22 Tst=(9.55*P2)/Ns
23 Sm=R2/X2
24 Z1=(R1+R2)+%i*(X1+X2)
25 Z2=abs(Z1)
26 I3=Vph/Z2
27 I4=abs(I3)
28 P3=3*((I4)^2)*R2
29 Tst1=(9.55*P3)/(Ns)
30 printf ('\n\n The Maximum Internal Torque=%0.1f N-m\n
  ',Tst)
31 printf ('\n\n Slip at Maximum Torque=%0.1f\n',Sm)
32 printf ('\n\n The Starting Torque=%0.1f N-m\n',Tst1
  )

```

Scilab code Exa 5.8 Ex8

```

1 clc
2 //variable initialisation
3 Vm=400 //input of motor in volt
4 F=50 //supply frequency in hertz
5 P=4 //Number Of Poles
6 R1=1 //resistance of stator in ohm
7 R2=0.4 //resistance of rotor in ohm
8 X1=1 //reactance of Motor in ohm
9 X2=1 //reactance of Motor in ohm
10 Xm=50 //reactance of Motor in ohm
11 Vc=231 //Constant Voltage Source In Volt
12 I1=28//Current from Constant Current Source in Amp
13 //Solution
14 Xe=(X1*Xm)/(X2+Xm)
15 Sm=R2/(Xe+X2)
16 Sm1=R2/(X2+Xm)
17 Ve=(Vc*Xm)/(X1+Xm)
18 Ws=(4*pi*F)/(P)

```

```

19 Test=(3/Ws)*(((Ve)^2)/(R2^2+(X2+Xe)^2))*R2
20 Tem=(3/Ws)*(((Ve)^2)/(2*(X2+Xe)))
21 Test1=(3/Ws)*(((I1*Xm)^2)/(R2^2+(X2+Xm)^2))*R2
22 Tem1=(3/Ws)*(((I1*Xm)^2)/(2*(X2+Xm)))
23 Im=I1*((R2/Sm1)+(%i*X2))/((R2/Sm1)+%i*(X2+Xm))
24 V1=sqrt(3)*abs(Im)*Xm
25 printf ('\n\n The Slip for maximum torque for Voltage
           source=%0.1f\n\n',Sm)
26 printf ('\n\n The Slip for maximum torque for current
           source=%0.1f\n\n',Sm1)
27 printf ('\n\n The Starting Torque for Voltage source=
           %0.1f N-m\n\n',Test)
28 printf ('\n\n The Maximum Torque for Voltage Source=
           %0.1f N-m\n\n',Tem)
29 printf ('\n\n The Starting Torque for Current Source=
           %0.1f N-m\n\n',Test1)
30 printf ('\n\n The Maximum Torque for Current Source=
           %0.1f N-m\n\n',Tem1)
31 printf ('\n\n The Supply voltage required=%0.1f Volt\
           \n\n',V1)
32 //The answers vary due to round off error

```

Scilab code Exa 5.9 Ex9

```

1 clc
2 //variable initialisation
3 Vph=2200 //Supply Voltage in volt
4 F=50 //supply frequency in Hz
5 Pout=2600 // Output Of Motor In KW
6 P=8 //Number Of Poles
7 N1=735 //Speed OF Motor In rpm
8 Rs=0.075 //Resistance of stator in ohm
9 Rr=0.1 //Resistance of rotor in ohm
10 Xs=0.45 //Reactance of Motor in ohm
11 Xr=0.55 //Reactance of Motor in ohm

```

```

12
13 // Solution
14 Ns=(120*F)/P
15 S=(Ns-N1)/Ns
16 Iph=Vph/sqrt((Rs+((Rr/S)^2))+((Xs+Xr)^2))
17 I1=sqrt(3)*Iph
18 Wms=(2*pi*Ns)/60
19 T1=(3*((Iph)^2))/(S*(Wms))
20 Ilm=Vph/(sqrt(3)*sqrt(((Rs+Rr)^2)+((Xs+Xr)^2)))
21 S2=1
22 Tst=(3*((Ilm)^2)*0.1)/(S2*Wms)
23 r1=Tst/T1//ratio of Tst and Tl
24 Tmax=(3/(2*Wms))*(((Vph/sqrt(3))^2)/((Rs+sqrt((Rs^2)
    +(Xs+Xr)^2))))
25 r2=Tmax/T1//ratio of Tmax and Tl
26 Rr2=0.15
27 Xr2=0.9
28 I11=(sqrt(3)*Vph)/(sqrt(((Rs+Rr)^2)+((Xs+Xr2)^2)))
29 Iph1=I11/(sqrt(3))
30 Tst1=(3*((Iph1)^2)*(Rr))/(Wms)
31 Rs1=Rs/3
32 Rr1=Rr/3
33 Xs1=Xs/3
34 Xr1=Xr/3
35 Inew=2*I1
36 X=sqrt(((Vph/(sqrt(3)*Inew))^2)-((Rs1+Rr1)^2))
37 Xe=X-Xs1-Xr1
38 printf('\n\n Ratio of starting torque and load
        torque=%0.1f \n\n',r1)//The answer provided in
        the textbook is wrong
39 printf('\n\n Ratio of maximum torque and load torque
        =%0.1f \n\n',r2)
40 printf('\n\n The Maximum line current during
        starting=%0.1f Amp\n\n',I11)//The answer provided
        in the textbook is wrong
41 printf('\n\n The maximum torque at starting=%0.1f N-
        m\n\n',Tst1)//The answer provided in the textbook
        is wrong

```

```
42 printf ('\n\n The required value of reactor=%0.1f ohm\n\n', xe)
```

Scilab code Exa 5.10 Ex10

```
1 clc
2 //variable initialisation
3 Vm=400 //Rated Voltage of motor in volt
4 Vs=440 //Supply Voltage of motor in volt
5 F=50 //Supply frequency in hertz
6 P=4 //Number Of Poles
7 N1=1475 //Speed OF Motor In rpm
8 R1=0.35 //Resistance of stator in ohm
9 R2=0.18 //Resistance of rotor in ohm
10 X1=0.9 //Reactance of Motor in ohm
11 X2=0.7 //Reactance of Motor in ohm
12 Xm=25 //Reactance of Motor in ohm
13
14 //Solution
15 Vph1=Vs/(sqrt(3))
16 Vph2=Vm/(sqrt(3))
17 Ns=(120*F)/(P)
18 S=(Ns-N1)/Ns
19 I2=(Vph2)/sqrt(((R1+(R2/S))^2)+((X1+X2)^2))
20 Pg=3*(I2^2)*(R2/S)
21 Sm=R2/sqrt((R1)^2+((X1+X2)^2))
22 Wms=(2*pi*Ns)/60
23 Tm=3*(Vph1^2)/((2*Wms)*(R1+sqrt((R1)^2+((X1+X2)^2))))
    )
24 Zi=%i*(Xm*((R1+(R2/S))+%i*(X1+X2)))/(R1+(R2/S)+%i*(X1+X2+Xm))
25 Z=abs(Zi)
26 printf ('\n\n The Slip=%0.1f\n\n', S)
27 printf ('\n\n The Air gap Power Angle=%0.1f Watts\n\n', Pg)
```

```

28 printf ('\n\n The Slip for maximum torque=%0.1f\n\n', 
29   Sm)
30 printf ('\n\n The Maximum Torque=%0.1f N-m\n\n', Tm)
31 printf ('\n\n The Input Impedance=%0.1f\n\n', Z)
31 //The answers vary due to round off error

```

Scilab code Exa 5.11 Ex11

```

1 clc
2 //variable Initialisation
3 Vm=240 //Terminal Voltage Of Motor In Volt
4 F=50 //Supply Frequency Of Motor
5 P=4 //Number Of Pole
6 R1=0.25 //Resistance Of Motor in Ohm
7 R2=0.60 //Resistance Of Motor in Ohm
8 X1=0.36 //Reactance in Ohm
9 X2=0.36 //Reactance in Ohm
10 Xm=17.3 //Reactance In Ohm
11 Nr1=1400 //Speed Of Rotor In RPM
12 Nr2=600 //Speed Of Rotor In RPM
13
14 //Solution
15 #Case=1
16 W=((2*pi)/60)*(Nr1)
17 Ns=(120*F)/(P)
18 S1=(Ns-Nr1)/Ns
19 S2=(Ns-Nr2)/Ns
20 Zr=(R2/S1)+%i*(X2)
21 Zs=R1+%i*(X1)
22 Zt=Zr+Zs
23 Zin=(%i*(Xm)*(Zt))/(%i*(Xm)+(Zt))
24 Tl=1.4*((10)^-3)*(W)^2
25 n=Nr1/60
26 I2=sqrt((S1*Tl*2*pi*n)/(3*R2*(1-S1)))
27 #Case=2

```

```

28 Zr1=(R2/S2)+%i*(X2)
29 Zs1=R1+%i*(X1)
30 Zt1=Zr1+Zs1
31 Zin1=(%i*(Xm)*(Zt1))/(%i*(Xm)+(Zt1))
32 W1=((2*pi)/60)*(Nr2)
33 T11=1.4*((10)^-3)*(W1)^2
34 n1=Nr2/60
35 I3=sqrt((S2*T11*2*pi*n1)/(3*R2*(1-S2)))
36 // Given base currents in Amp
37 Ib1=17.55
38 Ib2=100.27
39 Ip1=I2/Ib1
40 Ip2=I3/Ib2
41 printf('\n\n The per unit rotor Current for case 1=
        %0.1f\n\n',Ip1)
42 printf('\n\n The per unit rotor Current for case 2=
        %0.1f\n\n',Ip2)

```

Scilab code Exa 5.12 Ex12

```

1 clc
2 //variable Initialisation
3 Vm=400 //Terminal Voltage Of Motor In Volt
4 F=50 //Supply Frequency Of Motor
5 P=6 //Number Of Pole
6 R1=0.2 //Resistance Of Motor in Ohm
7 R2=0.2 //Resistance Of Motor in Ohm
8 X1=0.5 //Reactance in Ohm
9 X2=0.5 //Reactance in Ohm
10 Xm=15 //Reactance In Ohm
11 S=0.05 //Slip Of Motor
12
13 //Solution
14 Ns=(120*F)/(P)
15 Ws=((2*pi)/60)*(Ns)

```

```

16 Vph=Vm/sqrt(3)
17 S1=2-S
18 I2=(Vph)/sqrt(((R1+(R2/S1))^2)+((X1+X2)^2))
19 Im=Vph/Xm
20 I1=Im+I2
21 Tb=((3*((I2)^2))/(Ws))*(R2/S1)
22 printf('\n\n The Primary Current=%0.1f Amp\n\n',I1)
23 printf('\n\n The Braking Torque=%0.1f N-m\n\n',Tb)

```

Scilab code Exa 5.13 Ex13

```

1 clc
2 //variable Initialisation
3 Vm=400 //Terminal Voltage Of Motor In Volt
4 F=50 //Supply Frequency
5 P=6 //Number Of Pole
6 R1=1.5 //Resistance Of Motor in Ohm
7 R2=1.5 //Resistance Of Motor in Ohm
8 X1=2.5 //Reactance in Ohm
9 X2=2.5 //Reactance in Ohm
10 Nr1=900 //Speed Of Rotor In RPM
11 Nr2=400 //Speed Of Rotor In RPM
12
13 //Solution
14 Vph=Vm/sqrt(3)
15 Ns=(120*F)/(P)
16 S=(Ns-Nr1)/Ns
17 I2=(Vph)/sqrt(((R1+(R2/S))^2)+((X1+X2)^2))
18 Ws=((2*pi)/60)*(Ns)
19 T=((3*((I2)^2))/(Ws))*(R2/S)
20 //At Braking
21 Sb=2-S
22 I2b=(Vph)/sqrt(((R1+(R2/Sb))^2)+((X1+X2)^2))
23 Tb=((3*((I2b)^2))/(Ws))*(R2/Sb)
24 S1=(Ns+Nr2)/Ns

```

```

25 I3=(Vph)/sqrt(((R1+(R2/S1))^2)+((X1+X2)^2))
26 T1=((3*((I3)^2))/(Ws))*(R2/S1)
27 printf ('\n\n The Full load Torque=%0.1f N-m\n\n',T)
28 printf ('\n\n The Initial braking Torque=%0.1f N-m\n\n',
29     n', Tb)
30 printf ('\n\n The braking Torque at 400 rpm=%0.1f N-m
31 \n\n', T1)

```

Scilab code Exa 5.14 Ex14

```

1
2 clc
3 //variable Initialisation
4 Vm=400 //Terminal Voltage Of Motor In Volts
5 Pout=3 //Output Of Motor In KW
6 F=50 //Supply Frequency
7 P=4 //Number Of Pole
8 R1=2.5 //Resistance Of Motor in Ohm
9 R2=4.5 //Resistance Of Motor in Ohm
10 X1=6 //Reactance in Ohm
11 X2=6 //Reactance in Ohm
12 Nr1=1400 //Speed Of Rotor In RPM
13 Nr2=1300 //Speed Of Rotor In RPM
14
15 //Solution
16 Ns=(120*F)/(P)
17 S=(Ns-Nr1)/Ns
18 Vph=Vm/sqrt(3)
19 I2=(Vm)/sqrt(((R1+(R2/S))^2)+((X1+X2)^2))
20 Ws=((2*pi)/60)*(Ns)
21 T1=((3*((I2)^2))/(Ws))*(R2/S)
22 K=T1/((1-S)^2)
23 S1=(Ns-Nr2)/Ns
24 T11=K*((1-S1)^2)
25 Vs=sqrt(T11*S1*Ws*(((R1+(R2/S1))^2)+((X1+X2)^2)))

```

```

    /((3)*(R2))) //Wrongly calculated in textbook
26 printf ('\n\n The Voltage To be Applied=%0.1f Volts\n
           \n',Vs)
27 //The answer provided in the textbook is wrong

```

Scilab code Exa 5.15 Ex15

```

1 clc
2 //variable Initialisation
3 Vm=400 //Terminal Voltage Of Motor In Volt
4 F=50 //Supply Frequency
5 P=6 //Number Of Pole
6 R1=0.6 //Resistnce Of Motor in Ohm
7 R2=0.5 //Resistnce Of Motor in Ohm
8 X1=1.3 //Reactance in Ohm
9 X2=1.3 //Reactance in Ohm
10 Xm=50 //Reactance In Ohm
11 Nr=950 //Speed Of Rotor In RPM
12
13 //Solution
14 Ns=(120*F)/(P)
15 Wms=((2*pi)/60)*(Ns)
16 S=(Ns-Nr)/Ns
17 Vph=Vm/sqrt(3)
18 I2=(Vph)/sqrt(((R1+(R2/S))^2)+((X1+X2)^2))
19 Im=Vph/Xm
20 I1=Im+I2
21 Z1=(%i*(Xm)*((R2/S)+%i*(X2)))/((R2/S)+(%i*(X2+Xm)))
22 Zf=R1+%i*(X1)+(Z1)
23 Z2=%i*Xm*((R2/(2-S))+(%i*(X2)))/((R2/(2-S))+(%i*(X2+
           Xm)))
24 Zb=R1+%i*(X1)+(Z2)
25 Z3=Zf+Zb
26 Znew=abs(Z3)
27 I=Vph/Znew

```

```

28 Tp=(3*((I)^2)*((Xm)^2)*(R2/S))/((Wms)*(((R2/S)^2)+((X2+Xm)^2)))
29 Tn=-((3*((I)^2)*((Xm)^2)*(R2/(2-S)))/((Wms)*(((R2
/(2-S))^2)+((X2+Xm)^2))))
30 T=Tp+Tn
31 Wm=Wms*(1-S)
32 Tl=(8.4/1000)*(Wm^2) //Given
33 printf ('\n\n The Motor Speed=%0.1f rpm\n\n',Ns)
34 printf ('\n\n The motor Current=%0.1f Amp\n\n',I)
35 disp(" Since T=Tl , Motor will run Safely")

```

Chapter 6

Control of Induction Motor Drives through Stator Frequency

Scilab code Exa 6.1 Ex1

```
1 clc
2 //variable initialization
3 Vm=415 //input of motor in volt
4 F1=50 //supply frequency in hertz
5 F2=35 //supply frequency in hertz
6 F3=10 //supply frequency in hertz
7 N=1460 //speed of motor in rpm
8 P=4 //number of poles
9 R1=0.65 //resistance of stator in ohm
10 R2=0.35 //resistance of rotor in ohm
11 X1=0.95 //reactance of Motor in ohm
12 X2=1.43 //reactance of Motor in ohm
13 Xm=28 //reactance of Motor in ohm
14
15
16
17 // Solution
```

```

18 V1ph=Vm/sqrt(3)
19 Ns1=(120*F1)/P
20 Wsm1=(2*pi/60)*Ns1
21 Sm1=R2/sqrt((R1^2)+(X1+X2)^2) // Slip for maximum
   torque
22 Nr1=Ns1*(1-Sm1)
23 Tm1=3*((V1ph)^2)/(2*Wsm1*(R1+sqrt((R1)^2+(X1+X2)^2)))
   )
24
25 V2ph=Vm/sqrt(3)
26 X3=X1*(F2/F1)
27 X4=X2*(F2/F1)
28 Sm2=R2/sqrt((R1^2)+(X3+X4)^2) // Slip for maximum
   torque
29 Ns2=(120*F2)/P
30 Wsm2=(2*pi/60)*Ns2
31 Nr2=Ns2*(1-Sm2)
32 Tm2=3*((V2ph*F2/F1)^2)/(2*Wsm2*(R1+sqrt((R1)^2+(X3+
   X4)^2)))
33
34 V3ph=Vm/sqrt(3)
35 X5=X1*(F3/F1)
36 X6=X2*(F3/F1)
37 Sm3=R2/(sqrt((R1^2)+((X5+X6)^2))) // Slip for maximum
   torque
38 Ns3=(120*F3)/P
39 Wsm3=(2*pi/60)*Ns3
40 Nr3=Ns3*(1-Sm3)
41 Tm3=3*((V3ph*F3/F1)^2)/(2*Wsm3*(R1+sqrt((R1)^2+(X5+
   X6)^2)))
42 printf('\n\n speed at which maximum torque occurs
   for 50 Hz=%0.1f rpm\n\n',Nr1)
43 printf('\n\n maximum torque for 50 Hz=%0.1f N-m\n\n',
   ,Tm1)
44 printf('\n\n speed at which maximum torque occurs
   for 35 Hz=%0.1f rpm\n\n',Nr2)
45 printf('\n\n maximum torque for 35 Hz=%0.1f N-m\n\n',
   ,Tm2)

```

```
46 printf ('\n\n speed at which maximum torque occurs  
        for 10 Hz=%0.1f rpm\n\n',Nr3)  
47 printf ('\n\n maximum torque for 10 Hz=%0.1f N-m\n\n'  
        ,Tm3)
```

Scilab code Exa 6.2 Ex2

```
1 clc  
2 //variable initialization  
3 Pout=50 //output of induction motor in kilowatt  
4 Vm=400 //input of motor in volt  
5 F0=50 //supply frequency in hertz  
6 N1=1470 //speed of motor in rpm  
7 P=4 //number of pole  
8 Rs=0.42 //resistance of stator in ohm  
9 Rr=0.23 //resistance of rotor in ohm  
10 Xs=0.95 //reactance of stator in ohm  
11 Xr=0.85 //reactance of rotor in ohm  
12 Xm=28 //reactance of motor in ohm  
13 Sm=0.12 //slip of motor  
14 //Solution  
15 Vs=Vm/sqrt(3)  
16 W0=2*pi*F0  
17 K=Rr/(Sm*(Xs+Xr))  
18 F=K*F0 //Supply Frequency  
19 Tdm=3*P*Vs^2/(2*(K^2)*W0*(Xs+Xr))  
20 Ws=(K*W0*2)/(P)  
21 Wm=Ws*(1-Sm)  
22 N2=Wm*60/(2*pi)  
23 printf ('\n\n Supply Frequency=%0.1f Hz\n\n',F)  
24 printf ('\n\n The Breakdown Torque=%0.1f N-m\n\n',Tdm)  
25 printf ('\n\n The Speed at maximum torque=%0.1f rpm\n\n',N2)
```

Scilab code Exa 6.3 Ex3

```
1 clc
2 //variable initialization
3 Pout=50 //output of induction motor in kilowatt
4 Vm=400 //input of motor in volt
5 F0=50 //supply frequency in hertz
6 N1=1475 //speed of motor in rpm
7 P=4 //number of poles
8 Rs=0.42 //resistance of stator in ohm
9 Rr=0.23 //resistance of rotor in ohm
10 Xs=0.95 //reactance of stator in ohm
11 Xr=0.85 //reactance of rotor in ohm
12 Xm=30 //reactance of motor in ohm
13 Tdm=225 //Breakdown Torque In N-m
14 K=poly(0,'K')
15
16
17
18
19 //Solution
20 W0=2*%pi*F0
21 Vp=Vm/sqrt(3)
22 K=sqrt((3*2*(Vp^2))/(2*Tdm*W0*(Xs+Xr)))
23 W1=K*W0
24 F1=W1/(2*pi)
25 Sm=Rr/(K*(Xs+Xr))
26 Vs=2*K*W0/(P)
27 Wm=Vs*(1-Sm)
28 N=Wm*60/(2*pi)
29 printf('\n\n The Supply Frequency=%0.1f Hz\n\n',F1)
30 printf('\n\n The slip at maximum torque=%0.1f\n\n',
Sm)
31 printf('\n\n The speed at maximum torque=%0.1f rpm\n
```

\n', N)

Scilab code Exa 6.4 Ex4

```
1 clc
2 //variable initialization
3 Pout=50 //output of induction motor in kilowatt
4 Vm=420 //input of motor in volt
5 F0=50 //supply frequency in hertz
6 F1=58 // frequency in hertz
7 N1=1475 //speed of motor in rpm
8 P=4 //number of poles
9 Rs=0.4 //resistance of stator in ohm
10 Rr=0.21 //resistance of rotor in ohm
11 Xs=0.95 //reactance of stator in ohm
12 Xr=0.85 //reactance of rotor in ohm
13 Xm=32 //reactance of motor in ohm
14
15 //Solution
16 Vp=Vm/sqrt(3)
17 K=F1/F0
18 W0=2*%pi*F0
19 W=W0*K
20 Sm=Rr/(K*(Xs+Xr))
21 Vs=2*K*W0/P
22 Wm=Vs*(1-Sm)
23 N=Wm*60/(2*%pi)
24 Tdm1=(3*2*(Vp^2))/(2*(K^2)*W0*(Xs+Xr))
25 printf('\n\n The Slip at maximum torque=%0.1f\n\n', Sm)
26 printf('\n\n The Speed at maximum torque=%0.1f rpm\n\n', N)//The answers vary due to round off error
27 printf('\n\n The Breakdown torque=%0.1f N-m\n\n', Tdm1)
```

Scilab code Exa 6.5 Ex5

```
1 clc
2 //variable initialization
3 Pout=30 //output of induction motor in kilowatt
4 Vm=400 //input of motor in volt
5 F0=50 //supply frequency in hertz
6 F1=40 // frequency in hertz
7 P=4 //number of poles
8 Rs=0.33 //resistance of stator in ohm
9 Rr=0.22 //resistance of rotor in ohm
10 Xs=0.9 //reactance of stator in ohm
11 Xr=0.9 //reactance of rotor in ohm
12
13 //Solution
14 Vs=Vm/sqrt(3)
15 Sm=Rr/(sqrt((Rs^2)+((Xs+Xr)^2)))
16 Ir=Vs/sqrt(((Rs+(Rr/Sm))^2)+((Xs+Xr)^2))
17 cos_P=cosd(atand((Xs+Xr)/(Rs+(Rr/Sm))))
18 Pi=sqrt(3)*Vm*Ir*cos_P
19 P0=3*(Ir^2)*Rr*((1/Sm)-1)
20 n=(P0/Pi)*100
21
22 K=F1/F0 //for frequency of 40 Hz
23 Xs2=K*Xs
24 Xr2=K*Xr
25 Sm2=Rr/(sqrt((Rs^2)+((Xs2+Xr2)^2)))
26 Vs2=K*Vs
27 Ir2=Vs2/sqrt(((Rs+(Rr/Sm2))^2)+((Xs2+Xr2)^2))
28 cos_p2=cosd(atand((Xs2+Xr2)/(Rs+(Rr/Sm2))))
29 Pi2=3*Vs2*Ir2*cos_p2
30 P02=3*(Ir2^2)*Rr*((1/Sm2)-1)
31 n2=(P02/Pi2)*100
32 printf('\n\n The Efficiency at breakdown torque with
```

```

50Hz=%0.1f\n\n',n)
33 printf('\n\n The Efficiency at breakdown torque with
        40Hz=%0.1f\n\n',n2)
34 //The answers vary due to round off error

```

Scilab code Exa 6.6 Ex6

```

1 clc
2 //variable initialization
3 Vm=400 //input of motor in volt
4 F=50 //supply frequency in hertz
5 N=1500 //speed of motor in rpm
6 P=6 //number of poles
7 R1=2 //resistance of stator in ohm
8 R2=3 //resistance of rotor in ohm
9 X1=4 //reactance of Motor in ohm
10 X2=4 //reactance of Motor in ohm
11 S=1 //Slip Of Motor
12
13 //Solution
14 Ns=(120*F)/P
15 Ws=(2*pi/60)*Ns
16 Vph=Vm/sqrt(3)
17 Tst=((3/Ws)*((Vph^2)/((R1+(R2/S))^2+(X1+X2)^2)))*R2
18 Ist=Vph/sqrt((R1+R2)^2+(X1+X2)^2)
19 printf('\n\n The Starting Torque=%0.1f N-m\n\n',Tst)
20 printf('\n\n The starting Current=%0.1f Amp\n\n',Ist)
)

```

Chapter 7

Control of Induction Motor Drives from Rotor Side

Scilab code Exa 7.1 Ex1

```
1 clc
2 //variable initialization
3 V=440 //voltage in volts
4 P=6 //number of poles
5 f=50 //frequency in Hz
6 R=0.3 //rotor resistance in ohm
7 X=1 //leakage reactance in ohm
8 s=0.03 //slip
9 N=800 //speed in rpm
10 K=2.2 //stator to rotor ratio
11
12 //solution
13 Ns=(120*f)/6
14 w=(2*pi/60)*Ns
15 Tf=(3/w)*((V^2)*(R/s))*(1/(((R/s)^2)+(X^2)))
16 k=Tf/((Ns*(1-s))^2)
17 Tl=k*(N^2)
18 s1=((Ns-N)/Ns)
19 Re=(X^2)*(s*Tl*w)*(1/(3*(V^2)-(Tl*w)))
```

```

20 X1=14.78
21 X2=0.07
22 Ree=(X1*0.2)-0.3
23 Ree1=(X2*0.2)-0.3
24 //since negative value of resistance is not feasible
25 Ree=2.656
26 //Rotor -referred value of external resistance
27 Rex=Ree/K^(2)
28 printf ('\n\n The Resistance to be inserted in rotor
circuit=%0.1f ohm\n\n',Rex)

```

Scilab code Exa 7.2 Ex2

```

1 clc
2 //variable initialisation
3 V=440 //Supply voltage in volts
4 P=4 //number of poles
5 f=50 //Supply frequency in Hz
6 R=0.2 //rotor resistance in ohm
7 X=0.35 //leakage reactance in ohm
8 N1=1450 //speed in rpm
9 N2=1200 //speed in rpm
10 S2=0.2
11 //solution
12 Vph=V/sqrt(3)
13 Ns=(120*f)/P//Synchronous Speed
14 Wms=2*pi*Ns/60
15 S=(Ns-N1)/Ns
16 T=(3/Wms)*(Vph^2)*(R/S)/((R/S)^2+(X)^2) //The answer
provided in the textbook is wrong
17 K=T/(1-S)
18 T2=K*(1-S2)
19 Vph2=sqrt(T2*((R/S)^2+(X)^2)/((3/Wms)*(R/S)))
20 V1=Vph2*sqrt(3)
21 printf ('\n\n Torque=%0.1f N-m\n\n',T) //The answer

```

provided in the textbook is wrong

```
22 printf ('\n\n Line Voltage to be imposed=%0.1f Volts\n',Vph2)
```

Scilab code Exa 7.3 Ex3

```
1 clc
2 //variable initialization
3 V=440 //voltage in volts
4 P=6 //number of poles
5 f=50 //frequency in Hz
6 R1=2 //resistance in ohm
7 R2=2 //resistance in ohm
8 X1=3 //reactance in ohm
9 X2=4 //reactance in ohm
10 N1=945 //speed in rpm
11 N2=800 //speed in rpm
12
13 //solution
14 Ns=(120*f)/P
15 s=(Ns-N1)/Ns
16 w=2*pi*Ns/60
17 T=(3/w)*((V^(2)*(R2/s))/(((R1+(R2/s))^(2))+(X1+X2)
    ^(2)))
18 k=T/(1-s)^2 //The answer provided in the textbook is
    wrong
19 s1=(Ns-N2)/Ns
20 T1=k*((1-s1)^(2)) //The answer provided in the
    textbook is wrong
21 V2=sqrt((T1*w*(((R1+(R2/s1))^(2))+((X1+X2)^(2)))/((R2/s1
    )*3))) //The answer provided in the textbook is
    wrong
22 I=V2/((R1+(R2/s1))+(%i*(X1+X2))) //The answer
    provided in the textbook is wrong
23 I1=sqrt(3)*I //The answer provided in the textbook is
```

wrong

```
24 printf ('\n\n The Line Current=%0.1f Amp\n\n', I1)
```

Scilab code Exa 7.4 Ex4

```
1 clc
2 //variable initialisation
3 V=400 //Supply voltage in volts
4 P=24 //number of poles
5 f=50 //frequency in Hz
6 P1=100e+3 //power in Watt
7 P2=100e+3 //power in Watt
8 K=1.4 //Turns ratio
9 R=0.03 //resistance in ohmm
10 N1=240 //speed in rpm
11 N2=180 //speed in rpm
12
13 //solution
14 Vp=V/sqrt(3)
15 Ns=(120*f)/P
16 s=(Ns-N1)/Ns
17 w=(2*pi*N1)/60
18 T=P1/w
19 R1=K^(2)*R
20 X=sqrt((3*Vp^2*R1/(T*2*pi*Ns*s/60))-((R1/s)^(2)))
21 s1=(Ns-N2)/Ns
22 T1=T*(N2/N1)^2
23 A=(T*2*pi*Ns*s1/60)/(3*(Vp^2))
24 R22=poly(0,'R22')
25 0=(R22^2)*(A/(s1^2)+(A*X^2)-R22 // Polynomial
           equation obtained for R22
26 R22=0.745 // After solving equation value of Resistor
27 R2=(R22-R1)/K^2
28 printf ('\n\n The Resistance to connect in series=%0
           .1f ohm\n\n', R2)
```

Scilab code Exa 7.5 Ex5

```
1 clc
2 V= 100 //supply voltage in volts
3 f=50 //frequency in Hz
4 p=6 //number of poles
5 Rs=0.6 //parameters in ohm
6 Rr=0.45 //parameters in ohm
7 Xr=1.2 //parameters in ohm
8 Xs=1.2 //parameters in ohm
9 Xm=45 //parameters in ohm
10 Sm=1
11 R=0.4495
12
13 //solution
14 Re=((((Rs^2)+(Xs+Xr)^2)*Sm-Rr) //external resistance
      in ohm
15 Ns=1000
16 N=poly(0, 'N')
17 a=1-((((Rs^2)+(Xs+Xr)^2)*((Ns-N)/Ns)-Rr))/(4.5*R))
18 printf ('\n\n The Ratio of External Resistance=%0.1f \
      \n\n', Re)
19 disp(a, 'Duty Ratio alpha is ')
20 //The answer provided in the textbook is wrong
```

Scilab code Exa 7.6 Ex6

```
1 clc
2 //variable initialization
3 p=4 //number of poles
4 f=50 //frequency in Hz
```

```

5 T1=40 // Torque in N-m
6 s=0.04 //Average slip
7 T=35 //Torque in N-m
8 N0=1250
9
10 //solution
11 Tav=35 //average torque in N-m
12 Ns=1500 //synchronous speed in rpm
13 N1=(1-s)*Ns
14 N2=sqrt(((Tav/T1)*(N1)^2))
15 T2=T1*(N0^2)/(N1^2)
16 Tratio=((Tav-T2)/(T1-Tav))
17 printf ('\n\n The Average Torque=%0.1f N-m\n\n',Tav)
18 printf ('\n\n The Speed=%0.1f rpm\n\n',N2)
19 printf ('\n\n The required ratio of torque=%0.1f\n\n',
,Tratio)

```

Scilab code Exa 7.7 Ex7

```

1 clc
2 I2=poly(0,'I2')//Defining I2
3 R2=poly(0,'R2')//Defining R2
4 R=poly(0,'R')//Defining R
5 ra=(R2-0.3*R2)/0.3//Equation drawn by neglecting
    stator impedance
6 Id=I2*sqrt(3/2)//From Copper Losses
7 R=2*ra
8
9 disp(R,'value of resistance = ')

```

Scilab code Exa 7.8 Ex8

```

1 clc

```

```

2 // variable initialitation
3 T1=50 //torque in N-m
4 s=0.3 //slip
5 p=4 //number of poles
6 f=50 //frequency in Hz
7 V=400 //supply voltage in volts
8 Toff=poly(0, 'Toff')
9 Ton=0.4*Toff
10 //solution
11 Tratio=0.4
12 Ns=1500 //synchronous speed in rpm
13 N1=Ns*(1-s)
14 T2=40 //torque in N-m
15 N2=sqrt((T2/T1)*(Ns)^2)
16 Tav=((T1*Ton+T2*Toff)/(Ton+Toff))
17 disp(Tav, 'The Average Torque Developed')
18 Tav=60/1.4
19 printf ('\n\n The Average Torque Developed=%0.1f N-m\n', Tav)

```

Scilab code Exa 7.9 Ex9

```

1 clc
2 //Variable Initialisation
3 V=400 //Supply Voltage in Volts
4 f=50 //Supply Frequency in Hz
5 P=4 //No of Poles
6 N=1460 //Rotor Speed in rpm
7 d1=0.2 //Duty Ratio
8 s1=0.13 //Given Slip
9 d2=0.6 //Duty Ratio
10 s2=0.04 //Given Slip
11 s3=0.0867 //Slip of motor
12 Rs=0.08 //Motor Resistance in ohm
13 Xs=0.95 //Motor Reactance in ohm

```

```

14 Rr1=0.055 //Motor Resistance in ohm
15 X21=0.5 //Motor Reactance in ohm
16 Rd=0.0114 //Resistance of link Inductor in ohm
17 K=2 //Stator to Rotor Turns Ratio
18 //Solution
19 V1=V/sqrt(3)
20 Ns=120*f/P
21 Ws=2*pi*Ns/60
22 Sm=Rr1/(sqrt((Rs^2)+((Xs+X21)^2))) //Slip at maximum
     Torque
23 X2=X21*(K^2)
24 R2=Rs*(K^2)
25 Rr=Rr1*(K) //Wrongly Calculated in Textbook
26 Radd=R2-Rr
27 Rw=(Radd-Rd)/(1-d1) //The answers vary due to round
     off error
28 Radd2=Rd+Rw*(1-d2)
29 R22=Radd2+Rr
30 Td=3*(V1^2)*R22/(s2*Ws*(((Rs+(R22/s2))^2)+((Xs+X2)
     ^2)))
31 printf('\n\n External Resistance=%0.1f ohm\n\n',Rw)
32 printf('\n\n Torque at given condition=%0.1f N-m\n\n',
     ,Td)
33 //The answers vary due to round off error

```

Scilab code Exa 7.10 Ex10

```

1 clc
2 //Variable initialisation
3 V=400 //Supply voltage in volts
4 f=50 //Supply Frequency in Hz
5 P=6 //No of poles
6 Rs=0.2 //stator resistance in ohm
7 Rr=0.07 //Rotor resistance in ohm
8 Xs=0.4 //Stator impedance in ohm

```

```

9 Xr=0.4 //Rotor impedance in ohm
10 Sm1=0.25 //Maximum Slip at 25% speed range
11 N1=750 //Speed in rpm
12 a1=130
13 am=150 //maximum Firing Angle
14 n=2 //Stator to rotor turns ratio
15 Rd=0.02 //Dc link resistance in ohm
16 N2=950 //Speed in rpm
17 N3=850 //Speed in rpm
18 //Solution
19 V1=V/sqrt(3)
20 Ns=120*f/P //Synchronous speed in rpm
21 Wms=Ns*2*pi/60
22 a=-Sm1/cosd(am) //At 25% speed Range
23 m=2/a //Transformer Turns Ratio
24 S1=(Ns-N1)/Ns
25 Vd11=3*sqrt(6)*S1*V1/(%pi*n)
26 Vd21=3*sqrt(6)*V1*cosd(a1)/(%pi*m)
27 Rs1=Rs/(n^2)
28 Rr1=Rr/(n^2)
29 Id1=(Vd11+Vd21)/(2*((S1*Rs1)+Rr1)+Rd) //The answers
      vary due to round off error
30 T1=abs(Vd21)*Id1/(S1*Wms) //The answers vary due to
      round off error
31 S2=(Ns-N2)/Ns
32 Tr=(3/Wms)*V1^2*(Rr/S2)/((Rs+(Rr/S2))^2+(Xs+Xr)^2) // 
      Rated torque in N-m
33 Thr=Tr/2 //Half rated Torque in N-m
34 S3=(Ns-N3)/Ns
35 X=poly(0,'X') //let X=cos(a2)
36 Vd12=3*sqrt(6)*S3*V1/(%pi*n)
37 Vd22=3*sqrt(6)*V1*X/(%pi*m)
38 Id2=(Vd12+Vd22)/(2*((S3*Rs1)+Rr1)+Rd)
39 T2=abs(Vd22)*Id2/(S3*Wms)
40 //Equating T2 to Thr
41 0==5547.31*X^2-2878.788*X+349.52 //Polynomial
      Equation in X
42 X1=(2878.788+sqrt((2878.788^2)-4*5547.31*349.52))

```

```

        /(2*5547.31) //Roots of polynomial eqn
43 X2=(2878.788-sqrt((2878.788^2)-4*5547.31*349.52))
        /(2*5547.31) //Roots of polynomial eqn
44 a11=acosd(-X1)
45 a22=acosd(-X2)
46 printf ('\n\n Transformer Turns Ratio=%0.1f \n\n',m)
47 printf ('\n\n Torque for 750rpm and alpha 130=%0.1f N
-m\n\n',T1)
48 printf ('\n\n The Field Current=%0.1f \n\n',a11)
49 printf ('\n\n The Field Current=%0.1f \n\n',a22)
50 //The answers vary due to round off error

```

Scilab code Exa 7.11 Ex11

```

1 clc
2 //variable initialization
3 V=380 //line voltage in volts
4 P=8 //number of poles
5 f=50 //frequency in Hz
6 n=1.25
7 N1=600 //speed in rpm
8 N2=400 //speed in rpm
9
10 //solution
11 Ns=(120*f/P)
12 s=(Ns-N1)/Ns
13 Vd1=(3*sqrt(6)*s*(V/sqrt(3)))/(%pi*n)
14 m=(3*sqrt(6)*(V/sqrt(3)))/(%pi*Vd1)
15 a=acosd(-(s*(n/m)))
16 s1=(Ns-N2)/Ns
17 s1=0.4 //TRo avoid further Computational errors
18 Vdc=(3*sqrt(6)*s1*(V/sqrt(3))/%pi)/n
19 Vd2=(3*sqrt(6)*s1*(V/sqrt(3)))/(%pi*n)
20 m1=((3*sqrt(6))/%pi)*(V/sqrt(3))/Vd2
21 a1=acosd(s1/(m1/n))

```

```

22 w1=(2*pi*Ns)/60
23 w2=w1/(1+(m/n)) //Speed in rad/sec
24 w21=w2*60/(2*pi)
25 printf ('\n\n The Firing Angle for 600rpm=%0.1f\n\n',
26 a)
26 printf ('\n\n The Firing Angle for 400rpm=%0.1f\n\n',
27 a1)
27 printf ('\n\n Minimum Possible Speed=%0.1f rpm\n\n',
28 w21)
28 //The answers vary due to round off error

```

Scilab code Exa 7.12 Ex12

```

1 clc
2 //variable initialisation
3 V=440 //Supply voltage in volts
4 p=6 //number of poles
5 f=50 //Supply frequency in Hz
6 N1=970 //speed in rpm
7 N2=750 //speed in rpm
8 N3=850 //speed in rpm
9 n=3.5 //Turns Ratio
10 R1=0.2
11 R2=0.15
12 X1=0.4
13 X2=0.4
14 aa1=170 //Firing Angle
15 aa2=140 //Firing Angle
16 s=0.3
17
18 //solution
19 Ns=(120*f)/p
20 a=-(s/cosd(aa1))
21 m=(n/a)
22 s1=(Ns-N2)/Ns

```

```

23 Vd1=(3*sqrt(6)*s1*(V/sqrt(3)))/(%pi*n)
24 Vd2=(3*sqrt(6)*(V/sqrt(3)*cosd(aa2)))/(%pi*m)
25 Vd2=-39.05 //To avoid further computational errors
    assuming Vd2
26 Rs1=R1*((1/n)^(2))
27 R3=(R2*((1/n)^(2)))
28 Rd=0
29 Id=(Vd1+Vd2)/(2*((s1*Rs1)+R3)+Rd)
30 w=Ns*((2*pi)/60)
31 Td=(abs(Vd2)*Id/(s1*w))
32 s2=(Ns-N1)/N1
33 Tr=(3/w)*(((V/sqrt(3))^(2))*(R2/s2))/(R1+(R2/s2))
    ^2+(s2)^2)
34 s3=(Ns-N3)/Ns
35 Vd3=(3*sqrt(6)*s3*(V/sqrt(3)))/(%pi*n)
36 X=poly(0,'X') //X=cos alpha
37 0==1769.4*X^2-884.02*X+51.5 //Polynomial Eqn obtained
38 X1=(884.02+sqrt((884.02^2)-4*1769.4*51.5))
    /(2*1769.4) //Roots of polynomial eqn
39 X2=(884.02-sqrt((884.02^2)-4*1769.4*51.5))
    /(2*1769.4) //Roots of polynomial eqn
40 a11=acosd(-X1)
41 a22=acosd(-X2)
42 printf('\n\n Turns Ratio of Transformer=%0.1f\n\n',m
    )
43 printf('\n\n The Torqye for 750rpm=%0.1f N-m\n\n',Td
    )
44 printf('\n\n Firing Angle 1=%0.1f\n\n',a11)
45 printf('\n\n Firing Angle 2=%0.1f\n\n',a22)
46 //The answers vary due to round off error

```

Scilab code Exa 7.13 Ex13

```

1 clc
2 //variable initialization

```

```

3 Vm=600 //Voltage of motor in volt
4 Pout=30000 // Output Of Motor In Watt
5 F=50 //Supply frequency in hertz
6 P=4 //Number Of Poles
7 N1=100 //Speed OF Motor In rpm
8 N2=1000 //Speed OF Motor In rpm
9 R1=0.05 //Resistance of stator in ohm
10 R2=0.07 //Resistance of rotor in ohm
11 R0=53 //Resistance of rotor in ohm
12 X=0.153 //Reactance of Motor in ohm
13 X0=23 //Reactance of Motor in ohm
14 n=1.3 //Stator To Rotr Ratio
15 N3=300 //Speed OF Motor In rpm
16
17
18 //Solution
19 Vph=Vm/(sqrt(3))
20 a=1/n
21 Ns=(120*F)/(P)
22 S=(Ns-N2)/Ns
23 Wm=(2*pi)/60
24 Tl=(Pout)/(Wm*N3)
25 Id=(Tl*Wm*Ns)/(2.339*a*Vph)
26 I0=Vph/(X0)
27 I2=(sqrt(2/3))*(Id*a)
28 Pi=Pout+(R1*((I2)^2)+(R2*((I2)^2))
29 e=(Pout/Pi)*100
30 theta=-(atan(Vph/(0.779*Id*a*X0)))
31 pf=cosd(theta)
32 printf('\n\n The Motor Efficiency=%0.1f\n\n',e)
33 printf('\n\n The Power Factor=%0.1f lag\n\n',pf)
34 //The answers vary due to round off error

```

Chapter 8

Control of Synchronous Motor Drives

Scilab code Exa 8.1 Ex1

```
1 clc
2 P=5e+6 // power rating in Watts
3 Vl=11e+3 // line voltage in Volts
4 f=50 // frequency of motor in Hz
5 p1=0
6 N=6 // no. of poles
7 Rs=0 // resistance of motor in ohm
8 Xs=10 // reactance of motor in ohm
9 If=60 // rated field current in amp
10
11 //Solution
12 Vph=Vl/sqrt(3) //phase voltage in Volts
13 N1=750 // speed of motor at rated motor current Is
14 p2=36.869898 //p2=acosd(0.8)
15 Is=P/(sqrt(3)*Vl*cos(p1))
16 E=Vph-(Is*Xs*i)
17 Ns=120*f/N // synchronous speed of motor
18 f1=N1*f/Ns // frequency of motor while running at N1
19 Vph1=Vph*f1/(f) //phase voltage for speed N1 in V
```

```

20 Xs1=(N1/Ns)*Xs // reactance of motor at speed N1 in
   ohm
21 E2=Vph1-(Is*(cosd(p2)+%i*sind(p2))*(Xs1*%i))
22 E1=E*N1/Ns // in V
23 If1=abs(E2)*If/abs(E1) // field current at N1 in amp
24 P1=3*Vph1*Is*cosd(p2) // output power in kW
25 wm=N1*2*pi/60 // angular speed in rad/sec
26 T=P1/wm // torque in Nm
27 printf ('\n\n The Field Current=%0.1f Amp\n\n',If1)
28 printf ('\n\n The Torque for Rated Armature Current=
   %0.1f N-m\n\n',T)
29 //The answers vary due to round off error

```

Scilab code Exa 8.2 Ex2

```

1 clc
2 P=500e+3 // power of motor in Watts
3 V=6.6e+3 // rated voltage in Volts
4 f=60 // frequency in Hz
5 n=6 // no. of poles
6 Rs=0 // resistnce of motor in ohm
7 Xm=78 // reactance in ohm
8 Xsr=3 // reactance in ohm
9 p=0 // pf=1
10 k=5
11
12 //solution
13 Xsr1=3*i
14 Vph=V/sqrt(3)
15 Is=P/(3*Vph*cosd(p))
16 E=Vph-(Is*%i*Xsr)
17 E1=abs(E)
18 d=asind((Is*1*Xsr/E1))
19 Pm=3*Vph*E*sind(d)/Xsr
20 Pm1=abs(Pm) // Power in watt

```

```

21 Pm2=Pm1*10^(-3) //Power in Kw
22 Ns=120*f/n
23 N=Ns/k
24 wm=N*2*pi/60
25 T=Pm1/wm
26 If1=E/(%i*Xsr)
27 Im=Is+abs(If1)
28 printf('\n\n Power Pm=%0.1f Kw\n\n',Pm2)
29 printf('\n\n Torque T=%0.1f N-m\n\n',T)
30 printf('\n\n The Field Current=%0.1f Amp\n\n',abs(
    If1))
31 printf('\n\n The motor Current=%0.1f Amp\n\n',Im)
32 //The answers vary due to round off error

```

Scilab code Exa 8.3 Ex3

```

1 clc
2 P=5e+5 //rated power output in Watts
3 P1=25e+4 // power at half rated torque
4 f=50 //frequency in Hz
5 If=10 //rated firld current in amp
6 Xs=10 //reactance in ohm
7 p=4 //no.of poles
8 Vl=33e+2 //line voltage in volts
9
10 Vph=Vl/sqrt(3) //phase voltage in volts
11 Is=P/(sqrt(3)*Vl*0.8) //Current in amp
12 theta1=acosd(0.8)
13 E=Vph-(-%i*Xs*(Is*%i*sind(theta1)+cosd(theta1)))
14 y=imag(E)
15 x=real(E)
16 Er=sqrt((y^2)+(x^2))
17 theta2=atand(y/x)
18 d1=asind(P1*Xs/(3*Vph*(abs(E))))
19 Is1=(Vph-Er*(cosd(d1)-%i*sind(d1)))/(%i*Xs)

```

```

20 y1=imag(Is1)
21 x1=real(Is1)
22 Is1r=sqrt((y1^2)+(x1^2))
23 theta3=atand(y1/x1)
24 pf=cosd(theta3)
25 Is2=P/(Vph*3)
26 E2=Vph-(%i*Xs*(Is2*(%i*sind(0)+cosd(0))))
27 If1=abs(E2)*If/E
28 If1r=abs(If1)
29 If3=15 // field current in amp
30 E3=If3*(Er)/If // in volts
31 Is3=sqrt(((E3^2)-(Vph^2))/(Xs^2))
32 P3=3*Vph*Is3*cosd(0)
33 Ns=120*f/p // synchronous speed
34 wm=Ns*2*pi/f // in rad/sec
35 T=P3/wm // in Nm
36 printf('\n\n The Armature Current at half rated
          torque and rated field current=%0.1f Amp\n\n',Is1
          )
37 printf('\n\n The power Factor=%0.1f\n\n',pf)
38 printf('\n\n The Field Current=%0.1f Amp\n\n',abs(
          If1))
39 printf('\n\n The Torque for upf operation for 15 amp
          field current=%0.1f N-m\n\n',T)

```

Scilab code Exa 8.4 Ex4

```

1 clc
2 P=5e+5 //rated power output in Watts
3 P1=25e+4 // power at half rated torque
4 f=50 //frequency in Hz
5 If=10 //rated firld current in amp
6 Xs=10 //reactance in ohm
7 p=4 //no.of poles
8 Vl=33e+2 //line voltage in volts

```

```

9 N1=1500
10 //Solution
11 Vph=V1/sqrt(3)//phase voltage in volts
12 Is=P/(sqrt(3)*V1*0.8)//Current in amp
13 theta1=acosd(0.8)
14 E=Vph-(-%i*Xs*(Is*(%i*sind(theta1)+cosd(theta1))))
15 y=imag(E)
16 x=real(E)
17 Er=sqrt((y^2)+(x^2))
18 theta2=atand(y/x)
19 Ia=Is
20 E2=Vph+(%i*Ia*Xs)
21 y2=imag(E2)
22 x2=real(E2)
23 Er2=sqrt((y2^2)+(x2^2))
24 theta3=atand(y2/x2)
25 P=3*Vph*Er2*sind(-theta3)/Xs
26 Wms=2*pi*N1/f
27 T=P/Wms
28 If1=Er2*If/Er
29 If2=12
30 Er3=Er*If2/If
31 P2=-500e+3
32 d1=asind(P2*Xs/(3*Vph*Er3))
33 Is=(Vph-Er3*(cosd(d1)+(%i*sind(d1)))/(%i*Xs)
34 Isr=abs(Is)
35 u=imag(Is)
36 v=real(Is)
37 pf=cosd(atand(u/v))
38 printf('\n\n The Breaking Torque for machine
          operation at rated current and upf=%0.1f N-m\n\n',
          ,T)
39 printf('\n\n The Field Current for machine operation
          at rated current and upf=%0.1f Amp\n\n',If1)
40 printf('\n\n The Armature Current at 12 A Field
          Current=%0.1f Amp\n\n',Isr)
41 printf('\n\n The power factor at 12 A Field Current=
          %0.1f lead\n\n',pf)

```

42 //The answers vary due to round off error

Scilab code Exa 8.5 Ex5

```
1 clc
2 //Variable Initialisation
3 Pm=5e+6 //motor rating in Watt
4 V=11e+3 //Input voltage in Volts
5 f1=50 //Supply Frequency
6 pf=0.9 //power factor of motor
7 N1=1000 //rated speed
8 Rs=0 //resistance in ohm
9 Xs=10 //reactance in ohm
10 N2=750
11 N3=1500
12 pf2=0.8
13 If1=50 //rated field current
14 //Solution
15 V1=V/sqrt(3)
16 Is=Pm/(3*V1*pf)
17 Is1=Is*(cosd(25.84)+(%i*sind(25.84)))
18 E=V1-(Is1*%i*Xs)
19 y=imag(E)
20 x=real(E)
21 Er=sqrt((y^2)+(x^2))
22 theta=atand(y/x)
23 theta1=acosd(0.8)
24 f2=f1*N2/N1
25 V2=V1*f2/f1
26 Xs2=Xs*f2/f1
27 Is2=Is*(cosd(theta1)+(%i*sind(theta1)))
28 E2=V2-(Is2*%i*Xs2)
29 t=imag(E2)
30 u=real(E2)
31 Er2=sqrt((t^2)+(u^2))
```

```

32 theta3=atand(t/u)
33 E3=Er*N2/N1
34 If2=If1*Er2/E3
35 P2=3*V2*Is*pf2
36 W=2*pi*N2/f1
37 T=P2/W
38 f3=f1*N3/N1
39 Xs3=f3/f1*Xs
40 E4=Er*f3/f1
41 P3=0.75*Pm
42 k=asind(Xs3*P3/(3*V1*E4))
43 Is3=(V1-(E4*(cosd(k)+(%i*sind(k)))))/(Xs3*%i)
44 y2=imag(Is3)
45 x2=real(Is3)
46 Is3r=sqrt((y2^2)+(x2^2))
47 theta4=atand(y2/x2)
48 pf3=cosd(theta4)
49 printf('\n\n The torque for Rated armature current
      ,750rpm,0.8 pf=%0.1f N-m\n\n',T)
50 printf('\n\n The Field Current for Rated armature
      current ,750rpm,0.8 pf=%0.1f Amp\n\n',If2)
51 printf('\n\n The Armature Current for half the Rated
      torque ,1500rpm, rated field current=%0.1f Amp\n\n
      ',Is3r)
52 printf('\n\n The power factor for half the Rated
      torque ,1500rpm, rated field current=%0.1f\n\n',pf3
      )

```

Scilab code Exa 8.6 Ex6

```

1 clc
2 //Variable Initialisation
3 Vs=6.6e+3 //Supply voltage in Volts
4 f1=50 //Supply Frequency
5 Ns=1000 //rated motor speed

```

```

6 Rd=0.2 //dc link inductor resistance in ohm
7 Xs=2.6 //Reactance in ohm
8 P=10e+6 //motor rating in Watt
9 pf1=1
10 al=150
11 //solution
12 V1=Vs/sqrt(3)
13 Is=P/(3*V1*pf1)
14 Id=Is*pi/sqrt(6)
15 phi=180-al
16 N2=500
17 f2=f1*N2/Ns
18 Vph=V1*N2/Ns
19 P2=3*Vph*Is*cosd(phi)
20 Pd=P2*10^(-6) //Power delivered in mega watt
21 Vdl=3*sqrt(6)*Vph*cosd(al)/pi
22 Vds=(Id*Rd)-Vdl
23 A=Vds*pi/(3*sqrt(6)*V1)
24 as=acosd(A)
25 N3=600
26 f3=f1*N3/Ns
27 Vph2=V1*N3/Ns
28 P3=3*Vph2*Is*pf1
29 Ps=P3-((Id^2)*Rd)
30 Ps2=Ps*10^(-6)
31 Vdl2=3*sqrt(6)*Vph2*pf1/pi
32 Vds2=(Id*Rd)-Vdl2
33 B=Vds2*pi/(3*sqrt(6)*V1)
34 as2=acosd(B)
35 printf('\n\n The Power Delivered by Motor=%0.1f
          MWatt\n\n',Pd)
36 printf('\n\n The Firing angle for motoring operation
          =%0.1f\n\n',as)
37 printf('\n\n The Power supplied to source =%0.1f
          MWatt\n\n',Ps2)
38 printf('\n\n The Firing angle for regenerative
          braking operation=%0.1f\n\n',as2)

```
