

Scilab Textbook Companion for  
Electronics A Systems Approach  
by Neil Storey<sup>1</sup>

Created by  
Sufiyan Siddique  
BE  
Electronics Engineering  
Mumbai University  
College Teacher  
None  
Cross-Checked by  
None

November 26, 2017

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Electronics A Systems Approach

**Author:** Neil Storey

**Publisher:** Pearson Education Limited, UK

**Edition:** 4

**Year:** 2009

**ISBN:** 9780273719182

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 Basic Electrical Circuits and Components	5
2 Measurement of Voltages and Currents	11
3 Resistance and DC Circuits	15
4 Capacitance and Electric Fields	21
5 Inductance and Magnetic Fields	26
6 Alternating Voltages and Currents	31
7 Power in AC Circuits	38
8 Frequency Characteristics of AC Circuits	41
9 Transient Behaviour	49
13 Amplification	51
14 Control and Feedback	56
15 Operational Amplifiers	57

<b>16 Semiconductors and Diodes</b>	<b>60</b>
<b>17 Field effect Transistors</b>	<b>64</b>
<b>18 Bipolar Junction Transistors</b>	<b>70</b>
<b>19 Power Electronics</b>	<b>81</b>
<b>21 Noise and Electromagnetic Compatibility</b>	<b>83</b>
<b>23 Digital Systems</b>	<b>84</b>
<b>26 Implementing Digital Systems</b>	<b>91</b>

# List of Scilab Codes

Exa 1.1	Example 1 . . . . .	5
Exa 1.2	Example 2 . . . . .	6
Exa 1.3	Example 3 . . . . .	6
Exa 1.4	Example 4 . . . . .	7
Exa 1.5	Example 5 . . . . .	7
Exa 1.6	Example 6 . . . . .	8
Exa 1.7	Example 7 . . . . .	9
Exa 1.8	Example 8 . . . . .	9
Exa 1.9	Example 9 . . . . .	10
Exa 2.1	Example 1 . . . . .	11
Exa 2.2	Example 2 . . . . .	12
Exa 2.3	Example 3 . . . . .	12
Exa 2.4	Example 4 . . . . .	13
Exa 2.6	Example 6 . . . . .	13
Exa 3.1	Example 1 . . . . .	15
Exa 3.2	Example 2 . . . . .	15
Exa 3.3	Example 3 . . . . .	16
Exa 3.4	Example 4 . . . . .	17
Exa 3.5	Example 5 . . . . .	17
Exa 3.6	Example 6 . . . . .	18
Exa 3.7	Example 7 . . . . .	19
Exa 3.8	Example 8 . . . . .	20
Exa 4.1	Example 1 . . . . .	21
Exa 4.2	Example 2 . . . . .	21
Exa 4.3	Example 3 . . . . .	22
Exa 4.4	Example 4 . . . . .	23
Exa 4.5	Example 5 . . . . .	23
Exa 4.6	Example 6 . . . . .	24

Exa 4.7	Example 7 . . . . .	25
Exa 5.1	Example 1 . . . . .	26
Exa 5.2	Example 2 . . . . .	27
Exa 5.3	Example 3 . . . . .	27
Exa 5.4	Example 4 . . . . .	28
Exa 5.5	Example 5 . . . . .	29
Exa 5.6	Example 6 . . . . .	29
Exa 6.1	Example 1 . . . . .	31
Exa 6.2	Example 2 . . . . .	31
Exa 6.3	Example 3 . . . . .	32
Exa 6.4	Example 4 . . . . .	33
Exa 6.5	Example 5 . . . . .	33
Exa 6.6	Example 6 . . . . .	34
Exa 6.7	Example 7 . . . . .	35
Exa 6.8	Example 8 . . . . .	35
Exa 7.1	Example 1 . . . . .	38
Exa 7.2	Example 2 . . . . .	39
Exa 7.3	Example 3 . . . . .	39
Exa 8.1	Example 1 . . . . .	41
Exa 8.2	Example 2 . . . . .	42
Exa 8.3	Example 3 . . . . .	42
Exa 8.4	Example 4 . . . . .	43
Exa 8.5	Example 5 . . . . .	44
Exa 8.6	Example 6 . . . . .	45
Exa 8.7	Example 7 . . . . .	46
Exa 8.8	Example 8 . . . . .	47
Exa 8.9	Example 9 . . . . .	47
Exa 9.1	Example 1 . . . . .	49
Exa 9.2	Example 2 . . . . .	49
Exa 13.1	Example 1 . . . . .	51
Exa 13.2	Example 2 . . . . .	52
Exa 13.3	Example 3 . . . . .	52
Exa 13.4	Example 4 . . . . .	53
Exa 13.5	Example 5 . . . . .	54
Exa 13.6	Example 6 . . . . .	55
Exa 14.2	Example 2 . . . . .	56
Exa 15.4	Example 4 . . . . .	57
Exa 15.5	Example 5 . . . . .	57

Exa 15.6	Example 6 . . . . .	58
Exa 15.7	Example 7 . . . . .	59
Exa 16.1	Example 1 . . . . .	60
Exa 16.2	Example 2 . . . . .	60
Exa 16.3	Example 3 . . . . .	61
Exa 16.4	Example 4 . . . . .	62
Exa 16.5	Example 5 . . . . .	62
Exa 17.1	Example 1 . . . . .	64
Exa 17.2	Example 2 . . . . .	65
Exa 17.3	Example 3 . . . . .	65
Exa 17.4	Example 4 . . . . .	66
Exa 17.5	Example 5 . . . . .	67
Exa 17.6	Example 6 . . . . .	67
Exa 17.7	Example 7 . . . . .	68
Exa 18.1	Example 1 . . . . .	70
Exa 18.2	Example 2 . . . . .	71
Exa 18.3	Example 3 . . . . .	72
Exa 18.4	Example 4 . . . . .	73
Exa 18.6	Example 6 . . . . .	73
Exa 18.7	Example 7 . . . . .	74
Exa 18.8	Example 8 . . . . .	76
Exa 18.9	Example 9 . . . . .	77
Exa 18.10	Example 10 . . . . .	78
Exa 18.11	Example 11 . . . . .	79
Exa 19.1	Example 1 . . . . .	81
Exa 19.2	Example 2 . . . . .	81
Exa 21.1	Example 1 . . . . .	83
Exa 23.16	Example 16 . . . . .	84
Exa 23.17	Example 17 . . . . .	84
Exa 23.18	Example 18 . . . . .	85
Exa 23.19	Example 19 . . . . .	86
Exa 23.20	Example 20 . . . . .	87
Exa 23.21	Example 21 . . . . .	87
Exa 23.22	Example 22 . . . . .	88
Exa 23.23	Example 23 . . . . .	88
Exa 23.24	Example 24 . . . . .	89
Exa 26.1	Example 1 . . . . .	91
Exa 26.4	Example 4 . . . . .	91

# Chapter 1

## Basic Electrical Circuits and Components

Scilab code Exa 1.1 Example 1

```
1 //Chapter 1, Example 1.1
2
3 clc
4 //Initialisation
5 v1=15.8 //voltage
6 v2=12.3 //voltage
7 r=220 //
   resistance in ohm
8
9 //Calculation
10 v=v1-v2 //voltage
11 i=v/r //current in
   ampere
12
13 //Results
14 printf("Current , I = %.1 f mA" ,(i*1000))
```

---

### Scilab code Exa 1.2 Example 2

```
1 //Chapter 1, Example 1.2
2
3 clc
4 //Initialisation
5 i1=10 //current in
   ampere
6 i3=3 //current in
   ampere
7
8 //Calculation
9 i2=i1-i3 //current
   in ampere
10
11 //Results
12 printf("Current , I = %.1 f A",i2)
```

---

### Scilab code Exa 1.3 Example 3

```
1 //Chapter 1, Example 1.3
2
3 clc
4 //Initialisation
5 v2=7 //voltage
6 e=12 //emf
7
8 //Calculation
9 v1=e-v2 //voltage
10
11 //Results
12 printf("Voltage , V = %.1 f V",v1)
```

---

#### Scilab code Exa 1.4 Example 4

```
1 //Chapter 1, Example 1.4
2
3 clc
4 //Initialisation
5 r=50 //resistance
   in ohm
6 i=3 //current in
   ampere
7
8
9
10 //Calculation
11 p=i^2*r //Power in
   watts
12
13 //Results
14 printf("Power P = %.1 f Watt" ,p)
```

---

#### Scilab code Exa 1.5 Example 5

```
1 //Chapter 1, Example 1.5
2
3 clc
4 //Initialisation
5 r1=10 //
   resistance in ohm
6 r2=20 //
   resistance in ohm
7 r3=15 //
   resistance in ohm
8 r4=25 //
   resistance in ohm
9
```

```

10
11
12
13 // Calculation
14 r=r1+r2+r3+r4 //
    resistance in ohm
15
16
17 // Results
18 printf("Equivalent Resistance , R = %d Ohm" , r)

```

---

#### Scilab code Exa 1.6 Example 6

```

1 //Chapter 1, Example 1.6
2
3 clc
4 //Initialisation
5 r1=10 //
    resistance in ohm
6 r2=20 //
    resistance in ohm
7
8
9
10
11
12 // Calculation
13 r=(r1*r2)/(r1+r2) //resistance
    in ohm
14
15
16 // Results
17 printf("Equivalent Resistance , R = %.2 f Ohm" , r)

```

---

### Scilab code Exa 1.7 Example 7

```
1 //Chapter 1, Example 1.7
2
3 clc
4 //Initialisation
5 v1=10 //voltage
6 v2=0 //voltage
7 r1=200 //
   resistance in ohm
8 r2=300 //
   resistance in ohm
9
10
11 //Calculation
12 v=v1*(r2/(r1+r2)) //
   voltage
13
14
15 //Results
16 printf("Voltage , V = %d V" ,v)
```

---

### Scilab code Exa 1.8 Example 8

```
1 //Chapter 1, Example 1.8
2
3 clc
4 //Initialisation
5 v1=15 //voltage
6 v2=3 //voltage
7 r1=1000 //
   resistance in ohm
```

```

8 r2=500 //
   resistance in ohm
9
10
11 // Calculation
12 v=v2+((v1-v2)*(r2/(r1+r2))) // voltage
13
14
15 // Results
16 printf("Voltage , V = %d V" ,v)

```

---

#### Scilab code Exa 1.9 Example 9

```

1 //Chapter 1, Example 1.9
2
3 clc
4 //Initialisation
5 f=50 //Frequency in Hertz
6
7
8 // Calculation
9 t=1/f //Time Period in Sec
10
11
12 // Results
13 printf("Time Period , T = %d ms" ,(t*1000))

```

---

## Chapter 2

# Measurement of Voltages and Currents

Scilab code Exa 2.1 Example 1

```
1 //Chapter 2, Example 2.1
2 clc
3 //Initialisation
4 t=0.02 //time period in sec ,
   from graph
5 v1=7 //position peak voltage ,
   from graph
6 v2=7 //negative peak voltage ,
   from graph
7
8 //Calculation
9 f=1/t //frequency in hertz
10 vpp=v1+v2 //peak to peak voltage
11
12 //Result
13 printf("Period T = %.2f sec\n",t)
14 printf("Frequency F = %d Hz\n",f)
15 printf("Peak Voltage , Vp = %d V\n",v1)
16 printf("Peak to Peak Voltage , Vpp = %d V\n",vpp)
```

---

**Scilab code Exa 2.2 Example 2**

```
1 //Chapter 2, Example 2.2
2 clc
3 //Initialisation
4 t=50*10^-3 //time period in sec
   , from graph
5 v1=10 //position peak voltage
   , from graph
6 pi=3.14
7
8 //Calculation
9 f=1/t //frequency in hertz
10 w=2*pi*f //angular velocity
11
12 //Result
13 printf("Equation of Voltage signal is, \n")
14 printf("v = %d sin %d t",v1,round(w))
```

---

**Scilab code Exa 2.3 Example 3**

```
1 //Chapter 2, Example 2.3
2 clc
3 //Initialisation
4 vp=10 //voltage
5 f=10 //frequency in hertz
6 pi=3.14 //pi
7 phi=90 //phase angle
8
9 //Calculation
10 w=2*pi*f //angular frequency
```

```

11
12
13
14 //Results
15 printf("%d sin( %d t - %d)",vp,round(w),phi)

```

---

#### Scilab code Exa 2.4 Example 4

```

1 //Chapter 2, Example 2.4
2 clc
3 //Initialisation
4 v1=5 //voltage
5 v2=5 //voltage
6 r=10 //resistance in ohm
7
8
9
10 //Calculation
11 p1=v1^2/r //Power in watt when a
    constant 5 V applied
12 p2=v2^2/r //Power in watt when a sine
    wave of 5 V r.m.s is applied
13 p3=((v1^2)/2)/r //Power in watt when a sine
    wave of 5 V peak is applied
14
15 //Result
16 printf("(a) P = %.1 f W\n",p1)
17 printf("(b) Pav = %.1 f W\n",p2)
18 printf("(c) Pav = %.2 f W\n",p3)

```

---

#### Scilab code Exa 2.6 Example 6

```

1 //Chapter 2, Example 2.6

```

```

2  clc
3  //Initialisation
4  i2=1*10-3           //full scale deflection
    current in ampere
5  v=50                 //full scale deflection
    voltage
6  r=25                 //resistance in ohm
7
8  //Calculation
9  i3=1/i2             //reduction of the
    sensitivity of the meter
10 R=v/i2              //Resistance in ohm
11 rse=R-r             //Resistance in ohm
12
13 //Result
14 printf(" Series Resistance , Rse = %.3f Kohm\n",rse
    /1000)
15 printf(" \t\t\t\t %.1f Kohm",rse/1000)

```

---

# Chapter 3

## Resistance and DC Circuits

Scilab code Exa 3.1 Example 1

```
1 //Chapter 3, Example 3.1
2
3 clc
4 //Initialisation '
5 i1=8 //current in amp
6 i2=1 //current in amp
7 i3=4 //current in amp
8
9 //Calculation
10 i4=i3+i2-i1 //current in amp
11
12
13 //Results
14 printf("Current , I4 = %d A",i4)
```

---

Scilab code Exa 3.2 Example 2

```
1 //Chapter 3, Example 3.2
```

```

2
3 clc
4 //Initialisation '
5 v1=3 //voltage
6 v3=3 //voltage
7 e=12 //voltage
8
9 //Calculation
10 v2=v1+v3-e //voltage
11
12 //Results
13 printf(" Voltage , V = %d V" ,v2)

```

---

### Scilab code Exa 3.3 Example 3

```

1 //Chapter 3, Example 3.3
2 clc
3 //Initialisation
4 v1=30 //voltage
5 r1=10*10**3 //resistance in ohm
6 r2=10*10**3 //resistance in ohm
7 r3=10*10**3 //resistance in ohm
8
9 //Calculation
10 voc=v1/2 //open circuit voltage
11 r23=(r2*r3)/(r2+r3) //resistance in parallel
    in ohm
12 rt=r1+r23 //resistance in ohm
13 i1=v1/rt //current in ampere
14 isc=i1/2 //short circuit current
    in ampere
15 R=voc/isc //resistance in ohm
16
17
18 //Results

```

```

19 printf("For Thevenin Circuit \n")
20 printf("V = %d V\n",voc)
21 printf("R = %d kOhm\n\n",R/1000)
22 printf("For Norton Circuit \n")
23 printf("I = %d mA\n",isc*1000)
24 printf("R = %d kOhm",R/1000)

```

---

#### Scilab code Exa 3.4 Example 4

```

1 //Chapter 3, Example 3.4
2 clc
3
4 R1=25 //resistance in ohm
5 R2=400 //resistance in ohm
6
7 //To solve simultaneous equation by converting them
  into matrices form
8 a=[R1 -2;R2 -8]
9 b=[50;3200]
10 x=a\b
11
12 //Results
13 printf("Voc = %d V\n",x(1)) //display
  voltage Voc
14 printf("R = %d Ohm",x(2)) //display
  Resistance R

```

---

#### Scilab code Exa 3.5 Example 5

```

1 //Chapter 3, Example 3.5
2
3 clc
4 //Initialisation '

```

```

5 v1=15 //voltage
6 v2=20 //voltage
7 r1=100 //resistance in ohm
8 r2=200 //resistance in ohm
9 r3=50 //resistance in ohm
10
11 //Calculation
12 rp1=(r2*r3)/(r2+r3) //
    resistance in parallel in ohm
13 vp1=v1*(rp1/(r1+rp1)) //
    voltage V2
14 rp2=(r1*r3)/(r1+r3) //
    resistance in parallel in ohm
15 vp2=v2*(rp2/(r2+rp2)) //
    voltage V2
16 vp=vp1+vp2 // total voltage
17
18 //Results
19 printf("Voltage , V = %.2 f V" ,vp)

```

---

### Scilab code Exa 3.6 Example 6

```

1 //Chapter 3, Example 3.6
2
3 clc
4 //Initialisation '
5 v1=5 //voltage
6 i=2 //current in ampere
7 r1=10 //resistance in ohm
8 r2=5 //resistance in ohm
9
10 //Calculation
11 i1=v1/(r1+r2) //current
    in ampere
12 r=(r1*r2)/(r1+r2) //resistance

```

```

    in ohm
13 v=i*r           //voltage
14 i2=v/r2        //current in
    ampere
15 i3=i1+i2       //current in
    ampere
16
17 //Results
18 printf("Current , I = %.2 f A" ,i3)

```

---

### Scilab code Exa 3.7 Example 7

```

1 //Chapter 3, Example 3.7
2 clc
3 //Initialisation
4 v1=50           //voltage
5 v2=15           //voltage
6 v3=100         //voltage
7 r1=10           //resistance in ohm
8 r2=20           //resistance in ohm
9 r3=30           //resistance in ohm
10 r4=25          //resistance in ohm
11
12 //Calculation
13 //by making a two linear equations , and solving them
    by matrix method
14 a=[(-13/60) (1/20);(1/60) (-9/100)]
15 b=[-5;(-100/30)]
16 x=a\b
17 I1=x(2)/25     //current in ampere
18
19 //Results
20 printf("Current , I1 = %.1 f A" ,I1)

```

---

### Scilab code Exa 3.8 Example 8

```
1 //Chapter 3, Example 3.8
2 clc
3 Re=10 //resistance in ohm
4 //To solve simulataneous equation by converting them
   into matrices form
5 a=[-160 20 30;20 -210 10;30 10 -190]
6 b=[-50;0; 0]
7 x=a\b
8 Ve=Re*(x(3)-x(2)) //voltage
9
10 //Results
11 printf(" I1 = %.2 f mA\n",x(1)*1000)
12 printf(" I2 = %.2 f mA\n",x(2)*1000)
13 printf(" I3 = %.2 f mA\n",x(3)*1000)
14 printf(" Voltage , VE = %.2 f V\n",Ve)
```

---

# Chapter 4

## Capacitance and Electric Fields

Scilab code Exa 4.1 Example 1

```
1 //Chapter 4, Example 4.1
2
3 clc
4 //Initialisation '
5 c=10^-5 //capacitance in farad
6 v=10 //voltage
7
8
9 //Calculation
10 q=c*v //charge in coulombs
11
12
13
14 //Results
15 printf(" Charge , Q = %d uC" ,(q*10^6))
```

---

Scilab code Exa 4.2 Example 2

```

1 //Chapter 4, Example 4.2
2
3 clc
4 //Initialisation
5 eo=8.85*10-12 //dielectric constant
6 er=100 //relative permittivity
7 a=10*10-3*25*10-3 //area in metre
8 d=7*10-6 //distance between plates
9
10
11
12
13 //Calculation
14 c=(eo*er*a)/d //capacitance in
    farad
15
16
17
18 //Results
19 printf("Capacitance , C = %.1f nF",c*109)

```

---

### Scilab code Exa 4.3 Example 3

```

1 //Chapter 4, Example 4.3
2
3 clc
4 //Initialisation
5 v=100 //voltage
6 d=10-5 //distance between plates
7
8
9
10
11 //Calculation
12 e=v/d //capacitance in farad

```

```
13
14
15
16 //Results
17 printf("Electric Field Strength , E = %d ^ 7 V/m",e
        *10^-6)
```

---

#### Scilab code Exa 4.4 Example 4

```
1 //Chapter 4, Example 4.4
2
3 clc
4 //Initialisation
5 q=15*10**-6 //charge in coulomb
6 a=200*10**-6 //area in meter
7
8
9 //Calculation
10 d=q/a //electric flux density
11
12
13
14 //Results
15 printf("Electric Flux Density , D = %d mC/m^2",d
        *10**3)
```

---

#### Scilab code Exa 4.5 Example 5

```
1 //Chapter 4, Example 4.5
2
3 clc
4 //Initialisation '
```

```

5  c1=10*10**-6                                //capacitance in
    farad
6  c2=25*10**-6                                //capacitance in
    farad
7
8
9  //Calculation
10 c=c1+c2                                     //capacitance in farad
11
12
13
14 //Results
15 printf("Total Capacitance , C = %d uF",c*10**6)

```

---

#### Scilab code Exa 4.6 Example 6

```

1  //Chapter 4, Example 4.6
2
3  clc
4  //Initialisation '
5  c1=10*10**-6                                //capacitance in
    farad
6  c2=25*10**-6                                //capacitance in
    farad
7
8
9  //Calculation
10 c=(c1*c2)/(c1+c2)                          //equivalent
    parallel capacitance in farad
11
12
13
14 //Results
15 printf("Total Capacitance , C = %.2 f uF",c*10**6)

```

---

Scilab code Exa 4.7 Example 7

```
1 //Chapter 4, Example 4.7
2
3 clc
4 //Initialisation
5 c=10**-5 //capacitance in farad
6 v=100 //voltage
7
8
9 //Calculation
10 e=(1/2)*c*v**2 //energy stored
11
12
13
14 //Results
15 printf("Energy Stored , C = %d mJ",e*10**3)
```

---

# Chapter 5

## Inductance and Magnetic Fields

Scilab code Exa 5.1 Example 1

```
1 //Chapter 5, Example 5.1
2
3 clc
4 //Initialisation '
5 i=5 //current in amp
6 r=100*10**-3 //radius in meter
7 pi=3.14 //pi
8
9 //Calculation
10 l=2*pi*r //circumference
11 h=i/l //magnetic field
    strength
12
13
14
15 //Results
16 printf("Magnetic field strength , H = %.2f A/m",h)
```

---

### Scilab code Exa 5.2 Example 2

```
1 //Chapter 5, Example 5.2
2
3 clc
4 //Initialisation '
5 i=6 //current in amp
6 n=500 //no of turns
7 l=0.4 //mean
   circumference
8 pi=3.14 //pi
9 uo=4*pi*10**-7 //dielectric
   constant
10 a=300*10**-6 //area
11
12 //Calculation
13 f=i*n //force
14 h=f/l //magnetic field
   strength
15 B=uo*h //magnetic induction
16 phi=B*a //total flux
17
18 //Results
19 printf("(a) Force F = %d ampere-turns\n",f)
20 printf("(b) Magnetic Field Strength, H = %d A/m\n",h
   )
21 printf("(c) Magnetic Induction, B = %.2 f mT\n",B
   *10**3)
22 printf("(d) Total Flux, phi = %.2 f uWb\n",phi*10**6)
```

---

### Scilab code Exa 5.3 Example 3

```

1 //Chapter 5, Example 5.3
2
3 clc
4 //Initialisation '
5 di=3 //change in current w.r.t
      time
6 l=10*10**-3 //inductance in henry
7
8 //Calculation
9 v=l*di //voltage induced
10
11 //Results
12 printf("Voltage Induced V = %d mV",v*10**3)

```

---

#### Scilab code Exa 5.4 Example 4

```

1 //Chapter 5, Example 5.4
2
3 clc
4 //Initialisation '
5 n=400 //no of turns
6 l=200*10**-3 //mean circumference
7 pi=3.14 //pi
8 uo=4*pi*10**-7 //dielectric
      constant
9 a=30*10**-6 //area
10
11 //Calculation
12 L=(uo*a*n**2)/l //inductance
13
14 //Results
15 printf("Inductance L = %d uH",L*10**6)

```

---

### Scilab code Exa 5.5 Example 5

```
1 //Chapter 5, Example 5.5
2
3 clc
4 //Initialisation '
5 L1=10 //inductance
6 L2=20 //inductance
7
8
9 //Calculation
10 Ls=L1+L2 //inductance
    in series
11 Lp=(L1*L2)/(L1+L2) //inductance in
    parallel
12
13 //Results
14 printf("(a) Inductance in Series Ls = %d H\n",Ls)
15 printf("(b) Inductance in Parallel Lp = %.2 f H\n",Lp
    )
```

---

### Scilab code Exa 5.6 Example 6

```
1 //Chapter 5, Example 5.6
2
3 clc
4 //Initialisation '
5 L=10**-2 //inductance
6 I=5 //current in ampere
7
8
9 //Calculation
10 e=(1/2)*L*I**2 //stored energy
11
12 //Results
```

```
13 printf("Stored Energy = %d mJ", e*10**3)
```

---

# Chapter 6

## Alternating Voltages and Currents

Scilab code Exa 6.1 Example 1

```
1 //Chapter 6, Example 6.1
2 clc
3 //Initialisation
4 w=1000 //angular frequency
5 L=10**-3 //inudctance in henry
6
7
8 //Calculation
9 Xl=w*L //reactance in ohm
10
11 //Results
12 printf(" Reactance , Xl = %d Ohm" ,Xl)
```

---

Scilab code Exa 6.2 Example 2

```
1 //Chapter 6, Example 6.2
```

```

2  clc
3  //Initialisation
4  pi=3.14                               //pi
5  f=50                                  //frequency in hertz
6  C=2*10**-6                            //capacitance in farad
7
8
9  //Calculation
10 w=2*pi*f                               //angular frequency
11 Xc=1/(w*C)                             //Capacitive
    Reactance
12
13 //Results
14 printf("Reactance , Xc = %.2 f KOhm" ,Xc/1000)

```

---

### Scilab code Exa 6.3 Example 3

```

1  //Chapter 6, Example 6.3
2  clc
3  //Initialisation
4  pi=3.14                               //pi
5  f=100                                  //frequency in hertz
6  L=25*10**-3                            //inductance in henry
7  v1=5                                    //peak voltage
8
9  //Calculation
10 w=2*pi*f                               //angular frequency
11 Xl=w*L                                  //inductive reactance
12 il=v1/Xl                               //peak current
13
14 //Results
15 printf("Peak Current , IL = %d mA" ,il*1000)

```

---

#### Scilab code Exa 6.4 Example 4

```
1 //Chapter 6, Example 6.4
2 clc
3 //Initialisation
4 w=25 //angular frequency
5 C=10*10**-3 //capacitance in
   farad
6 Ic=2 //current in ampere
7
8 //Calculation
9
10 Xc=1/(w*C) //Capacitive
   Reactance
11 Vc=Ic*Xc //voltage across
   capacitor
12
13 //Results
14 printf("Voltage , V = %d V r.m.s",Vc)
```

---

#### Scilab code Exa 6.5 Example 5

```
1 //Chapter 6, Example 6.5
2 clc
3 //Initialisation
4 pi=3.14 //pi
5 f=50 //frequency in hertz
6 i=5 //current in ampere
7 r=10 //resistance in ohm
8 L=25*10**-3 //inductance in henry
9 VL=39.3 //from phasor diagram
10 VR=50 //from phasor diagram
11
12
13 //Calculation
```

```

14 Vr=i*r                                //voltage across
    resistor
15 w=2*pi*f                              //angular frequency
16 Xl=w*L                                 //inductive reactance
17 Vl=i*Xl                                //voltage across
    inductor
18 V=sqrt(VR**2+VL**2)                   //voltage
19 phi=atan(VL/VR)                       //phase angle
20
21 //Results
22 printf("Voltage , V = %.1f V\n",V)
23 printf("Phase Angle , phi = %.1f Degree",phi*180/pi)

```

---

#### Scilab code Exa 6.6 Example 6

```

1 //Chapter 6, Example 6.6
2 clc
3 //Initialisation
4 C=3*10**-8                              //capacitance in
    farad
5 pi=3.14                                  //pi
6 f=10**3                                  //frequency in
    hertz
7 V=10                                     //voltage
8 R=10**4                                  //resistance in ohm
9 i=5                                       //current in ampere
10 r=10                                    //resistance in ohm
11 L=25*10**-3                             //inductance in henry
12 VL=39.3                                 //from phasor diagram
13 VR=50                                    //from phasor diagram
14
15
16 //Calculation
17 w=2*pi*f                                //angular frequency
18 Xc=1/(w*C)                              //capacitive

```

```

    reactance in ohm
19 I=sqrt((V**2)/(R**2+Xc**2)) //current in ampere
20 phi=atan(Xc/R) //phase angle
21
22 //Results
23 printf("Current, I = %d uA\n",I*10**6)
24 printf("Phase Angle, phi = %.2f Degree",phi*180/pi)
    //wrong answer in textbook

```

---

#### Scilab code Exa 6.7 Example 7

```

1 //Chapter 6, Example 6.7
2 clc
3 //Initialisation
4 pi=3.14 //pi
5 f=50 //frequency in hertz
6 L=400*10**-3 //inductance in henry
7 C=50*10**-6 //capacitance in farad
8 R=200 //resistance in ohm
9
10 //Calculation
11 w=2*pi*f //angular frequency
12 Xl=w*L //inductive reactance
13 Xc=1/(w*C) //Capacitive
    Reactance
14 X=Xl-Xc //Complex part
15
16 //Results
17 printf("Complex Impedance = %d + j %d Ohm",R, round(
    X))

```

---

#### Scilab code Exa 6.8 Example 8

```

1 //Chapter 6, Example 6.8
2 clc
3 funcprot(0)
4 //Initialisation
5 C=200*10**-6 //capacitance in
   farad
6 R1=5 //resistance in ohm
7 R2=50 //resistance in ohm
8 L=50*10**-3 //inductance in henry
9 pi=3.14 //pi
10 w=500 //angular frequency
11 v=10 //voltage
12
13 //Calculation
14 Z1=R1-(%i*(1/(w*C))) //impedance in
   complex form
15 Z2=((R2*w**2*L**2)+( %i*R2**2*w*L))/(R2**2+(w**2*L
   **2)) //
   impedance in complex form
16 Z=Z2/(Z1+Z2) //
   impedance in complex form
17 V0=v*Z
18
19
20 function [r,th]=rect2pol(x,y)
21 //rectangle to polar coordinate conversion
22 //based on "Scilab from a Matlab User's Point of
   View", Eike Rietsch,
23 2002
24 r=sqrt(x^2+y^2);
25 th = atan(y,x)*180/%pi;
26 endfunction
27
28 [r,th]=rect2pol(real(V0),imag(V0))
   //calling a function
29
30 //Results

```

```
31 printf("v0 = %.1f sin( %d t + %.1f )",r,w,th)
```

---

# Chapter 7

## Power in AC Circuits

Scilab code Exa 7.1 Example 1

```
1 //Chapter 7, Example 7.1
2
3 clc
4 //Initialisation '
5 v=50 //voltage
6 i=5 //current
7 phi=30 //angle in
   degree
8 pi=3.14 //pi
9
10 //Calculation
11 s=v*i //apparent
   power
12 p=cos(phi*3.14/180) //
   power factor
13 ap=s*p //active
   power
14
15 //Results
16 printf("(a) Apparent Power, S = %d VA\n",s)
17 printf("(b) Power Factor = %.3f Degree\n",p)
```

```

18 printf("(c) Active Power, P = %.1f W\n", ap)
    //wrong answer in textbook
    //wrong answer in textbook

```

---

### Scilab code Exa 7.2 Example 2

```

1 //Chapter 7, Example 7.2
2
3 clc
4 //Initialisation
5 s=2000 //apparent
    power
6 p=0.75 //power factor
7 v=240 //voltage
8 //Calculation
9
10 ap=s*p //active
    power
11 phi=sqrt(1-(p**2)) //phase
    angle in radians
12 q=s*phi //reactive power
    in var
13 i=s/v //current in
    ampere
14
15
16 //Results
17 printf("(a) Apparent Power, S = %d VA\n", s)
18 printf("(b) Active Power, P = %d W\n", ap)
19 printf("(c) Reactive Power, Q = %d var\n", q)
20 printf("(d) Current, I = %.2f A\n", i)

```

---

### Scilab code Exa 7.3 Example 3

```

1 //Chapter 7, Example 7.3
2
3 clc
4 //Initialisation
5 s=2000 //apparent
   power
6 p=0.75 //power factor
7 v=240 //voltage
8 pi=3.14 //pi
9 f=50 //frequency
10
11 //Calculation
12
13 ap=s*p //active
   power
14 phi=sqrt(1-(p**2)) //phase
   angle in radians
15 q=s*phi //reactive power
   in var
16 i=s/v //current in
   ampere
17 xc=-v**2/q //capacitive
   reactance in ohm
18 c=1/(xc*2*pi*f) //
   capacitance in farad
19 s1=ap //new
   apparent power
20 i2=s1/v //new
   current in ampere
21
22 //Results
23 printf("(a) Apparent Power, S = %d VA\n",s1)
24 printf("(b) Active Power, P = %d W\n",ap)
25 printf("(c) Reactive Power, Q = %d var\n",q)
26 printf("(d) Current, I = %.2f A\n",i2)

```

---

# Chapter 8

## Frequency Characteristics of AC Circuits

Scilab code Exa 8.1 Example 1

```
1 //Chapter 8, Example 8.1
2 clc
3 //Initialisation
4 vi=10 //input voltage
5 vo=3 //output voltage
6 ii=2*10**-3 //input current in
    ampere
7 io=5*10**-3 //output current in
    ampere
8
9 //Calculation
10 av=vo/vi //voltage gain
11 ai=io/ii //current gain
12 ap=(vo*io)/(vi*ii) //power gain
13
14 //Result
15 printf("Voltage Gain, Av = %.1 f\n",av)
16 printf("Current Gain, Ai = %.1 f\n",ai)
17 printf("Power Gain, Ap = %.2 f\n",ap)
```

---

**Scilab code Exa 8.2 Example 2**

```
1 //Chapter 8, Example 8.2
2 clc
3 //Initialisation
4 p=2500 //power gain
5
6 //Calculation
7 pdb=10*log10(p) //power gain
8 //Result
9 printf("Power Gain (dB) = %.1f dB\n",pdb)
```

---

**Scilab code Exa 8.3 Example 3**

```
1 //Chapter 8, Example 8.3
2 clc
3 funcprot()
4 //Initialisation
5 p1=5 //power gain
6 p2=50 //power gain
7 p3=500 //power gain
8 v1=5 //voltage gain
9 v2=50 //voltage gain
10 v3=500 //voltage gain
11
12
13 //initialising a function for gain in dB
14 function [x]=pgain(a)
15     x=10*log10(a)
16 endfunction
17
```

```

18 function [x]=vgain(a)
19     x=20*log10(a)
20 endfunction
21
22 //calling a functions
23 [pd1]=pgain(p1)
24 [pd2]=pgain(p2)
25 [pd3]=pgain(p3)
26 [vd1]=vgain(v1)
27 [vd2]=vgain(v2)
28 [vd3]=vgain(v3)
29
30 //Result
31 printf("Power Gain (dB) of 5 = %.1 f dB\n",pd1)
32 printf("Power Gain (dB) of 50 = %.1 f dB\n",pd2)
33 printf("Power Gain (dB) of 500 = %.1 f dB\n",pd3)
34 printf("Voltage Gain (dB) of 5 = %.1 f dB\n",vd1)
35 printf("Voltage Gain (dB) of 50 = %.1 f dB\n",vd2)
36 printf("Voltage Gain (dB) of 500 = %.1 f dB\n",vd3)

```

---

#### Scilab code Exa 8.4 Example 4

```

1 //Chapter 8, Example 8.4
2 funcprot()
3 clc
4 //Initialisation
5 p1=20 //gain
6 p2=30 //gain
7 p3=40 //gain
8
9
10
11 //initialising a function for gain
12 function [x]=pgain(a) //function for
    power gain

```

```

13     x=10**(a/10)
14 endfunction
15
16 function [x]=vgain(a)           //function for
    voltage gain
17     x=10**(a/20)
18 endfunction
19
20 //calling a functions
21 [pd1]=pgain(p1)
22 [pd2]=pgain(p2)
23 [pd3]=pgain(p3)
24 [vd1]=vgain(p1)
25 [vd2]=vgain(p2)
26 [vd3]=vgain(p3)
27
28 //Result
29 printf("Power Gain (dB) of 20 = %.1 f dB\n",pd1)
30 printf("Voltage Gain (dB) of 30 = %.1 f dB\n\n",vd1)
31 printf("Power Gain (dB) of 40 = %.1 f dB\n",pd2)
32 printf("Voltage Gain (dB) of 20 = %.1 f dB\n\n",vd2)
33 printf("Power Gain (dB) of 30 = %.1 f dB\n",pd3)
34 printf("Voltage Gain (dB) of 40 = %.1 f dB\n",vd3)

```

---

#### Scilab code Exa 8.5 Example 5

```

1 //Chapter 8, Example 8.5
2 clc
3 //Initialisation
4 c=10*10**-6           //capacitance in
    farad
5 r=10**3              //resistance in ohm
6 pi=3.14              //pi
7
8 //Calculation

```

```

9  t=c*r           //time constant
10 wc=1/t         //angular frequency
11 f=wc/(2*pi)    //cyclic frequency
12
13 //Result
14 printf("Time Constant , T = %.2 f s\n",t)
15 printf("Angular Cut-off Frequency , F = %d rad/s \n",
        wc)
16 printf("Cyclic Cut-off Frequency , Fc = %.1 f Hz\n",f)

```

---

#### Scilab code Exa 8.6 Example 6

```

1 //Chapter 8, Example 8.6
2 clc
3 //Initialisation
4 f1=1000           //frequency in hertz
5 f2=10            //frequency in hertz
6 f3=100          //frequency in hertz
7 f4=20           //frequency in hertz
8 f5=10**6        //frequency in hertz
9 f6=50           //frequency in hertz
10
11 //Calculation
12 f11=f1*2        //an octave above 1
        kHz
13 f22=f2*2*2*2   //three octaves
        above 10 Hz
14 f33=f3/2       //an octave below
        100 Hz
15 f44=f4*10      //a decade above 20
        Hz
16 f55=f5/10/10/10 //three decades
        below 1 MHz
17 f66=f6*10*10   //two decades above
        50 Hz

```

```

18
19
20 //Result
21 printf("(a) an octave above 1 kHz = %d kHz \n",f11
    /1000)
22 printf("(b) three octaves above 10 Hz = %d Hz \n",
    f22)
23 printf("(c) an octave below 100 Hz = %d Hz \n",f33)
24 printf("(d) a decade above 20 Hz = %d Hz \n",f44)
25 printf("(e) three decades below 1 MHz = %d kHz \n",
    f55/1000)
26 printf("(f) two decades above 50 Hz = %d kHz \n",f66
    )

```

---

#### Scilab code Exa 8.7 Example 7

```

1 //Chapter 8, Example 8.7
2 clc
3 //Initialisation
4 c=10*10**-6 //capacitance in
    farad
5 r=10**3 //resistance in ohm
6 pi=3.14 //pi
7
8 //Calculation
9 t=c*r //time constant
10 wc=1/t //angular frequency
11 f=wc/(2*pi) //cyclic frequency
12
13 //Result
14 printf("Time Constant, T = %.2 f s\n",t)
15 printf("Angular Cut-off Frequency, F = %d rad/s \n",
    wc)
16 printf("Cyclic Cut-off Frequency, Fc = %.1 f Hz\n",f)

```

---

### Scilab code Exa 8.8 Example 8

```
1 //Chapter 8, Example 8.8
2 clc
3 //Initialisation
4 l=10*10**-3 //inductance in
   henry
5 r=100 //resistance in ohm
6 pi=3.14 //pi
7
8 //Calculation
9 t=l/r //time constant
10 wc=1/t //angular frequency
11 f=wc/(2*pi) //cyclic frequency
12
13 //Result
14 printf("Time Constant, T = %d ^-4 s\n",t*10**5)
15 printf("Angular Cut-off Frequency, F = %d ^4 rad/s \
   n",wc/10**3)
16 printf("Cyclic Cut-off Frequency, Fc = %.2 f kHz\n",f
   /1000)
```

---

### Scilab code Exa 8.9 Example 9

```
1 //Chapter 8, Example 8.9
2 clc
3 //Initialisation
4 l=15*10**-3 //inductance in
   henry
5 c=30*10**-6 //capacitance in
   farad
6 r=5 //resistance in ohm
```

```
7 pi=3.14 //pi
8
9 // Calculation
10 fo=1/(2*pi*sqrt(1*c)) //Resonant Frequency
11 q=(1/r)*sqrt(1/c) //Quality Factor
12 b=r/(2*pi*1) //Bandwidth
13
14 //Result
15 printf("Resonant Frequency, Fo = %d Hz \n",fo)
16 printf("Quality Factor, Q = %.2f\n",q)
17 printf("Bandwidth, B = %d Hz\n",b)
```

---

# Chapter 9

## Transient Behaviour

Scilab code Exa 9.1 Example 1

```
1 //Chapter 9, Example 9.1
2
3 clc
4 //Initialisation '
5 C=100*10**3           //capacitance in farad
6 R=100*10**-6         //resistance in
   ohm
7 t=25                 //time in
   seconds
8 V=20                 //voltage
9 //Calculation
10 T=C*R               //time constant in
   sec
11 v=V*(1-exp(-t/T))   //output voltage
12
13 //Results
14 printf("Output Voltage = %.2 f V",v)
```

---

Scilab code Exa 9.2 Example 2

```

1 //Chapter 9, Example 9.2
2 clc
3 //Initialisation
4 L=400*10**-3 //inductance in henry
5 R=20 //resistance in ohm
6 V=15 //voltage
7 i=300*10**-3 //current in amp
8 e=2.7183 //exponent
9
10 //Calculation
11 T=L/R //time constant in
    sec
12 I=V/R //current in amp
    from Ohms Law
13 t=(log10(I/(I-i))/log10(e))*T //time period
14
15
16
17 //Results
18 printf("t = %.1 f ms",t*1000)

```

---

# Chapter 13

## Amplification

Scilab code Exa 13.1 Example 1

```
1 //Chapter 13, Example 13.1
2
3 clc
4 //Initialisation '
5 ri=10**3 //resistance in ohm
6 rs=100 //resistance in ohm
7 rl=50 //resistance in
   ohm
8 ro=10 //resistance
   in ohm
9 vs=2 //voltage
10 ao=10 //output gain
11
12 //Calculation
13 vi=(ri/(rs+ri))*vs //input
   voltage
14 vo=ao*vi*(rl/(ro+rl)) //output
   voltage
15
16
17 //Results
```

```
18 printf("Output Voltage = %.2 f V" ,vo)
```

---

### Scilab code Exa 13.2 Example 2

```
1 //Chapter 13, Example 13.2
2
3 clc
4 //Initialisation '
5 ri=10**3 //resistance in ohm
6 rs=100 //resistance in ohm
7 rl=50 //resistance in
   ohm
8 ro=10 //resistance
   in ohm
9 vs=2 //voltage
10 ao=10 //output gain
11
12 //Calculation
13 vi=(ri/(rs+ri))*vs //input
   voltage
14 vo=ao*vi*(rl/(ro+rl)) //output
   voltage
15 av=vo/vi //voltage
   gain
16
17 //Results
18 printf("Voltage Gain Av = %.2 f" ,av)
```

---

### Scilab code Exa 13.3 Example 3

```
1 //Chapter 13, Example 13.3
2
3 clc
```

```

4 //Initialisation '
5 r1=50 //resistance in
    ohm
6 ro=0 //resistance
    in ohm
7 vs=2 //voltage
8 ao=10 //output gain
9
10 //Calculation
11 vi=vs //input voltage
12 vo=ao*vi*(r1/(ro+r1)) //output
    voltage
13
14
15 //Results
16 printf("Output Voltage = %.2f V",vo)

```

---

#### Scilab code Exa 13.4 Example 4

```

1 //Chapter 13, Example 13.1
2
3 clc
4 //Initialisation '
5 ri=10**3 //resistance in ohm
6 rs=100 //resistance in ohm
7 r1=50 //resistance in
    ohm
8 ro=10 //resistance
    in ohm
9 vs=2 //voltage
10 ao=10 //output gain
11
12 //Calculation
13 vi=(ri/(rs+ri))*vs //input
    voltage

```

```

14 vo=ao*vi*(r1/(ro+r1))           //output
    voltage
15 po=vo**2/r1                     //output
    power in watt
16
17 //Results
18 printf("Output Power = %.1f W",po)

```

---

### Scilab code Exa 13.5 Example 5

```

1 //Chapter 13, Example 13.5
2
3 clc
4 //Initialisation
5 ri=1000                          //resistance in ohm
6 r1=50                             //resistance in
    ohm
7 vi=1.82                          //input voltage
8 vo=15.2                          //output voltage
9
10
11
12 //Calculation
13
14 po=vo**2/r1                      //output
    power in watt
15 pi=vi**2/ri                     //input power
    in watt
16 ap1=po/pi                       //power gain
17
18 //Results
19 printf("Power Gain , Ap = %d",ap1)

```

---

### Scilab code Exa 13.6 Example 6

```
1 //Chapter 13, Example 13.6
2
3 clc
4 //Initialisation '
5 p=1400 //power gain
6
7 //Calculation
8 pdb=10*log10(p) //power gain
   in dB
9
10 //Results
11 printf("Power Gain (dB) = %.1 f dB",pdb)
```

---

# Chapter 14

## Control and Feedback

Scilab code Exa 14.2 Example 2

```
1 //Chapter 14, Example 14.2
2 clc
3 //Initialisation
4 A1=100000 //gain of an amplifier A
5 B=0.0001 //gain of an amplifier B
6 A2=200000 //gain of an amplifier A
7
8 //Calculation
9 G1=A1/(1+(A1*B)) //overall gain
10 G2=A2/(1+(A2*B)) //overall gain
11
12
13 //Results
14 printf("if gain of the amplifier A = 100,000\n")
15 printf("G = %d\n\n",G1)
16 printf("if gain of the amplifier A = 200,000\n")
17 printf("G = %d",G2)
```

---

# Chapter 15

## Operational Amplifiers

Scilab code Exa 15.4 Example 4

```
1 //Chapter 15, Example 15.4
2
3 clc
4 //Initialisation
5 b=2*10**4 //bandwidth in
   hertz
6
7 //Calculation
8 gain=10**6/b //gain
9
10 //Results
11 printf("Gain = %d",gain)
```

---

Scilab code Exa 15.5 Example 5

```
1 //Chapter 15, Example 15.5
2
3 clc
```

```

4 //Initialisation
5 g=2*10**5 //open loop gain
6 g2=20 //closed loop gain
7 ro=75 //ouput resistance
8 ri=2*10**6 //input resistance
9
10 //Calculation
11 ab=g/g2 //1 + AB
12 ro2=ro/ab //output resistance in
    ohm
13 ri2=ri*ab //input resistance in
    ohm
14
15 //Results
16 printf("Output Resistance = %.1f mOhm\n",ro2*1000)
17 printf("Input Resistance = %d GOhm",ri2/10**9)

```

---

#### Scilab code Exa 15.6 Example 6

```

1 //Chapter 15, Example 15.6
2
3 clc
4 //Initialisation
5 g=2*10**5 //open loop gain
6 g2=20 //closed loop gain
7 ro=75 //ouput resistance
8 ri=2*10**6 //input resistance
9 r1=1000 //resistance in ohm
10
11 //Calculation
12 ab=g/g2 //1 + AB
13 ro1=ro/ab //output resistance in
    ohm
14
15

```

```

16 //Results
17 printf("Output Resistance = %.1f mOhm\n",ro1*1000)
18 printf("Input Resistance = %d kOhm\n",r1/1000)

```

---

#### Scilab code Exa 15.7 Example 7

```

1 //Chapter 15, Example 15.7
2
3 clc
4 //Initialisation
5 g=2*10**5 //open loop gain
6 g2=1 //closed loop gain
7 ro=75 //ouput resistance
8 ri=2*10**6 //input resistance
9
10 //Calculation
11 ab=g/g2 //1 + AB
12 ro2=ro/ab //output resistance in
    ohm
13 ri2=ri*ab //input resistance in
    ohm
14
15 //Results
16 printf("Output Resistance = %.1f uOhm\n",ro2*10**6)
    //wrong answerin textbook
17 printf("Input Resistance = %d GOhm",ri2/10**9)

```

---

# Chapter 16

## Semiconductors and Diodes

Scilab code Exa 16.1 Example 1

```
1 //Chapter 16, Example 16.1
2
3 clc
4 //Initialisation
5 e=5 //emf i volt
6 r=1000 //resistance in ohm
7
8
9 //Calculation
10 i=e/r //current in amp
11 v=0.75 //voltage across diode
    from graph shown
12
13 //Results
14 printf("Current = %d mA\n",i*1000)
15 printf("Voltage = %.2f V",v)
```

---

Scilab code Exa 16.2 Example 2

```

1 //Chapter 16, Example 16.2
2 clc
3 //Initialisation
4 E=5 //voltage
5 R=1000 //resistance in ohm
6 Vd=0.7 //barrier voltage
7 ron=10 //internal resistance in
   ohm
8
9 //Calculation
10 I=E/R //current in ampere
11 I1=(E-Vd)/R //current in ampere
12 I2=(E-Vd)/(R+ron) //current in ampere
13
14 //Results
15 printf("When no voltage drop, I = %d mA\n",I*1000)
16 printf("When there is conduction voltage of the
   diode, I = %.1f mA\n",I1*1000)
17 printf("When there is conduction voltage and
   internal resistance if the diode, I2 = %.2f mA\n"
   ,I2*1000)

```

---

### Scilab code Exa 16.3 Example 3

```

1 //Chapter 16, Example 16.3
2 clc
3 //Initialisation
4 vz=3.6 //voltage
5 R1=200 //resistance in ohm
6 ron=10 //internal resistance in
   ohm
7 R=47 //chosen value of
   resistor in ohm
8 V=5.5 //minimum supply
   voltage

```

```

9  IL=0.018                                //current in ampere
10
11 // Calculation
12 I1=vz/R1                                //current in ampere
13 Pr=(V-vz)**2/R                          //power in watt
14 Pz=(((V-vz)/R)-IL)*vz                   //power in watt
15
16 // Results
17 printf("Pr(max) = %d mW\n",round(Pr*1000))
18 printf("Pz(max) = %d mW",round(Pz*1000))

```

---

#### Scilab code Exa 16.4 Example 4

```

1 //Chapter 16, Example 16.4
2
3 clc
4 //Initialisation
5 i=0.2                                    //current in ampere
6 c=0.01                                  //capacitance in
   farad
7 t=20*10**-3                             //time in sec
8
9 // Calculation
10 dv=i/c                                  //change in voltage w
   .r.t time
11 vc=t*dv                                 //peak ripple voltage
   on capacitor
12
13 // Results
14 printf("Peak Ripple Voltage = %.1f V",vc)

```

---

#### Scilab code Exa 16.5 Example 5

```
1 //Chapter 16, Example 16.5
2
3 clc
4 //Initialisation
5 dv=20 //change in voltage w.
      r.t time
6 t=10*10**-3 //time in sec
7
8 //Calculation
9 vc=t*dv //peak ripple voltage
      on capacitor
10
11 //Results
12 printf("Peak Ripple Voltage = %.1 f V",vc)
```

---

# Chapter 17

## Field effect Transistors

Scilab code Exa 17.1 Example 1

```
1 //Chapter 17, Example 17.1
2 clc
3 //Initialisation
4 rd=100*10**3 //resistance in ohm
5 gm=2*10**-3 //in seimens
6 RD=2*10**3 //resistance in ohm
7 RG=10**6 //resistance in ohm
8
9 //Calculation
10 ro=((rd*RD)/(rd+RD)) //
    Input Resistance
11 v=-gm*ro //Small Signal
    Voltage Gain
12 ri=RG //Input Resistance
13
14 //Results
15 printf("Small Signal Voltage Gain = %.1f \n",v)
16 printf("Input Resistance , ri = %d MOhm \n",ri/10**6)
17 printf("Ouput Resistance , ro = %d kOhm \n",round(ro
    /10**3))
```

---

### Scilab code Exa 17.2 Example 2

```
1 //Chapter 17, Example 17.2
2 clc
3 //Initialisation
4 C=10**-6 //capacitance in farad
5 RG=10**6 //resistance in ohm
6 pi=3.14 //pi
7
8
9 //Calculation
10 fc=1/(2*pi*C*RG) //frequency in Hz
11
12 //Results
13 printf("Fc = %.2 f Hz",fc )
```

---

### Scilab code Exa 17.3 Example 3

```
1 //Chapter 17, Example 17.3
2 clc
3 //Initialisation
4 VDD=15 //voltage
5 Vq=10 //quiescent output
   voltage
6 VGS=3 //voltage
7 RD=2.5*10**3 //resistance in Ohm
8
9 //Calculation
10 VR=VDD-Vq //voltage
11 ID=VR/RD //quiescent drain
   current
12 Rs=VGS/ID //resistance in ohm
```

```

13
14
15 // Results
16 printf("Rs = %.1 f kOhm\n",Rs/1000)
17 printf("ID = %d mA\n",ID*1000)
18 printf("VR = %d V",VR)

```

---

#### Scilab code Exa 17.4 Example 4

```

1 //Chapter 17, Example 17.4
2 clc
3 //Initialisation
4 VDD=15 //voltage
5 Vq=10 //quiescent output
   voltage
6 RD=2.5*10**3 //resistance in Ohm
7 Vp=-6 //voltage
8 IDSS=8*10**-3 //saturation
   drain current in amp
9
10 //Calculation
11 VR=VDD-Vq //voltage
12 ID=VR/RD //quiescent drain
   current
13 VGS=Vp*(1-sqrt(ID/IDSS)) //voltage
14 Rs=VGS/ID //resistance in ohm
15
16
17 // Results
18 printf("Rs = %.1 f kOhm\n",-Rs/1000)
19 printf("ID = %d mA\n",ID*1000)
20 printf("VGS = %d V\n",VGS)

```

---

### Scilab code Exa 17.5 Example 5

```
1 //Chapter 17, Example 17.5
2 clc
3 //Initialisation
4 r1=10**6 //resistance in
   ohm
5 r2=2*10**6 //resistance in
   ohm
6 Rd=3.3*10**3 //resistance in
   ohm
7 Rs=10**3 //resistance in
   ohm
8 c=10**-6 //capactance in
   farad
9 pi=3.14 //pi
10
11 //Calculation
12 ri=(r1*r2)/(r1+r2) //resistance in R1
   & R2 parallel
13 ro=Rd //output
   resistance
14 av=-Rd/Rs //votlage gain
15 fc=1/(2*pi*ri*c) //frequency in Hz
16
17 //Results
18 printf("Input resistance ri = %d kOhm\n",round(ri
   /1000))
19 printf("Output resistance ro = %.1 f kOhm\n",ro/1000)
20 printf("Small Signal Voltage Gain = %.1 f\n",av)
21 printf("Fo = %.2 f Hz ",fc)
```

---

### Scilab code Exa 17.6 Example 6

```
1 //Chapter 17, Example 17.6
```

```

2  clc
3  //Initialisation
4  rd=50*100*3           //resistance
    in ohm
5  gm=72*10**-3         //in siemens
6  Rd=3.3*10**3        //resistance in
    ohm
7  Rs=10**3            //resistance in
    ohm
8
9
10
11 //Calculation
12 av=-Rd/Rs           //voltage gain
    from eq 17.7
13 b=gm*Rd
14 c=gm*Rs
15 av1=-(b)/(1+(c)+((Rd+Rs)/rd)) //voltage gain
    from eq 17.8
16 av2=-(b)/(1+(c))   //voltage gain
    from eq 17.9
17
18 //Results
19 printf("From Eq 17.7, Gain = %.1 f\n",av)
20 printf("From Eq 17.8, Gain = %.3 f\n",av1)
21 printf("From Eq 17.9, Gain = %.3 f\n",av2)

```

---

### Scilab code Exa 17.7 Example 7

```

1  //Chapter 17, Example 17.7
2  clc
3  //Initialisation
4  gm=72*10**-3         //in siemens
5  Rd=3.3*10**3        //resistance in
    ohm

```

```
6
7
8
9 // Calculation
10 b=-gm*Rd //gain of the
    circuit
11
12
13 // Results
14 printf(" Gain = %.1 f\n", round(b))
```

---

# Chapter 18

## Bipolar Junction Transistors

Scilab code Exa 18.1 Example 1

```
1 //Chapter 18, Example 18.1
2 clc
3 //Initialisation
4 VCC=10 //voltage
5 VBE=0.7 //base emitter
   voltage
6 RB=910*10**3 //resistance in ohm
7 hfe=100 //HFE parameter of
   the transistor
8 RC=4.7*10**3 //resistance in ohm
9
10
11 //Calculation
12 IB=(VCC-VBE)/RB //base current
   in ampere
13 IC=hfe*IB //collector
   current in ampere
14 Vq=VCC-(IC*RC) //quiescent
   output voltage
15
16
```

```

17 //Results
18 printf("Quiescent Output Current = %.2 f mA\n",IC
    *1000)
19 printf("Quiescent Output Voltage = %.1 f V\n",Vq)

```

---

### Scilab code Exa 18.2 Example 2

```

1 //Chapter 18, Example 18.2
2 clc
3 //Initialisation
4 Ie=1.02*10**-3
5 RB=910*10**3 //resistance in ohm
6 hfe=100 //HFE parameter of
    the transistor
7 RC=4.7*10**3 //resistance in ohm
8 hoe=10*10**-6 //HOE
    parameter of the transistor
9
10 //Calculation
11 gm=40*Ie
12 hie=hfe/(40*Ie) //HIE
    parameter of the transistor
13 av=-gm*RC/((hoe*RC)+1) //small
    signal voltage gain
14 ri=(RB*hie)/(RB+hie) //Input
    Resistance
15 a1=1/hoe
16 ro=(RC*a1)/(RC+a1) //Output
    Resistance
17
18
19 //Results
20 printf("Small Signal Voltage Gain = %d \n",av)
21 printf("Input Resistance = %.1 f kOhm \n",ri/1000)
22 printf("Output Resistance = %.1 f kOhm \n",ro/1000)

```

---

Scilab code Exa 18.3 Example 3

```
1 //Chapter 18, Example 18.3
2 clc
3 //Initialisation
4 VCC=10 //voltage
5 R2=10*10**3 //resistance in ohm
6 R1=27*10**3 //resistance in ohm
7 RE=1*10**3 //resistance in ohm
8 RC=2.2 //resistance in ohm
9 VBE=0.7 //base emitter
   voltage
10
11
12
13 //Calculation
14 VB=VCC*(R2/(R1+R2)) //Quiescent
   base voltage
15 VE=VB-VBE //Quiescent
   emitter voltage
16 IE=VE/RE //Quiescent
   emitter current
17 IC=IE //Quiescent
   collector current
18 VO=VCC-(IC*RC) //Quiescent
   collector voltage
19
20
21
22
23 //Results
24 printf("Quiescent base voltage = %.2f V\n",VB)
25 printf("Quiescent emitter voltage = %d V\n",VE)
26 printf("Quiescent emitter current = %d mA\n",IE)
```

```

    *1000)
27 printf("Quiescent collector current = %d mA\n",IC
    *1000)
28 printf("Quiescent collector voltage = %.1f V\n",V0)
    //wrong answer on textbook

```

---

#### Scilab code Exa 18.4 Example 4

```

1 //Chapter 18, Example 18.4
2 clc
3 //Initialisation
4 RE=1.2*10**3 //resistance in ohm
5 RC=2.2*10**3 //resistance in ohm
6
7
8 //Calculation
9 av=-RC/RE //voltage gain
10
11
12 //Results
13 printf("Voltage gain = %.1f ",av) //wrong
    answer in the textbook

```

---

#### Scilab code Exa 18.6 Example 6

```

1 //Chapter 18, Example 18.6
2 clc
3 //Initialisation
4 vcc=15 //voltage
5 vc=9.5 //voltage
6 ic=10**-3 //collector
    current
7 Ie=10**-3 //emitter current

```

```

8 RE=5.6*10**3 //resistance in ohm
9 RC=1.3*10**3 //resistance in ohm
10 R2=13*10**3 //resistance in
    ohm, choosen R2 as approximately 10 times RE
11 pi=3.14 //pi
12 fc=10 //frequency in
    hertz
13
14
15 //Calculation
16 rc=(vcc-vc)/ic //resistance in
    ohm
17 re=rc/4 //resistance in ohm
18 vg=-RC/(RE+re) //voltage gain
19 R1=(R2*(vcc-2))/2 //resistance in
    ohm
20 Ri=(R1*R2)/(R1+R2) //input
    resistance in ohm
21 c=1/(2*pi*fc*Ri) //cut-off
    frequency
22
23
24
25 //Results
26 printf("C = %.1 f uF\n",c*10**6)
27 printf("R1 = %.1 f kOhm\n",R1/10**3)
28 printf("R2 = %d kOhm\n",R2/10**3)
29 printf("RC = %.1 f kOhm\n",rc/10**3)
30 printf("RE = %.1 f kOhm\n",re/10**3)

```

---

### Scilab code Exa 18.7 Example 7

```

1 //Chapter 18, Example 18.7
2 clc
3 //Initialisation

```

```

4 vcc=15 //voltage
5 RC=5.6*10**3 //resistance in ohm
6 RE=1.3*10**3 //resistance in ohm
7 R2=13*10**3 //resistance in
  ohm,
8 R1=82*10**3 //resistance in
  ohm
9 pi=3.14 //pi
10 fc=10 //frequency in
  hertz
11 VBE=0.7 //base to
  emitter voltage
12
13 //Calculation
14 VB=vcc*(R2/(R1+R2)) //Quiescent
  base voltage
15 VE=VB-VBE //Quiescent
  emitter voltage
16 IE=VE/RE //Quiescent
  emitter current
17 IC=IE //Quiescent
  collector current
18 VO=vcc-(IC*RC) //Quiescent
  collector voltage
19
20
21
22 //Results
23 printf("Quiescent base voltage = %.2f V\n",VB)
24 printf("Quiescent emitter voltage = %.2f V\n",VE)
25 printf("Quiescent emitter current = %.2f mA\n",IE
  *1000)
26 printf("Quiescent collector current = %.2f mA\n",IC
  *1000)
27 printf("Quiescent collector voltage = %.1f V\n",VO)

```

---

### Scilab code Exa 18.8 Example 8

```
1 //Chapter 18, Example 18.8
2 clc
3 //Initialisation
4 vcc=15 //voltage
5 RC=5.6*10**3 //resistance in ohm
6 RE=1.3*10**3 //resistance in ohm
7 R2=13*10**3 //resistance in
  ohm,
8 R1=82*10**3 //resistance in
  ohm
9 pi=3.14 //pi
10 fc=10 //frequency in
  hertz
11 VBE=0.7 //base to
  emitter voltage
12 hfe1=100
13 hfe2=400
14
15 //Calculation
16 VB=vcc*(R2/(R1+R2)) //Quiescent
  base voltage
17 VE=VB-VBE //Quiescent
  emitter voltage
18 IE=VE/RE //Quiescent
  emitter current
19 IC=IE //Quiescent
  collector current
20 VO=vcc-(IC*RC) //Quiescent
  collector voltage
21
22 re=1/(40*IE)
23 av=-RC/re //voltage gain
```

```

24 rp=(R1*R2)/(R1+R2)
25
26 //if hfe=100
27 hie1=hfe1*re
28 ri1=(rp*hie1)/(rp+hie1)
29
30 //if hfe=400
31 hie2=hfe2*re
32 ri2=(rp*hie2)/(rp+hie2)
33
34 ro=RC
35
36 //Results
37 printf("Small Signal Voltage Gain = %d\n",av)
38 printf("Small Signal Input Resistance is %d kOhm to
    %.1f kOhm\n",round(ri1/1000),(ri2/1000))
39 printf("Small Signal Output Resistance is %.1f kOhm\
    n", (RC/1000))

```

---

### Scilab code Exa 18.9 Example 9

```

1 //Chapter 18, Example 18.9
2 clc
3 //Initialisation
4 R1=2*10**3 //resistance in ohm
5 R2=5.2*10**3 //resistance in ohm
6 pi=3.14 //pi
7 c=2.2*10**-6 //capacitance in
    farad
8 ce=10*10**-6 //capacitance
    in farad
9 re=24 //resistance in
    ohm
10
11 //Calculation

```

```

12 fc1=1/(2*pi*c*R1)           //cut-off
    frequency
13
14 fc2=1/(2*pi*c*R2)           //cut-off
    frequency
15
16 fc=1/(2*pi*ce*re)           //cut-off
    frequency
17
18 //Results
19 printf("Coupling Capacitor is in the range %d Hz -
    %d Hz\n",round(fc2),round(fc1))
20 printf("Decoupling Capacitor , Ce = %d Hz",fc)

```

---

#### Scilab code Exa 18.10 Example 10

```

1 //Chapter 18, Example 18.10
2 clc
3 //Initialisation
4 VCC=10           //voltage
5 R2=10*10**3     //resistance in ohm
6 R1=27*10**3     //resistance in ohm
7 RE=100          //resistance in ohm
8 RC=2.2          //resistance in ohm
9 VBE=0.7         //base emitter voltage
10 av=1           //small sg voltage gain
11
12
13 //Calculation
14 VB=VCC*(R2/(R1+R2)) //Quiescent
    base voltage
15 VE=VB-VBE      //Quiescent
    emitter voltage
16 IE=VE/RE       //Quiescent
    emitter current

```

```

17 ri=(R1*R2)/(R1+R2)           //input
    resistance
18 ro=1/(40*IE)                 //output
    resistance
19
20
21
22 //Results
23 printf("Small Signal Voltage Gain = %d\n",av)
24 printf("Small Signal Input Resistance is %.1f kOhm\n
    ",(ri/1000))
25 printf("Small Signal Output Resistance is %.2f kOhm\
    n",(ro))

```

---

#### Scilab code Exa 18.11 Example 11

```

1 //Chapter 18, Example 18.11
2 clc
3 //Initialisation
4 VCC=10                       //voltage
5 R2=3*10**3                   //resistance in ohm
6 R1=7*10**3                   //resistance in ohm
7 RE=10**3                     //resistance in ohm
8 RC=3*10**3                   //resistance in
    ohm
9 VBE=0.7                      //base emitter voltage
10 av=1                         //small sg voltage gain
11 RE2=2*10**3                 //resistance in ohm
12 RC2=4*10**3                 //resistance in
    ohm
13
14
15 //Calculation
16 VB=VCC*(R2/(R1+R2))         //Quiescent
    base voltage

```

```

17 VE=VB-VBE //Quiescent
    emitter voltage
18 IE=VE/RE //Quiescent
    emitter current
19 VC1=VCC-(IE*RC) //Quiescent
    collector voltage
20 VB2=VC1 //bias voltage
21 VE2=VB2-VBE //emitter
    voltage
22 IC2=VE2/RE2 //collector
    current in ampere
23 VC2=VCC-(IC2*RC2) //collector
    voltage
24 Av=(-RC/RE)*(-RC2/RE2) //overall gain
25
26
27
28 //Results
29 printf("Quiescent output voltage = %.1f V\n",VC2)
30 printf("Overall Voltage Gain = %d",Av)

```

---

# Chapter 19

## Power Electronics

Scilab code Exa 19.1 Example 1

```
1 //Chapter 19, Example 19.1
2
3 clc
4 //Initialisation
5 r3=1.222*10**3 //resistance in ohm
6 r4=1*10**3 //resistance in ohm
7 v1=0.7 //voltage
8 vz=4.7
9
10 //Calculation
11 vo=(vz+v1)*((r3+r4)/r4) //Output Voltage
12
13
14 //Results
15 printf("Output Voltage Vo = %d V",round(vo))
```

---

Scilab code Exa 19.2 Example 2

```

1 //Chapter 19, Example 19.2
2
3 clc
4 //Initialisation
5 r1=5 //resistance in ohm
6 vo=10 //Output Voltage
7 vi=15 //input voltage
8
9 //Calculation
10 io=vo/r1 //current in ampere
11 po=vo*io //power delivered to
    load
12 pt=(vi-vo)*io //power delivered to
    output transistor
13
14
15 //Results
16 printf("Output Power on Load Po = %d W\n",round(po))
17 printf("Output Power on O/P Transistor Pt = %d W",
    round(pt))

```

---

# Chapter 21

## Noise and Electromagnetic Compatibility

Scilab code Exa 21.1 Example 1

```
1 //Chapter 21, Example 21.1
2
3 clc
4 //Initialisation
5
6 vo=2.5 //Output Voltage
7 vi=0.01 //input voltage
8
9 //Calculation
10 sn=20*log10(vo/vi) //signal to noise ratio
11
12
13 //Results
14 printf("S/N Ratio = %d dB",round(sn))
```

---

# Chapter 23

## Digital Systems

Scilab code Exa 23.16 Example 16

```
1 //Chapter 23, Example 23.16
2
3 clc
4 ////Initialisation
5 x="11010" //binary number to be
   convert
6
7
8 //Calculation
9 x1=bin2dec(x) //conversion to
   decimal
10
11 //Results
12 printf("Decimal of 11010 = %d",x1)
```

---

Scilab code Exa 23.17 Example 17

```
1 //Chapter 23, Example 23.17
```

```

2  clc
3  //Initialisation
4  x=26          //decimal number to be convert
5
6
7  //Calculation
8  z1=dec2bin(x)      //conversion to
   binary
9
10 //Results
11 printf("Binary of 26 = %s",z1)

```

---

#### Scilab code Exa 23.18 Example 18

```

1  //Chapter 23, Example 23.18
2
3  //Conversion of decimal to binary//
4  clc
5  //clears the console//
6  clear
7  //clears all existing variables//
8  q=0
9  b=0
10 s=0
11 //initialising//
12 //a=input(enter the decimal number to be converted
   to its binary form)
13 //taking input from the user//
14 a=34.6875
15 d=modulo(a,1)
16 //separating the decimal part from the integer//
17 a=floor(a)
18 a1=a
19 a=0
20 //removing the decimal part//

```

```

21 while(a>0)
22 //integer part converted to equivalent binary form//
23 x=modulo(a,2)
24 b=b+(10^q)*x
25 a=a/2
26 a=floor(a)
27 q=q+1
28 end
29 for i=1: 10
30 //taking values after the decimal part and
    converting to equivalent binary form//
31 d=d*2
32 q=floor(d)
33 s=s+q/(10^i)
34 if d>=1 then
35     d=d-1
36 end
37 end
38 l=dec2bin(a1)
39 k=b+s
40
41 disp('the decimal number in binary form is :')
42 printf("%s . %d",l,k*10**4)
43 //result is displayed//

```

---

#### Scilab code Exa 23.19 Example 19

```

1 //Chapter 23, Example 23.19
2
3 clc
4 //Initialisation
5 x="A013" //hex number to be
    convert
6
7

```

```

8 // Calculation
9 x1=hex2dec(x)           //conversion to
    decimal
10
11 // Results
12 printf("Decimal of A013 = %d",x1)

```

---

**Scilab code Exa 23.20 Example 20**

```

1 //Chapter 23, Example 23.17
2 clc
3 //Initialisation
4 x=7046           //decimal number to be convert
5
6
7 // Calculation
8 z1=dec2hex(x)   //conversion to hex
    number
9
10 // Results
11 printf("Hex of 7046 = %s",z1)

```

---

**Scilab code Exa 23.21 Example 21**

```

1 //Chapter 23, Example 23.21
2 clc
3 //Initialisation
4 x="F851"       //hex number to be convert
5
6
7 // Calculation
8 z1=hex2dec(x)  //conversion to
    decimal

```

```

9 z2=dec2bin(z1) //conversion to
    binary
10
11 //Results
12 printf("Binary of F851 = %s",z2)

```

---

#### Scilab code Exa 23.22 Example 22

```

1 //Chapter 23, Example 23.22
2 clc
3 //Initialisation
4 x="111011011000100" //binary numbr
    to be convert
5
6
7 //Calculation
8 z1=bin2dec(x) //conversion to
    decimal
9 z2=dec2hex(z1) //conversion to
    binary
10
11 //Results
12 printf("Hex of 111011011000100 = %s",z2)

```

---

#### Scilab code Exa 23.23 Example 23

```

1 //Chapter 23, Example 23.23
2 clc
3 //Initialisation
4 x=[9 4 5 0] //decimal number to be
    convert
5
6

```

```

7 // Calculation
8 //using for loop for converting each decimal to BCD
9 n=4
10 m=4
11 disp("BCD is ")
12 for i = 1:n
13     z=dec2bin(x(i),m)           //decimal to
        binary conversion
14     printf(z)
15     printf(" ")               //display of BCD
16 end

```

---

#### Scilab code Exa 23.24 Example 24

```

1 //Chapter 23, Example 23.16
2 clc
3
4 a=11100001110110           //input BCD
        digits
5 z =0;
6
7 d= modulo (a ,10000)
8 for j =1:3
9     y(j)= modulo (d ,10)
10    z=z+(y(j) *(2^(j -1)))
11    d=d/10
12    d= floor (d)
13 end
14
15 b=a /10000
16 b= floor (b)
17 c= modulo (b ,10000)
18 z1 =0
19 for j =1:3
20    y(j)= modulo (c ,10)

```

```

21     z1=z1 +(y(j) *(2^(j -1) ))
22     c=c/10
23     c= floor (c)
24 end
25
26 e=b /10000
27 e= floor (e)
28 e1= modulo (e ,10000)
29 z2 =0
30 for j =1:4
31     y(j)= modulo (e1 ,10)
32     z2=z2 +(y(j) *(2^(j -1) ))
33     e1=e1/10
34     e1= floor (e1)
35 end
36
37 f=e /10000
38 f= floor (f)
39 z3 =0
40 for j =1:2
41     y(j)= modulo (f ,10)
42     z3=z3 +(y(j) *(2^(j -1) ))
43     f=f/10
44     f= floor (f)
45 end
46
47
48 r=z3*1000+z2 *100+ z1 *10+ z
49 printf ( '(111000011101110)BCD to Decimal = %d ' ,r)
      //display of decimal numbers

```

---

# Chapter 26

## Implementing Digital Systems

Scilab code Exa 26.1 Example 1

```
1 //Chapter 26, Example 26.1
2
3 clc
4 //Initialisation
5 n=24 //no of bits
6
7
8 //Calculation
9 ad=2**n //no of locations
10
11
12 //Results
13 printf("No of Locations = %d ",ad)
```

---

Scilab code Exa 26.4 Example 4

```
1 //Chapter 26, Example 26.4
2
```

```
3  clc
4  //Initialisation
5  x=5           //decimal number to be convert
6  y=65536      //2^16 decimal number
7
8
9  //Calculation
10 z=y-x        //subtraction from
    2^16 number
11 z1=dec2bin(z) //conversion to
    binary
12
13 //Results
14 printf("-5 as a 16 bit signed number = %s",z1)
```

---