

Scilab Textbook Companion for  
Fundamentals Of Electrical Drive  
by Mohamad A. El- Sharkawi <sup>1</sup>

Created by

Abisha L J

BE

Electrical Engineering

St.Xavier's Catholic College of Engineering

College Teacher

None

Cross-Checked by

None

July 31, 2019

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Fundamentals Of Electrical Drive

**Author:** Mohamad A. El- Sharkawi

**Publisher:** Nelson Engineering

**Edition:** 1

**Year:** 2000

**ISBN:** 0534952224

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
2 Introduction to solid state Devices	6
3 Introduction to solid state switching circuits	11
4 Joint speed torque characterstics of electric motor and mechanical loads	34
5 speed torque characterstics of electric motor	37
6 speed control of direct current motors	46
7 speed control of induction motors	55
9 Braking of dc motors	72
10 Braking of induction motors	82
11 Dynamics of electric drive systems	86

# List of Scilab Codes

Exa 2.1	calculate base current in linear and saturation region . . . . .	6
Exa 2.2	calculate the approximate value of dc gate current . . . . .	7
Exa 2.3	To calculate the minimum value of snubbing inductance . . . . .	8
Exa 2.4	Design a snubbing circuit to protect a SCR from excessive change in volume by time . . . . .	9
Exa 3.1	calculate the average current . . . . .	11
Exa 3.2	calculate rms voltage rms current average voltage drop . . . . .	12
Exa 3.3	compute power dissipated in the load resistance . . . . .	14
Exa 3.4	compute power factor at the ac side . . . . .	16
Exa 3.5	calculate the triggering angle and the load power . . . . .	17
Exa 3.6	calculate conduction period . . . . .	18
Exa 3.7	calculate conduction period maximum and average diode current and average current of SCR . . . . .	20
Exa 3.8	calculate power delivered to the load when the triggering angle is 80 and 30 degree . . . . .	22
Exa 3.9	calculate maximum average voltage and triggering angle and load voltage . . . . .	23
Exa 3.10	calculate on time and switching period average voltage across load and diode average current and load power . . . . .	25

Exa 3.12	calculation of conduction period of each transistor . . . . .	27
Exa 3.13	calculate rms voltage applied to the motor .	28
Exa 3.14	calculate the rms current and the power delivered to battery during charging . . . . .	29
Exa 3.15	calculate the rms current and the power delivered to battery during discharging . . . . .	30
Exa 3.16	calculate minimum triggering angle and associated conduction period and average charging current . . . . .	32
Exa 4.1	compute the power consumed by the load .	34
Exa 5.1	calculate rated torque starting torque and starting current . . . . .	37
Exa 5.2	compute the motor efficiency . . . . .	38
Exa 5.3	calculate speed of motor copper loss starting torque of the motor . . . . .	39
Exa 5.4	calculate the change in starting torque and resistance added to achieve maximum torque	42
Exa 5.5	compute the excitation current to improve overall power factor . . . . .	43
Exa 5.6	compute the minimum excitation that the machine must maintain to provide the needed torque . . . . .	44
Exa 6.1	calculate added resistance to reduce the speed by 50 percentage and efficiency and resistance added to operate the motor in holding condition . . . . .	46
Exa 6.3	calculate armature current and motor speed and value of added resistance and extra field loss . . . . .	48
Exa 6.4	calculate the motor speed and the developed power . . . . .	50
Exa 6.5	calculate the motor speed and the power delivered to the load . . . . .	51
Exa 6.6	calculate the triggering angle of the motor .	52
Exa 6.7	calculate field current motor voltage and speed	53

Exa 7.1	compute the added resistance to reduce the speed by 20 percent and motor efficiency with and without added resistance and annual cost of operating motor . . . . .	55
Exa 7.2	calculate the magnitude of the injected voltage and the power delivered by the source of injected voltage . . . . .	57
Exa 7.3	calculate the starting current and starting torque with and without the voltage . . . . .	59
Exa 7.4	calculate the motor speed and current in dc link and rotor and stator rms current and power returned back to the source and additional losses . . . . .	60
Exa 7.5	calculate the motor speed at full voltage . .	63
Exa 7.6	compute maximum frequency and then motor current and power delivered at 60 Hz and at maximum frequency . . . . .	64
Exa 7.7	compute the motor speed and the starting current if the frequency decreased to 50 Hz .	66
Exa 7.8	compute the starting current for a constant v by f control . . . . .	67
Exa 7.9	compute the input current . . . . .	69
Exa 7.10	compute the frequency of the CSI to drive the machine at 900 rpm . . . . .	70
Exa 9.1	calculate no load and motor speed then developed torque and $E_a$ and terminal current and total losses during regenerative braking and also power delivered . . . . .	72
Exa 9.2	calculate the speed . . . . .	74
Exa 9.3	calculate the triggering angle . . . . .	75
Exa 9.4	calculate the triggering angle . . . . .	76
Exa 9.5	calculate the value of braking resistance . .	77
Exa 9.6	calculate the triggering angle . . . . .	78
Exa 9.7	calculate the triggering angle . . . . .	79
Exa 9.8	calculate new steady state speed and the armature current . . . . .	80
Exa 10.1	calculate motor speed and power delivered to the electrical supply . . . . .	82

Exa 10.2	calculate the duty ratio of the FWM . . . . .	83
Exa 10.3	calculate slip and current and also torque at all operating points . . . . .	84
Exa 11.1	calculate the motor speed . . . . .	86
Exa 11.3	calculate and show how to achieve the desired starting time . . . . .	87
Exa 11.4	calculate the time required to change the mo- tor speed . . . . .	88
Exa 11.5	calculate terminal voltage and traveling time during braking . . . . .	89
Exa 11.6	compute the starting time of the motor at no load and full load voltage . . . . .	90
Exa 11.7	compute the starting time . . . . .	91
Exa 11.8	compute the magnitude of the motor voltage	93
Exa 11.9	compute the value of braking resistance . . .	93
Exa 11.10	compute the starting time . . . . .	95



# List of Figures

2.1	calculate base current in linear and saturation region . . . . .	7
2.2	calculate the approximate value of dc gate current . . . . .	7
2.3	To calculate the minimum value of snubbing inductance . . . . .	8
2.4	Design a snubbing circuit to protect a SCR from excessive change in volume by time . . . . .	9
3.1	calculate the average current . . . . .	11
3.2	calculate rms voltage rms current average voltage drop . . . . .	13
3.3	compute power dissipated in the load resistance . . . . .	15
3.4	compute power factor at the ac side . . . . .	16
3.5	calculate the triggering angle and the load power . . . . .	17
3.6	calculate conduction period . . . . .	19
3.7	calculate conduction period maximum and average diode current and average current of SCR . . . . .	20
3.8	calculate power delivered to the load when the triggering angle is 80 and 30 dgree . . . . .	22
3.9	calculate maximum average voltage and triggering angle and load voltage . . . . .	24
3.10	calculate on time and switching period average voltage across load and diode average current and load power . . . . .	25
3.11	calculation of conduction period of each transistor . . . . .	27
3.12	calculate rms voltage applied to the motor . . . . .	28

3.13	calculate the rms current and the power delivered to battery during charging . . . . .	29
3.14	calculate the rms current and the power delivered to battery during discharging . . . . .	31
3.15	calculate minimum triggering angle and associated conduction period and average charging current . . . . .	32
4.1	compute the power consumed by the load . . . . .	34
5.1	calculate rated torque starting torque and starting current . .	38
5.2	compute the motor efficiency . . . . .	38
5.3	calculate speed of motor copper loss starting torque of the motor . . . . .	40
5.4	calculate the change in starting torque and resistance added to achieve maximum torque . . . . .	43
5.5	compute the excitation current to improve overall power factor	43
5.6	compute the minimum excitation that the machine must maintain to provide the needed torque . . . . .	45
6.1	calculate added resistance to reduce the speed by 50 percentage and efficiency and resistance added to operate the motor in holding condition . . . . .	47
6.2	calculate armature current and motor speed and value of added resistance and extra field loss . . . . .	49
6.3	calculate the motor speed and the developed power . . . . .	50
6.4	calculate the motor speed and the power delivered to the load	51
6.5	calculate the triggering angle of the motor . . . . .	52
6.6	calculate field current motor voltage and speed . . . . .	53
7.1	compute the added resistance to reduce the speed by 20 percent and motor efficiency with and without added resistance and annual cost of operating motor . . . . .	56
7.2	calculate the magnitude of the injected voltage and the power delivered by the source of injected voltage . . . . .	57
7.3	calculate the starting current and starting torque with and without the voltage . . . . .	59
7.4	calculate the motor speed and current in dc link and rotor and stator rms current and power returned back to the source and additional losses . . . . .	61

7.5	calculate the motor speed at full voltage . . . . .	63
7.6	compute maximum frequency and then motor current and power delivered at 60 Hz and at maximum frequency . . . . .	64
7.7	compute the motor speed and the starting current if the frequency decreased to 50 Hz . . . . .	66
7.8	compute the starting current for a constant v by f control . . . . .	67
7.9	compute the input current . . . . .	69
7.10	compute the frequency of the CSI to drive the machine at 900 rpm . . . . .	70
9.1	calculate no load and motor speed then developed torque and $E_a$ and terminal current and total losses during regenerative braking and also power delivered . . . . .	73
9.2	calculate the speed . . . . .	75
9.3	calculate the triggering angle . . . . .	75
9.4	calculate the triggering angle . . . . .	76
9.5	calculate the value of braking resistance . . . . .	77
9.6	calculate the triggering angle . . . . .	78
9.7	calculate the triggering angle . . . . .	79
9.8	calculate new steady state speed and the armature current . . . . .	80
10.1	calculate motor speed and power delivered to the electrical supply . . . . .	83
10.2	calculate the duty ratio of the FWM . . . . .	84
10.3	calculate slip and current and also torque at all operating points . . . . .	84
11.1	calculate the motor speed . . . . .	86
11.2	calculate and show how to achieve the desired starting time . . . . .	87
11.3	calculate the time required to change the motor speed . . . . .	88
11.4	calculate terminal voltage and traveling time during braking . . . . .	89
11.5	compute the starting time of the motor at no load and full load voltage . . . . .	90
11.6	compute the starting time . . . . .	91
11.7	compute the magnitude of the motor voltage . . . . .	92
11.8	compute the value of braking resistance . . . . .	94
11.9	compute the starting time . . . . .	95

# Chapter 2

## Introduction to solid state Devices

Scilab code Exa 2.1 calculate base current in linear and saturation region

```
1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 2
3 //example 2.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ic=10;//collector current in ampere
9 beta1=200; // current gain in the linear region
10 beta2=10; //current gain in the saturation region
11 Ib1=(Ic/beta1); //base current in the linear region
   in ampere
12 Ib2=(Ic/beta2); //base current in the saturation
   region in ampere
13 disp(Ib1,'The base current in the linear region in
   ampere is ')
```

```
Scilab 5.5.2 Console

The base current in the linear region in ampere is

0.05

The base current in the saturation region in ampere is

1.

-->
```

Figure 2.1: calculate base current in linear and saturation region

```
Scilab 5.5.2 Console

gate current required to trigger the SCR at 30 degree in milliamphere is

4.2869961

-->
```

Figure 2.2: calculate the approximate value of dc gate current

```
14 disp(Ib2, 'The base current in the saturation region  
in ampere is')
```

---

**Scilab code Exa 2.2** calculate the approximate value of dc gate current

```
1 //Book name: Fundamentals of electrical drives by  
Mohamad A. El- Sharkawi  
2 //chapter2  
3 //example 2.2
```

The minimum value of snubbing inductance in microhenry is

6.

-->

Figure 2.3: To calculate the minimum value of snubbing inductance

```

4  clc;
5  clear;
6  sv=(2^(1/2))*120*sind(30); //rms value of voltage
    source
7  K=0.2; // constant whose value dependent on device
    characteristics
8  bv=200; //base voltage in volts
9  ig=((log(sv/bv))/(-K)); //gate current in mA
10 disp(ig,'gate current required to trigger the SCR at
    30 degree in milliamphere is')
```

---

**Scilab code Exa 2.3** To calculate the minimum value of snubbing inductance

```

1  // Book Name: Fundametals of electrical drives by
    Mohamad A. El- Sharkawi
2  //chapter 2
3  //example 2.3
4  //edition 1
5  //publisher and place:Nelson Engineering
6  clc;
7  clear;
8  VBO=300; //base voltage in volts
```

```
Scilab 5.5.2 Console
The given snubber circuit is suitable for protecting the SCR from excessive 1000.000000 volt per microsec
-->
```

Figure 2.4: Design a snubbing circuit to protect a SCR from excessive change in voltage by time

```
9 de=100; //maximum di/dt of SCR in A/microsec
10 Vs=120; //source voltage rms value in volts
11 L=(VBO/(0.5*de));
12 disp(L, 'The minimum value of snubbing inductance in
    microhenry is')
```

---

**Scilab code Exa 2.4** Design a snubbing circuit to protect a SCR from excessive change in voltage by time

```
1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter2
3 //example 2.4
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ls=8; //snubbing inductor in microhenry
9 VBO=4000; //base voltage in volts
10 di=200; //rate of change of current (di/dt) in
    amperes per microsec
11 dv=1500; //rate of change of voltage (dv/dt) in volt
    per microsec
12 Cs=10; //snubbing capacitance in microfarad
13 Rs=sqrt(VBO/(0.5*di*Cs)); //snubbing resistance in
    ohms
```

```
14 dVscr=((Rs*VBO)/Ls);///rate of change of SCR voltage
    with respect to time
15 mprintf("The given snubber circuit is suitable for
    protecting the SCR from excessive %f volt per
    microsec",dVscr)
```

---




# Chapter 3
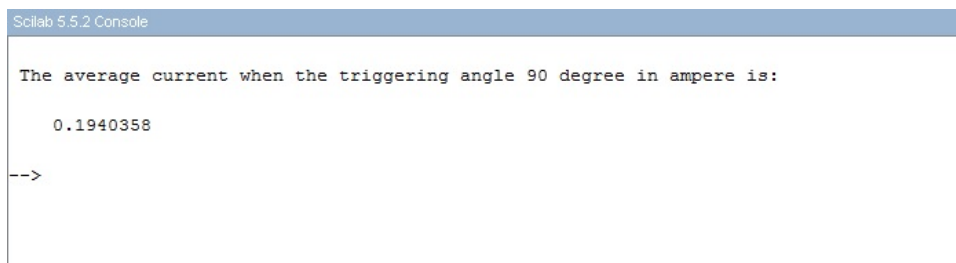
## Introduction to solid state switching circuits

Scilab code Exa 3.1 calculate the average current

```
1 o//Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
```



```
Scilab 5.5.2 Console
The average current when the triggering angle 90 degree in ampere is:
0.1940358
-->
```

Figure 3.1: calculate the average current

```

7 clear;
8 Vrms=110;           //source voltage of the
   circuit in volts
9 alpha=90;         //triggering angle in
   degree
10 Vm=Vrms*(2)^(1/2); //maximum voltage in volts
11 Vave=(Vm/(2*pi))*(1+cosd(alpha));
12 R=(0.2*(Vave)^2)+5; //load resistance in ohm
13 Iave=Vave/R;     //average current of the load
14 disp(Iave,'The average current when the triggering
   angle 90 degree in ampere is:')

```

---

Scilab code Exa 3.2 calculate rms voltage rms current average voltage drop

```

1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter3
3 //example 3.2
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vsrms=110;       //source voltage of the
   circuit in volts
9 Vm=Vsrms*(2)^(1/2); //maximum voltage in volts
10 R=2;           //resistance in ohm
11 alpha1=45;    //triggering angle in degree
12 alpha2=90;    //triggering angle in degree
13 //when a1=45
14 disp('case 1')
15 Vrms=(Vsrms/(2)^(1/2))*(1-(alpha1*(pi/180)/pi)+(
   sind(2*alpha1)/(2*pi)))^(1/2);
16 disp(Vrms,'rms voltage across the load resistance in

```

```
Scilab 5.5.2 Console

case 1

rms voltage across the load resistance in volt is:

    74.164597

rms current of the resistance in ampere is:

    37.082298

average voltage drop across the SCR in volt is:

- 42.265742

case 2

rms voltage across the load resistance in volt is:

    55.

rms current of the resistance in ampere is:

    27.5

average voltage drop across the SCR in volt is:

- 24.758699

-->
```

Figure 3.2: calculate rms voltage rms current average voltage drop

```

        volt is:')
17 Irms=Vrms/R ;
18 disp(Irms,'rms current of the resistance in ampere
    is:')
19 Vscr=-(Vm/(2*%pi))*(1+cosd(alpha1));
20 disp(Vscr,'average voltage drop across the SCR in
    volt is:')
21 //when a2=90
22 disp('case 2')
23 Vrms1=(Vsrms/(2)^(1/2))*(1-(alpha2*(%pi/180)/%pi)+(
    sind(2*alpha2)/(2*%pi)))^(1/2);
24 disp(Vrms1,'rms voltage across the load resistance
    in volt is:')
25 Irms1=Vrms1/R ;
26 disp(Irms1,'rms current of the resistance in ampere
    is:')
27 Vscr1=-(Vm/(2*%pi))*(1+cosd(alpha2));
28 disp(Vscr1,'average voltage drop across the SCR in
    volt is:')

```

---

**Scilab code Exa 3.3** compute power dissipated in the load resistance

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.3
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vrms=110; //The voltage on
    the ac side in volts
9 R=10; //Resistance value

```

```

Scilab 5.5.2 Console

Instantaneous power method:

Power dissipated in the load resistance in watt is:

    486.72183

Harmonic method:

The power computed by harmonic method in watt is:

    486.72183

-->|

```

Figure 3.3: compute power dissipated in the load resistance

```

of the resistive load in ohm
10 alpha=60; //triggering angle
of the converter in degree
11 Vm=110*(2)^(1/2); //maximum voltage
in volts
12 disp('Instantaneous power method:')
13 P=((Vm)^(2)/(8*pi*R))*(2*(pi-alpha*(pi/180))+sind
(2*alpha));
14 disp(P,'Power dissipated in the load resistance in
watt is:')
15 disp('Harmonic method:')
16 a1=(Vm/(2*pi*R))*(cosd(2*alpha)-1);
17 b1=(Vm/(4*pi*R))*(sind(2*alpha)+(2*(pi-alpha*(pi
/180)))));
18 c1=(a1^(2)+b1^(2))^(1/2);
19 pie1=atand(a1/b1);
20 P1=(Vm*c1*cosd(pie1))/2;
21 disp(P1,'The power computed by harmonic method in
watt is:')

```

The power factor on the ac side is

0.4011176

-->

Figure 3.4: compute power factor at the ac side

**Scilab code Exa 3.4** compute power factor at the ac side

```
1 //Book name: Fundamentals of electrical drives by
  Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.4
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vrms=110; //The voltage on
  the ac side in volts
9 R=10; //Resistance value
  of the resistive load in ohm
10 alpha=60; //triggering angle
  of the converter in degree
11 Vm=110*(2)^(1/2); //maximum voltage
```

The triggering angle in degree is

110.28424

The load power in watt is:

605.

-->

Figure 3.5: calculate the triggering angle and the load power

```

in volts
12 a1=(Vm/(2*pi*R))*(cosd(2*alpha)-1);
13 b1=(Vm/(4*pi*R))*(sind(2*alpha)+(2*(pi-alpha*(pi
    /180)))));
14 c1=(a1^(2)+b1^(2))^(1/2);
15 pie1=atand(a1/b1);
16 pie1=abs(pie1);
17 I1rms=c1/sqrt(2);
18 Irms=(Vrms/R)*sqrt(1-((alpha/pi)*(pi/180))+sin(2*
    alpha)/(2*pi));
19 pf=(I1rms/Irms)*cos(pie1);
20 disp(pf,'The power factor on the ac side is')
21 //The answers vary due to round off error

```

---

Scilab code Exa 3.5 calculate the triggering angle and the load power

```

1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.5
4 //edition 1
5 //publishing place:Thomson Learning
6 clc;
7 clear;
8 Vsrms=110;//The voltage on the ac side in volts
9 R=5;//Resistance value of the resistive load in ohm
10 Vrms=55;//voltage across the load
11 //iteration method
12 xold=1;//assumed value
13 x=(180/%pi)*(2.25+(sind(2*xold)/2));
14 err=100;//assumed value
15 while(err>0.0001)
16     xnew=(180/%pi)*(2.25+(sind(2*x)/2));
17     x=xnew;
18     err=abs(xnew-xold);
19     xold=x;
20 end
21 disp(x,'The triggering angle in degree is')
22 P=(Vrms)^2/R;
23 disp(P,'The load power in watt is:')
24 //The answer given in the book is wrong

```

---

### Scilab code Exa 3.6 calculate conduction period

```

1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.6
4 //edition 1

```



```

The value of beta in degree is

30.108882

The conduction period in degree is

- 29.891118

-->

```

Figure 3.6: calculate conduction period

```

5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 R=10;//resistance of the load in ohm
9 L=0.03;//inductance in H
10 Vrms=100;//source voltage in volt
11 f=60;//frequency in Hz
12 alpha=60;//triggering angle in degree
13 omega=2*%pi*f;
14 tau=L/R;
15 Q=atand((omega*L)/R);
16 //iteration method
17 xold=1;//assumed value
18 x=Q+asind(sind(Q-alpha)*exp((-1)*(((xold-alpha)*(%pi
    /180))/(omega*tau))));
19 err=10;//assumed value
20 while(err>0.01)
21     xnew=Q+asind(sind(Q-alpha)*exp((-1)*((x-alpha)*(%pi
    %pi/180)/(omega*tau))));
22     x=xnew;
23     err=abs(xnew-xold);
24     xold=x;
25 end

```

```
Scilab 5.5.2 Console

To find Conduction period:
The conduction period is 249 degree
To find maximum diode current:
The maximum diode current is 7.176458 ampere
To calculate average current of the diode:
The average current of the diode is 0.770542 ampere
To calculate average load current:
The average load current is 3.713805 ampere
To calculate average current of the SCR:
The average current of the SCR is 2.943263 ampere
-->
```

Figure 3.7: calculate conduction period maximum and average diode current and average current of SCR

```
26 disp(x, 'The value of beta in degree is ')
27 r=x-alpha;
28 disp(r, 'The conduction period in degree is ')
29 //The answer given in the book is wrong. While using
   the book answer both LHS and RHS are not equal.
```

---

Scilab code Exa 3.7 calculate conduction period maximum and average diode current

```
1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.7
4 //edition 1
5 //publisher and place:Nelson Engineering
```

```

6  clc;
7  clear;
8  Vs=110; //source voltage in volts
9  L=20e-3; //inductance of the circuit in henry
10 R=10; //resistance of the circuit in ohm
11 a=60; //trigerring angle in degree
12 r1=a*(%pi/180);
13 Vm=Vs*2^(1/2);
14 T=L/R; //Time constant of the circuit in sec
15 w=2*%pi*a; //rotational speed in rad/sec
16 mprintf("\n To find Conduction period:")
17 b=(%pi-(w*T*log(0.05)))*(180/%pi);
18 gama=b-a; //conduction period in degree
19 mprintf("\nThe conduction period is %d dgree",gama)
20 mprintf("\nTo find maximum diode current:")
21 Z=sqrt(R^2+(w*L)^2);
22 wtau=(w*L)/R;
23 Q=atand(wtau);
24 l=exp((-1)*((%pi-(a*(%pi/180)))/wtau));
25 c=(%pi-(a*(%pi/180)));
26 id=(Vm/Z)*(sind(Q)+((sind(Q-a))*l));
27 mprintf("\nThe maximum diode current is %f ampere",
    id)
28 mprintf("\nTo calculate average current of the diode
    :")
29 Idave=(id/(2*%pi))*(-wtau)*(exp((-1)*(b*(%pi/180)-
    %pi))-1);
30 mprintf("\nThe average current of the diode is %f
    ampere", Idave)
31 mprintf("\nTo calculate average load current:")
32 Vave=(Vm/(2*%pi))*(1+(cosd(a)));
33 Iave=Vave/R;
34 mprintf("\nThe average load current is %f ampere",
    Iave)
35 mprintf("\nTo calculate average current of the SCR:")
    )
36 ISCR=Iave-Idave;
37 mprintf("\nThe average current of the SCR is %f

```

```

To find the power delivered at a1=80 degree:

The power delivered at the triggering angle 80 degree in kilowatt is

    1.3195298

To find the power delivered at a2=30 degree:

The power delivered at the triggering angle 80 degree in kilowatt is

    2.0384507

-->|

```

Figure 3.8: calculate power delivered to the load when the triggering angle is 80 and 30 degree

ampere” , ISCR)

---

**Scilab code Exa 3.8** calculate power delivered to the load when the triggering angle

```

1 //Book name: Fundamentals of electrical drives by
  Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.8
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vab=208;//source voltage in volts
9 Vs=Vab/3^(1/2);//rms voltage in volts
10 Vm=Vs*2^(1/2);//maximum peak voltage in volts
11 R=10;//resistance of the circuit in ohm

```

```

12 a1=80; //triggering angle 1 in degree
13 a2=30; //triggering angle 2 in degree
14 if a1<60 then
15     disp(a1,'The current is discontinous')
16 else if (a2>60)
17     disp(a2,'The current is discontinous')
18 end
19 disp('To find the power delivered at a1=80 degree:')
20 B1=180;
21 p=((3*Vm^(2))/(8*pi*10))*(2*(B1-a1)*(pi/180)+sind
    (2*a1)-sind(2*B1)); //power delivered when
    triggering angle a1=180 degree
22 P=p*10^-3; //power interms of kilowatt
23 disp(P,'The power delivered at the triggering angle
    80 degree in kilowatt is')
24 disp('To find the power delivered at a2=30 degree:')
25 B2=120+a2;
26 p1=((3*Vm^(2))/(8*pi*10))*(2*(B2-a2)*(pi/180)+
    sind(2*a2)-sind(2*B2)); //power delivered when
    triggering angle a2=30 degree
27 P1=p1*10^-3; //power interms of kilowatt
28 disp(P1,'The power delivered at the triggering angle
    80 degree in kilowatt is')

```

---

**Scilab code Exa 3.9** calculate maximum average voltage and triggering angle and loa

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.9
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;

```

```

Scilab 5.5.2 Console

a)To find maximum average voltage across the load:

maximum average voltage across the load

    280.89869

b)To find the triggering angle at the average voltage of the load:

The triggering angle in degree is

    - 22.799939

c)To find load voltage when the triggering angle is -30 degree :

Load voltage when the triggering angle is -30 degree in volt is

    140.44935

-->|

```

Figure 3.9: calculate maximum average voltage and triggering angle and load voltage

```

7 clear;
8 Vab=208; //source voltage in volts
9 Vs=Vab/3^(1/2); //rms voltage in volts
10 Vm=Vs*2^(1/2); //maximum peak voltage in volts
11 disp('a)To find maximum average voltage across the
    load:')
12 Vavemax=(3*3^(1/2)*Vm)/%pi;
13 disp(Vavemax,'maximum average voltage across the
    load')
14 disp('b)To find the triggering angle at the average
    voltage of the load:')
15 xold=1; //assumed value
16 c=30; //constant value
17 x=asind((%pi/(3*sqrt(3)))-(cosd(xold+c)));
18 err=100; //assumed value
19 while(err>0.0001)
20     xnew=asind((%pi/(3*sqrt(3)))-(cosd(x+c)));
21     x=xnew;

```

```

Scilab 5.5.2 Console

a.To calculate on time and switching period:
The switching period and on time in milli second are 0.500000 0.150000
To calculate average voltage across the load:
The average voltage across the load is 24 volt
c.To calculate average voltage across the load:
The average voltage across the load is 56 volt
d.To calculate average current of the load:
The average current of the load is 6 ampere
e.To calculate load power:
The load power is 144 watt
-->

```

Figure 3.10: calculate on time and switching period average voltage across load and diode average current and load power

```

22     err=abs(xnew-xold);
23     xold=x;
24     end
25     disp(x,'The triggering angle in degree is')
26     disp('c)To find load voltage when the triggering
        angle is -30 degree :')
27     Vave=(3*3^(1/2)*Vm)/(2*pi);
28     disp(Vave,'Load voltage when the triggering angle is
        -30 degree in volt is')
29     //The part (b) answer given in the book is wrong

```

---

**Scilab code Exa 3.10** calculate on time and switching period average voltage across

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.10
4 //edition 1

```

```

5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 f=2; //switching
    frequency of chopper in kilohertz
9 Vs=80; //source voltage in
    volts
10 k=.3; //duty ratio
11 R=4; //load resistance in
    ohm
12 fprintf("\na.To calculate on time and switching
    period:")
13 t=1/f; //switching period in
    milli sec
14 ton=k*t; //on time in milli sec
15 fprintf("\nThe switching period and on time in milli
    second are %f %f",t,ton)
16 fprintf("\nTo calculate average voltage across the
    load:")
17 Vave=k*Vs;
18 fprintf("\nThe average voltage across the load is %d
    volt",Vave)
19 fprintf("\nc.To calculate average voltage across the
    load:")
20 Vdave=(1-k)*Vs; //obtained by integrating
    Vs with respect to ton and t
21 fprintf("\nThe average voltage across the load is %d
    volt",Vdave)
22 fprintf("\nd.To calculate average current of the
    load:")
23 Iave=Vave/R;
24 fprintf("\nThe average current of the load is %d
    ampere",Iave)
25 fprintf("\ne.To calculate load power:")
26 P=Vave*Iave;
27 fprintf("\nThe load power is %d watt",P)

```

---



The conduction period of each transistor in msec is

1.

-->

Figure 3.11: calculation of conduction period of each transistor

Scilab code Exa 3.12 calculation of conduction period of each transistor

```

1 //Book name: Fundamentals of electrical drives by
  Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.12
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 f=500; //frequency at
  the load side in Hz
9 t=1/f; //time for one
  cycle in sec
10 tseg=t/6; //time of the
  switching segment in sec
11 tcon=3*tseg; //conduction period
  of each transistor in sec
12 tcon1=tcon*10^3; //conduction period
  of each transistor in msec
13 disp(tcon1,'The conduction period of each transistor

```

```

The rms voltage applied to the motor winding with FWM in volts is:

61.237244

The rms voltage applied to the motor winding without FWM in volts is

122.47449

-->|

```

Figure 3.12: calculate rms voltage applied to the motor

in msec is ')

---

**Scilab code Exa 3.13** calculate rms voltage applied to the motor

```

1 //Book name: Fundamentals of electrical drives by
  Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.13
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 d=.25; //duty ratio
9 Vdc=150; //source voltage in
  volts
10 Vab=((2*d)/3)^(1/2)*Vdc; //rms voltage applied
  to the motor winding with FWM
11 disp(Vab,'The rms voltage applied to the motor
  winding with FWM in volts is:')
12 Vab1=(Vab/d^(1/2)); //rms voltage applied to
  the motor winding without FWM

```

```

The rms current delivered to the battery during charging is 1.186207 ampere
To find the power delivered to the battery during charging:
The power delivered to the battery during charging is 47.627706 degree
-->|

```

Figure 3.13: calculate the rms current and the power delivered to battery during charging

```

13 disp(Vab1, 'The rms voltage applied to the motor
    winding without FWM in volts is ')

```

---

Scilab code Exa 3.14 calculate the rms current and the power delivered to battery

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.14
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vs=110;
                                     //
    source voltage in volts
9 Vdc=150;
                                     //DC
    voltage in volts
10 Vm=Vs*2^(1/2);
    //maximum voltage in volts
11 a=90;

```

```

    //triggering angle in degree
12 R=1; //
    resistance in ohm
13 theta=asind(Vdc/Vm);
14 theta1=75; //
    approximated value of theta in degree
15 B=180-theta1; //The
    value of bete
16 gama=B-a; //
    conduction period in degree
17 VRrms=((Vdc^(2)*gama/180)+((Vm^(2)/(2*%pi))*(gama*(
    %pi/180)-(sind(2*B)-sind(2*a))/2)-((2*Vdc*Vm)/%pi
    )*(cosd(a)-cosd(B))))^(1/2);
18 Icrms=VRrms/R; //rms
    current
19 mprintf("\nThe rms current delivered to the battery
    during charging is %f ampere",Icrms)
20 mprintf("\nTo find the power delivered to the
    battery during charging:")
21 a1=((Vm/(R*%pi))*(((1-cosd(2*B))/2)-((1-cosd(2*a))
    /2)))-(((2*Vdc)/(R*%pi))*(sind(B)-sind(a)));
22 b1=((Vm/(R*%pi))*(gama*(%pi/180)+((sind(2*a)-sind(2*
    B))/2)))-(((2*Vdc)/(R*%pi))*(cosd(a)-cosd(B)));
23 pie1=atand(a1/b1);
24 I1crms=sqrt(a1^2+b1^2)/sqrt(2);
25 Ps=Vs*I1crms*cosd(pie1);
26 Ploss=Icrms*R;
27 Pcharge=Ps-Ploss;
28 mprintf("\nThe power delivered to the battery during
    charging is %f degree",Pcharge)

```

---

Scilab code Exa 3.15 calculate the rms current and the power delivered to battery

```

Scilab 5.5.2 Console
The total rms current during discharging is 70.000000 A
The power delivered to the ac source during discharging is 2.755219 kW
-->|

```

Figure 3.14: calculate the rms current and the power delivered to battery during discharging

```

1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.15
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vs=110;//source voltage in volts
9 Vdc=150;//DC voltage in volts
10 Vm=Vs*2^(1/2);//maximum voltage in volts
11 alphamin=0;//triggering angle in degree
12 R=1;//resistance in ohm
13 Beta=180;//The value of bete
14 gama=Beta-alphamin;//conduction period in degree
15 VRrms=sqrt(Vdc^(2)+((Vs*2^(1/2))^(2)/2)-((4*Vdc*Vm)/
   %pi));
16 VRrms=ceil(VRrms)
17 Idrms=VRrms/R;
18 mprintf("\nThe total rms current during discharging
   is %f A",Idrms)
19 a1=((Vm/(R*%pi))*(((1-cosd(2*Beta))/2)-((1-cosd(2*
   alphamin))/2)))-((2*Vdc)/(R*%pi))*(sind(Beta)-
   sind(alphamin));
20 b1=((4*Vdc)/(R*%pi))-(Vm/R);
21 pie1=atand(a1/b1);
22 I1drms=sqrt((a1^2+b1^2)/2);//rms value of

```

```

Scilab 5.5.2 Console
a.To calculate minimum triggering angle and associated conduction period:
The minimum triggering angle is 2 degree and the associated time period is 120 degree
To compute the average charging current for the minimum triggering angle:
The average charging current of minimum triggering angle is 11.736466 A
-->

```

Figure 3.15: calculate minimum triggering angle and associated conduction period and average charging current

```

    fundamental component
23 Pac=Vs*I1drms*cosd(pie1);
24 Pac=Pac*10(-3);
25 mprintf("\n\nThe power delivered to the ac source
    during discharging is %f kW",Pac)

```

---

**Scilab code Exa 3.16** calculate minimum triggering angle and associated conduction

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 3
3 //example 3.16
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vdc=250;
9 Vs=208;//line to line ac voltage
10 R=3;//system resistance between battery bank and
    source in ohm
11 Beta=122;
12 Vmax=(sqrt(2)*Vs)/sqrt(3);

```

```

13 mprintf(" \na.To calculate minimum triggering angle
    and associated conduction period:")
14 alphamin=60-asind(Vdc/(sqrt(3)*Vmax));
15 alphamin=ceil(alphamin);
16 gama=Beta-alphamin;
17 mprintf(" \nThe minimum triggering angle is %d degree
    and the associated time period is %d degree",
    alphamin,gama)
18 mprintf(" \nTo compute the average charging current
    for the minimum triggering angle:")
19 VR=Vdc+(((9*Vmax)/(2*%pi))*cosd(alphamin+150));
20 l=(((9*Vmax)/(2*%pi))*cosd(alphamin+150));
21 IRave=VR/R;
22 mprintf(" \nThe average charging current of minimum
    triggering angle is %f A",IRave)
23 //The answers vary due to round off error

```

---

# Chapter 4

## Joint speed torque characterstics of electric motor and mechanical loads

Scilab code Exa 4.1 compute the power consumed by the load

```
1 //Book name: Fundamentals of electrical drives by  
    Mohamad A. El- Sharkawi
```

Scilab 5.5.2 Console

```
The power consumed by the motor in kilowatt is:
```

```
2073.7049
```

```
-->
```

Figure 4.1: compute the power consumed by the load



```

2 //chapter 4
3 //example 4.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 m=5000; //mass of
    the electric bus in kg
9 d=1; //diameter
    of the wheel in m
10 r=d/2; //radius of
    the wheel in m
11 v=50; //speed of
    the bus going to uphill in kg/hr
12 a=30; //slope of the
    hill in degree
13 u=0.4; //friction
    coefficient
14 g=9.8; //gravitational
    acceleration
15 Fg=m*g; //gravitational
    force in newton(N)
16 F=Fg*cosd(a); //normal force in
    newton(N)
17 Fl=Fg*sind(a); //load pulling force
    in newton (N)
18 Fr=u*F; //friction force in
    newton(N)
19 Fm=Fl+Fr; //total force seen by
    motor in newton(N)
20 Tm=Fm*r; //Torque seen by the
    motor in Nm
21 omega=v/r; //angular speed
22 Pm=Tm*omega; //power consumed by
    the motor in watt
23 Pm=Pm*10^-3; //power consumed by the
    motor in kilowatt
24 disp(Pm,'The power consumed by the motor in kilowatt

```

is : ')

---

# Chapter 5

## speed torque characteristics of electric motor

Scilab code Exa 5.1 calculate rated torque starting torque and starting current

```
1 //Book name: Fundamentals of electrical drives by
  Mohamad A. El- Sharkawi
2 //chapter 5
3 //example 5.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 kpie=3; //flux in voltsec
9 Vt=600; //voltage in volts
10 Ra=2; //armature resistance in
  ohms
11 Ia=5; //armature current at
  fullload in ampere
12 Td=kpie*Ia; //rated torque in Nm
13 disp(Td, 'The rated torque in Nm is ')
14 Tst=(Vt*kpie)/Ra; //starting torque
```

```
Scilab 5.5.2 Console

The rated torque in Nm is

15.

The starting torque in Nm is

900.

The starting current in ampere is

300.

-->
```

Figure 5.1: caculate rated torque starting torque and starting current

```
15 disp(Tst, 'The starting torque in Nm is ')
16 Ist=Vt/Ra; //starting current
17 disp(Ist, 'The starting current in ampere is ')
```

---

### Scilab code Exa 5.2 compute the motor efficiency

```
Scilab 5.5.2 Console

The efficiency of the motor is 89 percentage

-->
```

Figure 5.2: compute the motor efficiency

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 5
3 //example 5.2
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 l=50; //load in hp
9 f=60; //frequency in
    hertz
10 n=1764; //full load speed in
    rpm
11 ns=1800; //synchronous speed
    of motor in rpm
12 Pr=.950; //rotational loss in
    kilowatts
13 Pcu=1.600; //stator copper loss in
    kilowatt
14 Pi=1.200; //iron loss in kilowatt
15 Pout=1/1.34; //output power at full
    load is 50 hp in kilowatt
16 Pd=Pout+Pr; //power developed in
    kilowatt
17 s=(ns-n)/ns; //slip of the motor
18 Pg=Pd/(1-s);
19 Pin=Pg+Pcu+Pi; //input power in kilowatt
20 efficiency=Pout/Pin; //motor efficiency
21 efficiency=efficiency*100; //efficiency in percentage
22 mprintf("The efficiency of the motor is %d
    percentage",efficiency)

```

---

Scilab code Exa 5.3 calculate speed of motor copper loss starting torque of the mo

Scilab 5.5.2 Console

a) . Motor speed :

The speed of the motor at full load in rpm is

1764.

b) .Copper loss of the rotor

The copper loss of the rotor in watt is

761.49863

c) .Starting torque

The starting torque in Nm is

100.99689

-->

Figure 5.3: calculate speed of motor copper loss starting torque of the motor

```

1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 5
3 //example 5.3
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 l=50; //load in hp
9 f=60; //frequency in hertz
10 V=440; //voltage of the motor in volts
11 p=4; //Number of poles of the motor
12 Tmax=2.5; //maximum torque of the motor
13 T=1; //motor torque
14 smax=0.1; //maximum slip
15 ns=(120*f)/p; //synchronous speed in rpm
16 disp('a). Motor speed :')
17 s=(T/Tmax)*(smax/2); //the equation is obtained from
   the equation  $T=3V^2s/wsR2$ 
18 n=ns*(1-s); //speed of the motor in rpm
19 disp(n, 'The speed of the motor at full load in rpm
   is ')
20 disp('b).Copper loss of the rotor')
21 Pd=1/1.34; //power developed or Pout in kilowatt
22 Pcu2=Pd*(s/(1-s)); //copper loss in kilowatt which is
   obtained from two equations  $Pcu2=Pg*s, Pd=Pg*(1-s)$ 
23 Pcu=Pcu2*103; //copper loss in watt
24 disp(Pcu, 'The copper loss of the rotor in watt is')
25 disp('c).Starting torque')
26 //At starting slip s=1
27 omega=(2*pi*n)/f;
28 Pout=Pd*103; //Pout value in watts
29 Tst=(smax2*Pout)/(s*omega);
30 disp(Tst, 'The starting torque in Nm is')
31 //The answers vary due to round off error

```

---

Scilab code Exa 5.4 calculate the change in starting torque and resistance added to

```
1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 5
3 //example 5.4
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 R1=3; //stator
   resistance in ohm
9 R2=2; //rotor
   resistance referred to stator in ohm
10 Xeq=10; //equivalent
   inductive reactance in ohm
11 l=10; //voltage reduction
   in percentage
12 V=1; //assumed value of V
13 TA=(1*V)^2; //starting torque at
   the rated voltage
14 TB=(0.9*V)^2; //starting torque
   after 10% voltage reduction
15 r=1-TB; //reduction in starting
   torque
16 r=r*100; //reduction in starting
   torque in percentage
17 mprintf("\nThe reduction in starting torque is %f
   percentage",r)
18 Radd=sqrt(R1^(2)+Xeq^(2))-R2;
19 mprintf("\nThe resistance added to the rotor circuit
   to achieve the maximum torque is %f",Radd)
20 //The answer given in the book is wrong
```

---



```
Scilab 5.5.2 Console

The reduction in starting torque is 19.000000 percentage
The resistance added to the rotor circuit to achieve the maximum torque is 8.440307
-->
```

Figure 5.4: calculate the change in starting torque and resistance added to achieve maximum torque

```
Scilab 5.5.2 Console

The total reactive power for .95 power factor lagging in KVAR is

13.147364

The excitation current required to improve overall power factor of the plant in A is

14.433723

-->
```

Figure 5.5: compute the excitation current to improve overall power factor

**Scilab code Exa 5.5** compute the excitation current to improve overall power factor

```
1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 5
3 //example 5.5
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 P=40; //load of an
```

```

    industrial plant in Mw
9  pf=.85;                                //power factor
    lagging
10 pfnew=.95                               //To improve new
    power factor
11 V=5000;                                 //motor rated
    voltage in volts
12 Xs=5;                                   //synchronous
    reactance in ohm
13 c=200;                                  //constant value
    given
14 Vt=V/3^(1/2);
15 a=acosd(pf);                            //power factor angle of
    the load in degree
16 Ql=P*tand(a);                           //load reactive power
    in KVAR
17 Qtot=P*tand(acosd(pfnew));              //total reactive
    power for .95 power factor lagging
18 disp(Qtot,'The total reactive power for .95 power
    factor lagging in KVAR is ')
19 Qm=Qtot-Ql;
20 Vt=(V/sqrt(3));
21 Ef=((Qm*Xs)/(3*Vt))+Vt;
22 If=Ef/c;
23 disp(If,'The excitation current required to improve
    overall power factor of the plant in A is ')

```

---

**Scilab code Exa 5.6** compute the minimum excitation that the machine must maintain

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 5
3 //example 5.6

```

The minimum excitation that machine must maintain to provide the needed torque in volt is:

946.3301

-->

Figure 5.6: compute the minimum excitation that the machine must maintain to provide the needed torque

```

4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=2300; //rated voltage of
    the synchronous motor in volt
9 Vt=V/3^(1/2);
10 f=60; //frequency in Hertz
11 p=6; //number of poles
12 Tl=5000; //constant torque of the
    load in Nm
13 Xs=6; //synchronous reactance
    of the motor in ohm
14 ns=(120*f)/p; //synchronous speed of
    the motor in rpm
15 omegas=(2*pi*ns)/60;
16 Ef=(Tl*omegas*Xs)/(3*Vt); //The minimum
    excitation that machine must maintain to provide
    the needed torque
17 disp(Ef,'The minimum excitation that machine must
    maintain to provide the needed torque in volt is:
    ')

```

---

# Chapter 6

## speed control of direct current motors

Scilab code Exa 6.1 calculate added resistance to reduce the speed by 50 percentag

```
1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 6
3 //example 6.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vs=150;//source voltage of DC shunt motor in volt
9 n1=1200;//synchronous speed in rpm
10 Ra=1;//armature resistance in ohm
11 Rf=150;//field resistance in ohm
12 I=10;//line current in ampere
13 If=(Vs/Rf);//Field current before adding the
   resistance in ampere
14 disp('a) Calculate the resistance that should be
   added to the armature circuit to reduce the speed
```

```

Scilab 5.5.2 Console

a) Calculate the resistance that should be added to the armature circuit to reduce the speed by 50%

The resistance which should be added to reduce the speed by 50% in ohm is:

7.8333333

b) To calculate the motor efficiency

The efficiency of the motor without adding resistance in % is:

77.9333333

The efficiency of the motor with adding resistance in % is:

35.6333333

c) To calculate the resistance to be added to the armature for the holding operation

The resistance to be added to the armature for the holding operation in ohm is:

15.666667

-->

```

Figure 6.1: calculate added resistance to reduce the speed by 50 percentage and efficiency and resistance added to operate the motor in holding condition

```

    by 50%')
15 //consider that the motoring point 1 represents
    without adding resistance & point 2 for the
    operating point at 50% load reduction
16 Ia1=I-If;//armature current without adding
    resistance
17 n2=0.5*n1;//50% speed is reduced
18 Ea1=Vs-(Ia1*Ra);//speed equation at operating point
    1
19 Radd=Ea1/(2*Ia1);//Obtained from the equation of Ea1
    /Ea2=n1/n2
20 disp(Radd,'The resistance which should be added to
    reduce the speed by 50% in ohm is:')
21 disp('b)To calculate the motor efficiency')
22 Prloss=100;//rotational loss in watt
23 Pfloss=If^(2)*Rf;//field loss in watt
24 Paloss=Ia1^(2)*Ra//armature losses in watt
25 Pin=Vs*I;//Input power in watt
26 Ploss=Prloss+Pfloss+Paloss;//Total losses before

```

```

    adding armature resistance in watt
27 Ploss1=Prloss+Pfloss+Paloss*(Ra+Radd); //Total losses
    after adding armature resistance in watt
28 eff=((Pin-Ploss)/Pin)*100; //efficiency of the motor
    without adding resistance in %
29 eff1=((Pin-Ploss1)/Pin)*100; //efficiency of the
    motor with adding resistance in %
30 disp(eff, 'The efficiency of the motor without adding
    resistance in % is:')
31 disp(eff1, 'The efficiency of the motor with adding
    resistance in % is:')
32 disp('c)To calculate the resistance to be added to
    the armature for the holding operation')
33 //set motor speed equal to zero
34 Radd=(Vs/Ia1)-Ra;
35 disp(Radd, 'The resistance to be added to the
    armature for the holding operation in ohm is:')

```

---

**Scilab code Exa 6.3** calculate armature current and motor speed and value of added

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 6
3 //example 6.3
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Vs=150; //source voltage of DC shunt motor in volt
9 n1=1200; //synchronous speed in rpm
10 Ra=2; //armature resistance in ohm
11 Rf=150; //field resistance in ohm
12 I=10; //line current in ampere

```

The armature current after inserting the resistance in ampere is:

11.25

The motor speed in rpm is:

1448.8636

The value of added resistance in ohm is:

37.5

The extra field loss due to the addition of resistance in watt is:

24.

-->

Figure 6.2: calculate armature current and motor speed and value of added resistance and extra field loss

```

13 If1=(Vs/Rf); //Field current before adding the
    resistance in ampere
14 //Assume the resistance added in the field circuit
    to reduce the field current by 20%
15 If2=.8; //Field current after adding the resistance
    in ampere
16 Ia1=I-If1; //Armature current before inserting the
    resistance in ampere
17 Ia2=(If1*Ia1)/If2; //Armature current after inserting
    the resistance in ampere
18 disp(Ia2,'The armature current after inserting the
    resistance in ampere is:')
19 Ea1=Vs-(Ia1*Ra);
20 Ea2=Vs-(Ia2*Ra);
21 n2=(If1*n1*Ea2)/(Ea1*If2);
22 disp(n2,'The motor speed in rpm is:')
23 Radd=(Vs-(If2*Rf))/If2;
24 disp(Radd,'The value of added resistance in ohm is:')
    )

```

```
Scilab 5.5.2 Console

The speed of the motor in rpm is:

    154.8879

The power developed by the motor in terms of watt is:

    162.19823

-->
```

Figure 6.3: calculate the motor speed and the developed power

```
25 P=If2^(2)*Radd;
26 disp(P, 'The extra field loss due to the addition of
    resistance in watt is:')
```

---

**Scilab code Exa 6.4** calculate the motor speed and the developed power

```
1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 6
3 //example 6.4
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 L=1; //load of shunt motor in hp
9 T=10; //constant torque of motor in Nm
10 Ra=5; //armature resistance of the motor in ohm
11 KQ=2.5; //The field constant in V sec
```



```
Scilab 5.5.2 Console
```

```
The speed of the motor is 246.561146 rpm  
The power developed by the motor is 258.198228 watt  
-->|
```

Figure 6.4: calculate the motor speed and the power delivered to the load

```
12 V=120; //source voltage in volt  
13 f=60; //supply frequency in Hertz  
14 a=60; //trigerring angle of the converter in degree  
15 b=150; //conduction period in degree  
16 Iave=T/KQ; //average current in ampere  
17 Vm=V*2^(1/2);  
18 W=((Vm/(2*%pi))*(cosd(a)-cosd(b+a))-(Iave*Ra))/((b  
    /360)*KQ); //angular speed of the motor  
19 n=W*(f/(2*%pi));  
20 disp(n, 'The speed of the motor in rpm is:')  
21 Pd=KQ*W*Iave; //power developed by the motor  
22 disp(Pd, 'The power developed by the motor in terms  
    of watt is:')
```

---

Scilab code Exa 6.5 calculate the motor speed and the power delivered to the load

```
1 //Book name: Fundamentals of electrical drives by  
    Mohamad A. El- Sharkawi  
2 //chapter 6  
3 //example 6.5  
4 //edition 1  
5 //publisher and place:Nelson Engineering  
6 clc;
```

```
The triggering angle of the motor is 21.731115 degree
-->
```

Figure 6.5: calculate the triggering angle of the motor

```
7 clear;
8 L=1; //load of shunt motor in hp
9 T=10; //constant torque of motor in Nm
10 Ra=5; //armature resistance of the motor in ohm
11 KQ=2.5; //The field constant in V sec
12 V=120; //source voltage in volt
13 f=60; //supply frequency in Hertz
14 a=60; //trigerring angle of the converter in degree
15 b=150; //conduction period in degree
16 Iave=T/KQ; //average current in ampere
17 Vm=V*2^(1/2);
18 W=((Vm/%pi)*(cosd(a)-cosd(b+a))-(Iave*Ra))/((b/180)*
    KQ); //angular speed of the motor
19 n=W*(60/(2*%pi));
20 mprintf("\nThe speed of the motor is %f rpm",n)
21 Pd=KQ*W*Iave; //power developed by the motor
22 mprintf("\nThe power developed by the motor is %f
    watt",Pd)
```

---

Scilab code Exa 6.6 calculate the triggering angle of the motor

```
1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 6
3 //example 6.6
```

```

Scilab 5.5.2 Console

Calculate the field current:
The field current is 15.554275 A
Calculate the motor voltage:
The motor voltage is 239.352296 volt
Calculate the motor speed :
The speed of the motor is 739.178134 rpm
-->

```

Figure 6.6: calculate field current motor voltage and speed

```

4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 T=60; //Constant load torque in Nm
9 V=120; //supply voltage in volt
10 KQ=2.5; //Field constant of the motor
11 Ra=2; //Armature resistance in ohm
12 n=200; //speed of the motor in rpm
13 Vm=V*2^(1/2); //maximum voltage in volt
14 w=(2*pi*n)/T; //angular speed
15 Iave=T/KQ;
16 b=((pi/(2*Vm))*((Ra*Iave)+(KQ*w)));
17 alpha=acosd(b);
18 mprintf("\nThe triggering angle of the motor is %f
           degree",alpha)

```

---

Scilab code Exa 6.7 calculate field current motor voltage and speed

```

1 //Book name: Fundamentals of electrical drives by

```

```

Mohamad A. El- Sharkawi
2 //chapter 6
3 //example 6.7
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ra=2;//armature resistance in ohm
9 Rf=3;//field resistance in ohm
10 V=320;//terminal voltage in volt
11 T=60;//full load torque in Nm
12 n=600;//motor speed in rpm
13 mprintf("\nCalculate the field current:")
14 KC=0.248;//calculated by solving two equations
15 Ia=sqrt(T/KC);
16 mprintf("\nThe field current is %f A",Ia)
17 mprintf("\nCalculate the motor voltage:")
18 n1=400;
19 omega1=(2*pi*n1)/T;
20 Vt=Ia*(Ra+Rf+(KC*omega1));
21 mprintf("\nThe motor voltage is %f volt",Vt)
22 mprintf("\nCalculate the motor speed :")
23 AR=Ra/Rf;
24 Ia=sqrt(T/(KC*AR));
25 w=(V/(KC*AR*Ia))-((Ra+(AR*Rf))/(KC*AR));
26 n2=(w*T)/(2*pi);
27 mprintf("\nThe speed of the motor is %f rpm",n2)

```

---

# Chapter 7

## speed control of induction motors

Scilab code Exa 7.1 compute the added resistance to reduce the speed by 20 percent

```
1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 p=6;//number of poles
10 f=60;//frequency in hertz
11 Pout=30*746;//rated output voltage in volts
12 R1=0.5;//stator resistance in ohm
13 R2=0.5;//rotor resistance referred to stator in ohm
14 Protational=500;//rotational loss in watt
15 Pcu=600;//core losses in watt
16 c=0.05;//cost of energy
```

```

The speed of the motor is 1151 rpm
The efficiency of the motor without added resistance is 88 percentage
The resistance added to reduce 20 percentage of the speed is 2.359865 ohm
The efficiency of the motor with added resistance is 70 percentage
The annual cost of the operating motor is $1189.760000
-->|

```

Figure 7.1: compute the added resistance to reduce the speed by 20 percent and motor efficiency with and without added resistance and annual cost of operating motor

```

17 t1=100; //time which the motor operates in a week
18 Pd=Pout+Protational; //developed power in watt
19 a=1; // the s^2 value from the equation s^2-s+0.039
20 b=-1; //the s value from the equation s^2-s+0.039
21 c=0.039; //the constant value from the equation s^2-s
    +0.039
22 s1=(-(b)+sqrt((b)^2-(4*a*c)))/(2*a);
23 s2=(-(b)-sqrt((b)^2-(4*a*c)))/(2*a); //roots to find
    the value of s from the equation s^2-s+0.03
24 s=s2; //s1 is very large hence neglected thus slip=s2
25 a1=120; //constant value in the formula
26 ns=(a1*f)/p; //synchronous speed in rpm
27 n=ns*(1-s);
28 mprintf("\nThe speed of the motor is %d rpm",n)
29 I2=sqrt((Pd*s)/(3*R2*(1-s))); //motor current in amps
30 Pwinding=3*I2^(2)*(R1+R2);
31 Pin=Pd+Pwinding+Pcu;
32 eta=Pout/Pin; //efficiency of the motor
33 eta=eta*100; //efficiency in percentage
34 mprintf("\nThe efficiency of the motor without added
    resistance is %d percentage",eta)
35 nnew=0.8*n; //speed after 20% reduction
36 snew=(ns-nnew)/ns;
37 rmsnew=nnew/60; //speed in rps

```

```
Scilab 5.5.2 Console
The magnitude of injected voltage is 8.249252 volt
The power delivered by the source of injected voltage is 536.991342 watt
-->
```

Figure 7.2: calculate the magnitude of the injected voltage and the power delivered by the source of injected voltage

```
38 omegadnew=(2*%pi*rmsnew);
39 rps=n/60; //speed in rps
40 omega=(2*%pi*rps);
41 Pdnew=(Pd*omegadnew)/omega;
42 Radd=R2*((snew-s)/s); //resistance added to reduce 20
    % of the speed
43 mprintf("\nThe resistance added to reduce 20
    percentage of the speed is %f ohm",Radd)
44 I2new=sqrt((Pdnew*snew)/(3*(R2+Radd)*(1-snew)))
45 Pwindingnew=3*I2^(2)*(R1+R2+Radd);
46 Pinnew=Pdnew+Pwindingnew+Pcu;
47 Poutnew=Pdnew-Protational;
48 etanew=Poutnew/Pinnew;
49 etanew=etanew*100;
50 mprintf("\nThe efficiency of the motor with added
    resistance is %d percentage",etanew)
51 Padd=3*I2^(2)*Radd;
52 Padd=Padd*10^(-3);
53 t=100*52; //total hours of operation in one year
54 C=Padd*t*c;
55 mprintf("\nThe annual cost of the operating motor is
    $%f",C)
56 //The answer may vary due to roundoff error
```

Scilab code Exa 7.2 calculate the magnitude of the injected voltage and the power

```
1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.2
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480; //terminal voltage in volt
9 p=4; //number of poles
10 f=60; //frequency in hertz
11 Td=60; //constant torque load in Nm
12 R1=0.4;
13 R2=0.1;
14 Xeq=4;
15 N1=2;
16 N2=1;
17 n=1000; //speed of the motor in rpm
18 a1=120;
19 ns=(a1*f)/p;
20 s=(ns-n)/ns;
21 R21=R2*(N1/N2)^(2);
22 theta=atand(Xeq/(R1+(R21/s)));
23 a=0.05;
24 b=8;
25 c=-80.74;
26 Vi11=(-b+sqrt(8^2-(4*a*c)))/(2*a); //obtained from
   the equation  $0.05 Vi^2+8Vi-80.74$ 
27 Vi12=(-b-sqrt(8^2-(4*a*c)))/(2*a); //obtained from
   the equation  $0.05 Vi^2+8Vi-80.74$ 
28 Vi1=Vi11; //because negative voltage is neglected
29 Vi=(Vi1*N2)/N1;
30 c1=122; //calculated constant values of the equation
31 c2=1.85; //calculated constant values of the equation
32 I2=(c1-Vi1)/c2;
33 V1=sqrt(3)*Vi; //line to line injected voltage
```



```
Scilab 5.5.2 Console
a)Without injected voltage Vi=0v
The starting current without injected voltage is 68.000000 A
The starting torque without injected voltage is 29.437298 Nm
b)With injected voltage Vi=9.5v
The starting current with injected voltage is 65.607743 A
The starting torque with injected voltage is 29.418859 Nm
-->
```

Figure 7.3: calculate the starting current and starting torque with and without the voltage

```
34 mprintf("\\nThe magnitude of injected voltage is %f
    volt",V1)
35 Pr=3*I2*Vi1*cosd(theta);
36 mprintf("\\nThe power delivered by the source of
    injected voltage is %f watt",Pr)
37 //The answers vary due to round off error
```

---

**Scilab code Exa 7.3** calculate the starting current and starting torque with and wi

```
1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.3
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 p=4;//number of poles
10 f=60;//frequency in hertz
```

```

11 Tl=60; //load torque in Nm
12 R1=0.4;
13 R2=0.1;
14 Xeq=4;
15 N1=2; //obtained from the equation N1/N2=2
16 n=1000; //motor speed in rpm
17 a=120;
18 ns=(a*f)/p;
19 rps=ns/60;
20 omegas=(2*pi*rps);
21 mprintf("\na) Without injected voltage Vi=0v")
22 Vs=V/sqrt(3);
23 R21=R2*(N1^(2));
24 I2st=Vs/sqrt((R1+R21)^(2)+Xeq^(2)); //starting
    current in A
25 I2st=ceil(I2st) //rounding off the starting current
26 Tst=(3*I2st^(2)*R1)/omegas; //staring torque
27 mprintf("\nThe starting current without injected
    voltage is %f A", I2st)
28 mprintf("\nThe starting torque without injected
    voltage is %f Nm", Tst)
29 mprintf("\nb) With injected voltage Vi=9.5v")
30 Vi=9.5; //injected voltage in volt
31 I2st1=(Vs-Vi)/sqrt((R1+R21)^(2)+Xeq^(2)); //starting
    current with injected resistance in A
32 thetar=atand(Xeq/(R1+R21));
33 Tst1=(3/omegas)*((I2st1^2*R1)+(I2st*Vi)*cosd(thetar)
    );
34 mprintf("\nThe starting current with injected
    voltage is %f A", I2st1)
35 mprintf("\nThe starting torque with injected voltage
    is %f Nm", Tst1)

```

---

```

To find speed of the motor:
The speed of the motor is 600.000000 rpm
To compute current in DC link:
The current in DC link is 61.242537 A
To compute rotor rms current:
The rotor rms current is 50.004322 A
To compute stator rms current:
The stator rms current is 50.004322 A
To compute power returned to the source:
The power returned to the source is 19.849556 watt
To compute the losses when additional resistance is added:
The power losses when additional resistance added is 19.849556 watt
-->|

```

Figure 7.4: calculate the motor speed and current in dc link and rotor and stator rms current and power returned back to the source and additional losses

**Scilab code Exa 7.4** calculate the motor speed and current in dc link and rotor and

```

1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.4
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 p=6;//number of poles
10 f=60;//frequency in hertz
11 Tout=300;//constant load torque in Nm
12 N1=1;
13 N2=1;
14 Prot=1e3;//rotational power in watt
15 alpha=120;//trigerring angle in degree
16 mprintf(" \nTo find speed of the motor:")

```

```

17 a=120; //constant value
18 ns=(a*f)/p;
19 n=ns*(1+((N1/N2)*cosd(alpha)));
20 mprintf("\nThe speed of the motor is %f rpm",n)
21 s=(ns-n)/ns;
22 mprintf("\nTo compute current in DC link:")
23 rps=n/60; //speed in rps
24 omega=(2*pi*rps);
25 Pout=Tout*omega;
26 Pd=Pout+Prot;
27 K=(3*sqrt(2))/pi;
28 I=(Pd/(1-s))/(K*V);
29 mprintf("\nThe current in DC link is %f A",I)
30 mprintf("\nTo compute rotor rms current:")
31 itr=sqrt(2/3); //solved integration value
32 I2=itr*I;
33 mprintf("\nThe rotor rms current is %f A",I2)
34 mprintf("\nTo compute stator rms current:")
35 I1=(N1/N2)*I2
36 mprintf("\nThe stator rms current is %f A",I1)
37 mprintf("\nTo compute power returned to the source:")
    )
38 Pr=Pd;
39 Pr=Pr*10^(-3);
40 mprintf("\nThe power returned to the source is %f
    watt",Pr)
41 mprintf("\nTo compute the losses when additional
    resistance is added:")
42 Td=Pd/omega;
43 rpss=ns/60; //speed in rps
44 omegas=(2*pi*rpss);
45 Radd=(V^2*s)/(Td*omegas); //additional resistance
    added in ohm
46 I2=sqrt(((s/(1-s))*(Pd/3))/Radd); //rotor current
47 Padd=3*I2^2*Radd; //additional power loss
48 Padd=Padd*10^(-3);
49 mprintf("\nThe power losses when additional
    resistance added is %f watt",Padd)

```

```
Scilab 5.5.2 Console
The speed of the motor after the reduction of the rated voltage is 1139 rpm
-->
```

Figure 7.5: calculate the motor speed at full voltage

---

Scilab code Exa 7.5 calculate the motor speed at full voltage

```
1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.5
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 p=6;//number of poles
10 Pout=30*746;//output power interms of watt
11 f=60;//frequency in hertz
12 R1=0.5;//stator resistance in ohm
13 R2=0.5;//rotor resistance reffered to stator in ohm
14 ns=1200;//synchronus speed in rpm
15 rps=ns/60;
16 omegas=(2*%pi*rps);//angular synchronous speed
17 Td=120;//load torque constant
18 s=(Td*omegas*R2)/V^2;
19 n=ns*(1-s);//the speed at full voltage in rpm
20 n=ceil(n)
21 Vnew=0.8*V;//when voltage is reduced by 20%
```

```

To compute the maximum frequency of the supply voltage:
The maximum frequency of the supply voltage is 67.702750 Hz
To calculate the motor current at f and fmax:
The motor current at 60 Hz is 23.676654 A
The motor current at 67.7Hz is 42.444229 A
To calculate the power delivered to the load at f and fmax:
The power delivered to the load at 60Hz is 21.991149 Kw
The power delivered to the load at 67.7Hz is 23.828538 Kw
-->

```

Figure 7.6: compute maximum frequency and then motor current and power delivered at 60 Hz and at maximum frequency

```

22 snew=(V^2*s)/Vnew^2; //new slip after the reduction
    of 20% of the rated voltage
23 nnew=ns*(1-snew); //new speed of the motor in rpm
24 nnew=ceil(nnew)
25 mprintf("The speed of the motor after the reduction
    of the rated voltage is %d rpm",nnew)

```

---

Scilab code Exa 7.6 compute maximum frequency and then motor current and power del

```

1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.6
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480; //terminal voltage in volt

```

```

 9 p=2; //number of poles
10 f=60; //frequency in hertz
11 Xeq=4; //inductive reactance in ohm
12 R1=0.2; //stator resistance in ohm
13 R2=0.3; //rotor resistance referred to stator in ohm
14 Td=60; //driving constant load torque in Nm
15 n=3500; //speed of the motor in rpm
16 a=120; //constant value
17 ns=(a*f)/p; //synchronous speed in rpm
18 mprintf("\nTo compute the maximum frequency of the
    supply voltage:")
19 Tmax=Td;
20 rpss=ns/60;
21 omegas=(2*%pi*rpss);
22 fmax=sqrt((V^2*f^2)/(Tmax*2*omegas*4));
23 mprintf("\nThe maximum frequency of the supply
    voltage is %f Hz",fmax)
24 mprintf("\nTo calculate the motor current at f and
    fmax:")
25 s=(ns-n)/ns; //slip at 60Hz
26 Vs=V/sqrt(3);
27 I2=Vs/sqrt((R1+(R2/s))^2+Xeq^2);
28 mprintf("\nThe motor current at 60 Hz is %f A",I2)
29 Xeqmax=(fmax/f)*Xeq;
30 smax=R2/sqrt(R1^2+Xeqmax^2);
31 nmax=((a*fmax)/p)*(1-smax);
32 I2max=Vs/sqrt((R1+(R2/smax))^2+Xeqmax^2);
33 mprintf("\nThe motor current at 67.7Hz is %f A",
    I2max)
34 mprintf("\nTo calculate the power delivered to the
    load at f and fmax:")
35 rps=n/60;
36 omega=(2*%pi*rps);
37 Pd=Td*omega; //developed power at 60Hz
38 Pd=Pd*10^(-3); //developed power in kilowatt
39 mprintf("\nThe power delivered to the load at 60Hz
    is %f Kw",Pd)
40 rpsmax=nmax/60;

```

```

The new motor speed at 50Hz is 2926.368922 rpm
The starting current at 50Hz is 82.218624 A
-->

```

Figure 7.7: compute the motor speed and the starting current if the frequency decreased to 50 Hz

```

41 omegamax=(2*%pi*rpsmax);
42 Pdmax=Td*omegamax;//developed power at 67.7Hz
43 Pdmax=Pdmax*10^(-3);//developed power in kilowatt
44 mprintf("\nThe power delivered to the load at 67.7Hz
           is %f Kw",Pdmax)

```

---

**Scilab code Exa 7.7** compute the motor speed and the starting current if the frequency

```

1 //Book Name: Fundamentals of electrical drives by
  Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.7
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 p=2;//number of poles
10 fst=60;//frequency in hertz
11 f=50;//decreased frequency in Hz
12 Xeq=4;//inductive reactance in ohm
13 R1=0.2;//stator resistance in ohm
14 R2=0.3;//rotor resistance referred to stator in ohm

```



```

To compute the starting current at 60Hz,480v:
The starting current at 60Hz,480v is 68.747028 A
To compute the starting current at 50Hz,400v:
The starting current at 50Hz,400v is 68.515520 A
The starting current is almost unchanged due to the v/f control
-->

```

Figure 7.8: compute the starting current for a constant v by f control

```

15 Td=60; //driving constant load torque in Nm
16 n=3500; //speed of the motor in rpm
17 ns=(120*f)/p; //synchronous speed in rpm
18 Vs=V/sqrt(3);
19 rps=ns/60;
20 omegas=(2*pi*rps);
21 s=(Td*omegas*R2)/V^2;
22 n=ns*(1-s); //the new motor speed at 50Hz in rpm
23 mprintf("\nThe new motor speed at 50Hz is %f rpm",n)
24 I2st=Vs/sqrt((R1+R2)^(2)+Xeq^(2)); //starting current
    in A
25 Xeqnew=(f/fst)*Xeq; //inductive reactance at 50Hz
26 I2stnew=Vs/sqrt((R1+R2)^(2)+Xeqnew^(2)); //starting
    current at 50Hz in A
27 mprintf("\nThe starting current at 50Hz is %f A",
    I2stnew)

```

---

Scilab code Exa 7.8 compute the starting current for a constant v by f control

```

1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 7

```

```

3 //example 7.8
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 p=2;//number of poles
10 f=60;//frequency in hertz
11 fd=50;//decreased frequency in Hz
12 Xeq=4;//inductive reactance in ohm
13 R1=0.2;//stator resistance in ohm
14 R2=0.3;//rotor resistance referred to stator in ohm
15 Td=60;//driving constant load torque in Nm
16 n=3500;//speed of the motor in rpm
17 VFR=V/f;//voltage frequency ratio
18 Vnew=fd*VFR;
19 a=120;//constant value
20 ns=(a*fd)/p;//synchronous speed in rpm
21 Vs=V/sqrt(3);
22 rps=n/60;
23 omegas=(2*pi*rps);
24 s=(Td*omegas*R2)/Vnew^2;
25 n=ns*(1-s);//the new motor speed at 50Hz in rpm
26 rpss=ns/60;
27 omega=(2*pi*rpss)/60;
28 mprintf("\nTo compute the starting current at 60Hz
          ,480v:")
29 I2st=Vs/sqrt((R1+R2)^(2)+Xeq^(2));//starting current
          in A
30 mprintf("\nThe starting current at 60Hz,480v is %f A
          ",I2st)
31 mprintf("\nTo compute the starting current at 50Hz
          ,400v:")
32 Vsnew=Vnew/sqrt(3);
33 Xeqnew=(fd/f)*Xeq;//inductive reactance at 50Hz
34 I2stnew=Vsnew/sqrt((R1+R2)^(2)+Xeqnew^(2));//
          starting current at 50Hz in A
35 mprintf("\nThe starting current at 50Hz,400v is %f A

```

```

The input current if the machine is in the linear region is 21.592850 A
The input current if the machine is in the saturation region is 37.523530 A
-->

```

Figure 7.9: compute the input current

```

    ”,I2stnew)
36 mprintf("\nThe starting current is almost unchanged
    due to the v/f control”)

```

---

#### Scilab code Exa 7.9 compute the input current

```

1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 7
3 //example 7.9
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 p=6;//number of poles
10 f=60;//frequency in hertz
11 Xl=3;//inductive reactance in ohm
12 Rs=.2;//stator resistance in ohm
13 X2=2;//rotor reactance in ohm
14 R2=0.1;//resistance referred to the stator in ohm
15 Xm=120;//magnetizing reactance in the linear region
    in ohm
16 Xm1=42;//magnetizing reactance in the saturation
    region in ohm

```

```

Scilab 5.5.2 Console
The frequency of the CSI to drive the machine at 900 rpm is 45.668298 Hz
-->

```

Figure 7.10: compute the frequency of the CSI to drive the machine at 900 rpm

```

17 Td=100; //constant load torque in Nm
18 n=900; //speed of the motor in rpm
19 ns=(120*f)/p; //synchronous speed of the machine in
    rpm
20 s=(ns-n)/ns; //slip of the machine
21 //If the machine is in the linear region
22 rps=ns/60;
23 omegas=(2*pi*rps);
24 Is=sqrt(((Td*s*omegas)*((R2/s)^2+(X2+Xm)^2))/(3*Xm
    ^2*R2));
25 costheta=0.7; //assumed power factor value
26 I1rated=(Td*omegas)/(sqrt(3)*V*costheta);
27 mprintf("\nThe input current if the machine is in
    the linear region is %f A",I1rated)
28 //if the machine is in saturation region
29 Is1=sqrt(((Td*s*omegas)*((R2/s)^2+(X2+Xm1)^2))/(3*Xm
    ^2*R2));
30 mprintf("\nThe input current if the machine is in
    the saturation region is %f A",Is1)

```

Scilab code Exa 7.10 compute the frequency of the CSI to drive the machine at 900

```

1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 7

```

```

3 //example 7.10
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480; //terminal voltage in
    volt
9 p=6; //number of poles
10 f=60; //frequency in hertz
11 Xl=3; //inductive reactance in
    ohm
12 Rs=.2; //stator resistance in ohm
13 X2=2; //rotor reactance in ohm
14 R2=0.1; //resistance referred to the
    stator in ohm
15 Xm=120; //magnetizing reactance in the
    linear region in ohm
16 Xm1=42; //magnetizing reactance in the
    saturation region in ohm
17 Td=100; //constant load torque in Nm
18 n=900; //speed of the motor in rpm
19 Is=21.6;
20 rps=n/60;
21 omega=(2*%pi*rps);
22 f=((3*Is^(2)*R2)/((2*%pi*Td)/f))+n)*(p/Xm);
23 mprintf("\\nThe frequency of the CSI to drive the
    machine at 900 rpm is %f Hz",f)

```

---

# Chapter 9

## Braking of dc motors

Scilab code Exa 9.1 calculate no load and motor speed then developed torque and Ea

```
1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 9
3 //example 9.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=440;//source voltage in volt
9 Ia=76;//armature current in ampere
10 ns=1000;//speed of the DC shunt motor in rpm
11 Ra=.377;//armature resistance of the motor in ohm
12 Rf=110;//field resistance of the motor in ohm
13 Prloss=1000;//rotational losses in watt
14 se=60;//seconds for 1 minute
15 Ea=V-(Ra*Ia);
16 rps=ns/se;
17 omega=(2*%pi*rps);//angular speed of the motor
18 KQ=Ea/omega;//field constant
```

```

a) To calculate no load speed of the motor:
The no load speed of the motor in rpm is 1069.653918
b)To calculate motor speed when Ia=60 ampere:
The speed of the motor in rpm is 1124.643854
c)To calculate the torque developed during regenerative braking:
The torque developed during regenerative braking in Nm is 235.685043
d)To calculate Ea during regenerative braking:
The back emf in volt is 462.620000
e)Power delivered by the source
The power delivered by the source in watt is 35200.000000
f)To calculate terminal current under regenerative braking:
The terminal current under regenerative braking in ampere is 56.000000
g)To calculate power generator during regenerative braking
power generator during regenerative braking in watt is 27757.200000
h)To calculate total losses under regenerative braking
The total losses under regenerative braking in watt is 4117.200000
i)To calculate power delivered under regenerative braking:
The power delivered under regenerative braking in watt is 23640.000000
-->|

```

Figure 9.1: calculate no load and motor speed then developed torque and Ea and terminal current and total losses during regenerative braking and also power delivered

```

19 disp('a) To calculate no load speed of the motor:')
20 omegao=V/KQ; //angular no load speed
21 no=(omegao*se)/(2*%pi);
22 mprintf("The no load speed of the motor in rpm is %f
    ",no)
23 disp('b)To calculate motor speed when Ia=60 ampere:')
    )
24 Ia3=60;
25 omega3=(V+(Ra*Ia3))/KQ;
26 n3=(omega3*se)/(2*%pi);
27 mprintf("The speed of the motor in rpm is %f",n3)
28 disp('c)To calculate the torque developed during
    regenerative braking:')
29 Tl3=KQ*Ia3;
30 mprintf("The torque developed during regenerative
    braking in Nm is %f",Tl3)
31 disp('d)To calculate Ea during regenerative braking:
    ')

```

```

32 Ea3=KQ*omega3;
33 mprintf("The back emf in volt is %f",Ea3)
34 disp('e)Power delivered by the source')
35 If=V/Rf;
36 I1=Ia+If;
37 Ps=I1*V;
38 mprintf("The power delivered by the source in watt
    is %f",Ps)
39 disp('f)To calculate terminal current under
    regenerative braking:')
40 I3=Ia3-If;
41 mprintf('The terminal current under regenerative
    braking in ampere is %f',I3)
42 disp('g)To calculate power generater during
    regenerative braking')
43 Pg=Ea3*Ia3;
44 mprintf("power generater during regenerative braking
    in watt is %f",Pg)
45 disp('h)To calculate total losses under regenerative
    braking')
46 Ploss=(Ra*(Ia3^(2)))+((V^(2))/Rf)+Prloss;
47 mprintf("The total losses under regenerative braking
    in watt is %f",Ploss)
48 disp('i)To calculate power delivered under
    regenerative braking:')
49 Pd=Pg-Ploss;
50 mprintf("The power delivered under regenerative
    braking in watt is %f",Pd)

```

---

**Scilab code Exa 9.2 calculate the speed**

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi

```



```
Scilab 5.5.2 Console
The speed at steady state operating point in rpm is -231.029801
-->
```

Figure 9.2: calculate the speed

```
Scilab 5.5.2 Console
The triggering angle required to keep the downward speed equal in magnitude to the upward speed in degree is 137.663441
-->
```

Figure 9.3: calculate the triggering angle

```
2 //chapter 9
3 //example 9.2
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ib=40;//current of the motor in ampere
9 Rb=2;//braking resistance in ohm
10 Ra=0.377;//armature resistance in ohm
11 KQ=3.93;//field constant
12 omega=-(Ib*(Ra+Rb))/KQ;//angular speed in rad/sec
13 se=60;//seconds in 1 minute
14 n=omega*(se/(2*pi));
15 mprintf("The speed at steady state operating point
    in rpm is %f",n)
```

---

**Scilab code Exa 9.3** calculate the triggering angle

```
1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 9
```

```

Scilab 5.5.2 Console
The triggering angle at the motor changes during the upward motion to keep the motor constant in degree is 86.168046
-->|

```

Figure 9.4: calculate the triggering angle

```

3 //example 9.3
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ra=.5;//armature resistance in ohm
9 KQ=3;//field constant
10 V=277;//source voltage in volt
11 Tup=100;//upward directional load torque in Nm
12 a=20;//triggering angle in degree
13 Tdw=200;//downward directional load torque in Nm
14 Vm=V*sqrt(2);
15 Veq=((2*Vm)/%pi)*cosd(a);
16 omega1=((Veq/KQ))-((Ra*Tup)/KQ^(2));
17 n1=omega1*(60/(2*%pi));//downward speed in rpm
18 b1=((-KQ*omega1)+((Ra*Tdw)/KQ))/((2*Vm)/%pi);
19 alpha2=acosd(b1);
20 mprintf("The triggering angle required to keep the
    downward speed equal in magnitude to the upward
    speed in degree is %f",alpha2)

```

---

**Scilab code Exa 9.4** calculate the triggering angle

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 9
3 //example 9.4
4 //edition 1

```

```

Scilab 5.5.2 Console
The maximum braking resistance in ohm is 55.287629
-->|

```

Figure 9.5: calculate the value of braking resistance

```

5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ra=.5;//armature resistance in ohm
9 KQ=3;//field constant
10 V=277;//source voltage in volt
11 Tup=100;//upward directional load torque in Nm
12 Vm=V*sqrt(2);
13 b1=((Ra*Tup)/KQ)/((2*Vm)/%pi);
14 alpha3=acosd(b1);//triggering angle at the upward
    motion
15 mprintf("The triggering angle at the motor changes
    during the upward motion to keep the motor
    constant in degree is %f",alpha3)

```

---

Scilab code Exa 9.5 calculate the value of braking resistance

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 9
3 //example 9.5
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;

```

```

Scilab 5.5.2 Console
The triggering angle for scr 3 and 4 to reduce the minimum braking current in degree is 119.721538
-->

```

Figure 9.6: calculate the triggering angle

```

8 Ra=1; //armature resistance in ohm
9 KQ=3; //field constant
10 V=320; //Terminal voltage in volts
11 n=1000; //motor speed in rpm
12 omega=(2*%pi*n)/60;
13 Ea1=KQ*omega;
14 Ia=(V-Ea1)/Ra; //normal field current in ampere
15 Ib=2*Ia; //maximum braking current which is twice the
    armature voltage in A
16 Rb=-(V+Ea1+(Ib*Ra))/Ib; //braking resistance
17 Rb=abs(Rb);
18 mprintf("The maximum braking resistance in ohm is %f
    ",Rb)
19 //the answer given in the book is wrong

```

---

#### Scilab code Exa 9.6 calculate the triggering angle

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 9
3 //example 9.6
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ra=1; //armature resistance in ohm
9 KQ=3; //field constant
10 V=480; //Terminal voltage in volts

```

```
Scilab 5.5.2 Console
The triggering angle for scr 3 and 4 in degree is 84.689097
-->
```

Figure 9.7: calculate the triggering angle

```
11 Tl=120; //load torque in Nm
12 alpha=30; //triggering angle of SCR 1 and 2
13 Vm=V*sqrt(2);
14 Iave1=Tl/KQ;
15 omega1=(((2*Vm)/%pi)*cosd(alpha)-(Iave1*Ra))/KQ;
16 se=60; //seconds in one minute
17 n1=(omega1*se)/(2*%pi);
18 Ib=-3*Iave1;
19 b1=-((KQ*omega1)-(3*Iave1))/((2*Vm)/%pi);
20 alpha2=acosd(b1);
21 mprintf("The triggering angle for scr 3 and 4 to
    reduce the minimum braking current in degree is
    %f",alpha2)
```

---

**Scilab code Exa 9.7** calculate the triggering angle

```
1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 9
3 //example 9.7
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ra=1; //armature resistance in ohm
```

```

Scilab 5.5.2 Console
The new steady state speed in is -190.985932 rpm
The armature current at new speed in is 60 A
-->

```

Figure 9.8: calculate new steady state speed and the armature current

```

9 KQ=3; //field constant
10 V=480; //Terminal voltage in volts
11 Tl=120; //load torque in Nm
12 Vm=V*sqrt(2);
13 Iave1=Tl/KQ;
14 omega3=0; //motor speed at holding condition
15 Iave3=-Iave1;
16 b1=((KQ*omega3)+(Ra*Iave3))/-(2*Vm)/%pi);
17 alpha2=acosd(b1);
18 mprintf("The triggering angle for scr 3 and 4 in
    degree is %f",alpha2)

```

---

**Scilab code Exa 9.8** calculate new steady state speed and the armature current

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 9
3 //example 9.8
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 Ra=0.5; //armature resistance in ohm

```

```

9 KQ=3; //field resistance
10 V=200; //source voltage in volt
11 T=180; //troque of the forklift in Nm
12 V1=-30; //terminal voltage of the motor in volt
13 omega5=((V1/KQ))-((Ra*T)/KQ^(2));
14 se=60; //seconds in one minute
15 n5=omega5*(se/(2*pi)); //new steady state speed at
    point 5 in rpm
16 fprintf("The new steady state speed in is %f rpm",n5
    )
17 I5=(V1-(KQ*omega5))/Ra; //current at point 5
18 fprintf("\n The armature current at new speed in is
    %d A", I5)

```

---

# Chapter 10

## Braking of induction motors

Scilab code Exa 10.1 calculate motor speed and power delivered to the electrical s

```
1 //Book name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 10
3 //example 10.1
4 //edition 1
5 //publishing place:Thomson Learning
6 clc;
7 clear;
8 V=208;//source voltage in volts
9 p=6;//number of poles
10 R1=0.6;//given resistance in ohm
11 R2=0.4;//given R'2 in ohm
12 Xeq=5;//given Xeq in ohm
13 Td=30;//load torque of the motor in ohm
14 f=60;//frequency for 3 phase line
15 ns=(120*f)/p
16 disp('a)To find the regenerative speed:')
17 T1=-Td//reversed load torque
18 rpss=ns/60;
```



```

Scilab 5.5.2 Console

a)To find the regenerative speed:
The regenerative speed is 1241.825938 rpm
b)To calculate the regenerative speed :
The power delivered to the electric supply is 3572.811096 watt
-->

```

Figure 10.1: calculate motor speed and power delivered to the electrical supply

```

19 omegas=(2*%pi*rpss); //angular speed
20 s=(Tl*omegas*R2)/V^2;
21 n=ns*(1-s);
22 mprintf("The regenerative speed is %f rpm",n)
23 disp('b)To calculate the regenerative speed :')
24 rps=n/60;
25 omega=(2*%pi*rps);
26 Pd=Td*omega;
27 I2=sqrt(-Pd/(3*(R2/s)*(1-s))); //to find I'2 which is
    taken as I2
28 Ploss=3*(R1+R2)*I2'^2)
29 Pds=Pd-Ploss;
30 mprintf("The power delivered to the electric supply
    is %f watt",Pds)

```

---

**Scilab code Exa 10.2** calculate the duty ratio of the FWM

```

1 //Book name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 10

```

```
Scilab 5.5.2 Console
```

```
The duty ratio of the FWM is 0.118652  
-->
```

Figure 10.2: calculate the duty ratio of the FWM

```
Scilab 5.5.2 Console
```

```
The torque developed is 60 Nm  
The slip is -0.041888  
The current of the induction motor does not surge to high value when the concurrent braking is implemented  
-->
```

Figure 10.3: calculate slip and current and also torque at all operating points

```
3 //example 10.2  
4 //edition 1  
5 //publishing place:Thomson Learning  
6 clc;  
7 clear;  
8 Vdc=200;//voltage at the dc link in volt  
9 I=25;//motor current in A  
10 R1=0.5;//stator resistance in ohm  
11 Ib=3*I;  
12 Vb=Ib*1.5*R1;//braking voltage in volt  
13 d=1.5*(Vb/Vdc)^2;  
14 mprintf("\n\nThe duty ratio of the FWM is %f",d)
```

---

Scilab code Exa 10.3 calculate slip and current and also torque at all operating p

```

1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 10
3 //example 10.3
4 //edition 1
5 //publishing place:Thomson Learning
6 clc;
7 clear;
8 n1=1150;//full load speed in rpm
9 V=300;//terminal voltage in volt
10 f=80;//frequency in Hz
11 Rr=0.5;//rotor resistance of the motor in ohm
12 Xeq=3;//equivalent inductive reactance in ohm
13 ns=1200;//nearest synchronous speed in rpm
14 rpss=ns/60;
15 omegas=(2*%pi*rpss);
16 s1=(ns-n1)/ns;
17 T6=(V^(2)*s1)/(omegas*Rr);//torque at the point 6
18 T6=ceil(T6);
19 mprintf("\\nThe torque developed is %d Nm",T6)//
   approximated value
20 s6=(T6*Rr*(-omegas))/V^(2);
21 mprintf("\\nThe slip is %f",s6)
22 n6=(-ns)*(1-s6);
23 mprintf("\\nThe current of the induction motor does
   not surge to high value when the concurrent
   braking is implemented")

```

---

# Chapter 11

## Dynamics of electric drive systems

Scilab code Exa 11.1 calculate the motor speed

```
1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.1
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
```

Scilab 5.5.2 Console

```
The motor speed after 5 sec is 456 rpm
-->
```

Figure 11.1: calculate the motor speed

```
To achieve the desired starting current the gear ratio n1/n2 must be between 0.632456
-->
```

Figure 11.2: calculate and show how to achieve the desired starting time

```
7 clear;
8 Kphi=3; //constant in Vsec
9 Ra=1; //resistance in ohm
10 La=10; //inductance in mH
11 V=600; //rated voltage of the
    motor in volt
12 Vt=150; //starting voltage in volt
13 Tl=20; //constant torque in Nm
14 m=6; //total moment of inertia in
    Nm sec^2
15 omegaf=(Vt/Kphi)-((Ra*Tl)/Kphi^(2));
16 nf=(omegaf*60)/(2*%pi);
17 mprintf("\nThe motor speed after 5 sec is %d rpm",nf
    )
18 //The plot obtained in the book is using a
    simulation software using specific design that is
    available in the software.In scilab or xcos
    there is no option to simulate DC shunt motor
```

---

Scilab code Exa 11.3 calculate and show how to achieve the desired starting time

```
1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.3
4 //edition 1
```

```
Scilab 5.5.2 Console
The time required to change the motor speed is 0.810097 sec
-->
```

Figure 11.3: calculate the time required to change the motor speed

```
5 //publishing place:Thomson Learning
6 clc;
7 clear;
8 Ra=2;//armature resistance in ohm
9 Tst1=2;//limited starting time in sec
10 Kphi=3;//field constant in V sec
11 Jm=1;//motor moment of inertia in Nm
12 J1=5;//load moment of inertia in Nm
13 tau=((J1+Jm)*Ra)/Kphi^(2);
14 Tst=3*tau;//starting time of the motor based on
    given data in sec
15 Jeq=(Tst1*(Kphi^(2)))/(3*Ra);
16 gr=sqrt((Jeq-Jm)/J1);//gear ratio n1/n2
17 mprintf("To achieve the desired starting current the
    gear ratio n1/n2 must be between %f",gr)
```

---

Scilab code Exa 11.4 calculate the time required to change the motor speed

```
1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.4
4 //edition 1
5 //publishing place:Thomson Learning
6 clc;
7 clear;
```

```

Scilab 5.5.2 Console
The terminal voltage that stop the motor and keep it at holding is 6.666667 V
The traveling time during the braking is 2 sec
-->

```

Figure 11.4: calculate terminal voltage and traveling time during braking

```

8 Ra=1; //armature resistance in ohm
9 Kphi=3; //field constant in V sec
10 Vt=500; //terminal voltage in volt
11 Vf=600; //increased motor voltage in volt
12 Td=20; //constant torque of thmotor in Nm
13 J=6; //total moment of inertia of the drive in Nm
14 omega0=(Vt/Kphi)-((Ra*Td)/Kphi^(2)); //initial speed
    in rad/sec
15 omegaf=(Vf/Kphi)-((Ra*Td)/Kphi^(2)); //final speed in
    rad/sec
16 tau=(J*Ra)/Kphi^(2);
17 t=- (tau*log((0.05*omegaf)/(omegaf-omega0))); //
    obtained from the equation of omega=omega(f)(1-e
    ^-t/tau)+omega(0)e^-t/tau
18 mprintf("The time required to change the motor speed
    is %f sec",t)

```

---

**Scilab code Exa 11.5** calculate terminal voltage and traveling time during braking

```

1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.5
4 //edition 1
5 //publishing place:Thomson Learning

```

```
Scilab 5.5.2 Console
The starting time of the motor at no load and full voltage and frequency is 5.182045 sec
-->
```

Figure 11.5: compute the starting time of the motor at no load and full load voltage

```
6  clc;
7  clear;
8  Ra=1; //armature resistance in ohm
9  Kphi=3; //field constant in V sec
10 Vt=500; //terminal voltage in volt
11 Td=20; //constant torque of the motor in Nm
12 J=6; //total moment of inertia of the drive in Nm
13 omegaf=0;
14 Vb=(omegaf+((Ra*Td)/Kphi^(2)))*Kphi;
15 mprintf("\nThe terminal voltage that stop the motor
    and keep it at holding is %f V",Vb)
16 tau=(J*Ra)/Kphi^(2);
17 t=3*tau; //the motor reaches the holding state when
    speed is 5% of initial speed
18 mprintf("\nThe traveling time during the braking is
    %d sec",t)
```

---

Scilab code Exa 11.6 compute the starting time of the motor at no load and full load

```
1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.6
4 //edition 1
5 //publishing place:Thomson Learning
```



```

Scilab 5.5.2 Console
The starting time of the induction machine is 4.311044 sec
-->

```

Figure 11.6: compute the starting time

```

6  clc;
7  clear;
8  V=480; //terminal voltage in volt
9  n=1120; //related full load speed of the motor in rpm
10 R1=1; //stator resistance in ohm
11 R2=1; //rotor resistance referred to stator in ohm
12 X1=5; //equivalent winding resistance in ohm
13 J=4; //inertia of the motor in NM sec^2
14 ns=1200; //nearest synchronous speed of the motor in
    rpm
15 K=1.196;
16 rps=ns/60;
17 omegas=(2*%pi*rps);
18 Tmax=V^(2)/(2*omegas*(R1+sqrt(R1^(2)+X1^(2))));
19 tau=(J*omegas)/Tmax;
20 smax=R2/sqrt(R1^(2)+X1^(2));
21 tst=(tau/K)*((0.25/smax)+(1.95*smax)+smax);
22 mprintf("The starting time of the motor at no load
    and full voltage and frequency is %f sec",tst)

```

---

Scilab code Exa 11.7 compute the starting time

```

1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.7

```

```
Scilab 5.5.2 Console
The magnitude of motor voltage during braking is 458.261365 volt
-->|
```

Figure 11.7: compute the magnitude of the motor voltage

```
4 //edition 1
5 //publishing place:Thomson Learning
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 n=1120;//related full load speed of the motor in rpm
10 R1=1;//stator resistance in ohm
11 R2=1;//rotor resistance referred to stator in ohm
12 Radd=1;//starting resistance inserted in the rotor
    circuit in ohm
13 X1=5;//equivalent winding resistance in ohm
14 J=4;//inertia of the motor in NM sec2
15 ns=1200;//nearest synchronous speed of the motor in
    rpm
16 rps=ns/60;
17 omegas=(2*%pi*rps);
18 smax=(R2+Radd)/sqrt(R1(2)+X1(2));
19 K=1.392;
20 Tmax=V(2)/(2*omegas*(R1+sqrt(R1(2)+X1(2))));
21 tau=(J*omegas)/Tmax;
22 tst=(tau/K)*((0.25/smax)+(1.95*smax)+smax);
23 mprintf("The starting time of the induction machine
    is %f sec",tst)
```

---

Scilab code Exa 11.8 compute the magnitude of the motor voltage

```
1 //Book Name: Fundamentals of electrical drives by
   Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.8
4 //edition 1
5 //publishing place:Thomson Learning
6 clc;
7 clear;
8 V=480; //terminal voltage in volt
9 n=1120; //related full load speed of the motor in rpm
10 R1=1; //stator resistance in ohm
11 R2=1; //rotor resistance referred to stator in ohm
12 X1=5; //equivalent winding resistance in ohm
13 J=4; //inertia of the motor in NM sec^2
14 ns=1200; //nearest synchronous speed of the motor in
   rpm
15 tbr=15; //time taken to stop the motor in sec
16 s1=2;
17 s2=1;
18 rps=ns/60;
19 omegas=(2*%pi*rps);
20 smax=R2/sqrt(R1^(2)+X1^(2));
21 Tmax=V^(2)/(2*omegas*(R1+sqrt(R1^(2)+X1^(2))));
22 tau=(2*tbr)/(((s1^(2)-s2^(2))/(2*smax))+(smax*log(s1
   /s2))+(2*smax*(s1-s2)));
23 Tmax1=(J*omegas)/tau;
24 Vbr=sqrt(Tmax1/Tmax)*V;
25 mprintf("The magnitude of motor voltage during
   braking is %f volt",Vbr)
26 //The answer provided in the textbook is wrong
```

---

```

Scilab 5.5.2 Console
The value of braking resistance to minimize the braking time is 2.805417 ohm
-->|

```

Figure 11.8: compute the value of braking resistance

**Scilab code Exa 11.9** compute the value of braking resistance

```

1 //Book Name: Fundamentals of electrical drives by
  Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.9
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 n=1120;//related full load speed of the motor in rpm
10 R1=1;//stator resistance in ohm
11 R2=1;//rotor resistance referred to stator in ohm
12 Xeq=5;//equivalent winding resistance in ohm
13 J=4;//inertia of the motor in NM sec^2
14 ns=1200;//nearest synchronous speed of the motor in
  rpm
15 K=1.196;
16 rps=ns/60;
17 omegas=(2*%pi*rps);
18 s1=2;
19 s2=1;
20 Tmax=V^(2)/(2*omegas*(R1+sqrt(R1^(2)+Xeq^(2))));
21 tau=(J*omegas)/Tmax;
22 smax=sqrt((s2^2-s1^2)/(((-log(s1/s2))-(2*(s1-s2)))
  *2));//the equation is obtained by
  differentiating tbr with respect to smax
23 Radd=(smax*sqrt(R1^2+Xeq^2))-R2;//equation to find

```

```
Scilab 5.5.2 Console
The starting time of the induction machine is 16.926780 sec
-->
```

Figure 11.9: compute the starting time

```
the Radd
24 mprintf("\\nThe value of braking resistance to
    minimize the braking time is %f ohm",Radd)
```

---

**Scilab code Exa 11.10** compute the starting time

```
1 //Book Name: Fundamentals of electrical drives by
    Mohamad A. El- Sharkawi
2 //chapter 11
3 //example 11.10
4 //edition 1
5 //publisher and place:Nelson Engineering
6 clc;
7 clear;
8 V=480;//terminal voltage in volt
9 n=1120;//related full load speed of the motor in rpm
10 R1=1;//stator resistance in ohm
11 R2=1;//rotor resistance referred to stator in ohm
12 X1=5;//equivalent winding resistance in ohm
13 J=4;//inertia of the motor in NM sec^2
14 ns=1200;//nearest synchronous speed of the motor in
    rpm
15 K=1.196;
```

```

16 Tl=60; //load torque in Nm
17 rps=ns/60;
18 omegas=(2*%pi*rps);
19 Tmax1=V^(2)/(2*omegas*(R1+sqrt(R1^(2)+X1^(2))));
20 Tmax=fix(Tmax1)
21 tau=(J*omegas)/Tmax;
22 smax=R2/sqrt(R1^(2)+X1^(2));
23 TR=Tl/Tmax;
24 A=2*(smax^(2)-((K*smax)/TR));
25 Q=A^(2)-(4*smax^(2));
26 B=1+A+smax^(2);
27 mB=abs(B);
28 D1=(-2/sqrt(Q))*(atanh(abs(2+A)/sqrt(Q)));
29 D=abs(D1);
30 tst=(tau/TR)*(1-(((0.5*A)-smax^(2))*(abs(A*D)+log10(
    mB)))));
31 mprintf("\nThe starting time of the induction
    machine is %f sec",tst)

```

---