

Scilab Textbook Companion for
Electronic Measurements And Instrumentation
by K. Lal Kishore¹

Created by
Vishal Changlani
Electronics and telecommunication Engineering
Electronics Engineering
Mumbai University
College Teacher
None
Cross-Checked by
None

June 7, 2018

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Electronic Measurements And Instrumentation

Author: K. Lal Kishore

Publisher: Pearson Education India

Edition: 1

Year: 2012

ISBN: 9788131721995

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Measurements and Instruments	5
2 Waveform Generators	38
3 Signal Analysers	43
4 Oscilloscopes	45
5 Special Types of CROs	53
6 DC and AC Bridges	62
7 Transducers	66

List of Scilab Codes

Exa 1.1	Determine the power dissipated and the probable error	5
Exa 4.1	Determine the percentage of non linearity in a saw tooth output waveform	6
Exa 1.2	Determine the resolution of the voltmeter in volts	7
Exa 1.3	Determine the resolution in volts for three and half digit DVM	7
Exa 1.4	To calculate the percentage error due to loading effect	8
Exa 1.5	To calculate value of shunt resistance	9
Exa 1.6	To find the value of R_{sh}	10
Exa 1.7	To determine the values of R_a alongwith R_b and R_c	11
Exa 1.9	To calculate the value of multiplier resistances	12
Exa 1.10	Determine the percentage errors of the reading due to ammeter loading	13
Exa 1.11	Determine the resistor values for full scale along with 20 percent 40 percent and 50 percent of deflection	13
Exa 1.12	To calculate the resistance of a shunt required to make a milli Ammeter	15
Exa 1.13	To find the current range of the ammeter	15
Exa 1.14	To determine the values of R_a along with R_b and R_c	16
Exa 1.15	To design a range switch for the DC volt section of a balanced bridge VTVM	17

Exa 1.16	To calculate the emf of the unknown source along with resolution of ammeter along with galvanometer having greatest sensitivity to imbalance	18
Exa 1.17	To find the value of multiplier resistance for 10 Vrms AC range	19
Exa 1.18	Determine the value of R_s	20
Exa 1.19	Design a thermocouple voltmeter for three ranges	21
Exa 1.20	Design a standard DC voltage source of 12 V	22
Exa 1.21	Design a volt box such that addition of R_1 and R_2 should be 10 M Ohms	23
Exa 1.22	To calculate the percentage error in the meter indication	23
Exa 1.23	To find the period of integration of dual slope integrating type DVM	24
Exa 1.24	To determine the limits of capacitance that it is guaranteed	25
Exa 1.25	To find the limiting error	26
Exa 1.26	To calculate the limiting error	26
Exa 1.27	To determine the resolution of a moving coil ammeter	27
Exa 1.28	To determine the limiting error	28
Exa 1.29	To determine the relative error for the series and parallel combination of resistances given	29
Exa 1.30	To find the arithmetic mean along with average and standard deviation for the readings given	30
Exa 1.31	To find the arithmetic mean along with average and standard deviation for the recorded observations	32
Exa 1.32	To estimate the approximate torque produced by the string	33
Exa 1.33	To determine the deflection in degrees	34
Exa 1.34	To find the deflection in degrees for a current of 1A while the instrument is spring controlled and when gravity controlled	35
Exa 1.35	To find the effective resistance	36

Exa 1.36	To determine the Cd and Q of the coil	36
Exa 2.1	To determine the frequency of oscillations in a Wien bridge oscillator	38
Exa 2.2	To design R and C elements of Wien bridge Oscillators	39
Exa 2.3	To find frequency of oscillations for an ordinary phase shift oscillator	39
Exa 2.4	To calculate frequency of transistor Colpitts oscillator	40
Exa 2.5	To determine the oscillation frequency of a Hartley oscillator	41
Exa 2.6	To calculate the value of the feedback ratio .	41
Exa 3.2	To determine the dynamic range of a spectrum analyser	43
Exa 3.3	To calculate the minimum detectable signal of a spectrum analyser	44
Exa 4.1	Determine the percentage of non linearity in a saw tooth output waveform	45
Exa 4.2	To determine the rise and decay time of the saw tooth time base voltage	46
Exa 4.3	To calculate the velocity of the electron beam of an oscilloscope	47
Exa 4.4	To determine the unknown applied voltage .	48
Exa 4.5	To determine the deflection sensitivity and the deflection factor	48
Exa 4.6	To find the Vrms of the sinusoidal voltage applied	49
Exa 4.7	To find the phase angle in each trace	50
Exa 4.8	To find the ratio of frequencies of vertical and horizontal signals	51
Exa 4.9	To find the frequency of the vertical signal for a Lissajous pattern	52
Exa 5.3	To determine the RC value of each section .	53
Exa 5.4	Calculate the phase shift between V2 and V1	54
Exa 5.5	Determine the power loss for a capacitor . .	55
Exa 5.6	Determine the frequency of the vertical input	56
Exa 5.7	Determine the possible phase angles of V2 with respect to V1	57

Exa 1.8	Estimate the boost required for electron gun accelerating voltage	57
Exa 5.8	Calculate the entering velocity of electrons and deflection produced on screen	58
Exa 5.9	To find the error in the meter indication . .	59
Exa 5.10	To calculate the velocity of the electron beam in the oscilloscope	60
Exa 6.1	To calculate the galvanometer deflection for imbalance in R4	62
Exa 6.2	To calculate the deflection of the galvanometer caused by the imbalance in the circuit .	63
Exa 6.3	To find the frequency for which the bridge is in balance and the value of R in arm DA . .	64
Exa 7.1	To determine the sensitivity of potentiometer	66
Exa 7.2	To determine the linear displacement	67
Exa 7.3	To determine the potentiometer resolution .	68
Exa 7.4	Determine the poissions ratio for thin circular wire	69
Exa 7.5	Determine the gauge factor of the device . .	69
Exa 7.6	To calculate the percentage change in resistance of strain gauge	70
Exa 7.7	To find the poissions ratio for strain gauge .	71
Exa 7.8	To determine the change in output voltage .	71
Exa 7.9	To determine the resistance at 75 degree celsius along with value of T3	72
Exa 7.10	To determine the limiting value of resistance k	73
Exa 7.11	To determine the resistance of the thermistor at 40 degree celsius	74
Exa 7.12	Determine the inductance of the coil	75
Exa 7.13	Determine the inductance of the coil for a variable reluctance type inductive transducer	75
Exa 7.14	Determine the sensitivity of LVDT	76
Exa 7.15	Determine linearity at given load	77
Exa 7.16	Determine output voltage for a displacement of 8 mm from central position	77
Exa 7.17	Determine the sensitivity of LVDT and the pressure	78

Exa 7.18	Determine the displacement for a capacitive transducer	79
Exa 7.19	To determine the value of the capacitance . .	80
Exa 7.20	Calculate the sensitivity and separation between the plates	81
Exa 7.21	Determine the sensitivity of the arrangement	81

Chapter 1

Measurements and Instruments

Scilab code Exa 1.1 Determine the power dissipated and the probable error

```
1 // Exa 1.1
2
3 clc;
4 clear;
5
6 // Given
7
8 I = 10; // Current in Amp
9 dI = 0.1; // Probability of error in I (Amp)
10 R = 100; // Resistor value in Ohms
11 dR = 2; // Probability of error in R (Ohms)
12
13
14 // Solution
15
16 printf('The power dissipated P = I^2*R \n');
17
18 printf(' The probable error can be determined with
        the help of Erss(Root Sum Square) Formula , i.e
        Error = sqrt((dR*I^2)^2 + (2*I*R*dI)^2) \n');
19
```

```

20 PE = sqrt((dR*I^2)^2 + (dI*2*I*R)^2); // Probable
      error
21 P = I^2 * R;
22
23 printf(' Error = %d W \n',round(PE));
24 printf(' Power dissipated P = %d kW \n',P*10^-3);

```

Scilab code Exa 4.1 Determine the percentage of non linearity in a saw tooth output

```

1 // Exa 4.1
2
3 clc;
4 clear;
5
6 // Given
7
8 // An oscilloscope
9
10 R = 400; // Resistance(k Ohms)
11 C = 0.025; // capacitance(micro Farad)
12 T = 0.4; // Time period of saw-tooth output waveform
            (msec)
13
14 // Solution
15
16 printf(' The percentage of non linearity i.e
           deviation in output can be given as t/(4*R*C)\n
           ');
17 PD = (T*10^-3)/(4*R*10^3*C*10^-6) ;
18
19 printf(' Therefore , by calculation , percent
           deviation = %d percent \n ',PD*100);

```

Scilab code Exa 1.2 Determine the resolution of the voltmeter in volts

```
1
2 // Exa 1.2
3
4 clc;
5 clear;
6
7 // Given
8
9 No_Div = 50; // No of divisions
10 V = 100; // Max voltage measured (V)
11
12 // Solution
13
14 printf(' Resolution is the smallest change in input
           that can be measured \n The meter can be read to
           1/2 division \n');
15 value = No_Div/V;
16 printf(' So, the resolution is 1/2 divisions and its
           value in volts is %.1f V \n', value);
17
18 printf(' Therefore , the resolution of instrument is
           0.5 V \n');
```

Scilab code Exa 1.3 Determine the resolution in volts for three and half digit DVM

```
1
2 // Exa 1.3
3
4 clc;
5 clear;
6
7 // Given
8
```

```

9 // A 3_1/2 digit DVM
10 V = 19.99; // Max voltage in Volts
11
12 // Solution
13
14 printf('The maximum number of counts that can be
           made with 9 3_1/2 digit DVM is 1999 \n The
           smallest change in input that can be measured is
           1 count \n');
15 // 1 count in volts corresponds to resolution :-
16 // 1999 counts = 19.99 V
17 // 1 count = ?
18 Resolution = 19.99/1999;
19
20 printf(' Resolution = %d mV \n', round(Resolution
           *10^3));

```

Scilab code Exa 1.4 To calculate the percentage error due to loading effect

```

1 // Exa 1.4
2
3 clc;
4 clear;
5
6 // Given
7
8 S = 10*10^3; // Sensitivity of voltmeter in Ohms/
                 Volt
9 V = 75; // Reading in Volts
10 Vmax = 100; // Max voltage in Volts
11 I = 1.5*10^-3; // reading in Amp
12
13 // Solution
14
15 printf('Consider Fig.1.10, it shows Rm as meter of

```

```

        voltmeter drawing some current \n Thus, loading
        of the source happens i.e., loading effect \n');
16 Rapparent = V/I;
17 Rm = Vmax * S;
18 // Rapparent = parallel combination of Rm and Rx
19 // Therefore Rx can be given as
20 Rx = (1/Rapparent - 1/Rm)^-1;
21 printf(' True value of Rx = %.2f K Ohms \n',Rx);
22
23 Error = 100* (Rx-Rapparent)/Rx; // Error in percent
24 printf(' The percentage error due to loading effect
        = %.1f percent \n',Error);
25
26 //The answers vary due to round off error

```

Scilab code Exa 1.5 To calculate value of shunt resistance

```

1 // Exa 1.5
2
3 clc;
4 clear;
5
6 // Given
7
8 Rm = 100; // Resistor value in Ohms
9 I = 10; // Current in Amp
10 Im = 1*10^-3; // Meter current in Amp
11
12 // Solution
13
14 Ish = I - Im;
15 Vm = Im * Rm; // Vm = Vsh
16 Vsh = Vm;
17 Rsh = Vsh/Ish;
18

```

```

19 printf('The value of shunt resistance Rsh = %.2f
          Ohms \n',Rsh);
20
21 //The answer provided in the textbook is wrong

```

Scilab code Exa 1.6 To find the value of Rsh

```

1 // Exa 1.6
2
3 clc;
4 clear;
5
6 // Given
7
8 Imax = 100*10^-6; // Initial range of Ammeter in Amp
9 Rm = 800; // Meter resistance in Ohms
10 I1max = 0.1; // Range to be extended in Amp
11 I2max = 10; // Range to be extended in Amp
12
13 // Solution
14
15 printf(' Referring Figs. 1.21 and 1.22 :- \n');
16
17 n = I1max/Imax;
18 Rsh = Rm/(n-1);
19 printf(' Ra + Rb + Rc = Rsh; \n ');
20 printf(' The value of Rsh by calculations = %.4f
          Ohms \n',Rsh);
21 printf(' Referring calculations done in textbook ,\n
          we can get values of Ra,Rb and Rc as follows :-
          \n ');
22 Rc = Imax*(Rsh+Rm)/I2max;
23 Rb = (Imax/I1max)*(Rsh+Rm) - Rc;
24 Ra = Rsh-(Rb+Rc);
25 printf(' Ra = %.3f Ohms, Rb = %.3f Ohms and Rc = %

```

```

26 .3 f Ohms \n ,Ra ,Rb ,Rc) ;
27 //The answer provided in the textbook is wrong for
    Rc and not at all given for Ra and Rb

```

Scilab code Exa 1.7 To determine the values of Ra alongwith Rb and Rc

```

1 // Formulae's from Example 1.6 are used here
2 // Exa 1.7
3
4 clc;
5 clear;
6
7 // Given
8
9 // Referring circuit given in Fig. 1.23
10 Rm = 1000; // Meter resistance in Ohms
11 Im = 100*10^-6; // Meter current in Amp
12 I1 = 1; // im Amp
13 I2 = 0.1; // in Amp
14 I3 = 10; // in Amp
15
16 // Solution
17
18 n = I3/I2;
19 Rsh = Rm/(n-1);
20 Rc = (Im/I2)*(Rsh+Rm);
21 Rb = Rc - (Im/I1)*(Rsh+Rm);
22 Ra = Rsh-(Rb+Rc);
23
24 printf('The Values of Ra, Rb and Rc are %.2f Ohms, %
    .2f Ohms and %.2f Ohms respectively \n',Ra,Rb,Rc)
    ;
25
26 //The answer provided in the textbook is wrong for

```

Scilab code Exa 1.9 To calculate the value of multiplier resistances

```
1 // Exa 1.9
2
3 clc;
4 clear;
5
6 // Given
7
8 // Referring Fig.1.26
9 Ifs = 50*10^-6; // Full scale deflection current in
Amp
10 Rm = 11; // Meter resistance in Ohms
11 R1 = 3; // Range in Volts
12 R2 = 10; // range in Volts
13 R3 = 30; // Range in Volts
14
15 // Solution
16
17 S = 1/Ifs; // Sensitivity in Ohms/V
18
19 printf('The values of multiplier resistances in the
different ranges are :- \n');
20 printf(' For 3-V range : ');
21 Rs1 = S*R1-Rm;
22 printf('%d k Ohms \n',Rs1/1000);
23 printf(' For 10-V range : ');
24 Rs2 = S*R2-Rm;
25 printf('%d k Ohms \n',Rs2/1000);
26 printf(' For 30-V range : ');
27 Rs3 = S*R3-Rm;
28 printf('%d k Ohms \n',Rs3/1000);
29
```

```
30 //The answer provided in the textbook is wrong for  
Rs1
```

Scilab code Exa 1.10 Determine the percentage errors of the reading due to ammeter

```
1 // Exa 1.10  
2  
3 clc;  
4 clear;  
5  
6 // Given  
7  
8 // Referring Fig. 1.28 and 1.29  
9 Rm = 78; // Meter resistance in Ohms  
10 Ra = 1000; // in Ohms  
11 Rb = 1000; // in Ohms  
12 Rc = 1000; // in Ohms  
13  
14 // Solution  
15  
16 Rth = Rc + Ra*Rb/(Ra+Rb);  
17  
18 // Let Im/Ie be 'x' where Ie = expected value and Im  
// be shown value  
19 x = Rth/(Rth+Rm);  
20  
21 Error = (1-x)*100;  
22  
23 printf('The meter reading shown is %d percent of the  
expected value. Therefore, Error = %d percent \n  
' ,100-round(Error),round(Error));
```

Scilab code Exa 1.11 Determine the resistor values for full scale along with 20 pe

```

1 // Exa 1.11
2
3 clc;
4 clear;
5
6 // Given
7
8 // An Ohm meter
9 Ifs = 0.001; // Current in Amp
10 V =5; // Supply voltage in Volts
11 Rm = 200; // Meter resistance in Ohms
12
13 // Solution
14
15 // Ifs = V/(Rm+Rp);
16
17 Rp =V/Ifs - Rm;
18
19 printf('Value of Rx with 20 percent full-scale
deflection :- \n');
20 P1 = 0.2;
21 Rx1 = (Rp+Rm)/P1 - (Rp+Rm);
22 printf('The resistor value for 20 percent of full
scale deflection = %d k Ohms \n',Rx1/1000);
23 printf(' Value of Rx with 40 percent full-scale
deflection :- \n');
24 P2 = 0.4;
25 Rx2 = (Rp+Rm)/P2 - (Rp+Rm);
26 printf('The resistor value for 40 percent of full
scale deflection = %.1f k Ohms \n',Rx2/1000);
27 printf(' Value of Rx with 50 percent full-scale
deflection :- \n');
28 P3 = 0.5;
29 Rx3 = (Rp+Rm)/P3 - (Rp+Rm);
30 printf('The resistor value for 50 percent of full
scale deflection = %d k Ohms \n',Rx3/1000);

```

Scilab code Exa 1.12 To calculate the resistance of a shunt required to make a milliammeter.

```
1 // Exa 1.12
2
3 clc;
4 clear;
5
6 // Given
7
8 // Referring Fig. 1.49
9 Ifs = 10; // Full scale deflection current in Amp
10 Im = 0.015; // Meter resistance in Amp
11 R = 5; // Resistance in Ohms
12
13 // Solution
14
15 Isg = Ifs - Im;
16 Rsg = Im*R/Isg;
17
18 printf('The value of shunt resistance for the milli
Ammeter = %.2f * 10^-3 Ohms \n', Rsg*1000);
```

Scilab code Exa 1.13 To find the current range of the ammeter

```
1 // Exa 1.13
2
3 clc;
4 clear;
5
6 // Given
7
8 Rm = 1; // Meter resistance in ohms
```

```

9 Vmax = 250; // Max voltage(V)
10 R1 = 4.999; // Series resistance in Ohms
11 R2 = 1/499; //Shunt resistance in Ohms
12 V = 500; // Volage to be measured(V)
13 // Solution
14
15 Imeter = V/(R1+Rm);
16 printf('Meter current Imeter = %.2f A \n ',Imeter);
17 printf('The current through the meter should not
        exceed %.1f A \n Hence, Voltage drop = %.2f V \n ',
        ,Imeter,Imeter*Rm);
18 Vdrop = Imeter*Rm;
19 // When Shunt resistance is connected accross meter
20 CurrentRange = Vdrop/R2 + Imeter;
21 Rs =(V-Imeter)/0.05;
22 printf(' Series resistance Rs = %d Ohms \n ',Rs);
23
24 //The answer provided in the textbook are incorrect

```

Scilab code Exa 1.14 To determine the values of Ra along with Rb and Rc

```

1 // Formulae's from Example 1.6 are used here
2
3 // Exa 1.14
4
5 clc;
6 clear;
7
8 // Given
9
10 // Referring Fig. 1.50
11 Im = 100*10^-6; // Meter resistance in Amp
12 Rm = 1000; // Meter resistance in Ohms
13 I1 = 1; // in Amp
14 I2 = 0.1; // in Amp

```

```

15 I3 = 0.01; // in Amp
16
17 // Solution
18
19 n = I3/Im;
20 Rsh = Rm/(n-1);
21 printf(' Ra + Rb + Rc = Rsh; \n ');
22 printf(' The value of Rsh by calculations = %.4f
    Ohms \n ',Rsh);
23
24 Rc = Im*(Rsh+Rm)/I1;
25 Rb = (Im/I2)*(Rsh+Rm) - Rc;
26 Ra = Rsh-(Rb+Rc);
27 printf(' Ra = %.3f Ohms, Rb = %.3f Ohms and Rc = %
    .3f Ohms \n ',Ra,Rb,Rc);
28
29 //The answer provided in the textbook is wrong for
    Ra calculation

```

Scilab code Exa 1.15 To design a range switch for the DC volt section of a balance

```

1 // Exa 1.15
2
3 clc;
4 clear;
5
6 // Given
7
8 // Refer fig. 1.73
9 Rtotal = 11*10^6; // Total resistance in Ohms
10 Vg = 1; // Voltage at gate of balancing circuit
11 Vmax = 1000; // Max voltage in Volts
12 // Solution
13
14 printf('When the selector switch is at 1000 V

```

```

position , and the mass input is 1000 V, the drop
across R7 should be 1 value \n');
15 R7 = (Vg/Vmax)*Rtotal;
16 printf('R7 = %d k Ohms \n',R7/1000);
17 printf('Similarly , when the selector switch is at
the 300 V position , the drop across (R6+R7)
should be 1 V \n');
18 R6 = (Vg/300)*Rtotal-R7;
19 printf('R6 = %.2f k Ohms \n',R6/1000);
20 R5 = (Vg/100)*Rtotal-(R7+R6);
21 printf('R5 = %.2f k Ohms \n',R5/1000);
22 R4 = (Vg/30)*Rtotal-(R7+R6+R5);
23 printf('R4 = %.2f k Ohms \n',R4/1000);
24 R3 = (Vg/10)*Rtotal-(R7+R6+R5+R4);
25 printf('R3 = %.2f k Ohms \n',R3/1000);
26 R2 = (Vg/3)*Rtotal-(R7+R6+R5+R4+R3);
27 printf('R2 = %.2f k Ohms \n',R2/1000);
28 R1 = Rtotal - (R2+R3+R4+R5+R6+R7);
29 printf('R1 = %.2f k Ohms \n',R1/1000);

```

Scilab code Exa 1.16 To calculate the emf of the unknown source along with resolution

```

1 // Exa 1.16
2
3 clc;
4 clear;
5
6 // Given
7
8 // Refer Fig.1.74
9 Rmv = 200; // Voltmeter resistance in Ohms
10 Vt = 3; // Terminal voltage(V)
11 S = 1; // Sensitivity in mm/microV
12 Rmi = 100; // Galvanometer resistance in Ohms
13 Deflection = 250; // in mm

```

```

14 S1 = 5; // sensitivity of second galvanometer in mm/
           micro Amp
15 Ri = 1000; // Internal resistance of 2nd
               galvanometer
16 // Solution
17
18 Ig = Deflection/S;
19 printf(' Current through the galvanometer = %d micro
           Amp \n', Ig);
20 Rtotal = Rmv+Rmi;
21 Vrtotal = Rtotal*Ig*10^-6; // in Volts
22 Ek = Vt - Vrtotal;
23 printf('The emf of the unknown source = %.3f V \n',
           Ek);
24 printf('1 mm corresponds to 1 micro Amp. Therefore ,
           Resolution = %d micro V/mm \n', Rtotal);
25
26 printf('For galvanometer A, 1 mm deflection for 300
           mV. So, Sa = 1/300 mm/microV \n');
27 Sa = 1/300; // Sensitivity of galvanometer A in mm/
               micro V
28 printf('For galvanometer B, - \n');
29 Rbtotla = Ri+Rmv;
30 // A 5mm deflcetion is caused by 1200 micro V
31 printf('Sb = 5/1200 mm/microV \n'); // mm/microV
32 printf('Galvanometer B provides the amplified
           sensitivity i.e, Since , Sb>Sa \n');

```

Scilab code Exa 1.17 To find the value of multiplier resistance for 10 Vrms AC ran

```

1 // Exa 1.17
2
3 clc;
4 clear;
5

```

```

6 // Given
7
8 // Refer Fig. 1.77
9 Ifs = 10^-6; // Full scale deflection current in Amp
10 Rm = 300; // Meter resistance in Ohms
11 Erms = 10; // in Volts
12 Idc = 1*10^-3; // in Amp
13 // Solution
14 S = 1/Ifs;
15 Rs = 0.45* Erms/Idc - Rm;
16 printf(' The value of multiplier resistance Rs = %.1
f k Ohms \n',Rs/1000);

```

Scilab code Exa 1.18 Determine the value of Rs

```

1 // Exa 1.18
2
3 clc;
4 clear;
5
6 // Given
7
8 Ifs = 10^-3; // Full scale deflection current in Amp
9 Rm = 500; // Meter resistance in Ohms
10 Range = 10; // Em = 10*Vrms
11 // Solution
12
13 Sdc = 1/Ifs; // Dc Sensitivity in Ohms/Volt
14 Sac = 0.9*Sdc; // Ac Sensitivity in Ohms/Volt
15
16 Rs = Sac * Range - Rm;
17 printf('The value of multiplier resistance Rs = %d
Ohms \n',Rs);

```

Scilab code Exa 1.19 Design a thermocouple voltmeter for three ranges

```
1 // Exa 1.19
2
3 clc;
4 clear;
5
6 // Given
7
8 // Design of thermocouple voltmeter
9 // Three ranges
10 V1 = 5; // Volts
11 V2 = 10; // Volts
12 V3 = 25; // Volts
13 Ifs = 50*10^-3; // Amp
14 Rm = 200; // Ohms
15 Imax = 5*10^-3; // Amps
16 Rheater = 200; // Ohms
17
18 // Solution
19
20 printf(' To get a FSD for 5,10 and 25V, current
           through the heater must be limited to 5mA \n');
21
22 printf('For a 5V range \n');
23 Rs1 = V1/Imax - Rm;
24 printf('Series resistance Rs = %d Ohms \n',Rs1);
25 printf('For a 10V range \n');
26 Rs2 = V2/Imax - Rm;
27 printf('Series resistance Rs = %d Ohms \n',Rs2);
28 printf('For a 25V range \n');
29 Rs3 = V3/Imax - Rm;
30 printf('Series resistance Rs = %d Ohms \n',Rs3);
31
```

32 //The answer provided in the textbook for Rs3 is wrong

Scilab code Exa 1.20 Design a standard DC voltage source of 12 V

```
1 // Exa 1.20
2
3 clc;
4 clear;
5
6 // Given
7
8 // Refer Fig. 1.86
9 Vdc = 12; // Volts
10 Vac = 20; // Volts
11 Vz = 12; // Volts
12 Iz = 10*10^-3; // in Amps
13
14 // Solution
15
16 R =(Vac-Vdc)/Iz;
17 printf('The value of resistance R = %d Ohms \n',R);
18 P = Vdc*Iz;
19 printf(' Power rating of the Zener = %d mW \n',P
    *1000);
20 printf(' Factor 2 is the safety factor \n The power
    rating of the resistor taking a safety factor of
    2 is P = ');
21 psafety = 2*(Vdc - Vz)/R;
22 printf(' %.2f W \n',psafety);
23 printf(' 1/16 W resistor curve serves the purpose \n
    ');
24
25 //The answer provided in the textbook for power
    rating is wrong
```

Scilab code Exa 1.21 Design a volt box such that addition of R1 and R2 should be 1

```
1 // Exa 1.21
2
3 clc;
4 clear;
5
6 // Given
7
8 // A Volt box design
9 Vs = 100; // Input voltage (V)
10 V2 = 5; // Output voltage (V)
11 Rs = 10*10^6; // Desired sum of resistance(R1+R2)
    Ohms
12
13
14 // Solution
15
16 // By voltage divider formula , we get
17 // R2/(R1+R2) = V2/Vs ;
18 // i.e, By simplifying
19 R2 = Rs*V2/Vs;
20
21 R1 = Rs - R2;
22 printf(' The desired values of R1 and R2 to satisfy
        Volt box requirements are %.1f M ohms and %.2f M
        ohms respectively \n ',R1/10^6,R2/10^6);
23
24 //The answer provided in the textbook is wrong
```

Scilab code Exa 1.22 To calculate the percentage error in the meter indication

```

1 // Exa 1.22
2
3 clc;
4 clear;
5
6 // Given
7
8 // A sine wave AC input
9
10 // Solution
11
12 printf('For a square wave, the form factor is 1.0,
           that is , the average and rms value are same \n');
13 printf(' For a sine wave, the form factor is 1.1,
           that is , the rms is 1.11 times the average \n');
14 printf(' Since the meter is calibrated for a sine
           wave, for a 1.0 V rms value of square wave, it
           indicates 1.11 V \n');
15 FFsq = 1.0;
16 FFsi = 1.11;
17 Perror = 100*(FFsi-FFsq)/FFsq;
18 printf(' The percentage error in the meter
           indication = %d percent \n',Perror);

```

Scilab code Exa 1.23 To find the period of integration of dual slope integrating type DVM

```

1 // Exa 1.23
2
3 clc;
4 clear;
5
6 // Given
7
8 // Dual slope integrating-type DVM
9 C = 0.1*10^-6; // Capacitor in Farads

```

```

10 R = 10*10^3; // Resistance in Ohms
11 Vr = 2; // Reference Voltage(Volts)
12 Vmax = 10; // maximum output of circuit(Volts)
13
14 // Solution
15
16 Tc = C*R; // Integrator Time Constant
17 Vo = Vr/Tc ; // Integrator output in Volt/sec
18
19 Ti = Vmax/Vo; //in sec
20
21 printf(' The period of integration of dual slope
integrating-type DVM = %d m sec \n',Ti*1000);
22
23 //The answer provided in the textbook is wrong

```

Scilab code Exa 1.24 To determine the limits of capacitance that it is guaranteed

```

1 // Exa 1.24
2
3 clc;
4 clear;
5
6 // Given
7
8 Am = 20; // Capacitance in Farads
9 dr= 5 ; // Percentage variation in capacitor value
10
11 // Solution
12
13 // A = Am ( ) Am dr/100 ; // A is guaranteed value
of capacitor
14
15 A_upperlimit = Am*(1+ dr/100) ;
16 A_lowerlimit = Am*(1- dr/100) ;

```

```
17
18 printf(' The guranteed limits of capacitance range
      from %.1f F to %.1f F \n',A_lowerlimit,
      A_upperlimit);
```

Scilab code Exa 1.25 To find the limiting error

```
1 // Exa 1.25
2
3 clc;
4 clear;
5
6 // Given
7
8 // A 0-250 range milliAmmeter
9 Er = 2; // Percentage accuracy of Ammeter in terms
          of FSR
10 I = 150; // Measurement of Ammeter in mA
11 Ifsr = 250; // Full scale reading of milliAmmeter (
               mA)
12
13 // Solution
14
15 dV = Er/100 * Ifsr; // Error in FSR reading
16 Lr = 100*dV/I;
17 printf('The limiting error = %.2f percent \n',Lr);
```

Scilab code Exa 1.26 To calculate the limiting error

```
1 // Exa 1.26
2
3 clc;
4 clear;
```

```

5
6 // Given
7
8 R = 50; // Resistance value (Ohms)
9 dR = 0.2; // variation in Resistance value (Ohms)
10 I = 4; // Current value measured (Amp)
11 dI = 0.02; // variation in current measurements (Amp)
    )
12
13 // Solution
14
15 Per_Limiting_Error_Resis = dR/R * 100;
16 Per_Limiting_Error_Curr = dI/I * 100;
17
18 P = I^2 * R;
19 dP = Per_Limiting_Error_Curr*2 +
      Per_Limiting_Error_Resis;
20
21 printf('The limiting error in resistance measurement
         = %.2f percent \n',Per_Limiting_Error_Resis);
22 printf(' The limiting error in current measurement =
         %.2f percent \n',Per_Limiting_Error_Curr);
23 printf(' The limiting error in power measurement =
         %.2f percent \n',dP);

```

Scilab code Exa 1.27 To determine the resolution of a moving coil ammeter

```

1 // Exa 1.27
2
3 clc;
4 clear;
5
6 // Given
7
8 // A moving coil Ammeter

```

```

9 FSR = 10; // Full scale reading in Amp
10 No_of_div = 100;
11
12 // Solution
13
14 one_scale_div = FSR/No_of_div ; // in Amp
15 Resolution = 1/2 * one_scale_div ; // Since , the
      instrument can read upto half of the full-scale
      division(Amp)
16 printf('Resolution = %d mA \n', Resolution*1000);

```

Scilab code Exa 1.28 To determine the limiting error

```

1 // Exa 1.28
2
3 clc;
4 clear;
5
6 // Given
7
8 // Limiting error for series and parallel
   combination of capacitors
9 c1 = 99; // Capacitor value in Mf
10 dc1 = 1; // Variation in capacitor value in Mf
11 c2 = 49; // Capacitor value in Mf
12 dc2 = 1; // Variation in capacitor value in Mf
13
14 // Solution
15
16 // C1 = c1( ) dc1;
17 // C2 = c2( ) dc2;
18 printf('For parallel combination , we have y = C1+C2
      \n');
19 dY_parallel = dc1 + dc2;
20 printf(' Limiting error for parallel combination = (

```

```

) %d Mf \n',dY_parallel);
21 printf(' For series combination , we have  $1/y = 1/C1$ 
+ $1/C2 \n'$ );
22 Yseries = c1*c2/(c1+c2);
23 dYseries = (-dc1+c1)*(-dc2+c2)/(c1+c2-dc1-dc2);
24 dY = Yseries - dYseries;
25 printf(' Limiting error for series combination = (
) %.3 f Mf \n',dY);
26
27 //The answer provided in the textbook is wrong

```

Scilab code Exa 1.29 To determine the relative error for the series and parallel combination

```

1 // Exa 1.29
2
3 clc;
4 clear;
5
6 // Given
7
8 // 3 resistances in series and parallel combination
9
10 r1 = 200; // First resistance in (Ohms)
11 dr1 = 5 ; // Percentage variation for first
             resistance
12 r2 = 100; // Second resistance in (Ohms)
13 dr2 = 5 ; // Percentage variation for second
             resistance
14 r3 = 50; // Third resistance in (Ohms)
15 dr3 = 5 ; // Percentage variation for third
             resistance
16
17 // Solution
18
19 printf('Lets say Rse be the series combination of

```

```

        resistances \n'); // series
20 Rse = r1+r2+r3;
21 Relative_Error_series = r1/Rse * dr1 + r2/Rse * dr2
    + r3/Rse * dr3; // in percentage
22 Error_series_Ohms = Rse * Relative_Error_series/100;
23 printf(' The Relative error for series combination(
    Rse) is %d percent which is equivalent to %.2f
    Ohms \n',Relative_Error_series>Error_series_Ohms)
    ;
24 printf(' Lets say Rpa be the parallel combination of
    resistances \n'); // parallel
25 Rpa = r1*r2*r3/(r2*r3+r1*r2+r1*r3); // lets say (x/
    y1+y2+y3)
26 Error_x = dr1+dr2+dr3;
27 Error_y1 = dr1+dr2;
28 Error_y2 = dr2+dr3;
29 Error_y3 = dr3+dr1;
30 Error_Y = r1/Rse * Error_y1 + r2/Rse * Error_y2 + r3
    /Rse * Error_y3;
31 Relative_Error_parallel = Error_x+ Error_Y; // in
    percentage
32 Error_parallel_Ohms = Rpa * Relative_Error_parallel
    /100 ;
33 printf(' The Relative error for parallel combination
    (Rpa) is %d percent which is equivalent to %.4f
    Ohms \n',Relative_Error_parallel,
    Error_parallel_Ohms);

```

Scilab code Exa 1.30 To find the arithmetic mean along with average and standard deviation

```

1 // Exa 1.30
2
3 clc;
4 clear;
5

```

```

6 // Given
7
8 // Various Inductance Measurements
9 L1 = 1.003; // First reading in mH
10 L2 = 0.998; // second reading in mH
11 L3 = 1.001; // third reading in mH
12 L4 = 0.991; // fourth reading in mH
13 L5 = 1.009; // Fifth reading in mH
14 L6 = 0.996; // sixth reading in mH
15 L7 = 1.005; // seventh reading in mH
16 L8 = 0.997; // eight reading in mH
17 L9 = 1.008; // nineth reading in mH
18 L10 = 0.994; // tenth reading in mH
19 n = 10; // total no of readings
20
21 // Solution
22
23 AM = (L1+L2+L3+L4+L5+L6+L7+L8+L9+L10)/n;
24 printf('The arithmetic mean = %.4f mH \n',AM);
25
26 // Deviation for each reading will be -
27 d1 = L1 - AM; // deviation for 1st reading
28 d2 = L2 - AM; // deviation for 2nd reading
29 d3 = L3 - AM; // deviation for 3rd reading
30 d4 = L4 - AM; // deviation for 4th reading
31 d5 = L5 - AM; // deviation for 5th reading
32 d6 = L6 - AM; // deviation for 6th reading
33 d7 = L7 - AM; // deviation for 7th reading
34 d8 = L8 - AM; // deviation for 8th reading
35 d9 = L9 - AM; // deviation for 9th reading
36 d10 = L10 - AM; // deviation for 10th reading
37
38 Avg_deviation = (d1+d2+d3+d4+d5+d6+d7+d8+d9+d10)/n;
39 printf(' The average deviation = %d mH \n',
        Avg_deviation);
40
41 SD = sqrt((d1^2+d2^2+d3^2+d4^2+d5^2+d6^2+d7^2+d8^2+
           d9^2+d10^2)/(n-1));

```

```
42 printf('The standard deviation = %.3f mH \n', SD);  
43  
44 //The answer provided in the textbook is wrong
```

Scilab code Exa 1.31 To find the arithmetic mean along with average and standard deviation

```
1 // Exa 1.31  
2  
3 clc;  
4 clear;  
5  
6 // Given  
7  
8 // Various Current Measurements  
9  
10 I1 = 41.7; // First reading in A  
11 I2 = 42; // second reading in A  
12 I3 = 41.8; // third reading in A  
13 I4 = 42; // fourth reading in A  
14 I5 = 42.1; // Fifth reading in A  
15 I6 = 41.9; // sixth reading in A  
16 I7 = 42; // seventh reading in A  
17 I8 = 41.9; // eight reading in A  
18 I9 = 42.5; // nineth reading in A  
19 I10 = 41.8; // tenth reading in A  
20 n=10; // Total no of observations  
21 I = [41.7;42;41.8;42;42.1;41.9;42;41.9;42.5;41.8];  
22  
23 // Solution  
24  
25 AM = (I1+I2+I3+I4+I5+I6+I7+I8+I9+I10)/n;  
26 printf('The arithmetic mean = %.4f A \n', AM);  
27  
28 // Deviation for each reading will be -  
29 d1 = I1 - AM; // deviation for 1st reading
```

```

30 d2 = I2 - AM; // deviation for 2nd reading
31 d3 = I3 - AM; // deviation for 3rd reading
32 d4 = I4 - AM; // deviation for 4th reading
33 d5 = I5 - AM; // deviation for 5th reading
34 d6 = I6 - AM; // deviation for 6th reading
35 d7 = I7 - AM; // deviation for 7th reading
36 d8 = I8 - AM; // deviation for 8th reading
37 d9 = I9 - AM; // deviation for 9th reading
38 d10 = I10 - AM; // deviation for 10th reading
39
40 SD = sqrt((d1^2+d2^2+d3^2+d4^2+d5^2+d6^2+d7^2+d8^2+
41 d9^2+d10^2)/(n-1));
42 printf(' The standard deviation = %.3f A \n',SD);
43
44 Y = 0.6745*SD;
45 printf(' Probable error of one reading = %.3f A \n',
46 Y);
47
48 Vm = Y/sqrt(n-1);
49 printf(' Probable error of mean = %.3f A \n',Vm);
50
51 // The answers vary due to round off error

```

Scilab code Exa 1.32 To estimate the approximate torque produced by the string

```

1 // Exa 1.32
2
3 clc;
4 clear;
5
6 // Given
7
8 E = 1.2 * 10^4 ; // Phosphor Young's Modulus (kg per

```

```

    mm^2)
9 l = 400; // Length of strip (mm)
10 w = 0.5; // Width of strip (mm)
11 t = 0.08; // Thickness of strip (mm)
12 Theta = 90; // In degrees
13
14
15 // Solution
16
17 T = (E*w*t^2)/(12*l);
18
19 printf('By using the torque formula having E as
youngs modulus , we get T = %.3f kg-mm \n',T);
20
21 //The answer provided in the textbook is wrong

```

Scilab code Exa 1.33 To determine the deflection in degrees

```

1 // Exa 1.33
2
3 clc;
4 clear;
5
6 //Given
7
8 W = 0.005; // Weight in Kg
9 l = 2.4*10^-2; // Distance in m
10 Td = 1.05*10^-4; // Deflection torque in kg-m
11
12 // Solution
13
14 Theta = asind(Td/(W*l));
15 printf('Deflection torque is given by , Td = W*l*sin(
theta)\n Therefore theta = %.1f degrees \n',
Theta);

```

Scilab code Exa 1.34 To find the deflection in degrees for a current of 1A while t

```
1 // Exa 1.34
2
3 clc;
4 clear;
5
6 // Given
7
8 I1 = 10; // Current which produces deflection of 90
degrees
9 Theta1 = 90; // In degrees
10 I2 = 5; // Current for which theta is to be
calculated
11
12 // Solution
13
14 //The deflection which produces a current of 1A when
instrument is spring controlled
15 // Tc      theta
16 // theta      I^2
17
18 theta2 = (I2/I1)^2 * Theta1 ;
19 printf('The deflection which produces a current of 1
A when instrument is spring controlled is equal
to = %.1f degrees \n',theta2);
20 //The deflection which produces a current of 1A when
instrument is gravity controlled
21 // Tc      sin(theta)
22 // theta      I^2
23
24 theta2_gravity = asind((I2/I1)^2 *sind(Theta1)) ;
25 printf(' The deflection which produces a current of
1A when instrument is gravity controlled = %.2f
```

```
    degrees \n',theta2_gravity);  
26  
27 // The value of I given as 1A in problem statement  
   is incorrect to satisfy the problem answer(  
   correct value is 5A)
```

Scilab code Exa 1.35 To find the effective resistance

```
1 // Exa 1.35  
2  
3 clc;  
4 clear;  
5  
6 // Given  
7  
8 f = 450; // Resonating frequency in kHz  
9 C = 250; // Capacitor value at resonating frequency  
           (pf)  
10 Q = 105; // Q-meter reading at resonance  
11 Rsh = 0.75; // Value of shunt resistance in ohms  
12  
13 // Solution  
14  
15 L = 1/((2*pi*f*10^3)^2*C*10^-12); // in H  
16 w=2*pi*f*10^3;  
17 R = (w*L)/Q - Rsh;  
18 x= round(w*L/Q);  
19 printf(' The value of resistance ,R = %.2f Ohms \n',  
        double(w*L/Q)-Rsh);  
20  
21 // The answer vary due to round off error
```

Scilab code Exa 1.36 To determine the Cd and Q of the coil

```

1 // Exa 1.36
2
3 clc;
4 clear;
5
6 // Given
7
8 f1 = 1*10^6; // first resonant frequency in Hz
9 C1 = 480*10^-12; // Capacitor value at f1 in Farad
10 f2 = 2*10^6; // second resonant frequency in Hz
11 C2 = 120*10^-12; // Capacitor value at f2 in Farad
12 R = 10; // Resistance in Ohms
13
14 // Solution
15
16 Cd = (C1-4*C2)/3; // Distributive capacitor
17 Q = 1/((2*pi*f1)*R*(C1+Cd));
18
19 printf('The value of Cd and Q of the coil are %.1f
      pf and %.2f respectively ',Cd*10^12,Q);
20
21 //The answer provided in the textbook cannot be
      confirmed(The formulae for Cd mentions L2
      variable whose value is not given in problem
      statement)

```

Chapter 2

Waveform Generators

Scilab code Exa 2.1 To determine the frequency of oscillations in a Wien bridge oscillator

```
1 // Exa 2.1
2
3 clc;
4 clear;
5
6 // Given
7
8 // A wien bridge oscillator under consideration
9 R = 55*10^3; // Resistance in Ohms
10 // R = R1 = R2 ... given
11 C = 800*10^-12; // Capacitor in Farad
12 // C = C2 = C1 .. given
13
14 // Solution
15
16 f = 1/(2*pi*R*C) ;
17
18 printf(' The frequency of oscillations = %.1f Hz \n'
, f);
```

Scilab code Exa 2.2 To design R and C elements of Wien bridge Oscillators

```
1 // Exa 2.2
2
3 clc;
4 clear;
5
6 // Given
7
8 // A wien bridge oscillator under consideration
9
10 fo= 10^6 ; // frequency of oscillations in Hz
11
12 // Solution
13
14 printf(' Let R = 3 k Ohms \n');
15
16 R = 3000; // Ohm's
17 // since , fo = 1/(2*pi*R*C) ; therefore ,
18 C = 1/(2*pi*fo*R);
19
20 printf(' Substituting that , the value of capacitor
   = %d pf \n',C*10^12);
```

Scilab code Exa 2.3 To find frequency of oscillations for an ordinary phase shift

```
1 // Exa 2.3
2
3 clc;
4 clear;
5
6 // Given
```

```

7
8 // A phase shift oscillator
9
10 R = 800*10^3; // in Ohm's
11 // R = R1 = R2 = R3 .. given
12 C = 100*10^-12; // in Farad
13 // C = C1 = C2 = C3 .. farad
14
15 // Solution
16
17 fo = 1/(2*pi*R*C*sqrt(6));
18
19 printf(' The frequency of oscillations = %d Hz \n',
fo);

```

Scilab code Exa 2.4 To calculate frequency of transistor Colpitts oscillator

```

1 // Exa 2.4
2
3 clc;
4 clear;
5
6 // Given
7
8 // Transistor Colpitts oscillator
9 L = 100*10^-3; // Inductance(H)
10 C1 = 0.005*10^-6; // Capacitor(F)
11 C2 = 0.01*10^-6; // Capacitor(F)
12
13 // Solution
14
15 C = C1*C2/(C1+C2);
16 printf(' By calculation , C = %.2f pf \n',C*10^12);
17 fo = 1/(2*pi*sqrt(L*C));
18

```

```
19 printf(' The frequency of oscillator = %.1f kHz \n',
      ,fo*10^-3);
20
21 // The answer provided in the textbook is wrong
```

Scilab code Exa 2.5 To determine the oscillation frequency of a Hartley oscillator

```
1 // Exa 2.5
2
3 clc;
4 clear;
5
6 // Given
7
8 // A Hartley oscillator under consideration
9 L1 = 100*10^-3; // Inductance(H)
10 L2 = 1*10^-3; // Inductance(H)
11 M = 50*10^-3; // Inductance(H)
12 C = 100*10^-12; // Capacitor(F)
13
14 // Solution
15
16 L = L1+L2+2*M;
17 printf(' By calculation , L = %d H \n',L*10^3);
18
19 f = 1/(2*pi*sqrt(L*C));
20
21 printf(' The frequency of oscillation = %d kHz \n',
      f*10^-3);
22
23 // The answer provided in the textbook is wrong
```

Scilab code Exa 2.6 To calculate the value of the feedback ratio

```
1 // Exa 2.6
2
3 clc;
4 clear;
5
6 // Given
7
8 // An Amplifier under consideration
9 Av = 40; // Voltage gain
10 Vi = 0.1; // Input voltage without feedback(V)
11 Vi_fb = 2.4; // Input voltage with feedback(V)
12
13 // Solution
14
15 A = Av*Vi_fb/Vi;
16
17 // Av = A/(1-B*A) ; therefore ,
18 B = (1-A/Av)/A;
19
20 printf(' The value of feedback ratio = %.6f \n ',B);
```

Chapter 3

Signal Analysers

Scilab code Exa 3.2 To determine the dynamic range of a spectrum analyser

```
1 // Exa 3.2
2
3 clc;
4 clear;
5
6 // Given
7
8 Noise = -90; // Minimum detectable signal (dbm)
9 Ip = 300 ; // power level of third-order product(dbm)
10
11 // Solution
12
13 printf(' The expression for the dynamic range of the
14 spectrum analyser = 2/3*(Ip-MDS) \n So, by
15 calculations :-\n');
16 DR = 2/3*(Ip-Noise);
17 printf(' Dynamic range %.1f dB \n',DR);
18 // The answer provided in the textbook is wrong
```

Scilab code Exa 3.3 To calculate the minimum detectable signal of a spectrum analyser

```
1 // Exa 3.3
2
3 clc;
4 clear;
5
6 // Given
7
8 NF = 30; // Noise figure in dB
9 BW = 1; // Bandwidth of 3 dB filter in kHz
10
11 // Solution
12
13 printf(' The noise level of the spectrum analyser is
           related to the noise figure and the IF bandwidth
           by the following equation - \n MDS = -114 dbm +
           10*log(BW/1MHz) + NF \n so , by calculation :- '
           );
14
15 MDS = -114 + 10*log10(BW*10^3/10^6)+NF;
16
17 printf(' MDS = %d dBm \n ', MDS);
18
19 // The answer provided in the textbook is wrong
```

Chapter 4

Oscilloscopes

Scilab code Exa 4.1 Determine the percentage of non linearity in a saw tooth output

```
1 // Exa 4.1
2
3 clc;
4 clear;
5
6 // Given
7
8 // An oscilloscope
9
10 R = 400; // Resistance(k Ohms)
11 C = 0.025; // capacitance(micro Farad)
12 T = 0.4; // Time period of saw-tooth output waveform
           (msec)
13
14 // Solution
15
16 printf(' The percentage of non linearity i.e
           deviation in output can be given as t/(4*R*C)\n
           ');
17 PD = (T*10^-3)/(4*R*10^3*C*10^-6) ;
18
```

```
19 printf(' Therefore , by calculation , percent  
deviation = %d percent \n ',PD*100);
```

Scilab code Exa 4.2 To determine the rise and decay time of the saw tooth time base

```
1 // Exa 4.2  
2  
3 clc;  
4 clear;  
5  
6 // Given  
7  
8 f = 83.3 ; // frequency of sinusoidal voltage in  
// KHz  
9  
10 // Solution  
11 // part a  
12  
13 printf('Being synchronised , the frequency of the saw  
-tooth wave will be a submultiple of the signal .  
\n');  
14  
15 printf(' Frequency of saw-tooth curve = %.2f kHz \n '  
,f/10);  
16 F = f/10;  
17 printf(' Period of the saw-tooth curve = %.1f  
microsec \n',(1/F)*10^3);  
18  
19 // since , Sine wave y = A sin theta  
20 // but y/A = 0.5(since , end of trace was at position  
// half the amplitude away from x-axis)  
21 theta = asind(1/2) ;  
22 printf(' The 10th wave is in short of a complete  
since wave by %d degrees \n ',theta);  
23 printf(' Therefore , No of full waves of sine form
```

```

seen on the screen are 9 11/12 waveforms \n';
24
25 // Rise time +decay time = period of wave = 120
   microsec
26 T = 120 ; // period in microsec
27 Rise_by_decay = (119/12) / (10- 119/12);
28 DecayTime = Rise_by_decay/T;
29 printf(' Decay time = %.1f microsec \n',round(
   DecayTime));
30 printf(' Rise time = %.1f microsec \n',T-DecayTime);
31
32 // part b
33
34 printf(' Since , increase time base frequency = 10/4
   times the final value \n');
35
36 L = (10/4)* theta ;
37 printf(' Length of trace blanked in degrees due to
   flyback time = %d degrees \n ',L);
38 T_new = T*4/10;
39 printf('Period of new time base = %d microsec \n',
   T_new);
40 printf(' Rise time as per new time base = %d
   microsec \n ',T_new-1);

```

Scilab code Exa 4.3 To calculate the velocity of the electron beam of an oscilloscope

```

1 // Exa 4.3
2
3 clc;
4 clear;
5
6 // Given
7
8 Va = 2500; // Applied voltage(Volts)

```

```

9 e = 1.602*10^-19; // Charge of electron (C)
10 m = 9.107*10^-31; // Mass of electron (Kg)
11
12 // Solution
13
14 // For Electron beam in the oscilloscope , its
   velocity is given as-
15 V = sqrt(2*e*Va/m);
16
17 printf(' The velocity of electron beam of an
   oscilloscope = %.3f * 10^6 m/sec \n',V/10^6);

```

Scilab code Exa 4.4 To determine the unknown applied voltage

```

1 // Exa 4.4
2
3 clc;
4 clear;
5
6 // Given
7
8 Def_sensitivity = 0.05; // Deflection sensitivity in
   mm/V
9 Spot_deflection = 5; // in mm
10
11 // Solution
12
13 AppliedVoltage = Spot_deflection/Def_sensitivity ;
14
15 printf(' The applied voltage = %d V \n',
   AppliedVoltage);

```

Scilab code Exa 4.5 To determine the deflection sensitivity and the deflection fac

```

1 // Exa 4.5
2
3 clc;
4 clear;
5
6 // Given
7
8 // A CRT under consideration
9 l = 20; // length of x-deflection plates in mm
10 d = 5; // distance between x-deflection plates in mm
11 s = 250; // distance between screen and center of
    plate in mm
12 Va = 3000; // applied accelerating voltage in volts
13
14 // Solution
15
16 Def_sensitivity = l*s/(2*d*Va) ;
17 printf(' The deflection sensitivity = %.5f mm/V \n',
    Def_sensitivity);
18 printf(' The deflection factor = %.1f V/mm \n',1/
    Def_sensitivity);

```

Scilab code Exa 4.6 To find the Vrms of the sinusoidal voltage applied

```

1 // Exa 4.6
2
3 clc;
4 clear;
5
6 // Given
7
8 l = 25; // length of x-deflection plates in mm
9 d = 1; // distance between x-deflection plates in mm
10 s = 200; // distance between screen and centre of
    plate in mm

```

```

11 Va = 3000; // applied accelerating voltage in volts
12 Lt = 100; // length of trace in mm
13
14 // Solution
15
16 // Deflection produced = y/Vd = s*l/(2*d*Va)
17
18 y = 1/2 *(Lt);
19 // Therefore ,
20 Vd = 2*d*Va*y/(l*s) ;
21
22 Vrms = Vd/sqrt(2) ;
23
24 printf(' The Vrms of the applied sinusoidal voltage
= %.1f V \n',Vd);
25
26 Def_sensitivity = l*s/(2*d*Va) ;
27 printf(' The deflection sensitivity = %.5f mm/V \n'
,Def_sensitivity);
28
29 // The answer provided in the textbook is wrong

```

Scilab code Exa 4.7 To find the phase angle in each trace

```

1 // Exa 4.7
2
3 clc;
4 clear;
5
6 // Given
7
8 // Two sinusoidal voltage signals are applied to
// vertical and horizontal plates of CRO
9
10 // Solution

```

```

11 printf('Theta = asin(dvo/DV);
12 // Referring fig(a)
13 Theta_a = asind(0) ; // dvo = 0
14 printf(' Theta for trace shown in fig(a) = %d
15 degrees\n',Theta_a);
15 // Referring fig(b)
16 Theta_b = asind(3/6) ; // dvo = 3 and DV =6
17 printf(' Theta for trace shown in fig(b) = %d
18 degrees\n',Theta_b);
18 // Referring fig(c)
19 Theta_c = asind(1/1) ; // dvo = DV = 1
20 printf(' Theta for trace shown in fig(c) = %d
21 degrees\n',Theta_c);

```

Scilab code Exa 4.8 To find the ratio of frequencies of vertical and horizontal si

```

1 // Exa 4.8
2
3 clc;
4 clear;
5
6 // Given
7
8 // Referring closed Lissajous pattern as shown in
8 // fig .
9 wx = 2; // no of positive x-peak
10 wy = 3; // no of positive y-peak
11
12 // Solution
13
14 fy_fx = wy/wx ;
15 printf(' Ratio of frequencies between vertical and
15 horizontal signals = %.1f \n',fy_fx);

```

Scilab code Exa 4.9 To find the frequency of the vertical signal for a Lissajous pattern

```
1 // Exa 4.9
2
3 clc;
4 clear;
5
6 // Given
7
8 // Referring Lissajous pattern shown in figure
9 wx = 1 ; // Sum of x-peak pattern
10 wy = 2.5; // sum of y-peak pattern
11 fx = 3; // frequency of horizontal signal
12
13 X = wy/wx ; // X is ratio of fy/fx
14
15 // Therefore , fy = 2.5*fx
16
17 printf(' Frequency of vertical signal = %.1f kHz \n
18 ',X*fx);
19 // The answer provided in the textbook is wrong
```

Chapter 5

Special Types of CROs

Scilab code Exa 5.3 To determine the RC value of each section

```
1 // Exa 5.3
2
3 clc;
4 clear;
5
6 // Given
7
8 fs = 10000; // frequency of modulated signal(Hz)
9 fm = 200*10^3; // modulation frequency(Hz)
10 Ri = 10; // Input resistance(ohms)
11 e2_by_e1 = 1.3; // limit for lowest frequency(in %)
12
13 // Solution
14
15 F_lower = fm - fs ;
16
17 printf(' For a double-section filter , \n e2/e1 =
18 1/sqrt(1+(w*Rf*Cf)^2) \n');
19 // Therefore ,
20 function y=f(x)
```

```

21     y =(1/(sqrt(2*pi*F_lower*x)^2+1))-e2_by_e1/100;
22 endfunction
23 [x,v,info] = fsolve(0,f);
24 printf(' The product of Rf*Cf = %.4f sec \n ',x);
25 printf(' Let Rf = 10^5 Ohms, so that attenuation is
26      10:1. Therefore , Cf = ');
27 Cf = x*10^-7;
28 printf(' %.3f pf \n ',Cf*10^12);
29 // The answer provided in the textbook is wrong

```

Scilab code Exa 5.4 Calculate the phase shift between V2 and V1

```

1 // Exa 5.4
2
3 clc;
4 clear;
5
6 // Given
7
8 // The Lissajous pattern
9 Y2 = 2.5; // slope of the major axis(in div)
10 Y1 = 1.2; // slope of the vertical axis(in div)
11
12 // Solution
13
14 printf(' The phase shift V2 and V1 can be given as
15      sin(Theta) = Y1/Y2 \n -where V1 and V2 are
16      voltages applied to X and Y axis respectively \n
17      ');
18
19 Theta = asind(Y1/Y2) ;
20 printf(' Since , the ellipse is lying in the I and
21      the III quadrant , \n The angle is theta or 360-
22      theta , i.e, %.2f or %.2f \n ',Theta,360-Theta);

```

Scilab code Exa 5.5 Determine the power loss for a capacitor

```
1 // Exa 5.5
2
3 clc;
4 clear;
5
6 // Given
7
8 S = 0.6*10; // sensitivity of oscillograph in V per
    cm
9 A = 2; // Area of oscilloscope area in cm^2
10 dx = 4; // x-axis deflection in cm
11 dy = 3; // y-axis deflection in cm
12
13 // solution
14
15 printf(' Ref fig. 5.5(a and b) -If Ic leads Vc by 90
    degree , C will be a lossless ideal capacitor ,
    and it will have infinite resistance R. Therefore
    , Ic is leading Vc by <90 degree . Theta is loss
    of the capacitor \n ');
16 printf(' Power factor = cos(theta) = 1 when theta =
    o degree) \n ');
17
18 pf = 1;
19
20 Vcondenser = (1/sqrt(2)) * S * dx*200; // since one-
    two thousandth od C voltage is applied to the x-
    plates
21 Icondenser = (1/sqrt(2)) * S * 1/100000 ; // since Y
    -plates are impressed with voltage 100000 times
    the magniture of condenser I.
22
```

```

23 Pcondenser = Vcondenser * Icondenser;
24
25 printf( ' If p.f =1, the ellipse could have a major
      axis of %d cm and a minimum axis of %d cm \n' ,2*
      dx ,2*dy );
26
27 printf( ' Total area = %.2f cm^2 \n' ,%pi/4 * 2*dx*2*
      dy );
28
29 printf( ' power loss of the capacitor = %.4f W \n' ,
      Pcondenser*A/(12/%pi));
30
31 // The answer provided in the textbook is wrong

```

Scilab code Exa 5.6 Determine the frequency of the vertical input

```

1 // Exa 5.6
2
3 clc;
4 clear;
5
6 // Given
7
8 // A stationary Lissajous pattern
9 Vy = 6 ; // max value on vertical axis
10 Vx = 5; // max value on horizontal axis
11 fx = 1500; // horizontal input frequency(Hz)
12
13 // Solution
14
15 // fy/fx = No of pts the target meets per bottom(x-
      axis)/No of pts the target meets per bottom(y-
      axis)
16
17 fy = (Vy/Vx)*fx;

```

```
18
19 printf('The frequency of vertical axis = %d Hz \n',
      fy);
```

Scilab code Exa 5.7 Determine the possible phase angles of V2 with respect to V1

```
1 // Exa 5.7
2
3 clc;
4 clear;
5
6 // Given
7
8 b2 = 2.5 ; // Max no of divisions on y-axis
9 b1 = 1.25; // point of intersection on y-axis (div)
10
11 // Solution
12
13 printf(' Let theta be the phase angle of V2 w.r.t V1
           where V1 and V2 are the voltages applied to x
           and y axis respectively \n');
14 // Sin theta = b1/b2;
15 Theta = asind(b1/b2);
16
17 printf(' Therefore , the phase angle of V2 w.r.t V1
           = %d degrees \n. But another possible value is
           (360-theta) i.e. %d degrees \n',Theta,360-Theta);
```

Scilab code Exa 1.8 Estimate the boost required for electron gun accelerating voltage

```
1 // Exa 5.1
2
3 clc;
```

```

4 clear;
5
6 // Given
7
8 E1 = 1/100; // exposure set for grid line impression
    (sec)
9 E2 = 10; // second exposure duration(sec)
10 R = 10^-4; // persistence of CRO screen(sec)
11 I1 = 1; // Trace intensity for exposure 1(candle
    power)
12 I2_normal = 4 ; // trace intensity for normal
    settings(candle power)
13
14 // Solution
15
16 printf(' The emission of light that would be
        received by photographic paper in both exposures
        must be the same \n Also, the product of time
        and light is to be the same. \n');
17 I_req = I1*E1/R;
18 printf(' Hence, the image intensity required = %d \
        \n' ,I_req );
19 I_boost = I_req/I2_normal;
20 printf(' Therefore , the intensity boost required =
        %d times \n' , I_boost);
21
22 printf(' The light emitted is proportional to the
        kinetic energy of the electron while it strikes
        the screen , which is equal to sqrt(V) , where V
        is the velocity while striking \n');
23 printf(' Therefore , the accelerating voltage of
        the accelerating anode should be increased by %d
        times \n' ,sqrt(I_boost));

```

Scilab code Exa 5.8 Calculate the entering velocity of electrons and deflection pr

```

1 // Exa 5.8
2
3 clc;
4 clear;
5
6 // Given
7
8 Va = 2000; // Anode voltage (Volts)
9 Vd = 100; // Deflecting plates voltage (Volts)
10 a = 1.5*10^-2; // axial length in m
11 Sd = 30*10^-2; // screen distance in m
12 Ld = 5*10^-2; // deflecting plates length in m
13
14 // Solution
15
16 // Let ,
17 x = 1.76*10^11 ; // e/m ratio in c/kg
18 L = Sd + Ld/2 ;
19 D = (Ld*L*Vd)/(2*a*Va) ; // Deflection produced(m)
20 Vo = sqrt(2*x*Va); // velocity of electrons in m/kg
21
22
23 printf(' The deflection produced on screen = %.3f cm
24 \n',D*100);
24 printf(' The velocity of the electrons when they
25 enter the field of the deflecting plates = %.4f *
26 10^7 m/kg \n', Vo/10^7);
25
26 // The answer provided in the textbook is wrong

```

Scilab code Exa 5.9 To find the error in the meter indication

```

1 // Exa 5.9
2
3 clc;

```

```

4 clear;
5
6 // Given
7
8 // A saw-tooth waveform is applied to an average
   diode voltmeter(Refer Fig. 5.24)
9
10 printf('For a saw-tooth waveform, the rms value = Vm
           /T \n -where Vm js max voltage value and T being
           the time period \n');
11
12 printf(' Average value Va, 0.433 Vrms \n ');
13
14 printf('Similarly , Iav = 0.433*Vrms/R \n ');
15
16 printf(' Error = 100 * (0.433*Vrms - (0.433/R)*0.45
           / (0.45*(Vrms/R))) = -3.8 percent \n');
17 printf(' The meter reading is 3.8 percent less than
           the expected value \n');

```

Scilab code Exa 5.10 To calculate the velocity of the electron beam in the oscillo-

```

1 // Exa 5.10
2
3 clc;
4 clear;
5
6 // Given
7
8 Va = 2000; // voltage applied to anodes(V)
9 l = 50*10^-3; // length of horizontal plates(m)
10 m = 9.1*10^-31; // mass of electron in kg
11 e = 1.6*10^-19; // velocity of electron in m/s
12 // Max transit time is T/4
13

```

```
14 // Solution
15
16 V = sqrt(2*Va*e/m);
17 Fc = V/(4*l);
18 printf(' The velocity of electron = %.3f * 10^8 m/s
          \n',V*10^-8);
19 printf(' The cutoff frequency = %.3f MHz \n',Fc
          /10^6);
```

Chapter 6

DC and AC Bridges

Scilab code Exa 6.1 To calculate the galvanometer deflection for imbalance in R4

```
1 // Exa 6.1
2
3 clc;
4 clear;
5
6 // Given data
7
8 // Referring bridge shown in fig. 6.8
9 R1 = 1000; // Ohms
10 R2 = 4000; // Ohms
11 R3 = 100; // Ohms
12 R4 = 400; // Ohms
13 Rg = 100; // Ohms
14 Si = 100; // Sensitivity in mm/microAmp
15 V = 3; // Voltage applied
16 R4_imbalance = 1; // resistance added in R4 to
    create imbalance
17
18 // Solution
19
20 printf('The bridge is originally in balance.
```

```

Therefore , R1/R3 = R2/R4 \n');
21 printf('Let there be imbalance in the bridge circuit
           because of increase in value of R4 value by 1
           Ohm \n');
22 printf('Therefore , R4 = 400+X Ohms \n');
23 printf('Thevenins Resistance Rth = (100*1000)
           /(100+1000) + (4000*(400+X))/(4400+X) \n'; // 
           Rth = R1*R3/(R1+R3) + R2*R4/(R2+R4)
24 printf('Neglecting X \n');
25 // Therefore
26 Rth = R1*R3/(R1+R3) + R2*R4/(R2+R4);
27 printf('Rth becomes %d ohms \n', round(Rth));
28 printf('Eth = [R3/(R1+R3) + R4/(R2+R4)]*E; \n');
29 // Applying binomial expansion and neglecting X^2
   term , X is small
30 // Therefore
31 X = R4_imbalance;
32
33 Eth = V*10*X/48400;
34 printf('Applying binomial expansion , Eth = %.2f    V
           \n', round(Eth*10^6));
35 Ig = Eth/(Rth+Rg); // Galvanometer current
36 D = Ig*Si; // Deflection in mm
37 printf('Galvanometer Current Ig = %.3f    A \n', Ig
           *10^6);
38 printf('Galvanometer deflection D = %.2f mm \n', D
           *10^6);
39
40 // The answer provided in the textbook is wrong

```

Scilab code Exa 6.2 To calculate the deflection of the galvanometer caused by the

```

1 // Exa 6.2
2
3 clc;

```

```

4 clear;
5
6 // Given
7
8 // Fig. 6.9 shows wheatstone bridge
9 R1 = 1000; // Ohms
10 R2 = 100; // Ohms
11 R3 = 400; // Ohms
12 Rx = 41; // Ohms(Unknown resistance)
13 V = 1.5; // Voltage supplied
14 Rg = 50; // Galvanometer resistance (ohms)
15 Si = 2; // current sensitivity in mm/microAmp
16
17
18 // Solution
19
20 Rth = (R1*R3/(R1+R3)) + R2*Rx/(R2+Rx);
21 Eth = V*(R3/(R1+R3) - Rx/(R2+Rx));
22 Ig = Eth/(Rth+Rg);
23 d = Ig*Si;
24 printf('The thevenins equivalent resistance = %.1f
          Ohms \n', round(Rth));
25 printf(' The thevenins equivalent voltage = %.1f mV
          \n', abs(Eth*10^3));
26 printf(' The current through the galvanometer = %.2f
          micro Amp \n', abs(Ig*10^6));
27 printf(' The deflection produced by the galvanometer
          caused by the imbalance in the circuit = %.2f mm
          \n', abs(d*10^6));

```

Scilab code Exa 6.3 To find the frequency for which the bridge is in balance and t

```

1 // Exa 6.3
2
3 clc;

```

```

4 clear;
5
6 // Given
7
8 // Fig 6.41 shows an AC bridge
9 R1 = 800; // Ohms
10 C1 = 0.4; // microFarad
11 R2 = 500; // Ohms
12 C2 = 1.0; // microFarad
13 R3 = 1200; // Ohms
14
15
16 // Solution
17
18 // Z = R + j X;
19 // Z1 = 800 + j /(w*C1)
20 // Y2 = 1/R2 - j *(w*C2)
21 //Z3 = 1200
22
23 printf('At balance , Z1/Z4 = Z2/Z3 \n');
24
25 printf(' Rearranging the equation , Z4 = Z1*Z3*Y2 \n'
   );
26 printf(' Equating the real and imaginary parts on
      both sides , \n');
27 Z4 = R1*R3*1/R2;
28 w = sqrt(C1*C2);
29 printf(' The value of R in arm DA to produce a
      balance = %d ohms \n',Z4);
30 printf(' The value of frequency at balance = %.4f Hz
      \n',w/(2*pi));
31
32 // The answers given in textbook for R and f are
   incorrect

```

Chapter 7

Transducers

Scilab code Exa 7.1 To determine the sensitivity of potentiometer

```
1 // Exa 7.1
2
3 clc;
4 clear;
5
6 // Given
7
8 NonLinearity = 1 ; // in percentage
9 P = 5; //Power rating in Watts
10 StepSize = 50; // in Ohms
11 Rmin = 10 ; // in Ohms
12 Rmax = 10000 ; // in Ohms
13
14 // Solution
15
16 printf('Max Error in linearity = Non-linearity = 1
    percent \n');
17 printf(' Therefore , Rp/Rm should be less than 0.1 \n
    ');
18 // If Rp/Rm < 0.1
19 // per_Error = 15 * (Rp/Rm)
```

```

20 // Therefore
21 Rp = (1/15)*Rmax;
22 printf(' If Rp/Rm < 0.1 \n Therefore we can choose a
           potentiometer with a total resistance Rp = %.2f
           Ohms at the maximum. Any value of Rp less than %
           .2f Ohms would be all right as far as the non-
           linearity is concerned \n',Rp,Rp);
23
24 printf(' However, lower the value of Rp lower will
           be the sensitivity. Therefore we choose 650 Ohms
           potentiometer from the family , which will have
           maximum sensitivity and at the same time have non
           -linearity less than 10 percent \n');
25 Rp_selected = 650; // Ohms
26
27 Max_Ecx = sqrt(P*Rp_selected);
28 s = Max_Ecx/360; // Sensitivity
29
30 printf(' The sensitivity of potentiometer = %.2f V/
           degree \n',s);

```

Scilab code Exa 7.2 To determine the linear displacement

```

1 // Exa 7.2
2
3 clc;
4 clear;
5
6 // Given
7
8 l = 50; // length of potentiometer in mm
9 R = 5000; // Total resistance of potentiometer in
            Ohms
10 Rt = 1850; // Resistance of potentiometer in Ohms
11

```

```

12 // Solution
13
14 R_length = R/l ; // Resistance per unit length
15 R_normal = R/(l*10^-3*0.5);
16 printf(' Resistance of normal position = %d Ohms \n',
        ,R_normal);
17 R_change = R_normal - Rt;
18 printf(' Change in resistance = %d Ohms \n',
        ,R_change);
19 Displacement = R_change/R_length ;
20 printf(' The linear displacement when the
            resistance of the potentiometer is 1850 ohms = %
            .2f mm \n',Displacement);
21
22 // The answer provided in the textbook is wrong

```

Scilab code Exa 7.3 To determine the potentiometer resolution

```

1 // Exa 7.3
2
3 clc;
4 clear;
5
6 // Given
7
8 N = 50; // No of turns of potentiometer per mm
9 Number_of_Resolution = 4; // No of resolutions of
                           potentiometer
10
11 // Solution
12
13 Resolution = 1/N;
14 printf(' Resolution of potentiometer = %.3f mm \n',
        Resolution);
15 printf(' 4 resolutions of potentiometer with one

```

```
rotation = %.1f mm \n',10^3*Resolution/
Number_of_Resolution);
```

Scilab code Exa 7.4 Determine the poissions ratio for thin circular wire

```
1 // Exa 7.4
2
3 clc;
4 clear;
5
6 // Given
7
8 G = 3.8; // Gauge factor
9
10 // Solution
11
12 P = (G-1)/2;
13 printf(' Poissons ratio of thin circular/wire of
soft iron = %.1f \n',P);
```

Scilab code Exa 7.5 Determine the gauge factor of the device

```
1 // Exa 7.5
2
3 clc;
4 clear;
5
6 // Given
7
8 L = 0.1 ; // Initial length of wire in m
9 R = 120; // Initial resistance of wire in ohms
10 delta_L = 0.1*10^-3; // change in length of wire in
m
```

```
11 delta_R = 0.21; // change in resistance of wire in  
12 // ohms  
13 // Solution  
14  
15 e = delta_L/L;  
16 G = (delta_R/R)/e;  
17  
18 printf(' The gauge factor of device = %.2f \n',G);
```

Scilab code Exa 7.6 To calculate the percentage change in resistance of strain gau

```
1 // Exa 7.6  
2  
3 clc;  
4 clear;  
5  
6 // Given  
7  
8 S = 1400; // Stress in Kgf/cm^2  
9 E = 2.1*10^6; // Youngs Modulus in Kgf/cm^2  
10 G = 2; // Gauge factor  
11  
12 // Solution  
13  
14 e = S/E;  
15 change_in_R = G*e;  
16  
17 printf(' Percentage change in resistance of strain  
18 gauge = %.3f \n',change_in_R*100);  
19 // The answer provided in the textbook vary due to  
// round off
```

Scilab code Exa 7.7 To find the poissions ratio for strain gauge

```
1 // Exa 7.7
2
3 clc;
4 clear;
5
6 // Given
7
8 Gf = 2 ; // Gauge factor of strain gauge
9 S = 1000; // Stress in kg/cm^2
10 E = 2*10^6; // Youngs Modulus in kg/cm^2
11
12 // Solution
13
14 e = S/E; // strain
15
16 dR_R = e*Gf; // change in resistance
17 // Gf = 1+2u;
18 // Therefore
19 u = (Gf - 1)/2; // poissons ratio
20
21 printf('The percentage change in resistance of
        strain gauge = %.1f \n', dR_R*100);
22 printf(' Poissons ratio = %.2f \n', u);
```

Scilab code Exa 7.8 To determine the change in output voltage

```
1 // Exa 7.8
2
3 clc;
4 clear;
```

```

5
6 R = 200; // strain gauge resistance in Ohms
7 G = 2.5; // Gauge factor
8 RL = 400; // load resistance in Ohms
9 V = 24; // input voltage in volts
10 S = 140; // applied stress in mgf/m^2
11 Y = 200; // Modulus of elasticity in GN/m^2
12
13 // Solution
14
15 V_normal = V*(R/(R+RL));
16
17 printf('Voltage across strain gauge = %d V \n',
V_normal);
18 e = (S*10^-3)/Y;
19 // Strain e = dell_L/L
20 //dell_R/R = G* dell_L/L;
21 // so,
22 dell_R = R*G*e;
23
24
25 //strain gauge under strained condition
26 V_strained = (R+dell_R) * V/(R+dell_R+RL);
27 printf(' Voltage across strain gauge under strained
condition = %.4f ohms \n',V_strained);
28
29 dif = V_normal - V_strained;
30 printf(' Change in output voltage = %.2f mV \n',abs(
dif*10^3));

```

Scilab code Exa 7.9 To determine the resistance at 75 degree celsius along with va

```

1 // Exa 7.9
2
3 clc;

```

```

4 clear;
5
6 // Given
7
8 // A platinum resistance thermometer
9 R1 = 120; // resistance in ohms at 25 c
10 T1 = 25; // temperature in c
11 T2 = 75; // temperature in c
12 Alpha_T = 0.00392; // temperature coefficient of
    resistance at 25 c
13 R3 = 180; // resistance in ohms at unknown temp T3
14
15 // Solution
16
17 R2 = R1*(1+Alpha_T*(T2-T1)); // resistance at 75 c
18 printf(' The resistance at 75 c = %.2f ohms \n',R2
    );
19
20 // now, to get T3 corresponding to R3= 180 ohms
21
22 // R3 = R2*(1+Alpha_T*(T3-T1));
23 // Rearranging above equation to get T3 as
24 T3 = (R3/R1 -1)/Alpha_T + T1;
25
26 printf(' The temperature corresponding to resistance
    180 ohms = %.2f c \n',T3);

```

Scilab code Exa 7.10 To determine the limiting value of resistance k

```

1 // Exa 7.10
2
3 clc;
4 clear;
5
6 // Given

```

```

7
8 // A copper resistance thermometer
9
10 R1 = 15; // resistance in ohms at 20 c
11 T1 = 20; // temperature in c
12 T2 = 175; // max temperature in c
13 Alpha_T = 0.00425; // temperature coefficient of
    resistance at 25 c
14
15 // Solution
16
17 R2 = R1*(1+Alpha_T*(T2-T1)); // resistance at 175
    c
18 printf(' The limiting value of resistance = %.2f
    ohms \n',R2);

```

Scilab code Exa 7.11 To determine the resistance of the thermistor at 40 degree ce

```

1 // Exa 7.11
2
3 clc;
4 clear;
5
6 // Given
7
8 // A thermistor
9 R1 = 120; // resistance in ohms at 25 c
10 T1 = 25; // temperature in c
11 T2 = 40; // temperature in c
12 Alpha_T = -0.05; // temperature coefficient of
    resistance over range 25–50 c
13
14 // Solution
15
16 R2 = R1*(1+Alpha_T*(T2-T1)); // resistance at 175

```

```
    c  
17 printf(' The resistance of thermistor at 40    c = %d  
          ohms \n',R2);
```

Scilab code Exa 7.12 Determine the inductance of the coil

```
1 // Exa 7.12  
2  
3 clc;  
4 clear;  
5  
6 // Given  
7  
8 // A variable inductive transducer  
9 L1 = 2.5; // inductance in mH  
10 N1 = 50; // No of effective turns at L1  
11 N2 = 52; // No of effective turns at L2  
12  
13 // Solution  
14  
15 printf(' Since L directly proportional to N^2 \n');  
16 printf(' L1/N1^2 = L2/N2^2 \n');  
17 printf(' Therefore , L2 i.e , \n');  
18  
19 L2 = L1*(N2/N1)^2;  
20 printf(' The inductance of coil when the effective  
          turns of the coil are 52 = %.2f mH \n',L2);
```

Scilab code Exa 7.13 Determine the inductance of the coil for a variable reluctance

```
1 // Exa 7.13  
2  
3 clc;
```

```

4 clear;
5
6 // Given
7
8 // A variable reluctance-type inductive transducer
9 L1 = 5; // Inductance of transducer in mH
10 lg1 = 1.5; // Length of iron piece in mm
11 d = 0.025; // Distance by which iron piece is moved
               towards electro magnet (mm)
12
13 // Solution
14
15 air_gap = lg1-d;
16 printf(' Length of air gap = %.3f mm \n',air_gap);
17 New_Inductance = L1 + lg1/air_gap;
18
19 printf(' The coil inductance becomes = %.2f mH \n',
           New_Inductance);
20
21 // The answer provided in the textbook is wrong

```

Scilab code Exa 7.14 Determine the sensitivity of LVDT

```

1 // Exa 7.14
2
3 clc;
4 clear;
5
6 // Given
7
8 // An LVDT
9 vo = 2.6; // Output voltage(volts) of LVDT
10 d = 0.4; // displacement in mm
11
12 // Solution

```

```

13
14 printf(' The sensitivity s = RMS value of output
           voltage/Displacement \n');
15
16 S = vo/d; // sensitivity
17
18 printf(' Therefore , s = %.1f V/mm \n',S);

```

Scilab code Exa 7.15 Determine linearity at given load

```

1 // Exa 7.15
2
3 clc;
4 clear;
5
6 // Given
7
8 // An LVDT
9 Vo = 1.25; // Output voltage
10 Dmax = 0.0025; // max. deviation of linearity
11 L = 0.75; // weight of load in kgf
12
13 // Solution
14
15 Linearity = (Dmax/Vo)*100;
16 printf(' The linearity at a given load 0.65 / kgf = %
           .1f percent \n',Linearity);

```

Scilab code Exa 7.16 Determine output voltage for a displacement of 8 mm from cent

```

1 // Exa 7.16
2
3 clc;

```

```

4 clear;
5
6 // Given
7
8 // An LVDT
9 vo = 5; // secondary voltage (volts) of LVDT
10 d = 12.5; // displacement in mm
11 d0 = 8; // displacement from central position in mm
12
13 // Solution
14
15 printf(' The sensitivity s = RMS value of output
           voltage/Displacement \n');
16
17 S = vo/d; // sensitivity
18
19 printf(' Therefore , s = %.1f V/mm \n',S);
20
21 printf(' Output voltage for a displacement of 8mm
           from its central position = %.1f V \n',S*d0);

```

Scilab code Exa 7.17 Determine the sensitivity of LVDT and the pressure

```

1 // Exa 7.17
2
3 clc;
4 clear;
5
6 // Given
7
8 // An LVDT to measure deflection of bellows
9 S1 = 40; // sensitivity in V/mm
10 d = 0.125; // displacement in mm
11 P1 = 0.8*10^6; // pressure in N/m^2
12 Vo2 = 3.5 ; // Output of LVDT for pressure P2

```

```

13
14 // Solution
15
16 // output voltage for the pressure p1
17 Vo1 = S1*d; // in volts
18
19 L_sensitivity = Vo1/P1;
20
21 // For P2 calculations when V = 3.5
22 P2 = Vo2/L_sensitivity;
23
24 printf('The sensitivity of LVDT and pressure when
           the output voltage of LVDT is 3.5 V \n are %.2f
           * 10^-6 V/N/m^2 and %.1f * 10^5 N/m^2
           respectively \n',L_sensitivity*10^6,P2*10^-5);

```

Scilab code Exa 7.18 Determine the displacement for a capacitive transducer

```

1 // Exa 17.18
2
3 clc;
4 clear;
5
6 // Given
7
8 // Capacitive Transducer
9 d = 0.05; // plate separation in mm
10 C = 5*10^-12; // Capacitance in farad
11 dell_C = 0.75*10^-12; // change in capacitance in
                           farad
12
13 // Solution
14
15 // C = e*A/d;
16 eA = C*d;

```

```
17
18 //Now,
19 dell_x = eA/dell_C;
20 printf('The displacement that caused a change in
capacitance is %.3f mm \n',dell_x);
```

Scilab code Exa 7.19 To determine the value of the capacitance

```
1
2 // Exa 17.19
3
4 clc;
5 clear;
6
7 // Given
8
9 // A Capacitive Transducer
10 d = 2.5; // plate separation in mm
11 A = 600; // Area (in mm^2)
12 P = 8*10^5; // Pressure applied in N/m^2
13 x = 0.5; // deflection produced in mm
14 C = 400*10^-12; // Capacitance in farad
15
16 // Solution
17
18 // Since , C = e*A/d
19 e = C*d/A;
20
21 printf('Since we have to find capacitance when no
pressure is applied. At that time plate
separation = %d mm \n', d-x);
22
23 d1 = d-x; // plate separation(mm) after pressure
applied
24 C1 = e*A/d1;
```

```
25
26 printf(' The value of capacitance , C with d = 2mm =
    %d micro farad \n', C1*10^12);
```

Scilab code Exa 7.20 Calculate the sensitivity and separation between the plates

```
1 // Exa 7.20
2
3 clc;
4 clear;
5
6 // Given
7
8 // A Capacitence Transducer
9 A = 5*10^-4; // Area in m^2
10 C = 9.5*10^-12; // Capacitance in farad
11 er = 81; // Relative dielectric constant
12 e0 = 8.854*10^-12; // Absolute dielectric constant
    in F/m
13
14 // Solution
15
16 // C = e0*er*A/d;
17 // Therefore
18 d = e0*er*A/C;
19 printf('The plate separation d = %.2f mm \n', d*10^3)
    ;
20 S = e0*er*A/d^2;
21
22 printf(' Sensitivity s = %.3f * 10^-8 F/m \n', S
    *10^8);
```

Scilab code Exa 7.21 Determine the sensitivity of the arrangement

```

1 // Exa 7.21
2
3 clc;
4 clear;
5
6 // Given
7
8 // A 5-plate transducer
9 n = 5; // no of plates
10 l = 20*10^-3; // length of plate in m
11 b = 20*10^-3; // breadth of plate in m
12 d = 0.25*10^-3; // separation between plates in m
13
14 // Solution
15
16 A = l*b; // Area in mm^2
17 er = 1; // Relative dielectric constant
18 e0 = 8.854*10^-12; // Absolute dielectric constant
    in F/m
19
20 S = (n-1)*e0*er*A/d^2;
21
22 printf('Sensitivity of the arrangement = %.3f * '
    10^-9 F/m \n',S*10^9);
23
24 // The answer provided in the textbook is wrong

```
