

Scilab Textbook Companion for
Electrical And Electronic Systems
by Neil Storey¹

Created by
Ebby George
M.tech
Mathematics
NITK
College Teacher
None
Cross-Checked by
None

November 12, 2017

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Electrical And Electronic Systems

Author: Neil Storey

Publisher: Prentice Hall

Edition: 1

Year: 2004

ISBN: 9780130930460

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
2 basic electric circuits and components	5
5 signals and data transmission	10
6 amplification	13
8 operational amplifier	17
9 digital electronics	21
11 measurement of voltages and currents	26
12 resistance and dc circuits	31
13 capacitance and electric fields	34
14 inductance and magnetic fields	38
15 alternating voltages and currents	42
16 power in ac circuits	47
18 transient behaviour	50

19 semiconductor diodes	52
20 field effect transistors	54
21 bipolar transistors	56
23 electric motors and generators	57

List of Scilab Codes

Exa 2.1	Current I	5
Exa 2.2	Calculate I2	5
Exa 2.3	Calculate V1	6
Exa 2.4	Calculate P	6
Exa 2.5	Calculate R	7
Exa 2.6	Calculate R	7
Exa 2.7	Calculate V	8
Exa 2.8	Calculate V	8
Exa 2.9	Calculate T	9
Exa 5.1	An 32 bit word	10
Exa 5.2	An 32 bit word resolution	11
Exa 5.5	Bandwidth	12
Exa 6.1	Output voltage of and amplifier	13
Exa 6.2	Voltage Gain Av	14
Exa 6.3	Ouput voltage of and amplifier	14
Exa 6.4	Output Power Po	15
Exa 6.5	Power Gain Ap	15
Exa 6.6	Power Gain dB	16
Exa 8.3	Gain	17
Exa 8.4	Input Resistance	17
Exa 8.5	Input Resistance	18
Exa 8.6	Input Resistance	19
Exa 9.8	Decimal Equivalent	21
Exa 9.9	Binary Equivalent	22
Exa 9.10	Decimal equivalent	22
Exa 9.11	A013	23
Exa 9.12	The hexadecimal equivalent of 7046	24
Exa 9.13	Decimal equivalent	24

Exa 9.14	hexadecimal equivalent of 111011011000100	25
Exa 11.1	Peak to Peak Voltage	26
Exa 11.2	Find time	26
Exa 11.3	Calculate v_1	27
Exa 11.4	Calculate P_{av}	28
Exa 11.5	Calculate Resistor	28
Exa 11.6	Calculate Resistor	29
Exa 12.1	Calculate Magnitude	31
Exa 12.2	Calculate V_2	31
Exa 12.5	Voltage V	32
Exa 12.6	Output Current I	33
Exa 13.1	Charge q	34
Exa 13.2	Capacitance C	34
Exa 13.3	Electric Field Strength E	35
Exa 13.4	Calculate D	35
Exa 13.5	Calculate C	36
Exa 13.6	Calculate C	36
Exa 13.7	Calculate E	37
Exa 14.1	Magnetic Field Strength H	38
Exa 14.2	Total Flux ϕ	38
Exa 14.3	Voltage V	39
Exa 14.4	Inductance L	40
Exa 14.5	Inductance in parallel L	40
Exa 14.6	Stored Energy	41
Exa 15.1	Reactance X_L	42
Exa 15.2	Reactance X_L	42
Exa 15.3	Peak Current I_L	43
Exa 15.4	Voltage appear across the capacitor V	43
Exa 15.5	Calculate V	44
Exa 15.6	Calculate V	45
Exa 15.7	Calculate Z	45
Exa 16.1	Active Power P	47
Exa 16.2	Current I	48
Exa 16.3	Current I	48
Exa 18.1	Calculate v	50
Exa 18.2	Calculate t	50
Exa 18.3	Calculate v	51
Exa 19.1	Peak Ripple Voltage	52

Exa 19.2	Peak Ripple Voltage	52
Exa 20.1	Low frequency cut off	54
Exa 20.2	Calculate R_d	55
Exa 21.1	Decimal Equivalent	56
Exa 23.3	Output Voltage V	57

Chapter 2

basic electric circuits and components

Scilab code Exa 2.1 Current I

```
1 clear
2 // Initialisation
3 v1=15.8 //voltage across r1
4 v2=12.3 //voltage across r2
5 r2=220 //resistance R2 in ohm
6
7 // Calculation
8 v=v1-v2 //voltage difference across
   the resistor
9 i=v/r2 //current in ampere
10
11 //Result
12 printf("\n Current , I = %.1f mA",i*1000)
```

Scilab code Exa 2.2 Calculate I2

```

1 clear
2 //Initialisation
3 i1=10 //current in amp
4 i3=3 //current in amp
5
6
7 //Calculation
8 i2=i1-i3 //current in amp
9
10 //Result
11 printf("\n I2 = %d A",i2)

```

Scilab code Exa 2.3 Calculate V1

```

1 clear
2 //Initialisation
3 E=12 //EMF in volt
4 v2=7 //volt
5
6
7 //Calculation
8 v1=E-v2 //volt
9
10 //Result
11 printf("\n V1 = %d V",v1)

```

Scilab code Exa 2.4 Calculate P

```

1 clear
2 //Initialisation
3 i=3 //current in amp
4 r=50 //resistance in ohm
5

```

```

6
7 // Calculation
8 p=(i**2)*r //power in watt
9
10 //Result
11 printf("\n P = %d W",p)

```

Scilab code Exa 2.5 Calculate R

```

1 clear
2 //Initialisation
3 r1=10 //resistance in ohm
4 r2=20 //resistance in ohm
5 r3=15 //resistance in ohm
6 r4=25 //resistance in ohm
7
8
9 //Calculation
10 r=r1+r2+r3+r4 //series
    resistance in ohm
11
12 //Result
13 printf("\n R = %d ohm",r)

```

Scilab code Exa 2.6 Calculate R

```

1 clear
2 //Initialisation
3 r1=10 //resistance in ohm
4 r2=20 //resistance in ohm
5
6
7

```

```

8 //Calculation
9 r=(r1*r2)/(r1+r2)**-1 //
    parallel resistance in ohm
10
11 //Result
12 printf("\n R = %.2 f ohm",r)

```

Scilab code Exa 2.7 Calculate V

```

1 clear
2 //Initialisation
3 r1=200 //resistance in ohm
4 r2=300 //resistance in ohm
5
6
7 //Calculation
8 v=(10*r2)/(r1+r2) //resistance
    in ohm
9
10 //Result
11 printf("\n V = %d V",v)

```

Scilab code Exa 2.8 Calculate V

```

1 clear
2 //Initialisation
3 r1=1*10**3 //resistance in ohm
4 r2=500 //resistance in ohm
5 v1=15 //voltage
6 v2=3 //voltage
7
8 //Calculation

```

```
9 v=v2+((v1-v2)*((r2)*(r1+r2)**-1))
                                     //resistance in ohm
10
11 //Result
12 printf("\n V = %d V",v)
```

Scilab code Exa 2.9 Calculate T

```
1 clear
2 //Initialisation
3 f=50                               //frequency in hertz
4
5
6 //Calculation
7 t=(1*f**-1)                         //time period
8
9
10 //Result
11 printf("\n T = %d ms",t*10**3)
```

Chapter 5

signals and data transmission

Scilab code Exa 5.1 An 32 bit word

```
1 clear
2 // Initialisation
3 n=8 //8 bit
4 n2=16 //16 bit
5 n3=32 //32 bit
6
7 // Calculation
8 c=2**n //value for 8
   bit
9 c2=2**n2 //value for 16
   bit
10 c3=2**n3 //value for 32
   bit
11
12 //Result
13 printf("\n An 8-bit word can take 2^8 = %d values\n",c)
14
15 printf("\n An 16-bit word can take 2^16 = %d values\n",c2)
16
```

```
17 printf("\n An 32-bit word can take 2^32 = %f x 10^9
    values\n",c3/10**9)
```

Scilab code Exa 5.2 An 32 bit word resolution

```
1 clear
2 //Initialisation
3 n=8 //8 bit
4 n2=16 //16 bit
5 n3=32 //32 bit
6
7
8 //Calculation
9 c=2**n //value for 8
    bit
10 p=(1*c**-1)*100 //percent
11 c2=2**n2 //value for 16
    bit
12 p2=(1*c2**-1)*100 //percent
13 c3=2**n3 //value for 32
    bit
14 p3=(1*c3**-1)*100 //percent
15
16 //Result
17 printf("\n An 8-bit word resolution = %.2f percent\n
    ",p)
18
19 printf("\n An 16-bit word resolution = %.4f percent\n
    ",p2)
20
21 printf("\n An 32-bit word resolution = %.9f percent\n
    ",p3)
```

Scilab code Exa 5.5 Bandwidth

```
1 clear
2 //Initialisation
3 f1=7000 //Human Speech
   Frequency Upper limit in HZ
4 f2=50 //Human Speech
   Frequency Lower limit in Hz
5
6 //Calculation
7 B=f1-f2 //Bandwidth in Hz
8
9 //Result
10 printf("\n Bandwidth = %.1f kHz",B*1000**-1)
```

Chapter 6

amplification

Scilab code Exa 6.1 Output voltage of and amplifier

```
1 clear
2 //Initialisation
3 Ri=1000 //Input Resistance of
    amplifier in Ohm
4 Rs=100 //Output Resistance of
    sensor in Ohm
5 Rl=50 //Load Resistance
6 Ro=10 //Output Resistance of
    amplifier in Ohm
7 Av=10 //Voltage gain
8 Vs=2 //Sensor voltage
9
10 //Calculation
11 Vi=Ri*Vs*(Rs+Ri)**-1 //Input Voltage
    of Amplifier
12 Vo=Av*Vi*Rl*(Ro+Rl)**-1 //Output
    Voltage of Amplifier
13
14 //Result
15 printf("\n Ouput voltage of and amplifier = %.1f V",
    Vo)
```

Scilab code Exa 6.2 Voltage Gain Av

```
1 clear
2 //Initialisation
3 Vo=15.2 //Output Voltage of Amplifier
4 Vi=1.82 //Input Voltage of Amplifier
5
6 //Calculation
7 Av=Vo/Vi //Voltage gain
8
9 //Result
10 printf("\n Voltage Gain, Av = %.2 f",Av)
```

Scilab code Exa 6.3 Ouput voltage of and amplifier

```
1 clear
2 //Initialisation
3 Av=10 //Voltage gain
4 Vi=2 //Input Voltage of
   Amplifier
5 Rl=50 //Load Resistance
6 Ro=0 //Output Resistance of
   amplifier in Ohm
7
8
9 //Calculation
10 Vo=Av*Vi*Rl/(Ro+Rl) //Output Voltage
   of Amplifier
11
12 //Result
13 printf("\n Ouput voltage of and amplifier = %.1 f V",
   Vo)
```

Scilab code Exa 6.4 Output Power Po

```
1 clear
2 //Initialisation
3 Vo=15.2 //Output
   Voltage
4 Rl=50 //Load
   Resistance
5
6 //Calculation
7 Po=(Vo**2)/Rl //Output
   Power
8
9 //Result
10 printf("\n Output Power , Po = %.1 f W" ,Po)
```

Scilab code Exa 6.5 Power Gain Ap

```
1 clear
2 //Initialisation
3 Vi=1.82 //Input Voltage of
   Amplifier
4 Ri=1000 //Input Resistance of
   amplifier in Ohm
5 Vo=15.2 //Output Voltage of
   Amplifier
6 Rl=50 //Load Resistance
7
8
9 //Calculation
10 Pi=(Vi**2)*Ri**-1 //Input Power in
   Watt
```

```

11 Po=(Vo**2)*Rl**-1 //Output Power in
    Watt
12 Ap=Po/Pi //Power Gain
13
14
15 //Result
16 printf("\n Power Gain , Ap = %d" ,Ap)

```

Scilab code Exa 6.6 Power Gain dB

```

1 clear
2 //
3 //Initialisation
4 P=1400 //Power gain
5
6 //Calculation
7 pdb=10*log10(P) //Power Gain in dB
8
9 //Result
10 printf("\n Power Gain (dB) = %.1 f dB" ,pdb)

```

Chapter 8

operational amplifier

Scilab code Exa 8.3 Gain

```
1 clear
2 // Initialisation
3 f=20*10**3           //bandwidth frequency in KHz
4
5 // Calculation
6 gain=(10**6)/(f)     //gain
7
8 //Result
9 printf("\n Gain = %d",gain)
```

Scilab code Exa 8.4 Input Resistance

```
1 clear
2 // Initialisation
3 OG=2*10**5           //Open Loop Gain
4 CG=20                //Closed Loop
   Gain
5 OR1=75               //Output
   Resistance
```

```

6 IR1=2*10**6 //Input
  Resistance
7
8 // Calculation
9 AB=OG*CG**-1 //factor (1+
  AB)
10 OR2=OR1/AB //Output
  Resistance
11 IR2=IR1*AB //Input
  Resistance
12
13 //Result
14 printf("\n Output Resistance = %.1f mOhm\n",OR2
  *1000)
15
16 printf("\n Input Resistance = %d GOhm",IR2*10**-9)

```

Scilab code Exa 8.5 Input Resistance

```

1 clear
2 // Initialisation
3 OG=2*10**5 //Open Loop Gain
4 CG=20 //Closed Loop
  Gain
5 OR1=75 //Output
  Resistance
6 IR1=2*10**6 //Input
  Resistance
7 R1=20*10**3 //Resistnce in
  Ohm
8 R2=10**3 //Resistnce in
  Ohm
9
10 // Calculation
11 AB=OG*CG**-1 //factor (1+AB)

```

```

12 OR2=OR1*AB**-1                                //Output
    Resistance
13 //the input is connected to a virtual earth point by
    the resistance R2,
14 //so the input resistance is equal to R 2 ,
15 IR2=R2                                        //Input
    Resistance
16
17 //Result
18 printf("\n Output Resistance = %.1f mOhm\n",OR2
    *1000)
19
20 printf("\n Input Resistance = %d KOhm",IR2*10**-3)

```

Scilab code Exa 8.6 Input Resistance

```

1 clear
2 //Initialisation
3 OG=2*10**5                                    //Open Loop Gain
4 CG=1                                          //Closed Loop Gain
5 OR1=75                                       //Output
    Resistance
6 IR1=2*10**6                                  //Input
    Resistance
7
8 //Calculation
9 AB=OG*CG**-1                                //factor (1+AB)
10 OR2=OR1*AB**-1                              //Output
    Resistance
11 IR2=IR1*AB                                  //Input
    Resistance
12
13 //Result
14 printf("\n Output Resistance = %d uOhm\n",OR2*10**6)
15

```

```
16 printf("\n Input Resistance = %d GOhm", IR2*10**-9)
```

Chapter 9

digital electronics

Scilab code Exa 9.8 Decimal Equivalent

```
1 clear
2 // Initialization
3 ni1=11010 //binary number
4
5 // Calculation
6 ni=ni1
7 deci = 0
8 i = 0
9 while (ni > 0)
10     rem = ni-int(ni/10.)*10
11     ni = int(ni/10.)
12     deci = deci + rem*2**i
13     i = i + 1
14 end
15
16 w=deci //calling the function
17
18 //Declaration
19 printf("\n Decimal Equivalent = %f",w)
```

Scilab code Exa 9.9 Binary Equivalent

```
1 clear
2 // Initialization
3 ni=26 //Decimal number
4
5 // Calculation
6
7 bini = 0
8 i = 1
9 while (ni > 0)
10     rem = ni-int(ni/2)*2
11     ni = int(ni/2)
12     bini = bini + rem*i
13     i = i * 10
14 end
15 w= bini
16
17
18
19 //Declaration
20 printf("\n Binary Equivalent = %d",w)
```

Scilab code Exa 9.10 Decimal equivalent

```
1 clear
2 //Initializaton
3
4 no=34.6875 //decimal number
5 n_int = int(no) // Extract the integral part
6 n_frac = no-n_int // Extract the fractional part
7
```

```

 8 //Calculation
 9
10 bini = 0
11 i = 1
12 ni = n_int
13 while (ni > 0)
14     rem = ni-int(ni/2)*2
15     ni = int(ni/2)
16     bini = bini + rem*i
17     i = i * 10
18 end
19
20 // Function to convert binary fraction to decimal
    fraction
21 binf = 0
22 i = 0.1,
23
24 nf = n_frac
25
26 while (nf > 0)
27     nf = nf*2
28     rem = int(nf)
29     nf = nf-rem
30     binf = binf + rem*i
31     i = i/10
32 end
33
34
35
36 //Result
37 printf("\n Decimal equivalent of 34.6875 = %.4f", (
    bini+binf))

```

Scilab code Exa 9.11 A013

```

1 clear
2 //initialization
3 n='A013' //Hex number
4
5 //Calculation
6 w=hex2dec(n) //Hex to Decimal Conversion
7
8
9 //Result
10 printf("\n W = %d",w)

```

Scilab code Exa 9.12 The hexadecimal equivalent of 7046

```

1 clear
2 //Variable declaration
3 n=7046 //Hex number
4
5 //Calculations
6 h = dec2hex(n) //decimal
   to hex conversion
7
8 //Result
9 printf ("The hexadecimal equivalent of 7046 is %s ",
   h)

```

Scilab code Exa 9.13 Decimal equivalent

```

1 clear
2 //Initializaton
3
4 n='f851' //Hex Number
5
6 //Calculation

```

```

7
8 w=hex2dec(n) //Hex to Decimal Conversion
9 w1 =dec2bin(w)
10
11
12 //Result
13 printf("\n Binary of f851 = %s", (w1))

```

Scilab code Exa 9.14 hexadecimal equivalent of 111011011000100

```

1 clear
2 //Initialiation
3 ni1=111011011000100 //binary number
4
5 //Calculation
6
7 deci = 0
8 i = 0
9 ni=ni1
10 while (ni > 0)
11     rem = ni-int(ni/10.)*10
12     ni = int(ni/10.)
13     deci = deci + rem*2**i
14     i = i + 1
15     end
16 w=deci //calling the function
17 h = dec2hex(w) //decimal
    to hex conversion
18
19 //Result
20 printf("The hexadecimal equivalent of
    111011011000100 is %s", h)

```

Chapter 11

measurement of voltages and currents

Scilab code Exa 11.1 Peak to Peak Voltage

```
1 clear
2 // Initialisation
3 t=0.02 //time period in seconds
   from diagram
4 v1=7 //peak voltage from diagram
5
6
7 // Calculation
8 f=1*t**-1 //frequency in Hz
9 v2=2*v1 // Peak to Peak Voltage
10
11 // Result
12 printf("\n Frequency = %d Hz\n",f)
13
14 printf("\n Peak to Peak Voltage = %d V\n",v2)
```

Scilab code Exa 11.2 Find time

```
1 clear
2 //
3 //Initialisation
4 t=0.05 //time period in seconds
   from diagram
5 v1=10 //peak voltage from
   diagram
6
7
8 //Calculation
9 f1=1*t**-1 //frequency in Hz
10 w1=2*pi*f1 //Angular velocity
11
12 //Result
13 printf("\n %d sin %.1 ft Hz\n",v1,w1)
```

Scilab code Exa 11.3 Calculate v1

```
1 clear
2 //
3 //Initialisation
4 t=0.1 //time period in seconds
   from diagram
5 v1=10 //peak voltage from
   diagram
6 t1=25*10**-3
7
8 //Calculation
9 f1=1*t**-1 //frequency in Hz
10 w1=2*pi*f1 //Angular velocity
11 phi=-(t1*t**-1)*360 //phase angle
12
13 //Result
```

```

14 printf("\n phi = %d degree",phi)
15
16 printf("\n %d sin(%dt%d) Hz\n",v1,w1,phi)

```

Scilab code Exa 11.4 Calculate Pav

```

1 clear
2 //
3 //Initialisation
4 v1=5 //constant 5V
5 r=10 //resistance in
    Ohm
6 vrms=5 //sine wave of 5
    V r.m.s
7 vp=5 //5 V peak
8
9 //Calculation
10 p=(v1**2)*r**-1 //Power in
    watts
11 p2=(vrms**2)*r**-1 //Power average
    in watts
12 a=(vp*sqrt(2)**-1)**2
13 p3=a*r**-1 //Power average
    in watts
14
15 //Result
16 printf("\n (1) P = %.1 f W\n",p)
17
18 printf("\n (2) Pav = %.1 f W\n",p2)
19
20 printf("\n (3) Pav = %.2 f W\n",p3)

```

Scilab code Exa 11.5 Calculate Resistor


```

1 clear
2 //Initialisation
3 fsd1=50*10**-3 //full scale
   deflection of ammeter in Ampere
4 fsd2=1*10**-3 //full scale
   deflection of moving coil meter in Ampere
5 Rm=25 //resistance of moving
   coil meter in Ohms
6
7 //Calculation
8 Rsm=fsd1*fsd2**-1 //sensitivity factor
9 Rsh=Rm*49**-1 //shunt resistor
10
11 //Result
12 printf("\n Therefore , Resistor = %d mOhm\n",round(
   Rsh*10**3))

```

Scilab code Exa 11.6 Calculate Resistor

```

1 clear
2 //Initialisation
3 fsd1=50 //full scale
   deflection of voltmeter in Volts
4 fsd2=1*10**-3 //full scale
   deflection of moving coil meter in Ampere
5 Rm=25 //resistance of moving
   coil meter in Ohms
6
7 //Calculation
8 Rsm=fsd1*fsd2**-1
9 Rse=Rsm-Rm
10
11 //Result
12 printf("\n Rse = %.3 f KOhm\n",Rse*10**-3)
13

```

```
14 printf("\n Therefore , Resistor ~ %d KOhm\n",round(  
    Rse*10**-3))
```

Chapter 12

resistance and dc circuits

Scilab code Exa 12.1 Calculate Magnitude

```
1 clear
2 // Initialization
3 i1=8 //current in
   Amp
4 i2=1 //current in Amp
5 i3=4 //current in Amp
6
7 // Calculation
8 i4=i2+i3-i1 //current
   in Amp
9
10 // Results
11 printf("\n Magnitude , I4 = %d A",i4)
```

Scilab code Exa 12.2 Calculate V2

```
1 clear
2 // Initialization
```

```

3 e=12 //EMF source in volt
4 v1=3 //node voltage
5 v3=3 //node voltage
6
7 //Calculation
8 v2=v1+v3-e //node voltage
9
10 //Results
11 printf("\n V2 = %d V",v2)

```

Scilab code Exa 12.5 Voltage V

```

1 clear
2 //Initialization
3 r1=100 //Resistance in Ohm
4 r2=200 //Resistance in Ohm
5 r3=50 //Resistance in Ohm
6 v1=15 //voltage source
7 v2=20 //voltage source
8
9 //Calculation
10 //Considering 15 V as a source & replace the other
    voltage source by its internal resistance ,
11 r11=(r2*r3)/(r2+r3)**-1 //resistance in
    parallel
12 v11=v1*(r11/(r1+r11)) //voltage
13 //Considering 20 V as a source & replace the other
    voltage source by its internal resistance ,
14 r22=(r1*r3)/(r1+r3)**-1 //resistance in
    parallel
15 v22=v2*(r22/(r2+r22)) //voltage
16
17 //output of the original circuit
18 v33=v11+v22
19

```

```
20
21
22 // Results
23 printf("\n Voltage , V = %.2 f",v33)
```

Scilab code Exa 12.6 Output Current I

```
1 clear
2 // Initialization
3 r1=10 //Resistance in Ohm
4 r2=5 //Resistance in Ohm
5 v2=5 //voltage source
6 i=2 //current in Amp
7
8 // Calculation
9 // Considering 5 V as a source & replace the current
   source by its internal resistance ,
10 i1=v2*(r1+r2)**-1 //current using
   Ohms law
11 // Considering current source & replace the voltage
   source by its internal resistance ,
12 r3=(r1*r2)*(r1+r2)**-1 //resistance in
   parallel
13 v3=i*r3 //voltage using Ohms
   law
14 i2=v3*r2**-1 //current using Ohms
   law
15 i3=i1+i2 //total current
16
17 // Results
18 printf("\n Output Current , I = %.2 f A",i3)
```

Chapter 13

capacitance and electric fields

Scilab code Exa 13.1 Charge q

```
1 clear
2 // Initialization
3 c=10*10**-6 // capacitance
   in Farad
4 v=10 // voltage
5
6 // Calculation
7 q=c*v // charge in
   coulomb
8
9 // Results
10 printf("\n Charge , q = %.1 f uC" ,q*10**6)
```

Scilab code Exa 13.2 Capacitance C

```
1 clear
2 // Initialization
3 l=25*10**-3 //length in meter
```

```

4 b=10*10**-3           //breadth in meter
5 d=7*10**-6           //distance between plates in
    meter
6 e=100                 //dielectric constant of
    material
7 e0=8.85*10**-12     //dielectric constant of air
8
9 //Calculation
10 c=(e0*e*1*b)*d**-1 //Capacitance
11 //Results
12 printf("\n Capacitance , C = %.1f nF" ,c*10**9)

```

Scilab code Exa 13.3 Electric Field Strength E

```

1 clear
2 //Initialization
3 v=100                 //voltage
4 d=10**-5             //distance in meter
5
6 //Calculation
7 e=v*d**-1           //Electric Field
    Strength
8
9 //Results
10 printf("\n Electric Field Strength , E = %d ^7 V/m" ,
    round(e*10**-6))

```

Scilab code Exa 13.4 Calculate D

```

1 clear
2 //Initialization
3 q=15*10**-6          //charge in coulomb
4 a=200*10**-6        //area

```

```

5
6 // Calculation
7 d=q/a //electric flux
   density
8
9 //Results
10 printf("\n D = %d mC/m^2",d*10**3)

```

Scilab code Exa 13.5 Calculate C

```

1 clear
2 // Initialization
3 C1=10*10**-6 //capacitance in
   Farad
4 C2=25*10**-6 //capacitance in
   Farad
5
6 // Calculation
7 C=C1+C2 //capacitance in Farad
8
9 //Results
10 printf("\n C = %d uF",C*10**6)

```

Scilab code Exa 13.6 Calculate C

```

1 clear
2 // Initialization
3 C1=10*10**-6 //capacitance in
   Farad
4 C2=25*10**-6 //capacitance in
   Farad
5
6 // Calculation

```



```
7 C=(C1*C2)/(C1+C2)           //capacitance
   in Farad
8
9 //Results
10 printf("\n C = %.2 f uF",C*10**6)
```

Scilab code Exa 13.7 Calculate E

```
1 clear
2 //Initialization
3 C1=10*10**-6                 //capacitance in
   Farad
4 V=100                        //voltage
5
6 //Calculation
7 E=(0.5)*(C1*V**2)           //Energy stored
8
9 //Results
10 printf("\n E = %.1 f mJ",E*10**3)
```

Chapter 14

inductance and magnetic fields

Scilab code Exa 14.1 Magnetic Field Strength H

```
1 clear
2 // Initialization
3 i=5 //current in ampere
4 l=0.628 //circumference
5
6
7 // Calculation
8 h=i/l //magnetic field
   strength
9
10 // Results
11 printf("\n Magnetic Field Strength , H = %.2 f A/m" ,h)
```

Scilab code Exa 14.2 Toal Flux phi

```
1 clear
2 //
3 // Initialization
```

```

4 i=6 //current in ampere
5 n=500 //turns
6 l=0.4 //circumference
7 uo=4*pi*10**-7 //epsilon zero constant
8 a=300*10**-6 //area
9
10 //Calculation
11 f=n*i //Magnetomotive Force
12 h=f/l //magnetic field
    strength
13 b=uo*h //magnetic induction
14 phi=b*a //flux
15
16 //Results
17 printf("\n (a) Magnetomotive Force , H = %.2 f ampere-
    turns",f)
18
19 printf("\n (b) Magnetic Field Strength , H = %.2 f A/m
    ",h)
20
21 printf("\n (c B = %.2 f mT",b*10**3)
22 printf("\n (d Toal Flux , phi = %.2 f uWb",phi*10**6)

```

Scilab code Exa 14.3 Voltage V

```

1 clear
2 //Initialization
3 l=10*10**-3 //inductance in henry
4 di=3
5
6
7 //Calculation
8 v=l*di //voltage
9
10 //Results

```

```
11 printf("\n Voltage , V = %d mV",v*10**3)
```

Scilab code Exa 14.4 InductanceL

```
1 clear
2 //
3 // Initialization
4 n=400 //turns
5 l=200*10**-3 //circumference
6 uo=4*pi*10**-7 //epsilon zero constant
7 a=30*10**-6 //area
8
9 // Calculation
10 L=(uo*a*n**2)/l //Inductance in henry
11
12 // Results
13 printf("\n Inductance ,L = %d uH",L*10**6)
```

Scilab code Exa 14.5 Inductance in parallelL

```
1 clear
2 //
3 // Initialization
4 l1=10 //Inductance in henry
5 l2=20 //Inductance in henry
6
7 // Calculation
8 ls1=l1+l2 //Inductance in henry
9 lp=((l1*l2)*(l1+l2)**-1) //Inductance in henry
10 // Results
11 printf("\n (a) Inductance in series ,L = %d uH",ls1)
12
```

```
13 printf("\n (b) Inductance in parallel ,L = %.2f uH",  
lp)
```

Scilab code Exa 14.6 Stored Energy

```
1 clear  
2 //  
3 //Initialization  
4 l=10**-2 //Inductance in henry  
5 i=5 //current in ampere  
6  
7 //Calculation  
8 s=0.5*l*i**2 //stored energy  
9  
10 //Results  
11 printf("\n Stored Energy = %d mJ",s*10**3)
```

Chapter 15

alternating voltages and currents

Scilab code Exa 15.1 Reactance X_L

```
1 clear
2 // Initialisation
3 w=1000 //Angular Frequency
4 L=10**-3 //Inductance
5
6 // Calculation
7 Xl=w*L //Reactance
8
9 //Result
10 printf("\n Reactance , Xl = %d Ohm",Xl)
```

Scilab code Exa 15.2 Reactance X_L

```
1 clear
2 //
3
```

```

4 //Initialisation
5 f=50 //frequency
6 C=2*10**-6 //Capacitance
7
8 //Calculation
9 w=2*pi*f //Angular Frequency
10 Xc=1/(w*C) //Reactance
11
12 //Result
13 printf("\n Reactance , Xl = %.2 f KOhm" ,Xc/1000)

```

Scilab code Exa 15.3 Peak Current IL

```

1 clear
2 //
3
4 //Initialisation
5 f=100 //frequency
6 l=25*10**-3 //Inductance
7 V1=5 //AC Voltage (Sine)
8
9 //Calculation
10 w=2*pi*f //Angular Frequency
11 Xl=w*l //Reactance
12 I1=V1*Xl**-1
13
14 //Result
15 printf("\n Peak Current , IL = %d mA" ,I1*10**3)

```

Scilab code Exa 15.4 Voltage appear across the capacitor V

```

1 clear
2 //

```

```

3
4 //Initialisation
5 Ic=2 //sinusoidal Current
6 C=10*10**-3 //Capacitance
7 w=25 //Angular Frequency
8
9
10
11 //Calculation
12 Xc=1/(w*C) //Reactance
13 Vc= Ic*Xc //Voltage
14
15 //Result
16 printf("\n Voltage appear across the capacitor , V =
    %d V r.m.s" ,Vc)

```

Scilab code Exa 15.5 Calculate V

```

1 clear
2 //
3
4 //Initialisation
5 I=5 //sinusoidal Current
6 R=10 //Resistance in Ohm
7 f=50 //Frequency in Hertz
8 L=0.025 //Inductance in Henry
9
10
11 //Calculation
12 Vr=I*R //Voltage across
    resistor
13 Xl=2*%pi*f*L //Reactance
14 VL= I*Xl //Voltage across
    inductor
15 V=sqrt((Vr**2)+(VL**2)) //total voltage

```



```

16 phi=atan(VL*Vr**-1)           //Phase Angle in radians
17
18 //Result
19 printf("\n (a V = %.1 f V",V)
20 printf("\n (b V = %.2 f V",phi*180/%pi)

```

Scilab code Exa 15.6 Calculate V

```

1 clear
2 //
3
4 //Initialisation
5 R=10**4           //Resistance in Ohm
6 f=10**3           //Frequency in Hertz
7 C=3*10**-8        //Capacitance in Farad
8 V=10              //Voltage
9
10 //Calculation
11 Xc=1/(2*%pi*f*C) //Reactance
12 a=((10**4)**2)+(5.3*10**3)**2
13 I=sqrt((V**2)/a) //Current in Amp
14 Vr=I*R           //Voltage
15 Vc=Xc*I          //Voltage
16 phi=atan(Vc/Vr) //Phase Angle in radians
17
18 //Result
19 printf("\n (a) Current , I = %d uA",round(I*10**6))
20
21 printf("\n (b V = %.2 f V",-phi*180/%pi)

```

Scilab code Exa 15.7 Calculate Z

```

1 clear

```

```

2 //
3
4 //Initialisation
5 I=5 //sinusoidal Current
6 R=200 //Resistance in Ohm
7 f=50 //Frequency in Hertz
8 L=400*10**-3 //Inductance in Henry
9 C=50*10**-6 //Capacitance in Henry
10
11 //Calculation
12 Vr=I*R //Voltage across
    resistor
13 Xl=2*%pi*f*L //Reactance
14 Xc=1/(2*%pi*f*C) //Reactance
15 i=Xl-Xc
16
17 //Result
18 printf("\n Z = %d + j %d Ohms",R,i)

```

Chapter 16

power in ac circuits

Scilab code Exa 16.1 Active Power P

```
1 clear
2 //
3
4 //Initialisation
5 V=50 //Voltage
6 I=5 //Current in Ampere r.m.s
7 phase=30 //in degrees
8
9 //Calculation
10 S=V*I //apparent power
11 pf=cos(phase*%pi/180) //power factor
12 apf=S*pf //active power
13
14 //Result
15 printf("\n (a) Apparent power , S = %d VA",S)
16
17 printf("\n (b) Power Factor = %.3 f",pf)
18
19 printf("\n (c) Active Power , P = %.1 f",apf)
```

Scilab code Exa 16.2 Current I

```
1 clear
2 //
3
4 //Initialisation
5 pf=0.75 //power factor
6 S=2000 //apparent power in
   VA
7 V=240 //Voltage in volts
8
9 //Calculation
10 apf=S*pf //active power
11 sin1=sqrt(1-(pf**2))
12 Q=S*sin1 //Reactive Power
13 I=S*V**-1 //Current
14 //Result
15 printf("\n Apparent Power, P = %d W",S)
16
17 printf("\n Active Power, P = %d W",apf)
18
19 printf("\n Reactive Power, Q = %d var",Q)
20
21 printf("\n Current I = %.2f A",I)
```

Scilab code Exa 16.3 Current I

```
1 clear
2 //
3
4 //Initialisation
5 pf=0.75 //power factor
```

```

6 S=1500 //apparent power in
  W
7 V=240 //Voltage in volts
8 P1 = 2000 //apparent power
9 P2 = 1500 //active power
10 Q = 1322 //reactive power
11 I = 8.33 //current in amp
12 f=50 //frequency in
  hertz
13
14 //Calculation
15 Xc=V**2/Q //reactive
  capacitance
16 C=1/(Xc*2*%pi*f) //capacitance
17 I=S*V**-1 //current
18 apf=S*pf //active power
19 //Result
20 printf("\n Apparent Power, S = %d W",S)
21
22 printf("\n Active Power, P = %d W", apf)
23
24 printf("\n Reactive Power, Q = %d var",Q)
25
26 printf("\n Current I = %.2f A",I)

```

Chapter 18

transient behaviour

Scilab code Exa 18.1 Calculate v

```
1 clear
2 // Initialisation
3 c=100*10**-6 //capacitance in farad
4 r=100*10**3 //resistance in ohm
5 v=20 //voltage
6 t=25 //time in seconds
7 e=2.71828 //mathematical constant
8
9 // Calculation
10 T=c*r //time in seconds
11 v1=v*(1-e**(-t*T**-1)) //voltage
12
13 //Result
14 printf("\n v = %.2 f V",v1)
```

Scilab code Exa 18.2 Calculate t

```
1 clear
```

```

2 //
3
4 //Initialisation
5 l=400*10**-3 //inductance in henry
6 i1=300 //current in milliamp
7 r=20 //resistance in ohm
8 v=15 //volt
9 t1=25 //time in seconds
10 e=2.71828 //mathematical constant
11
12 //Calculation
13 T=1/r //time in seconds
14 i=(v*r**-1)*10**3 //current in amp
15 t2=((log(i/(i-i1)))/(log(e)))*0.02 //expression to
    find time t
16
17 //Result
18 printf("\n t = %.1 f mSec",t2*10**3)

```

Scilab code Exa 18.3 Calculate v

```

1 clear
2 //Initialisation
3 c=20*10**-6 //capacitance in farad
4 r=10*10**3 //resistance in ohm
5 v=5 //volt
6 v2=10 //volt
7
8 //Calculation
9 T=c*r //time in seconds
10
11 //Result
12 printf("\n v = %d - %d*e^(-t/%.1 f) V",v2,v,T)

```

Chapter 19

semiconductor diodes

Scilab code Exa 19.1 Peak Ripple Voltage

```
1 clear
2 //Introduction
3 i=0.2 //current in amp
4 C=0.01 //Capacitance in farad
5 t=20*10**-3 //time in sec
6
7 //Calculation
8 dv=i/C //change in voltage w.r.t time
9 v=dv*t //peak ripple voltage
10
11 //Result
12 printf("\n Peak Ripple Voltage = %.1 f V" ,v)
```

Scilab code Exa 19.2 Peak Ripple Voltage

```
1 clear
2 //Introduction
3 i=0.2 //current in amp
```



```
4 C=0.01 //Capacitance in farad
5 t=10*10**-3 //time in sec
6
7 //Calculation
8 dv=i/C //change in voltage w.r.t time
9 v=dv*t //peak ripple voltage
10
11 //Result
12 printf("\n Peak Ripple Voltage = %.1f V",v)
```

Chapter 20

field effect transistors

Scilab code Exa 20.1 Low frequency cut off

```
1 clear
2 //
3
4 //Introduction
5 gm=2*10**-3
6 rd=2*10**3 //resistance in
   ohm
7 C=10**-6 //capacitance in
   farad
8 R=10**6 //resistance in
   ohm
9
10
11 //Calculation
12 G=-gm*rd //Small signal
   voltage gain
13 fc=1/(2*%pi*C*R) //frequency in Hz
14
15 //Result
16 printf("\n Small signal voltage gain = %d ",G)
17
```

```
18 printf("\n Low frequency cut off = %.2 f Hz",fc)
```

Scilab code Exa 20.2 Calculate Rd

```
1 clear
2 //
3
4 //Introduction
5 idd=4*10**-3 //current in
   ampere
6 vo=8 //voltage
7 vdd=12 //voltage
8
9 //Calculation
10 Rd=vo*(vdd-idd)**-1
11
12 //Result
13 printf("\n Rd = %.2 f kOhm",Rd)
```

Chapter 21

bipolar transistors

Scilab code Exa 21.1 Decimal Equivalent

```
1 clear
2 // Initialization
3 ni=11010 //binary number
4
5 // Calculation
6 deci = 0
7 i = 0
8 while ni>0
9     rem = ni-int(ni/10.)*10
10    ni = int(ni/10.)
11    deci = deci + rem*2**i
12    i = i + 1
13
14 end
15 //Declaration
16 printf("\n Decimal Equivalent = %f",deci)
```

Chapter 23

electric motors and generators

Scilab code Exa 23.3 Output Voltage V

```
1 clear
2 //
3 // Initialization
4 vcc=10 //voltage
5 vbe=0.7 //voltage , base-to-
    emitter junction
6 rb=910*10**3 //resistance in ohm
7 hfe=200
8 rc=2.7*10**3 //resistance in ohm
9
10 // Calculation
11 ib=(vcc-vbe)/rb //base current in
    ampere
12 ic=hfe*ib //collector in current
    in ampere
13 vo=vcc-(ic*rc) //output voltage
14
15 // Result
16 printf("\n Output Current , I = %.2 f mA",ic*10**3)
17
18 printf("\n Output Voltage , V = %.1 f V",vo)
```

