

Scilab Textbook Companion for
Electrical Measurements And Measuring
Instruments
by J. B. Gupta¹

Created by
Gundla Keerthi Vani
Mba
Others
Princeton P.g College
College Teacher
None
Cross-Checked by
None

July 31, 2019

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Electrical Measurements And Measuring Instruments

Author: J. B. Gupta

Publisher: S.k. Kataria & Sons.

Edition: 5

Year: 2015

ISBN: 8188458260

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Measurements and Measurement systems	5
3 Error in Measurement and Their Analysis	16
4 Measuring system fundamentals	40
5 Analog ammeters and voltmeters	47
6 Extensions of instrument range	83
7 Analog measurement of power and wattmeters	117
8 Measurement of energy and energy meters	144
9 Measurement of Speed and Frequency and Power factor	154
10 Measurement of Resistance	158
11 Potentiometers	181
12 AC bridges	190
13 Magnetic measurements	217

14 Digital Measurement of Electrical Quantities	232
15 Signal Analyzers	242
16 Cathode Ray Oscilloscope	244

List of Scilab Codes

Exa 1.1	calculate the static sensitivity and deflection factor	5
Exa 1.2	determine the efficiency of the instrument	6
Exa 1.3	Find the range of the instrument and scale range	7
Exa 1.4	determine the measurement sensitivity of the instrument	8
Exa 1.5	Calculate the non linearity as a percent of full scale deflection	8
Exa 1.6	Determine the maximum error	9
Exa 1.7	Determine the temperature	10
Exa 1.8	Find the error in measurment	11
Exa 1.9	Also find the percentage error	12
Exa 1.10	calculate the resistance of voltage measuring device	13
Exa 1.11	Determine actual value of current measured value of current and percentage error in the measurement and accuracy	14
Exa 3.1	Determine the absolute error of measurement	16
Exa 3.2	Determine the true value of power	17
Exa 3.3	Determine the relative error	17
Exa 3.4	Determine the limits of inductance	18
Exa 3.5	calculate the limiting value of current	19
Exa 3.6	Determine the limiting error in per cent	20
Exa 3.7	calculate the limiting error	20
Exa 3.9	Calculate the power dissipated in the resistor and the uncertainty in power	21

Exa 3.10	calculate the limiting error in the computed value of power dissipation	22
Exa 3.11	Determine the resolution in the instrument in volt	23
Exa 3.12	Determine the limiting error of the resultant capacitance	24
Exa 3.13	calculate the uncertainty in the combined resistance	25
Exa 3.14	find the resistance in series and parallel	26
Exa 3.15	power and limiting error of the power	28
Exa 3.16	calculate the nominal power and limiting error of power	29
Exa 3.17	calculate the nominal value of unknown resistance and error in percent and limiting error in ohm	30
Exa 3.18	calculate the absolute error	30
Exa 3.19	determine the magnitude of unknown inductance	32
Exa 3.20	determine the uncertainty in the measurement of Z	33
Exa 3.21	calculate the standard deviation	34
Exa 3.22	find mean and standard deviation and probable error	35
Exa 3.23	find mean and standard deviation and probable error and probable error of mean and range	36
Exa 3.24	determine arithmetic mean and average deviation and variance and probable error of one reading and probable error of the mean	37
Exa 4.1	find the torque	40
Exa 4.2	determine deflection	41
Exa 4.3	determine the suitable dimensions for spring	41
Exa 4.4	determine the deflection	43
Exa 4.5	find the deflection when spring controlled and gravity controlled	44
Exa 4.6	determine the value of current when spring controlled and gravity controlled	45
Exa 4.7	find the deflecting torque	46
Exa 5.1	calculate the deflection	47

Exa 5.2	Determine the spring constant	48
Exa 5.3	find the reading of the voltmeter	49
Exa 5.4	find the effect of the inductance of the meter	50
Exa 5.5	find the percentage error	51
Exa 5.6	Find the value of capacitance	51
Exa 5.7	find the capacitance	53
Exa 5.8	estimate the rate of change of self deflection	53
Exa 5.9	determine the current passing in a moving iron instrument	54
Exa 5.10	calculate the percentage increase of resistance	55
Exa 5.11	find the deflection	56
Exa 5.12	determine the control constant of spring	57
Exa 5.13	calculate the value of current in the wire	58
Exa 5.14	Finding the minimum resistance	59
Exa 5.15	Find the total inductance	60
Exa 5.16	Find the difference in the readings	61
Exa 5.17	Determine the range of the instrument and current and deflection	62
Exa 5.18	Calculate the reading of an electro dynamometer	63
Exa 5.19	Find the magnification	64
Exa 5.20	Determine the magnification	65
Exa 5.21	Determine the current	66
Exa 5.22	Determine the form factor of the current wire	67
Exa 5.23	Estimate the peak and rms values of current and calculate the error	68
Exa 5.24	Determine the capacitance	69
Exa 5.25	determine the reading of moving coil ammeter and moving iron ammeter and hot wire ammeter	69
Exa 5.26	find the reading on hot wire and moving coil in the circuit	70
Exa 5.27	Determine the reading of the ammeter	71
Exa 5.28	Calculate the power dissipated in the rectifying device	72
Exa 5.29	Determine the value of v	74
Exa 5.30	Find the potential difference	75
Exa 5.31	Find the change in capacitance	76

Exa 5.32	Finding the capacitance	77
Exa 5.33	Determine the pd for different deflections . .	78
Exa 5.34	Determine the pd for required to pull the plate three quarter way in	79
Exa 5.35	Calculate the spring constant	80
Exa 5.36	Determine the deflection of the instrument .	81
Exa 5.37	Determine the voltage	82
Exa 6.1	Finding the value of shunt resistance	83
Exa 6.2	Find the current range of instrument and the value of resistance	84
Exa 6.3	Find the shunt resistance required	85
Exa 6.4	Calculate the resistance parallel and series .	86
Exa 6.5	Finding the current range of instrument . .	87
Exa 6.6	Finding the shunt current and the value of R	88
Exa 6.7	Finding the resistance that must put in series	90
Exa 6.8	Calculate the error	91
Exa 6.9	Calculate the error	92
Exa 6.10	Determine the ratio of R and r	93
Exa 6.11	Finding the reading of instruments	94
Exa 6.12	Finding the series resistance would be neces- sary to increase its range	95
Exa 6.13	Determine the capacitance of the condenser multiplier required	96
Exa 6.14	Calculating the necessary values of resistor .	97
Exa 6.15	Explaining conversion of multi range voltmeter	98
Exa 6.16	Calculate the flux density and current ratio and phase angle	99
Exa 6.17	Calculate the flux in the core and ratio error	100
Exa 6.18	Determine the ratio and phase angle errors	101
Exa 6.19	Finding the primary current and ratio error and number of turns of winding	102
Exa 6.20	Determine the primary current and phase an- gle of the transformer	104
Exa 6.21	Calculate the ratio error and phase angle er- ror	105
Exa 6.22	Find the ratio and phase angle errors	106
Exa 6.23	Estimate CT ratio and phase angle error . .	108
Exa 6.24	Find the ratio and phase angle errors	109

Exa 6.25	Determine the phase angle and ratio error .	110
Exa 6.26	Determine the phase angle and ratio error .	111
Exa 6.27	Estimate the iron loss	112
Exa 6.28	Find the phase angle error at no load and load in VA at unity power factor	113
Exa 6.29	Calculate the ratio and phase angle errors .	115
Exa 7.1	Calculate the power	117
Exa 7.2	Calculate the percentage error	118
Exa 7.3	Estimate the percentage error in the wattmeter	119
Exa 7.4	Calculate the percentage error in wattmeter reading	120
Exa 7.5	Finding the error in wattmeter	121
Exa 7.6	Find the actual reading reading on the wattmeter	122
Exa 7.7	Calculate the percentage errors	123
Exa 7.8	Calculate the actual power and current . . .	124
Exa 7.9	Estimate the torque	126
Exa 7.10	Calculate the power factor of inductive load	127
Exa 7.11	Calculate the power absorbed by the load and load impedance and power factor	128
Exa 7.12	Write the suitable transformation ratio7 . .	129
Exa 7.13	Calculate the new multiplying factor of wattmeter	129
Exa 7.14	Calculate the percentage error	130
Exa 7.15	Calculate the input power and power factort	131
Exa 7.16	Calculate the power and power factor of the load	132
Exa 7.17	Find the reading of the each instrument . .	133
Exa 7.18	Find the reading OF TWO wattmeters . . .	134
Exa 7.19	Determine the values of Rand L connected in the phase	135
Exa 7.20	Find the wattage shown by three wattmeters and power taken by the load	136
Exa 7.21	Find the current and reading of two wattmeters connected to measure the power	137
Exa 7.22	Find the power factor of the system and the value of capacitance	138
Exa 7.23	Find the line currents and reading on wattmeters whose current coils are in A and B	139
Exa 7.24	Find the power of the network	141

Exa 7.25	Calculate the wattmeter reading	142
Exa 8.1	Determine the meter constant in revolution	144
Exa 8.2	Calculate the power	145
Exa 8.3	Calculate the error and state whether the meter is fast or slow	146
Exa 8.4	Calculate the full load speed of the meter .	147
Exa 8.5	Determine the load in kWh	147
Exa 8.6	Find out the percentage error	148
Exa 8.7	Calculate the percentage error	149
Exa 8.8	Calculate how many units are recorded as error	150
Exa 8.9	Determine the speed of the disc	151
Exa 8.10	Find out the error in registration and error in rpm of the meter	151
Exa 8.11	Calculate the power factor	152
Exa 9.1	Determine the frequency of output pulses . .	154
Exa 9.2	Determine the speed of the shaft	155
Exa 9.3	Determine the speed of the shaft	155
Exa 9.4	Find the frequency	156
Exa 10.1	Calculate the apparent resistance and actual resistance and the error	158
Exa 10.2	Determine the resulting error	159
Exa 10.3	Determine the value of unknown resistance .	160
Exa 10.4	Determine the value of resistor under test .	161
Exa 10.5	Determine the value of resistor under test .	162
Exa 10.6	Calculate the unknown resistance	163
Exa 10.7	Determine the value of unknown resistance	164
Exa 10.8	Determine the value of unknown resistance	164
Exa 10.9	Determine the dials required to adjusted for obtaining the required accuracy	165
Exa 10.10	Calculate the limiting values of unknown resistance	166
Exa 10.11	Find the magnitude and direction of the current flowing through galvanometer	167
Exa 10.12	Determine the sensitivity of the bridge . . .	168
Exa 10.13	Determine the ratio of galvanometer sensitivities	169
Exa 10.14	Determine the smallest change in the resistance	170

Exa 10.15	Determine the value of resistance	171
Exa 10.16	Determine the maximum value of the resistance and internal resistance	172
Exa 10.17	Calculating how far are the balance positions	173
Exa 10.18	Calculate the insulation resistance of the cable	174
Exa 10.19	Calculate the insulation resistance of the cable	175
Exa 10.20	Calculate the insulation resistance of the cable	175
Exa 10.21	Calculate the value of R	176
Exa 10.22	Calculate the insulation resistance of the cable	177
Exa 10.23	Determine Rsh AND Rse AND maximum value of Rsh and scale error	178
Exa 10.24	Determine the value of current	179
Exa 11.1	Determine emf and current and voltage and percentage error in ammeter and voltmeter .	181
Exa 11.2	Calculate the resolution of potentiometer .	182
Exa 11.3	Calculate the working current and resistance and measurement range and the resolution of the instrument	183
Exa 11.4	Calculate the inductance of the coil	185
Exa 11.5	Calculate the resistance and reactance of the coil	185
Exa 11.6	Calculate the resistance and reactance of the coil	186
Exa 11.7	Determine the core loss in the choke coil . .	187
Exa 11.8	Determine the true reading of the wattmeter and the load power factor	188
Exa 12.1	Determine whether to balance the bridge . .	190
Exa 12.2	Determine whether or not the bridge is complete balance	191
Exa 12.3	Find the resistance and inductance of the coil	193
Exa 12.4	Find the resistance and inductance	194
Exa 12.5	Find the resistance and inductance of the unknown resistance	194
Exa 12.6	Find the resistance and inductance	195
Exa 12.7	Find the resistance and inductance	196
Exa 12.8	Find the resistance and inductance	197
Exa 12.9	Find the Resistance and Capacitance	198

Exa 12.10	Find the series equivalent inductance and resistance of the network	198
Exa 12.11	Find the resistance and inductance of the choke coil	199
Exa 12.12	Derive the balance condition and calculate the effective impedance of the specimen . .	200
Exa 12.13	Find out the phase angle error and unknown capacitance	201
Exa 12.14	Calculate the resistance and capacitance and also the dissipation factor of the unknown capacitor	202
Exa 12.15	Calculate the power factor	203
Exa 12.16	Derive the variable resistance	204
Exa 12.17	Find the equivalent resistance	205
Exa 12.18	Find the dissipation factor	206
Exa 12.19	Calculate the capacitance and dielectric loss angle of bushing	207
Exa 12.20	Calculate the power factor and equivalent series resistance of the capacitor	207
Exa 12.21	Find the resistance and inductance of the coil	208
Exa 12.22	Calculate the value of L and C	209
Exa 12.23	Determine the resistive and reactive component of unknown impedance	210
Exa 12.24	Determine the self capacitance and inductance of the coil	211
Exa 12.25	Determine the self capacitance	211
Exa 12.26	Determine the self capacitance of the coil . .	212
Exa 12.27	Determine the effective inductance and resistance of unknown coil	213
Exa 12.28	Determine the percentage error	214
Exa 12.29	Determine the self capacitance	214
Exa 12.30	Determine the self capacitance	215
Exa 13.1	Find the magnetic field strength	217
Exa 13.2	Find the constant of the galvanometer . . .	218
Exa 13.4	Find the capacity of the condenser	219
Exa 13.5	Calculate the shunt required for the use with search coil	219

Exa 13.6	Find the resistance of the shunt to be connected in parallel with the flux meter	220
Exa 13.7	Calculate the flux density in the core	221
Exa 13.8	Find the relative permeability of the specimen	222
Exa 13.9	Compute the flux density and relative permeability	223
Exa 13.10	Calculate the relative permeability	224
Exa 13.11	Find the quantity of the electricity	225
Exa 13.12	Calculate the hysteresis loss in watts per kg	226
Exa 13.13	At what frequency will the iron loss be doubled if the flux density is kept the same . . .	227
Exa 13.14	Estimate the hysteresis and eddy current losses	228
Exa 13.15	Calculate the eddy current loss per kg	229
Exa 13.16	Calculate the percentage change in hysteresis loss	229
Exa 13.17	Calculate the iron in watts loss per kg	230
Exa 14.1	Determine the full scale output	232
Exa 14.2	Find out the voltage	233
Exa 14.3	Determine the display indication	234
Exa 14.4	Calculate the frequency of the system	235
Exa 14.5	Find the maximum likely errors	236
Exa 14.6	Calculate the resolution	237
Exa 14.7	Find the resolution	238
Exa 14.8	Find the resolution	239
Exa 14.9	Find the resolution	240
Exa 15.1	Find the dynamic range	242
Exa 15.2	Find the minimum detectable signal of a spectrum	242
Exa 16.1	Find the rms value and also the electrostatic deflection sensitivity	244
Exa 16.2	Find the input voltage	245
Exa 16.3	Calculate the maximum velocity of electrons	246
Exa 16.4	Find the beam speed and deflection sensitivity of the tube and deflection factor	246
Exa 16.5	Determine the deflection sensitivity	247
Exa 16.6	Deduce the formula used	248
Exa 16.7	Calculate the deflection voltage	249

Exa 16.8	Find the Phase angle	249
Exa 16.9	Find the pulse duration	251
Exa 16.10	Find the ratio of frequencies of vertical and horizontal signals	251
Exa 16.11	Find out the frequency of vertical signal . .	252
Exa 16.12	Determine the frequency of vertical input . .	253
Exa 16.13	Determine the mark to space ratio of the pulse	253

Chapter 1

Measurements and Measurement systems

Scilab code Exa 1.1 calculate the static sensitivity and deflection factor

```
1 //


---


2 //chapter 1 example 1
3
4 clc;
5 clear all;
6
7 //variable declaration
8 d = 2.4; //magnitude of output
   response in mm
9 R = 6; //magnitude of input in
10
11 //calculations
12 S = d/(R); //static sensitivity in mm/
13 D = R/(d); //deflection factor in /mm
14
15 //result
16 mprintf("static sensitivity = %3.2f mm/ ",S);
```



```
17 mprintf("\n deflection factor = %3.2f /mm",D);
18
19 //
```

Scilab code Exa 1.2 determine the efficiency of the instrument

```
1 //
2 //chapter 1 example 2
3
4 clc;
5 clear all;
6
7 //variable declarations
8 If = 5; //full-scale reading of instrument
   in A
9 Ra = 0.01; //ammeter resistance in ohm
10
11
12 //calculations
13 Pf = ((If)^2)*(Ra); //power
   sonsumption for full-scale deflection is W
14 n = (If)/(Pf); //instrument
   efficiency in A per watts
15
16 //result
17 mprintf("power sonsumption for full-scale deflection
   = %3.2f W",Pf);
18 mprintf("\ninstrument efficiency = %3.0f A per watts
   ",n);
19
20
```

21 //

Scilab code Exa 1.3 Find the range of the instrument and scale range

1 //

2 //chapter 1 example 3

3

4 `clc`;

5 `clear all`;

6

7 //variable declaration

8 `n = 100;` //highest multiplier switch
in mA

9 `N = 100;` //number of divisions

10

11

12 //calculations

13 `R = (N*10-3)*n;` //Range of
instrument in A

14 `S = 0-n;` //scale range

15

16 //result

17 `mprintf("Range of instrument = %3.2f A",R);`

18 `mprintf("\nScale Range = 0%3.2f",S);`

19

20 //

Scilab code Exa 1.4 determine the measurement sensitivity of the instrument

```
1 //


---



---


2 //chapter 1 example 4
3
4 clc;
5 clear all;
6
7 //variable declaration
8 T1 = 200; //Temperature in C
9 T2 = 225; //Temperature in C
10 R1 = 305; //Resistance in
11 R2 = 310; //Resistance in
12
13 //calculations
14 S = (R2-R1)/(T2-T1); //dr/dt in per C
15
16 //result
17 mprintf("measurement sensitivity S = %3.2f per
18 C ",S);
19
20 //


---



---


```

Scilab code Exa 1.5 Calculate the non linearity as a percent of full scale deflect

```
1 //


---



---


2 //chapter 1 example 5
3
```

```

4  clc;
5  clear all;
6
7  //variable declaration
8  R0      = 100;           //resistance in
9  R100    = 138.50;      //resistance in
10 R200    = 175.83;      //resistance in
11 T1      = 0;           //Temperature in
    C
12 T2      = 200;        //Temperature in
    C
13 T3      = 100;        //Temperature in
    C
14
15 //calculations
16 T        = ((T2-T1)/(R200-R0))*(R100-R0); //change
    in temperatre in C
17 D        = T-T3;      //
    deviation in C at T3 temperature
18 p        = (D/(T2))*100; //per cent
    full scale deflection non linearity in %
19
20 //result
21 mprintf("per cent full scale deflection %3.4f
    percent",p);
22
23
24 //

```

Scilab code Exa 1.6 Determine the maximum error

```
1 //
```

```

2 //chapter 1 example 6
3
4 clc;
5 clear all;
6
7 //variable declaration
8 l    = 0.2;           //percent linearity
9 r    = 300;          //full-scale reading
10 R    = 20;           //resistance in k
11 V    = 2;            //voltage in V
12
13 //calculations
14 d    = (l*r)/(100);  //maximum displacement
    deviation in
15 R1    = (l*R)/(100); //maximum resistance
    displacement in
16 //a displacement of 300 corresponds to 2V ,therefore
    0.6 corresponds to a voltage of (0.6/300)*2
17 ev    = (d/(r))*V;   //maximum voltage error in
    mV
18
19 //result
20 mprintf("maximum displacement deviation =%3.1f    ",
    d);
21 mprintf("\nmaximum resistance displacement %3.2f k
    ",R1);
22 mprintf("\n maximum voltage error  %3.2f mV", (ev
    *10^3));
23
24 //

```

Scilab code Exa 1.7 Determine the temperature

```
1 //


---



---


2 //chapter 1 example 7
3
4 clc;
5 clear all;
6
7 //variable declaration
8 t1      =500;           //temperature in C
9 t2      =1250;         //temperature in C
10 r      = 0.12;        //dead space in pyrometer in per
                          cent of span
11
12 //calculations
13 S      = t2-t1;        //span the algebraic
                          difference between the upper and lower range
                          values
14 d      = (r/(100))*S;  //dead space in C
15
16 //result
17 mprintf(" a change of %3.2f C must occur before it
          is detected",d);
18
19 //
```

Scilab code Exa 1.8 Find the error in measurment

```
1 //
```

```

2 //chapter 1 example 8
3
4 clc;
5 clear all;
6
7 //variable declaration
8 E0    = 12;           //open -circuit voltage in V
9 R0    = 1;           //output resistance in k
10 RL   = 25;          //output resistance in k
11
12
13 //calculations
14 EL    = E0/(1+(R0/RL)); //measured value of
    voltage in V
15 Er    = EL-E0;           //error in
    measurement in V
16 p     = ((EL-E0)/(E0))*100; //percentage
    error in %
17
18 //result
19 mprintf("measured value of voltage = %3.3f V",EL);
20 mprintf("\nerror in measurement= %3.3f V",Er);
21 mprintf("\npercentage error = %3.3f percent low",p)
    ;
22
23
24 //

```

Scilab code Exa 1.9 Also find the percentage error

```

1 //

```

```

2 //chapter 1 example 9
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 s = 4000; //instrument sensitivity in k
10 R = 10; //range of scale
11 R0 = 20; //output resistance in k
12 E0 = 7.5; //open circuit voltage
13
14 //calculations
15 RL = s*R; //instrument resistance in k
16 RL1 = RL*10^-3;
17 EL = E0/(1+(R0/(RL1))); //measured value of
    voltage in V
18 p = ((EL-E0)/(E0))*100; //percentage
    error in %
19
20 //result
21 mprintf("measured value of voltage = %3.2f V",EL);
22 mprintf("\npercentage error = %3.2f V percentage
    low",p);

```

Scilab code Exa 1.10 calculate the resistance of voltage measuring device

```

1 //


---


2 //chapter 1 example 10
3
4 clc;
5 clear all;
6

```



```

7 //variable declaration
8 E0    = 50;           //internal voltage source in V
9 R0    = 100;         //resistance in k
10 r    = 99;          //accuracy in %
11
12 //calculations
13 //Em = E0/(1+(R0/RL))
14 //Em = E0*(r in %)
15 //E0/(1+(R0/RL)) = E0*(r in %)
16 Em    = (E0*r)/(100);
17 x     = E0/(Em);
18 y     = x-1;
19 Rm    = R0/(y);      //resistance of voltage in k
20
21 //result
22 mprintf("resistance of voltage = %3.2f k ",Rm);

```

Scilab code Exa 1.11 Determine actual value of current measured value of current a

```

1 //


---


2 //chapter 1 example 11
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 E    = 20;           //voltage in V
10 R1   = 2;           //resistance in k
11 R2   = 2;           //resistance in k
12 R3   = 1;           //resistance in k
13 R    = 200;         //resistance whe current is
                       connected to terminals in

```

```

14
15
16 //calculations
17 Io      = (E/(R1+((R2*R3)/(R2+R3))))*(R2/(R2+R3));
           //nortons equivalent current in k
18 Rout    = R3+((1/(R1))+1/(R2));           //output
           resistance in k
19 IL      = Io*((R1*1000)/((R1*1000)+R));   //
           measured value of current in mA
20 e       = ((IL-Io)/(Io))*100;           //
           percentage error in %
21 A       = 100+e;                       //accuracy of
           measurement in %
22
23 //result
24 //mprintf("resistance of voltage = %3.2f k ",Rm);
25
26 mprintf("actual value of current flowing through
           1000 is %3.2f mA",Io');
27 mprintf("\nmeasured value of current when 200 is
           connected is %3.2f mA",IL);
28 mprintf("\npercentage error = %3.1f percentage(low)
           ",e);
29 mprintf("\naccuracy of measurement = %3.1f
           percentage ",A);

```

Chapter 3

Error in Measurement and Their Analysis

Scilab code Exa 3.1 Determine the absolute error of measurement

```
1 //


---


2 //chapter 3 example 1
3
4 clc;
5 clear all;
6
7 //variable declaration
8 Am      = 10.25;           //measured value in
9 A       = 10.22;         //True value in
10
11 //calculations
12 dA      = Am-A;          //absolute error in
13
14 //result
15 mprintf("abslotue error = %3.2 f    ",dA);
```

Scilab code Exa 3.2 Determine the true value of power

```
1  clc;
2  clear all;
3
4  //variable declaration
5  Am      = 25.34;           //measured value in
    watts
6  dA      = -0.11;         //absolute error in
    watts
7
8
9  //calculations
10 A       = Am-dA;         //True value in
    wttts
11
12 //result
13 mprintf("abslotue error = %3.2f watts",A);
```

Scilab code Exa 3.3 Determine the relative error

```
1  //


---



---


2  //chapter 3 example 2
3
4  clc;clear all;
5
6
7  //variable declaration
8  Am      = 205.3*10**-6;   //measured
    value in
```

```

9 A      = 201.4*10**-6;           //True value
   in
10
11 //calculations
12 e0     = Am-A;                 //absolute error in
13 r      = (e0/(A))*100;        //relative error in
   %
14
15 //result
16 mprintf("abslotue error = %3.2e F ",e0);
17 mprintf("\nrelative error = %3.2f percentage",r);

```

Scilab code Exa 3.4 Determine the limits of inductance

```

1 //


---


2 //chapter 3 example 4
3 clc;
4 clear all;
5
6 //variable declaration
7 ep     = 5;                    //percentage error
8 Am     = 20;                  //measuredd value in H
9
10 //calculations
11 er     = ep/(100);           //relative error
12 //A = Am+dA
13 //dA = er*Am
14 A      = Am*(1+er);          //limiting value of
   inductance in H
15 A1     = Am*(1-er);          //limiting value of
   inductance in H
16

```

```

17 //result
18 mprintf("limits of inductance =%3.2 f H",A);
19 mprintf("\n and = %3.2 f H",A1);

```

Scilab code Exa 3.5 calculate the limiting value of current

```

1 //


---


2 //chapter 3 example 5
3 clc;
4 clear all;
5
6 //variable declaration
7 er      = 1.5*10^-2;           //accuracy
8 A1      = 10;                 //current
   in A
9 A2      = 2.5;               //current in
   A
10
11 //calculations
12 dA      = er*A1;             //magnitude
   of limiting error of the instrument
13 er1     = dA/(A2);          //magnitude of
   current
14 A11     = A2*(1+er1);       //current
   in A
15 A12     = A2*(1-er1);       //current
   in A
16 er2     = (dA/(A2))*100;    //limiting
   error in %
17
18 //result
19 mprintf("limiting values of current =%3.2 f A and
   %3.2 f",A11,A12);

```

```
20 mprintf(" \nlimiting error = %3.1f percentage ',er2);
```

Scilab code Exa 3.6 Determine the limiting error in per cent

```
1 //  
2 //chapter 3 example 6  
3  
4 clc; clear all;  
5  
6 //variable declaration  
7 e      = 0.01;           //acuuracy  
8 v      = 150;           //voltage in V  
9 v1     = 83;           // measured voltage in V  
10  
11 //calculations  
12 dV     = e*v;           //magnitude of the  
    limiting error of the instrument in V  
13 er     = (dV/(v1))*100; //percentage limiting  
    error at v1 voltage in %  
14  
15 //result  
16 mprintf("limmiting error in case of 83V is = %3.2 f  
    percentage ',er);
```

Scilab code Exa 3.7 calculate the limiting error

```
1 //  
2 //chapter 3 example 7  
3
```

```

4
5 clc;clear all;
6
7 //variable declaration
8 er      = 0.01;           // limiting error
9 P       = 1000;          //power in watts
10 P1     = 100;           // true power in watts
11
12 //calculations
13 dP      = er*P;          //magnitude of
    instrument error of the instrument watts
14 eP      = (dP/(P1))*100; //percentage limiting
    error at 100 W power in %
15
16 //result
17 mprintf("percentage limiting error at 100 W power =
    %3.2f percentage ',eP);;

```

Scilab code Exa 3.9 Calculate the power dissipated in the resistor and the uncertainty

```

1 //


---


2 //chapter 3 example 9
3
4 clc;clear all;
5
6 //variable declaration
7 v       = 110.2;         //voltage drop in V
8 i       = 5.3;          //current in A
9 v1      = 0.2;          //uncertainty in
    measurements in V
10 i1     = 0.6;          //uncertainty in
    measurments in A
11

```



```

12 //calculations
13 erv      = (v1/(v))*100;      //limiting error to
    voltage drop in %(ranging + to -)
14 eri      = (i1/(i))*100;      //limitng error in
    current in %(ranging + to -)
15 P        = v*i;              //power dissipated
    in the resistor in W
16 eP       = (erv+eri);        //limting error in
    the power dissipation in %(ranging + to -)
17 p        = eP*P*10^-2;      //power with
    limiting error in W
18 e        = erv+eri;        //limiting
    error in power dissipation
19 P1       = P+p;              //power
    dissipation is given in W
20 P11      = P-p;              //power
    dissipation is given in W
21
22 //result
23 mprintf("power dissipated = %3.2f W ,P);
24 mprintf("\nlimiting error in the power dissipation =
    %3.1f percentage",e)
25 mprintf("\nuncertainty in power ranging in %3.2f W
    to %3.2f",P11,P1);

```

Scilab code Exa 3.10 calculate the limiting error in the computed value of power d

```

1 //


---


2 //chapter 3 example 10
3
4 clc;clear all;
5
6 //variable declaration

```

```

7 R      = 100;           //resistance in
8 dR      = 0.2;         //resistance error in (
    ranging + to -)
9 I      = 2;           //current in A
10 dI     = 0.01;       //error in current in A(ranging
    + to -)
11
12 //calaculatons
13 eR     = (dR/(R))*100; //percentage limiting
    error to resistance in %(ranging + to -)
14 eI     = (dI/(I))*100; //percentage limiting
    error to current in %(ranging + to -)
15 P      = (I^2)*R;     //power dissioation in
    W
16 eP     = (2*eI)+eR;   //worst ossible
    combination of errors the limiting error in the
    power dissipation in %
17 p      = (eP*10^-2)*P; //error in
    power in watts
18 P1     = P+p;        //power dissipation
    in W
19 P2     =P-p;        //power dissipation
    in W
20
21 //result
22 mprintf("limiting error = %3.2f percentage ',eP);
23 mprintf("\npower dissipation %3.2f W %3.2f W",P2,P1)
    ;

```

Scilab code Exa 3.11 Determine the resolution in the instrument in volt

```

1 //


---


2 //chapter 3 example 11

```

```

3
4 clc;clear all;
5
6 //variable declaration
7 V      = 200;      //full-scale reading i V
8 n      = 100;     //number of divivsons of scale
9
10 //calculations
11 n1     = V/(n);   //1 scale division in V
12 R      = n1/(5); //1/5 th of scale division in V
13
14 //result
15 mprintf("resolution = %3.2 f V",R);

```

Scilab code Exa 3.12 Determine the limiting error of the resultant capacitance

```

1 //


---


2 //chapter 3 example 12
3
4 clc;clear all;
5
6 //variable declaration
7 u      = 150;     //capacitance in uF
8 du     = 2.4;    //capacitance in uF
9 v      = 120;    //capacitance in uF
10 dv    = 1.5;    //capacitance in uF
11
12 //calculations
13 y      = u+v;    //resultant capacitance when
    capacitors are connectedd in parallel in uF
14 dy     = du+dv; //limiting error in uF(ranging +
    to -)
15 er     = (dy/(y))*100; //relative limiting error in %

```

```

    (ranging + to -)
16
17 //result
18 mprintf("limiting error of the resultant capacitance
    = %3.2f percentage ',er);

```

Scilab code Exa 3.13 calculate the uncertainty in the combined resistance

```

1 //


---


2 //chapter 3 example 13
3 clc;clear all;
4
5 //variable declaration
6 R1    = 1000;           //resistance in
7 R2    = 500;           //resistance in
8 eR1   = 1;             //error resistance
9 eR2   = 1;             //error resistance
10
11 //calculations
12 R     = (R1*R2)/(R1+R2);           //resistance in
13 X     = R1*R2;
14 Y     = R1+R2;
15 dX    = (eR1+eR2);                 //error in X
16 //dY   = (dR1/Y)+(dR2/Y);
17 //dY   = (R1/Y)*(dR1/R1)+((R2/Y)*(dR2/R2)
18 dY    = ((R1/(Y))*(eR1))+((R2/(Y))*(eR2));           //
    error in Y
19 eP    = dX+dY;                       //
    percentage error in equivalent parallel resistance
    in %
20 e     = R*(eP/(100));                 //error(
    maximum possible) in equivalent parallel
    resistance in

```

```

21
22
23 //result
24 mprintf("percentage error = %3.2f percentage",eP);
25 mprintf("\nerror in equivalent parallel resistance =
    %3.2f    ",e);

```

Scilab code Exa 3.14 find the resistance in series and parallel

```

1 //


---


2 //chapter 3 example 14
3
4 clc;clear all;
5
6 //variable declaration
7 R1      = 200;           //resistance in
8 R2      = 100;         //resistance in
9 R3      = 50;          //resistance in
10 dR1     = 5;           //change in
    resistance(dR1/R1) in %
11 dR2     = 5;           //change in
    resistance(dR2/R2) in %
12 dR3     = 5;           //change in
    resistance(dR3/R3) in %
13 y1      = 20000;
14 y2      = 5000;
15 y3      = 10000;
16
17
18 //calculations
19 Rse     = R1+R2+R3;    //equivalent
    resistance in
20 R       = ((R1/(Rse))*(dR1))+((R2/(Rse))*(dR2))+((R3

```

```

21 e      = Rse*(R/(100));           //
      relative limiting error of series equivalent in

22 X      = R1*R2*R3;
23 Y      = (R2*R3)+(R1*R3)+(R1*R2);
24 RP     = X/(Y);                   //
      equivalent resistance in

25 eX     = dR1+dR2+dR3;             //
      error in X in %

26 dy1    = dR1+dR2;                 //
      error(dy1/y1) n y1 in %

27 dy2    = dR2+dR3;                 //
      error(dy2/y2) in y2 in %

28 dy3    = dR3+dR1;                 //
      error(dy3/y3) in y3 in %

29 eY     = ((y1/(Y))*(dy1))+((y2/(Y))*(dy2))+((y3/(Y)
      )*(dy3));                       //percentage error in %

30 pemax  = eX+eY;                   //
      percentage error (maximum possible) in equivalent
      parallel resistance in %

31 emax   = RP*(pemax/(100));         //error
      maximum possible in equivalent parallel
      resistance in

32
33 //result
34 mprintf("equivalent resistance = %3.2f ",Rse);
35 mprintf("\nrelative limiting error of series
      resistance = %3.2f percentage",R);
36 mprintf("\nrelative limiting error of series
      equivalent = %3.2f ",e);
37 mprintf("\npercentage error (maximum possible) in
      equivalent parallel resistance= %3.2f percetage",
      pemax);
38 mprintf("\nerror maximum possible in equivalent
      parallel resistance =%3.4f ',emax);

```

Scilab code Exa 3.15 power and limiting error of the power

```
1 //


---



---


2 //chapter 3 example 15
3
4 clc;clear all;
5
6 //variable decelaration
7 er      = 0.015;           //limiting error
8 V       = 100;           //range of
    voltmeter in V
9 I       = 150;           //range of ammeter
    in mA
10 V1      = 70;           //magnitude of
    voltage being measured in V
11 I1      = 80;           //magnitude of
    current being measured in mA
12
13 //calculations
14 dV      = er*V;           //magnitude(dV/V of
    limiting error of the voltmeter in V
15 eV      = (dV/(V1))*100; //percentage(dI/I)
    limitng error at this voltage in %
16 dI      = er*I;           //magnitude of
    limitng error off the ammeter in mA
17 eI      = (dI/(I1))*100; //percentage limitng
    error at this current in %
18 P       = V1*(I1/(1000)); //power in
    W
19 dPx     = eV+eI;         //relative limiting error(
    dPx/Px) in power measurement in %
20
```

```

21 //result
22 mprintf("relative limitng error in power measurement
    = %3.4f percentage",dPx);

```

Scilab code Exa 3.16 calculate the nominal power and limiting error of power

```

1
2 //

```

```

3 //chapter 3 example 16
4
5 clc;clear all;
6
7 //variable declaration
8 E      =200;           //limiting voltage in V
9 R      = 1000;        //resistance in
10 eE     = 1;           //relative limiting error(dE/E)
    in %
11 eR     = 5;           //relative limitng error(dR/R)
    in %
12
13 //calculations
14 P      = (E**2)/(R);   //normal power consumed in
    W
15 eP     = ((2*eE)+eR);  //relative limiting
    error(dP/P) in measurement of power in %
16 dP     = P*(eP/(100)); //limitng
    error of power in watts
17
18 //result
19 mprintf("Normal power consumed = %3.2f W",P);
20 mprintf("\nrelative limitng error in power
    measurement= %3.2f percentage rangng +eP to -eP",
    eP);

```



```
21 mprintf("\nlimitng error of power = %3.2f percentage
    ",dP);
```

Scilab code Exa 3.17 calculate the nominal value of unknown resistance and error i

```
1 //


---


2 //chapter 3 example 17
3 clc;
4 clear all;
5
6 //variable declaration
7 R1      = 500;          //resistance in
8 R2      = 615;          //resistance in
9 R3      = 100;          //resistance in
10 dR1     = 1;           //limiting error(dR1/R1) in %
11 dR2     = 1;           //limiting error(dR1/R1) in %
12 dR3     = 0.5;         //limiting error(dR1/R1) in %
13
14 //calculations
15 R4      = (R1*R2)/(R3); //unknown resistance in
16 dR4     = dR1+dR2+dR3; //relative error of
    unknown resistance in % ranging - to +
17 e      = R4*(dR4/(100)); //limitng error in
18
19 //result
20 mprintf("unknown resistance = %.2f    ",R4);
21 mprintf("\nrelative error of unknown resistance
    ranging - to + = %3.2f percentage ",dR4);
22 mprintf("\nlimitng error = %3.2f    ",e);
```

Scilab code Exa 3.18 calculate the absolute error

```

1 //


---


2 //chapter 3 example 18
3
4 clc;clear all;
5
6 //variable declartaion
7 r = 0.5*10^-3; //in mm
8 p1 = 200; //in Pa
9 p2 = 150; //in Pa
10 Q = 4*10^-7; //in m**3/s
11 l = 1; //length in m
12 dr = 0.01;
13 dp1 = 3;
14 dp2 = 2
15 dQ = 0
16 dl = 0;
17
18 //calculations
19 u = ((%pi)*((r^4)*((p1*10^3)-(p2*10^3)))/((8*Q*l))
); //absolute error inkr/m-s
20 er = (dr/((r/(10^-3))))*100; //
dr/r in %
21 ep1 = (dp1/(p1))*100; //dp1/p1
in %
22 ep2 = (dp2/(p2))*100; //dp2/p2
in %
23 eQ = (dQ/(Q))*100; //dQ/Q in %
24 el = (dl/(l))*100; //dl/l in %
25 p = p1-p2; //dp/p in Pa
26 ep = (((p1/(p))*(ep1))+(p2/(p))*(ep2)); //
percentage error in % anging - to +
27 eu = (4*er)+(ep+eQ+el); //percentage
error in % ranging - to +
28 ua = u*(eu/100); //absolute
error in kg/m-s
29

```

```

30 //result
31
32 mprintf("absolute error = %3.3e kg/m-s",u);
33 mprintf("\nabsolute error = %3.2e kg/m-s",ua);

```

Scilab code Exa 3.19 determine the magnitude of unknown inductance

```

1 //


---


2 //chapter 3 example 19
3
4 clc;clear all;
5
6 //variable declaration
7 C = 1*10^-6; //capacitance in F
8 dC = 1; //error capacitance in %
9 P = 1000; //resistance in
10 dP = 0.4; //error in resistance in %
11 Q = 2000; //resistance in
12 dQ = 1; //error in resistance in %
13 S = 2000; //resistance in
14 dS = 0.5; //error in resistance in %
15 r = 200; //resistance in
16 dr = 0.5; //error in resistance in %
17
18 //calculations
19 Lx = ((C*P)*((r*(Q+S))+(Q*S)))/(S); //
    unknown inductance in Henry
20 u = Q+S; //in
21 du = ((Q/(u))*(dQ))+((S/(u))*(dS)); //
    percentage error in %
22 v = r*(Q+S);
23 dv = dr+du; //percentage error of v in %
24 x = Q*S;

```

```

25 dx      = dQ+dS;           //percentage error of x in %
26 y      = (r*(Q+S))+(Q*S);
27 dy      = ((v/(y))*(dQ))+((x/(y))*(dx));    //
           percentage error in %
28 dLx     = dC+dP+dS+dy;
29
30 //result
31 mprintf("unknown inductance = %3.2f henry",Lx);
32 mprintf("\npercentage error on inductance = %3.1f
           percentage",dLx);

```

Scilab code Exa 3.20 determine the uncertainty in the measurement of Z

```

1 //


---




---


2 //chapter 3 example 20
3
4 clc;clear all;
5
6 //variable declaration
7 R      = 100;           //resistance in
8 dR     = 5;            // error (dR/R) in %
9 L      = 2;            //inductance
10 r     = 50;
11 dL    = 10;           // error (dL/L) in %
12
13 //calculations
14 u     = R**2;
15 du    = 2*dR;         //percentage error(du/u) in %
16 v     = ((2*(%pi)*(r))**2)*(L**2);
17 dv    =2*dL;         //percentage error(dv/v) in %
18 x     = u+v;
19 dx    =((u/(x))*(du))+((v/(x))*(dv));    //
           percentage error(dx/x)in %

```

```

20 Z      = sqrt(x);
21 dZ     = dx/(2);           //uncertainty (dZ/Z) in %
22
23 //result
24 mprintf("uncertainty in the measurement = %3.3 f
percentage",dZ);

```

Scilab code Exa 3.21 calculate the standard deviation

```

1 //


---


2 //chapter 3 example 21
3 clc;clear all;
4
5 //variable declaration
6 x1    = 49.7;           //voltage in V
7 x2    = 50.1;           //voltage in V
8 x3    = 50.2;           //voltage in V
9 x4    = 49.6;           //voltage in V
10 x5   = 49.7;           //voltage in V
11 n     =5;
12
13 //calculations
14 x     =(x1+x2+x3+x4+x5)/(5); //arithmic mean
15 d1    =x-x1;           //deviation
16 d2    =x-x2;           //deviation
17 d3    =x-x3;           //deviation
18 d4    =x-x4;           //deviation
19 d5    =x-x5;           //deviation
20 d     = (d1**2)+(d2**2)+(d3**2)+(d4**2)+(d5**2);
21 sigma = sqrt(d/(n-1)); //standard deviation
22
23 //result
24 mprintf("arithmic mean = %3.2 f ",x);

```

```
25 mprintf(" \nstandard deviation = %3.3f",sigma);
```

Scilab code Exa 3.22 find mean and standard deviation and probable error

```
1 //


---


2 //chapter 3 example 22
3 clc;clear all;
4
5 //variable declaration
6 x1 = 41.7; //voltage in V
7 x2 = 42; //voltage in V
8 x3 = 41.8; //voltage in V
9 x4 = 42; //voltage in V
10 x5 = 42.1; //voltage in V
11 x6 = 41.9; //voltage in V
12 x7 = 42.5; //voltage in V
13 x8 = 42; //voltage in V
14 x9 = 41.9; //voltage in V
15 x10 = 41.8; //voltage in V
16 n =10;
17
18 //ccalculations
19 x =(x1+x2+x3+x4+x5+x6+x7+x8+x9+x10)/(10); //
    arithmetic mean
20 d1 =x-x1; //deviation
21 d2 =x-x2; //deviation
22 d3 =x-x3; //deviation
23 d4 =x-x4; //deviation
24 d5 =x-x5; //deviation
25 d6 =x-x6; //deviation
26 d7 =x-x7; //deviation
27 d8 =x-x8; //deviation
28 d9 =x-x9; //deviation
```

```

29 d10    =x-x10;           //deviation
30 d      = (d1^2)+(d2^2)+(d3^2)+(d4^2)+(d5^2)+(d6^2)+(
      d7^2)+(d8^2)+(d9^2)+(d10^2);
31 sigma  = sqrt(d/(n-1)); //standard deviation
32 r      = 0.6745*sigma;   //probable error of one
      reading
33
34 //result
35 mprintf("arithmetic mean = %3.2f ",x);
36 mprintf("\nstandard deviation = %3.3f",sigma);
37 mprintf("\nprobable error of ne reading = %3.3f",r);

```

Scilab code Exa 3.23 find mean and standard deviation and probable error and proba

```

1 //


---


2 //chapter 3 example 23
3
4 clc;clear all;
5
6 //variable declaration
7 x1    = 41.7;           //voltage in V
8 x2    = 42;             //voltage in V
9 x3    = 41.8;          //voltage in V
10 x4    = 42;            //voltage in V
11 x5    = 42.1;          //voltage in V
12 x6    = 41.9;          //voltage in V
13 x7    = 42.5;          //voltage in V
14 x8    = 42;            //voltage in V
15 x9    = 41.9;          //voltage in V
16 x10   = 41.8;          //voltage in V
17 n     =10;
18
19 //ccalculations

```

```

20 x      =(x1+x2+x3+x4+x5+x6+x7+x8+x9+x10)/(10);      //
    arithmetic mean
21 d1     =x-x1;          //deviation
22 d2     =x-x2;          //deviation
23 d3     =x-x3;          //deviation
24 d4     =x-x4;          //deviation
25 d5     =x-x5;          //deviation
26 d6     =x-x6;          //deviation
27 d7     =x-x7;          //deviation
28 d8     =x-x8;          //deviation
29 d9     =x-x9;          //deviation
30 d10    =x-x10;         //deviation
31 d      = (d1**2)+(d2**2)+(d3**2)+(d4**2)+(d5**2)+(d6
    **2)+(d7**2)+(d8**2)+(d9**2)+(d10**2);
32 sigma  = sqrt(d/(n-1));      //standard deviation
33 r      = 0.6745*sigma;      //probable error of one
    reading
34 rm     = r/(sqrt(n-1));      //probable error of mean
    in V
35 R      = x7-x1;          //range in V
36 //result
37 mprintf(" arithmetic mean = %3.2 f",x);
38 mprintf("\nstandard deviation = %3.3 f",sigma);
39 mprintf("\nprobable error of one reading = %3.3 f",r)
    ;
40 mprintf("\nprobable error of mean = %3.5 f V',rm);
41 mprintf("\nRange = %3.2 f V',R);

```

Scilab code Exa 3.24 determine arithmetic mean and average deviation and variance

```

1 //


---


2 //chapter 3 example 24
3 clc;clear all;

```



```

4
5 //variable declaration
6 x1    = 1.570;      //voltage in V
7 x2    = 1.597;      //voltage in V
8 x3    = 1.591;      //voltage in V
9 x4    =1.562;      //voltage in V
10 x5   =1.577;      //voltage in V
11 x6    = 1.580;      //voltage in V
12 x7    = 1.564;      //voltage in V
13 x8    = 1.586;      //voltage in V
14 x9    = 1.550;      //voltage in V
15 x10   = 1.575;      //voltage in V
16 n     =10;
17
18 //ccalculations
19 x      =(x1+x2+x3+x4+x5+x6+x7+x8+x9+x10)/(10);    //
    arithmetic mean
20 d1     =x1-x;      //deviation
21 d2     =x2-x;      //deviation
22 d3     =x3-x;      //deviation
23 d4     =x4-x;      //deviation
24 d5     =x5-x;      //deviation
25 d6     =x6-x;      //deviation
26 d7     =x7-x;      //deviation
27 d8     =x8-x;      //deviation
28 d9     =x9-x;      //deviation
29 d10    =x10-x;     //deviation
30 D      =(abs(d1)+abs(d2)+abs(d3)+abs(d4)+abs(d5)+abs(
    d6)+abs(d7)+abs(d8)+abs(d9)+abs(d10))/(n);
31 d      = ((d1^2)+(d2^2)+(d3^2)+(d4^2)+(d5^2)+(d6^2)+(
    d7^2)+(d8^2)+(d9^2)+(d10^2));
32 sigma  = sqrt(d/(n-1));      //standard deviation
33 r      = 0.6745*sigma;      //probable error of one
    reading
34 v      = sigma^2;
35 rm     = r/(sqrt(n-1));      //probable error of mean
    in V
36

```

```
37 //result
38 mprintf(" arthimetic mean = %3.3f",x);
39 mprintf("\naverage deviation = %3.3f gramme",D);
40 mprintf("\nstandard deviation = %3.5f gramme*2",
    sigma);
41 mprintf("\nprobable error of one reading = %3.5f
    gramme",r);
42 mprintf("\n variance= %3.3e gramme^2",v);
43 mprintf("\nprobable error of mean = %3.4f gramme",rm
    );
```

Chapter 4

Measuring system fundamentals

Scilab code Exa 4.1 find the torque

```
1 //


---


2 //chapter 4 example 1
3 clc;
4 clear all;
5
6
7 //variable decalartion
8 L = 0.4; //length of the strip in m
9 W = 0.0005; //width of the strip in m
10 t = 0.00008 //thickness in m
11 E = 1.2*10^10; //young's modulus in kg/m**2
12 d = 90; //deflection in
    degrees
13
14 //calucaltions
15 theta = %pi/(2); //deflection in radians
16 T = ((E*W*(t^3))/(12*L*2))*(%pi); //
```

```

    torque exerted in Kg-m
17
18 //result
19
20 mprintf("torque exerted T = %3.2e Kg-m",T);

```

Scilab code Exa 4.2 determine deflection

```

1 //


---


2 //chapter 4 example 2
3 clc;
4 clear all;
5
6
7 //variable decalartion
8 W      = 0.005;           //controlling weight
   in Kg
9 L      = 0.024;         //length in m
10 Td     = 1.05*10**-4;   //deflecting Torque in
   kg-m
11
12 //calculations
13 x      = Td/(W*L);
14 //Td = W*L*sin(theta)
15 theta  = asin(x);
16 theta1 = (theta*180)/(%pi);
17
18 //result
19 mprintf("deflection = %3.0f    ",theta1);

```

Scilab code Exa 4.3 determine the suitable dimensions for spring

```

1 //


---


2 //chapter 4 example 3
3
4 clc;
5 clear all;
6
7
8 //variable decalartion
9 Smax    = 3.0*10^6;           //maximum stress in kg/m**2
10 E      = 1.2*10^10;         //young's modulus
    in kg/m**2
11 w      = 0.0006;           //width of spring in m
12 Td     = 1.2*10^-4;         //deflecting torque in
    kg-m
13 d      = 90;                //deflection in
    degrees
14
15 //calucaltions
16 theta = %pi/(2);           //deflection in radians
17 //since T      = ((E*W*(t*3))/(12*L))*theta
18 //t^3/l      = (12*Tc)/(E*W*theta)
19 Tc     = Td/(2);           //controlling
    torque of each spring in kg-m
20 //x = t**3/l
21 x      = (12*Tc)/((E*w*theta)); //
    equqation 1
22 //y = l/t
23 y      = (E*theta)/(2*Smax); //equation 2
24 //by multiplying equations 1 and 2 (x*y =t**2 =z)
25 z      = x*y;
26 t      = sqrt(z);          //thickness of spring
    strip in mm
27 l      = y*t;              //length on m
28
29 //result
30 mprintf("thickness of spring strip = %3.2f mm", (t

```

```

    *10^3));
31 mprintf(" \nlength in = %3.2 f m",l);

```

Scilab code Exa 4.4 determine the deflection

```

1 //


---


2 //chapter 4 example 4
3 clc;
4 clear all;
5
6 //variable declaration
7 theta1 = 90; //deflection in
8 x = 0.5; //I2/I1
9
10 //calculations
11 //Td proprtional to I
12 //theta proprtional to I
13 theta2 = theta1*(x); //deflection for the
    current equal to the half of the current in
    spring controlled instrument in
14 //Tc proprtional to sin(theta)
15 //sin(theta) proprtional to I
16 y = sin((%pi/(2)))
17 theta21 = asin(x*y); //deflection for the
    current equal to the half of the current in
    gravity controlled instrument in
18 theta22 = (theta21*180)/(%pi);
19
20 //result
21 mprintf("deflection for the current equal to the
    half of the current in spring controlled
    instrument = %3.2 f ",theta2);
22 mprintf(" \ndeflection for the current equal to the

```

```
half of the current in gravity controlled
instrument = %3.2f    ",theta22);
```

Scilab code Exa 4.5 find the deflection when spring controlled and gravity control

```
1 //


---


2 //chapter 4 example 5
3 clc;
4 clear all;
5
6
7 //variable decelaration
8 theta1 = 90; //deflection in
9 I1 = 10;
10 I2 =5;
11
12 //calculations
13 //Td proprtional to I^2
14 //Theta proprtional to I^2
15 theta2 = theta1*((I2/(I1))^2); //
    deflection for I1 A spring controlled instrument
    in
16 //Tc proprtional to sin(theta)
17 //sin(theta) proprtional to I**2
18
19 x = (I2/((I1)))
20 theta21 = asin(x**2)*(sin(%pi/(2))); //
    deflection for I1 A Gravity controlled
    instrument in
21 theta22 = (theta21*180)/(%pi);
22
23 //result
24 mprintf(" deflection for I1 A spring controlled
```

```

    instrument = %3.2f    ",theta2);
25 mprintf(" \ndeflection for I1 A Gravity controlled
    instrument = %3.1f    ",theta22);

```

Scilab code Exa 4.6 determine the value of current when spring controlled and grav

```

1 //


---


2 //chapter 4 example 6
3
4 clc;
5 clear all;
6
7 //Variable declaration
8 I1      = 10;           //current in A
9 theta1  = 60;           //deflection in
10 theta2  = 40;          //deflection in
11
12
13 //calculations
14 I2      = (I1)*(theta2/(theta1));           //current in
    case spring controlled ammeter in A
15 x      = sin((theta2*%pi)/(180));
16 y      = sin((theta1*%pi)/(180));
17 I21    = (I1)*(x/y);           //current in case
    gravity controlled ammeter in A
18
19
20 //result
21 mprintf(" current in case spring controlled ammeter =
    %3.2f A",I2);
22 mprintf(" \ncurrent in case gravity controlled
    ammeter = %3.2f A",I21);

```

Scilab code Exa 4.7 find the deflecting torque

```
1 //


---


2 //chapter 4 example 7
3
4 clc;
5 clear all;
6
7
8 //variable declaration
9 Td      = 1.13*10^-3;           //deflecting torque in
   Nm
10 m      = 5*10^-3;
                                     //
   weight in kg
11 g      = 9.81;                 //gravity
12 theta  = 60;                   //deflection in
13
14 //calculations
15 d      = Td/(m*g*sin(((theta*%pi)/(180)))); //
   distance of the controlling weight from spindle
   in mm
16
17 //result
18 mprintf("distance of the controlling weight from
   spindle = %3.1f mm", (d*10^3));
```

Chapter 5

Analog ammeters and voltmeters

Scilab code Exa 5.1 calculate the deflection

```
1 //  


---

  
2 //chapter 5 example 1  
3  
4 clc;clear all;  
5  
6 //variable declaration  
7 K      = 24*10^-6;      //spring constant in Nm/  
      radian  
8 I      = 5;           //current in A  
9  
10 //calculations  
11 //L      = 20+10*theta - 2*(theta^2)  
12 //partial differentiate w.r.t to theta  
13 //dL/dtheta = x = 10- 4*theta  
14 //dL/dtheta = 2*K*theta/(I^2)  
15 //x          = 10-4*theta  
16 //y          = theta/x
```

```

17 y      = ((I^2)/(2*K))*10^-6;
18 theta  = (10*y)/(1+(4*y));      //defelction for
    current in radians
19 theta1  = ((theta*180)/(%pi));
20
21 //result
22
23 mprintf(" deflection = %3.1f      ', theta1);

```

Scilab code Exa 5.2 Determine the spring constant

```

1 //


---


2 //chapter 5 example 2
3
4 clc;clear all;
5
6 //Variable declaration
7 I      = 5;          //current in A
8 d      = 30;        //
    deflection
9 I2     = 10;
10
11 //calculations
12 //L     = 10+5*theta - 2*(theta^2)      //
    inductancein uH
13 //partial differentiate w.r.t to theta
14 //dL/dtheta = x = 5- 4*theta
15 //dL/dtheta = 2*K*theta/(I^2)
16 //x       = 10-4*theta
17 theta    = %pi/(6);
18 K        = (((5-(4*theta))*10^-6)*(I^2))/(2*theta)
    //spring constant in Nm/radian
19 x        = ((2*K)/(I2^2))*10^6;

```

```

20 theta2    = (5)/(x+4);
21
22 //result
23
24 mprintf("spring constant = %3.4e Nm/radian",K);
25 mprintf("\ndeflection for 10 A current = %3.3f
    radian",theta2);

```

Scilab code Exa 5.3 find the reading of the voltmeter

```

1 //


---


2 //chapter 5 example 3
3 clc;
4 clear all;
5
6 //variable declaration
7 R    = 500;      //resistance in
8 r    = 2000;    //non inductive resistance
    in
9 V    = 250;     //voltage in V
10 f    = 50;     //frequency in Hz
11 L    = 1;      //inductance in H
12
13
14 //calculations
15 x    = (r+R)^2;
16 W    = (2*%pi*f*L)^2;
17 Z    =sqrt(x+W); //impedance of the
    instrument circuit
18 I    = V/(Z);  //current drawn by
    instrument in A
19 I2   = V/(R+r); //since voltmeter reads
    correctly on dc supply on 250 V,corresponding

```

```

    current in A
20 V1 = V*(I/(I2)); //voltmeter reading
    when connected to 250V ,50Hz supply
21
22 //result
23 mprintf("voltmeter reading = %3.1d V",V1);

```

Scilab code Exa 5.4 find the effect of the inductance of the meter

```

1 //


---


2 //chapter 5 example 4
3 clc;clear all;
4
5 //variable declaration
6 Vac = 500; //voltage in V
7 Iac = 0.1; //current in A
8 f = 50; //frequency in Hz
9 L = 0.8; //inductance in H
10 Vdc = 300; //voltage in V
11 Z =5000;
12
13 //calculations
14 W = 2*(%pi)*f*L;
15 R = (sqrt((Z^2)-(W^2))); //resistance in
16 Idc = Vdc/(R); //instrument current in
    A
17 V = (Vac/(Iac))*(Idc); //Reading of
    instrument when connected to 300V in V
18
19 //result
20 mprintf("Reading of instrument when connected to 300
    V = %3.1f V",V);

```

Scilab code Exa 5.5 find the percentage error

```
1 //


---



---


2 //chapter 5 example 5
3 clc;clear all;
4
5 //variable decalaration
6 Iac = 0.1; //current in A
7 f = 50; //frequency in Hz
8 L = 0.8; //inductance in H
9 Vac = 300; //voltage in V
10 V = 200; //true value in V
11
12 //calculations
13 XL = 2*%pi*f*L; //instrument reactance in
14 Z = Vac/(Iac); //instrument impedance in
15 R1 = sqrt((Z^2)-(XL^2)); //instrument resistance (
R+r) in
16 Idc = V/(R1); //instrument current when
connected to 200V dc supply
17 V1 = (Idc*Vac)/(Iac); //reading of the
instrument when connected to 200V dc supply
18 e = ((V1-V)/(V))*100;
19
20 //result
21 mprintf("percentage error = %3.2f percentage",e);
```

Scilab code Exa 5.6 Find the value of capacitance

1

```

2 //


---


3 //Chapter 5 example 6
4
5 clc;clear all;
6
7 //variable declaration
8 R      = 50;           //resistance of the magnetic
   coil in
9 Rt     = 500;        //resistance in
10 L      = 0.09;       //inductance of the
   voltmeter in H
11 f      = 50;
12 I      = 1;
13
14
15 //calculations
16 r      = Rt-R;       //swamping resistance in
17 X      = (2*%pi*f*r)^2;
18 Y      = L*X;
19 Y1     = I*L;
20 //L      = C*r^2/(I+w^2*C^2*r^2)
21 //C*r^2  = L*I+L*w^2*C^2*r^2
22 //C*r^2  =y1+x*(C^2)
23 //x*(C^2)-C*r^2+y1;
24 a      = X;
25 b      = -r^2;
26 c      = Y1;
27 x      = (-b-sqrt((b^2)-(4*a*c)))/(2*a);
   //we consider the positive value
28
29
30
31 //result
32 mprintf("swamping resistance = %3.2e",x);

```

Scilab code Exa 5.7 find the capacitance

```
1 //


---



---


2 //chapter 5 example 7
3 clc;clear all;
4
5 //variable declaration
6 R      = 50;           //resistance of the magnetic
   coil in
7 Rt     = 500;        //resistance in
8 L      = 0.09;       //inductance of the
   voltmeter in H
9
10 //calculations
11 r      =Rt-R;
12 C      = (L/(r^2));  //capacitance to be
   placed in u F
13
14 //result
15 mprintf("capacitance to be placed to make the
   instrument read correctly bot dc as well as ac =
   %3.3 fe uF", (C*10^6));
```

Scilab code Exa 5.8 estimate the rate of change of self deflection

```
1 //


---



---


2 //chapter 5 example 8
3 clc;clear all;
```



```

4
5 //variable decalaration
6 Td      = 4*10^-5;          //full-scale defelcting
      torque in N-m
7 I        = 10;              //full-scale current in
      A
8
9 //calculations
10 //Td      = (1/2)*(I^2)*(dL/dtheta);
11 //dL/dtheta = x
12 x        = (2*Td)/(I^2);
13
14 //result
15 mprintf('rate of change of selfinductance = %3.1f uH
      /rad"',(x*10^6));

```

Scilab code Exa 5.9 determine the current passing in a moving iron instrument

```

1 //


---


2 //chapter 5 example 9
3 clc;clear all;
4
5 //variable declaration
6 //dL/dtheta = x
7 y        = 2.3*10^-6;
8 Td1      = 5*10**-7;
9 t        = 52;
10
11 //calculations
12 x        = y*(180/%pi);
13 Td       = Td1*t;
14 //Td     = (1/2)*(I**2)*(dL/dtheta);
15 I        = sqrt((Td*2)/(x)); //current in A

```

```

16
17 //result
18 mprintf("current = %3.2f A",I);

```

Scilab code Exa 5.10 calculate the percentage increase of resistance

```

1 //


---


2 //chapter 5 example 10
3
4 clc;clear all;
5
6 //variable declaration
7 R      = 400;          //resistance in
8 V      = 150;        //voltmeter reading in V
9 I      = 0.05;       //current in A
10 alphac = 0.004;     //temperature coefficient of
    copper
11 alphas = 0.00001;   //temperature coefficient of
    eureka
12 f      = 100;       //frequency in Hz
13 L      = 0.75;     //inductance in H
14
15
16 //calculations
17 //R1    = R+r;
18 R1     = V/(I);     //total reistance in
19 r      = R1-R;      //swamping resistancein
20 R11    = (R*(1+alphac))+ (r*(1+alphas)); //total
    resistance for 1 C rise in temperature in
21 e      = ((R11-R1)/(R1))*100; //percentage
    rise in resistance per degree rise in
    temperature
22 W      = 2*pi*f*L; //inductive

```

```

    reactance in
23 Z      = sqrt((R1^2)+(W^2));           //impedance in
24 v      = V*(R1/(Z));                 //reading indicated on
    100 Hz in V
25
26
27 //result
28 mprintf("R1 =%3.0f",W);
29 mprintf("percentage rise in resistance per degree
    rise in temperature = %3.4f percentage",e);
30 mprintf("\nreading indicated on 100 Hz= %3.1f V",v);

```

Scilab code Exa 5.11 find the deflection

```

1 //


---


2 //chapter 5 example 11
3 clc;clear all;
4
5 //variable declaration
6 V      = 300;           //voltage in V
7 R      = 12000;        //coil resistance in
8 B      = 6*10^-2;      //flux density in Wb/m**2
9 l      = 0.04;         //length in m
10 r     = 0.03;         //width in m
11 N     = 100;
12 Tc    = 25*10^-7;     //torque in Nm per degree
13
14 //calculations
15 i     = V/(R);        //current in A
16 Td    = N*B*i*l*r;    //deflecting Torque in Nm
17 //Tc=Td;
18 //Tc =(25*10^-7)*theta

```

```

19 theta = Td/(Tc);           //defelction in
20
21 //result
22 mprintf('defelction = %3.0f    ",theta);

```

Scilab code Exa 5.12 determine the control constant of spring

```

1 //


---


2 //chapter 5 example 12
3 clc;clear all;
4
5 //variable declaration
6 V      = 0.1;           //voltage in V
7 R      = 200;          //coil resistance in
8 B      = 0.2;          //flux density in Wb/m^2
9 l      = 0.03;         //length in m
10 r     = 0.025;        //width in m
11 N     = 100;
12 Tc    = 25*10^-7;     //torque in Nm per degree
13 theta = 100;         //deflection in
14 p     = 1.7*10^-8;    //specific resistance of
    coil in    -m
15 d     = 30;
16 d1    = 25;
17
18
19 //calculations
20 i     = V/(R);        //current in A
21 Td    = N*B*i*l*r;    //deflecting Torque
    in Nm
22 K     = Td/(theta);   //control constant
    of spring in N-m
23 l     = (d+d1)*2*100*10^-3; //length of copper

```

```

    coil in m
24 R1      = (R*20)/(100);
25 a      = (p*1)/(R1);           //area of x-section of
    copper wire inm^2
26 D      = sqrt((4*a)/(%pi));   //diameter of
    wire in mm
27
28 //result
29
30 mprintf(" diameter fo wire = %3.3 f mm", (D*10^3));

```

Scilab code Exa 5.13 calculate the value of current in the wire

```

1 //


---


2 //chapter 5 example 13
3
4 clc;clear all;
5
6 //variable declaration
7 V1  = 50*10^-3;           //voltage in V
8 I1  = 5;                  //current in A
9 I2  = 10;                 //current in A
10 v1  =4;
11 v2  =4.2;
12
13 //calculations
14 //v1    = (r+R1)*I1
15 //v1    = (r+R1)*I2
16 //since potential difference is same in both cases
17 //v1= v2
18 R1    = V1/(I1);
19 R2    = V1/(I2);
20 r      = ((v2*R2)-(v1*R1))/(v1-v2);

```

```

21 v      = (r+R1)*v1;          //potential difference
    in V
22 I      = v/(r);            //current when neither
    meter in the circuit in A
23
24 //result
25 mprintf("current when neither meter in the circuit =
    %3.2f A",I);

```

Scilab code Exa 5.14 Finding the minimum resistance

```

1 //


---


2 //chapter 5 example 14
3 clc;clear all;
4
5 //variable declaration
6 V      = 250;              //voltage in V
7 RA     = 100;              //resistance in
8 RB     = 400;              //resistance in
9 x      = 0.005;            //error in measuring voltage
    in
10
11
12 //calculations
13 I      = V/(RA+RB);        //current flowing through
    resistance in A
14 VB     = I*RB;             //potential drop across
    resistance in V
15 //Req  = RA+((r*RB)/(r+RB))
16 //Ieq  =V/Req = V/ RA+((r*RB)/(r+RB))
17 //Ieq  = (V*(r+RB))/((RA*(r+RB))+r*RB)
18 //V1   = Ieq*(r*RB)/(r+RB)
19 // V1  = (V*(r+RB))*(r*RB)/((r+RB)*((RA*(r+RB))+r*

```

```

    RB)))
20 //V1    = (V*r*RB)/((r+RB)*((RA*(r+RB))+(r*RB)))
21 //V1    = (200*r)/(80+r)
22 V1     = VB*(1-x);      //voltage measured with 0.5%
    error
23 r      = (V1*80)/(200-V1);      //solving equations
    we get minimum resistance in
24
25 //result
26 mprintf("minimum resistance = %3.2f    ",r);

```

Scilab code Exa 5.15 Find the total inductance

```

1 //


---


2 //chapter 5 example 15
3 clc;clear all;
4
5 //variable decalartaion
6 C      = 1*10**-7;      //spring torsion
    constant in N-m/degree
7 I      = 10;           //current in A
8 theta  = 110;          //full-deflection in
9 L1     = 2*10**-6;     //initial inductance in
    uH
10
11 //calculations
12 Td     =C*theta;       //full-scale
    deflceting torque in N-m
13 //dM/dtheta =x
14 x      = Td/(I^2);
15 theta1 = ((theta*%pi)/(180)); //converstion of
    radians to degrees
16 dM     = x*theta1;    //change in inductance

```

```

    in uH
17 M      = L1+dM;          //total inductance in uH
18
19 //result
20
21 mprintf("total inductance = %3.3f uH", (M*10^6));

```

Scilab code Exa 5.16 Find the difference in the readings

```

1 //


---


2 //chapter 5 example 16
3
4 clc;clear all;
5
6 //variable declaration
7 theta    = 90;          //full-deflection in
8 Td       = 0.4*10^-4;   //full-scale
    deflecting torque in Nm
9 I        = 0.05;       //current in A
10 M       = 0.25;       //initial inductance in
    H
11 V       = 50;         //voltage in V
12 I       = 0.05;       //current in A
13 f       = 50;         //frequency in Hz
14 V2      = 25;
15 R       = 1000;
16
17
18 //calculations
19 //dM/dtheta = x
20 x       = (Td/(I^2));   //change in inductance in
    H
21 dM      = (Td/(I^2))*((theta*%pi)/(180));

```



```

//change in inductance in H
22 M1      = M+dM;           //total mutual inductance in
    H
23 R        = V/(I);         //the resistance of
    voltmeter in
24 Z        =sqrt((R**2)+((2*%pi*f*M1)**2));      //
    toatal impedance in
25 V1       = (V/(Z))*R;     //voltmeter reading in V
26 d        = V-V1;         //difference in reading in
    V
27 I1       = V2/(R);        //current through
    instrument in A
28 theta1   = ((theta*%pi)/(180))*((I1/(I))^2);
    //defelction
29 M2       = M+(x*theta1);  //total mutual
    inductance in H
30 Z1       = sqrt((R**2)+((2*%pi*f*M2)**2));     //
    toatal impedance in
31 V21      = (V2*R)/(Z1);   //voltmeter reading
    in V
32 d1       = V2-V21;        //difference in
    voltmeter reading in V
33
34 //result
35 mprintf("impedancewhile measuring the voltage = %3.3
    f ",Z1);
36 mprintf("\ndifference in reading = %3.1 f V",d);
37 mprintf("\ndifference in reading when 25v is used =
    %3.2 f V",d1);

```

Scilab code Exa 5.17 Determine the range of the instrument and current and deflect

```
1 //
```

```

2 //chapter 5 example 17
3 clc;
4 clear all;
5
6 //variable declaration
7 theta1 = 90;           //defelction in
8 theta2 = 360;         //defelction in
9 theta3 = 180;         //defelction in
10 I1      = 30;         //current in A
11 I4      = 25;         //current in A
12
13 //T is proportional to I**2
14 //T is proportional to theta
15 //theta is proportional to math.sqrt (I)
16 //calculations
17 I2 = I1*sqrt((theta2/(theta1)));           //current
    corresponding to deflection of 360
18 I3 = I1*sqrt((theta3/(theta1)));           //current
    corresponding to deflection of 180
19 theta4 = theta1*((I4/I1)^2);           //defelction
    corresponding tocurrent of 25 A
20
21 //result
22 mprintf("current corresponding to deflection of 360
    = %3.2f A",I2);
23 mprintf("ncurrent corresponding to deflection of
    180 = %3.2f A",I3);
24 mprintf("ndefelction corresponding tocurrent of
    25 A = %3.2f ",theta4);

```

Scilab code Exa 5.18 Calculate the reading of an electro dynamometer

```
1 //
```

```

2 //Chapter 5 example 18
3
4 clc;
5 clear all;
6
7 //variable declaration
8 p      = 80;
9 q      = 60
10
11 //i      = 80-60*sqrt(2)*sin(theta+%pi/6)
12 //i^2    = x = (80)^2 - ((2*80*60*sqrt* sin(theta+(
      %pi/6))0^2) + ((80^2)*(sin(theta+(%pi/6))^2))
13 //x      = a-b*(sin(theta+(%pi/6))^2)+(c)*(sin(theta+(
      %pi/6))^2)
14 //x      = (80)^2 - ((2*80*60*sqrt* sin(theta+(%pi/6))0^2)
      + (((80^2)/2)*(1-(cos(theta+(%pi/6))^2)))
15 //x      = a-(b*sin(theta+(%pi/6)))+(c/2)-cos(theta
      +((pi/6)^2))
16 a      = p^2;
17 b      = (2*(q^2)*(sqrt(2)));
18 c      = (q*sqrt(2))^2;
19 //x      = (1/2*%pi)*{(integral(x*dtheta))}(0-2*%pi)
20 //applying integration
21 y      = (a+(c/2));
22 x      = (1/%pi)*y*(%pi);          //Irms^2
23 Irms   = sqrt(x);          //reading in A
24
25
26 //result
27 mprintf("electrodynamometer instrument indicates
      the rms value of the current therefore the
      dreading will be equla ")
28 mprintf(" Irms = %3.2 f A", Irms);

```

Scilab code Exa 5.19 Find the magnification

```

1 //


---


2 //chapter 5 example 19
3 clc;
4 clear all;
5
6 //variable declaration
7 L      = 150;          //length of working wire at
                        room temperature in mm
8 alpha  = 16*10^-6;    //coefficient of linear
                        expansion
9 T      = 85;          //temperature in      C
10 Si     =1;           //initial sag in mm
11 //calculations
12 dL     = alpha*L*T;   //increase in length of the
                        wire when gets heated through 85
                        C in mm
13 M      = sqrt(L/(2*dL)); //magnification with no
                        intial sag
14 S      = sqrt((L*dL)/(2)); //Sag in mm
15 Sn     = S-Si;       //net increase in Sag in mm
16 M1     = Sn/(dL);    //magnification with initial
                        Sag of 1 mm
17
18 //result
19 mprintf("magnification with no intial sag = %3.2f",
          M);
20 mprintf("\nSag = %3.2f mm",S);
21 mprintf("\nnet increase in Sag =%3.2f mm",Sn);
22 mprintf("\nmagnification with initial Sag of 1 mm =
          %3.2f",M1);

```

Scilab code Exa 5.20 Determine the magnification

```

1 //

```

```

2 //chapter 5 example 20
3 clc;
4 clear all;
5
6 //variable declaration
7 L = 170; //length of the wire in mm
8 dL = 0.2; //increase in length in mm
9 L1 = 100; //length of the second wire in mm
10
11 //calculations
12 S = sqrt((L*dL)/(2)); //Sag in mm
13 S1 = sqrt((L1*S)/(2)); //Sag in mm
14 M = S1/(dL); //magnification
15
16 //result
17 mprintf("magnification = %3.1f",M);

```

Scilab code Exa 5.21 Determine the current

```

1 //

```

```

2 //Chapter 5 example 21
3
4 clc;
5 clear all;
6
7 //variable declaration
8 I = 10; //current in A
9 //e = (alpha*(dt))+(b(dt^2))= alpha*dt
10 //dt = (K1*(I^2)*R)
11 //theta = K2*e
12 //theta = K2*e = K2*K1*alpha*dt = K2*K1*alpha

```

```

        *(I^2)*R
13 //thetaF      = K3*(I^2)
14 //K3          = (thetaF)/(I^2);
15 x            = 1/(I^2);
16 mprintf("K3      = %3.2 f *thetaf",x);
17 //K3          =thetaF*x
18 mprintf("\ntheta      = theatF/3");
19 //I           = sqrt((thetaF/3)*((K3)))
20 //I           = sqrt((thetaF/3)/K3)
21 I            =sqrt((1/3)*((1/x)))
22
23
24 //result
25 mprintf("\ncurrent = %3.2 f A",I);

```

Scilab code Exa 5.22 Determine the form factor of the current wire

```

1 //


---


2 //chapter 5 example 22
3
4 clc;
5 clear all;
6
7 //variable declaration
8 Irms      = 32;           //measured reading
   reading in A
9 Ir        = 30;           //rectifier ammeter
   reading in A
10 Ks       = 1.11;        //form factor for sinusoidal
   wave
11
12 //calculations
13 Iav      = Ir/(Ks);      //average value of current

```

```

    under measurement in A
14 e      = ((Irms)/(Iav));          //percentage
    error in %
15
16 //result
17
18 mprintf("form factor = %3.3 f ",e);

```

Scilab code Exa 5.23 Estimate the peak and rms values of current and calculate the

```

1 //


---


2 //chapter 5 example 23
3 clc;
4 clear all;
5
6 //variable declaration
7 Ir      = 2.22;          //measured reading
    reading in A
8 Ks      = 1.11;        //form factor for sinusoidal
    wave
9
10 //calculations
11 Iav     = Ir/(Ks);     //average value of current
    under measurement in A
12 Imax    = 2*Iav;      //peak value of current in A
13 Irms    = Imax/(sqrt(3)); //RMS value of
    current in
14 e      = ((Ir-Irms)/(Irms))*100; //
    percentage error in %
15
16 //result
17 mprintf("peak value of current = %3.2 f A",Imax);
18 mprintf("\nRMS value of current = %3.3 f A",Irms);

```

```
19 mprintf("\npercentage error = %3.2f percentage(low)"
    ,e);
```

Scilab code Exa 5.24 Determine the capacitance

```
1 //


---


2 //chapter 5 example 24
3
4 clc;clear all;
5
6 //variable declaration
7 Iav    = 40*10^-3;    //average value of current
    in mA
8 Ks     = 1.11;    //assuming form factor for
    sinusoidal wave
9 f      = 50;    //frequency in Hz
10 V     = 10^5; //voltage in V
11
12 //calculations
13 Irms   = Iav*Ks;    //RMS value of current in A
14 //Irms = V/Xc = 2*pi*f*C*V
15 C      = Irms/(2*pi*f*V);    //capacitance to
    be connected in pF
16
17 //result
18
19 mprintf("capacitance to be connected = %3.0f pF", (C
    *10^12));
```

Scilab code Exa 5.25 determine the reading of moving coil ammeter and moving iron


```

1 //


---


2 //chapter 5 example 25
3
4 clc;clear all;
5
6 //variable declaration
7 Emax      = 200;      //emf of peak value in V
8 R          = 10;      //resistance in
9
10 //calculations
11 Imax      = Emax/(R);      //peak value of current
    in A
12 Iav       = (2*Imax)/(%pi); //reading of moving
    -coil ammeter in A
13 Irms      = Imax/(sqrt(2)); //reading of moving
    -iron ammeter in A
14
15 //result
16 mprintf("reading of moving -coil ammeter = %3.2 f A",
    Iav);
17 mprintf("\nreading of moving -iron ammeter = %3.2 f
    A", Irms);
18 mprintf("\nreading of hot-wire ammeter = %3.2 f A",
    Irms);

```

Scilab code Exa 5.26 find the reading on hot wire and moving coil in the circuit

```

1 //


---


2 //Chapter 5 example 26
3
4 clc;

```

```

5 clear all;
6
7 //variable declaration
8 Vmax      = 100;           //maximum value of
    applied voltage in V
9 R         = 2;           //resistance in
10
11
12 //calculations
13 Imax      = Vmax/R;       //maximum value of
    current flowing through instruments in A
14 mprintf("x = (Imax^2)*((sin(theta))^2)");
15 //Irms    = sqrt((1/2*%pi)*{(integral(x*dtheta))
    }(0-%pi))
16 Irms      = sqrt(((Imax^2)/(2*%pi))*((%pi/2)));
17 mprintf("\n y = (Imax*sin(theta))");
18 //Iav     = sqrt((1/2*%pi)*{(integral(y*dtheta))
    }(0-%pi))
19 Iav       = Imax/%pi;
20
21
22 //result
23 mprintf("\nthe hot-wire ammeter reads rms value = %3
    .2 f A", Irms);
24 mprintf("\nmoving coil ammeter reads average value =
    %3.2 f A", Iav);

```

Scilab code Exa 5.27 Determine the reading of the ammeter

```

1 //


---


2 //Chapter 5 example 27
3
4 clc;

```

```

5 clear all;
6
7
8 //variable declaration
9 //V = (5*sin(theta))+(0.6*sin(3*theta))\
10
11 a = 5;
12 b = 0.6;
13 rd = 35; //resistance in
14 ra = 30; //resistance in
15
16 //calculations
17 R = (3*rd)+ra; //resistance in
18 //i = v/R
19 //i = (5*sin(theta)/R)+(0.6*(sin(3*theta)/R)
20 )
21 x1 = a/R;
22 y1 = b/R;
23 //i = (x1*sin(theta))+(y1*sin(3*theta))
24 //Iav = ((1/%pi)*{(integral(i*dtheta))}(0-%pi)
25 ))
26 //Iav = (1/%pi)*((0.5*sin(theta))-(0.006/3)*
27 cos(3*theta))
28 //solving above equation we get (1/%pi)*(1)
29 p = (-0.05*((cos((180*%pi/180))-cos(0))))
30 -((0.002*((cos(3*180*%pi/180))-cos(3*0))));
31 z = (1/%pi)*p; //average value in
32 mA
33
34
35 //result
36 mprintf("average value reading of PMMC ammeter = %3
37 .1 f mA", (z*10^3));

```

Scilab code Exa 5.28 Calculate the power dissipated in the rectifying device

```

1 //


---




---


2 //Chapter 5 example 28
3
4 clc;
5 clear all;
6
7
8 //variable declaration
9 V          = 230;           //RMS value of voltage
   applied in volts
10 r1         = 115;         //resistance in
11 r2         = 115;         //resistance in
12 r3         = 575;         //resistance in
13
14
15
16 //calculations
17 Vmax       =230*sqrt(2);
18 R1         =r1+r2;        //resiatance in one
   directions in
19 R2         =r2+r3;        //resiatance in other
   directions in
20 Imax1      = Vmax/R1;     //current (maximum
   value) in one direction in A
21 Imax2      = Vmax/R2;     //current (maximum
   value) in other direction in A
22 //Iav      = Iav1-Iav2
23 //x        = (Imax1*sin(theta))
24 //Iav      = ((1/2*%pi)*{(integral(x*dtheta))}(0-
   %pi))
25 //y        = (Imax2*sin(theta))
26 //Iav      = ((1/2*%pi)*{(integral(y*dtheta))}(0-
   %pi))
27 z1         = -((cos(180*%pi/180))-cos(0))
28 z2         = -((cos(180*%pi/180))-cos(0))
29 A          = ((Imax1*z1)-(Imax2*z2));

```

```

30 Iav      = A/(2*%pi);
31 //x1      = (Imax1*sin(theta))^2
32 //I1      = ((1/2*%pi)*{(integral(x1*dtheta))}(0-
    %pi))
33 //y1      = (Imax2*sin(theta))^2
34 //I2      = ((1/2*%pi)*{(integral((1-cos(2*theta))
    /2*dtheta))}(0-%pi)) - {(integral((1-cos(2*theta))
    /2*dtheta))}(0-%pi))
35 //Irms= I1+I2
36 //Irms    = ((1/2*%pi)*{(integral(y1*dtheta))}(0-%pi))
    )
37 Z1        = -((cos(2*180*%pi/180))-cos(180*%pi/180)
    );
38 Z2        = -((cos(2*180*%pi/180))-cos(180*%pi
    /180));
39 Irms1     = (((Imax1^2)/(2*2*%pi))*(%pi-0))+(((
    Imax2^2)/(2*2*%pi))*(%pi-0))-Z1+Z2
40 Irms      =sqrt(Irms1);
41 P         = (1/2)*(((V^2)/R1)+((V^2)/R2));
42 Irms11    = 1;
43 Irms22    = 1/3;
44 Pd        = (((Irms11^2)*r2)+((Irms22^2)*r3))/2;
45
46
47 //result
48 mprintf("Iav = %3.2f A",Irms1);
49 mprintf("\npower taken from the mains = %3.2f",P);
50 mprintf("\npower dissipated in rectifying device =%3
    .2f W",Pd);

```

Scilab code Exa 5.29 Determine the value of v

```
1 //
```

```

2 //Chapter 5 example 29
3
4 clc;
5 clear all;
6
7
8 //variable declaration
9 V1      = 1000;           //potential of vane in volts
10
11 //calculations
12 //v      = VA-VB
13 mprintf("theta 10 S D");
14 mprintf("\ntheta praportional to Tt praportional to
15          2*V1*V");
16 mprintf("\n10 praportional to 2 praportional to 1000
17          ");
18
19 //result
20 mprintf("v      = %3.2 f volt",v);

```

Scilab code Exa 5.30 Find the potential difference

```

1 //


---


2 //chapter 5 example 30
3
4 clc;clear all;
5
6 //variable declaration
7 d      = 0.08;           //diameter in m
8 D      = 0.004;         //distance between plates in m
9 F      = 0.002;         //force in Newton

```

```

10
11 //calculations
12 e0 = 8.85*10^-12; //permittivity in N
13 A = (%pi/4)*(d^2); //area of the plates in
    m**2
14 x = (F*2*(D^2))/(e0*A);
15 V = sqrt(x); //potential difference in
    V
16
17 //result
18 mprintf("potential difference = %3.1f V",V);
19 mprintf("\nNote:final answer in textbook is wrong
    printed")

```

Scilab code Exa 5.31 Find the change in capacitance

```

1 //


---


2 //chapter 5 example 31
3
4 clc;
5 clear all;
6
7 //variable declaration
8 d = 0.1; //diameter in m
9 F = 0.005; //force in Newton
10 V = 10000; //potential difference in V
11 e0 = 8.85*10^-12; //permittivity in N
12 d2 = 26.4*10^-3; //distance between plates in
    mm
13 d1 = 25.4*10^-3; //distance between plates in
    mm
14
15 //calculations

```

```

16
17 A      = (%pi/4)*(d^2);      //area of the plates in
    m**2
18 x      = sqrt((e0*A)/(2*F));
19 d2     = x*V;                //distance between
    plates in mm
20 //C     = e0*A/d
21 x1     = 1/d1;
22 x2     = 1/d2;
23 C      = e0*A*(x1-x2);      //change in capacitance
    in uF
24
25 //result
26 mprintf("change in capacitance due to change in
    distance between plates from 26.4 to 25.4 mm = %3
    .2f u uF", (C*10^12));

```

Scilab code Exa 5.32 Finding the capcaitance

```

1 //


---


2 //chapter 5 example 32
3
4 clc;
5 clear all;
6
7 //variable declaration
8 K      = 0.0981*10^-6;
9 theta  = 80;                //full scale of
    deflection in
10 V      = 1000;             //voltage in V
11 C      = 10*10^-12;        //capacitance in
    F
12

```



```

13 //calculations
14 //x      =dC/dtheta = (2*K*theta)/V^2
15 x        = (2*K*theta)/V^2;           //rate of change
        of capacitance
16 dC       = x*(theta/180)*%pi;
17 C1       = C+dC;
18
19 //result
20 mprintf("capacitance when reading 1kV = %3.3e F",C1)
    ;

```

Scilab code Exa 5.33 Determine the pd for different deflections

```

1 //


---


2 //chapter 5 example 33
3
4 clc;
5 clear all;
6
7 //variable declaration
8 //x = dC/d(theta)
9 //Td = (1/2)*(V^2)*(dC/d(theta))
10 x      = 0.5*10^-12;           //dC/d(theta) in
        pF/degree
11 y      = 1.5*10^-12;           //dC/d(theta) in
        pF/degree
12 T      = 8*10^-6;             //torison constant in Nm
13 N1     =100;
14 N2     =35;
15
16 //calculations
17 x1     = x*(180/%pi);         //dC/d(theta) in
        pF/radian

```

```

18 y1      = y*(180/%pi);           //dC/d(theta) in
    pF/radian
19 //Td      = Tc = T*N*(%pi/180)
20 Td      = T*N1*(%pi/180);       //
    deflecting torque in N-m
21 V1      = sqrt((2*Td)/x1);       //voltage
    required in V
22 Td1     = T*N2*(%pi/180);       //
    deflecting torque in N-m
23 V2      = sqrt((2*Td1)/y1);     //voltage
    required in V
24
25 //result
26 mprintf("voltage deflection at 100 = %3.0f V",V1);
27 mprintf("\nvoltage deflection at 100 = %3.0f V",V2);

```

Scilab code Exa 5.34 Determine the pd for required to pull the plate three quarter

```

1 //


---


2 //chapter 5 example 34
3
4 clc;
5 clear all;
6
7 //variable declaration
8 e0      =8.854*10^-12;
9 d       =0.05;
10 er     = 1;
11 a      = 0.25;
12 V1     = 12000;           //voltage in V
13 V2     = 32000;         //voltage in V
14
15

```

```

16 // calculations
17 //x-x0      = (1/2)*((V^2)/k)*(dc/dx)
18 //C         =(2*e0*er*A)/d
19 //dC       =(2*e0*er*a*x)/d
20 // y = dC/dx = (2*e0*er*a)/d
21 y          = (2*e0*er*a)/d;
22 X1         = 0.25/4;
23 // A =x1+x01      = (1/2)*((V1^2)/k)*(dc/dx)
24 X2         = 0.25/2;
25 //B = x2+x01      = (1/2)*((V2^2)/k)*(dc/dx)
26 //C          = B/A  =(V2/V1)^2
27 C          = (V2/V1)^2;
28 x01        = (X2-(C*X1))/(1-C);
29 k          = ((1/2)*((V1^2))*(y))/(X1-x01);
30 X3         = (3/4)*0.25;
31 V          = sqrt(((X3-x01)*2*k)/y);           //
           voltage in V
32
33 //result
34 mprintf("voltage required to pull the plate three
           quarte way in = %3.3f KV", (V*10^-3));

```

Scilab code Exa 5.35 Calculate the spring constant

```

1 //


---


2 //chapter 5 example 35
3
4 clc;
5 clear all;
6
7 //variable declaration
8 e      = 8.85*10^-12;
9 V      = 10000;           //voltage in V

```

```

10 r          = 40*10^-3;          //radius in m
11
12 //calcaulations
13 d          = (4/2)*10^-3;      //voltage in V
14 theta      = (100)*(%pi/180);
15 k          = (2.5*e*(r^2)*(V^2))/(d*theta);
16
17 //result
18 mprintf("spring constant = %3.3e Nm per radian",k);

```

Scilab code Exa 5.36 Determine the deflection of the instrument

```

1 //


---


2 //chapter 5 example 36
3
4 clc;
5 clear all;
6
7 //variable declaration
8 theta1     = 105;              //deflection in
9 I1         = 20;               //current in A
10 I2        = 20;               //current in A
11 f1        = 50;               //frequency in Hz
12 f2        = 75;               //frequency in Hz
13
14
15 //calculations
16 theta      = (theta1)*((I2/I1)^2)*(f2/f1);
17
18 //result
19 mprintf("deflection of the instrument while
    measuring 20 A = %3.1f ",theta);

```

Scilab code Exa 5.37 Determine the voltage

```
1 //


---


2 //chapter 5 example 37
3 clc;
4 clear all;
5
6 //variable declaration
7 V1          = 240;          //voltage in V
8 theta1      = 300;          // defelection in
9 theta2      = 180;          // defelection in
10
11 //calculations
12 //T praportional to V^2/Z)*(f*cos(alpha)*(sin(beta))
13 //T praportional V^2
14 //theta praportional to V^2
15 V2          = V1*sqrt(theta2/theta1);
16
17 //result
18 mprintf("voltage for deflection of 180 =%3.0 f ",
          V2);
```

Chapter 6

Extensions of instrument range

Scilab code Exa 6.1 Finding the value of shunt resistance

```
1 //


---


2 //chapter 6 example 1
3
4 clc;
5 clear all;
6
7 //variable declaration
8 Im = 50*10^-6; //full scale
   deflection current in A
9 Rm = 1000; //instrument resistance in
10 I = 1; //total current to be
   measured in A
11
12 //calculations
13 Rs = (Rm/((I/(Im))-1)); //resistance of
   ammeter in
14
15
```

```

16 //result
17 mprintf("resistance of ammeter shunt required Rs =
    %3.7f    ",Rs);

```

Scilab code Exa 6.2 Find the current range of instrument and the value of resistance

```

1 //
=====

2 //chapter 6 example 2
3 clc;clear all;
4
5 //variable declaration
6 Rm      = 1;
                                     //
    instrument resistance in
7 Rse     = 4999;
    //series resistance in
8 V       = 250;
                                     //full
    -scale deflection voltage in V
9 Rs      = 4999;                    //Shunt resistance in
    (Rs =1/(499))
10 I1     = 50;
                                     //
    full-scale defelction current in A
11
12 //calculations
13 Rs1     = 1/(Rs);
14 Im      = V/(Rm+Rse);              //full-scale
    deflection current in A
15 I       = Im*(1+(Rm/Rs1));        //current in A
16 N       = I1/(Im);
17 Rsh     = Rm/(N-1);              //shunt
    resistance in

```

```

18
19 //result
20 mprintf("full-scale defelction current in Im = %3.2 f
    A",Im);
21 mprintf("\ncurrent range of instrument when used as
    an ammeter with coil connected across shunt is I
    = %3.2 f A",I);
22 mprintf("\nShunt resistance for the instrument to
    give a full-scale deflection of 50A is Rsh = %3.4
    f ",Rsh);

```

Scilab code Exa 6.3 Find the shunt resistance required

```

1 //


---


2 //chapter 6 example 3
3
4 clc;clear all;
5
6 //variable declaration
7 Rm    = 10;
                                     //
    instrument resistance in
8 Im    = 0.05;                       //full
    scale defelection current in A
9 I     =100;                          //
    current to be measured in A
10 V    = 750;
                                     //
    voltage to be measured in V
11
12 //calculations
13 R     = (V/(Im))-Rm; //series resistance in
14 N     = I/(Im);     //power

```



```

    of shunt
15 Rs    = Rm/(N-1);           //resistance in
16
17
18
19 //result
20 mprintf("resistance to be connected in series to
    enable the instrument to measure current upto 1A
    is %3.5f    ",R);
21 mprintf("\nshunt resistance required for full-scale
    defelction with 10v is %3.4f    ",Rs);

```

Scilab code Exa 6.4 Calculate the resistance parallel and series

```

1 //


---


2 //chapter 6 example 4
3 clc;clear all;
4
5 //variable declaration
6 Rm    = 5;
    //
    instrument resistance in
7 Im    = 15*10^-3;           //full
    scale defelection current in A
8 I     =1;                   //
    current to be measured in A
9 V     = 10;                 //
    voltage to be measured in V
10
11 //calculations
12 N     = I/(Im);           //power
    of shunt

```

```

13 Rs    = Rm/(N-1);           //resistance in
14 R     = (V/(Im))-Rm; //series resistance in
15
16
17 //result
18 mprintf("resistance to be connected in parallel to
    enable the instrument to measure current upto 1A
    is %3.5f    ",Rs);
19 mprintf("\nshunt resistance required for full-scale
    defelction with 10v is %3.4f    ",R);

```

Scilab code Exa 6.5 Finding the current range of instrument

```

1 //


---


2 //chapter 6 example 5
3 clc;clear all;
4
5 //variable declaration
6 Rm = 2;
    //
    instrument coil resistance in
7 V = 250;
    //
    full-scale reading in V
8 Rs = 5000;
    //
    series resistance in
9 Rsh = 2*10^-3;
    //
    shunt resistance in
10
11
12 //calculations

```

```

13 Im    = V/((Rm+Rs));
    //current flowing through the instrument for full
    -scale deflection in A
14 Is    = (Im*Rm)/(Rsh);           //current through
    shunt resistance in A
15 I     = Im+Is;
                                           //
    current range of instrument in A
16
17 //result
18 mprintf("current flowing through the instrument for
    full-scale deflection is %3.5fA",Im);
19 mprintf("\ncurrent through shunt resistance is %3.2f
    A",Is);
20 mprintf("\ncurrent range of instrument is %3.1f A",I)
    ;

```

Scilab code Exa 6.6 Finding the shunt current and the value of R

```

1 //


---


2 //chapter 6 example 6
3 clc;clear all;
4
5 //variable declaration
6 Rsh  = 0.02;           //shunt
    resistance in
7 V    = 0.5;           //potential
    difference across the shunt in V
8 Rm   = 1000;         //resistance in
9 I1   = 10;           //current
    in A
10 I2  = 75;           //current

```

```

    in A
11 I      = 100;           //current in A
12 x      = 40;           //deflection %
13
14 //calculations
15 Is      = V/(Rs);      //
    current through shunt in A
16 Im      = V/(Rm);      //current
    through ammeter for full-scale defelction in A
17 V1      = I1*Rsh;
    //voltage across shunt for 10A in V
18 R1      = V1/(Im);     //resistance for the
    ammeter for a current of 10 A for full-scale
    defelction in
19 V2      = I2*Rsh;
    //voltage across shunt for 75A in V
20 R2      = V2/(Im);     //resistance for the
    ammeter for a current of 75 A for full-scale
    defelction in
21 I3      = I*(100/(x)); //full-scale
    defelction current when 100 A gives 40%
    defelction
22 V3      = I3*Rsh;
    //voltage across shunt for 250 A in V
23 R3      = V3/(Im);     //resistance for the
    ammeter for a current of 250 A for full-scale
    defelction in
24
25
26 //result
27 mprintf("current through ammeter for full-scale
    defelction is %3.2f mA",(Im*103));
28 mprintf("\\nResistance for the ammeter for a current
    of 10 A for full-scale defelction is %3.2f ",R1
    );
29 mprintf("\\nResistance for the ammeter for a current
    of 75 A for full-scale defelction is %3.2f ",R2
    );

```

```

30 mprintf("\nResistance for the ammeter for a current
    of 250 A for full-scale deflection is %3.2f ",
    R3);

```

Scilab code Exa 6.7 Finding the resistance that must put in series

```

1 //


---


2 //chapter 6 example 7
3
4 clc;clear all;
5
6 //variable declaration
7 B      = 0.5;           //flux density of the
    magnetic field in Wb/m**2
8 N      = 100;          //number of turns in coil
9 l      = 0.04;         //length in m
10 r     = 0.03;         //width in m
11 Tc    = 120*10^-6;    //controlling torque
    in N-m
12 v     = 1;           //volts per division in V
13 n     = 100;         //number of division on full
    -scale
14 Rm    = 0;
15
16 //calculations
17 x     = B*N*l*r;
18 I     = Tc/(x);      //current for full-scale
    deflection in A
19 V     = n*v;         //full-scale reading of
    instrument in V
20 R     = (V/(I))-(Rm); //External
    resistance required to be put in series with the
    coil in

```

```

21
22 //result
23 mprintf("current for full-scale deflection is %3.3f
        A",I);
24 mprintf("\nExternal resistance required to be put in
        series with the coil is %3.2f ",R);

```

Scilab code Exa 6.8 Calculate the error

```

1 //


---


2 //chapter 6 example 8
3 clc;clear all;
4
5
6 //variable decalaration
7 Rm      = 5;           //coil resistance in
8 Rm1     = 0.00075;    //coil resistance in
9 Im      = 0.015;     //full-scale defelction
        current in A
10 I       = 100;      //current to be measured in
        A
11 T1      = 0.004;    //temperature coeficient of
        copper in / / C
12 T2      = 0.00015;  //temperature coeficient
        of manganin in / / C
13 T       =10;        //rise in temperature in C
14
15 //calculations
16 N       = I/(Im);    //multiplying power of shunt
17 Rs      = Rm/(N-1); //resistance of manganin shunt
        in
18 Rc      = Rm*(1+(T1*T)); //coil resitance with 10 C
        in temperature in

```

```

19 Rsh      = Rm1*(1+(T2*T));    //shunt resitance with
    10 C in temperature in
20 In       = (Rsh/((Rc+Rsh)))*100; //new instrument
    current in A
21 r        = (In/(Im))*100;     //new instrument
    reading in A
22 e        = ((r-I)/(I))*100;   //percentage error
    in %
23
24
25 //result
26 mprintf('percentage error %3.3f percentage",e);

```

Scilab code Exa 6.9 Calculate the error

```

1 //


---


2 //chapter 6 example 9
3 clc;clear all;
4
5 //variable declaration
6 Rm      = 25;                //instrument resistance in
7 V       = 25*10^-3;         //full-scale deflection
    voltage in V
8 V1      = 10;                //voltage to be measured in
    V
9 t       = 10;
10 alphac = 0.004;
11 alpham = 0.00015;
12
13 //calculations
14 Im      = V/(Rm);           //full-scale deflection in mA
15 R       = (V1/(Im))-Rm;    //external resistance in

```

```

16 Rt      = Rm+R;
17 Rm1 = Rm*(1+(alphac*t));    //instrument resistance
    with 10 C rise in temperature in
18 R1      = R*(1+(alphan*t)); //series resistance with
    10 C rise in temperature in
19 R2      = Rm1+R1;          //total resistance in the
    voltmeter circuit in
20 V2      = V1*(Rt/(R2));    //reading of voltmeter at 10
    C rise in temperature in V
21 er      = ((V2-V1)/(V1))*100; //percentage error in %
22
23 //result
24 mprintf('percentage error = %3.2f percentage',er);

```

Scilab code Exa 6.10 Determine the ratio of R and r

```

1 //


---


2 //chapter 6 example 10
3
4 clc;clear all;
5
6 //variable declaration
7 alpha0 = 0.0043;
8 t1      = 25;           //temperature in C
9 t2      = 45;           //temperature in C
10 e       = 1.1;         //percentage error in %
11
12 //calculations
13 R1      = ((1+(alpha0*t2))/(1+(alpha0*t1)));
14 //r1    = R1*r
15 //I2    = V/r1+R
16 //e     = (I1-I2)/100
17 //I2    = 0.989 I1

```



```

18 //I2      = V/1.0776 r+R
19 //I1      = V/R+r
20 //V/(1.0776 r+R) = 0.989V/R+r
21 //R/r     = 5.96
22 x         = 5.96;
23
24 //result
25 mprintf("R/r= %3.2 f",x);

```

Scilab code Exa 6.11 Finding the reading of instruments

```

1 //


---


2 //chapter 6 example 11
3
4 clc;clear all;
5
6 //variable declaration
7 Rm1      = 1000;      //resistance of ammeter of A1 in
8
9 Rs1      = 0.05;     //resistance of shunt connected
   across ammeter A1 in
10 Rm2     = 1500;     //resistance of ammeter of A2 in
11
12 Rs2     = 0.02;     //resistance of shunt connected
   across ammeter A2 in
13 I       =10;       //current in A
14
15 //calculations
16 //in normal connecetion
17 I1     = (Rs1/(Rs1+Rm1))*I;      //current through in
   A
18 I2     = (Rs2/(Rs2+Rm2))*I;      //current through in
   A

```

```

17 //when shunts are interchanged
18 I11 = (Rs2/(Rs2+Rm1))*I; //current through
    in A
19 I12 = (Rs1/(Rs1+Rm2))*I; //current through
    in A
20 A1 = (I11/(I1))*I; //current through
    ammeter in A
21 A2 = (I12/(I2))*I; //current through
    ammeter in A
22
23 //calculations
24
25 mprintf("reading of ammeter A1 = %3.0d A",A1)
26 mprintf("\nreading of ammeter A2 = %3.0f A",A2);

```

Scilab code Exa 6.12 Finding the series resistance would be necessary to increase

```

1 //


---


2 //chapter 6 example 12
3
4 clc;clear all;
5
6 //variable declaration
7 Rv = 2400; //resistance in
8 L = 0.6; //instrument inductance in H
9 f = 60; //frequency in Hz
10
11 //calculations
12 XL = 2*pi*f*L; //instrument reactance
    in
13 Z = sqrt((Rv^2)+(XL^2)); //instrument
    impedance in
14 //when the instrument range is extended from 120V to

```

```

        600V the impedance will have to be made 5 times
        in order to have the same current
15 //math.sqrt((RV**2)+XL^2) = 5*Z
16 x    = (5*Z)^2;
17 y    = XL^2;
18 z    = x-y;
19 a    = (sqrt(z));
20 R    = a-Rv;          //series resistance in
21
22 //result
23 mprintf("instrument reactance = %3.1f    ",XL);
24 mprintf("\nseries resistance = %3.2f    ",R);

```

Scilab code Exa 6.13 Determine the capacitance of the condenser multiplier require

```

1 //


---


2 //chapter 6 example 13
3 clc;clear all;
4
5 //variable declaration
6 Cv    = 70*10^-12;    //capacitance in F
7 V     =10000;        //electrostatic
    measurement in V
8 Vv    = 100;        //reading in V
9
10 //calculations
11 Vc    = V-Vv;       //voltage across series capacitor
    in V
12 //since the capacitors are connected in series ,te
    charge on each is same
13 //Vv*Cv = Vc*C
14 C     = (Vv*Cv)/(Vc);    //capacitance in uuF
15

```

```

16 //result
17 mprintf("capacitance of the condenser = %3.4f uuF "
    ,(C*10^12));

```

Scilab code Exa 6.14 Calculating the necessary values of resistor

```

1 //


---


2 //chapter 6 example 14
3 clc;clear all;
4
5 //variable declaration
6 Rm =40; //resistance in
7 Im = 1; //current in mA
8 I1 = 10; //current in mA
9 I2 = 20; //current in mA
10 I3 = 30; //current in mA
11 I4 = 40; //current in mA
12 I5 = 50; //current in mA
13
14 //calculations
15 R1 = Rm/(((I1/(Im))-1);
16 R2 = (R1+Rm)/(((I2/(Im))));
17 R3 = (R1+Rm)/(((I3/(Im))));
18 R4 = (R1+Rm)/(((I4/(Im))));
19 R5 = (R1+Rm)/(((I5/(Im))));
20 r1 = R1-R2; //resistance in
21 r2 = R2-R3; //resistance in
22 r3 = R3-R4; //resistance in
23 r4 = R4-R5; //resistance in
24 r5 = R5; //resistance in
25
26 //result
27 mprintf("resistance of various section of the

```

```

ayrtons shunt are = %3.4f      , %3.4f      , %3.4f
      , %3.4f      , %3.4f      ",r1,r2,r3,r4,r5);

```

Scilab code Exa 6.15 Explaining conversion of multi range voltmeter

```

1 //


---


2 //chapter 6 example 15
3 clc;clear all;
4
5 //variable declaration
6 Si = 0.1*10^-3; //current sensitivity in mA
7 Rm = 500; //meter resistance in
8 V1 = 10; //full -scale voltage in V
9 V2 =50; //volage range in V
10 V3 =100; //volage range in V
11 V4 =500; //volage range in V
12
13 //calculations
14 Sv = (1/(Si))*10^-3; //voltage sensitivity in
 //V
15 Rm1 =500*10**-3; //Rm in k
16 RT1 = Sv*V1; //total resistance required
 //in k
17 R1 = RT1-Rm1; //additional resistance in
 //k
18 RT2 = Sv*V2; //total resistance required
 //in k
19 R2 = RT2-Rm1-R1; //additional resistance
 //in k
20 RT3 = Sv*V3; //total resistance required
 //in k
21 R3 = RT3-Rm1-R2-R1; //additional
 //resistance in k

```

```

22 RT4    = Sv*V4;          //total resistance required
    in k
23 R4     = RT4-Rm1-R1-R2-R3;      //additional
    resistance in k
24
25 //result
26 mprintf("additional resistance = %3.2f k ",R1);
27 mprintf("\nadditional resistance = %3.2f k ",R2);
28 mprintf("\nadditional resistance = %3.2f k ",R3);
29 mprintf("\nadditional resistance = %3.2f k ",R4);

```

Scilab code Exa 6.16 Calculate the flux density and current ratio and phase angle

```

1 //


---


2 //chapter 6 example16
3
4 clc;clear all;
5
6 //variable declaration
7 Tp    = 1;      //numberof turns on primary
8 Ts    = 200;    //numberof turns on secondary
9 Is    = 5;      //secondary current in A
10 Zs   = 1;      // secondary burden in
11 f     = 50;    //frequency in Hz
12 a     = 0.0011; //cross sectional area of core
    in m**2
13 S     = 0.91;  //stamping faactor
14 KT    =200;    //turns ratio
15 M     =80;     //ampere turns
16 Vs    =5;      //voltage
17
18 //calculations
19 Vs    = Is*Zs; //secondary voltage in V

```

```

20 phimax    = Vs/(4.44*f*Ts);    //flux in the core in
    mWb
21 A         = a*S;              //net crss sectional area in m
    **2
22 Bmax      = phimax/(A);       //flux density in the core
    in T
23 Im        = M/(Tp);           //magnetising current in A
24 Ip        = sqrt(((KT*Is)^2)+(Im**2)); //primary
    current in A
25 Ir        = Ip/(Is);          //current ratio
26 b         = ((180/(%pi))*(Im/(KT*Is))); //phase
    angle in (degrees)
27
28 //result
29 mprintf("flux density in the core = %3.4f T",Bmax);
30 mprintf("\ncurrent ratio = %3.2f",Ir);
31 mprintf("\nphase angle = %3.2f    ",b);

```

Scilab code Exa 6.17 Calculate the flux in the core and ratio error

```

1 //


---


2 //chapter 6 example 17
3
4 clc;clear all;
5
6 //variable declaration
7 Tp    = 1;    //number of turns in primary
8 KT    = 200;  //turns ratio
9 Is    = 5;    //secondary current in A
10 Rs   = 1.5;  //secondary burden in
11 f    = 50;   //frequency in Hz
12 L    =1.5;   //iron loss in Watts
13 Ie   = 40;   //current in A

```

```

14
15 //calculaations
16 Ts      = KT*Tp;           //number of turns in secondary
17 Vs      = Is*Rs;           //secondary voltage in V
18 phimax   = Vs/(4.44*f*Ts); //flux inn the core in
    mWb
19 Il      = L/(Vs);         //iron-loss in the secondary
    side in A
20 Ip      = KT*Il;         //iron-loss current in
    primary side in A
21 x       = (KT*Is)+Ie;
22 e       = ((-Ie/((x))))*100; //ratio error in
    %
23
24 //result
25 mprintf("flux in the core = %3.3e percentage mWb", (
    phimax*10^3));
26 mprintf("\nratio error = %3.4f percentage",e);

```

Scilab code Exa 6.18 Determine the ratio and phase angle errors

```

1 //


---


2 //chapter 6 example 18
3
4 clc;
5 clear all;
6
7 //variable declraration
8 Ts = 300; //number of turns in secondary winding
9 Tp = 1; //number of turns in primary winding
10 Is =5; //current in A
11 Zs = (1.5)+(i*1) //secondary impedance
12 MMF = 100;

```



```

13 Pi = 1.2;           //iron loss in watts
14 KN = 300;          //turn ratio
15
16
17 //calculations
18 KT =Ts/Tp;         //turn ratio
19 Es = Is*Zs;        //secondary voltage in volts
20 Es1 = sqrt(((real(Es))^2)+((imag(Es))^2));
21 Im =MMF/Tp;        //magnetising current
    in A
22 E = Pi/Es1;        //energy component of
    exciting current on secondary side in A
23 Ie = KT*E;         //energy component of
    exciting current on primary side in A
24 IO = Im+%i*Ie;     //exciting current on
    primary side in A
25 IO1 =sqrt(((real(IO))^2)+((imag(IO))^2));
26 alpha = atan(Ie/Im);
27 alpha1 = (alpha*180)/%pi;
28 theta = atan(imag(Zs)/real(Zs));
29 theta1 = (theta*180)/%pi;
30 KC = KT+((IO1*sin(((theta1+alpha1)*%pi)/180))/Is);
    //actual current ratio
31 e = ((KN-KC)/KC)*100;           //percentage
    ratio error in %
32 b = (IO1*cos(((theta1+alpha1)*%pi)/180))/(KT*Is)
    ;           //phase angle in radians
33 b1 = b*(180/%pi);
34
35
36 //result
37 mprintf("percentage ratio error =%3.2f    percentage
    ",e);
38 mprintf("\nphase angle = %3.2f    ",b1);

```

Scilab code Exa 6.19 Finding the primary current and ratio error and number of turns

```

1 //


---


2 //chapter 6 example 19
3 clc;
4 clear all;
5
6 //variable declraration
7 Ts = 200; //number of turns in secondary winding
8 Tp = 1; //number of turns in primary winding
9 Is = 5; //current in A
10 Zs = (1.2+0.2j)+(i*(0.5+0.3j)); //secondary
    impedance
11 MMF = 100;
12 Pi = 1.2; //iron loss in watts
13 Ie = 50; //energy component of eddy current
    in A
14
15
16
17 //calculations
18 KT =Ts/Tp //turn ratio
19 //Es = Is*Zs //secondary voltage in
    volts
20 Im =MMF/Tp //magnetising current in A
21 I0 = Im+i*Ie //exciting current on primary
    side in A
22 I01 =sqrt(((real(I0))^2)+((imag(I0))^2))
23 alpha = atan(Ie/Im)
24 alpha1 = (alpha*180)/%pi
25
26 theta = atan(imag(Zs)/real(Zs))
27 theta1 = (theta*180)/%pi
28 Ip = (KT*Is)+(I01*sin(theta+alpha)) //
    primary current in A
29 e = ((-I01*sin(((theta1+alpha1)*%pi)/180))/Ip)*100

```

```

        //ratio error
30 N    = (I01*sin(((theta1+alpha1)*%pi)/180))/Is
        //number of secondary turns to be
        reduced
31
32 //result
33 mprintf("ratio error = %3.1f percentage",e);
34 mprintf("\nnumber of secondary turns to be reduced
        = %3.0f ",N);

```

Scilab code Exa 6.20 Determine the primary current and phase angle of the transformer

```

1
2 //


---


3 //chapter 6 example 20
4
5 clc;
6 clear all;
7
8 //variable declaration
9 Ts = 300; //number of turns in secondary winding
10 Tp = 3; //number of turns in primary winding
11 Is = 5; //current in A
12 Zs = (0.583)+%i*(0.25); //secondary impedance
13 n1 =10;
14 n2 =5;
15
16 //calculations
17 KT =Ts/Tp; //turn ratio
18 Es = Is*Zs; //secondary voltage in volts
19 Nm = n1*Es; //total magnetising amp-turns
20 Ni =n2*Es; //total iron loss amp-turns

```

```

21 Im =Nm/Tp; //magnetising componenet of exciting
    current in A
22 Ie = Ni/Tp; //
23 IO = Im+%i*Ie; //exciting current on primary side
    in A
24 IO1 =sqrt(((real(IO))^2)+((imag(IO))^2))
25 alpha = atan(Ie/Im); //energy component of
    exciting current in A
26 alpha1 = (alpha*180)/%pi
27 theta = atan(imag(Zs)/real(Zs));
28 theta1 = (theta*180)/%pi
29 x = sin(((theta1+alpha1)*%pi)/180)
30 Ip = (KT*Is)+(IO1*x); //primary current in A
31 y = cos(((theta1+alpha1)*%pi)/180);
32 b =(180/%pi)*((IO1*y)/(KT*Is)); //phase
    angle
33
34
35 //result
36 mprintf("primary current = %3.0d A",Ip);
37 mprintf("\nphase angle = %3.3f ",b);

```

Scilab code Exa 6.21 Calculate the ratio error and phase angle error

```

1 //


---


2 //Chapter 6 Example 21
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 R = 25; //rate burden in VA

```

```

10 Is      = 5;           //current in A
11 r       = 6;           //Rs/Es ratio of resistance
    to reactance
12 IL      = 0.2;         //iron loss in W
13 Im      = 1.5;         //magnetising compnent of
    current in A
14
15
16 //calculations
17 KT      = 100/5;       //turn ratio
18 Es      = R/Is;        // Secondary rated
    voltage in V
19 Zs      = Es/Is;       //total secondary
    impedance in
20 theta   = (atan(1/r))*180/%pi;    //angle in

21 Zs1     = (Zs*cos(theta*%pi/180))+(Zs*sin(theta
    *%pi/180))*%i;
22 Ie      = KT*0.04;     //energy component
    of exciting current on primary side
23 r       = (((Im*sin(theta*%pi/180)))+(Ie*cos(
    theta*%pi/180)))/((KT*Is)+(Ie*cos(theta*%pi/180))
    +(Im*sin(theta*%pi/180)))*100;    //percentage
    ratio error in %
24 beta    = (180/%pi)*(((Im*cos(theta*%pi/180))-(
    Ie*sin(theta*%pi/180)))/(KT*Is));    //phase
    angle erro in
25
26 //result
27 mprintf("percentage ratio error = -%3.1f percentage
    ",r);
28 mprintf("\nphase angle error = %3.4f    ",beta);

```

Scilab code Exa 6.22 Find the ratio and phase angle errors

```

1 //


---


2 //Chapter 6 Example 22
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 r      = 12.5;           //rate burden in VA
10 Is    = 5;             //secondary rated current in
    A
11 f      = 50;           //frequency in Hz
12 L      = 0.96*10^-3;
13 Im     = 16;           //magnetising component
    of exciting current in A
14 Ie     = 12;           //energy component of
    exciting current in A
15 Is     = 5;           //secondary rated
    current in A
16
17
18 //calculations
19 KN     = 1000/5;       ///nominal ration
20 KT     = 196/1;       //turn ratio
21 Es     = r/Is;        //secondary rated
    voltage in V
22 Zs     = Es/Is;       //secondary impedance in
23 Xs     = 2*pi*f*L;    //secondary reactance in
24 theta  = (asin(Xs/Zs))*180/pi; //
    secondary circuit phase angle in
25 KC     = KT+(((Ie*cos(theta*pi/180))+(Im*sin(
    theta*pi/180))))/Is);
26 e      = ((KN-KC)/KC)*100; //ratio error
27 beta   = (180/pi)*(((Im*cos(theta*pi/180))-

```

```

    Ie*sin(theta*pi/180))/(KT*Is));           //phase
    angle erro in
28
29 //result
30 mprintf("ratio error = %3.2f percentage ",e);
31 mprintf("\nphase angle error = %3.2f    ",beta);

```

Scilab code Exa 6.23 Estimate CT ratio and phase angle error

```

1 //


---


2 //chapter 6 example 23
3
4 clc;
5 clear all;
6
7 //variable declaration
8 KT = 8;           //turn ratio
9 Ie = 0;           //current in A
10 I0 = 0.08;
11 R1 = 1.5;         //resistance in
12 R2 = 0.4;         //resistance in
13 L1 =60*10^-3;    //inductance in H
14 L2 =0.7*10^-3;  //inductance in H
15 f = 50;          //frequency in Hz
16 phi = 0;         //angle in
17
18 //calculations
19 Im = 0.01*KT;    //Im = 1% of primary current =
    0.01*Ip = 0.01*KT*Is
20 alpha =atan(Ie/Im); //phase angle in radians
21 R = R1+R2;       //resistance of burden
22 L = L1+L2;       //inductance in H
23 theta = (atan((2*pi*f*L)/R))*pi/180); //phase

```

```

    angle in
24 KC = KT+((I0*sin(theta+alpha))/Is);
25 KC = KT+((0.08*Is*sin(theta+alpha))/Is);
26 KC = KT+(0.08*sin(theta+alpha));          //actual
    current ratio
27 b = (I0*cos(theta+phi))/(KT*Is);
28
29 //result
30 mprintf("actual current ratio = %3.1f ",KC);
31 mprintf("\nphase angle error = %3.2d ",b);

```

Scilab code Exa 6.24 Find the ratio and phase angle errors

```

1 //


---


2 //chapter 6 example 24
3 clc;
4 clear all;
5
6 //variable declaration
7 KT = 201;          //turn ration
8 Is = 5;           //secondary current in A
9 Im = 7;           //magnetising component of exciting
    current in A
10 Ie = 3;          //cross-loss component of exciting
    current in A
11 delta =0;
12
13 //calculations
14 Kn = 1000/5;      //nominal ratio
15 alpha =atan(Ie/Im); //angle in
16 alpha1 = (alpha*180)/%pi;
17 theta = delta-(((acos(0.8))*180)/%pi); //
    from figure taken the value of gamma

```



```

18 z    = cos((theta*%pi)/180);
19 z1   = sin((theta)*%pi)/180);
20 Kc   = KT+(((Ie*z)+(Im*z1))/Is);           //actual
        current in A
21 e    = ((Kn-Kc)/Kc)*100; //ratio error
22 b    = (180/%pi)*(((Im*z)-(Ie*z1))/(KT*Is));
23
24 //result
25 mprintf("ratio error = %3.3f percentage",e);
26 mprintf("\nphase angle error = %3.3f    ",b);

```

Scilab code Exa 6.25 Determine the phase angle and ratio error

```

1
2 //

```

```

3 //chapter 6 example 25
4
5 clc;
6 clear all;
7
8 //variable declaration
9 KT = 201;           //turn ration
10 Ie = 3;            //cross loss current in A
11 Im = 7;           //magnetising component of exciting
        current in A
12 delta =0;
13 Kn = 200;
14
15 //calculations
16
17 theta = delta+(((acos(0.8))*180)/%pi); //from
        figure taken the value of gamma
18 z    = cos((theta*%pi)/180);

```

```

19 z1 = sin(((theta)*%pi)/180);
20 Kc = KT+(((Ie*z)+(Im*z1))/Is);          //actual
      current in A
21 e   = ((Kn-Kc)/Kc)*100;                //ratio error
22 b   = (180/%pi)*(((Im*z)-(Ie*z1))/(KT*Is));
23
24 //result
25 mprintf("ratio error = %3.3f percentage",e);
26 mprintf("\nphase angle error = %3.4f    ",b);

```

Scilab code Exa 6.26 Determine the phase angle and ratio error

```

1
2 //

```

```

3 //chapter 6 example 26
4 clc;
5 clear all;
6
7 //variable declaration
8 KT = 199;          //turn ration
9 Is = 5;           //secondary current in A
10 Im = 7;          //magnetising component of exciting
      current in A
11 Ie = 4;          //cross-loss component of exciting
      current in A
12 delta =0;
13
14 //calculations
15 KN = 1000/5      //nominal ratio
16 alpha =atan(Ie/Im) //angle in
17 alpha1 = (alpha*180)/%pi
18 theta = delta+(((acos(0.8))*180)/%pi) //from
      figure taken the value of gamma

```

```

19 z    = cos((theta*%pi)/180)
20 z1   = sin(((theta)*%pi)/180)
21 Kc   = KT+(((Ie*z)+(Im*z1))/Ie) //actual current in
    A
22 e    = ((KN-Kc)/Kc)*100 //ratio error
23 b    = (180/%pi)*(((Im*z)-(Ie*z1))/(KT*Is))
24 theta1 = delta-(((acos(0.8))*180)/%pi) //from
    figure taken the value of gamma
25 z11  = cos((theta1*%pi)/180)
26 z12  = sin(((theta1)*%pi)/180)
27 Kc1  = KT+(((Ie*z11)+(Im*z12))/Is) //actual current
    in A
28 e1   = ((KN-Kc1)/Kc1)*100 //ratio error
29 b1   = (180/%pi)*(((Im*z11)-(Ie*z12))/(KT*Is))
30
31
32 //result
33 mprintf("ratio error = %3.2f percentage",e);
34 mprintf("\nphase angle error = %3.1f ",b);
35 mprintf("\nratio error = %3.2f percentage",e1);
36 mprintf("\nphase angle error = %3.2f ",b1);

```

Scilab code Exa 6.27 Estimate the iron loss

```

1 //


---


2 //chapter 6 example 27
3
4 clc;
5 clear all;
6
7 //variable declaration
8 KT = 198; //turn ratio
9 e = 0; //ratio error

```

```

10 Is = 5; // secondary current in A
11 P = 5; //load in VA
12 Rs = 0.02; //resistance in
13 KN = 200; //KN=KC since e=0
14 KC = 200;
15
16 //calculations
17 V2 = P/Is; //secondary voltage in V
18 Es = V2+(Is*Rs); //secondary induced emf in V
19 Ep = Es/KT; //primary induced emf
20 Ie = (KC-KT)*Is; //eddy current loss in A
21 IL = Ep*Ie; //iron loss in W
22
23 //result
24 mprintf("iron loss = %3.3 f mW" ,(IL*10^3));

```

Scilab code Exa 6.28 Find the phase angle error at no load and load in VA at unity

```

1 //


---


2 //Chapter 6 Example 28
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 Vs = 100+0*%i; //secondary terminal
    voltage in V
10 Rp = 97.5; //primary resistance
    in
11 Xp = 67.4; //primary reactance
    in
12 Xl = 110; // total equivalent

```

```

reactance in
13 K          =1000/100;
14
15
16
17 //calculations
18 //Es        = Vs+(Is*(Rs+Xs*%i));
19 Es         = Vs;
20 Ep         = 10*(100+0*%i);          //induced emf in
primary winding in V
21 IO        = 0.02*(0.4-0.9165*%i);    //no
load current in A
22 Zp        = Rp+Xp*%i;
23 Vd        = IO*Zp;
24 Vp        = Ep+Vd;
25 beta      = (atan((imag(Vp))/real(Vp)))*180/%pi;
//phase angle between primary
and secondary voltage in
26 Xs1       = X1-Xp;                  //reactance of
secondary winding in
27 //Es       = Vs+(Is*Zs);           //induced emf
in secondary winding
28 //IP       = (Is/10)+IO;
29 //V        = Ip*Zp = (IS/10)+0.008-0.01833*i
30 //V        = (9.75*Is)+2.015)-((1.2478-6.74*Is)*%i)
..... equation 1
31 //Vp       = K*(ES+IP*ZP)
32 //VP       =(1002.015+18.35*%i)-(1.2478-11*Is)*%i
.... equation 2
33 //comparing equation 1 and 2 we get
34 //1.2478-11*Is =0;
35 Is        = 1.2478/11;             //secondary current
in A
36 v         = Vs*Is;
37
38 //result
39 mprintf("phase angle between primary and secondary
voltage = %3.2f lagging",beta);

```

```

40 mprintf("\nvolt ampere rating for zero phase angle =
    %3.2f",v);
41 mprintf("\nnote:Is values is taken as 0.114 wchich
    is approximate when answer is 0.1134");

```

Scilab code Exa 6.29 Calculate the ratio and phase angle errors

```

1 //


---


2 //Chapter 6 Example 29
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 Vs      = 63+0*i;           //secondary terminal
    voltage in V
10 Zs1     = 2+1*i;           //equivalent mpedance
    referred to primary in
11 Zb      = 100+200*i;       //secondary burden
    in
12 KN      =60.5;
13
14
15
16 //calculations
17 KT      = 3810/63;         //turn ratio
18 Ep      = KT*Vs;           //primary induced emf in
    V
19 Zp1     = (KT^2)*Zs1;      //equivalent
    impedance
20 Zs12    = sqrt(((real(Zp1))^2)+((imag(Zp1))^2));
21 Is      = Vs/Zb;           //secondary current

```

```

    in A
22 Is1    = sqrt(((real(Is))^2)+((imag(Is))^2));
23 Ip     = Is/KT;           //primary current in
    A
24 Ip1    = sqrt(((real(Ip))^2)+((imag(Ip))^2));
25 Vp     = Ep+(Ip*Zp1);    //applied voltage to
    primary in V
26 Vp1    = sqrt(((real(Vp))^2)+((imag(Vp))^2));
27 beta   = (atan((imag(Vp))/real(Vp)))*180/%pi;
    //phase angle error in
28 e      = (((KN*Vs)-Vp)/Vp)*100;           //
    ratio error in percentage
29 //beta   = (atan((imag(Zp1))/real(Zp1)))*180/
    %pi;
30
31 //result
32 mprintf("phase angle error = %3.2f    ",beta);
33 mprintf("ratio error = %3.1f percentage ",e);

```

Chapter 7

Analog measurement of power and wattmeters

Scilab code Exa 7.1 Calculate the power

```
1 //


---


2 //chapter 7 example 1
3
4 clc;clear all;
5
6
7 //variable declaration
8 P = 250; //wattmeter reading in watts
9 Rp = 2000; //pressure coil circuit resistance
   in
10 VL = 200; //load voltage in V
11
12 //calculations
13 p = (VL^2)/Rp; //power lost in pressure coil in
   watts
14 P1 = P-p; //power lost in the pressure coil
   circuit in watts
```



```

15
16
17 //result
18 mprintf("power lost in the pressure coil circuit =
    %3.2f watts",P1);

```

Scilab code Exa 7.2 Calculate the percentage error

```

1 //


---


2 //chapter 7 example 2
3
4 clc;clear all;
5
6 //variable declaration
7 x = 0.004;
8 y = 0.707; //power factor lagging
9 y1 = 0.5; //power factor lagging
10
11 //calculaitons
12 theta = atan(x) //theta in degrees
13 a = cos(theta)
14 b = sin(theta)
15 phi = acos(y)
16 c = cos(phi)/(a*cos(theta-phi)) //correction
    factor
17 A = cos(phi)/sin(phi);
18 e = (b/(A+b))*100 //percentage error in %
19 phi1 = acos(y1)
20 c1 = cos(phi1)/(a*cos(theta-phi1)) //correction
    factor
21 B = cos(phi1)/sin(phi1);
22 e1 = (b/(B+b))*100 //percentage error in %
23

```

```

24 //result
25 mprintf("correction factor when 0.707 pf lagging =
    %3.3f",c);
26 mprintf("\npercentage error =%3.2f percentage ",e);
27 mprintf("\ncorrection factor when 0.707 pf lagging
    = %3.3f",c1);
28 mprintf("\npercentage error =%3.1f percentage ",e1)

```

Scilab code Exa 7.3 Estimate the percentage error in the wattmeter

```

1 //


---


2 //chapter 7 example 3
3
4 clc;clear all;
5
6 //variable declaration
7 V = 240; //voltage in V
8 I = 8; //current in A
9 x = 0.1; //pf lagging
10 Rp = 8000; //resistance in
11 f = 50; //frequency in Hz
12 L = 63.6*10^-3 //inductance
13
14 //calculations
15 phi = acos(x);
16 phi1 =(phi*180)/%pi;
17 P = V*I*x; //load power
18 P1 = (V^2)/Rp; //power lost in the pressure coil
    circuit in watts
19 Pt = P+P1; //neglecting inductance of the
    voltage coil the reading of wattmeter would be in
    watts
20 Xp = 2*%pi*f*L; //reactance in

```

```

21 theta    = atan(Xp/Rp);
22 theta1   = (theta*180)/%pi;
23 A = cos(theta1);
24 B       =cos(phi1-theta1);
25 C      = cos(phi1);
26 w      = Pt*(A)*(B/C); //wattmeter reading
27 e      = ((w-P)/P)*100; //percentage error in %
28
29 //result
30 mprintf("phi value in textbook is taken wrong
          correct is 84 .16 but value is 84 .26 so
          textbook answer is coming wrong")
31 mprintf("\npercentage error in %3.2f percentage ",e)
    ;

```

Scilab code Exa 7.4 Calculate the percentage error in wattmeter reading

```

1 //


---


2 //chapter 7 example 4
3
4 clc;clear all;
5
6 //variable declaration
7 w  = 23; //wattmeter reading in watts
8 Rp = 2000; //resistance in
9 f  = 100; //frequency in Hz
10 L = 10*10^-3 //inductance
11 V = 240; //voltage in V
12 I = 4.5; //current in A
13
14 //calculations
15 Xp = 2*%pi*f*L; //reactance in
16 theta = atan(Xp/Rp);

```

```

17 theta1 =(theta*180)/(%pi)
18 //cos(phi)=P/V*I
19 //phi = acos(P/V*I)
20 //w = Pt*(cos(theta))*(cos(phi-theta))/cos(phi);
    //wattmeter reading
21 W1      = V*I;          //V*I in watts
22 //phi   = acos(P/W) = acos(P/1080)
23 //W     = P*cos(theta)*(cos(phi-theta))/cos(phi)
24 //W     =23 =P*cos(0.18)*cos((acos(P/1080))-0.18)/(P
    /V*I)
25 //let cos(acos(P/1080)-0.18) =A
26 //B = cos(0.18)
27 //W=23 = (P*B*A)/(P/(V*I))
28 // W= B*A*V*I
29 //A     = W/(B*V*I)
30 B      = cos((theta1*%pi)/180);
31 A      = w/(B*V*I);
32 //cos(acos(P/1080)-0.18) =A
33 //C =acos(P/1080) = acos(A)+0.18
34 A1     =(acos(A))*(180/%pi);
35 C     = A1+0.18
36 D     = cos(C*%pi/180)
37 P     =1080*D;
38 e     = ((w-P)/P)*100;          //percentage error in %
39
40 //result
41 mprintf("percentage error in %3.2f percentage ",e);

```

Scilab code Exa 7.5 Finding the error in wattmeter

```

1 //


---


2 //chapter 7 example 5
3 clc;clear all;

```

```

4
5 //variable declaration
6 f   = 50;           //frequency in Hz
7 L   = 5*10^-3      //inductance
8 V   = 100;         //voltage in V
9 I   = 10;          //current in A
10 R1  = 3000;        //resistance in
11
12 //calculations
13 x    = ((2*pi*f*L)/R1);           //tan(theta)
14 theta = atan(x); //the angle by which the current
    in pressure coil lags behind the voltage
15 //W = V*I*sin(90+theta) = V*I*cos(theta) = V*I*tan(
    theta)
16 //W=V*I*theta //since theta is small
17 W    = V*I*x; //reading of wattmeter in watt
18
19 //result
20 mprintf("error = %3.2 f watts",W);

```

Scilab code Exa 7.6 Find the actual reading reading on the wattmeter

```

1 //


---


2 //chapter 7 example 6
3 clc;clear all;
4
5 //variable declaration
6 RL  = 2; //resistance in
7 f    =50; //frequency in Hz
8 L    = 0.25; //inductance in H
9 V    = 200; //voltage in V
10 LP  = 5.6*10^-3; //inductance in H
11 RP  =1000;

```

```

12
13 //calculations
14 XL = 2*%pi*f*L; //load reactance in
15 ZL = RL+XL*i; //load impedance
16 IL = V/ZL; //load current in A
17 XLP = 2*%pi*f*LP; //reactance in
18 ZP = RP+XLP*i; //pressure coil circuit
    impedance in
19 IP = V/ZP; //pressure coil current in A
20 theta = (atan(imag(IP)/real(IP)))*180/%pi;
21 Ic = IL+IP;
22 Ic1 = sqrt(((imag(Ic))^2)+((real(Ic))^2))
23 phi = (atan(imag(Ic)/real(Ic)))*180/%pi;
24 A = (phi-theta);
25 x = cos((A*%pi)/180);
26 y =cos((theta*%pi)/180);
27 W = V*Ic1*y*x; //actual reading of wattmeter in
    watts
28
29 //result
30 mprintf("actual reading of wattmeter = %3.4f watts"
    ,W);

```

Scilab code Exa 7.7 Calculate the percentage errors

```

1 //


---


2 //chapter 7 example 7
3 clc;clear all;
4
5 //variable declaration
6 V = 250; //load voltage in V
7 I = 12; //load current in A
8 Rc = 0.1; //resistance in

```

```

 9 Rp = 6500;           //resistance in
10 x  = 1;             //pf cos(phi)
11 y  = 0.4;          //pf cos(phi)
12
13 //calculations
14 P   = V*I*x;        //power input to the apparatus
    in W
15 PL  = (I^2)*Rc;     //power lost in current coil in
    W
16 e   = (PL/P)*100;   //percentage error in %
17 Pc  = (V^2)/Rp;    //power lost in presuure coil in W
18 e   = (Pc/P)*100;   //percentage error in %
19 P1  = V*I*y;        //power input to the apparatus
    in W
20 PL1 = (I^2)*Rc;     //power lost in current coil in
    W
21 e1  = (PL1/P1)*100; //percentage error in %
22 Pc1 = (V^2)/Rp;    //power lost in presuure coil in W
23 e1  = (Pc1/P1)*100; //percentage error in %
24
25 //result
26 mprintf("percentage error when pf 1 lagging %3.2f
    percentage",e);
27 mprintf("\npercentage error when pf 0.4 lagging %3
    .2f percentage",e1);

```

Scilab code Exa 7.8 Calculate the actual power and current

```

1 //


---


2 //Chapter 7 Example 8
3
4
5 clc;

```

```

6 clear all;
7
8 //variable declaration
9 theta1      =1;           //pressure coil phase angle
   in
10 theta2      =2;           //pressure coil phase angle
   in
11 P1          = 700;        //wattmeter reading in W
12 P2          = 620;        //wattmeter reading in W
13 V           = 240;        //voltage in V
14
15
16 //calculations
17 x           = P1/P2;
18 //P1        =P*cos(theta2)*cos(phi-theta2)/cos(phi)
19 //P2        = P*cos(theta1)*cos(phi-theta1)/cos(phi)
   )
20 //P1/P2     = cos(theta2)*cos(phi-theta2)/cos(phi)/
   cos(theta1)*cos(phi-theta1)/cos(phi)
21 //x         = cos(theta2)*cos(phi-theta2)/cos(phi)/
   cos(theta1)*cos(phi-theta1)/cos(phi)
22 //x         = (cos(theta2)/cos(theta1))*(cos(phi-
   theta2)/cos(phi-theta1))
23 //x         = y*(cos(phi-theta2)/cos(phi-theta1))
24 //(cos(phi-theta2)/cos(phi-theta1)) = x/y
25 y           = (cos(theta2*%pi/180)/cos(theta1*%pi
   /180));
26 z           = x/y;
27 //(cos(phi-theta2)/cos(phi-theta1)) = ((cos(thet2*
   %pi/180))*cos(phi))+(sin(thet2*%pi/180))*sin(phi)
   )/((cos(theta1*%pi/180))*cos(phi))+(sin(thet1*%pi
   /180))*sin(phi))
28 //z         = ((cos(thet2*%pi/180))*cos(phi))+(sin(thet2
   *%pi/180))*sin(phi))/((cos(theta1*%pi/180))*cos(
   phi))+(sin(thet1*%pi/180))*sin(phi))
29 t           = ((z*cos(theta1*%pi/180))-(cos(theta2*
   %pi/180)))/((sin(theta2*%pi/180))-(z*sin(theta1*
   %pi/180)));

```



```

30 phi          = (atan(t))*180/%pi;
31 pf           = cos(phi*%pi/180);
32 C            = (phi-theta2)
33 c            = cos(C*%pi/180);
34 a            = (cos(theta2*%pi/180));
35 b            = a*c;
36 B            = P1*pf;
37 P            = B/b;
38 I            = P/(V*pf);
39
40 //result
41 mprintf(" actual power = %3.3 f W",P);
42 mprintf("\ncurrent drawn = %3.2 f A",I);

```

Scilab code Exa 7.9 Estimate the torque

```

1 //


---


2 //chapter 7 example 9
3 clc;clear all;
4
5 //variable declaration
6 Np          = 500;           //number of turns on
   moving coil
7 Ip          = 0.05;         //current through moving
   coil in A
8 B           = 0.012;        // flux density in
   the air gap in T
9 d           = 0.03;         //diameter in m
10 theta1     = 30;
11 theta2     = 90;
12 x          = 0.866;        //power factor
   cos(phi)
13

```

```

14 //calculations
15
16 A      = (%pi/4)*(d^2);           //area  of x-
      section of moving coilin m^2
17 phimax      = B*A;           //maximum flux
      through moving coil in Wb
18 //Mmax      = (phimax*Np)/Ic
19 //Mmax*Ic    = X      = phimax*Np
20 X          = (phimax*Np);
21 //T          = Ip*Ic*Mmax*cos(phi)*sin(theta)
22 //T          = Ip*Ic*(X/Ic)*cos(phi)*sin(theta)
23 //T          = Ip*(X)*cos(phi)*sin(theta)
24 T1          = Ip*X*x*sin(theta1*%pi/180);
25 T2          = Ip*X*x*sin(theta2*%pi/180);
26
27 //result
28 mprintf("torque in when 30  = %3.4e  N-m",T1);
29 mprintf("\ntorque in when 90  = %3.4e  N-m",T2);

```

Scilab code Exa 7.10 Calculate the power factor of inductive load

```

1 //


---


2 //chapter 7 example 10
3
4 clc;clear all;
5
6 //variable declaration
7 V1 = 200;           //voltage across an inductive load
      in volts
8 V2 = 180;           //voltage across an nono- inductive
      resistor in volts
9 V3 = 300;           //voltage across the two in series
      in volts

```

```

10
11 //calculations
12 x = ((V3^2)-(V1^2)-(V2^2))/(2*V1*V2); //cos(phi)
13
14 //result
15 mprintf("power factor cos (phi) = %3.3f lagging",x);

```

Scilab code Exa 7.11 Calculate the power absorbed by the load and load impedance a

```

1 //


---


2 //chapter 7 example 11
3
4 clc;clear all;
5
6 //variable declaration
7 I1 = 2.5; //current across an inductive load
   in A
8 I2 = 2.4; //current across an non- inductive
   resistor in A
9 I3 = 4.5; //current across the two in series
   in A
10 V = 250; //supply voltage in V
11
12
13 //calculations
14 R = V/I2; // non- inductive resistance in
15 P = ((I3^2)-(I1^2)-(I2^2))*(R/2); //power absorbed
   by the load in watts
16 Z = V/I1; //load impedance in
17 x = ((I3^2)-(I1^2)-(I2^2))/(2*I1*I2); //cos(phi)
18
19 //result
20 mprintf("power absorbed by the load = %3.2f watts",P

```

```

    );
21 mprintf("\nload impedance = %3.2f    ",Z);
22 mprintf("\npower factor cos (phi) = %3.4f lagging",x
    );

```

Scilab code Exa 7.12 Write the suitable transformation ratio7

```

1 //


---


2 //chapter 7 example 12
3 clc;clear all;
4
5 //variable declaration
6 V1 = 6600; //primary voltage in V
7 V2 = 110; //secondary voltage in V
8 I1 = 50; //primary current in A
9 I2 = 5; //secondary voltage in A
10
11 //calculations
12 r = V1/V2; //hence transformation ratio of
    PT
13 r1 = I1/I2; //transformation ratio of CT
14
15 //result
16 mprintf("transformation ratio of CT = %3.2f ",r1);

```

Scilab code Exa 7.13 Calculate the new multiplying factor of wattmeter

```

1 //


---


2 //chapter 7 example 13

```

```

3  clc;clear all;
4
5  //variable declaration
6  m   = 10;           //wattmeter multiplying factor
7
8  //calculations
9  x   = 100/5;        //CT ratio
10 y   = 1000/100;    //PT ratio
11 W   = x*y*m;        //new multiplying factor of
    wattmeter
12
13 //result
14 mprintf("new multiplying factor of wattmeter = %3.2 f
    ",W);

```

Scilab code Exa 7.14 Calculate the percentage error

```

1  //


---


2  //chapter 7 example 14
3  clc;
4  clear all;
5
6  //variable declaration
7
8  V   = 6000;         //load voltage in V
9  I   = 100;          //load current in A
10 p   = 0.5;          //power factor cos(phi) lagging
11 theta = 0;          //since wattmeter reads
    correctly
12 x1   = 20;           // current transformers
    nominal ratio
13 x2   = 60;           // potenetial transformers
    nominal ratio

```

```

14 e1      =-0.005;           // ration error
15 e2      = 0.01;           // ratio error
16
17 //calculations
18 P       = V*I*p;           //actual power consumed in W
19 phi     =acos(p);
20 phi1    = (phi*180)/%pi;
21 d       = -1;             //phase angle in
22 b       = 2;             //phase angle in
23 g       = phi1+d-theta1-b; //phase angle in
24 theta1  =theta*180/%pi
25 g1      = g*180/%pi;
26 A       =cos(phi1)
27 K       = (cos(phi1*%pi/180))/((cos(theta1*%pi/180))*
cos(g*%pi/180));
28 CT      = x1*(1+e1);      //actual
transformation ratio of CT
29 PT      = x2*(1+e2);      //actual
transformation ratio of PT
30 P1      = P/(K*CT*PT);    //power indicated by
wattmeter in kW
31 T       = P/(x1*x2);      //true reading of
wattmeter in kW
32 e       = ((P1-T)/T)*100; //percentage
error in %
33 //result
34 mprintf("phase angle between the currents in CC and
PC of wattmeter %3.2f ",K);
35 mprintf("\npercentage error = %3.0f percentage ",e);

```

Scilab code Exa 7.15 Calculate the input power and power factort

```
1 //
```

```

2 //chapter 7 example 15
3 clc;
4 clear all;
5
6 //variable declaration
7 W1 = 300; //wattmeter reading in kW
8 W2 = 100; //wattmeter reading in kW
9
10 //calculations
11 P = W1+W2; //input power in kW
12 phi = atan(((W1-W2)/(W1+W2))*sqrt(3)); //phase
    angle in radians
13 phi1 = (phi*180)/%pi;
14 pf = cos((phi1*%pi)/180); //power factor
    lagging
15
16
17 //result
18 mprintf("input power = %3.2 f kW",P);
19 mprintf("power factor = %3.3 f lagging",pf);

```

Scilab code Exa 7.16 Calculate the power and power factor of the load

```

1 //


---




---


2 //chapter 7 example 16
3
4 clc;clear all;
5
6 //variable declaration
7 W1 = 20; //wattmeter reading in kW
8 W2 = -5; //wattmeter reading in kW
9
10 //calculations

```

```

11 P    = W1+W2;           //input power in kW
12 phi  = atan(((W1-W2)/(W1+W2))*sqrt(3)); //phase
      angle in
13 pf   =cos(phi);       //power factor lagging
14
15 //result
16 mprintf("input power = %3.2f kW",P);
17 mprintf("\npower factor = %3.4f lagging",pf);

```

Scilab code Exa 7.17 Find the reading of the each instrument

```

1 //


---


2 //chapter 7 example 17
3
4 clc;clear all;
5
6 //variable declaration
7 P    = 30000; //total power in kW
8 pf   = 0.4; //power factor assuming lagging
9
10 //calculations
11 phi  = acos(pf); //phase angle in radians
12 phi1 = (phi*180)/%pi;
13 y    = sqrt(3);
14 z    = y*pf;
15 x    = P/(y*pf); //VL*IL in VA
16
17 //W = VL*IL*cos(30-phi)
18 //VL*IL = x;
19 W1   = x*cos((30*%pi/180)-(phi1*%pi/180)); //
      reading of wattermeter in W
20 W2   = x*cos((30*%pi/180)+(phi1*%pi/180)); //
      reading of wattermeter in W

```



```

21
22 //result
23 mprintf("reading of wattermeter %3.2 f W %3.0 f W",W1,
    W2);
24 mprintf("\nNote:x value is taken approximate value ,
    so the w1 and w2 differing ")
25 mprintf("\nif power factor is leading the readings
    of wattmeters interchange ");

```

Scilab code Exa 7.18 Find the reading OF TWO wattmeters

```

1 //


---


2 //chapter 7 example 18
3
4
5 clc;clear all;
6
7 //variable declaration
8 VL =400; //voltage in V
9 IL = 10; //current in A
10 //r = W1/W2
11 //tan(phi) = sqrt(3)*((W1-W2)/(W1+W2))
12 //tan(phi) = sqrt(3)*((1-(W2/W1))/(1+(W2/W1)))
13 //tan(phi) = sqrt(3)*((1-r)/(1+r))
14 //cos(phi) = 1/sec(phi) = 1/sqrt(1+(tan(phi)
    ^2) = 1/sqrt(1+(3*((1-r)/(1+r))^2)
15 r = 0.5;
16 z = ((1-r)/(1+r))^2;
17 pf = 1/sqrt(1+(3*z));
18 phi = (acos(pf)*180/%pi);
19 W1 = VL*IL*cos((30*%pi/180)-(phi*%pi/180));
    //wattmeter reading in W
20 W2 = VL*IL*cos((30*%pi/180)+(phi*%pi/180));

```

```

    //wattmeter reading in W
21
22 //result
23 mprintf("wattmeter reading = %3.2 f W", W1);
24 mprintf("\nwattmeter reading = %3.2 f W",W2);

```

Scilab code Exa 7.19 Determine the values of Rand L connected in the phase

```

1 //


---


2 //chapter 7 example 19
3
4 clc;
5 clear all;
6
7 //variable declaration
8 W1 = 3000; //wattmeter reading in W
9 W2 = 1000; //wattmeter reading in W
10 f = 50; //frequency in HZ
11 V = 400; //voltage in V
12
13
14 //calculations
15 VP = V/sqrt(3); //voltage in V
16 P = W1+W2; //input
    power in kW
17 phi = atan(((W1-W2)/(W1+W2))*sqrt(3));
    //phase angle in radians
18 phi1 = phi*180/%pi;
    //phase angle in degrees
19 pf = cos(phi1*%pi/180);
    //power factor lagging
20 IL = P/((sqrt(3))*V*pf);

```

```

//line current in A
21 ZP      =VP/IL;
    //impedance of the circuit per phase in
22 R      = ZP*pf;           //resistance
    per phase
23 XL      = sqrt((ZP^2)-(R^2));           //
    reactance per phase in
24 L      = XL/(2*pi*f);           //
    inductance per phase in H
25
26 //result
27 mprintf("resistance per phase = %3.2f ",R);
28 mprintf("\ninductance per phase in = %3.3f H",L);

```

Scilab code Exa 7.20 Find the wattage shown by three wattmeters and power taken by

```

1 //


---


2 //chapter 7 example 20
3
4 clc;
5 clear all;
6
7 //variable declaration
8 IPR = 8;    //current in line R in A
9 IPY = 10;   //current in line Y in A
10 IPB = 6;   //current in line B in A
11 VP = 120;  //voltage in V
12 pf = 1;    //power factor
13
14 //calculations
15 W1 = VP*IPR*pf; //wattage shown by wattmeter
    having current coil in line R in watts
16 W2 = VP*IPY*pf; //wattage shown by wattmeter

```

```

    having current coil in line Y in watts
17 W3 = VP*IPB*pf; //wattage shown by wattmeter
    having current coil in line B in watts
18 p = W1+W2+W3; //power taken by lighting load in
    watts
19
20 //result
21 mprintf("wattage shown by wattmeter having current
    coil in line R = %3.2f watts",W1);
22 mprintf("\nwattage shown by wattmeter having current
    coil in line Y = %3.2f watts",W2);
23 mprintf("\nwattage shown by wattmeter having current
    coil in line B = %3.2f watts",W3);
24 mprintf("\npower taken by lighting load = %3.2f
    watts",p);

```

Scilab code Exa 7.21 Find the current and reading of two wattmeters connected to m

```

1 //


---




---


2 //chapter 7 example 21
3
4 clc;
5 clear all;
6
7 //variable declaration
8 R = 10; //resistance in
9 XL = 10; //reactance in
10 VL = 440; //load voltage in V
11
12 //calculations
13 Z = sqrt((R^2)+(XL^2)); //impedance of each
    choking coil in
14 VP = VL/sqrt(3); //phase voltage in V

```

```

15 IP = VP/Z;      //phase current in A
16 IL = IP;       //line current in A
17 phi = atan(XL/R); //phase angle in
18 phi1 = phi*180/%pi;
19
20 W1 = VL*IL*cos((30*%pi/180)-(phi1*%pi/180));
    //wattmeter reading in W
21 W2 = VL*IL*cos((30*%pi/180)+(phi1*%pi/180));
    //wattmeter reading in W
22
23 //result
24 mprintf("line current = %3.2 f A",IL);
25 mprintf("\nwattmeter reading = %3.2 f W",W1);
26 mprintf("\nwattmeter reading = %3.2 f W",W2);

```

Scilab code Exa 7.22 Find the power factor of the system and the value of capacitance

```

1 //


---


2 //chapter 7 example 22
3
4 clc;
5 clear all;
6
7 //variable declaration
8 W1 = 5000;      //wattmeter reading in W
9 W2 = -1000;    //wattmeter reading in W
10 VL = 440;     //load voltage in V
11 f = 50;      //frequency in Hz
12 VP = 440;
13
14 //calculations
15 P = W1+W2;    //total power in the load
    circuit in W

```

```

16 phi = atan(((W1-W2)/(W1+W2))*sqrt(3)); //phase
    angle in
17 phi1      = phi*180/%pi;
18 pf  = cos(phi); //power factor
19 IP  = P/((sqrt(3)*VL*pf)); //load current per phase
    in A
20 IP1      = IP/sqrt(3);
21 ZP  = VP/IP1; //load impedance per phase
22 RP  = ZP*pf; //load resistance per phase
    in
23 XP  =ZP*sin(phi); //load reactance per phase
    in
24 pf1 = 0.5; //power factor
25 phi2      = (acos(pf1))*180/%pi;
26 //reading of wattmeter will be zero
27 XP1 = RP*tan((phi2)*%pi/180); //reactnace in
    circuit per phase in
28 XC  =XP-XP1; //value of capacitive
    reactance in troduced in each phase in
29 C   = 1/(2*%pi*f*XC); //value of capacitive
    reactance introduced in each phase of delta
    connected in uF
30
31 //result
32 mprintf("value of capacitive reactance introduced in
    each phase of delta connected = %3.0f uF", (C
    *10^6));

```

Scilab code Exa 7.23 Find the line currents and reading on wattmeters whose current

```
1 //
```

```
2 //chapter 7 example 23
```

```
3
```

```

4  clc;
5  clear all;
6
7  //variable declaration
8  VAB1      = 400+0*%i;      //voltage in V
9  VBC1      = -200-346.41*%i;    //voltage in V
10 VCA1      = -200+346.41*%i;   //voltage in V
11 VAB       =400;
12 VBC       = 400;
13 VCA       = 400;
14 TVAB      = 0;
15 TVBC      = -120;
16 TVCA      =120;
17 PAB       = 20000;          //Wwattmetr readig VA
18 PBC       = 30000;          //Wwattmetr readig VA
19 PCA       = 20000;          //Wwattmetr readig VA
20
21
22 //calculations
23 IAB       = PAB/VAB;        //magnitude of IABC
24 IBC       = PBC/VAB;        //magnitude of IABC
25 ICA       = PCA/VAB;        //magnitude of IABC
26 c1        = 0;
27 c2        = (acos(0.8)*180/%pi);
28 c3        = -(acos(0.6)*180/%pi);
29 angle1    = c1-TVAB;
30 angle2    = c2-TVBC;
31 angle3    = c3-TVCA;
32 IAB1      = (IAB*cos(angle1))+(IAB*sin(angle1))*
    %i;
33 IBC1      = (IBC*cos(angle2*%pi/180))+(IBC*sin(-
    angle2*%pi/180))*%i;
34 ICA1      = (ICA*cos(angle3*%pi/180))+(ICA*sin(-
    angle3*%pi/180))*%i;
35 IA       = IAB1-ICA1;
36 IB       = IBC1-IAB1;
37 IC       = ICA1-IBC1;
38 W1       = -(VBC1)*IA;

```

```

39 W2          = VCA1*IB;
40
41
42
43 //result
44 mprintf("line current IA      = %3.2 f %3.2 f *j A",real
         (IA),imag(IA));
45 mprintf("\nline current IA      = %3.2 f%3.2 f*j A",real
         (IB),imag(IB));
46 mprintf("\nline current IA      = %3.2 f + %3.2 f*j A",
         real(IC),imag(IC));
47 mprintf("\nreading of wattmeter W1      = %3.2 f W",W1
         );
48 mprintf("\nreading of wattmeter W2      = %3.2 f W",W2
         );

```

Scilab code Exa 7.24 Find the power of the network

```

1 //


---




---


2 //chapter 7 example 24
3 clc;
4 clear all;
5
6 //variable declaration
7 W1 = 2000; //reading of wattmeter in watts
8 W2 = 1000; //reading of wattmeter in watts
9
10 //calculations
11 Q = sqrt(3)*(W1-W2); //reactive power of the
    network in V A
12 P = Q/(sqrt(3)); //wattmeter reading when
    current coil is connected in one phase and the
    potential coil across the two phases in VA

```



```

13
14 //result
15 mprintf("Wattmeter reading = %3.2f reactive volt
    amperes",P);

```

Scilab code Exa 7.25 Calculate the wattmeter reading

```

1 //


---


2 //chapter 7 example 25
3 clc;
4 clear all;
5
6 //variable declaration
7 VL = 415; //voltage in V
8 IL = 20; //current in A
9 pf = 0.8; //phase angle
10
11 //calculations
12 phi =acos(pf) //phase angle in
13 phi1 = (phi*180)/%pi
14 x = cos((30-phi1)*%pi/180)
15 W1 = VL*IL*x //wattmeter reading in W
16 W2 = VL*IL*cos((30+phi1)*%pi/180) //wattmeter
    reading in W
17 //total KVAR = sqrt(3)*(W1-W2)
18 // W = totalKVAR/sqrt(3)
19 //W = (sqrt(3)*(W1-W2))/sqrt(3); //wattmeter
    reading
20 W = W1-W2 //wattmeter reading
21
22 //result
23 mprintf("reading on wattmeter 1 = %3.2d W",W1);
24 mprintf("\nreading on wattmeter 2 = %3.2d W",W2);

```

```
25 mprintf("\\nreading on wattmeter = %3.2 f W",w);
```

Chapter 8

Measurement of energy and energy meters

Scilab code Exa 8.1 Determine the meter constant in revolution

```
1 //  


---

  
2 //chapter 8 example 1  
3  
4 clc;clear all;  
5  
6 //variable declaration  
7 P      = 360;      //power in W  
8 t      = 100;     //time in seconds  
9 n      = 10;      //revolutions  
10  
11 //calculations  
12 E      = (P*(t/(3600)))/(1000); //energy  
        consumed in kWh  
13 M      = n/(E);   //meter constant in  
        revolutions/KWh  
14  
15 //result
```

```
16 mprintf("meter constant in revolutions/KWh = %3.2 f "
    ,M);
```

Scilab code Exa 8.2 Calculate the power

```
1 //


---


2 //chapter 8 example 2
3
4
5 clc;clear all;
6
7 //variable declaration
8 V      = 220;      //voltage in V
9 I      = 5;        //current in A
10 Rp    = 8800;     //resistance of pressure in
11 V1     = 6;       //voltage excited in V
12
13 //calculations
14 P1     = V*I;     //power consumed in
    current coil circuit in W
15 P2     = (V^2)/(Rp); //power consumed
    in pressure coil circuit in W
16 P      = P1+P2;  //total power
    consumed in W
17 P11    = V1*I;   //power consumed in
    current coil circuit in W
18 P21    = (V1^2)/(Rp); //power consumed
    in pressure coil circuit in W
19 PP     = P11+P21; //total power
    consumed in W
20
21 //result
22 mprintf("total power consumed for direct load
```

```

    arrangement = %3.2f W",P);
23 mprintf(" \ntotal power consumed for phantom loading
    with current circuit = %3.1f W",PP);

```

Scilab code Exa 8.3 Calculate the error and state whether the meter is fast or slow

```

1 //


---


2 //chapter 8 example 3
3
4 clc;clear all;
5
6 //variable declaration
7 T      = 0.5;           //time in hours
8 V      = 220;          //voltage in V
9 I      = 5;            //current in A
10 P     = 525;           //consumption registered in
    Wh
11 P1    =0.525;          //consumption registered in
    kWh
12
13 //calculations
14
15 E     = ((V*I)/(1000))*T; //energy consumed in
    kWh
16 e     = ((P1-E)/(E))*100; //percentage error
    in %
17
18 //result
19 mprintf(" percentage error = %3.2f percentage(slow)
    ",e);

```

Scilab code Exa 8.4 Calculate the full load speed of the meter

```
1 //


---



---


2 //chapter 8 example 4
3
4
5 clc;clear all;
6
7 //variable declaration
8 M1      = 5;      //meter constant in A-s/rev
9 V       = 250;   //voltage in V
10 t      = 60;    //time in minute
11
12 //calculations
13 M2      = M1*V;  //meter constant in W-s/rev with
    rated voltage of 250V
14 M3      = M2/(1000*3600); //meter constant in
    kWh/rev
15 M       = 1/(M3); //meter constant in rev/
    kWh
16 E       = (M2/(t*1000)); //energy consumed in
    1 minute at full-load
17 S       = M*E;   //full-load speed in rpm
18
19 //result
20 mprintf("meter constant in revolutions per kWh = %3
    .2d",M);
21 mprintf("full-load speed = %3.2d rpm",S);
```

Scilab code Exa 8.5 Determine the load in kWh

```
1 //
```

```

2 //chapter 8 example 5
3
4 clc;clear all;
5
6 //variable declaration
7 n      = 15;          //number of revolutions made
8 M      = 750;        //meter constant in revolutions
                      per kWh
9 T      = 30;         //time in seconds
10
11 //calculations
12 E      = n/(M);      //Energy consumed in 30 seconds
13 L      = (E*3600)/T; //load in kW
14
15 //result
16 mprintf("Energy consumed in 30 seconds = %3.2 f kWh",
          E);
17 mprintf("\nLoad = %3.2 f kW",L);

```

Scilab code Exa 8.6 Find out the percentage error

```

1 //


---


2 //chapter 8 example 6
3
4
5 clc;clear all;
6
7 //variable declaration
8 M      = 500;        //meter constant in revolutions
                      per kWh
9 n      = 40;         //number of revolutions made
10 T1     = 58.1;      //time in seconds

```

```

11 P      = 5;      //power in kW
12
13 //calculations
14 x      =P*T1;
15 E      =(x/3600);      //Energy consumed in 58.1
      seconds
16 E1     = n/(M);      //energy consumption
      registeredin kWh
17 e      = ((E1-E)/E)*100;      //percentage error in %
18
19 //result
20 mprintf("percentage error = %3.2f percentage",e);

```

Scilab code Exa 8.7 Calculate the percentage error

```

1 //


---


2 //chapter 8 example 7
3 clc;clear all;
4
5 //variable declaration
6 V      = 230;      //voltage in V
7 I      = 4.4;      //current in A
8 T      = 3;      //time in minutes
9 x      =1;      //cos(0)=1
10 n     = 10;      //number of revolutions made
11 M     = 200;      //meter constant in revolutions
      per kWh
12
13 //calculations
14 E      = (V*I*(T/(60))*x)/(1000);      //Energy
      consumed i3 minutes
15 E1     = n/(M);      //energy consumption
      registeredin kWh

```



```

16 e      = ((E1-E)/(E))*100;          //percentage error
    in %
17
18 //result
19 mprintf("percentage error = %3.3f percentage",e);

```

Scilab code Exa 8.8 Calculate how many units are recorded as error

```

1 //


---


2 //chapter 8 example 8
3
4 clc;clear all;
5
6 //variable declaration
7 L      = 1;          //Load in kW
8 S      = 10.2;      //speed of the disc in rpm
9 T1     = 12;        //time in hours
10 M     = 600;       //meter constant in revolutions per
    kWh
11
12 //calculations
13 T2     = T1*60;    //time in minutes
14 E      = L*T1;    //actual energy consumed in 12 hours
    in kWh
15 N      = S*T2;    //Revolutions made by the disc in 12
    hours
16 E1     = N/(M);   //Energy consumption recorded by the
    meter
17 e      = E1-E;    //error in kWh
18
19 //result
20 mprintf("error = %3.2f kWh more",e);

```

Scilab code Exa 8.9 Determine the speed of the disc

```
1 //


---


2 //chapter 8 example 9
3
4 clc;clear all;
5
6 //variable declaration
7
8 V      = 240; //voltage in V
9 I      = 8;   //current in A
10 T     = 1;   //time in minutes
11 x     =0.6;  //power factor
12 M     = 600; //meter constant in revolutions per
    kWh
13
14 //calculations
15 E     = (V*I*(T/(60))*x)/(1000); //Energy
    consumed 1 minute
16 S     = E*M; //speed of the disc in
    rev/minute
17
18 //result
19 mprintf("speed of the disc = %3.2f rev/minute",S);
```

Scilab code Exa 8.10 Find out the error in registration and error in rpm of the me

```
1 //
```

```

2 //chapter 8 example 10
3
4 clc;clear all;
5
6 //variable declaration
7 V      = 230; //voltage in V
8 I      = 10; //current in A
9 T      = 30; //time in minutes
10 x     =0.8; //power factor
11 n     = 890; //number of revolutions made
12 M     = 1200; //meter constant in revolutions
    per kWh
13 E     = 58.25; //dial reading at the end of
    test
14 E1    = 57.35; //dial reading at the start
    of test
15
16 //calculations
17 Ea    = (V*I*(T/(60))*x)/(1000); //Energy
    consumed 1 minute
18 Em    = E-E1; //energy consumption
    recorded by the meter in kWh
19 e     = Em-Ea; //error in registration
    in kWh
20 N     = M*Em; //actual revolutions
    required to be made by the meter for an energy
    consumption of 0.90kWh
21 e     = (n-N)/(T); //error in rpm
22
23 //result
24 mprintf("error = %3.2 f rpm",e);

```

Scilab code Exa 8.11 Calculate the power factor

```
1 //
```

```

2 //chapter 8 example 11
3
4 clc;clear all;
5
6 //variable declaration
7 V = 230;           //voltage in volts
8 I = 4;            //current in A
9 I1 = 5;           //current in A
10 cosphi = 1;       //power factor
11 h = 6;           //hours
12 R = 2208;        //revolutios made by meter
13 R1 = 1472;       //revolutios made by meter
14 E1 = 400;        //energy consumption
15 h1 = 4;
16
17 //calculations
18 E = (V*I*cosphi*h)/(1000); //energy
    consumption in kWh
19 M = R/(E);        //meter constant in
    rev/kWh
20 cosphi2 = (R1/(E1)*(1000/(V*I1*h1))); //power
    factor of the load is cosphi2 for second
    measuremnet
21
22 //result
23 mprintf("meter constant = %3.2f revolutions/kWhr",M)
    ;
24 mprintf("\npower factor of the load is cosphi2 for
    second measuremnet = %3.2f",cosphi2);

```

Chapter 9

Measurement of Speed and Frequency and Power factor

Scilab code Exa 9.1 Determine the frequency of output pulses

```
1 //  


---

  
2 //chapter 9 example 1  
3  
4 clc;clear all;  
5  
6 //variable declaration  
7 N = 1500; //speed of shaft in rpm  
8 T =120; //number of teeth on rotator  
9  
10 //calculatins  
11 f = (N/60)*T; //frequency of output pulses in  
    pulses per second  
12  
13 //result  
14 mprintf("frequency of output pulses in pulses = %3.2  
    f pulses per second",f);
```

Scilab code Exa 9.2 Determine the speed of the shaft

```
1 //


---



---


2 //chapter 9 example 2
3
4 clc;clear all;
5
6 //variable declaration
7 R = 4; //digital counter reading
8 G = 0.001; //gating period in s
9 T = 150; //number of teeth on rotor
10
11 //calculations
12 f = R/(G); //number of pulses per second
13 N = (f/T)*60; //rotational speed in rpm
14
15 //result
16 mprintf("rotational speed = %3.2f rpm",N);
```

Scilab code Exa 9.3 Determine the speed of the shaft

```
1 //


---



---


2 //chapter 9 example 3
3
4 clc;clear all;
5
6 //variable declaration
```

```

7 H    = 120;    //number of holes on the rotating
    disc
8 f    = 5400;   //frequency of output pulses in per
    second
9
10 //calculations
11 N    = (f/(H))*60;    //rotational speed in rpm
12
13 //result
14 mprintf("rotational speed = %3.2f rpm",N);

```

Scilab code Exa 9.4 Find the frequency

```

1 //


---


2 //chapter 9 example 4
3 clc;
4 clear all;
5
6 //variable declaration
7 f1 = 60;    //frequency in Hz
8 f2 = 50;    //frequency in Hz
9 C1 = 10^-6; //inductance of circuit
10 R1 = 100;  //resistance in
11 C2 = 1.5*10^-6; //capacitance
12
13 //calculations
14 L1 = 1/(4*((%pi)^2)*((f1)^2)*C1); //inductance of
    circuit in H
15 w = 2*%pi*f2;
16 Z1 = R1+(%i)*((w*L1)-(1/(w*C1))); //impedance
    of circuit at 50 Hz
17 //Z2 = R1+(%i)*((w*L2)-(1/(w*C2))); //
    impedance of circuit at 50 Hz

```

```
18 //real(Z2)      = real(Z1)
19 //((w*L2)-(1/(w*C2))) = real(Z1)=963
20 x              =abs((w*L1)-(1/(w*C1)))
21 y              = 1/(w*C2);
22 L2             =(x+y)/w;
23 z              = sqrt(1/(L2*C2));
24 f2  = (1/(2*pi))*(z);
25
26 //result
27 mprintf("resonant frequency of circuit = %3.1f  Hz",
          f2);
```

Chapter 10

Measurement of Resistance

Scilab code Exa 10.1 Calculate the apparent resistance and actual resistance and t

```
1 //


---


2 //chapter 10 example 1
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 V = 100; //voltmeter reading in V
10 I = 0.005; //ammeter reading in A
11 S = 1000; //sensitivity of voltmeter in
    per volt
12 v = 150; //voltmeter range in V
13
14 //calculations
15 Rv = S*v; //voltmeter resistance in
16 Rm = V/I; //apparent value of unknown
    resistor in
17 y = V/(I*Rv);
```

```

18 x      = I*(1-y);
19 Rx     = V/x;           //actual value of
    unknown resistor in
20 er     = ((Rm-Rx)/Rx)*100; //error due
    to loading effect of voltmeter in %
21
22 //result
23 mprintf("apparent value of unknown resistor = %3.2f
    ",Rm);
24 mprintf("\nactual value of unknown resistor = %3.2f
    ",Rx);
25 mprintf("\nerror due to loading effect of voltmeter
    = %3.2f percentage",er);

```

Scilab code Exa 10.2 Determine the resulting error

```

1 //


---


2 //chapter 10 example 2
3
4
5 clc;clear all;
6
7 //variable declaration
8 RA     = 2.5;           //resistance of ammeter
9 RV     = 6000;         //resistance of voltmeter
10 V      = 38.4;         //voltage in V
11 I      = 0.4;          //current in A
12
13 //calculations
14 Rx     = sqrt(RA*RV); //value of unknown
    resistance in
15 Rm     = V/I;          //measured value of unknown
    resistance in

```

```

16 Rx1          = V/(I*(1-(V/(I*RV))));      //true value
    of unknown resistance in
17 EA          = (1/2)*(1/100)*1;          //error on
    ammeter reading in A
18 EV          = (1/2)*(50/100);          //error on
    voltmeter reading in V
19 PEA         = (EA/I)*100;              //percentage
    error at 0.4 A reading in %
20 PEV         = (EV/V)*100;              //percentage
    error at 38.4 A reading in %
21 E           = sqrt((PEA^2)+(PEV^2));    //error
    due to ammeter and voltmeter in %
22 AE         = (E/100)*Rx1;              //absolute error
    due to ammeter and voltmeter in
23 R1         = Rx1+AE;                   //resistance in
24 R2         = Rx1-AE;                   //resistance in

25
26 //result
27 mprintf("resistance is specified as %3.3f and %3.3f
    ",R1,R2);

```

Scilab code Exa 10.3 Determine the value of unknown resistance

```

1 //


---


2 //chapter 10 example 3
3
4 clc;
5 clear all;
6
7
8 //variable declaration

```

```

 9 V    = 120;           //voltage in V
10 I    = 8;            //current in A
11 RA   = 0.3;          //resistance in
12 AR   = 0.01;         //maximum reading of ammeter in A
13 VR   = 0.1;          //maximum reading of voltmeter in V
14 AR1  = 10;           //ammeter rane 0–10 A
15 AV1  = 150;          //voltmeter range in 0–150 V
16 EA   = 0.25;         //constructional error of ammeter in
    %
17 EV   = 0.5;          //constructional error of voltmeter
    in %
18
19
20 //calculations
21 Rm    = V/I;          //measured value of unknown
    resistance in
22 Rx    = Rm-RA;        //true value of unknown
    resistance in
23 EA1   = (AR/AR1)*100; //reading error of
    ammeter in %
24 EV1   = (VR/AV1)*100; //reading of voltmeter in %
25 dI    = EA+EA1;      //error in ammeter reading
    in %
26 dv    = EV+EV1;      //error in voltmeter reading
    in %
27 d     =dI+dv;        //total error in % ranging – to
    +
28 R1    = Rx+d;        //Value of Rx is specified as
29 R2    = Rx-d;        //Value of Rx is specified as
30
31 //result
32 mprintf(" Value of Rx is specified = %3.3f,%3.3f  ",
    R1,R2);

```

Scilab code Exa 10.4 Determine the value of resistor under test

```

1 //


---


2 //chapter 10 example 4
3 clc;
4 clear all;
5
6 //variable declaration
7 S = 0.02; //resistance of standard resistor in
8 Vs = 0.98; //voltage drop across standard
  resistor in V
9 Vx = 0.735; //voltage drop across resistor
  under test in V
10
11 //calculations
12 X = (S*Vx)/Vs; //Resistance of resistor under
  test in
13
14 //result
15 mprintf("Resistance of resistor under test= %3.3 f
  ",X);


---



```

Scilab code Exa 10.5 Determine the value of resistor under test

```

1 //


---


2 //chapter 10 example 5
3 clc;clear all;
4
5 //variable declaration
6 Vx1 = 0.835; //indicated calue of voltage
  drop across the unknown resistance in V
7 emf = -25*10-6; //thermal emf with unknown

```

```

    resistance in V
8 S   = 0.10025;      //resistance of standard
    resistor in
9 Vs  = 0.984;       //voltage drop across standard
    resistor in V
10
11 //calculations
12 Vx  = Vx1-emf;
13 X   = (S*Vs)/Vs;   //Resistance of resistor under
    test in
14
15 //result
16 mprintf("unknown resistor = %3.5f      ",X);

```

Scilab code Exa 10.6 Calculate the unknown resistance

```

1 //


---


2 //chapter 10 example 6
3
4 clc;clear all;
5
6 //variable decalartion
7 p   = 200.62;      //resistance in
8 q   = 400;         //resistance in
9 P   = 200.48;     //resistance in
10 Q  = 400;         //resistance in
11 S  = 100.03;     //resistance in
12 r  = 700;        //resistance in
13
14 //calculations
15 X      = ((P/Q)*S)+((q*r)/(p+q))*((P/Q)-(p/q));
16
17 //result

```

```
18 mprintf("unknown resistance = %3.4f u ",X);
```

Scilab code Exa 10.7 Determine the value of unknown resistance

```
1 //
2 //chapter 10 example 7
3
4
5 clc;clear all;
6
7
8 //variable declaration
9 P = 100; //resistance in
10 Q = 10; //resistance in
11 S = 46; //resistance in
12
13 //calculations
14 R = (P/Q)*S; //unknown resistance in
15
16 //result
17 mprintf("unknown resistance = %3.2f ",R);
```

Scilab code Exa 10.8 Determine the value of unknown resistance

```
1 //
2 //chapter 10 example 8
3
4 clc;clear all;
5
```

```

6 //variable declaration
7 S   = 6;           //resistance in
8 AB  = 25;         //length of AB in cm
9 BC  = 75;         //length of BC in cm
10
11 //calculations
12 R   = (AB/BC)*S;   //unknown resistance in
13
14 //result
15 mprintf("unknown resistance = %3.0f    ",R);

```

Scilab code Exa 10.9 Determine the dials required to adjusted for obtaining the re

```

1 //


---


2 //chapter 10 example 9
3
4 clc;clear all;
5
6 //variable decalartion
7 R   =5000;         //a resistance of apporximately
   //required to balance a bridge in
8 E   = 0.1;        //in per cent
9
10 //calculations
11 R2  = R+(R*(E/100)); //limiting value in
12 R1  = R-(R*(E/100)); //limiting value in
13
14 //result
15 mprintf("limiting value %3.0f    to %3.0f    ",R1,R2
   //);
16 mprintf("\nThus dials of 1000,100,10,1    would have
   //to be adjusted");

```

Scilab code Exa 10.10 Calculate the limiting values of unknown resistance

```
1 //


---



---

  
2 //chapter 10 example 10
3
4
5 clc;
6 clear all;
7
8 //variable declaration
9 P = 100; //resistance in
10 Q = 100; //resistance in
11 S = 230; //resistance in
12 dP = 0.02; //limiting error(dP/P) in %
13 dQ = 0.02; //limiting error(dQ/Q) in %
14 dS = 0.01; //limiting error(dS/S) in %
15
16 //calculations
17 R = (P/Q)*S; //unknown resistance in
18 dR = dP+dQ+dS; //limiting error(dR/R) in %
19 dR1 = (dR*R)/100;
20 R1 = R-dR1; //limitng values of unknown
    resistance in
21 R2 = R+dR1; //limitng values of unknown
    resistance in
22
23 //result
24 mprintf("unknown resistance = %3.0f ",R);
25 mprintf("limitng values of unknown resistance %3.3f
    to %3.3f ",R1,R2);
```

Scilab code Exa 10.11 Find the magnitude and direction of the current flowing thro

```
1 //


---


2 //chapter 10 example 11
3
4 clc;clear all;
5
6 //variable declaration
7 P = 1000; //resistance in arm AC in
8 Q = 1000; //resistance in arm AD in
9 S = 100; //resistance in arm CB in
10 R = 101; //resistance in arm BD in
11 Rg = 50; //galvanometer resistance in
12 E = 2; //voltage in V
13
14 //calculations
15 R1 = (Q*S)/P; //resistance required in arm BD
    for balance bridge
16 dR = R-R1; //the deviation from balanced
    condition in
17 Eth = E*((R1+dR)/(R1+dR+S))-(P/(P+Q)); //
    thevenin's open circuit voltage in V
18 Rth = (((R1+dR)*S)/(R1+dR+S))+((P*Q)/(P+Q)); //
    thevenin's equivalent resistance of bridge in
19 Ig = Eth/(Rth+Rg); //galvanometer current
    in A
20
21 //result
22 mprintf("galvanometer current = %3.3f uA", (Ig*10^6))
    ;
23 mprintf("\nsince the point B is at higher potential
    with respect to point A ,current will floe from
```

```
terminal A");
```

Scilab code Exa 10.12 Determine the sensitivity of the bridge

```
1 //
2 //chapter 10 example 12
3 clc;clear all;
4
5 //variable declaration
6 P = 100; //resistance in arm AB in
7 Q = 1000; //resistance in arm BC in
8 S = 2000; //resistance in arm CD in
9 R = 202; //resistance in arm BD in
10 Rg = 200; //galvanometer resistance in
11 E = 5; //voltage in V
12 Si = 5; //current sensitivity of the
    galvanometer in mm/uA
13
14 //calculations
15 Si1 = 5*10^9; //current sensitivity of the
    galvanometer in mm
16 R1 = (P*S)/Q; //resistance required in arm BD
    for balance bridge
17 dR = R-R1; //the deviation from balanced
    condition in
18 Eth = E*(((R1+dR)/(R1+dR+S))-(P/(P+Q))); //
    thevenin's open circuit voltage in V
19 Rth = (((R1+dR)*S)/(R1+dR+S))+((P*Q)/(P+Q)); //
    thevenin's equivalent resistance of bridge in
20 Ig = Eth/(Rth+Rg); //galvanometer current
    in A
21 d = Si1*Ig; //deflection of the
    galvanometre theta in mm
```

```

22 S    = d/dR;           //sensitivity of the bridge
    in mm/
23
24 //result
25 mprintf("galvanometer current = %3.2e A",Ig);
26 mprintf("\ndeflection of the galvanometre theta = %3
    .1 f mm", (d*10^-3));
27 mprintf("\nsensitivity of the bridge = %3.2 f mm/ "
    ,(S*10^-3));

```

Scilab code Exa 10.13 Determine the ratio of galvanometer sensitivities

```

1 //


---


2 //chapter 10 example 13
3 clc;
4 clear all;
5
6 //variable declaration
7 P    = 1000;           //resistance in arm AB in
8 Q    = 100;           //resistance in arm BC in
9 R    = 200;           //resistance in arm BD in
10 Si1 = 10;           //sensitivity
11 Si2 = 5;            //sensitivity
12 Rg1 = 400;
13 Rg2 = 100;
14
15 //calculations
16 S    = R*Q/P;         //resistance required in arm
    CD in
17 Rth = ((R*S/(R+S))+(P*Q/(P+Q)));           //thevenin's
    equivalent resistance of bridge in
18 //theta = (Si*E*S*dR)/((R+S)^2)*(Rth+Rg1)
19 //theta2/theta1 = (Si*E*S*dR)/((R+S)^2)*(Rth+Rg1)

```

```

    *(((R+S)^2)*(Rth+Rg1)/(Si*E*S*dR))
20 r      = (Si2/Si1)*((Rth+Rg1)/(Rth+Rg2)); //ratio
    deflection of two galvanometer
21
22 //result
23 mprintf("ratio deflection of two galvanometer =
    %3.3f ",r);
24 mprintf("\nthe first galvanometer (internal
    resistance 400 and sensitivity 10 mm/uA) is
    less sensitive to a small unbalance on the given
    bridge ,through on its own it is more sensitive
    than the other galavanometer")

```

Scilab code Exa 10.14 Determine the smallest change in the resistance

```

1 //


---


2 //chapter 10 example 14
3
4 clc;
5 clear all;
6
7 //variable declaration
8 P = 500; //resistance in arm AB in
9 Q = 500; //resistance in arm BC in
10 S = 500; //resistance in arm CD in
11 R = 500; //resistance in arm BD in
12 Rg = 100; //galvanometer in
13 E = 10; //battery voltage in V
14 Rth = 500; //thevenin's equivalent resistance of
    bridge
15 Ig = 10^-9; //galavanometer capable of
    detecting Ig current in A
16

```

```

17 //calculations
18 //Eth = (E*dR)/(4*R);
19 x = E/(4*R); //thevenin or open -circuit
    voltage in dR
20 //Ig = Eth/(Rth+Rg)
21 y = x/(Rth+Rg); //current through galvanometer
22 dR = (Ig*(Rth+Rg))/x; //the smallest change in
    resistance that can be detected in
23
24 //result
25 mprintf("the smallest change in resistance that can
    be detected = %3.2 f m ",(dR*10^3));

```

Scilab code Exa 10.15 Determine the value of resistance

```

1 //


---


2 //chapter 10 example 15
3 clc;clear all;
4
5 //variable declaration
6 P = 200; //resistance in arm in
7 Q = 200; //resistance in arm in
8 S = 200; //resistance in arm in
9
10 R = 200; //resistance in arm in
11 p = 0.5; //power in W
12 r = 2; //r is internal resistance of
    battery in
13 E = 24; //voltage in V
14
15 //calculations
16 //P = (I^2)*R; power disiiipation in W
17 I = sqrt(p/R);

```

```

18 V    = I*2*R;           //the maximum voltage ,that can
    be applied to the bridge in V
19 I1   = 2*I;           //current through series resistor in
    A
20 //E = V+(2*I*(r+R)    battery emf E
21 R1   = ((E-V)/I1)-r; //series resistance in
22
23 //result
24 mprintf("current = %3.2f A",I);
25 mprintf("\nseries resistance = %3.2f      ",R1);

```

Scilab code Exa 10.16 Determine the maximum value of the resistance and internal r

```

1 //


---


2 //chapter 10 example 16
3
4 clc;clear all;
5
6 //variable declaration
7 P    = 10000;           //resistance in arm AB in
8 Q    = 10;             //resistance in arm BC in
9 S    = 5000;           //resistance in arm BD in
10 Si  = 10^8;           //sensitivity
11 Rg   =100;             //galvanometer resistance in
12 E    = 12;             //voltage in V
13 d    = 2.5;           //deflection in mm
14
15
16
17 //calculations
18 R    = P*S/Q;           //resistance required in arm
    CD in
19 Rth  = ((R*S/(R+S))+(P*Q/(P+Q))); //thevenin 's

```

```

    equivalent resistance of bridge in
20 dR = ((d*(Rth+Rg)*((R+S)^2))/(Si*E*S)); //
    change in defelection in
21
22 //result
23 mprintf("the maximum value of resistance that can be
    measured with the given arrangement = %3.2f ",
    R);
24 mprintf("\nchange in defelction = %3.2f k ",(dR
    *10^-3));

```

Scilab code Exa 10.17 Calculating how far are the balance positions

```

1 //


---


2 //Chapter 10 Example 17
3
4
5 clc;clear all;
6
7 //variable declaration
8 r = 0.0250; //resistance in
9 R = 1.0125; //resistance in
10 S = 1 //sensitivity
11 P1 = 10; //resistance in
12 Q1 = 10; //resistance in
13 P2 = 9.95; //resistance in
14 Q2 = 10.05; //resistance in
15 l = 100;
16
17 //calculations
18 r1 = r/100; //resistance in per scale
    division
19 x1 = P1/Q1;

```



```

20 x2      = P2/Q2;
21 //P/Q    = (R+(l1*r))/(S+(1-l1)*r)
22 //(s*x)+((1-l1)*r) = R+(l1*r)
23 //(S*x)+(l*r)-(l1*r) = R+(L1*r)
24 //(S*x)+(l*r)-R = (l1*r)+(l1*r)
25 l1      = ((S*x1)+(l*r1)-R)/(r1+r1);           // scale
           divisions
26 l12     = ((S*x2)+(l*r1)-R)/(r1+r1);           // scale
           divisions
27
28 //result
29 mprintf("hence the balance is obtainde at %3.0f and
           75 scale divisions",l1);
30 mprintf("\nhence the balance is obtainde at %3.0f
           and 95 scale divisions",l12);

```

Scilab code Exa 10.18 Calculate the insulation resistance of the cable

```

1 //


---


2 //chapter 10 example 18
3
4 clc;clear all;
5
6 //variable declaration
7 V1 = 250;           //voltage in V
8 V2 = 92;           //voltage in V
9 t  = 60;           //time in seconds
10 C = 600*10^-12;   //capacitance in F
11
12 //calculations
13 //V2 = V1*e^(t/C*R)
14 R = t/(C*log(V1/V2))
15

```

```

16 //result
17 mprintf("insulation resistance = %3.0f M    ",(R
    *10^-6));

```

Scilab code Exa 10.19 Calculate the insulation resistance of the cable

```

1 //


---


2 //chapter 10 example 19
3
4 clc;clear all;
5
6 //variable declaration
7 V1 = 100;      //voltage in V
8 V2 = 80;      //voltage in V
9 t = 20;       //time in seconds
10 C = 300*10^-12; //capacitance in F
11
12 //calculations
13 //V2 = V1*e^(t/C*R)
14 R = t/(C*log(V1/V2))
15
16 //result
17 mprintf("insulation resistance = %3.2e M    ",(R
    *10^-6));

```

Scilab code Exa 10.20 Calculate the insulation resistance of the cable

```

1 //


---


2 //chapter 10 example 20

```

```

3  clc;clear all;
4  //variable declaration
5  V1  = 200;      //voltage in V
6  V2   = 126;     //voltage in V
7  t    = 30;     //time in seconds
8  V12  = 200;    //voltage in V
9  V22   = 100;   //voltage in V
10
11 //calculations
12 //let CR = a
13 //V2      = V1*e^(t/C*R)
14 a        = t/log(V1/V2);      //C*R
15 //R1      = (10*R)/(10+R)
16 a1       = t/log(V12/V22);    //C*R1
17 //a1/a    =R1/R=x
18 x        = a1/a;
19 //since R1      = (10*R)/(10+R)
20 //x*(10+R)*R = 10*R
21 //(x*10)+R*x = 10
22 R = (10-(x*10))/x;      //Resistance in
23
24 //result
25 mprintf("resistance = %3.2f M    ",R);

```

Scilab code Exa 10.21 Calculate the value of R

```

1  //


---


2  //chapter 10 example 21
3  clc;clear all;
4
5  //variable declaration
6  V1  = 450;      //voltage in V
7  V2   = 280;     //voltage in V

```

```

8 t    = 15.2;      //time in minutes
9 t1   = 10.8;     //time in minutes
10 C   = 2.5*10^-6; //capacitance in F
11
12 //calculations
13 t12  = t*60;     //time in seconds
14 t22  = t1*60;   //time in seconds
15 //V2   = V1*e^(t/C*R)
16 x    = V1/V2;
17 y    = log(x);
18 R    = t12/(C*y);
19 R1   =t22/(C*y);
20 //R1    = t1/(C*log(V1/V2));
21 //1/R'  = (1/R1)-(1/R)
22 R11  = (R1*R)/(R-R1); //unknown resistance in

23
24 //result
25 mprintf("unknown resistance= %3.2d M  ",(R11*10^-6)
);

```

Scilab code Exa 10.22 Calculate the insulation resistance of the cable

```

1 //


---




---


2 //chapter 10 example 22
3 clc;
4 clear all;
5
6 //variable declaration
7 r    = 250;      //number of scale divisions
           galvanometer can read
8 s    = 2.5;     //universal shunt multiplier
9 r1   = 350;     //number of scale reading

```

```

10 s1 = 1000; //universal shunt multiplier when
    standard resistor is connector
11 S = 1000000;
12
13 //calculations
14 //IR praportional to galvanometer*universal shunt
    multiplier
15 IR = r*s; //current through the circuit with
    unknown resistance Rconnected
16 Is = r1*s1; //current through the circuit with
    standard resistance in S
17 R1 = (Is/IR)*S; //insulation resistance of cable
    in
18
19 //result
20 mprintf("insulation resistance of cable = %3.2f M "
    ,(R1*10^-6));

```

Scilab code Exa 10.23 Determine Rsh AND Rse AND maximum value of Rsh and scale error

```

1 //


---


2 //chapter 10 example 23
3 clc
4 clear all
5
6 //variable declaration
7 V = 3; //battery voltage in volts
8 Rm = 60; //resistance in
9 Ifm = 1.2; //full-scale deflection meter
    current in mA
10 Rh = 1500; //half-scale deflection
    resistance in
11 V1 = 0.3; //at 10 % drop in battery

```

```

    voltage in V
12
13 //calculations
14 If    = V/Rh;    //battery current for full-scale
    deflection in A
15 If1   = If*10^3;    //battery current for
    full-scale deflection in mA
16 Ish   = If1-Ifm;    //current through zero
    adjuster resistor i.e,shunt resistor in mA
17 Rsh   = (Ifm*Rm)/Ish;    //resistance in
18 Rse   = Rh-((Rsh*Rm)/(Rsh+Rm));    //current
    limiting resistor i.e,series resistor
19 V3    = V-V1;    //voltage in V
20 If2   = V3/Rh;    //battery current at full-
    scale deflection in A
21 If21  = If2*10^3;    //battery current at full
    -scale deflection in mA
22 Ish1  =If21-Ifm;    //current through shunt
    resistor in mA
23 Rsh1  = (Ifm*Rm)/Ish1;    //shunt resistor in
24 Rh1   = Rse+((Rm*Rsh1)/(Rm+Rsh1));    //total
    internal circuit resistance in
25 e     =((Rh-Rh1)/(Rh1))*100;    //percentage
    error in %
26
27 //calculation
28 mprintf("resistance = %3.2f    ",Rsh);
29 mprintf("\ncurrent limiting resistor = %3.2f    ",
    Rse);
30 mprintf("\nshunt resistor = %3.2f    ",Rsh1);
31 mprintf("\npercentage error = %3.3f percentage ",e);

```

Scilab code Exa 10.24 Determine the value of current

```
1 //
```

```

2 //chapter 10 example 24
3
4 clc;
5 clear all;
6
7 //variable declaration
8 V = 3; //battery voltage in volts
9 Rm = 2; //meter resistance in
10 Ifm = 10; //full scale deflection meter current in
    mA
11 Rh = 0.5; //half scale deflection resistance in
12
13 //calculations
14 Im = 0.5*Ifm; //half-scale deflection of
    the movement
15 Vm = Im*Rm; //voltage across movement
    in mV
16 Ix = (Vm*10^-3)/Rh; //current through
    resistor in A
17 Ix1 = Ix*10^3; //urrent through
    resistor in mA
18 IB = Im+Ix1; //total battery current
    in mA
19 V1 = V-(Vm*10^-3); //voltage drop across
    current lo V
20 Rse = V1/(IB*10^-3); //current limiting
    resistor in
21
22 //result
23 mprintf("current limiting resistor = %3.1f ",Rse);

```

Chapter 11

Potentiometers

Scilab code Exa 11.1 Determine emf and current and voltage and percentage error in

```
1 //


---


2 //chapter 11 example 1
3
4 clc;clear all;
5
6 //variable declartion
7 v = 1.0186; //emf of standard cell in volts
8 l = 60; //length in cm
9 l1 = 75; //length in cm
10 l2 = 66; //length in cm
11 l3 = 84; //length in cm
12 l4 = 40; //length in cm
13 l5 = 72; //length in cm
14 S = 2; //resistance in
15 r = 100; //ratio of volt ratio box
16 S1 = 2.5; //resistance in
17 I = 0.28; //ammeter reading in ampere
18 v1 =1.25; //voltmeter reading in volts
19
```



```

20 //calculations
21 v0 = v/l; //the voltage drop per cm length of
    potentiometer wire in volt
22 V1 = v0*l1; //emf of cell which balances at
    75 cm in volts
23 V2 = v0*l2; //emf of cell which balances at
    66 cm in volts
24 I1 = v/S; //current flowing through 2
    resistance in A
25 V3 = v0*l3; //emf of cell which balances at
    84 cm in volts
26 v31 = V3*r; //voltage of supply main in volts
27 V4 = v0*l4; //emf of cell which balances at
    40 cm in volts
28 I4 =V4/S1; //current flowing through 2.5
    resistance in A
29 e = ((I-I4)/I4)*100; //percentage error in the
    ammeter reading in %
30 V5 = v0*l5; //emf of cell which balances at
    72 cm in volts
31 e1 = ((v1-V5)/V5)*100; //percentage error in the
    voltmeter reading in %
32
33 //result
34 mprintf("emf of cell which balances at 75 cm = %3.5
    f volts",V1);
35 mprintf("\ncurrent flowing through 2 resistance =
    %3.5f A",I1);
36 mprintf("\nvoltage of supply main in volts = %3.5f
    volts",v31);
37 mprintf("\npercentage error in the ammeter reading =
    %3.1d percentage high",e);
38 mprintf("\npercentage error in the voltmeter reading
    = %3.2f percentage ",e1);

```

Scilab code Exa 11.2 Calculate the resolution of potentiometer

```
1 //


---



---


2 //chapter 11 example 2
3 clc;
4 clear all;
5
6 //variable declaration
7 R = 10; //resistance of slide wire in
8 n = 15; //number of steps of dial
9 r = 10; //resistance of each dial in
10 I = 0.01; //working current in A
11 N = 100; //number of divisions of slide
12 a = 0.2; //each division of slide can read
    upto a accurately of its span
13
14 //calculations
15 R1 = (n*r)+R; //total resistance of
    potentiometer in
16 V = I*R1; //voltage range of the potentiometer
    V
17 v = R*I; //voltage drop across slide wire V
18 x = v/N; //each division represents in V
19 y = x*a; //resolution of potentiometer in V
20
21 //result
22 mprintf("resolution of potentiometer = %3.4f V",y);
```

Scilab code Exa 11.3 Calculate the working current and resistance and measurement

```
1 //
```

```

2 //chapter 11 example 3
3 clc;
4 clear all;
5
6 //variable declaration
7 R = 400; //total resistance of slide-wire of
    200 cmin
8 L1 = 101.8; //length of slide wire in cm
9 L = 200; //length of wire in cm
10 v1 = 1.018; //voltage drop across 101.8cm
    length of slide wire in V
11 v = 3; //battery voltage in V
12 a = 0.2; //it is possible to read a of 1 mm
13
14 //calculations
15 R1 = (R/L)*L1; //resistance of slide wire of
    101.8 cm in
16 I1 = v1/R1; //working current in A
17 RT = v/I1; //total resistance of battery
    circuit in
18 RR = RT-R; //resistance of series rheostat in

19 r = I1*R; //measuring range in V
20 //since 200cm length represents 2 V
21 //1 mm length represents = z
22 z = (r/L)*(1/10); //voltage represented for 1mm
    length
23 Ri = z*a; //resolution of instrument in mV
24
25 //result
26 mprintf("working current = %3.1e A", (I1*10^3));
27 mprintf("\nresistance of series rheostat = %3.2f "
    ,RR);
28 mprintf("\nmeasuring range = %3.2f V", r);
29 mprintf("\nresolution of the instrument = %3.2f mV"
    ,(Ri*10^3));

```

Scilab code Exa 11.4 Calculate the inductance of the coil

```
1 //


---


2 //chapter 11 example 4
3
4 clc;
5 clear all;
6
7 //variable declaration
8 R1 = 0.1; //standard resistance in
9 V2 = 0.613; //voltage drop across standard
   resistance in V
10 a = 100;
11 r = 0.781; //volt ration box
12 theta = 50.48;
13 theta1 = 12.6;
14 f = 50; //frequency in in HZ
15
16 //calculations
17 I = V2/R1; //current through coil in A
18 V1 = a*r; //voltage drop across inductive
   coil in V
19 theta2 = theta -theta1;
20 L = V1*sin(theta2*180/%pi)/(2*%pi*f*I); //
   inductance of coil in H
21
22 //result
23 mprintf("inductance of coil =%3.2f H",L);
```

Scilab code Exa 11.5 Calculate the resistance and reactance of the coil

```

1 //


---


2 //chapter 11 example 5
3
4 clc;clear all;
5
6 //variable declaration
7 R1 = 1; //standard resistance in
8 V3 = 0.952-0.340*i; //voltage through the coil
   in A
9 a = 10; //multiplying power of potential
   divider
10 V2 = 1.35+1.28*i; //voltage across potential in A
11
12 //calculations
13 x = complex([0.952,-0.342])
14 y = complex([1.35,1.28])
15 I = x/R1; //current through coil in A
16 I = x/R1 //current through coil in A
17 I1 = 0.952-0.340*i;
18 V1 = a*y //voltage across coil in V
19 V11 = 13.5+12.8*i;
20 Z = V11/I1
21 R = real(Z) //resistance of coil in
22 X = imag(Z) //reactance of coil
23
24 //result
25 mprintf("%g + %gi\n",R,X);
26 mprintf("resistance of coil = %3.4f ",R);
27 mprintf("\nreactance of coil = %3.2f ",X);

```

Scilab code Exa 11.6 Calculate the resistance and reactance of the coil

```
1 //
```

```

2 //chapter 11 example 6
3
4 clc;
5 clear all;
6
7 //variable declaration
8 R      = 1;           //resistace in
9 V2     = 0.238-%i*0.085; //voltage across
    standard resistor in V
10 P     = 10;         //multiplying ower of
    potential divider
11 V1    = 0.3375+%i*0.232; //voltage across
    potential divider in V
12
13
14
15 //calculations
16 I     = V2/R;       //current through coil
    in A
17 V2    = P*V1;      //voltage across the
    coil in V
18 Z     = V2/I;      //impedance of coil in
19 R1    = real(Z);   // resistance of
    coil in
20 X1    = imag(Z);   //reactance of coil in
21
22 //result
23 mprintf("resistance = %3.2 f    ",R1);
24 mprintf("\nreactance = %3.3 f    ",X1);

```

Scilab code Exa 11.7 Determine the core loss in the choke coil

```

1 //


---


2 //chapter 11 example 7
3
4 clc;
5 clear all;
6
7 //variable declaration
8 R1      = 1.0;          //resistace in
9 V1      = 0.8-%i*0.75; //voltage drop
           across the resistance in volt
10 V2     = 1.2+%i*0.3;  //voltage across the
           coil in volt
11
12 //calculations
13 I       = V1/R1;      //current through coil in A
14 x       = (atan(imag(V1)/real(V1)))*180/%pi;
15 y       = (atan(imag(V2)/real(V2)))*180/%pi;
16 phi    = y-x;
17 a       =sqrt(((real(V2))^2)+((imag(V2))^2));
18 b       =sqrt(((real(I))^2)+((imag(I))^2));
19 V3     = a*cos(phi*%pi/180); //resistive
           drop the coil in V
20 P       = a*b*cos(phi*%pi/180); //power loss
           in the coil in W
21
22
23 //result
24 mprintf("iron loss in the coil =%3.3f watt",P);


---



```

Scilab code Exa 11.8 Determine the true reading of the wattmeter and the load power

```

1 //


---



```

```

2 //chapter 11 example 8
3
4 clc;
5 clear all;
6
7 //variable declaration
8 R1    = 0.1;           //standard resistance in
9 V1    = 0.35-%i*0.1;  //voltage drop across
    resistance in V
10 V2   = 0.8-%i*0.15;  //voltage across coil in V
11
12 //calculations
13 I     = V1/R1;,       //current through coil in A
14 V     = 300*V2;       //apply voltage V
15 x1    = real(I);
16 y1    = abs(imag(I));
17 V1    = sqrt((x1^2)+(y1^2));
18 x     = real(V);
19 y     = imag(V);
20 I1    = sqrt((x^2)+(y^2));
21 P     = (x1*x)+(y1*y);
22 //pf   = P/(V1*I);    //power factor of the
    load circuit in lagging
23 pf    = P/(V1*I1);    //power factor of
    the load circuit in cos(phi)
24
25 //result
26 mprintf("power factor of the load circuit = %3.3f
    lagging",pf);

```

Chapter 12

AC bridges

Scilab code Exa 12.1 Determine whether to balance the bridge

```
1 //


---


2 //Chapter 12 example 1
3 clc;clear all;
4
5 //variable declaration
6 Z1          = 100;           //resistance of arm in
7 Z2          = 50;           //resistance of arm in
8 Z3          = 200;          //resistance of arm in
9 Z4          = 100;          //resistance of arm in
10 theta1     = 30;           //phase angle in
11 theta2     = 0;           //phase angle in
12 theta3     = -90;          //phase angle in
13 theta4     = 30;           //phase angle in
14
15 //calculations
```

```

16 x      = Z1*Z4;      //magnitude
17 y      = Z2*Z3;      //magnitude
18 thetax  = theta1+theta4;
19 thetay  = theta2+theta3;
20
21 //result
22 mprintf("x      = %3.2 f",x)
23 mprintf("\nx      = %3.2 f",y);
24 mprintf("\nsince x =y\n');
25 mprintf("\nthe first condition is satisfied');
26 mprintf("\nthetax = %3.2 f",thetax);
27 mprintf("\nthetay  = %3.2 f",thetay);
28 mprintf("\nsecond condition is not saatisfied ');
29 mprintf("\nIt means bridge is unbalancedthrough
      first condition for equality of magnitude product
      satisfied,obviously balance is not possible
      under above conditions");

```

Scilab code Exa 12.2 Determne whether or not the bidge is complete balance

```

1 //


---


2 //Chapter 12 Example 2
3
4 clc;
5 clear all;
6
7 //variable declaration
8 Z1      = 1000;      //resistance of arm in
9 Z2      = 500;      //resistance of arm in
10 Z3     = 1000;      //resistance of arm in

```

```

11 Z4          = 509.9;           //resistance of arm
    in
12 ZX4         =100+500*%i;
13 theta1     = -90;           //angle in
14 theta2     = 0;            //angle in
15 theta3     = 0;            //angle in
16 theta4     = -90;          //angle in
17 theta41    = 78.69;
18
19 //calculations
20
21 thetax      = theta1+theta41;
22 thetay      = theta2+theta3;
23 x           = Z2*Z3;
24 //Z1*Z4 =Z2*Z3
25 //1/Z1     = A      = Z4/Z2*Z3   = Z4/x
26 A          = ZX4/x;
27 //1/Z1     = 1/R1 +(w*C1)*%i
28 Zx3        = (Z1*Z4)/Z2;
29 thetax3     = theta1+theta41-theta2;
30 Z3         = (Zx3*cos(thetax3*%pi/180))+(Zx3*sin(
    thetax3*%pi/180));
31
32
33 //result
34 mprintf(" thetax      = %3.2 f      ",thetax);
35 mprintf("\nthetax      = %3.2 f      ",thetay);
36 mprintf("\nbalance can be restored by modifying the
    circuit so asto satisfy the phase angle condition
    ");
37 mprintf("\ncomparing equations 1 and 2 R1      = %3
    .2 f" ,1/real(A));
38 mprintf("\ncomparing equations 1 and 2 1/w*C1   =
    %3.2 e" ,imag(A));
39 mprintf("\n1/w*C1 is already equal to 1000      so
    the bridge can be easily balanced by adding 5000
    accross capacitor in arm 1");
40 mprintf("\nsince R3 is already of 1000      so the

```

```

    bridge can be easily balanced by adding
    capacitance 200 in series across in arm 3");
41 mprintf("Note:there was a possibility that with the
    addition of resistance R1 in armm 1 as first
    option or with teh addition of capacitance C3 in
    arm 3");

```

Scilab code Exa 12.3 Find the resistance and inductance of the coil

```

1 //


---


2 //Chapter 12 Example 3
3
4
5 clc;clear all;
6
7 //variable declaration
8 R2      = 100;           //resistance of arm in
9 R3      = 32.7;         //resistance of arm in
10 R4     = 100;           //resistance of arm in
11 R      = 1.36;          //resistance of arm in
12 L      = 47.8;          //inducatance in mH
13
14
15 //calculations
16 R1      = ((R2*R3)/(R4))-R;           //resistance of coil
    in
17 L1      = (R2/(R4))*L;           //in case of balanced
    position of bridge in mH
18
19 //result
20 mprintf("Resistance pf the coil = %3.2 f ",R1);
21 mprintf("\ninductance in case of balanced bridge =
    %3.2 f mH" ,L1);

```

Scilab code Exa 12.4 Find the resistance and inductance

```
1 //
2 //Chapter 12 Example 4
3
4 clc; clear all;
5
6 //variable declaration
7 R2      = 1000;      //resistance of arm in
8 R3      = 1000;      //resistance of arm in
9 R4      = 1000;      //resistance of arm in
10 C4      = 0.5*10^-6; //capacitance in F
11
12 //calculations
13 R1      = ((R2*R3)/(R4)); //resistance of coil in
14 L1      = C4*R2*R3;      //inductance of inductor
    in H
15
16 //result
17 mprintf("resistance of coil = %3.2f ",R1);
18 mprintf(" \ninductance of inductor = %3.2f H",L1);
```

Scilab code Exa 12.5 Find the resistance and inductance of the unknown resistance

```
1 //
2 //Chapter 12 Example 5
```

```

3
4 clc;clear all;
5
6 //variable declaration
7 R2      = 1000;      //resistance of arm in
8 R3      = 218;      //resistance of arm in
9 R4      = 1000;      //resistance of arm in
10 C4     = 10*10^-6;  //capacitance in F
11 r      = 469;
12
13 //calculations
14 R1     = ((R2*R3)/(R4));  //resistance of coil in
15 x      = (r*(R3+R4))+(R3*R4)
16 L1     = (C4*R2*x)/(R2);  //inductance of
    inductor in H
17
18 //result
19 mprintf("resistance of coil = %3.2f ",R1);
20 mprintf("\ninductance of inductor = %3.2f H",L1);

```

Scilab code Exa 12.6 Find the resistance and inductance

```

1 //


---


2 //Chapter 12 Example 6
3
4 clc;clear all;
5
6 //variable declaration
7 R2      = 400;      //resistance of arm in
8 R3      = 400;      //resistance of arm in
9 R4      = 400;      //resistance of arm in
10 C4     = 2*10^-6;  //capacitance in F

```

```

11 r          = 500;          //resistance in
12
13 //calculations
14 R1         = ((R2*R3)/(R4)); //resistance of coil in

15 x         = (r*(R3+R4))+(R3*R4)
16 L1        = (C4*R2*x)/(R3); //inductance of
           inductor in H
17
18 //result
19 mprintf("resistance of coil = %3.2f ",R1);
20 mprintf("\ninductance of inductor = %3.2f Henry",L1)
   ;

```

Scilab code Exa 12.7 Find the resistance and inductance

```

1 //


---


2 //Chapter 12 Example 7
3
4 clc;clear all;
5
6 //variable declaration
7 R2         = 1000;          //resistance of arm in
8 R3         = 500;           //resistance of arm in
9 R4         = 1000;          //resistance of arm in
10 C4        = 3*10**-6;      //capacitance in F
11 r         = 100;
12
13 //calculations
14 R1         = ((R2*R3)/(R4)); //resistance of coil in

15 x         = (r*(R3+R4))+(R3*R4)
16 L1        = (C4*R2*x)/(R4); //inductance of

```

```

    inductor in H
17
18 //result
19 mprintf("resistance of coil = %3.2f    ",R1);
20 mprintf("\ninductance of inductor = %3.2 fHenry",L1);

```

Scilab code Exa 12.8 Find the resistance and inductance

```

1 //


---


2 //Chapter 12 Example 8
3
4 clc;clear all;
5
6 //variable declaration
7 R2      = 1000;      //resistance of arm in
8 R3      = 16800;    //resistance of arm in
9 R4      = 833;      //resistance of arm in
10 C4     = 0.38*10^-6; //capacitance in F
11 f      = 50;       //frequency in Hz
12
13 //calculations
14 w      = 2*(%pi)*f;
15 L1     = (R2*R3*C4)/(1+((w^2)*(R4^2)*(C4^2)));
    //inductance in H
16 R1     = (R2*R3*R4*(w^2)*(C4^2))/(1+((w^2)*(R4^2)*(
    C4^2))); //resistance in
17
18
19 //result
20 mprintf("inductance of inductor = %3.2 fHenry",L1);
21 mprintf("\nresistance of coil = %3.2f    ",R1);

```

Scilab code Exa 12.9 Find the Resistance and Capacitance

```
1 //


---



---


2 //Chapter 12 Example 9
3
4 clc;clear all;
5
6 //variable declaration
7 R2      = 1000;      //resistance of arm in
8 R3      = 1000;      //resistance of arm in
9 R1      = 500;       //resistance of arm in
10 L1     = 0.18;      //inductance in H
11
12 //calculations
13 f      = 5000/(2*(%pi)); //frequency in
      Hz
14 w      = 2*(%pi)*f;
15 x      = R1/((w^2)*L1); //R4*C4 be x
16 z      = ((w^2)*(x^2));
17 a      = (1+z);
18 C4     = (L1*a)/(R2*R3);
19 //from 1 and 2 equations
20 //R4    = R4*C4/C4 = x/C4
21 R4     = (x)/(C4); //resistance in
22
23 //result
24 mprintf("resistance = %3.2f ",R4);
```

Scilab code Exa 12.10 Find the series equivalent inductance and resistance of the

```

1 //


---


2 //Chapter 12 Example 10
3
4 clc;clear all;
5
6 //variable declaration
7 R2      = 1000;      //resistance of arm in
8 R3      = 10000;    //resistance of arm in
9
10 R4      = 2000;     //resistance of arm in
11 C4      = 1*10**-6; //capacitance in F
12 w       = 3000;    //radian per second
13
14 //calculations
15 L1      = (R2*R3*C4)/(1+((w^2)*(R4^2)*(C4^2)));
16 //inductance in H
17 R1      = (R2*R3*R4*(w^2)*(C4^2))/(1+((w^2)*(R4^2)*(
18 C4^2))); //resistance in
19
20 //result
21 mprintf("\ninductance of inductor = %3.2 f H",L1);
22 mprintf("resistance of coil = %3.2 f ",R1);

```

Scilab code Exa 12.11 Find the resistance and inductance of the choke coil

```

1 //


---


2 //Chapter 12 Example 11
3
4 clc;clear all;
5

```

```

6 //variable declaration
7 R2      = 2410;      //resistance of arm in
8 R3      = 750;      //resistance of arm in
9 R4      = 64.9;     //resistance of arm in
10 R      = 0.4;      //resistance in
11 C4      = 0.35*10^-6; //capacitance in F
12 f      = 500;      //frequency in Hz
13
14 //calculations
15 w      = 2*(%pi)*f; //radian per second
16 R41    = R4+R;      //resistance in
17 L1     = (R2*R3*C4)/(1+((w)*(R4^2)*(C4^2)));
           //inductance in H
18 R1     = (R2*R3*R41*(w^2)*(C4^2))/(1+((w^2)*(R41^2)
           *(C4^2))); //resistance in
19
20 //result
21 mprintf("resistance of coil = %3.2f ",R1);
22 mprintf("\ninductance of inductor = %3.4f Henry",L1)
   ;

```

Scilab code Exa 12.12 Derive the balance condition and calculate the effective imp

```

1 //


---




---


2 //Chapter 12 example 12
3
4 clc;
5 clear all;
6
7 //variable declaration
8 R2      = 834;      //resistance of arm in
9 R3      = 100;     //resistance of arm in
10 R4     = 64.9;     //resistance of arm in

```

```

11 R          = 0.4;           //resistance in
12 C4         = 0.1*10^-6;    //capacitance in F
13 C2         = 0.124*10^-6;  //capacitance in F
14 f          = 2000;        //frequency in Hz
15
16 //calculations
17 L1         = R2*R3*C4;      //inductance in H
18 R1         = (R3*C4/C2);    // resistance in
19 Z          = R1+(2*%pi*f*L1)*%i; //
    effective impedance
20 Z1         = sqrt(((real(Z))^2)+(((imag(Z))^2)));
21 angle      = (atan((imag(Z))/real(Z)))*180/%pi;
22
23 //result
24 mprintf("L1          = %3.2e",L1);
25 mprintf("\nR1          = %3.2f",R1);
26 mprintf("\neffective impedance of test specimen =%3
    .2f      angle %3.2f      ",Z1,angle);

```

Scilab code Exa 12.13 Find out the phase angle error and unknown capacitance

```

1 //


---


2 //Chapter 12 example 13
3
4 clc;clear all;
5
6 //variable declaration
7 R1          = 1000;         //resistance of arm in
8 R2          = 1000;         //resistance of arm in
9 R3          = 2000;         //resistance of arm in
10 R4         = 2000;         //resistance of arm in
11 C1         = 1*10^-6;      //capacitance in F
12 f          = 1000;

```

```

13 r1          =10;           //resistance in
14
15 //calculations
16 W           = 2*%pi*f;
17 C2          = (C1*R1)/(R2); //capacitance in F
18 r2          = ((R2*(R3+r1))-(R1*R4))/(R1); //
    Resistance in
19 d1          = (W*r1*C1)*(180/%pi); //phase
    angle error in
20 d2          = (W*r2*C2)*(180/%pi); //phase
    angle error in
21
22 //calculations
23 mprintf("phase angle error = %3.1f ",d1);
24 mprintf("\nphase angle error = %3.1f ",d2);

```

Scilab code Exa 12.14 Calculate the resistance and capacitance and also the dissip

```

1 //


---




---


2 //Chapter 12 example 14
3
4 clc;clear all;
5
6 //variable declaration
7
8 R2          = 4.8;         //resistance of arm in
9 R3          = 2000;       //resistance of arm in
10 R4         = 2850;       //resistance of arm in
11 C2         = 0.5*10^-6;  //capacitance in F
12 f          = 500;        //frequency in Hz
13 r2         =0.4;        //resistance in
14
15 //calculations

```

```

16 w          = 2*(%pi)*f;
17 C1         = C2*(R4/(R3));    //unknown capacitance in
    F
18 x          =R2+r2
19 r1         = (R3/R4)*(x);    //resistance in
20 D          = w*C1*r1;        //dissipation factor
21
22 //result
23 mprintf("unknown capacitance = %3.2e uF", (C1*10^6));
24 mprintf("\nresistance = %x3.2 f    ", x);
25 mprintf("\ndissipation factor = %3.5 f", D);

```

Scilab code Exa 12.15 Calculate the power factor

```

1 //


---


2 //Chapter 12 example 15
3
4 clc;clear all;
5
6 //variable declaration
7 R2          = 100;            //resistance of arm in
8 R4          = 309;            //resistance of arm in
9 C4          = 0.5*10^-6;      //capacitance in F
10 C3          = 109*10^-12;    //capacitance in F
11 f          = 50;             //frequency in Hz
12
13 //calculations
14 w          =2*(%pi)*f;
15 Cx         = (R4*C3)/(R2);    //equivalent series
    capacitance in F
16 Rx         = (C4*R2)/(C3);    //series resistance
    in
17 p          = w*Rx*Cx;        //power factor of

```

```

        the specimen (sind =tand)
18
19
20 //result
21 mprintf("power factor of the specimen = %3.5 f",p)
    ;

```

Scilab code Exa 12.16 Derive the variable resistance

```

1  clc;clear all;
2
3  //variable decalaration
4  R4    = 1000;          //resistance in
5  C3    = 50*10^-12;    //capacitance in F
6  A     = 314*10^-4;    //area in m**2
7  D     = 0.3*10^-2;    //thickness in m
8  er    = 2.3;          //dielectric constant
9  e0    = 8.854*10^-12; //dielectric constant
10 d     = 9;             //loss angle in
11 f     = 50;
12
13 //calculations
14 //calculations
15 C1    = (er*e0*A)/D;   //capacitance in F
16 w     = 2*%pi*f;
17 x     = tan(d*%pi/180);
18 R1    = 1/(w*C1*x);    //resistance in
19 C4    = 1/((w^2)*C1*R1*R4); //variable
    capacitor in F
20 R2    = (C3*R4*((cos(d*%pi/180))^2))/(C1); //
    variable resistance in
21
22 //result
23 mprintf("Variable capacitor = %3.1 f M    ",(R1*10^-6)
    );

```

```
24 mprintf("\nvariable resistance = %3.0f ",R2);
```

Scilab code Exa 12.17 Find the equivalent resistance

```
1 //
2 //chapter 12 example 17
3
4
5
6 clc;
7 clear all;
8
9 //variable declaration
10 R1      = 3100;           //resistance of arm in
11 R2      = 25000;        //resistance of arm in
12 R4      = 100000;       //resistance of arm in
13 C1      = 5.2*10^-6;    //capacitance in F
14 f       = 25000;       //frequency in Hz
15
16 //calculations
17 //C3     = C1*((R2/R4)-(R1/R3))
18 //X      = C1*(R2/R4)
19 //Y      = C1*(R1/R3)
20 w       = 2*pi*f;
21 x       = 1/((w^2)*R1*C1);
22 //R3    = x/C3
23 A       = (C1*R2)/R4;
24 B       = 1+(C1*R1/x);
25 C3     = A/B;           //capcitance in uuF
26 R3     = x/C3;         //equivalent parallel
```



```

    resistance in
27
28 //result
29 mprintf("equivalent parallel resistance = %3.2f K
    ",(R3*10^-3));

```

Scilab code Exa 12.18 Find the dissipation factor

```

1 //


---


2 //Chapter 12 example 18
3
4 clc;clear all;
5
6 //variable declaration
7 R3      = 2000;      //resistance of arm in
8 R4      = 2950;      //resistance of arm in
9 R2      = 5;         //resistance of arm in
10 r2     = 0.4;       //resistance in
11 C2     = 0.5*10^-6; //capacitance in F
12 f      = 450;       //frequency in Hz
13
14 //calculations
15 r1     = (R3*(r2+R2))/R4 //resistance in
16 C1     = ((R4/R3)*C2) //capacitance in F
17 tand   = 2*(%pi)*f*C1*r1 //dissipation power ,C1
    in uF
18
19 //result
20 mprintf("resistance = %3.2f ",r1);
21 mprintf("\ncapacitance = %3.2e uF", (C1*10^6));
22 mprintf("\ndissipation factor = %3.2e ",(tand));

```

Scilab code Exa 12.19 Calculate the capacitance and dielectric loss angle of bushing

```
1 //


---


2 //Chapter 12 example 19
3
4 clc;clear all;
5
6 //variable declaration
7 R3      = 300;           //resistance of arm in
8 R4      = 72.6;        //resistance of arm in
9 C2      = 500*10^-12;   //capacitance in F
10 C4     = 0.148*10^-6;  //capacitance in F
11 f       = 50;          //frequency in Hz
12
13 //calculations
14 Cx      = (R4*C2)/(R3); //capacitance in F
15 Rx      = (R3*C4)/(C2); //resistance in
16 x       = 2*(%pi)*f*Cx*Rx;
17 d       = atan(x);     //dielectric loss angle of
    bushing in
18 d1     = (d*180)/%pi;
19 //result
20
21 mprintf("\ncapacitance = %3.2e uF", (Cx));
22 mprintf("resistance = %3.2f K ", (Rx*10^-3));
23 mprintf("\ndielectric loss angle of bushing = %3.3f
    ", d1);
```

Scilab code Exa 12.20 Calculate the power factor and equivalent series resistance

```

1 //


---


2 //Chapter 12 example 20
3
4 clc;clear all;
5
6 //variable declaration
7 R3      = 130;           //resistance of arm in
8 R4      = 318;           //resistance of arm in
9 C2      = 106*10**-12;   //capacitance in F
10 C4     = 0.35*10**-6;   //capacitance in F
11 f      = 50;           //frequency in Hz
12
13 //calculations
14 Cx     = (R4*C2)/(R3);   //capacitance in F
15 Rx     = (R3*C4)/(C2);   //resistance in
16 x      = 2*(%pi)*f*Cx*Rx; //power factor
17
18
19 //result
20
21 mprintf("capacitance = %3.2e uF", (Cx));
22 mprintf("\nresistance = %3.2f K ", (Rx*10^-3));
23 mprintf("\npower factor = %3.3f ", x);

```

Scilab code Exa 12.21 Find the resistance and inductance of the coil

```

1
2 //


---


3 //Chapter 12 example 21
4
5 clc;clear all;

```

```

6
7 //variable declaration
8 M1    = 15.9;           //mutual inductance in mH
9 M2    = 0.1;           //mutual inductance in mH
10 r1   = 25.9;          //resistance in
11 r2   = 12.63;         //resistance in
12
13 //calculations
14 L1    = 2*(M1-M2);     //self inductance in mH
15 R1    = r1-r2;        //resistance in
16
17 //result
18 mprintf("self inductance = %3.2f mH",L1);
19 mprintf("\nresistance = %3.2f    ",R1);

```

Scilab code Exa 12.22 Calculate the value of L and C

```

1 //


---


2 //Chapter 12 example 22
3
4 clc;clear all;
5
6 //variable declaration
7 f1    = 2*10^6;        //frequency from second data in
                        Hz
8 f2    = 1*10^6;        //frequency from first data in
                        Hz
9 C1    = 230*10^-12;    //capacitance in F
10 C2    = 8*10^-12;     //capacitance in F
11
12 //calculations
13 C      = C1+C2;
14 L      = 1/((((2*(%pi)*f1)^2)*C)); //inductance

```

```

    in uH
15 Cx      = 1/(((2*(%pi)*f2)^2)*L);          //
    capacitance in pF
16
17 //result
18 mprintf("inductance = %3.2 f uH", (L*10^6));
19 mprintf("\ncapacitance = %3.2 f pF", (Cx*10^12));

```

Scilab code Exa 12.23 Determine the resistive and reactive component of unknown im

```

1 //


---


2 //Chapter 12 example 23
3
4 clc;clear all;
5
6 //variable declaration
7 f      = 165*10^3;          //frequency in Hz
8 C1     = 208*10^-12;       //capacitance in F
9 C2     = 184*10^-12;       //capacitance in F
10 Q1    = 80;                //Q-factor
11 Q2    = 50;                //Q-factor
12
13 //calculations
14 x      = C2*Q2;
15 y      = C1*Q1;
16 w      = 2*(%pi)*f;
17 Rm     = (1/(w))*((1/(x))-(1/(y)));      //resistive
    component of unknown impedance in
18 Xm     = (1/(w))*((1/C2)-(1/C1));      //reactive
    component of unknown impedance in
19
20
21 //result

```

```

22 mprintf("resistive component of unknown impedance =
    %3.2 f    ",Rm);
23 mprintf("\nreactive component of unknown impedance =
    %3.0 f    ",Xm);

```

Scilab code Exa 12.24 Determine the self capacitance and inductance of the coil

```

1
2 //


---


3 //Chapter 12 example 21
4
5 clc;clear all;
6
7 //variable declaration
8 M1    = 15.9;           //mutual inductance in mH
9 M2    = 0.1;           //mutual inductance in mH
10 r1    = 25.9;         //resistance in
11 r2    = 12.63;        //resistance in
12
13 //calculations
14 L1    = 2*(M1-M2);     //self inductance in mH
15 R1    = r1-r2;        //resistance in
16
17 //result
18 mprintf("self inductance = %3.2 f mH",L1);
19 mprintf("\nresistance = %3.2 f    ",R1);

```

Scilab code Exa 12.25 Determine the self capacitance

```

1 //


---


2 //Chapter 12 example 25
3 clc; clear all;
4
5 //variable declaration
6 f1      = 3;          //frequency in MHz
7 f2      =6;          //frequency in MHz
8 C1      = 251;       //capacitance in pF
9 C2      = 50;        //capacitance in pF
10
11 //calculations
12 Cd      = (C1-(4*C2))/(3);          //self capacitance
      of the coil in uuF
13 //since f1 = 2f2
14
15
16 //result
17 mprintf("self capacitance of the coil = %3.2f pF",Cd
      );


---



```

Scilab code Exa 12.26 Determine the self capacitance of the coil

```

1 //


---


2 //Chapter 12 example 26
3 clc; clear all;
4
5 //variable declaration
6 C1      = 1530;       //capacitance in pF
7 C2      = 162;       //capacitance in pF
8 f1      = 3;         //frequency in MHz
9 f2      =1;          //frequency in MHz

```

```

10
11 //calculations
12 //f1    = 1/((2*math.pi)*(math.sqrt(L*(C2+Cd))))
13 //f1    = 1/((2*math.pi)*(math.sqrt(L*(C2+Cd))))
14 //f2    = 3*f1
15 Cd      = (C1-(9*C2))/(8);           //self capacitance
      of the coil in pF
16
17 //result
18 mprintf("self capacitance of the coil = %3.2 f pF",Cd
      );

```

Scilab code Exa 12.27 Determine the effective inductance and resistance of unknown

```

1 //


---


2 //Chapter 12 example 27
3
4 clc;clear all;
5
6 //variable declaration
7 f      = 450*10^3;           //resistance inHz
8 C      = 250*10^-12;        //capcaitance in F
9 Rsh    = 0.75;              //resistance in
10 Q      = 105;               //Q-factor
11
12 //calculations
13 w      = 2*(%pi)*f;
14 L      = 1/(((w)^2)*(C));    //inductance in uH
15 R      = ((w*L)/(Q))-Rsh;    //resistance of the
      coil in
16
17 //result
18 mprintf("inductance = %3.2 f uH", (L*10^6));

```



```

19
20 mprintf(" \n resistance of the coil = %3.2 f ",R);

```

Scilab code Exa 12.28 Determine the percentage error

```

1 //


---


2 //Chapter 12 example 28
3
4 clc; clear all;
5
6 //variable declaration
7 f      = 500*103;           //resistance inHz
8 C      = 120*10-12;        //capcaitance in F
9 R      = 5;                 //resistance in
10 r     = 0.02;              //resistance across oscilltory
    circuit in
11
12 //calculations
13 w      = 2*(%pi)*f;
14 Qt     = 1/(w*C*R);         //the true or effective Q of
    the coil
15 Qi     = 1/(w*C*(R+r));     //the indicated or
    calculated Q of the coil
16 e      = ((Qt-Qi)/(Qt))*100; //percentage error in %
17
18 //result
19 mprintf(" percentage error =%3.2 f percentage ",e);

```

Scilab code Exa 12.29 Determine the self capacitance

```

1 //


---


2 //Chapter 12 example 29
3
4 clc;clear all;
5
6 //variable declaration
7 C1      = 95*10^-12;      //capacitance in F
8 f1      = 800*10^3;      //frequency in Hz
9 f2      = 2.5*10^6;      //frequency in Hz
10
11 //calculations
12 w2      = 2*%pi*f;
13 L       = 1/((w2)^2)*Cd;
14 L       = 1/((w2)^2)*(C1+Cd)
15 //comparing above equations
16 // Cd    =(((w1)**2)*C1)/(((w2)**2)-(w1)**2))
17 Cd      =(((f1)^2)*C1)/(((f2)^2)-((f1)^2));      //
           capacitance in pF
18
19 //result
20 mprintf("capacitance = %3.2f pF", (Cd*10^12));

```

Scilab code Exa 12.30 Determine the self capacitance

```

1 //


---


2 //Chapter 12 example 30
3
4 clc;clear all;
5
6 //variable declaration
7 f1      = 1*10^6;      //frequency in Hz

```

```

8 f2    = 2*10^6;           //frequency in Hz
9 C1    = 480*10^-12;     //capacitance in F
10 C2   = 90*10^-12;      //capacitance in F
11 R    = 10;             //resistance
12
13 //calculations
14 Cd    = (C1-(4*C2))/3;   //self capacitance of
    the coil in pF
15 Q1    = 1/(2*pi*f1*(C1+Cd)*R); //the
    indicated or effective Q of the coil
16 Q11   = 1/(2*pi*f1*(C1)*R); //the true Q
    of the first instrument
17 Q2    = 1/(2*(%pi)*f2*(C2+Cd)*R); //the
    indicated or effective Q for the second
    instrument
18 Q22   = 1/(2*(%pi)*f2*(C2)*R); //the true
    Q of the second instrument
19
20 //result
21 mprintf("the indicated or effective Q of the coil
    = %3.1 f ",Q1);
22 mprintf("\nthe true Q of the first instrument = %3
    .3 f",Q11);
23 mprintf("\nthe indicated or effective Q for the
    second instrument = %3.3 f",Q2);
24 mprintf("\nthe true Q of the second instrument =
    %3.2 f",Q22);

```

Chapter 13

Magnetic measurements

Scilab code Exa 13.1 Find the magnetic field strength

```
1 //


---


2 //Chapter 13 example 1
3
4 clc;clear all;
5
6 //variable declaration
7 l = 0.6; //length of solenoid in m
8 N = 600; //number of turns
9 I = 2; //current passing through solenoid in
  A
10 ur = 1; //air coiled solenoid
11 r = 0.025; //radius in m
12
13 //calculations
14 H = (N*I)/(l); //magnetic field at the centre
  in AT/metre
15 u0 = 4*(%pi)*(10^-7); //flux
16 a = ((%pi)/(4))*(r^2); //area
17 phi = ur*u0*H*a; //flux passing through
```

```

    thesecondary coil
18
19 //calculations
20 mprintf("magnetic field = %3.2f AT/metre",H);
21 mprintf("flux = %3.2e Wb",phi);

```

Scilab code Exa 13.2 Find the constant of the galvanometer

```

1 //


---


2 //Chapter 13 example 2
3 clc;clear all;
4
5 //variable declaration
6 m = 100; //number of turns
7 n = 1000; //turns per m
8 theta1 = 10; //first throw in mm
9 theta2 = 9.5; //second throw in mm
10 I = 10; //current in A
11 R = 500; // resistance in
12 A = 0.002; //area in m**2
13
14 //calculations
15 //Q = (8*(math.pi)*(10**-7)*N*Ns*I*A)/(l*R)
//in columbs
16 //Q = (8*(math.pi)*(10**-7)*n*l*m*I*A)/(l*R)
17 //Q = (8*(math.pi)*(10**-7)*n*m*I*A)/(R)
18 lamda = log(theta1/(theta2));
19 theta = theta1*(1+(lamda/(2)));
20 K = (8*(%pi)*(10^-7)*n*m*I*A)/(R*theta); //
galvanometer constant in C/mm
21
22 //result
23

```

```
24 mprintf("galvanometer constant = %3.2e C/mm",K);
```

Scilab code Exa 13.4 Find the capacity of the condenser

```
1 //  
  
2 //Chapter 13 example 4  
3  
4  
5 clc;clear all;  
6  
7 //variable declaration  
8 T0 = 4; //time of swing in seconds  
9 Ig = 0.001; //current in A  
10 lamda = 0;  
11 theta = 50; //steady deflection in scale  
    divisions  
12 theta1 = 220; //maximum throw in scale division  
13 V = 100; //potential of the condenser in V  
14  
15 //calculations  
16 Q = (T0/(2*%pi))*(Ig/theta)*(1+(lamda/2))*theta1;  
    //quantity of electricity discharged in uC  
17 C = Q/(V); //capacity of the condenser in F  
18  
19 //result  
20 mprintf("capacity of the condenser = %3.2d uF", (C  
    *10^6));
```

Scilab code Exa 13.5 Calculate the shunt required for the use with search coil

```

1 //


---


2 //Chapter 13 example 5
3 clc;clear all;
4
5 //variable declaration
6 N      = 1;      //number of turns on search coil
7 Rc     = 0.025;  //resistance of search coil in
8 Nw    = 1.5*10^-4; //number of wb-turns required
           for deflection of 1 division
9 M      = 120000; //reluctance of magnetic circuit
10 MMF   = 8000;  //magnetic circuit is excited in
           ampere-turn
11 f     = 1.5*10^-4; //fluxmeter without shunt (K
           /N = phi/theta)
12 theta =120;
13
14 //calculations
15 phi   = (MMF/(M)); //flux produced in WB
16 //phi = ((Rs+Rc)/Rs)*((K*theta)/N)
17 Rs    = (Rc*f*theta)/(phi-(f*theta)); //
           resistance of shunt in
18
19 //result
20 mprintf("resistance of shunt = %3.2e ",Rs);

```

Scilab code Exa 13.6 Find the resistance of the shunt to be connected in parallel

```

1 //


---


2 //Chapter 13 example 6
3
4 clc;clear all;

```

```

5
6 //variable declaration
7 Rc = 1; //resistance in
8 N = 5; //multiplying factor
9
10 //calculations
11 //N = (Rs+Rc)/Rs
12 Rs = Rc/(N-1); //shunt resistance in
13
14 //result
15 mprintf("shunt resistance = %3.2f ",Rs);

```

Scilab code Exa 13.7 Calculate the flux density in the core

```

1 //


---


2 //Chapter 13 example 7
3
4 clc;clear all;
5
6 //variable declaration
7 R1 = 180; //resistance in
8 R2 = 20; //resistance in
9 A = 0.005; //area in m^2
10 Ns = 1000; //number of turns on search coil
11 G1 = 100*10^-6; //galvanometer constant C
12 G2 = 100; //galvanometer throw
13
14 //calculations
15 Rs = R1+R2; //total resistance of secondary
    circuit in
16 Q = G1*G2; //charge passed through ballistic
    galvanometer in C
17 //Q = i*t = (E/Rs)*t = ((2*phi*Ns)/(t*Rs))*t =

```



```

    (2*phi*Ns)/Rs
18 phi = (Q*Rs)/(2*Ns); //flux in Wb
19 B = phi/(A); //flux density in Wb/m^2
20
21 //result
22
23 mprintf("flux density = %3.2f Wb/m^2",B);

```

Scilab code Exa 13.8 Find the relative permeability of the specimen

```

1 //


---


2 //Chapter 13 example 8
3
4 clc;clear all;
5
6 //variable declaration
7 d = 0.1; //diameter in m
8 a = 33.5*10^-6; //cross sectional area of iron
   ring in m^2
9 Ns = 220; //number of turns on secondary
   coil
10 Nm = 320; //number of turns on magnetising
   winding
11 I = 10; //current in A
12 B = 2.5*10^-3; //flux in Wb
13 n = 102; //reading of scale
14 g = 272; //galvanometer throw
15
16
17 //calculations
18 l = (%pi)*d; //mean length of iron ring in m
19 H = (Nm*I)/(l); //magnetising force with 10 A
   current

```

```

20 K      = B/(n);
21 //2*phi*Ns = K*g
22 phi     = (K*g)/(2*Ns); //flux in Wb
23 B1      = phi/(a); //flux density in Wb/m**2
24 u0      = 4*%pi*10^-7;
25 //B     = u0*ur*H
26 x       = u0*H;
27 //B     = x*ur
28 //ur    = B/x
29 ur      = B1/x; //relative permeability
30
31 //result
32 mprintf("relative permeability = %3.1f",ur);

```

Scilab code Exa 13.9 Compute the flux density and relative permeability

```

1 //


---


2 //Chapter 13 example 9
3 clc;clear all;
4
5 //variable declaration
6 R = 2000; //resistance in
7 l = 1; //mean length of iron ring in m
8 A = 350*10^-6; //area in m**2
9 Ns = 200; //number of turns on secondary
   coil
10 G1 = 1*10^-6; //galvanometer constant C
11 G2 = 100; //galvanometer throw
12 N = 100;
13
14 //calculations
15 u0 = 4*(%pi)*10^-7;
16 H = (N*I)/(l); //magnetising force with 10 A

```

```

    current
17 Q      = G1*G2;      //charge passed through ballistic
    galvanometer in C
18 //Q = i*t = (E/Rs)*t = ((2*phi*Ns)/(t*Rs))*t =
    (2*phi*Ns)/Rs
19 phi    = (Q*R)/(2*Ns);    //flux in Wb
20 B      = phi/(A);        //flux density in Wb/m**2
21 ur     = (B/(u0*H));     //relative permeability
22
23 //result
24 mprintf("flux density = %3.3f Wb/m**2",B);
25 mprintf("\nrelative permeability = %3.0f",ur);

```

Scilab code Exa 13.10 Calculate the relative permeability

```

1 //


---


2 //Chapter 13 example 10
3
4 clc;clear all;
5
6 //variable declaration
7 d      = 0.3;      //diameter in m
8 a      = 4*10^-4;  //cross sectional area of iron
    ring in m**2
9 N      = 80;      //number of turns on magnetising
    coil
10 Ns     = 30;      //number of turns on secondary coil
11 F      = 0.1*10^-3; //flux meter constant in Wb-
    turn
12 D      = 46;      //deflection factor
13 I      = 2;      //current in A
14
15 //calculations

```

```

16 //phi = (N*I*u0*ur*a)/l
17 // phi = x*l
18 //lat x = (N*I*u0*a)/l
19 l = d*pi;
20 u0 = 4*(%pi)*10^-7;
21 x = (N*I*u0*a)/(l);
22 // total change in Wb-turns y = 2*phi*Ns = 2*x*ur*Ns
23 y = 2*x*Ns;
24 df = F*D; //change in flux measured by the flux
meter in wb-turns
25 ur = df/y; //relative permeability
26
27 //result
28 mprintf("relative permeability = %3.0d",ur);
29 mprintf("\n Note: textbook answer represents the
approximate value")

```

Scilab code Exa 13.11 Find the quantity of the electricity

```

1 //


---


2 //Chapter 13 example 13
3
4 clc;clear all;
5
6 //variable declaration
7 Q = 1000; //Charge passed through
galvanometer in uC
8 theta1 = 60;
9 d = 10; //defelction in mm
10 r = 1000; //m=circular scale
11
12 //calculations
13 theta2 = %pi/(3) //conversion of degrees to

```

```

        radians
14 K    = Q/(theta2);    //galvanometer constant in uC/
        radian
15 theta = d/(2*r);    //angle turned through by
        reflected ray for aswing of 10 mm
16 Q1    = K*theta;    //charge for a swing of
        0.005 radian in uC
17
18 //result
19 mprintf("charge for a swing of 0.005 radian = %3.2f
        uC",Q1);

```

Scilab code Exa 13.12 Calculate the hysteresis loss in watts per kg

```

1 //


---


2 //Chapter 13 example 12
3
4 clc;clear all;
5
6 //variable declaration
7 f    = 50;    //number of reversals
8 m    = 1;    //mass
9 d    = 7.8*10**3;    //density
10 A    = 4800;    //area of the loop m^3
11 x    = 200;    //in AT/m
12 x1   = 10;    // 1 unit in mm
13 y1   = 10;    // 1 unit in mm
14 y    = 0.1;    //in T
15
16 //claculations
17 V    = m/d;    //volume of magnetic
        material in m^3
18 l    = A*(x/x1)*(y/y1);

```

```

19 l1    = l*v*f;           //hysteresis loss in
    watts per kg at 50 Hz
20
21 //result
22 mprintf("hysteresis loss at 50 Hz = %3.3f  watts per
    kg ",l1);

```

Scilab code Exa 13.13 At what frequency will the iron loss be doubled if the flux

```

1  clc;
2  clear all;
3
4  //variable declaration
5  f    = 60;           //supply frequency in Hz
6  Pi   = 360;         //iron loss in W
7  f    = 60;
8  //Pe   =6*Ph;
9  //Pi   = Pe+Ph
10 //360= (6*Ph)+Ph
11 Ph   = Pi/7;       //hysteresis loss in W
12 Pe   = Pi-Ph;     //eddy current loss in W
13 //Ph1   = (f1/f)*Ph
14 Ph1  = (1/f)*Pe;   //hysteresis loss in watts
15 //Ph1   =Ph1*f1
16 //Pe1   = ((f1/f)^2)*Pe
17 Pe1  =((1/f)^2)*Pe; //eddy current loss
18 //Pe1   = Pe1*Pe
19 Pi1  =Ph1+Pe1;
20 Pi1  = 2*Pi;
21 //720   = 0.857*f1+(0.0857*f1^2)
22 f1    =86.8
23
24
25 //result
26 mprintf("new supplyfrequency = %3.2 f HZ" ,f1);

```

Scilab code Exa 13.14 Estimate the hysteresis and eddy current losses

```
1 //
2 //Chapter 13 example 14
3
4 clc;
5 clear all;
6
7 //variable declaration
8 //Ph = A*f
9 //Pe = B*f^2
10 //Pi = Ph+Pe
11 Pi = 17.2; //power in W
12 f = 50; //frequency in Hz
13 Pi1 = 28.9; //iron loss in W
14
15 m = 13; //weight in kg
16
17 //calculations
18 //17.2 = 40*A+((40)^2)*B
19 //28.9 = 60*A+((60)^2)*B
20 A = 0.326667
21 B = 0.002583
22 Ph = (A*f)/m //hysteresis loss per kg in W
23 Pe = (B*(f^2))/m //eddy current loss per kg in W
24
25 //result
26 mprintf("hysteresis loss per kg = %3.2 f W",Ph);
27 mprintf("\neddy current loss per kg = %3.3 f W",Pe);
```

Scilab code Exa 13.15 Calculate the eddy current loss per kg

```
1 //


---



---


2 //Chapter 13 example 15
3 clc;
4 clear all;
5
6 //variable declaration
7 A = 0.5;
8 B = 0.01;
9 f = 50;
10 n = 10;
11
12 //calculations
13 Pe = B*(f^2); //eddy current loss at 50 Hz in
    W
14 Pe1 = Pe/n; //eddy current loss per kg at 50 Hz
    in watts
15
16 //result
17 mprintf("eddy current loss per kg at 50 Hz = %3.2 f
    watts",Pe1);
```

Scilab code Exa 13.16 Calculate the percentage change in hysteresis loss

```
1 //


---



---


2 //Chapter 13 example 16
3
4 clc;
5 clear all;
6
```



```

7 //variable declaration
8 x   = 0.8;           //Kf2/Kf1
9 y   =1.2;
10
11 //Pe2/Pe1 = (Kf2/Kf1)^2
12 p   = x^2;
13 //Pe2   = p*Pe1;    //
14 //p1    = (Pe1-Pe2)/Pe1;
15 p1  = (1-p)*100;    //percentage change in
    hysteresis current loss
16 p2  = y^2;
17 p12 = (y-1)*100;   //percentage change in
    hysteresis current loss
18 p3  = (p2-1)*100;  //percentage change in eddy
    current loss in %
19
20 //result
21 mprintf("percentage change in hysteresis current
    loss = %3.3f percentage decrease",p1);
22 mprintf("\npercentage change in hysteresis current
    loss = %3.3f percentage increase",p12);
23 mprintf("\npercentage change in eddy current loss in
    = %3.2f percentage increase",p3);

```

Scilab code Exa 13.17 Calculate the iron in watts loss per kg

```

1 //


---


2 //Chapter 13 example 17
3
4 clc;
5 clear all;
6
7 //variable declaration

```

```

8 w = 0.03; //width of plates in m
9 n = 51; //number of plates
10 t = 0.000489; //thickness in m^3
11 f = 50; //frequency in Hz
12 Bmax = 1;
13 N = 600;
14 P1 = 3; //copper loss in watts
15 m = 11; //weight in kg
16
17 //calculations
18 A = w*n*t; //mean area of plates in m^3
19 E = 4.44*f*Bmax*A*N; //induced voltage in V
20 //from graph corresponding to voltage of 100 volts
21 P2 = 30.5; //total losses in watts
22 P = P2-P1; //iron loss in watts
23 PL = P/m; //loss per kg in watts
24
25 //result
26 mprintf("iron loss per kg = %3.2f watts",PL);

```

Chapter 14

Digital Measurement of Electrical Quantities

Scilab code Exa 14.1 Determine the full scale output

```
1 //


---


2 //Chapter 14 example 1
3 clc;
4 clear all;
5
6 //variable declaration
7 VREF =10; //reference voltage in V
8
9
10 //calculations
11 W1 = VREF/2; //the second MSB weight in V
12 W2 = VREF/4; //the third MSB weight in V
13 W3 = VREF/8 //the fourth (or LSB ) MSB
    weight in V
14 W = VREF+W1+W2+W3; //full scale output in
    V
15 r = W/4; //resolution in V
```

```

16
17 //result
18 mprintf("the second MSB weight =%3.2d",W1);
19 mprintf("\nthe third MSB weight =%3.2d",W2);
20 mprintf("\nthe fourth (or LSB ) weight =%3.2d",W3);
21 mprintf("\nthe resolution of DAC is equal to the
    weight of the LSB = %3.2f V",W3);
22 mprintf("\nfull scale output = %3.2f V",r);

```

Scilab code Exa 14.2 Find out the voltage

```

1 //


---


2 //Chapter 14 example 2
3
4 clc;
5 clear all;
6
7 //variable declaration
8 D      = 16;           //output voltage in V
9
10 //calculations
11 Dn1    = D/(2^1);     //first MSB output in
    V
12 Dn2    = D/(2^2);     //second MSB output in
    V
13 Dn3    = D/(2^3);     //third MSB output in
    V
14 Dn4    = D/(2^4);     //fourth MSB output in
    V
15 Dn5    = D/(2^5);     //fifth MSB output in
    V
16 Dn6    = D/(2^6);     //Sixth MSB output in
    V

```

```

17 V          = Dn1+Dn2+Dn3+Dn4+Dn5+Dn6;
18 Vout       = ((D*(2^0))+(D*(2^1))+(0*(2^2))+(D
    *(2^3))+(0*(2^4))+(D*(2^5)))/(2^6);          //for
    digital input 101011
19
20 //result
21 mprintf(" first MSB output = %3.2f V",Dn1);
22 mprintf("\n second MSB output = %3.2f V",Dn2);
23 mprintf("\n third MSB output = %3.2f V",Dn3);
24 mprintf("\n fourth MSB output = %3.2f V",Dn4);
25 mprintf("\n fifth MSB output = %3.2f V",Dn5);
26 mprintf("\n Sixth MSB output = %3.2f V",Dn6);
27 mprintf("\nthe resolution is equal to the weight of
    the LSB = %3.2f V",Dn6);
28 mprintf("\nthe full scale output for digital input
    of 101011 =%3.2f V",V);
29 mprintf("\nthe voltage output for a digital input of
    101011 = %3.2f V",Vout);

```

Scilab code Exa 14.3 Determine the display indication

```

1 //


---


2 //Chapter 14 example 3
3
4 clc;
5 clear all;
6
7 //variable declaration
8
9 T = 2500;          //transitions per second
10 t1 = 0.1;         //time in s
11 t2 = 1;           //time in s
12 t3 = 10;          //time in s

```

```

13
14 //calculations
15 C1      = T*t1;          //counter can count or
      display
16 C2      = T*t2;          //counter can count or
      display
17 C3      = T*t3;          //counter can count or
      display
18
19 //result
20 mprintf(" counter can count or display when 0.1 s =
      %3.2d",C1);
21 mprintf(" \ncounter can count or display when 1 s =
      %3.2d",C2);
22 mprintf(" \ncounter can count or display when 10 s =
      %3.2d",C3);

```

Scilab code Exa 14.4 Calculate the frequency of the system

```

1 //


---


2 //Chapter 14 example 4
3 clc;
4 clear al;
5
6 //variable declaration
7 N      = 45;          //count
8 t      = 0.01;       //gate enable time in s
9
10 //calculations
11 f      = N/t;        //frequency in Hz
12
13 //result
14 mprintf(" frequency = %3.1 f kHz" ,(f*10^-3));

```

Scilab code Exa 14.5 Find the maximum likely errors

```
1 //
2 //Chapter 14 example 5
3 clc;
4 clear all;
5
6 //variable declaration
7 t      = 5*10^6;    //time readding in ms
8 t2     = 500;     //time readding in ms
9 x      = 0.005;    //accuracy in percent of
    reading
10 t3     = 500*10^3; //time readding in ms
11
12 //calculations
13 e      = ((x/100)*t)+1; //maximum likely
    timing error in ms
14 e1     = ((x/100)*t2)+1; //maximum timing
    error in ms
15 a      = t2*10^6;    //maximum accuracy
    mininum error will be obtained when the time is
    read on the us read
16 e3     = ((x/100)*t3)+1; //maximum timing
    error in ms
17
18 //result
19 mprintf("maximum likely timing error when time
    reading is 05000000 ms = %3.2f ms",e);
20 mprintf("\nmaximum timing error when time reading
    is 00000500 ms = %3.2f ms",e1);
21 mprintf("\nmaximum error when time reading is
    00500000 = %3.2f ms",e3);
```

Scilab code Exa 14.6 Calculate the resolution

```
1 //
2 //Chapter 14 example 6
3
4 clc;
5 clear all;
6
7 //variable declaration
8 n =3; //number of full digits
9 v1 = 1; //voltage in V
10 v2 = 10; //voltage in V
11 v3 = 5; //voltage in V
12 a = 0.5; //accuracy of reading in %
13 r = 2; //reading in V
14
15 //calculations
16 R = 1/(10^n); //resolution
17 V1 = R*v1; //for full scale range of 1V ,
    the resolution in V
18 V2 = R*v2; //for full scale range of 10V ,
    the resolution in V
19 v = v3*R; //the digit in least significant
    digit has a value of in V
20 e = ((a/100)*r)+v; //total possible error
    on in V
21
22 //result
23 mprintf("for full scale range of 1V ,the resolution
    = %3.4f V",V1);
24 mprintf("\nfor full scale range of 10V ,the
    resolution = %3.4f V",V2);
```



```
25 mprintf("\ntotal possible error = %3.5f V",e);
```

Scilab code Exa 14.7 Find the resolution

```
1 //


---



---

  
2 //Chapter 14 example 7  
3 clc;  
4 clear all;  
5  
6 //variable declaration  
7 n =4; //number of full digits  
8 v1 = 1; //voltage in V  
9 v2 = 10; //voltage in V  
10  
11 //calculations  
12 R = 1/(10^n); //resolution  
13 R1 = R*v1; //resolution on 1V range in V  
14 R2 = R*v2; //resolution on 10V range in V  
15  
16 //result  
17 mprintf("R = %3.4f V",R);  
18  
19 mprintf("\nthere are 5 digits in 4 (1/2) display  
 digit display ,so 15.84 would display as 15.840")  
 ;  
20 mprintf("\nR1 = %3.4f V",R1);  
21 mprintf("\nmany reading upto 4 th decimal can be  
 displayed ");  
22 mprintf("\nhence 0.5243 can be displayed as 0.5243")  
23 mprintf("\n R2 = %3.4f V",R2);  
24 mprintf("\nmany reading upto third decimal can be  
 displayed ");  
25 mprintf("\nhence 0.5243 can be displayed as 0.524
```

instead of 0.5243”);

Scilab code Exa 14.8 Find the resolution

```
1 //
2 //Chapter 14 example 8
3
4 clc;
5 clear all;
6
7 //variable declaration
8 n =3;           //number of full digits
9 v1 = 10;        //voltage in V
10 v2 = 100;      //voltage in V
11
12 //calculations
13 R = 1/(10^n);  //resolution
14 R1 = R*v1;     //resolution on 1V range in V
15 R2 = R*v2;     //resolution on 10V range in V
16
17 //result
18 mprintf("R = %3.4 f V",R);
19
20 mprintf("\nthe meter cannot distinguish the values
    that differ from each by less than 0.001 of full
    scale");
21 mprintf("\nR1 = %3.4 f V",R1);
22 mprintf("\nany decimal upto second decimal can be
    displayed ");
23 mprintf("\nhence 15.45 can be displayed as 15.45")
24 mprintf("\n R2 = %3.4 f V",R2);
25 mprintf("\nany deccimal upto one decimal can be
    displayed ");
```

```
26 mprintf("\nhence 25.65 can be displayed as 025.6
    instead of 25.65");
```

Scilab code Exa 14.9 Find the resolution

```
1 //
2 //Chapter 14 example 9
3
4 clc;
5 clear all;
6
7 //variable declaration
8 n =4; //number of full digits
9 v1 = 10; //voltage in V
10 V1 = 1; //voltage in V
11 V2 =10; //voltage in V
12
13 //calculations
14 R = 1/(10^n); //resolution
15 R1 = R*v1; //resolution on 1V range in V
16 R2 = R*V1; //resolution on 1V range in V
    for display 0.6132 V
17 R3 = R*V2; //resolution on 10V range in V
    for display 0.6132 V
18
19 //result
20 mprintf("R = %3.4 f V",R);
21 mprintf("\nR1 = %3.4 f V",R1);
22 mprintf("\nmany decimal upto third decimal can be
    displayed ");
23 mprintf("\nhence 13.97 can be displayed as 13.970")
24 mprintf("\n R2 = %3.4 f V",R2);
25 mprintf("\nmany deccimal upto fourth decimal can be
```

```
    displayed on 1V");
26 mprintf("\\nhence 0.6132 can be displayed as 0.6132 V"
    );
27 mprintf("\\n R3 = %3.4f V",R3);
28 mprintf("\\nany deccimal upto third decimal can be
    displayed on 10 V ");
29 mprintf("\\nhence 0.6132 can be displayed as 0.613 V")
    ;
```

Chapter 15

Signal Analyzers

Scilab code Exa 15.1 Find the dynamic range

```
1 //  


---

  
2 //Chapter 15 example 1  
3 clc; clear all;  
4  
5 //variable declaration  
6 Ip    = 25;           //power level ot the third-order  
    intercept in dBm  
7 M     = -85;         //minimum detectable signal in  
    dBm  
8  
9 //calculations  
10 Rd   = (2/3)*(Ip-M);  
11  
12 //result  
13 mprintf("dynamic range = %3.0 f dB",Rd);
```

Scilab code Exa 15.2 Find the minimum detectable signal of a spectrum

```

1 //


---


2 //Chapter 15 example 2
3
4 clc;clear all;
5
6 //variable decalaration
7 N      = 20;           //noise figure indB
8 B      = 1000;        //bandwidth in Hz
9
10 //calculations
11 x      = B/(10^6);
12 //log(10**-3)= (-3)*log(1) = -3
13 M      = (-114)+((10*(-3))*(1))+N;    //log(1) = 1
14
15 //result
16 mprintf("minimum detectable signal = %3.2f dBm",M);

```

Chapter 16

Cathode Ray Oscilloscope

Scilab code Exa 16.1 Find the rms value and also the electrostatic deflection sens

```
1 //


---


2 //Chapter 16 example 1
3
4
5 clc; clear all;
6
7 //variable declaration
8 l = 0.025; //length of plates in m
9 d = 0.005; //distance between plates in m
10 S = 0.2; //the distance between the screen
    and centre of plates in m
11 Va =3000; //accelerating voltage in V
12 x =0.1; //trace length(2*y) in m
13
14
15 //cacualtions
16 //y = lSv/(2*d*Va)
17 Vd = (d*Va*x)/(l*S); //deflection voltgae in V
18 Vrms = Vd/(sqrt(2)); //rms value of sinusoidal
```

```

    voltage applied to the X-deflecting plates in V
19 Sd      = (1*S)/(2*d*Va);      //deflection voltage
    in mm/V
20
21 //result
22 mprintf("rms value of sinusoidal voltage applied to
    the X-deflecting plates = %3.2d V",Vrms);
23 mprintf("\ndeflection sensitivity = %3.3f mm/V", (Sd
    *10**3));

```

Scilab code Exa 16.2 Find the input voltage

```

1 //


---


2 //Chapter 16 example 2
3
4 clc;clear all;
5
6 //variable declaration
7 l      = 0.02;    //length of plates in m
8 d      = 0.005;   //distance between plates in m
9 S      = 0.3;     //the distance between the screen
    and centre of plates in m
10 Va    =2000;     //accelerating voltage in V
11 Y     =0.03;     //trace length in m
12
13
14 //cacualtions
15 //y    = lSv/(2*d*Va)
16 Vd    = (d*Va*x)/(1*S); //deflection voltgae in V
17 Vrms  = Vd/(sqrt(2)); //rms value of sinusoidal
    voltage applied to the X-deflecting plates in V
18 Vin  = Vrms/(Vd); //input voltage required in V
19

```



```

20 //result
21 mprintf(" nput voltage required = %3.3f V",Vin);

```

Scilab code Exa 16.3 Calculate the maximum velocity of electrons

```

1 //


---


2 //Chapter 16 example 3
3
4 clc;clear all;
5
6 //variable declaration
7 Va = 1000; //accelerating voltage in V
8 e = 1.6*10^-19; //charge of electron in C
9 m = 9.1*10^-31; //mass of electron in kg
10
11
12 //calcuations
13 V = sqrt(2*Va*(e/m)); //maximum velocity of
    electrons in m/s
14
15 //result
16 mprintf("maximum velocity of electrons = %3.3e m/s",
    V);

```

Scilab code Exa 16.4 Find the beam speed and deflection sensitivity of the tube an

```

1 //


---


2 //Chapter 16 example 4
3

```

```

4  clc;clear all;
5
6  //variable declaration
7  Va  = 2000;    //accelerating voltage in V
8  e    = 1.6*10^-19;    //charge of electron in C
9  m    = 9.1*10^-31;    //mass of electron in kg
10 l    = 0.015;    //length of plates in m
11 d    = 0.005;    //distance between plates in m
12 S    = 0.5;    //the distance between the screen
    and centre of plates in m
13
14 //calcuations
15 V    = sqrt(2*Va*(e/m));    //beam speed in m/s
16 Sd    = (1*S)/(2*d*Va);    //deflection
    sensitivity of the tube in mm/V
17 D    = 1/(Sd);    //deflection factor in V
    /mm
18
19 //result
20 mprintf("Beam speed = %3.3e m/s",V);
21 mprintf("\ndeflection sensitivity of the tube %3.3f
    mm/V", (Sd*10^3));
22 mprintf("\ndeflection factor = %3.4f V/mm", (D
    *10^-3));

```

Scilab code Exa 16.5 Determine the deflection sensitivity

```

1  //


---


2  //Chapter 16 example 5
3
4  clc;clear all;
5
6  //variable declaration

```

```

7 l      = 0.02;    //length of plates in m
8 d      = 0.005;  //distance between plates in m
9 S      = 0.2;    //the distance between the screen
                and centre of plates in m
10 Va    = 2500;   //accelerating voltage in V
11
12 //calculations
13 Sd     = (l*S)/(2*d*Va); //deflection
                sensitivity of the tube in mm/V
14
15 //result
16 mprintf("deflection sensitivity of the tube %3.2f mm
            /V", (Sd*10^3));

```

Scilab code Exa 16.6 Deduce the formula used

```

1 //


---


2 //Chapter 16 example 6
3
4 clc;clear all;
5
6 //variable declaration
7 l      = 2.5;    //length of plates in cm
8 d      = 1;     //distance between plates in cm
9 theta  = 1;     //angular defelecction of electron
                beam in degrees
10 Va    = 1000;  //accelerating voltage in V
11
12 //calculations
13 //tan(theta) = l*Vd/(2*d*Va)
14 x      = tan(((theta*%pi)/180));
15 Vd     =(( 2*d*Va)/(l))*x; //required voltage in
                V

```

```

16
17 //result
18 mprintf(" Voltage required across the deflection
    plates = %3.2f V",Vd);

```

Scilab code Exa 16.7 Calculate the deflection voltage

```

1 //


---


2 //Chapter 16 example 7
3
4 clc;clear all;
5
6 //variable declaartion
7 l    = 0.025;    //length of plates in m
8 d    = 0.005;    //distance between plates in m
9 S    = 0.2;      //the distance between the screen
    and centre of plates in m
10 Va   = 2500;    //accelerating voltage in V
11
12 //calculations
13 //y    = (s*(d/2))/(l/2)
14 y    = (S*d)/(l);    //defelction in m
15
16 //result
17 mprintf(" deflection= %3.2f m",y);

```

Scilab code Exa 16.8 Find the Phase angle

```

1 //


---



```

```

2 //Chapter 16 example 8
3
4 clc;clear all;
5
6 //variable declaration
7 //as shown in pattern is straight line
8 dvo = 0;
9 Dv = 6;
10 //pattern is ellipse
11 dvo1 = 3;
12 Dv1 =6;
13 //pattern is circle
14 dvo2 = 1;
15 Dv2 = 1;
16 //pattern is ellipse
17 dvo3 = 3;
18 Dv3 =5;
19
20 //calculations
21 y4 =dvo1/(Dv1);
22 phi1 = asin(dvo/(Dv)); //phase angle in degrees
23 phi2 = asin(dvo1/(Dv1)); //phase angle in
    degrees
24 phi3 = asin(dvo2/(Dv2)); //phase angle in
    degrees
25 phi4 = asin(dvo3/(Dv3)); //phase angle in
    degrees
26 phi22 = 180-((phi2*180)/(%pi));
27 phi44 = 180-((phi4*180)/(%pi));
28
29 //result
30
31 mprintf("phase angle = %3.2f ",((phi1*180)/%pi));
32 mprintf(" \nphase angle = %3.2f or %3.2f ",((
    phi2*180)/%pi),(phi22));
33 mprintf(" \nbut from figure ellipse is inn 2nd and
    fourt quarterso the valid value of phase angle is
    %3.2f ",phi2);

```

```

34 mprintf(" \nphase angle = %3.2 f      ",((phi3*180)/(%pi)
    ));
35 mprintf(" \nphase angle = %3.2 f      or %3.2 f      ",(((
    phi4*180)/%pi)),(phi4));
36 mprintf(" \nbut from figure ellipse is inn 2nd and
    fourt quarterso the valid value of phase angle is
    %3.2 f      ",phi4);

```

Scilab code Exa 16.9 Find the pulse duration

```

1 //


---


2 //Chapter 16 example 9
3 clc;clear all;
4
5 //variable declaration
6 f      = 2000;      //frequency in Hz
7 D      = 0.2;      //duty cycle
8
9 //calculations
10 T     = 1/(f);     //time period in ms
11 d     = D*T;      //pulse duration in ms
12
13 //result
14 mprintf(" pulse duration = %3.2 f ms", (d*10^3));

```

Scilab code Exa 16.10 Find the ratio of frequencies of vertical and horizontal sig

```

1 //


---


2 //Chapter 16 example 10

```

```

3
4 clc;clear all;
5
6 //variable declartion
7 wy      = 3;      //positive Y-axis in pattern
8 wx      = 2;      //positive X-axis in pattern
9
10 //calculations
11 f      =wy/(wx);  //frequency of vertical and
    horizontal signal
12
13 //result
14 mprintf("frequency of vertical and horizontal signal
    = %3.1f",f);

```

Scilab code Exa 16.11 Find out the frequency of vertical signal

```

1 //


---


2 //Chapter 16 example 11
3
4 clc;clear all;
5
6 //variable declaration
7 y1      = 2;      //positive y- peaks in pattern
8 y2      = 0.5;    //positive y-peaks in pattern
9 x1      = 0.5;    //positive x-peaks in pattern
10 x2      = 0.5;    //positive x-peaks in pattern
11 F       = 3;      //frequency of horizontal voltage
    signal in kHz
12
13 //calculations
14 fx      = x1+x2;  //frequency of X
15 fy      = y1+y2;  //frequency of Y

```

```

16 f      = fy/(fx);
17 fv     = f*F;      //frequency of vertical voltage
    signal in kHz
18
19 //Result
20 mprintf("frequency of vertical voltage signal in =
    %3.1 f kHz",fv);

```

Scilab code Exa 16.12 Determine the frequency of vertical input

```

1 //


---


2 //Chapter 16 example 12
3 clc;clear all;
4
5 //variable declaration
6 fx     = 1000;     //frequency of horizontal input in
    Hz
7 Pv     = 2;       //pointsof tangency to vertical line
8 Ph     = 5;       //pointsof tangency to horizontal
    line
9
10 //calculations
11 fy     = fx*(Ph/(Pv)); //frequency ofvertical
    input in Hz
12
13 //result
14 mprintf("frequency ofvertical input = %3.2 f Hz",fy);

```

Scilab code Exa 16.13 Determine the mark to space ratio of the pulse


```

1 //


---


2 //Chapter 16 example 13
3
4 clc;clear all;
5
6 //variable declaration
7 d = 1; //1 division is equal to 1 cm
8 M = 0.4; //mark in cm
9 S = 1.6; //mark in cm
10 A = 2.15; //amplitude in cm
11 t = 10; //time-base control setting in us
12 p = 0.2; //amplitude control setting
13
14 //calcculations
15 R = M/S; //mark to space ratio
16 T = (M+S)*t; //time for mark and space in
    divisions
17 f = 1/T; //pulse in frequency kHz
18 P = A*p; //magnitude of pule voltage
    in V
19
20 //Result
21 mprintf("mark-to-space ratio = %3.2f",R);
22 mprintf("\npulse frequency = %3.2f kHz",f);
23 mprintf("\nmagnitude of pulse voltage = %3.2f V",P);


---



```