

Scilab Textbook Companion for
Introduction To Mechatronics And
Measurement Systems
by David G. Alciatore And Michael B.
Hiland ¹

Created by
Sandeep Kumar C
B.tech
Electronics Engineering
Sreenidhi Institute Of Science And Technology
College Teacher
None
Cross-Checked by
None

June 10, 2019

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Introduction To Mechatronics And Measurement Systems

Author: David G. Alciatore And Michael B. Histanand

Publisher: Tata Mcgraw Hill

Edition: 4

Year: 2012

ISBN: 978-0-07-338023-0

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
2 Electric Circuits and Components	5
3 Semiconductor Electronics	16
6 Digital Circuits	22
8 Data Acquisition	29
9 Sensors	31

List of Scilab Codes

Exa 2.1	Resistance of a Wire	5
Exa 2.2	Resistance Color Codes	6
Exa 2.3	Kirchhoff Voltage Law	7
Exa 2.4	Circuit Analysis	8
Exa 2.5	Input and Output Impedance	10
Exa 2.6	AC Signal Parameters	11
Exa 2.7	AC Circuit Analysis	12
Exa 3.1design	Zener Diode Voltage Regulator Design	16
Exa 3.2	Zener Regulation Performance	17
Exa 3.2design	LED Switch	18
Exa 3.4	Guaranteeing That a Transistor Is in Saturation	20
Exa 6.1	Binary Arithmetic	22
Exa 6.2	Combinational Logic	23
Exa 6.3	Simplifying a Boolean Expression	25
Exa 6.4	Sum of Products and Product of Sums	26
Exa 8.2	Aperture Time	29
Exa 9.1	Strain Gage Resistance Changes	31
Exa 9.2	Thermocouple Configuration with Nonstandard Reference	32

Chapter 2

Electric Circuits and Components

Scilab code Exa 2.1 Resistance of a Wire

```
1 //Example 2.1, Page Number 16
2 //Resistance of a Wire
3 clc;
4
5 //Inputs
6 roh = 1.7*(10^-8) //Resistivity of copper wire
   in ohm-metre.
7 D=(10^-3) //Diameter of copper wire in metres.
8 rad=((D)/(2)) //Radius of copper wire in metres
9 L=10 //Length of copper wire in metres.
10
11 //Outputs
12 A=(3.14)*(rad^2) //Cross-sectional area of
   copper wire in metre-square
13 Rt=((roh*L)/(A)) //Total resistance of copper
   wire in ohm
14
15 //Results
```

```

16 mprintf("Cross-sectional area of copper wire: %.10f
    metre-square\n",A);
17 mprintf("Total wire resistance of copper wire is: %
    .5f ohm",Rt);
18
19 //Outputs
20 //Cross-sectional area of copper wire: 0.0000007850
    metre-square (or) (7.8)*(10^-7) metre-square
21 //Total wire resistance of copper wire is: 0.21656
    ohm

```

Scilab code Exa 2.2 Resistance Color Codes

```

1 //Example 2.2, Page Number 18
2 //Resistance Color Codes
3 clc;
4
5 //Inputs
6 //Colour bands:a = green, b = brown, c = red, and
    tol = gold
7 //a=5           Green colour code
8 //b=1           Brown colour code
9 c=2             //Red colour code
10 ab=51
11 tol=(0.05*((ab)*(10^c)))           //Tolerance band
    for given colour codes.
12
13 //Outputs
14 R_max=((ab)*(10^c))+tol           //Maximum resistance of
    given colour codes in ohms
15 R_min=((ab)*(10^c))-tol           //Minimum resistance of
    given colour codes in ohms
16
17 //Results
18 mprintf("Maximum resistance: %.5f ohms\n",R_max);

```

```

19 mprintf("Minimum resistance: %.5f ohms",R_min);
20
21 //Outputs
22 //Maximum resistance: 5355.00000 ohms
23 //Minimum resistance: 4845.00000 ohms
24
25 //Final answers in the solution of the book are
    rounded off.

```

Scilab code Exa 2.3 Kirchhoff Voltage Law

```

1 //Example 2.3, Page Number 23
2 // Kirchhoffs Voltage Law
3 clc;
4
5 //Inputs
6 Vin=10           //Input voltage in volts
7 Res=1000        //Resistance in ohms
8
9 //Outputs
10 //By Kirchhoff's Voltage Law
11 Vr=Vin          //Load Voltage across the load
    resistance in volts
12 //By ohms law
13 I=(Vr)/(Res)    //Load current flowing through
    load resistance in amperes
14
15 //Results
16 mprintf("Load current flowing through load
    resistance: %.5f ampere\n",I);
17
18 //Outputs
19 // Load current flowing through load resistance:
    0.01000 ampere (or) 10mA.

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 2.4 Circuit Analysis

```
1 //Example 2.4, Page Number 28
2 //Circuit Analysis
3 clc;
4
5 //Inputs
6 //Given resistances in circuit:
7 R1=1000 //Resistance in ohms
8 R2=2000 //Resistance in ohms
9 R3=3000 //Resistance in ohms
10 R4=4000 //Resistance in ohms
11 R5=5000 //Resistance in ohms
12 R6=6000 //Resistance in ohms
13 //Given voltage sources in circuit:
14 V1=10 //Voltage source in volts
15 V2=20 //Voltage source in volts
16
17 //Solving given resistances into an equivalent
    circuit:
18 //Outputs
19 //Resistors R2 and R4 are in series ,with an
    equivalent resistance of(R2+R4),and this is in
    parallel with resistor R3
20 R234=(((R2+R4)*(R3))/((R2+R4)+R3)) //Equivalent
    resistance of R2,R3,R4 in ohms
21 R56=((R5*R6)/(R5+R6)) //Equivalent resistance
    of R5,R6 in ohms
22 //Applying KVL in left loop:
23 Iout=(V1/R1) //Current through
    resistance R1 in amperes
```

```

24 //Voltage drop across resistance R234 determined
    from Voltage division rule in the assumed current
        direction of I234 through R234:
25 V234=((V1-V2)*((R234)/(R234+R56))) //Voltage
    across resistance R234 in volts
26 //The desired output voltage Vout calculated from V1
    and voltage drop V234 across R234 resistance is
    :
27 Vout=((V1)-(V234)) //Desired output
    voltage to be calculated in volts
28
29 //Results
30 mprintf("Equivalent resistance of R2,R3,R4: %.5f
    ohms\n",R234);
31 mprintf("Equivalent resistance of R5,R6 : %.5f ohms\
    n",R56);
32 mprintf("Current through resistance R1: %.5f ampere\
    n",Iout);
33 mprintf("Voltage across resistance R234: %.5f volts\
    n",V234);
34 mprintf("Desired output voltage to be calculated: %
    .5f volts\n",Vout);
35
36 //Outputs
37 //Equivalent resistance of R2,R3,R4: 2000.00000 ohms
38 //Equivalent resistance of R5,R6 : 2727.27273 ohms
39 //Current through resistance R1: 0.01000 ampere
40 //Voltage across resistance R234: -4.23077 volts
41 //Desired output voltage to be calculated: 14.23077
    volts

```

This code can be downloaded from the website www.scilab.in This code

can be downloaded from the website www.scilab.in

Scilab code Exa 2.5 Input and Output Impedance

```
1 //Example 2.5, Page Number 34
2 //Input and Output Impedance
3 clc;
4
5 //Inputs
6 //Given parameters of the circuit:
7 Vs=10 //Given source voltage in volts
8 R1=1000 //Resistance in ohms
9 R2=1000 //Resistance in ohms
10 Zin=1*(10^6) //Input impedance of
    voltmeter in ohms
11 Zout=50 //Output impedance of voltage
    source in ohms
12
13 //Outputs
14 Req=((R1*R2)/(R1+R2)) //Equivalent resistance
    due to resistance R1 and R2 in ohms
15 R_eq=(((Req*Zin)/(Req+Zin))+Zout) //
    Equivalent resistance due to resistance R1, input
    impedance of voltmeter Zin and output impedance
    of voltage source Zout in ohms
16 Vm=(((R_eq-Zout)/(R_eq))*(Vs)) //Actual
    voltage Vm measured by voltmeter in volts
17 //The measured voltage Vm equals Vs for Zin=infinity
    and Zout=0.
18
19 //Results
20 mprintf("Equivalent resistance due to resistance R1
    and R2: %.5f ohms\n",Req);
21 mprintf("Equivalent resistance due to resistance R1,
    input impedance of voltmeter Zin and output
    impedance of voltage source Zout: %.5f ohms\n",
```

```

    R_eq);
22 mprintf(" Actual voltage Vm measured by voltmeter: %
    .5f volts\n",Vm);
23
24 //Outputs
25 //Equivalent resistance due to resistance R1 and R2:
    500.00000 ohms
26 //Equivalent resistance due to resistance R1,input
    impedance of voltmeter Zin and output impedance
    of voltage source Zout: 549.75012 ohms
27 //Actual voltage Vm measured by voltmeter: 9.09050
    volts

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 2.6 AC Signal Parameters

```

1 //Example 2.6 , Page Number 38
2 //AC Signal Parameters
3 clc;
4
5 //Inputs
6 //V(t)=5.sin( t 1 )           Input Voltage in
    volts
7
8 //Outputs
9 Vm=5.0           //Signal amplitude in volts
10 w=1             //Signal radian frequency in radian per
    second
11 f=((w)/(2*3.14)) //Signal frequency in
    hertz
12 phi=-1          //Phase angle of the given input
    signal in radian
13 phi_deg=((180)/(3.14)*(phi)) //Phase angle in

```

```

        degrees
14
15 //Results
16 mprintf("Signal amplitude: %.5f volts\n",Vm);
17 mprintf("Signal radian frequency: %.5f rad/sec\n",w)
    ;
18 mprintf("Signal frequency: %.5f hertz\n",f);
19 mprintf("Phase angle of the given input signal: %.5f
    radians\n",phi);
20 mprintf("Phase angle: %.5f degrees\n",phi_deg);
21
22 //Outputs
23 //Signal amplitude: 5.00000 volts
24 //Signal radian frequency: 1.00000 rad/sec
25 //Signal frequency: 0.15924 hertz
26 //Phase angle of the given input signal: -1.00000
    radians
27 //Phase angle: -57.32484 degrees

```

Scilab code Exa 2.7 AC Circuit Analysis

```

1 //Example 2.7, Page Number 42
2 //AC Circuit Analysis
3 clc;
4
5 //Inputs
6 R1=1000 //Resistance in
    ohms
7 R2=3000 //Resistance in
    ohms
8 C=0.2*(10^-6) //Capacitance in
    farads
9 L=0.5 //Inductance in henry
10 //Vin=5*cos(3000*t+(pi/2)) Input Voltage in
    volts

```

```

11 //From the given input signal we can derive below
    parameters:
12 w=3000 //Input signal radian frequency
    in radian per second
13
14 //Outputs
15 Vin=(5*i) //Input signal in
    rectangular form with signal amplitude of 5V and
    phase of 90 degrees in volts
16 Zc=((-1)/(w*C))*i //Complex form of the
    capacitor impedance in ohms
17 Zl=((w*L))*i //Complex form of the
    capacitor impedance in ohms
18 R2_Zl=((R2)+(Zl)) //Complex form of
    combined impedance of R2 and Zl in ohms
19 R2_Zl_Zc=(((R2_Zl)*(Zc))/(R2_Zl+Zc)) //
    Complex form of combined impedance of parallel
    combination of R2_Zl and Zc in ohms
20 Zeq=((R2_Zl_Zc)+(R1)) //
    Complex form of equivalent impedance of the
    entire circuit in ohms
21 I1=(Vin/Zeq) //Current through
    R1 resistance in amperes
22 [mag0,phase0]=polar(I1) //Polar
    form of current I1 with magnitude in amperes and
    phase in radian
23
24 //Using current division rule:
25 I=(((R2+Zl)/((R2+Zl)+Zc))*(I1)) //Current
    through capacitor in amperes
26 [mag1,phase1]=polar(I) //Polar
    form of current I with magnitude in amperes and
    phase in radian
27
28 //so the capacitor current leads the input reference
    by 159.8 or 2.789 rad, and the resulting current
    is
29 //I(t)=2.22cos(3000t+2.789)mA

```

```

30
31 //Results
32 disp(Vin,"Input signal in rectangular form in volts:
    ");
33 disp(Zc,"Complex form of the capacitor impedance in
    ohms:");
34 disp(Zl,"Complex form of the inductance impedance in
    ohms:");
35 disp(R2_Zl,"Complex form of combined impedance of R2
    and Zl in ohms:");
36 disp(R2_Zl_Zc,"Complex form of combined impedance of
    parallel combination of R2_Zl and Zc in ohms:");
37 disp(Zeq,"Complex form of equivalent impedance of
    the entire circuit in amperes:");
38 disp(I1,"Current through R1 resistance in amperes:")
    ;
39 disp(I,"Current through capacitor in amperes:");
40 disp(mag0,"Polar form of current I1 with magnitude
    in amperes:");
41 disp(phase0,"Polar form of current I1 with phase in
    radian:");
42 disp(mag1,"Polar form of current I with magnitude in
    amperes:");
43 disp(phase1,"Polar form of current I with phase in
    radian:");
44 printf("Resulting current in amperes:0.0022224*cos
    (3000*t+ 2.7886023) amperes")
45
46 //Outputs
47 // Complex form of the inductance impedance in ohms
    :1500.i
48 //Complex form of combined impedance of R2 and Zl in
    ohms:3000. + 1500.i
49 //Complex form of combined impedance of parallel
    combination of R2_Zl and Zc in ohms:923.07692 -
    1615.3846i
50 //Complex form of equivalent impedance of the entire
    circuit in amperes:1923.0769 - 1615.3846i

```

```
51 //Current through R1 resistance in amperes
    :-0.0012805 + 0.0015244i
52 //Current through capacitor in amperes:-0.0020854 +
    0.0007683i
53 //Polar form of current I1 with magnitude in amperes
    :0.0019908
54 //Polar form of current I1 with phase in radian
    :2.2694562
55 //Polar form of current I with magnitude in amperes
    :0.0022224
56 //Polar form of current I with phase in radian
    :2.7886023
57 //Resulting current in amperes:0.0022224*cos(3000*t+
    2.7886023) amperes
58
59
60
61 //Phase angles of polar forms are in radian.
```

This code can be downloaded from the website www.scilab.in

Chapter 3

Semiconductor Electronics

Scilab code Exa 3.1design Zener Diode Voltage Regulator Design

```
1 //Design Example 3.1, Page Number 84
2 //Zener Diode Voltage Regulator Design
3 clc;
4
5 //Inputs
6 Rl_max=240 //Maximum load resistance in ohms
7 Pz_max=1 //Maximum power rating of the
   zener diode in watts
8 Vin=24 //Nominal input voltage in volts'
9 Vz=15 //Zener breakdown voltage in
   volts
10
11 //Outputs
12 R_min=((Vin-Vz)/(Pz_max+((Vz^2)/(Rl_max))))*(Vz)
   //Minimum required current-limiting
   resistance in ohms
13
14 //Results
15 mprintf("Minimum required current-limiting
   resistance: %.5f ohms\n",R_min);
16 //The closest acceptable standard resistance value
```

```

        is 75 ohms
17
18 //Outputs
19 //Minimum required current-limiting resistance:
        69.67742 ohms

```

Scilab code Exa 3.2 Zener Regulation Performance

```

1 //Example 3.2, Page Number 83
2 //Zener Regulation Performance
3 clc;
4
5 //Inputs
6 Vin_min=20           //Minimum input voltage in volts
7 Vin_max=30           //Maximum input voltage in
    volts
8 Vz=15                //Zener breakdown voltage in
    volts
9 P_dissp=1            //Maximum power rating of
    zener diode in watts
10 Rd=14                //Zener dynamic resistance in
    ohms
11 Delta_Vin=(Vin_max-Vin_min) //Input
    voltage range in volts
12
13 //Outputs
14 //To limit the maximum power dissipation to less
    than 1W, the current through the diode must be
    limited to:
15 Iz_max=((P_dissp)/(Vz)) //Maximum zener
    current through zener diode in amperes
16 R_min=((Vin_max-Vz)/(Iz_max)) //Minimum load
    resistance for keeping the zener diode in
    breakdown region in ohms
17 //The closest acceptable standard resistance value

```

```

    is 240
18 R_min_practical=240 //Minimum
    load resistance for keeping the zener diode in
    breakdown region in ohms
19 Delta_Vout=((Rd)/(Rd+R_min_practical))*(Delta_Vin))
    //Output voltage range in volts
20 //When zener diode is in breakdown region Vout=Vz.
21 Volt_reg=((Delta_Vout)/(Vz))*100 //Voltage
    regulation percentage
22
23 //Results
24 mprintf("Maximum zener current through zener diode:
    %.5f ampere\n", Iz_max);
25 mprintf("Minimum load resistance for keeping the
    zener diode in breakdown region: %.5f ohms\n",
    R_min);
26 mprintf("Output voltage range: %.5f volts\n",
    Delta_Vout);
27 mprintf("Voltage regulation percentage: %.5f \n",
    Volt_reg);
28
29 //Outputs
30 //Maximum zener current through zener diode: 0.06667
    ampere
31 //Minimum load resistance for keeping the zener
    diode in breakdown region: 225.00000 ohms
32 //Output voltage range: 0.55118 volts
33 ////Voltage regulation percentage: 3.6745

```

Scilab code Exa 3.2design LED Switch

```

1 //Design Example 3.2, Page Number 98
2 //LED Switch
3 clc;
4

```

```

5 //Inputs
6 Vout_min=0 //Output minimum voltage in
  volts
7 Vout_max=5 //Output maximum voltage in
  volts
8 Vcc=5 //DC supply voltage in volts
9 Iout_max=5*(10^-3) //Maximum output current
  in amperes
10 Vbe=0.7 //Base-Emitter voltage in
  volts
11 Vce=0.2 //Collector-Emitter
  voltage in volts
12 Rc=100 //Collector resistance in ohms
13 Rb=10*(10^3) //Base resistance in ohms
14 //The LED requires 20 40 mA to provide a bright
  display.
15 Vf_drop=2 //Forward bias voltage drop of
  LED in volts
16
17 //Outputs
18 //When the digital output is 0V,the transistor is in
  cutoff:
19 Ib_cutoff=(Vcc-Vbe)/Rb //Base
  current when transistor is in cutoff in amperes
20 //When the digital output is 5V,the transistor is in
  saturation:
21 Ic_sat=(Vcc-Vf_drop-Vce)/Rc //
  Collector current when transistor is in
  saturation in amperes
22 //The 100 ohm collector resistance limits the LED
  current to a value within the desired range for
  the LED to be bright (20 40 ) mA
23
24 //Results
25 mprintf("Base current when transistor is in cutoff:
  %.5f amperes\n",Ib_cutoff);
26 mprintf("Collector current when transistor is in
  saturation: %.5f amperes\n",Ic_sat);

```

```

27
28 //Outputs
29 //Base current when transistor is in cutoff: 0.00043
    amperes
30 //Collector current when transistor is in saturation
    : 0.02800 amperes

```

Scilab code Exa 3.4 Guaranteeing That a Transistor Is in Saturation

```

1 //Example 3.4, Page Number 94
2 //Guaranteeing That a Transistor Is in Saturation
3 clc;
4
5 //Inputs
6 Ic_max=200*(10^-3)           //Maximum collector
    current in amperes
7 Vce_sat=0.2                 //Collector-Emitter
    saturation current in volts
8 Beta=100                   //Common emitter DC current gain
9 Vcc=10                      //DC supply voltage in volts
10 Vbe=0.7                    //Base-Emitter saturation
    current in volts
11 Rb=10*(10^3)               //Base resistor in ohms
12 Rc=(10^3)                  //Collector resistor in ohms
13
14 //Outputs
15 Ic=(Vcc-Ic_max)/Rc         //Collector current
    in amperes
16 //Because the DC current gain hFE(Beta) is about
    100,Ib must be at least Ic/100 or 0.098mA. Because
    Vbe=0.7 V
17 Ib=(Ic/100)                //Base current in
    amperes
18 //Base current can be related to the input voltage
    as:

```

```
19 Vin_min=(Ib*Rb)+Vbe //Minimum input
    voltage required for saturation in volts
20
21 //Results
22 mprintf("Minimum input voltage required for
    saturation: %.5f volts\n",Vin_min);
23
24
25 //Outputs
26 // Minimum input voltage required for saturation:
    1.68000 volts
27
28
29
30 //Normally you would use a voltage larger than this
    (e.g., 2 to 5 times larger) to ensure that the
    transistor is fully saturated, even with
    variances in parameters.
```

This code can be downloaded from the website www.scilab.in

Chapter 6

Digital Circuits

Scilab code Exa 6.1 Binary Arithmetic

```
1 //Example 6.1, Page Number 200
2 //Binary Arithmetic
3 clc;
4
5 //Inputs
6 //Binary to decimal conversion
7 a=bin2dec('1001') //Binary input for addition
8 b=bin2dec('0011') //Binary input for addition
9 u=bin2dec('1001') //Binary input for
    multiplication
10 v=bin2dec('0011') //Binary input for
    multiplication
11
12 //Outputs
13 c=a+b //Addition of given numbers
14 d=dec2bin(c) //Decimal to binary
    conversion
15 w=u*v //Multiplication of given
    numbers
16 x=dec2bin(w) //Decimal to binary
    conversion
```

```

17
18 //Results
19 disp('Addition of the given binary numbers: ')
20 disp(d)
21 disp('Multiplication of the given binary numbers: ')
22 disp(x)
23
24 //Outputs
25 //Addition of the given binary numbers: 1100
26
27 //Multiplication of the given binary numbers: 11011

```

Scilab code Exa 6.2 Combinational Logic

```

1 //Example 6.2, Page Number 204
2 //Combinational Logic
3 clc;
4
5 //Inputs
6 //Binary to decimal conversion
7 A=[0;0;0;0;1;1;1;1] //Binary input A
8 B=[0;0;1;1;0;0;1;1] //Binary input B
9 C=[0;1;0;1;0;1;0;1] //Binary input C
10
11 //Outputs
12 Z=bitcmp(C,1) //Bit
    compliment of input C
13 D=bitand(A,B) //AND
    operation of inputs A,B
14 E=bitor(D,Z) //OR
    operation of D and Z(Compliment of C)
15 F=bitcmp((bitand(E,Z)),1) //NAND
    operation of E and Z(Compliment of C)
16
17 //Results

```



```

18 disp('Input A')
19 disp("  A")
20 disp(A)
21 disp('Input B')
22 disp("  B")
23 disp(B)
24 disp('Input C')
25 disp("  C")
26 disp(C)
27 disp('AND operation of inputs A,B:')
28 disp("  D")
29 disp(D)
30 disp('OR operation of D and Z(Compliment of C):')
31 disp("  E")
32 disp(E)
33 disp('NAND operation of E and Z(Compliment of C):')
34 disp("  F")
35 disp(F)
36
37 //Outputs
38
39 //Input A      Input B      Input C      AND operation
      of inputs A,B:      OR operation of D and Z(
      Compliment of C):      NAND operation of E and
      Z(Compliment of C):
40
41 // A          B          C          E          D
      F
42 // 0.          0          0          1          0
      0
43 // 0.          0          1          0          0
      1

```

```

44 // 0.          1          0          1          0
45 // 0.          1          1          0          0
46 // 1.          0          0          1          0
47 // 1.          0          1          0          0
48 // 1.          1          0          1          1
49 // 1.          1          1          1          1

```

1

This code can be downloaded from the website www.scilab.in

Scilab code Exa 6.3 Simplifying a Boolean Expression

```

1 //Example 6.3, Page Number 207
2 //Simplifying a Boolean Expression
3 clc;
4
5 //Inputs

```

```

6 //Given boolean expression :
7 //X=(A.B.C)+(B.C)+(A'.B)
8
9 //Outputs
10 //Results
11 disp("Given boolean expression:")
12 disp('X=(A.B.C)+(B.C)+(A''B)')
13 disp("The above equation can be rewritten using the
        associative law and the fundamental law as Z.1=Z"
        )
14 disp('X=A.(B.C)+1.(B.C)+(A''B)')
15 disp("Using distributive law")
16 disp('X=(A+1).(B.C)+(A''B)')
17 disp('X=(B.C)+(A''B)')
18 disp("Because A+1=1 and 1.(B.C)=B C")
19 disp("Furthermore, using the associative and
        distributive laws")
20 disp('X=B.(C+A''')')
21
22 //Outputs
23 // Given boolean expression :
24 //X=(A.B.C)+(B.C)+(A'B)
25 //The above equation can be rewritten using the
        associative law and the fundamental law as Z.1=Z
26 //X=A.(B.C)+1.(B.C)+(A'B)
27 //Using distributive law
28 //X=(A+1).(B.C)+(A'B)
29 //X=(B.C)+(A'B)
30 //Because A+1=1 and 1.(B.C)=B C
31 //Furthermore, using the associative and
        distributive laws
32 //X=B.(C+A')

```

Scilab code Exa 6.4 Sum of Products and Product of Sums

```

1 //Example 6.4, Page Number 212
2 //Sum of Products and Product of Sums
3 clc;
4
5 //Inputs
6 //Given inputs
7 A=[0;0;1;1] //Input A
8 B=[0;1;0;1] //Input B
9
10 //Outputs
11 S=bitxor(A,B) //Sum of A and B
12 C=bitand(A,B) //Carry of A
    and B
13
14 //Results
15 disp("Input A")
16 disp(A)
17 disp("Input B")
18 disp(B)
19 disp("Sum of A and B:")
20 disp(S)
21 disp("Carry of A and B")
22 disp(C)
23 disp('The sum-of-products method applied to output S
    yields:')
24 disp('S=(A''+B)+(A+B''')')
25 disp('The product-of-sums method applied to output S
    yields:')
26 disp('S=(A+B).(A''+B''')')
27 disp('The sum-of-products method applied to output C
    yields:')
28 disp('C=A.B')
29 disp('The product-of-sums method applied to output C
    yields:')
30 disp('C=(A+B).(A+'B).(A''+B''')')
31
32 //Outputs
33

```

	Input A	Input B	Sum of
	A and B:	Carry of A and B	
34	// 0	0	0
35	// 0	0	
36	// 0	1	1
		0	
37	// 1.	0	1
		0	
38	// 1.	1	0
		1	
39			
40	//The sum-of-products method applied to output S		
	yields:		
41	//S=(A'+B)+(A+B')		
42	//The product-of-sums method applied to output S		
	yields:		
43	//S=(A+B).(A'+B')		
44	//The sum-of-products method applied to output C		
	yields:		
45	//C=A.B		
46	//The product-of-sums method applied to output C		
	yields:		
47	//C=(A+B).(A+'B).(A'+B')		
48			
49			
50	//If we use the product-of-sums result for S and the		
	sum-of-products result for C,we obtain a circuit		
	using the fewest number of gates		

Chapter 8

Data Acquisition

Scilab code Exa 8.2 Aperture Time

```
1 //Example 8.2, Page Number 355
2 //Aperture Time
3 clc;
4
5 //Inputs
6 n=10 //No of bit resolution
7 BW=10*(10^3) //Bandwidth of signal in
   hertz
8
9 //Outputs
10 N=(2^n) //Number of output states
11 delta_Ta=(2/(N*2*3.14*BW)) //Aperture
   time in seconds
12 Ts=((1/(2*BW))) //Minimum
   sampling rate in seconds
13
14 //Results
15 mprintf("Number of output states: %.5f\n",N);
16 mprintf("Aperture time: %.13f seconds\n",delta_Ta);
17 mprintf("Minimum sampling rate: %.6f seconds\n",Ts);
18
```

```
19 //Outputs
20 //Number of output states: 1024.00000
21 //Aperture time: 0.0000000311007 seconds (or) 31.100
    nanoseconds
22 //Minimum sampling rate: 0.000050 seconds (or) 50
    microseconds
23
24
25 //Even for this low-resolution converter, the
    required aperture time (32 nsec) is much smaller
    than the required sample period (50,000 nsec).
```

Chapter 9

Sensors

Scilab code Exa 9.1 Strain Gage Resistance Changes

```
1 //Example 9.1, Page Number 395
2 //Strain Gage Resistance Changes
3 clc;
4
5 //Inputs
6 R=120 //Strain gage in ohms
7 F=2 //Gage factor
8 strain=100*(10^-6) //Strain experienced by
   gage
9
10 //Outputs
11 R_change=R*F*strain //Resistance of the
   gage change from the unloaded state to the loaded
   state in ohms
12
13 //Results
14 mprintf("Resistance of the gage change from the
   unloaded state to the loaded state: %.5f ohms\n",
   R_change);
15
16
```



```

17 //Outputs
18 //Resistance of the gage change from the unloaded
    state to the loaded state: 0.02400 ohms

```

Scilab code Exa 9.2 Thermocouple Configuration with Nonstandard Reference

```

1 //Example 9.2,Page Number 413
2 //Thermocouple Configuration with Nonstandard
    Reference
3 clc;
4
5 //Inputs
6 //A standard two-junction thermocouple configuration
    is being used to measure the temperature in a
    wind tunnel.
7 //The reference junction is held at a constant
    temperature of 10 Celsius.
8 //We have only a thermocouple table referenced to 0
    Celsius .
9 Junc_Temp=[0;10;20;30;40;50;60;70;80;90;100]
    //Junction temperature in celsius
10 V_out
    =[0;0.507;1.019;1.536;2.058;2.585;3.115;3.649;4.186;4.725;5.268]
    //Output voltages in millivolts
11 V_100_to_0=5.268*(10^-3) //Voltage
    measured for a temperature of 100 Celsius
    relative to a reference junction at 0 Celsius in
    volts
12 V_10_to_10=0.507*(10^-3) //Voltage
    measured for a temperature of 10 Celsius
    relative to a reference junction at 10 Celsius in
    volts
13
14 //Outputs
15 //By law of intermediate temperature:

```

```

16 V_100_to_10= (V_100_to_0)-(V_10_to_10)           //
    Voltage measured for a temperature of 100 Celsius
    relative to a reference junction at 10 Celsius
    in volts
17
18 //Results
19 disp('Junction temperature in celsius list')
20 disp(Junc_Temp)
21 disp('Output voltages in millivolts list')
22 disp(V_out)
23
24 mprintf("Voltage measured for a temperature of 100
    Celsius relative to a reference junction at 10
    Celsius: %.5f volts\n",V_100_to_10);
25
26
27 //Outputs
28 //Junction temperature in celsius list
    Output voltages in millivolts list
29
30 //    0
    0
31 //    10
    0.507
32 //    20
    1.019
33 //    30
    1.536
34 //    40
    2.058
35 //    50
    2.585

```

36 // 60

3.115

37 // 70

3.649

38 // 80

4.186

39 // 90

4.725

40 // 100

5.268

41 // Voltage measured for a temperature of 100 Celsius
relative to a reference junction at 10 Celsius:
0.00476 volts (or) 4.76 millivolts
