Scilab Manual for
Power Electronics Lab
by Prof C Harinatha Reddy
Electrical Engineering
G Pulla Reddy Engineering College [1]

Solutions provided by
Prof C Harinatha Reddy
Electrical Engineering
G Pulla Reddy ENgineering College (Autonomous)

November 26, 2026

[1]Funded by a grant from the National Mission on Education through ICT, http://spoken-tutorial.org/NMEICT-Intro. This Scilab Manual and Scilab codes written in it can be downloaded from the "Migrated Labs" section at the website http://scilab.in

Contents

List of Scilab Solutions 3

1 Uncontrolled 1-phase Half and Full wave rectifier with R load 5

2 Uncontrolled 3-phase Half wave and Full wave rectifier 6

3 Controlled 1-phase Half and Full wave rectifier with R Load 9

4 Controlled 3-phase Half and Full wave rectifier with R Load 12

5 Step Down and Step up chopper with R load 17

6 1-phase AC- voltage controller with R load 20

7 1-phase Inverter (Half Bridge and H bridge) with R load 22

List of Experiments

List of Figures

2.1 Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load 7
2.2 Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load 7
2.3 Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load 8
2.4 Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load 8

3.1 Circuit Diagram of 1phase Half Wave controlled Rectifier with R load 10
3.2 Circuit Diagram of 1phase Full Wave uncontrolled Rectifier with R load 11

4.1 Circuit Diagram of 3phase Half controlled Rectifier with R load 13
4.2 Circuit Diagram of 3phase Half controlled Rectifier with R load 14
4.3 Circuit Diagram of 3phase Full Wave controlled Rectifier with R load 15
4.4 Circuit Diagram of 3phase Full Wave controlled Rectifier with R load 16

5.1 Circuit Diagram of StepDownchopper with R load 18
5.2 Circuit Diagram of Step Up chopper with R load 19

6.1 Circuit Diagram of 1phase AC Vokltage controller with R load 21

7.1 Circuit Diagram of Half bridge Inverter with R load 23
7.2 Circuit Diagram of Half bridge Inverter with R load 24
7.3 Circuit Diagram of Full bridge Inverter with R load 25
7.4 Circuit Diagram of Full bridge Inverter with R load 26

Experiment: 1

Uncontrolled 1-phase Half and Full wave rectifier with R load

This code can be downloaded from the website wwww.scilab.in This code

can be downloaded from the website wwww.scilab.in

Experiment: 2

Uncontrolled 3-phase Half wave and Full wave rectifier

This code can be downloaded from the website wwww.scilab.in

This code can be downloaded from the website wwww.scilab.in

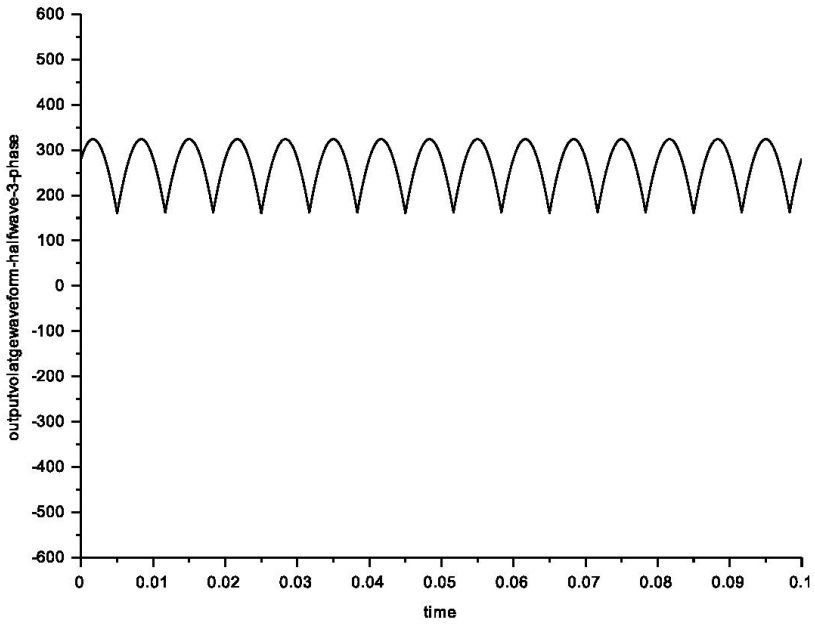


Figure 2.1: Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load

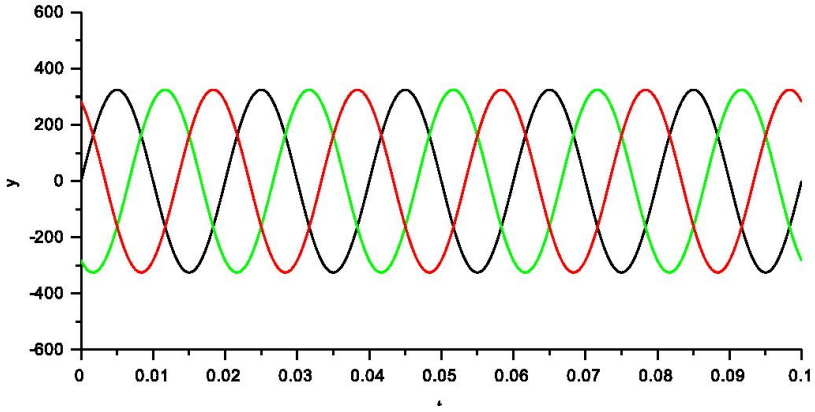


Figure 2.2: Circuit Diagram of 3phase Half Wave uncontrolled Rectifier with R load

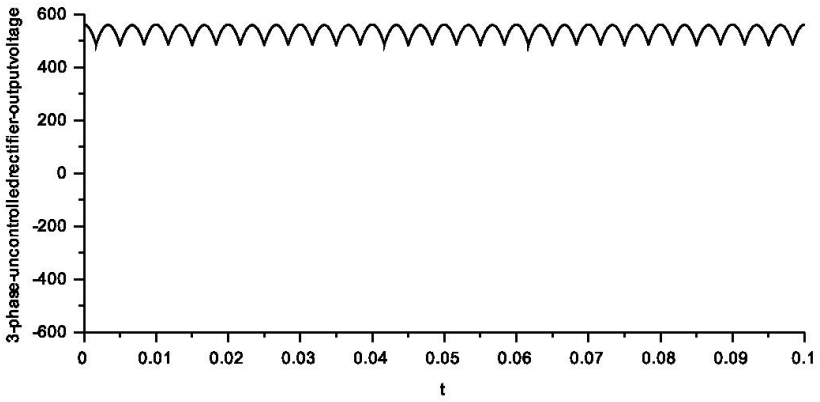


Figure 2.3: Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load

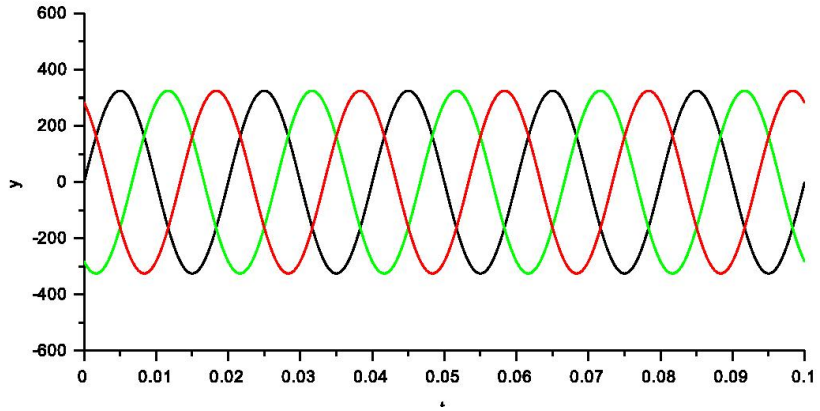


Figure 2.4: Circuit Diagram of 3phase Full Wave uncontrolled Rectifier with R load

Experiment: 3

Controlled 1-phase Half and Full wave rectifier with R Load

This code can be downloaded from the website wwww.scilab.in This code

can be downloaded from the website wwww.scilab.in

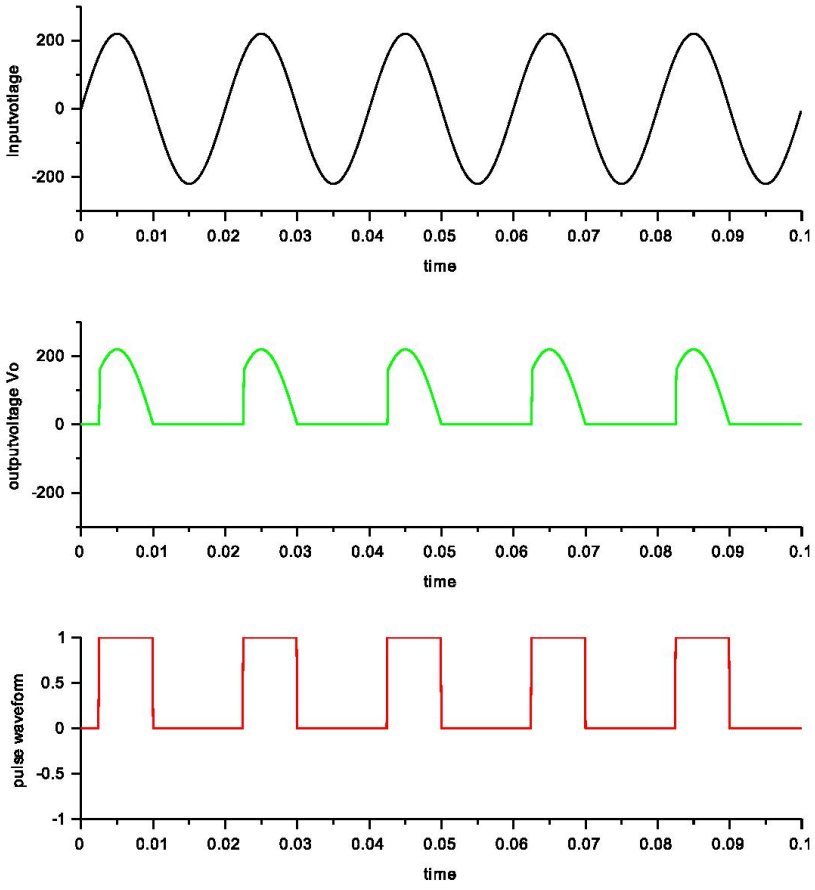


Figure 3.1: Circuit Diagram of 1phase Half Wave controlled Rectifier with R load

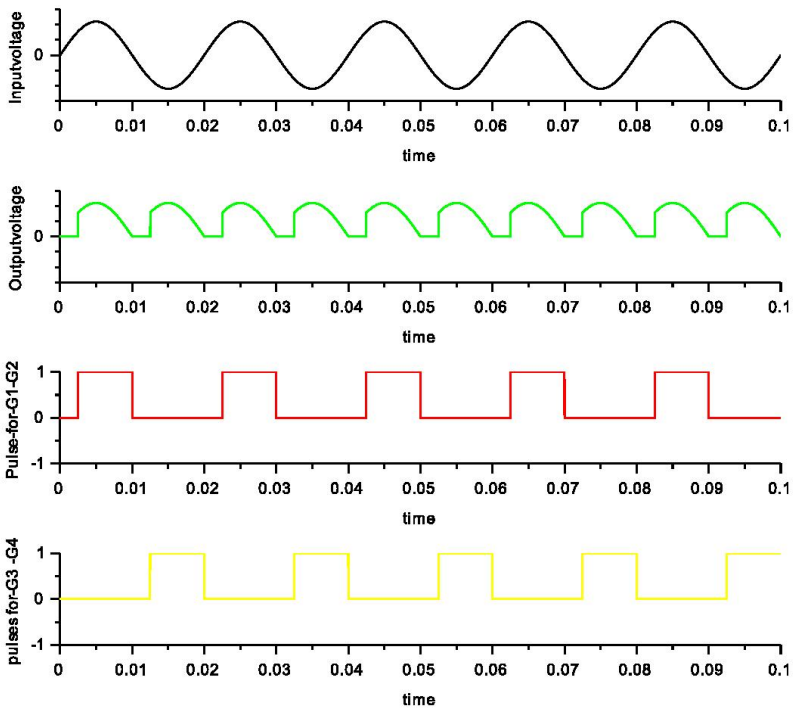


Figure 3.2: Circuit Diagram of 1phase Full Wave uncontrolled Rectifier with R load

Experiment: 4

Controlled 3-phase Half and Full wave rectifier with R Load

This code can be downloaded from the website wwww.scilab.in

This code can be downloaded from the website wwww.scilab.in

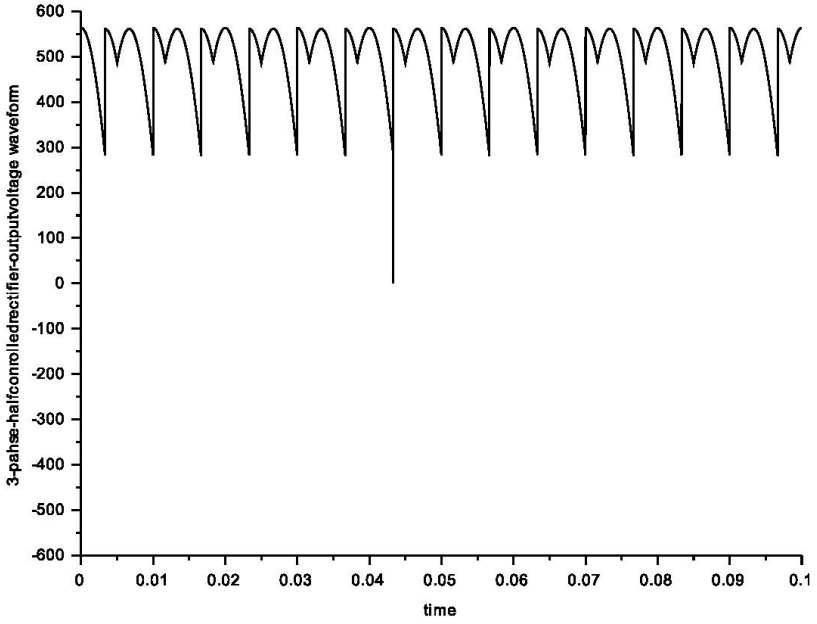


Figure 4.1: Circuit Diagram of 3phase Half controlled Rectifier with R load

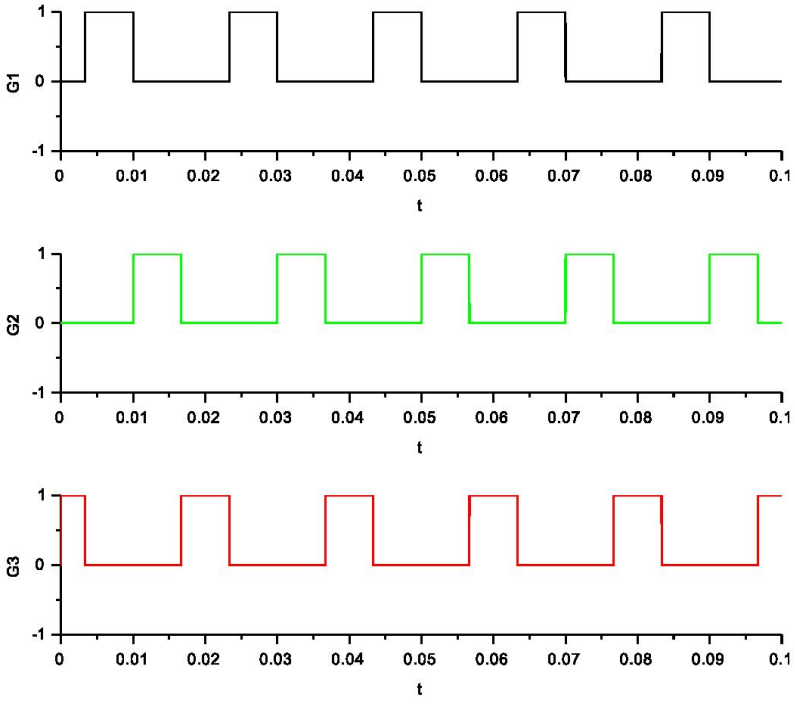


Figure 4.2: Circuit Diagram of 3phase Half controlled Rectifier with R load

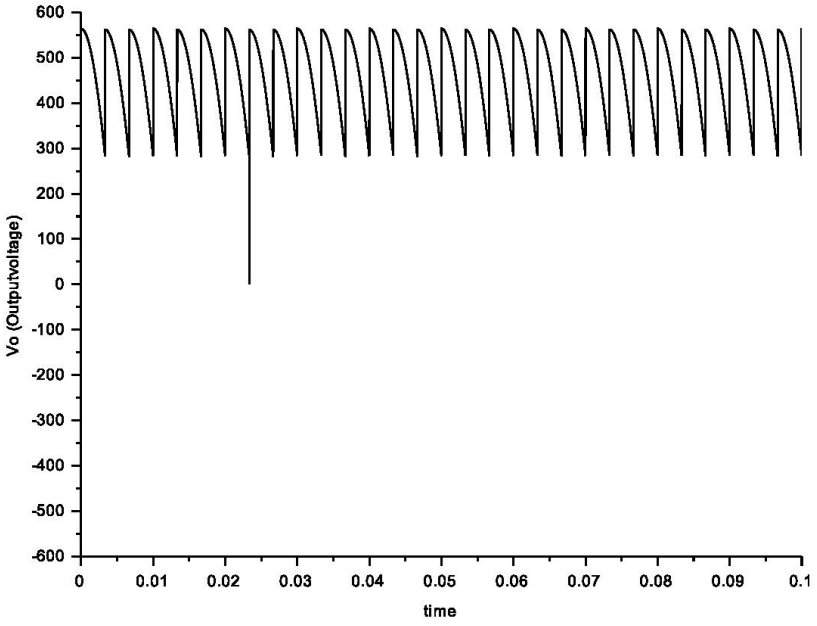


Figure 4.3: Circuit Diagram of 3phase Full Wave controlled Rectifier with R load

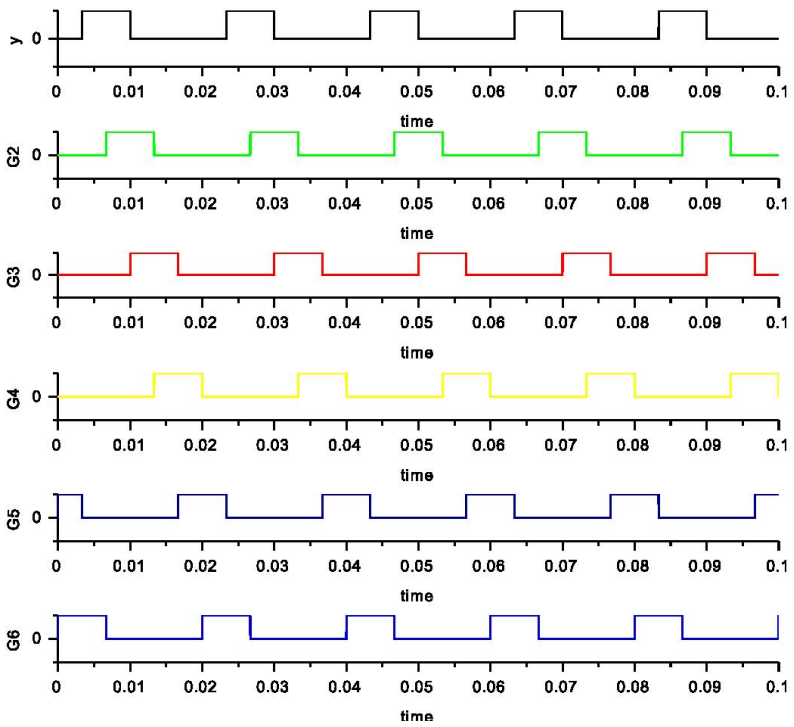


Figure 4.4: Circuit Diagram of 3phase Full Wave controlled Rectifier with R load

Experiment: 5

Step Down and Step up chopper with R load

This code can be downloaded from the website wwww.scilab.in

This code can be downloaded from the website wwww.scilab.in

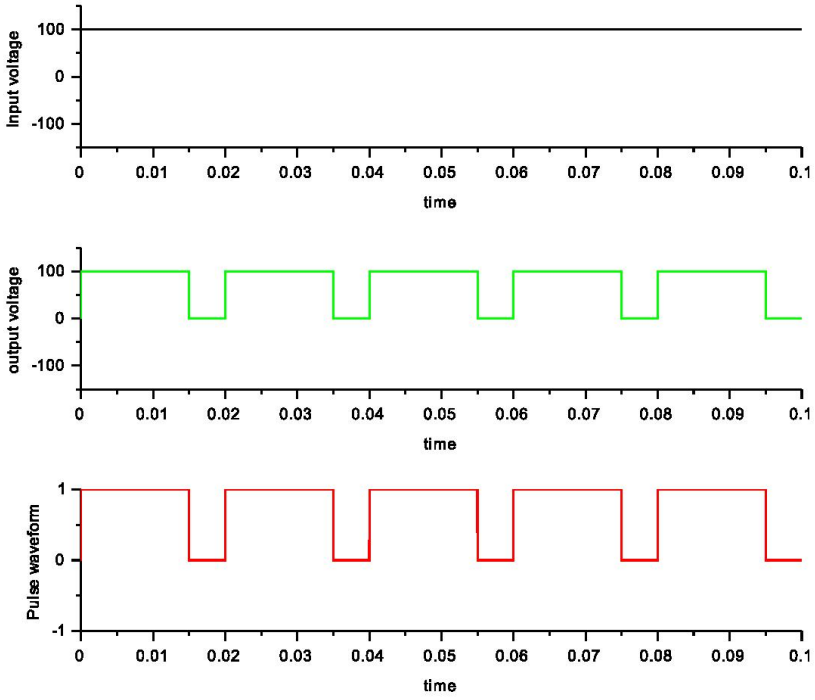


Figure 5.1: Circuit Diagram of StepDownchopper with R load

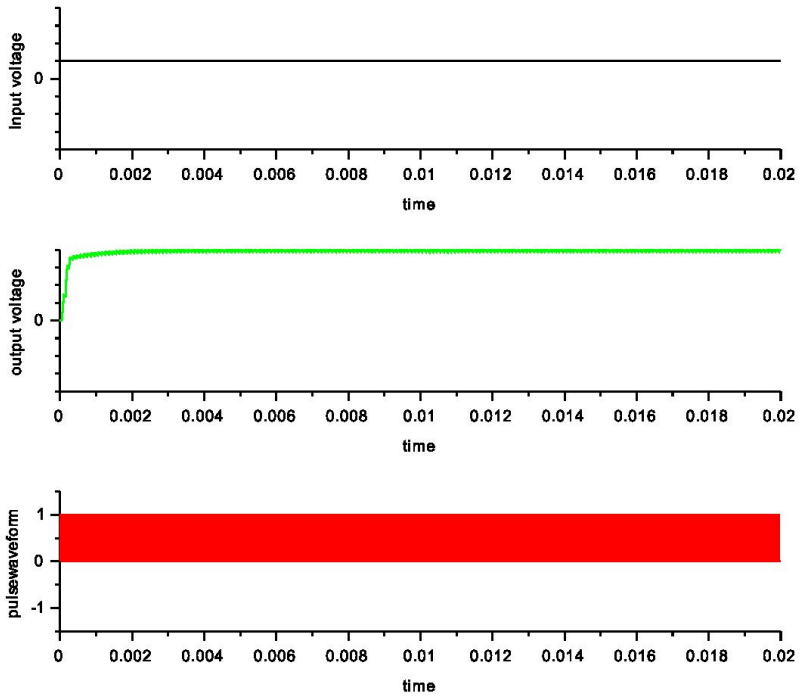


Figure 5.2: Circuit Diagram of Step Up chopper with R load

Experiment: 6

1-phase AC- voltage controller with R load

This code can be downloaded from the website wwww.scilab.in

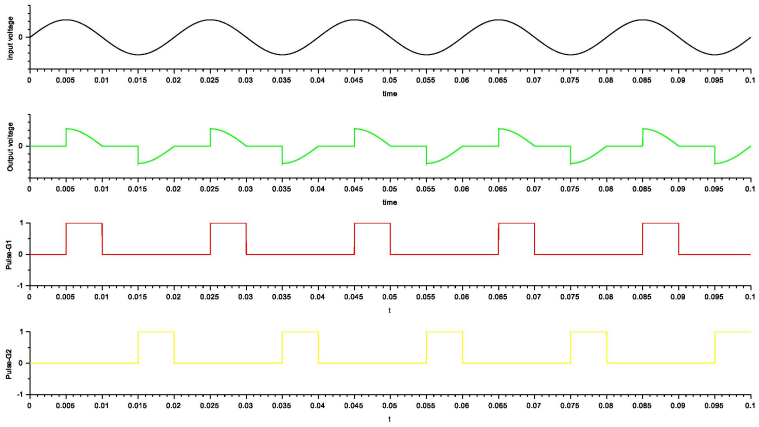


Figure 6.1: Circuit Diagram of 1phase AC Vokltage controller with R load

Experiment: 7

1-phase Inverter (Half Bridge and H bridge) with R load

This code can be downloaded from the website wwww.scilab.in This code

can be downloaded from the website wwww.scilab.in

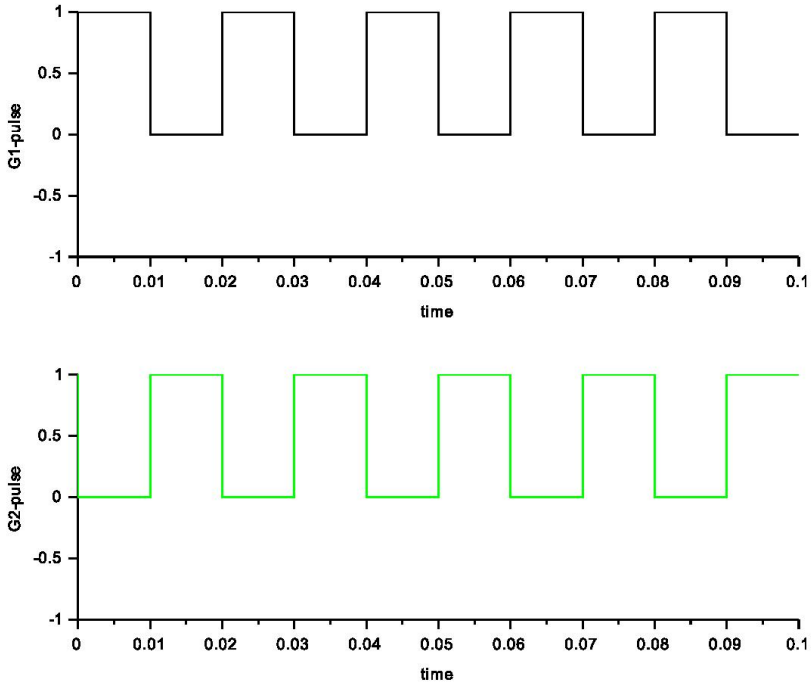


Figure 7.1: Circuit Diagram of Half bridge Inverter with R load

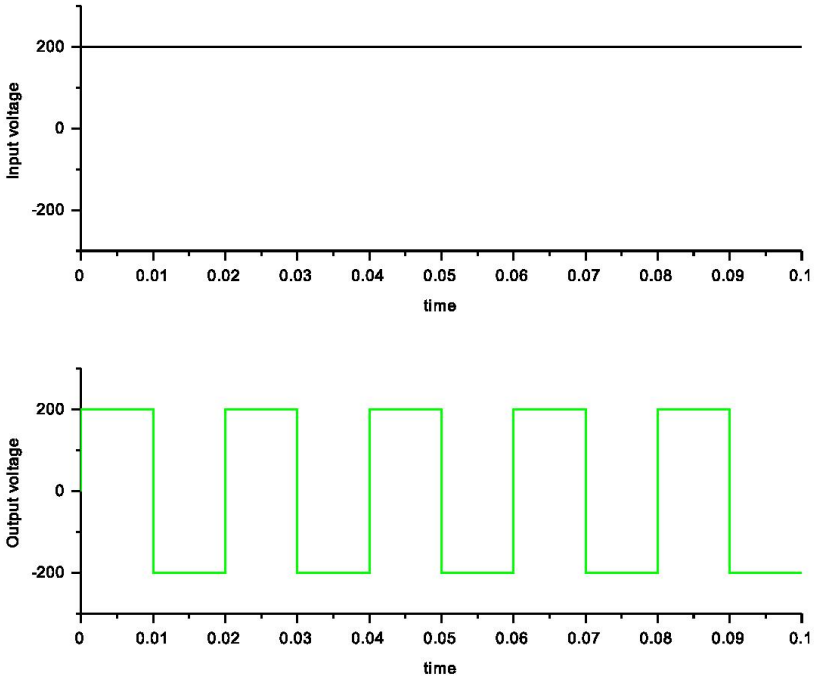


Figure 7.2: Circuit Diagram of Half bridge Inverter with R load

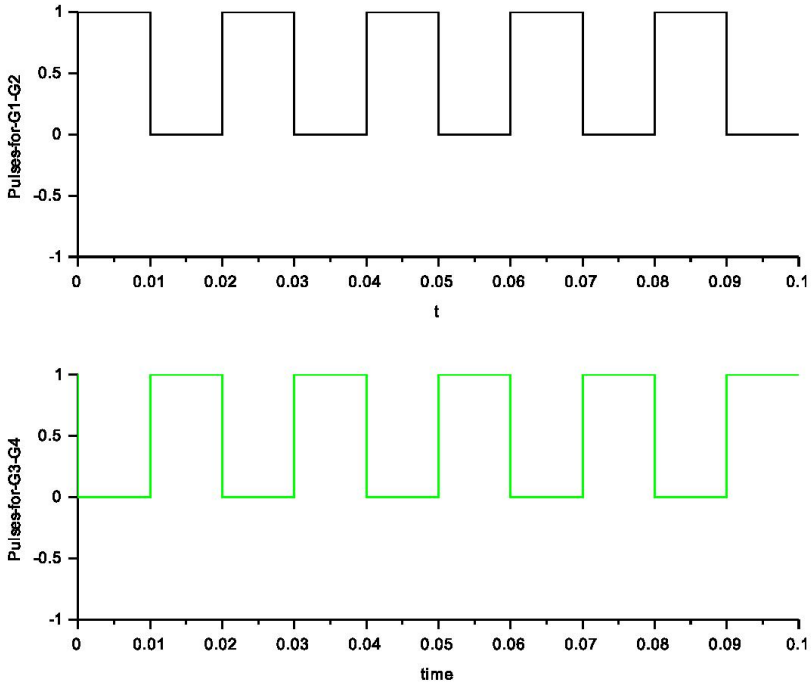


Figure 7.3: Circuit Diagram of Full bridge Inverter with R load

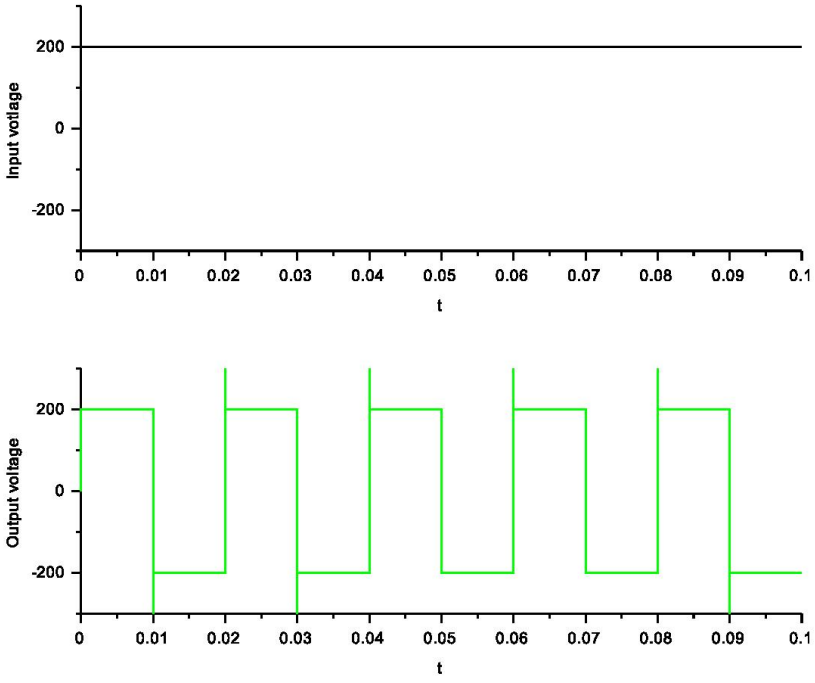


Figure 7.4: Circuit Diagram of Full bridge Inverter with R load